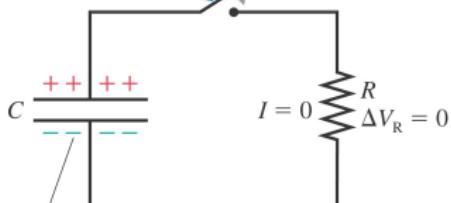


# RC Circuits (32.9)


(a) Before the switch closes

The switch will close at  $t = 0$ .



Charge  $Q_0$   
 $\Delta V_C = Q_0/C$

(b) After the switch closes

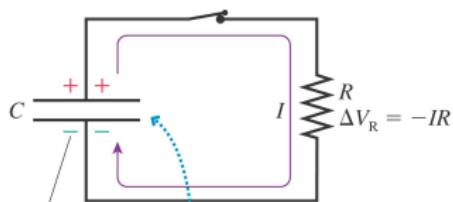

Charge  $Q$   
 $\Delta V_C = Q/C$

The current is reducing the charge on the capacitor.

- We have only been discussing DC circuits so far. However, using a capacitor we can create an **RC circuit**.
- In this example, a capacitor is charged but the switch is open, meaning no current flows.
- The switch closes and current flows through the resistor, discharging the capacitor. The current stops once the capacitor is discharged.
- The voltage around the loop is

$$\Delta V_C + \Delta V_R = \frac{Q}{C} - IR = 0$$

# RC Circuits

- The rate of charge leaving the capacitor is equal to the rate of charge passing through the circuit (the current)

$$I = -\frac{dQ}{dt}$$

- The loop then becomes (dividing by R and rearranging)

$$\frac{Q}{C} - IR = 0$$

$$\frac{Q}{C} + \frac{dQ}{dt}R = 0$$

$$\frac{Q}{RC} + \frac{dQ}{dt} = 0$$

$$\frac{dQ}{Q} = -\frac{1}{RC}dt$$

- We can solve this by integrating it.

# RC Circuits

- The integral is

$$\int_{Q_0}^Q \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$

- We can do that integral

$$\ln Q|_{Q_0}^Q = \ln Q - \ln Q_0 = \ln \left( \frac{Q}{Q_0} \right) = -\frac{t}{RC}$$

- Solving for  $Q$  gives



$$Q = Q_0 e^{-t/RC} = Q_0 e^{-t/\tau}$$

where  $\tau = RC$  is the **time constant** of the circuit.

- The resistor current is then

$$I = -\frac{dQ}{dt} = \frac{Q_0}{\tau} e^{-t/\tau} = \frac{Q_0}{RC} e^{-t/\tau} = \frac{\Delta V_C}{R} e^{-t/\tau} = I_0 e^{-t/\tau}$$


# RC Circuits

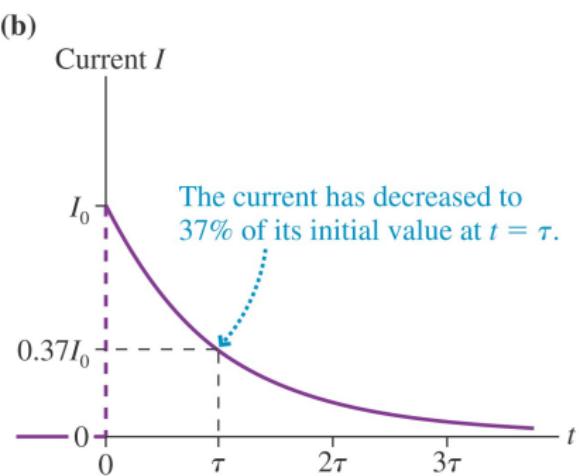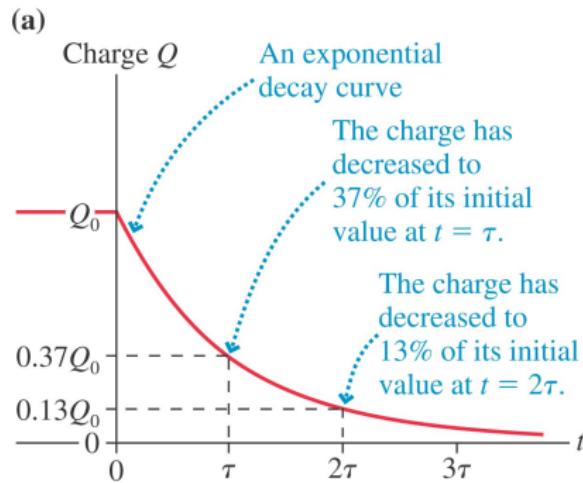

# Charging a Capacitor


(a)

Switch closes at  $t = 0$  s.

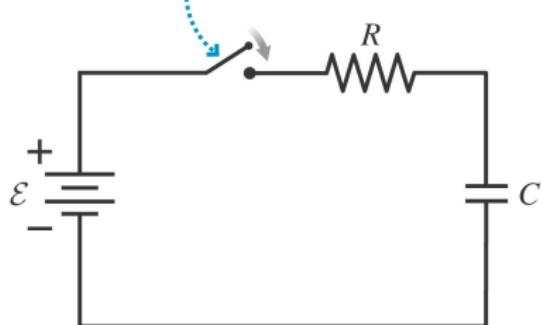

Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley

(b)

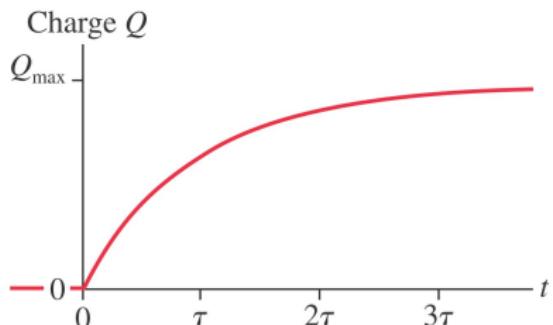

Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley