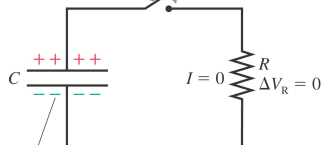


RC Circuits (32.9)


(a) Before the switch closes

The switch will close at $t = 0$.



Charge Q_0
 $\Delta V_C = Q_0/C$

(b) After the switch closes

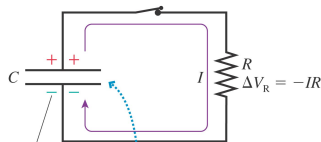

Charge Q
 $\Delta V_C = Q/C$


The current is reducing the charge on the capacitor.

- We have only been discussing DC circuits so far. However, using a capacitor we can create an **RC circuit**.
- In this example, a capacitor is charged but the switch is open, meaning no current flows.

RC Circuits (32.9)


(a) Before the switch closes

The switch will close at $t = 0$.

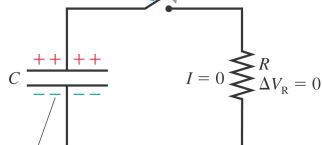

Charge Q_0
 $\Delta V_C = Q_0/C$

(b) After the switch closes

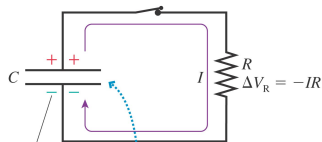

Charge Q
 $\Delta V_C = Q/C$


The current is reducing the charge on the capacitor.

- We have only been discussing DC circuits so far. However, using a capacitor we can create an **RC circuit**.


RC Circuits (32.9)

(a) Before the switch closes

The switch will close at $t = 0$.

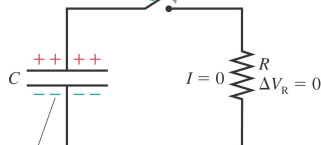

(b) After the switch closes

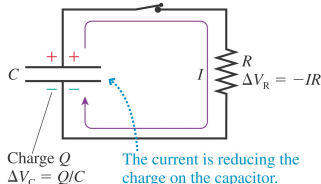


- We have only been discussing DC circuits so far. However, using a capacitor we can create an **RC circuit**.
- In this example, a capacitor is charged but the switch is open, meaning no current flows.
- The switch closes and current flows through the resistor, discharging the capacitor. The current stops once the capacitor is discharged.

RC Circuits (32.9)


(a) Before the switch closes

The switch will close at $t = 0$.

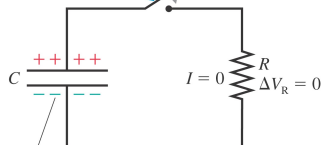

Charge Q_0
 $\Delta V_C = Q_0/C$

(b) After the switch closes

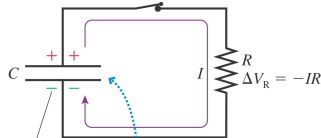

Charge Q
 $\Delta V_C = Q/C$

The current is reducing the charge on the capacitor.

- We have only been discussing DC circuits so far. However, using a capacitor we can create an **RC circuit**.
- In this example, a capacitor is charged but the switch is open, meaning no current flows.
- The switch closes and current flows through the resistor, discharging the capacitor. The current stops once the capacitor is discharged.
- The voltage around the loop is

$$\Delta V_C + \Delta V_R = \frac{Q}{C} - IR = 0$$

RC Circuits

- The rate of charge leaving the capacitor is equal to the rate of charge passing through the circuit (the current)

$$I = -\frac{dQ}{dt}$$

RC Circuits

- The rate of charge leaving the capacitor is equal to the rate of charge passing through the circuit (the current)

$$I = -\frac{dQ}{dt}$$

- The loop then becomes (dividing by R and rearranging)

$$\frac{Q}{C} - IR = 0$$

RC Circuits

- The rate of charge leaving the capacitor is equal to the rate of charge passing through the circuit (the current)

$$I = -\frac{dQ}{dt}$$

- The loop then becomes (dividing by R and rearranging)

$$\frac{Q}{C} - IR = 0$$

RC Circuits

- The rate of charge leaving the capacitor is equal to the rate of charge passing through the circuit (the current)

$$I = -\frac{dQ}{dt}$$

- The loop then becomes (dividing by R and rearranging)

$$\begin{aligned}\frac{Q}{C} - IR &= 0 \\ \frac{Q}{C} + \frac{dQ}{dt}R &= 0\end{aligned}$$

RC Circuits

- The rate of charge leaving the capacitor is equal to the rate of charge passing through the circuit (the current)

$$I = -\frac{dQ}{dt}$$

- The loop then becomes (dividing by R and rearranging)

$$\frac{Q}{C} - IR = 0$$

$$\frac{Q}{C} + \frac{dQ}{dt}R = 0$$

$$\frac{Q}{RC} + \frac{dQ}{dt} = 0$$

RC Circuits

- The rate of charge leaving the capacitor is equal to the rate of charge passing through the circuit (the current)

$$I = -\frac{dQ}{dt}$$

- The loop then becomes (dividing by R and rearranging)

$$\begin{aligned}\frac{Q}{C} - IR &= 0 \\ \frac{Q}{C} + \frac{dQ}{dt}R &= 0 \\ \frac{Q}{RC} + \frac{dQ}{dt} &= 0 \\ \frac{dQ}{Q} &= -\frac{1}{RC}dt\end{aligned}$$

- We can solve this by integrating it.

RC Circuits

- The integral is

$$\int_{Q_0}^Q \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$

RC Circuits

- The integral is

$$\int_{Q_0}^Q \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$

- We can do that integral

$$\ln Q \Big|_{Q_0}^Q = \ln Q - \ln Q_0 = \ln \left(\frac{Q}{Q_0} \right) = -\frac{t}{RC}$$

RC Circuits

- The integral is

$$\int_{Q_0}^Q \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$

- We can do that integral

$$\ln Q \Big|_{Q_0}^Q = \ln Q - \ln Q_0 = \ln \left(\frac{Q}{Q_0} \right) = -\frac{t}{RC}$$

- Solving for Q gives

$$Q = Q_0 e^{-t/RC} = Q_0 e^{-t/\tau}$$

where $\tau = RC$ is the **time constant** of the circuit.

RC Circuits

- The integral is

$$\int_{Q_0}^Q \frac{dQ}{Q} = -\frac{1}{RC} \int_0^t dt$$

- We can do that integral

$$\ln Q \Big|_{Q_0}^Q = \ln Q - \ln Q_0 = \ln \left(\frac{Q}{Q_0} \right) = -\frac{t}{RC}$$

- Solving for Q gives


$$Q = Q_0 e^{-t/RC} = Q_0 e^{-t/\tau}$$

where $\tau = RC$ is the **time constant** of the circuit.

- The resistor current is then


$$I = -\frac{dQ}{dt} = \frac{Q_0}{\tau} e^{-t/\tau} = \frac{Q_0}{RC} e^{-t/\tau} = \frac{\Delta V_C}{R} e^{-t/\tau} = I_0 e^{-t/\tau}$$

RC Circuits

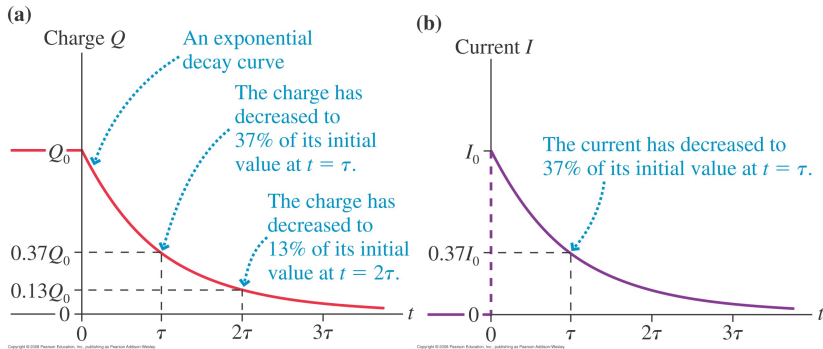


Charging a Capacitor

(a) Switch closes at $t = 0$ s.

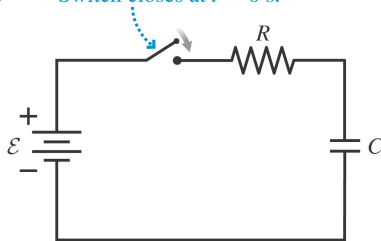

Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley

(b)

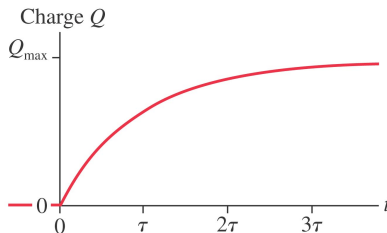

Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley