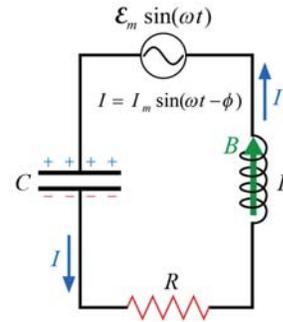


MAIN POINTS

Series LCR Circuit Driven by an AC Generator Sustains Oscillations

Energy supplied by a generator is dissipated by the resistor and stored in the capacitor and inductor.



Phasors

Phasors are vectors that rotate at the generator frequency and can be used to determine the current and the voltages in the circuit.

Reactances are defined to relate the maximum voltage across each element to the maximum current in the circuit.

$$X_L \equiv \omega L$$


$$X_C \equiv \frac{1}{\omega C}$$

The maximum current (I_m) and the phase (ϕ) between the current and the driving voltage can be determined from the impedance triangle.

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$I_m = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}} \equiv \frac{\mathcal{E}_m}{Z}$$

Voltage Phasor Diagram

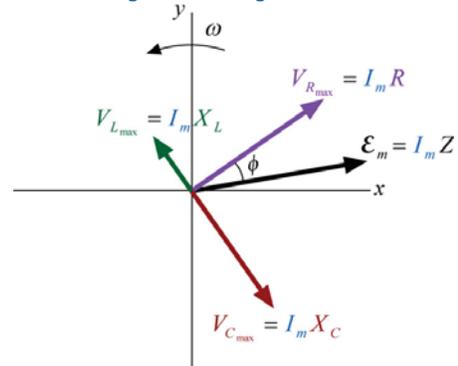

Impedance Phasor Diagram

