

# *Electricity & Magnetism*

## *Lecture 8: Capacitors*

Today's Concept:

Capacitors

(Capacitors in a circuits, Dielectrics, Energy in capacitors)

- ⑩ Yesterday's homework credit 100% until next week.
  - Because of the maintenance outage lasted longer
- ⑩ There are practise problems on flipit that you can work.

– Review Problems

- 31. Coulomb's Law
- 32. Electric Fields
- 33. Electric Flux and Field Lines
- 34. Gauss' Law
- 35. Electric Potential Energy
- 36. Electric Potential
- 37. Conductors and Capacitors

# Stuff you asked about:

- “the formula for calculating capacitance in parallel and series are the opposite of the formula for resistance “
- “Please go over the Capacitors with and without a dielectric from checkpoint.”
- “this stuff is a lot harder than what we’ve been doing before, one thing i don’t understand is when you disconnect a battery from a capacitor what exactly happens, how come it still has a charge?? ”
- “can we add our own formulas to the sheet like how we did for phys 120 last term?”
  - Within reason.

# *Capacitors, connected and unconnected*


- ★ A capacitor that is **un**connected to a battery has constant charge:  $V = Q/C$  ( $V$  is determined by  $Q$ )
- ★ A capacitor connected to a battery has a constant voltage.  $Q = CV$  ( $Q$  is determined by  $V$ )
- ★ Capacitors in parallel have the same voltage. Charge may redistribute among them:  $Q_1/C_1 = Q_2/C_2 = Q_2/C_2 \dots$
- ★ Capacitors in series have the same charge.

# Dielectric

- ★ Charged capacitor, not connected to battery
- ★ Dielectric makes  $\Delta V$  smaller

air capacitor


$$\kappa = 1$$

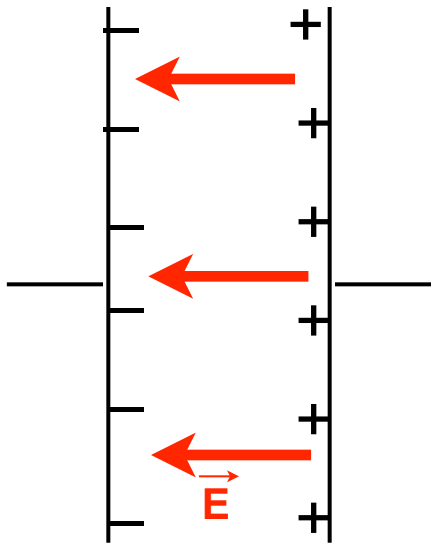

$$C = \epsilon_0 A/L$$

dielectric capacitor


$$\kappa > 1$$

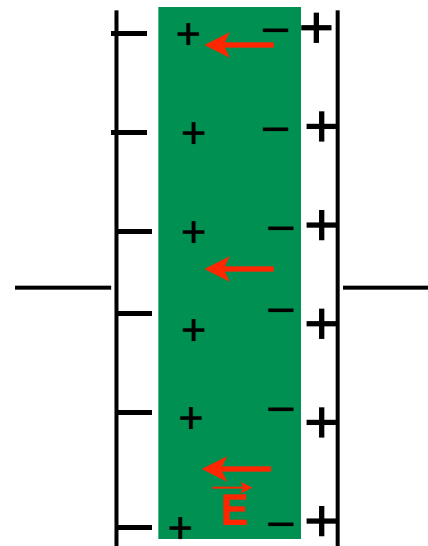

$$C = \kappa \epsilon_0 A/L$$


$E$  inside dielectric is smaller than  $E$  outside.  
The charge on the surface of the dielectric partially cancels the  $E$  field from the charge on the plates.  
Therefore the  $\Delta V$  between the plates is less.

# Simple Capacitor Circuit

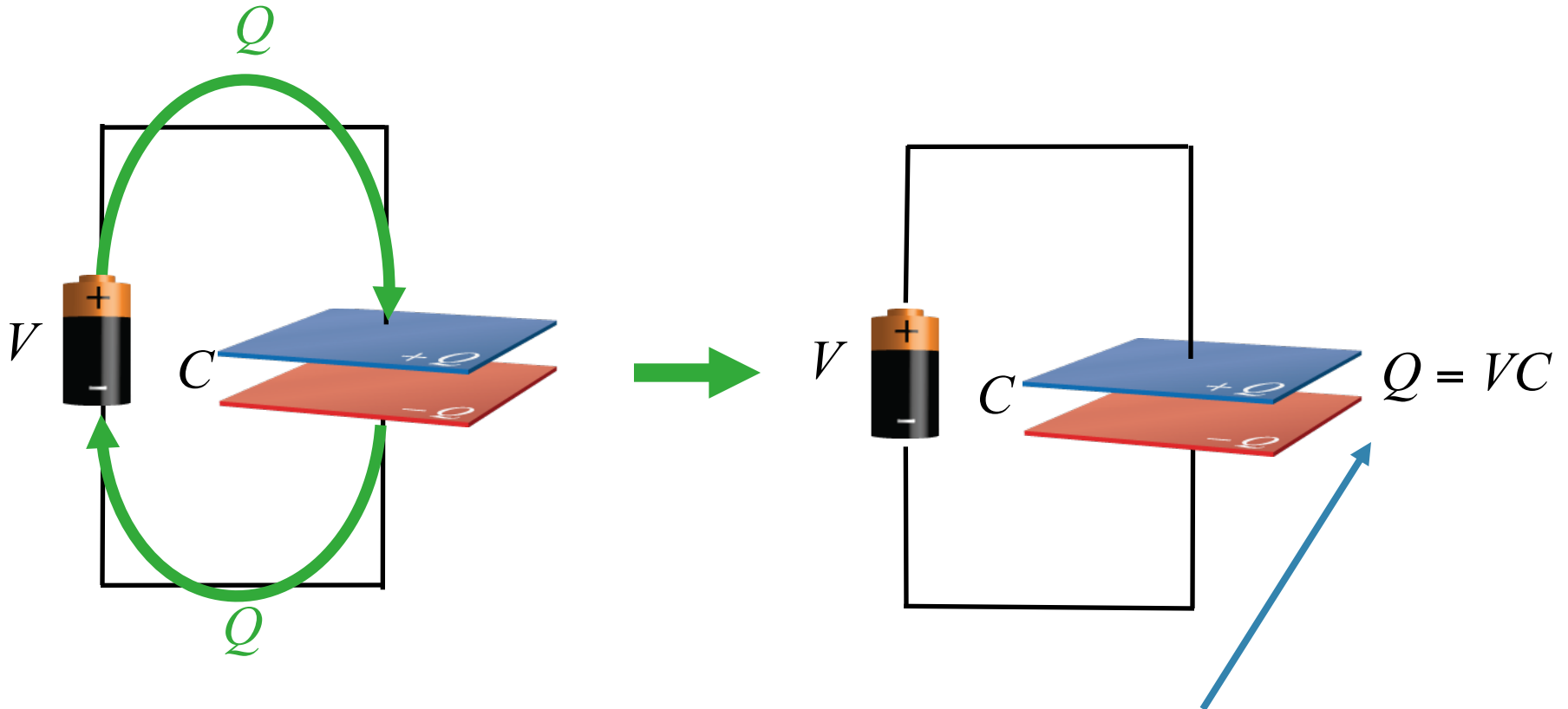


This “ $Q$ ” really means that the battery has moved charge  $Q$  from one plate to the other, so that one plate holds  $+Q$  and the other  $-Q$ .

# Dielectrics

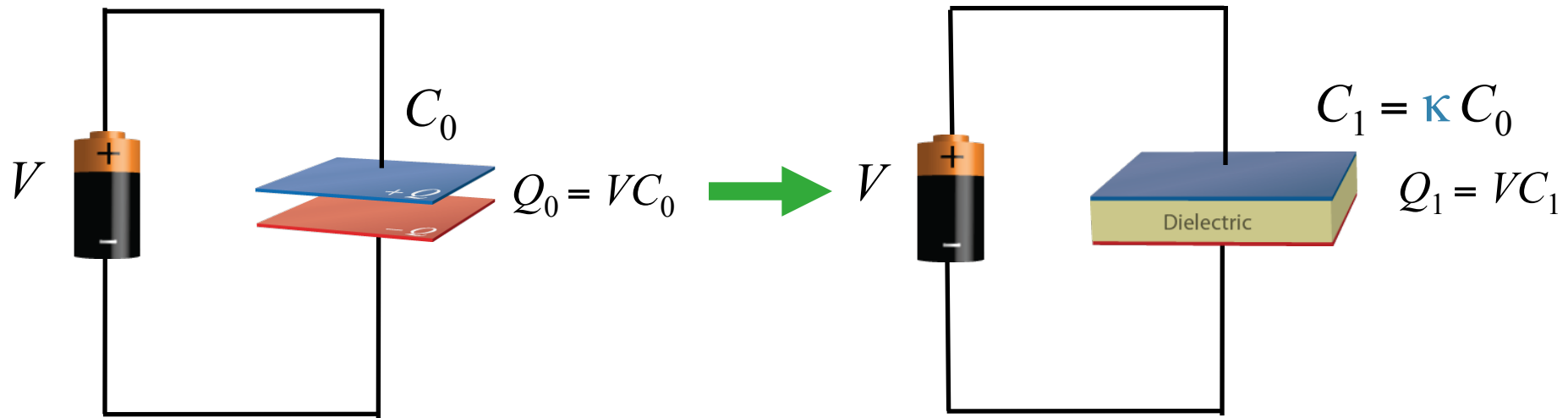

By adding a dielectric you are just making a new capacitor with larger capacitance (factor of  $\kappa$ )

# Parallel Capacitor Circuit

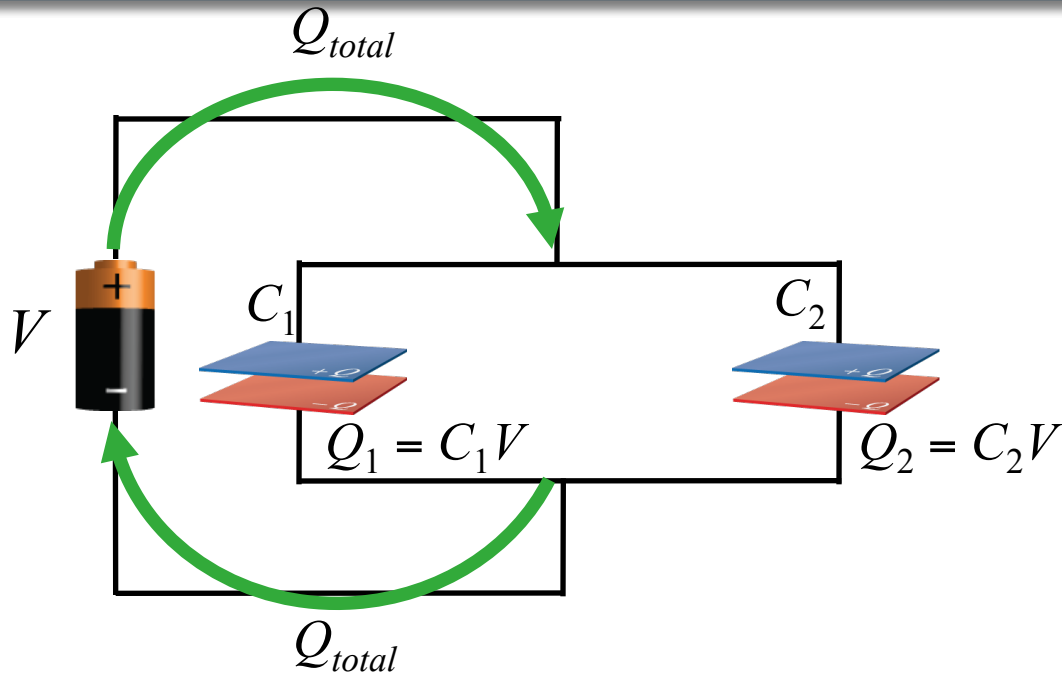


**Key point:**  $V$  is the same for both capacitors

**Key Point:**  $Q_{total} = Q_1 + Q_2 = VC_1 + VC_2 = V(C_1 + C_2)$

$$C_{total} = C_1 + C_2$$



# Series Capacitor Circuit

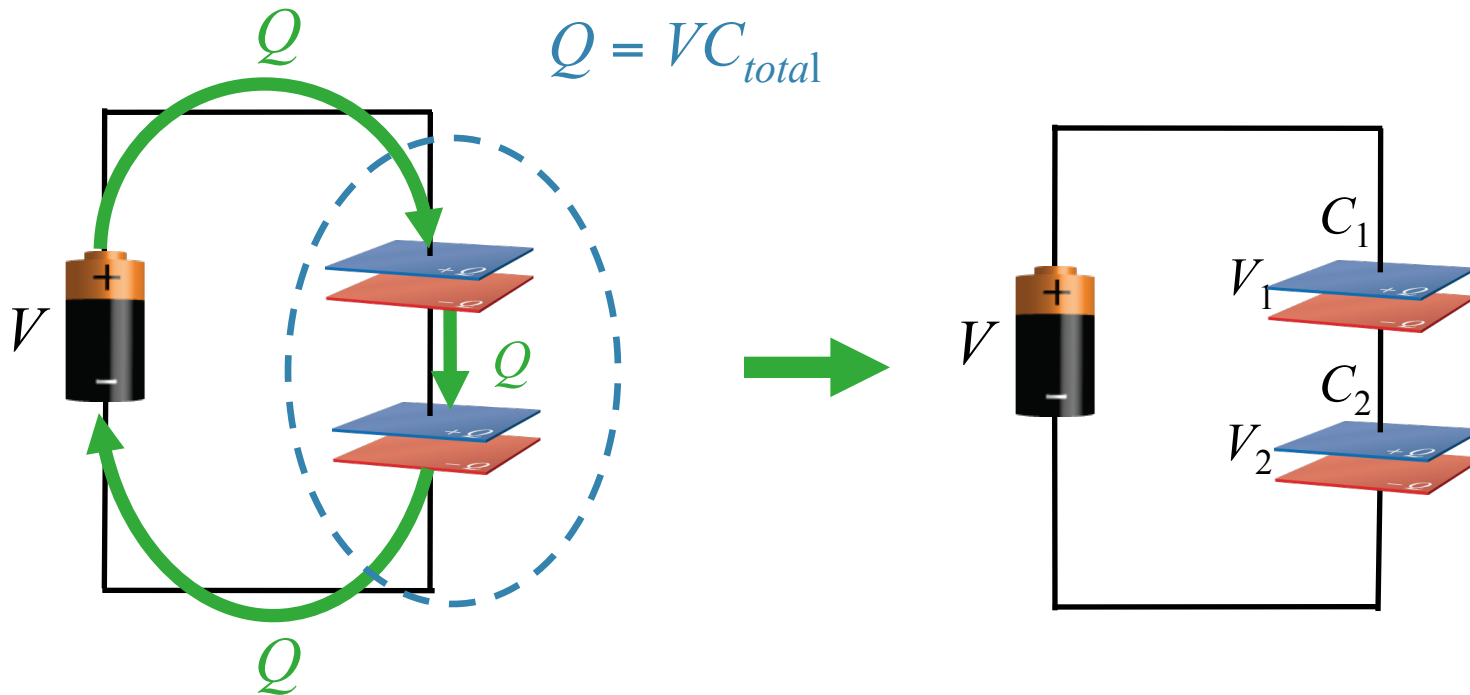

**Key point:**  $Q$  is the same for both capacitors



**Key point:**  $Q = VC_{total} = V_1C_1 = V_2C_2$

**Also:**  $V = V_1 + V_2 \quad \longrightarrow \quad Q/C_{total} = Q/C_1 + Q/C_2$


$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2}$$
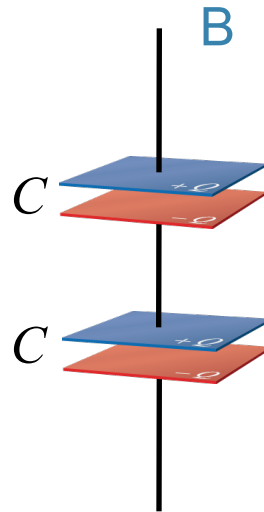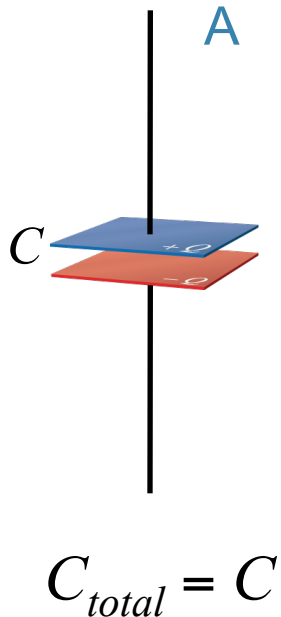
# CheckPoint: Three Capacitor Configurations

The three configurations shown below are constructed using identical capacitors. Which of these configurations has lowest total capacitance?




$$C_{total} = C/2$$

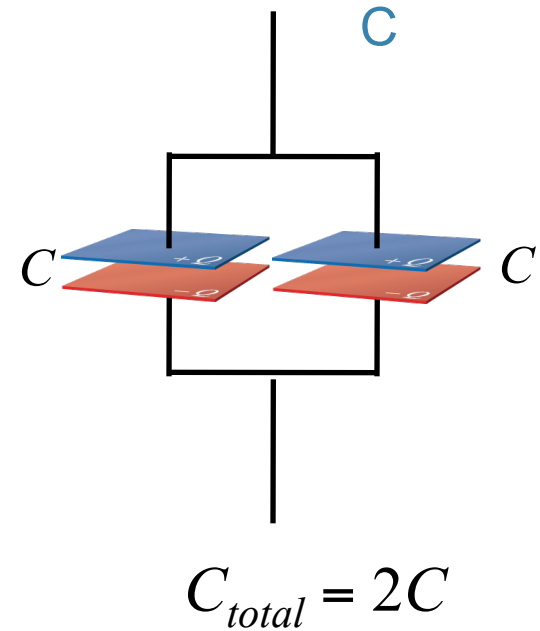


D: All 3 are the same

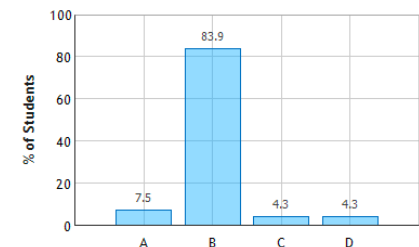Three Capacitor Configurations: Question 1 (N = 93)



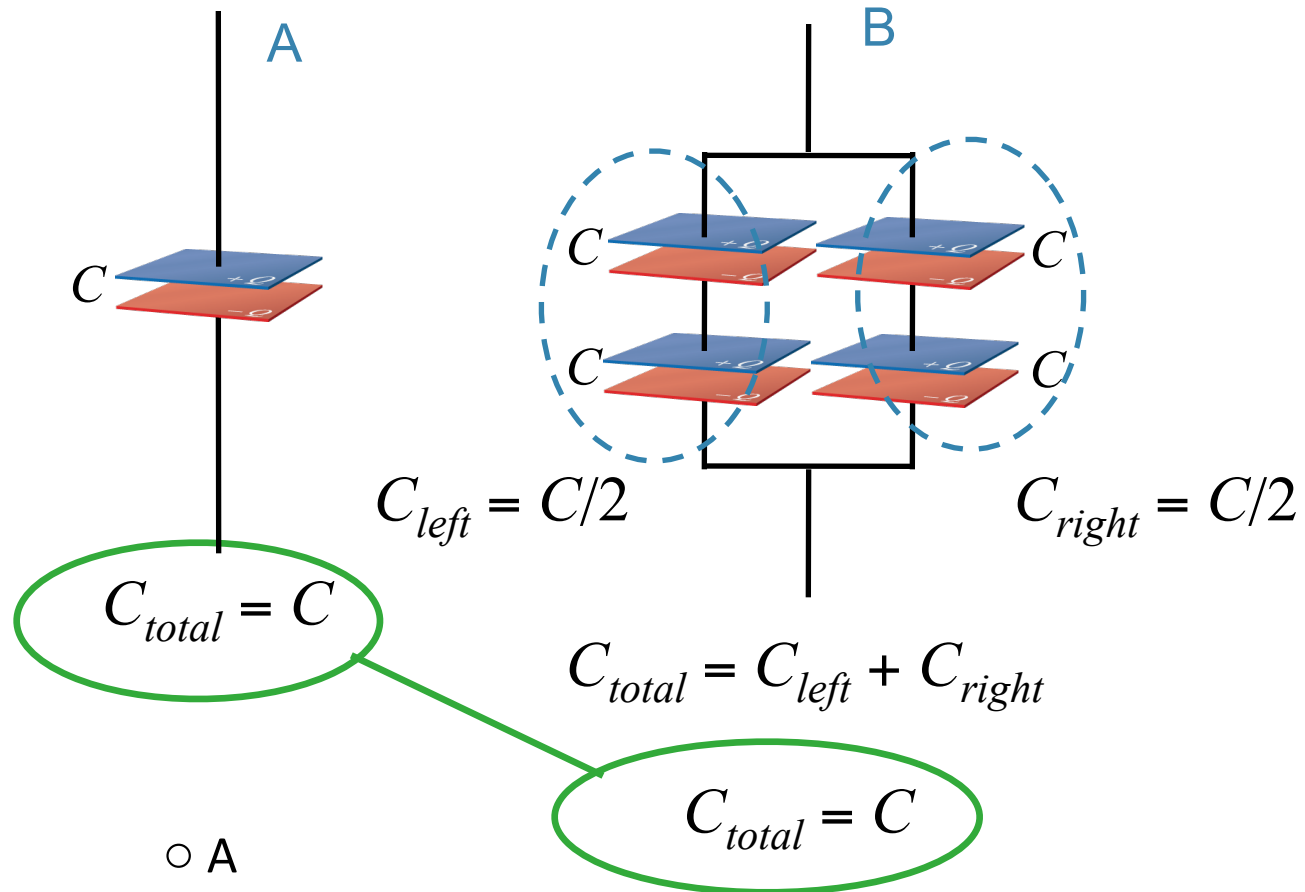
# Checkpoint: Two Capacitor Configurations

The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?



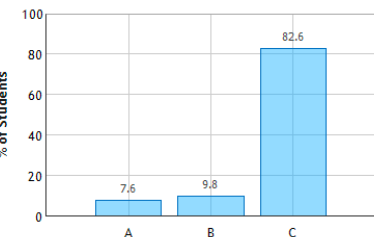Two Capacitor Configurations: Question 1 (N = 92)




☐ A

☐ B

☐ Both configurations have the same capacitance

# Clicker Question: Capacitor Network

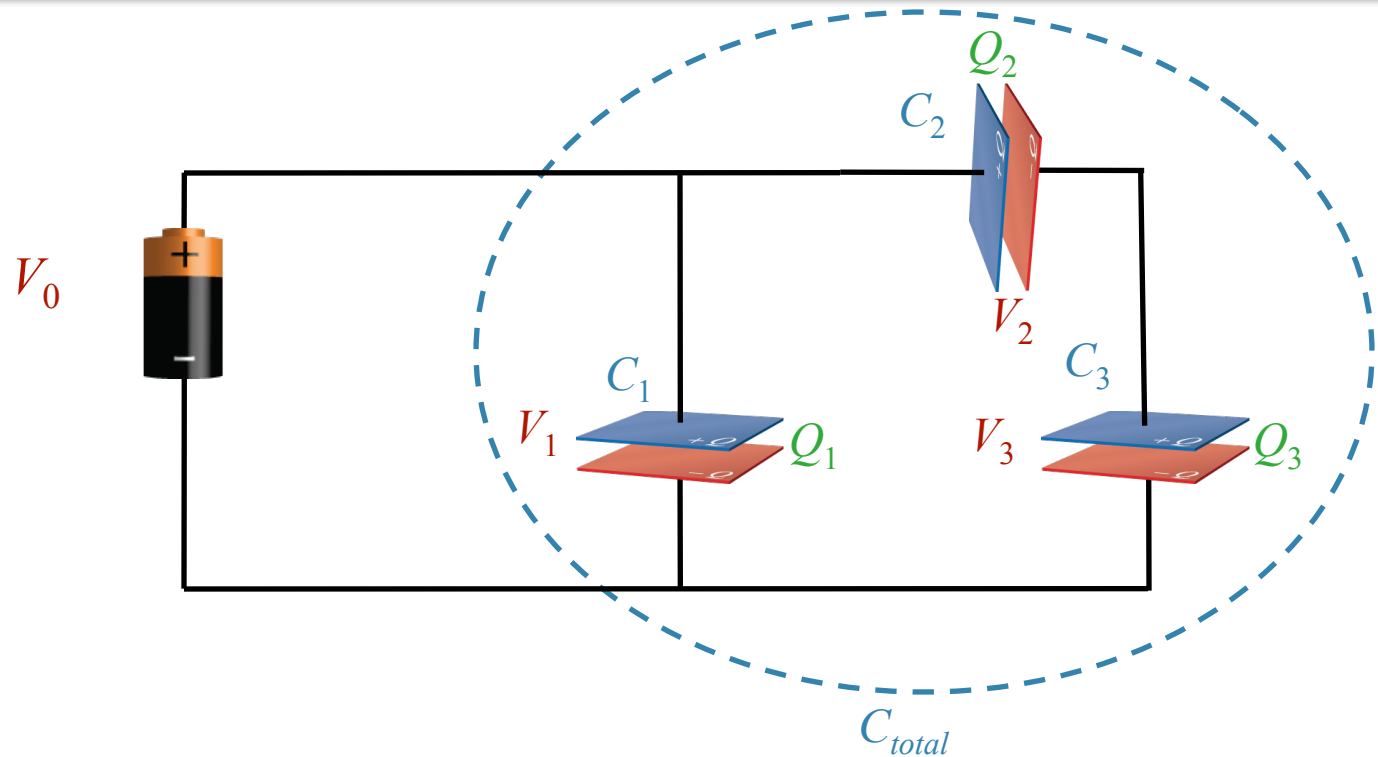

Which of the following is **NOT** necessarily true:

- A)  $V_0 = V_1$
- B)  $C_{total} > C_1$
- C)  $V_2 = V_3$**
- D)  $Q_2 = Q_3$
- E)  $V_1 = V_2 + V_3$

# CheckPoint: Capacitor Network

A circuit consists of three unequal capacitors  $C_1$ ,  $C_2$ , and  $C_3$  which are connected to a battery of voltage  $V_0$ . The capacitance of  $C_2$  is twice that of  $C_1$ . The capacitance of  $C_3$  is three times that of  $C_1$ . The capacitors obtain charges  $Q_1$ ,  $Q_2$ , and  $Q_3$ .

Compare  $Q_1$ ,  $Q_2$ , and  $Q_3$ .


A.  $Q_1 > Q_3 > Q_2$

B.  $Q_1 > Q_2 > Q_3$


C.  $Q_1 > Q_2 = Q_3$

D.  $Q_1 = Q_2 = Q_3$

E.  $Q_1 < Q_2 = Q_3$

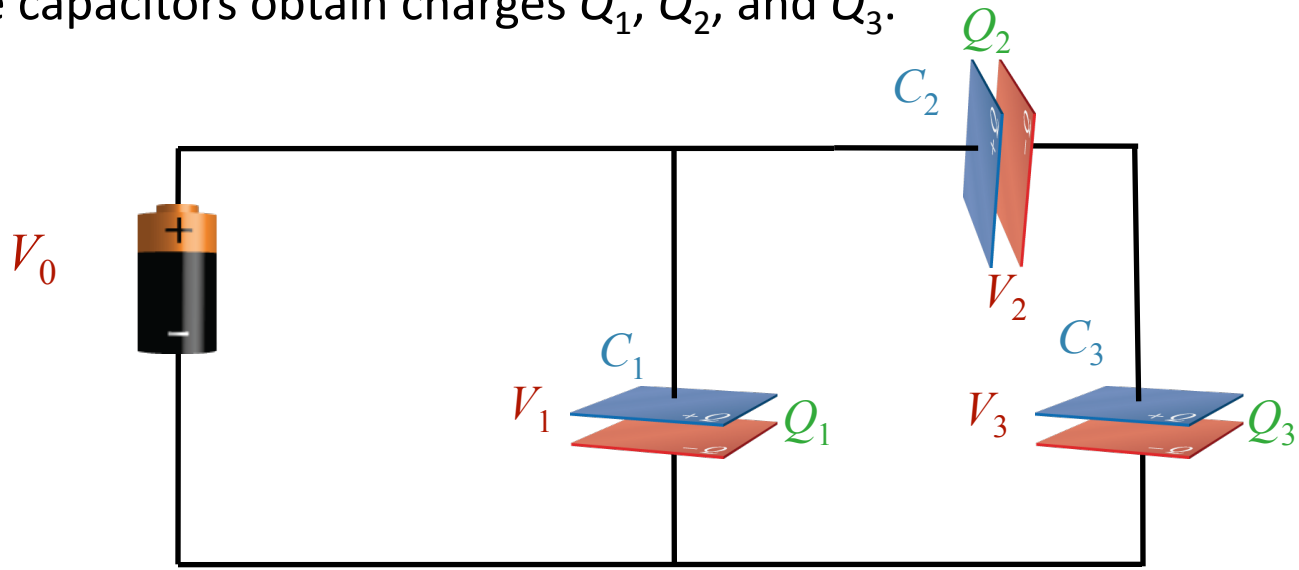


Capacitor Network: Question 1 (N = 91)

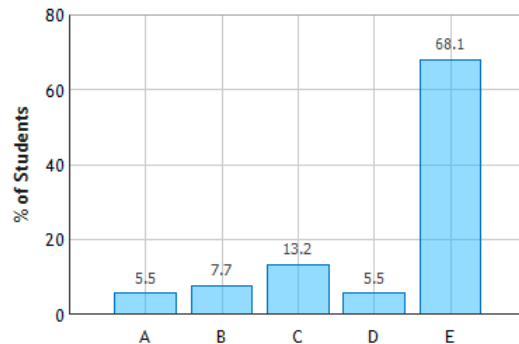
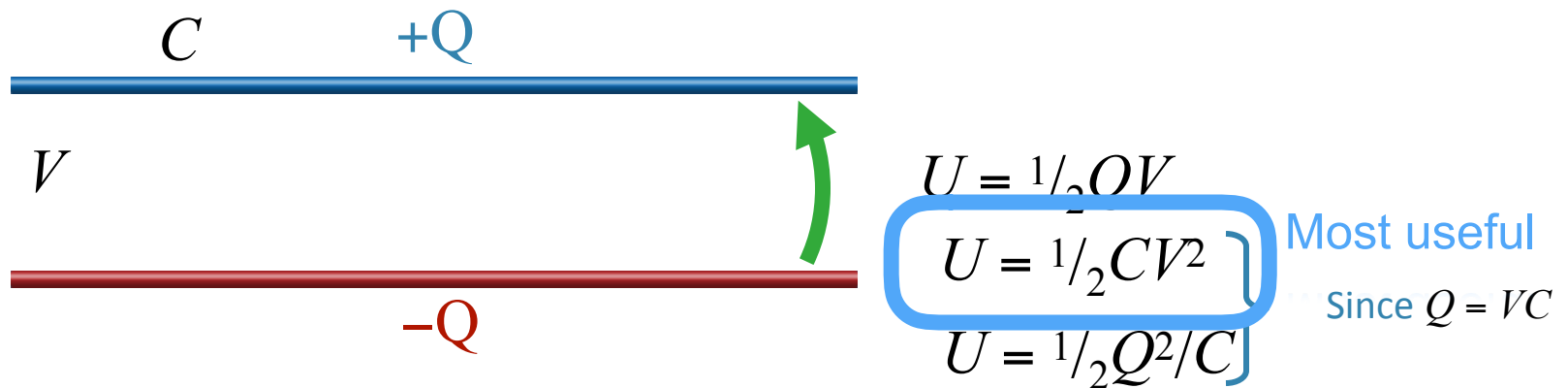
# Energy in a Capacitor


In Prelecture 7 we calculated the work done to move charge  $Q$  from one plate to another:



This is potential energy waiting to be used...

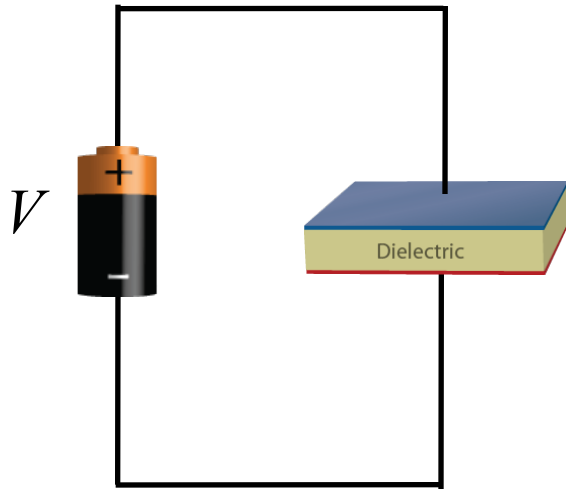
# Messing with Capacitors

If connected to a battery  $V$  stays constant



$$\left. \begin{array}{l} V_1 = V \\ C_1 = \kappa C \end{array} \right\} \rightarrow \begin{array}{l} Q_1 = C_1 V_1 \\ = \kappa C V = \kappa Q \end{array}$$

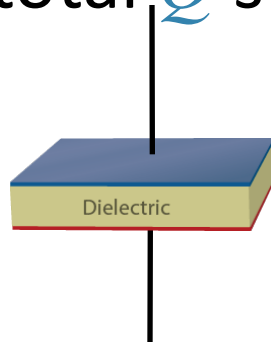
If isolated then total  $Q$  stays constant



$$\left. \begin{array}{l} Q_1 = Q \\ C_1 = \kappa C \end{array} \right\} \rightarrow \begin{array}{l} V_1 = Q_1 / C_1 \\ = Q / \kappa C = V / \kappa \end{array}$$
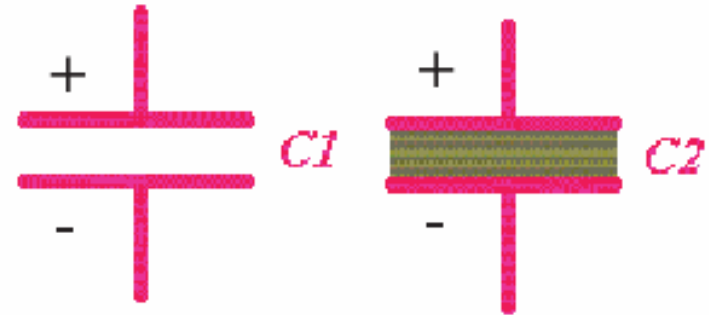
# CheckPoint: Capacitors and Dielectrics 1

Two identical parallel plate capacitors are given the same charge  $Q$ , after which they are disconnected from the battery. After  $C_2$  has been charged and disconnected, it is filled with a dielectric.



Compare the voltages of the two capacitors.

A.  $V_1 > V_2$

B.  $V_1 = V_2$

C.  $V_1 < V_2$


“The electric field decreases on the second due to the dielectric, so its voltage must decrease.”

“The little brown thing is stopping the pikachus from reaching the other side.”

“Dielectrics don't change voltages.”

“Capacitance lowers in case 2, meaning  $V$  increases in case 2.”

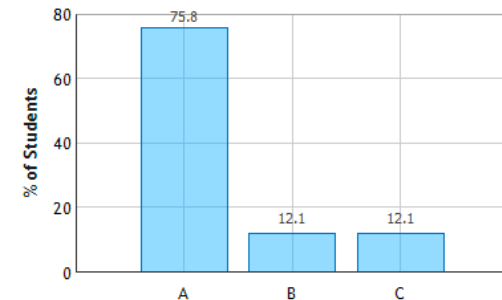Capacitors with and without a Dielectric:  
Question 1 (N = 91)






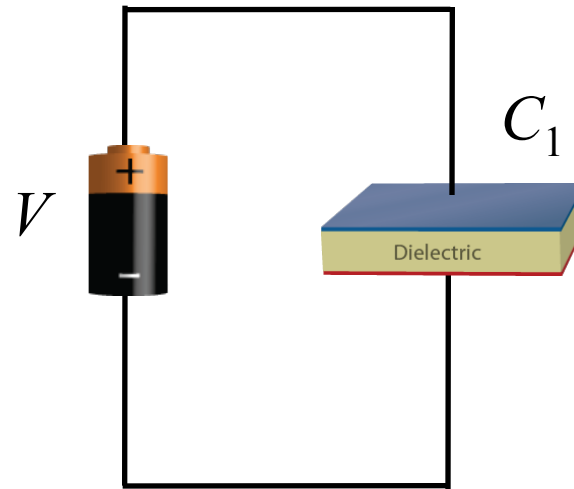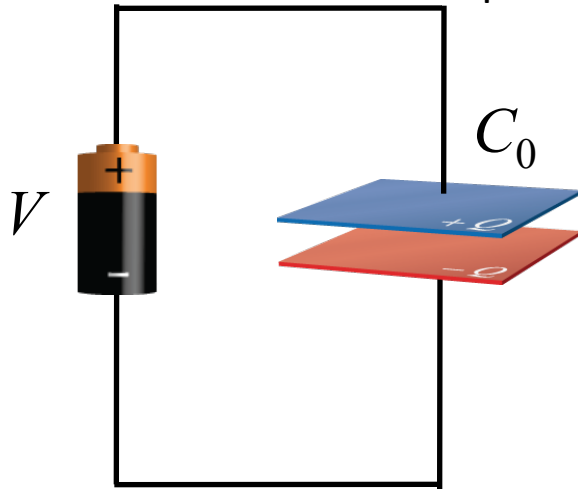
# Clicker Question: Messing with Capacitors



Two identical parallel plate capacitors are connected to identical batteries. Then a dielectric is inserted between the plates of capacitor  $C_1$ . Compare the energy stored in the two capacitors.



A)  $U_1 < U_0$

B)  $U_0 = U_1$

C)  $U_1 > U_0$

Compare using  $U = \frac{1}{2}CV^2$

$$U_1/U_0 = \kappa$$

→ Potential Energy goes UP

# CheckPoint: Capacitors and Dielectrics 2


Two identical parallel plate capacitors are given the same charge  $Q$ , after which they are disconnected from the battery. After  $C_2$  has been charged and disconnected, it is filled with a dielectric.

Compare the potential energy stored by the two capacitors.

A.  $U_1 > U_2$

B.  $U_1 = U_2$

C.  $U_1 < U_2$

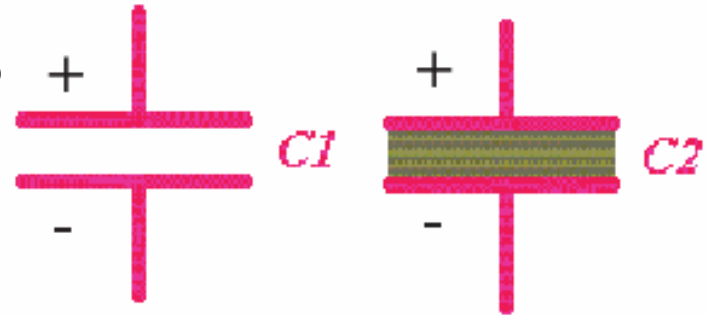


“If the electric field goes down, then so does the potential energy of the second system..”

“Dielectrics don't affect potential.”


“ $U = QV$ . Since voltage remains constant and charge increases, potential energy must also increase.”

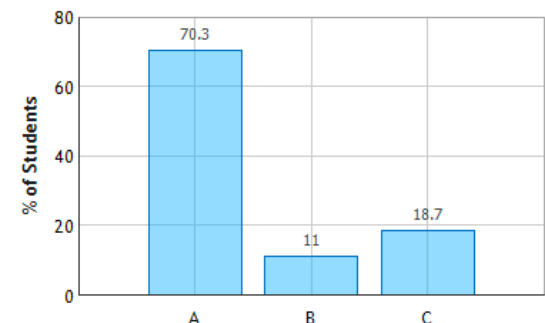Capacitors with and without a Dielectric:  
Question 3 (N = 91)


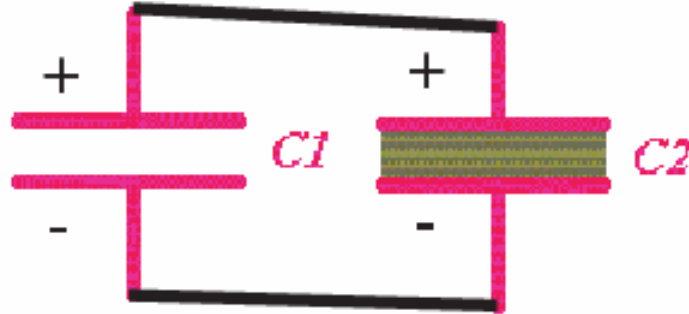
# CheckPoint: Capacitors and Dielectrics 3

The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?




$V$  must be the same !

- A) The charges will flow so that the charge on C1 will become equal to the charge on C2.
- B) The charges will flow so that the energy stored in C1 will become equal to the energy stored in C2
- C) The charges will flow so that the potential difference across C1 will become the same as the potential difference across C2.
- D) No charges will flow. The charge on the capacitors will remain what it was before they were connected.


Q:  $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \rightarrow Q_1 = \frac{C_1}{C_2} Q_2$

U:  $U_1 = \frac{1}{2} C_1 V^2$   
 $U_2 = \frac{1}{2} C_2 V^2 \rightarrow U_1 = \frac{C_1}{C_2} U_2$

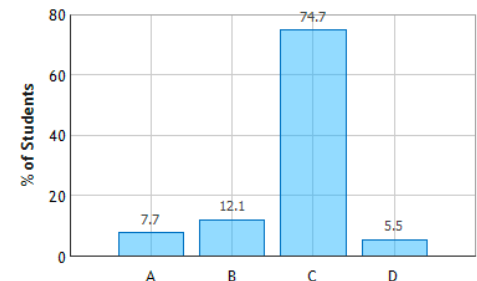Capacitors with and without a Dielectric:  
Question 5 (N = 91)



# Calculation

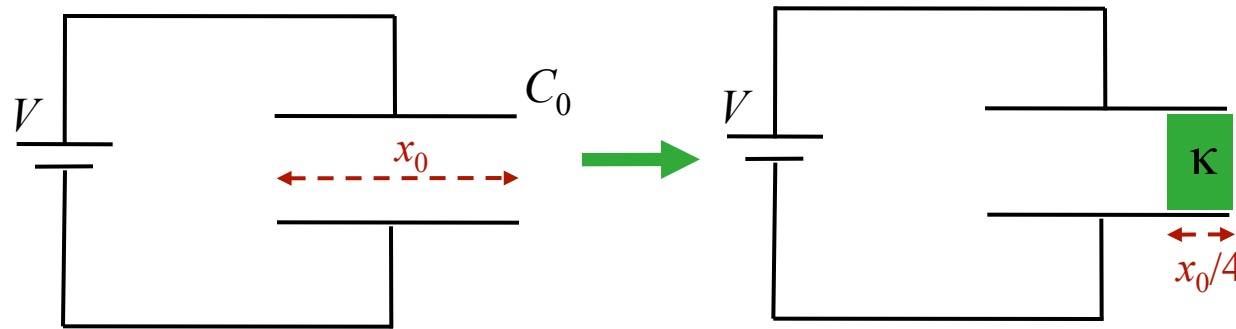

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.

Conceptual Analysis:

$$C \equiv \frac{Q}{V}$$

What changes when the dielectric added?

- A) Only  $C$     B) only  $Q$     C) only  $V$     **D)  $C$  and  $Q$**     E)  $V$  and  $Q$

Adding dielectric changes the physical capacitor




$C$  changes

$V$  does not change and  $C$  changes



$Q$  changes

# Calculation

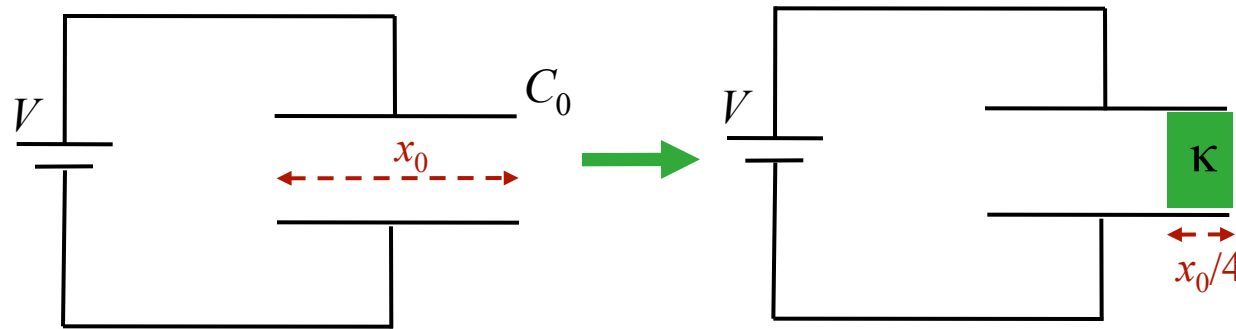

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.

## Strategic Analysis:

- Calculate new capacitance  $C$
- Apply definition of capacitance to determine  $Q$

To calculate  $C$ , let's first look at:



A)  $V_{left} < V_{right}$


B)  $V_{left} = V_{right}$

C)  $V_{left} > V_{right}$

What is  $Q_f$ , the final charge on the capacitor?

The conducting plate is an equipotential !

# Calculation

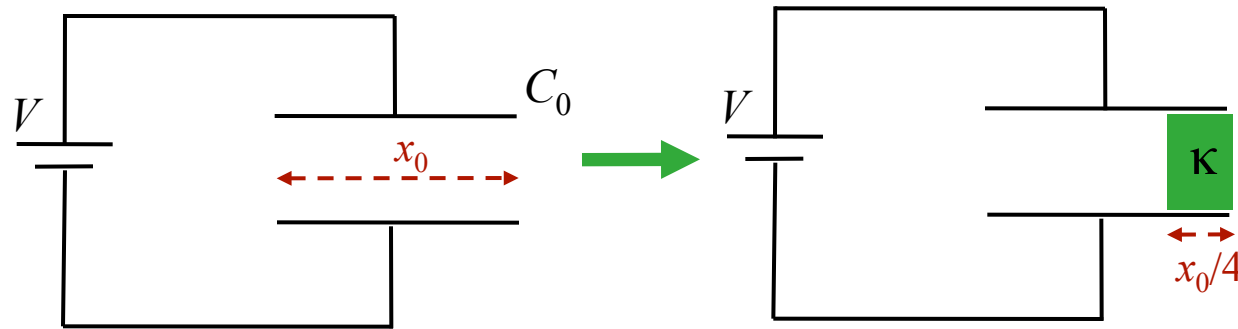


An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.

Can consider capacitor to be two capacitances,  $C_1$  and  $C_2$ , in parallel

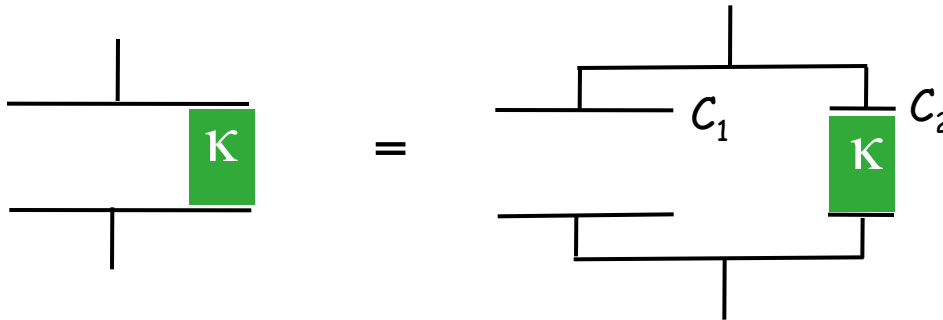What is  $Q_f$ , the final charge on the capacitor?




What is  $C_1$  ?

- A)  $C_1 = C_0$    B)  $C_1 = \frac{3}{4}C_0$    C)  $C_1 = \frac{4}{3}C_0$    D)  $C_1 = \frac{1}{4}C_0$

In general. For parallel plate capacitor:  $C = \epsilon_0 A/d$

$$\begin{array}{l} A = \frac{3}{4}A_0 \\ d = d_0 \end{array} \quad \rightarrow \quad C_1 = \frac{3}{4}(\epsilon_0 A_0/d_0) \quad \rightarrow \quad C_1 = \frac{3}{4}C_0$$

# Calculation

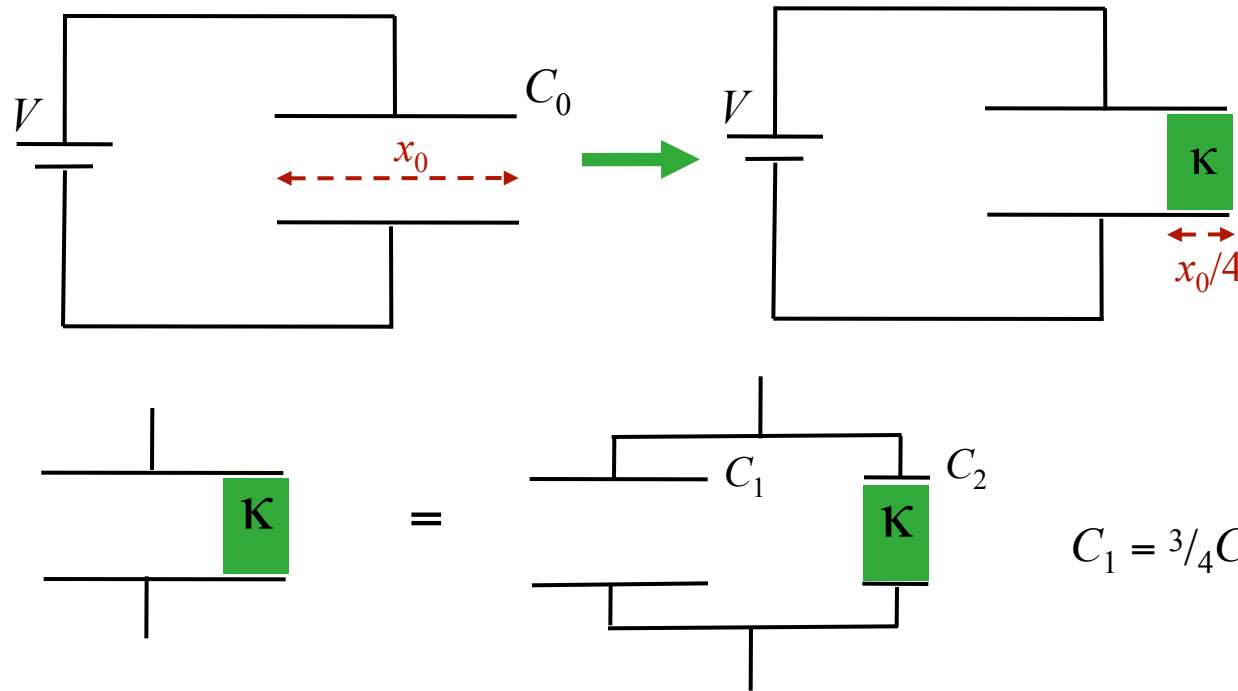

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.

What is  $Q_f$ , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

What is  $C_2$  ?

A)  $C_2 = \kappa C_0$

B)  $C_2 = \frac{3}{4} \kappa C_0$


C)  $C_2 = \frac{4}{3} \kappa C_0$

**D)  $C_2 = \frac{1}{4} \kappa C_0$**

In general. For parallel plate capacitor filled with dielectric:  $C = \kappa \epsilon_0 A/d$


$$\begin{matrix} A = \frac{1}{4}A_0 \\ d = d_0 \end{matrix} \quad \rightarrow \quad C = \frac{1}{4}(\kappa \epsilon_0 A_0/d_0) \quad \rightarrow \quad C_2 = \frac{1}{4} \kappa C_0$$

# Calculation

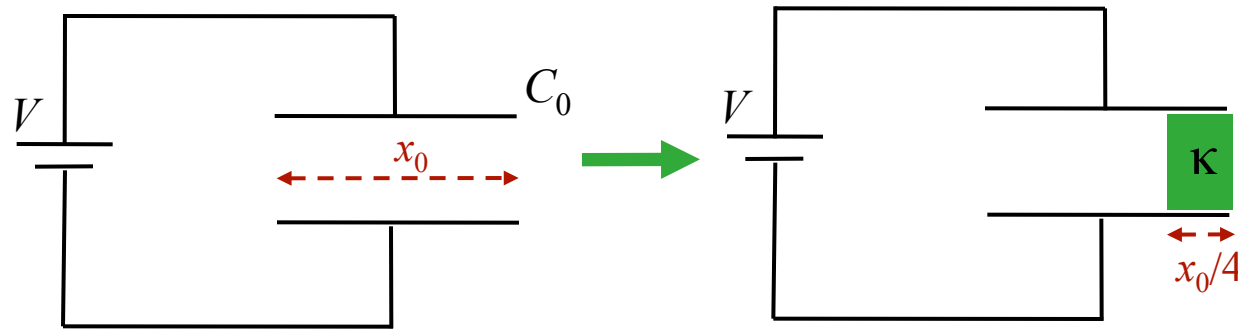

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

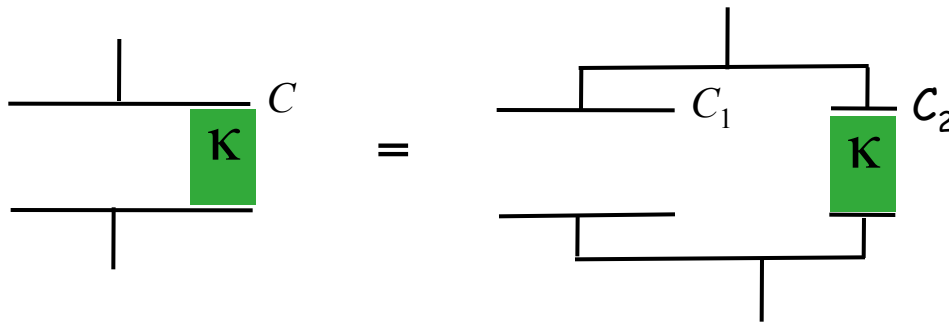A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.



$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$

What is  $Q_f$ , the final charge on the capacitor?

What is  $C$ ?

A)  $C = C_1 + C_2$

B)  $C = C_1 + \kappa C_2$


C)  $C = \left( \frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

$C$  = parallel combination of  $C_1$  and  $C_2$ :  $C = C_1 + C_2$

$\rightarrow C = C_0 \left( \frac{3}{4} + \frac{1}{4}\kappa \right)$




# Calculation

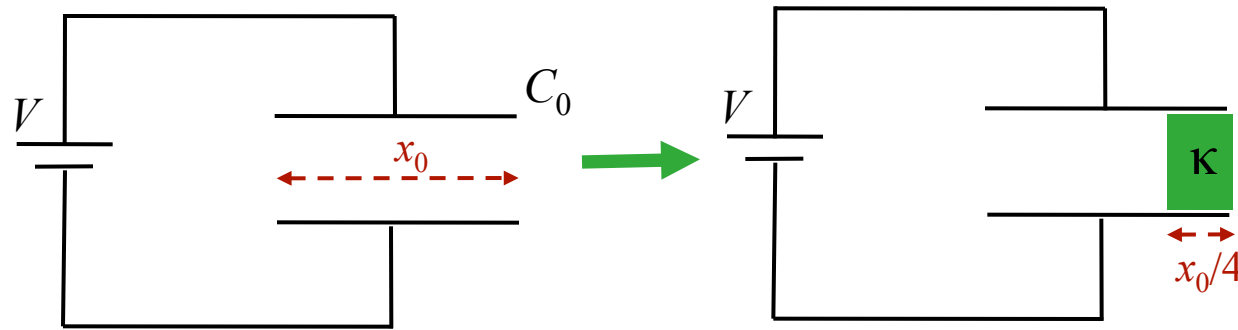

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$ .

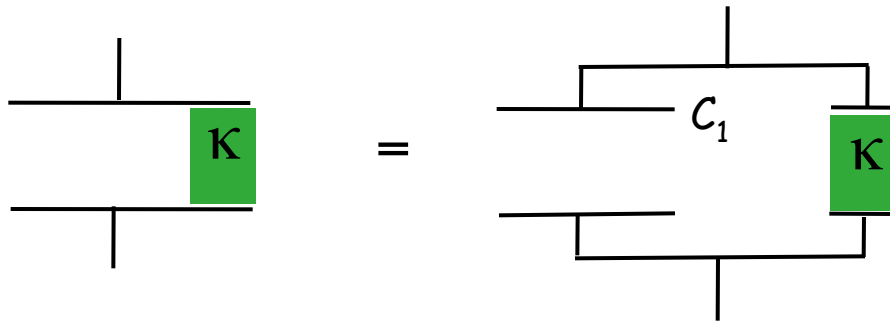A dielectric ( $\kappa$ ) of width  $x_0/4$  is inserted into the gap as shown.



What is  $Q_f$ , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$


$$\rightarrow C = C_0 \left( \frac{3}{4} + \frac{1}{4}\kappa \right)$$

What is  $Q$ ?

$$C \equiv \frac{Q}{V} \rightarrow Q = VC$$

$$Q = VC_0 \left( \frac{3}{4} + \frac{1}{4}\kappa \right)$$

# Different Problem

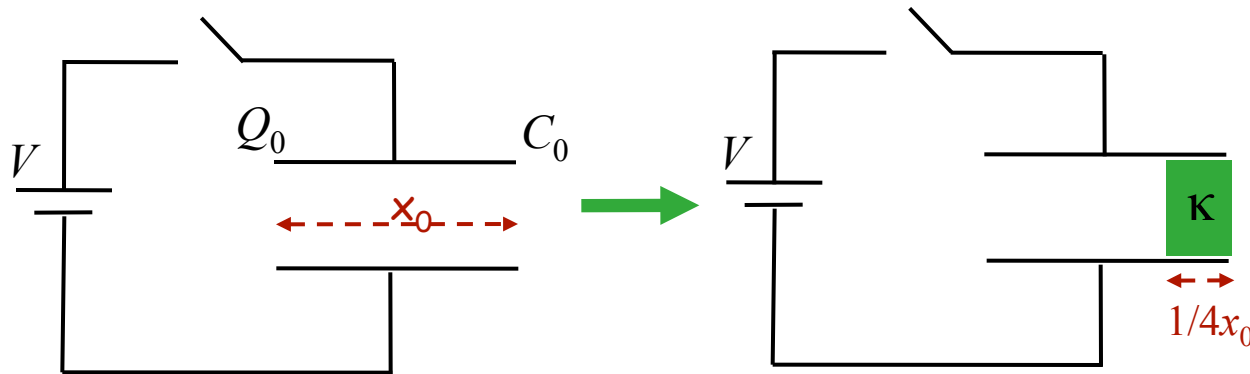

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$  and then **battery is disconnected**.

A dielectric ( $\kappa$ ) of width  $1/4 x_0$  is inserted into the gap as shown.

What is  $V_f$ , the final voltage on the capacitor?

A)  $V_f < V$

B)  $V_f = V$

C)  $V_f > V$

$Q$  stays same: no way to add or subtract


$\rightarrow Q = Q_0 = C_0 V$

We know  $C$ : (property of capacitor)

$\rightarrow C = C_0 (3/4 + 1/4 \kappa)$

$\rightarrow V_f = Q/C = V/(3/4 + 1/4 \kappa)$

# Different Problem

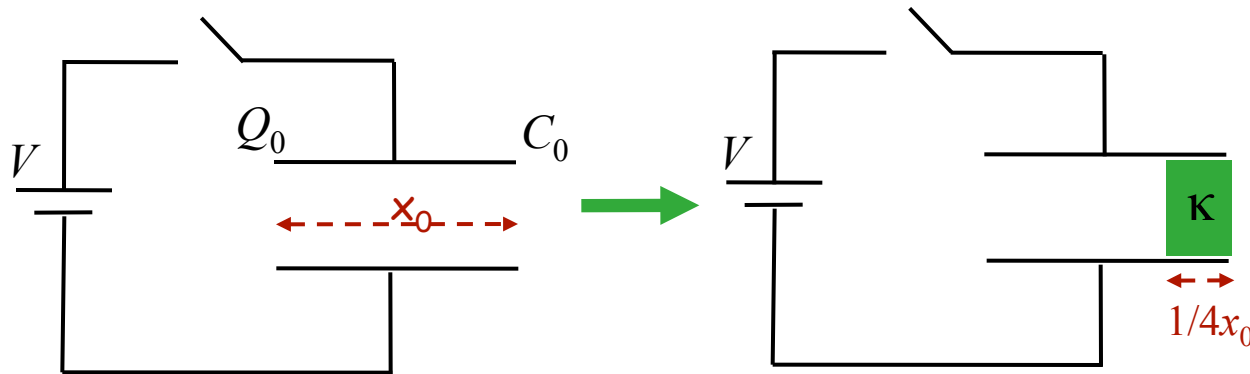

An air-gap capacitor, having capacitance  $C_0$  and width  $x_0$  is connected to a battery of voltage  $V$  and then **battery is disconnected**.

A dielectric ( $\kappa$ ) of width  $1/4 x_0$  is inserted into the gap as shown.

$$V_f = Q/C = V/(3/4 + 1/4 \kappa)$$

How did energy stored in capacitor change when dielectric inserted?

What is  $V_f$ , the final voltage on the capacitor?

A)  $U$  increased    B)  $U$  stayed same    **C)  $U$  decreased**

$$U = \frac{1}{2} Q^2/C$$

$Q$  remained same

$C$  increased



$U$  decreased

# *Capacitors, connected and unconnected*

- ★ A capacitor that is **un**connected to a battery has constant charge:  $V = Q/C$  ( $V$  is determined by  $Q$ )
- ★ A capacitor connected to a battery has a constant voltage.  $Q = CV$  ( $Q$  is determined by  $V$ )
- ★ Capacitors in parallel have the same voltage. Charge may redistribute among them:  $Q_1/C_1 = Q_2/C_2 = Q_2/C_2 \dots$
- ★ Capacitors in series have the same charge.