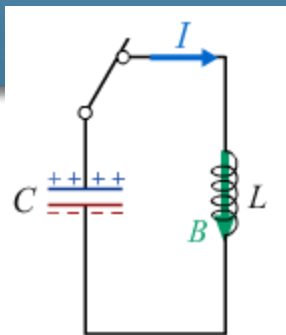





Electricity & Magnetism

Lecture 19



Today's Concepts:

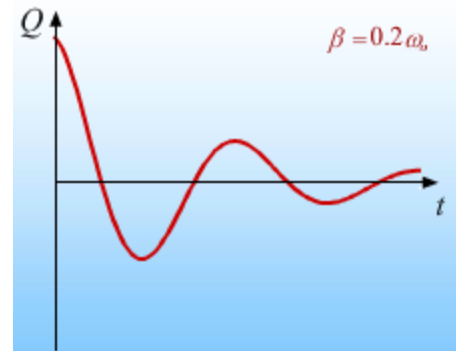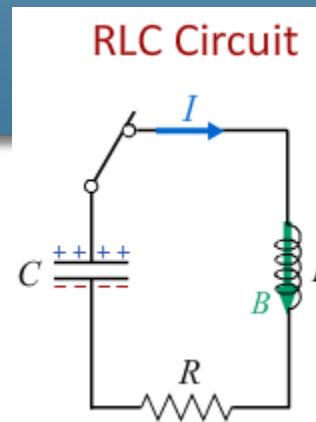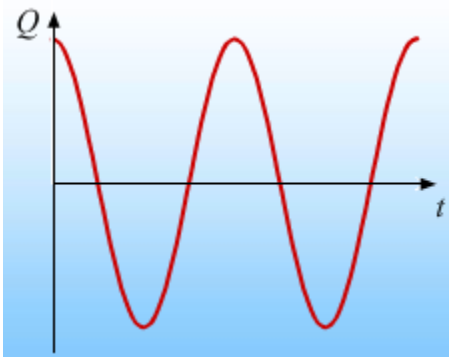- A) Oscillation Frequency
- B) Energy
- C) Damping



Confused — Confident



I am ...

- A. Confused
- B. Somewhat Confused
- C. So-so
- D. Somewhat Confident
- E. Confident

Your Comments

“All of this stuff, I wish we could go slower but I know we cant.”

TOO TRUE: Hang in there, we'll do our best to work on the issues....

What is the use of LC and RLC circuits?

“There are a lot of formulas in this section”


“Please explain the meaning of $\cos(\omega t + x)$ ”

Differential Equations Do Determine
Much Behaviour in Physics. We will
show corresponding equations in
mechanics today

“Why do capacitors start off with a charge
of zero when the switch is opened?
shouldn't they start off with charge? “


It all depends on how the circuit was started.
You have to determine the initial conditions
from the problem statement

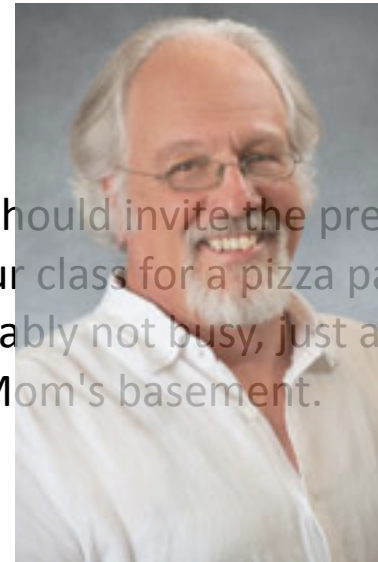We should invite the prelecture narrator over
to our class for a pizza party. I mean, he's
probably not busy, just a voice actor living in
his Mom's basement.



Prof. Gary Glading

LC Circuit

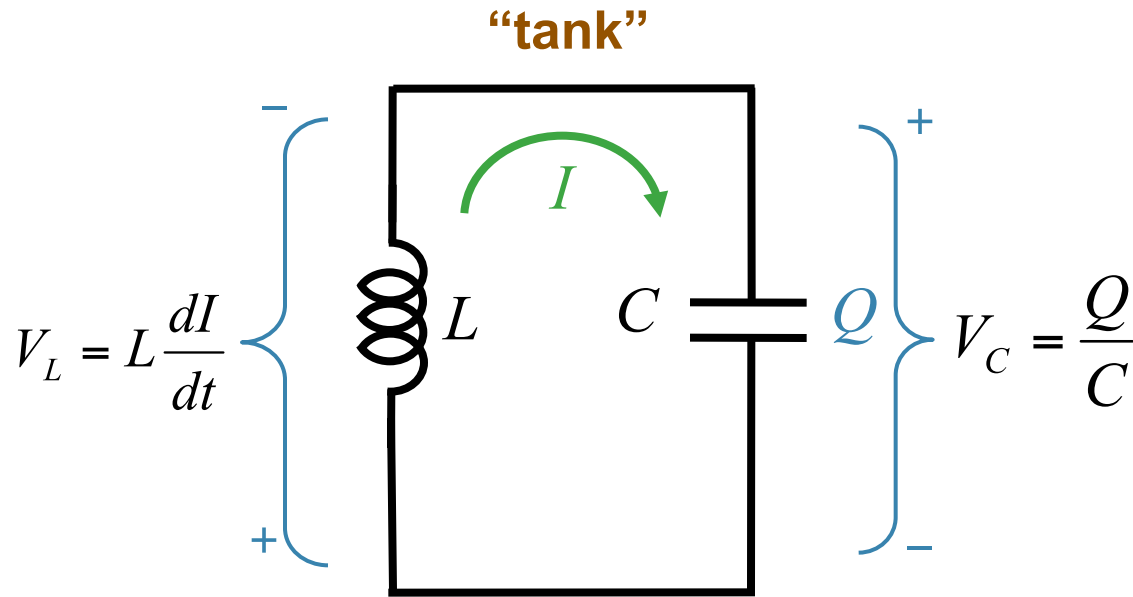

Circuit Equation: $\frac{Q}{C} + L \frac{dI}{dt} = 0$

$$I = \frac{dQ}{dt} \longrightarrow \frac{d^2 Q}{dt^2} = -\frac{Q}{LC} \longrightarrow \frac{d^2 Q}{dt^2} = -\omega^2 Q$$


where

$$\omega = \frac{1}{\sqrt{LC}}$$

$$m \leftrightarrow L$$


$$\frac{d^2 Q}{dt^2} = -\omega^2 Q$$

$$\omega = \frac{1}{\sqrt{LC}}$$

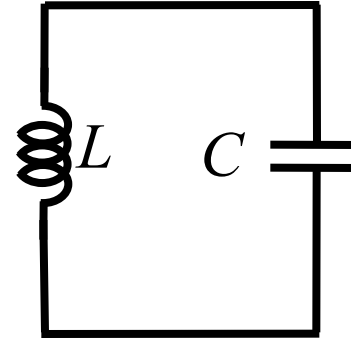

$$\frac{d^2 x}{dt^2} = -\omega^2 x$$

$$\omega = \sqrt{\frac{k}{m}}$$

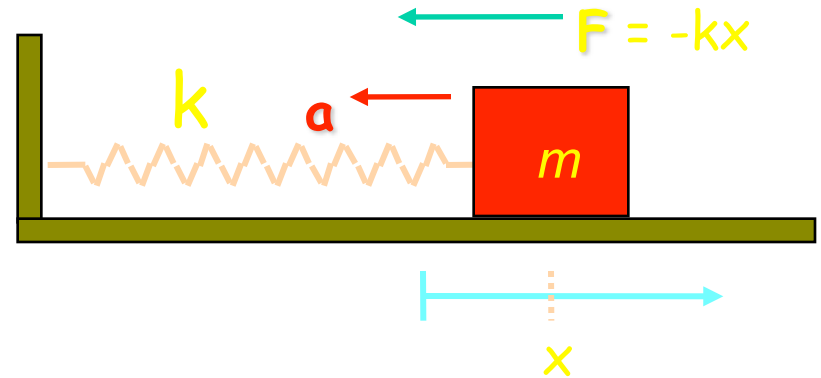



Same thing if we notice that

$$k \leftrightarrow \frac{1}{C}$$

and


$$m \leftrightarrow L$$

Time Dependence

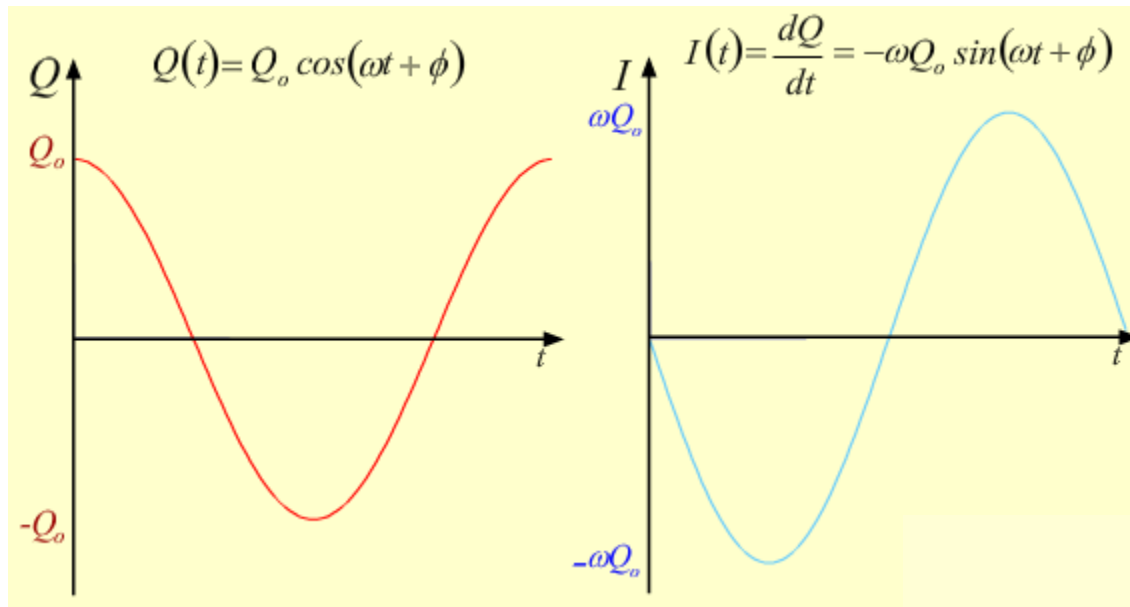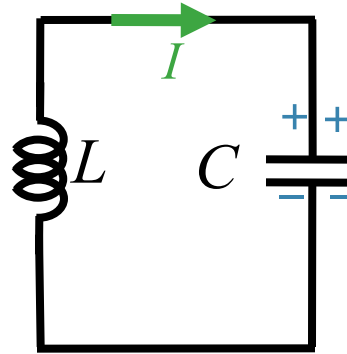

LC Circuits


click to play

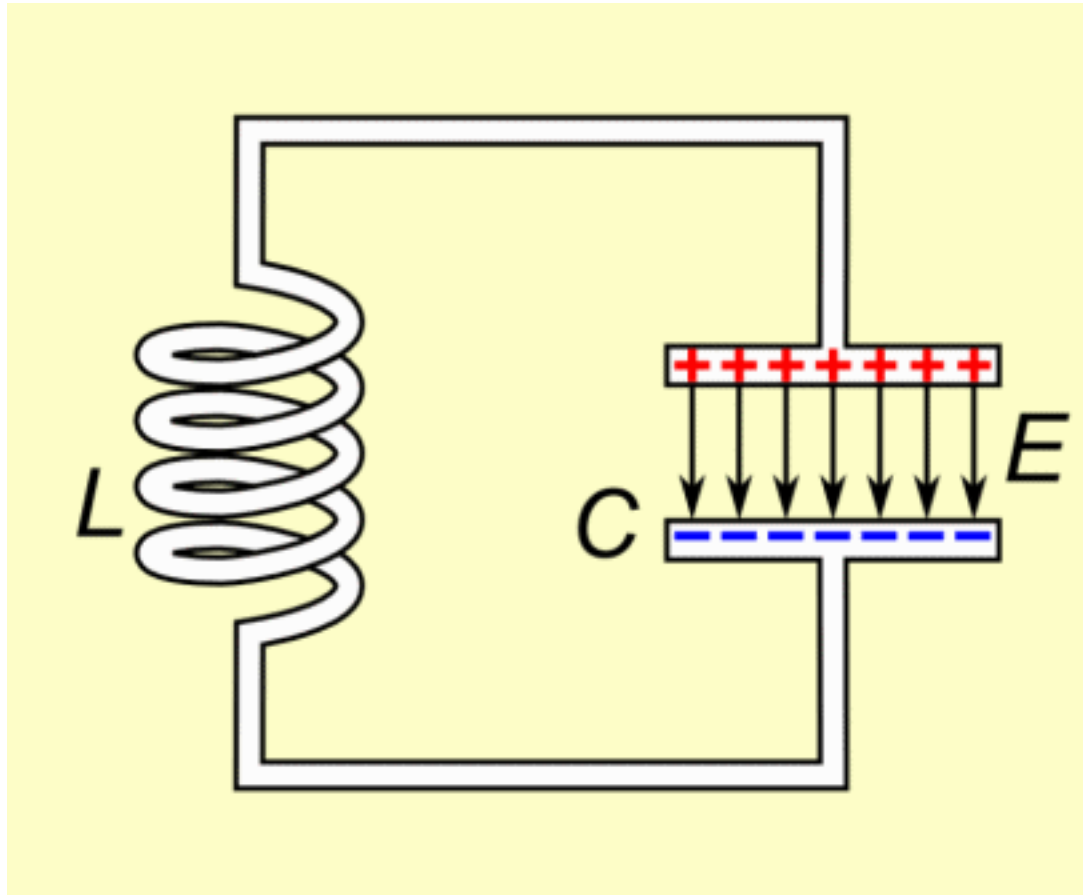

CheckPoint 2



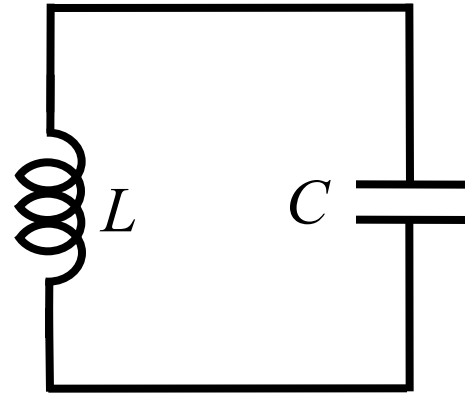At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.



What is the potential difference across the inductor at $t = 0$?

A) $V_L = 0$


B) $V_L = Q_{max}/C$

C) $V_L = Q_{max}/2C$

since $V_L = V_C$

The voltage across the capacitor is Q_{max}/C . Kirchhoff's Voltage Rule implies that must also be equal to the voltage across the inductor

LC Circuit: Question 1 (N = 50)

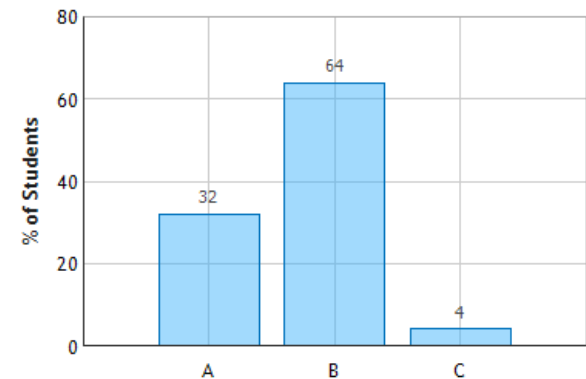


Pendulum.

CheckPoint 4



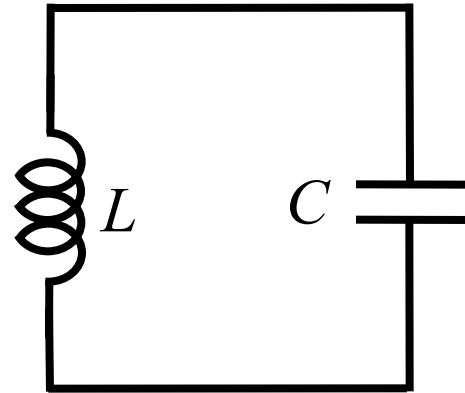At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.




What is the potential difference across the inductor when the current is maximum?

A) $V_L = 0$

B) $V_L = Q_{max}/C$

C) $V_L = Q_{max}/2C$

LC Circuit: Question 3 (N = 50)

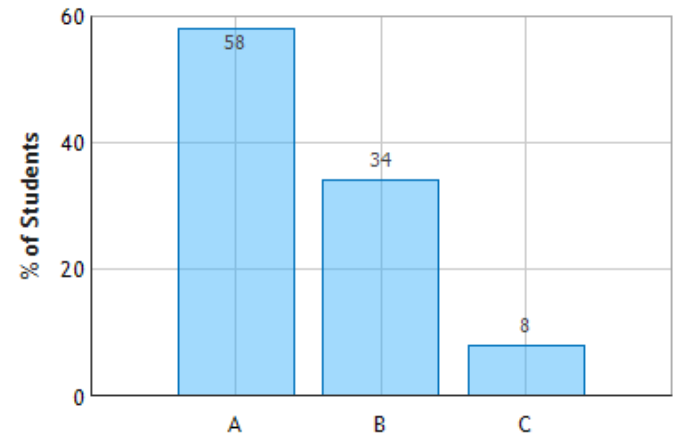


dI/dt is zero when current is maximum

CheckPoint 6



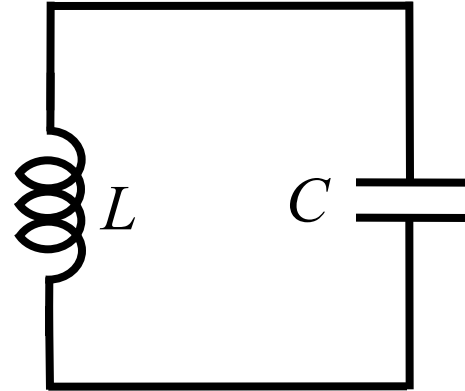At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.



How much energy is stored in the capacitor when the current is a maximum ?

A) $U = Q_{max}^2 / (2C)$

B) $U = Q_{max}^2 / (4C)$

C) $U = 0$


Total Energy is constant!

$$U_{Lmax} = \frac{1}{2} L I_{max}^2$$

$$U_{Cmax} = Q_{max}^2 / 2C$$

$I = max$ when $Q = 0$


LC Circuit: Question 5 (N = 50)

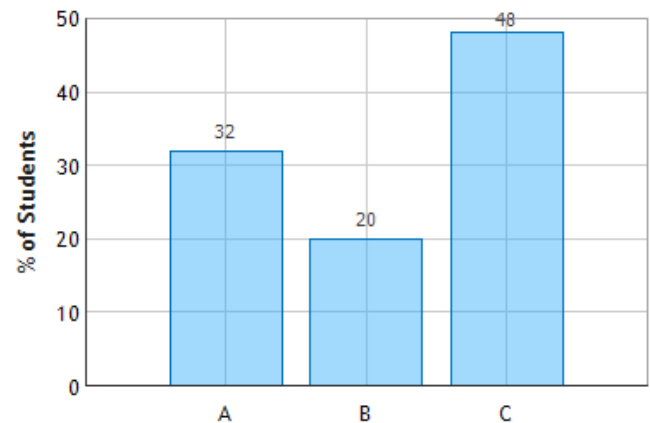

CheckPoint 8



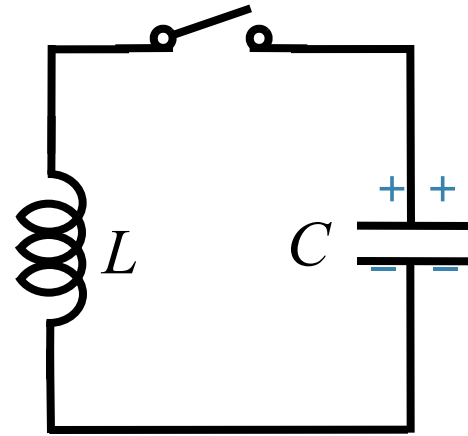The capacitor is charged such that the top plate has a charge $+Q_0$ and the bottom plate $-Q_0$. At time $t = 0$, the switch is closed and the circuit oscillates with frequency $\omega = 500$ radians/s.



$$L = 4 \times 10^{-3} \text{ H}$$
$$\omega = 500 \text{ rad/s}$$

What is the value of the capacitor C ?


A) $C = 1 \times 10^{-3} \text{ F}$

B) $C = 2 \times 10^{-3} \text{ F}$

C) $C = 4 \times 10^{-3} \text{ F}$

$$\omega = \frac{1}{\sqrt{LC}} \longrightarrow C = \frac{1}{\omega^2 L} = \frac{1}{(25 \times 10^4)(4 \times 10^{-3})} = 10^{-3} \text{ F}$$

LC Circuit 2: Question 1 (N = 50)

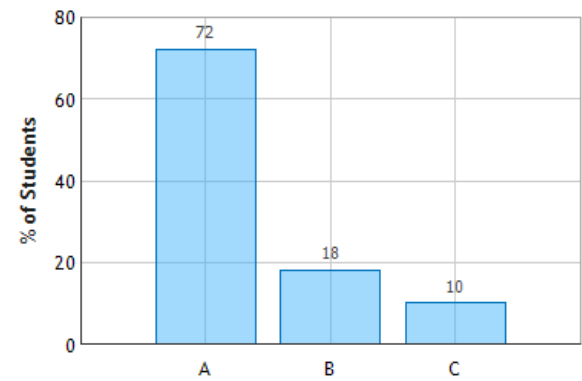


Prelecture



At $t = 0$ the capacitor is fully charged.

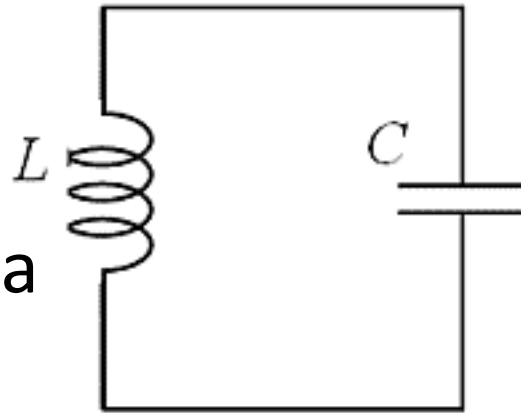Expressions for the charge and current as a function of time are shown to the right.



$$Q(t) = Q_{\max} \cos(\omega t)$$

$$I(t) = I_{\max} \sin(\omega t)$$

What is the current through the circuit, at the instant the charge on the capacitor is $Q_{\max}/2$?

A) $I < I_{\max}/2$







B) $I = I_{\max}/2$

C) $I > I_{\max}/2$

The total energy in the circuit is constant and is the sum of the energy in the capacitor (proportional to Q^2) and the energy in the inductor (proportional to I^2).

If $Q = Q_{\max}/2$ then only $1/4$ of the total energy is in the capacitor, so $3/4$ of the energy must be in the inductor, which means that $I = \sqrt{3/4} I_{\max}$, which is bigger than $I_{\max}/2$.

CheckPoint 10

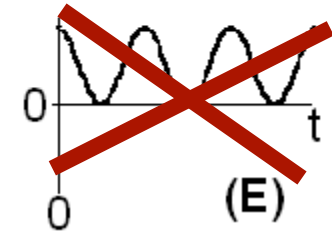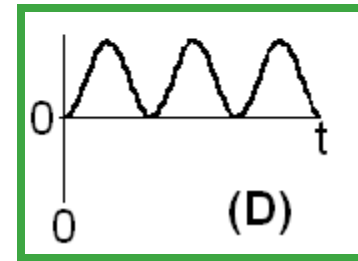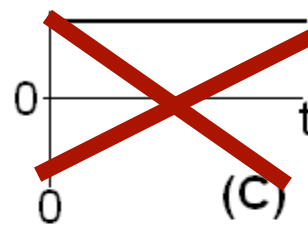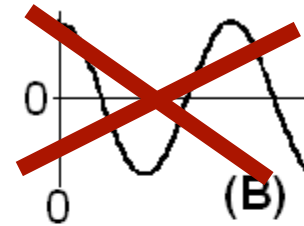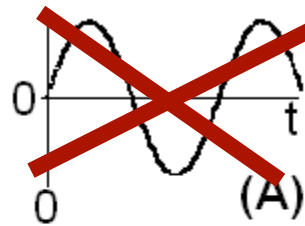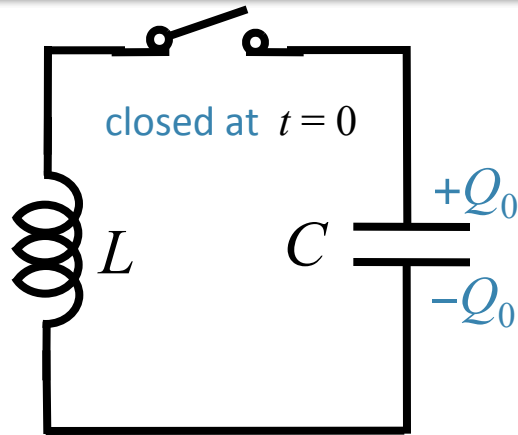


Which plot best represents the energy in the inductor as a function of time starting just after the switch is closed?

$$U_L = \frac{1}{2}LI^2$$

Energy proportional to $I^2 \Rightarrow$ cannot be negative

Current is changing $\Rightarrow U_L$ is not constant


Initial current is zero

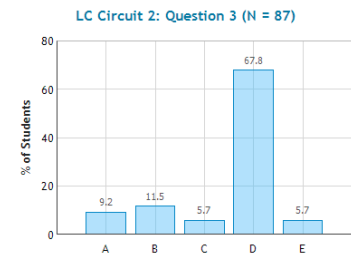


CheckPoint 12



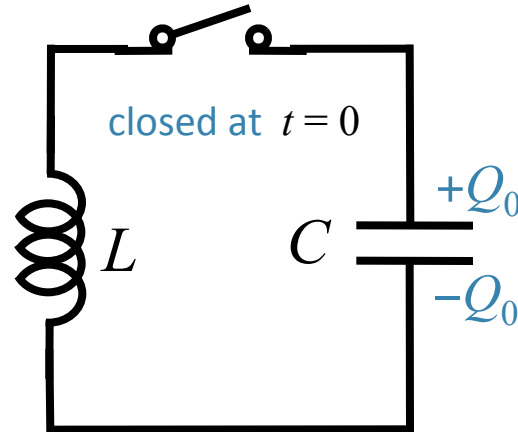When the energy stored in the capacitor reaches its maximum again for the **first time after $t = 0$** , how much charge is stored on the top plate of the capacitor?



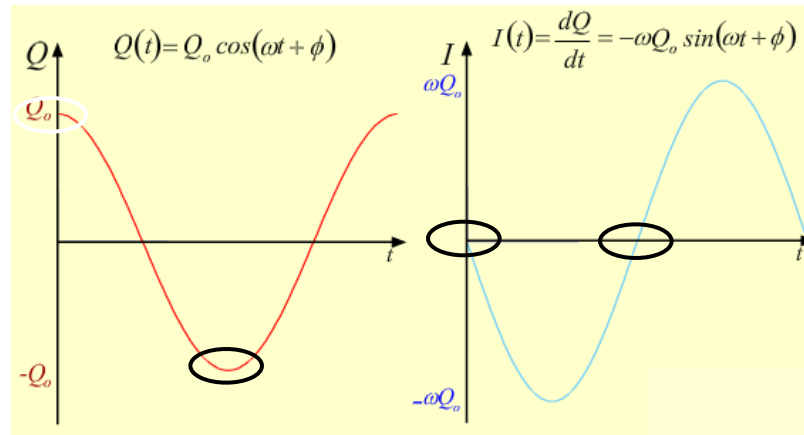- A) $+Q_0$
- B) $+Q_0/2$
- C) 0
- D) $-Q_0/2$
- E) $-Q_0$**




Q is maximum when current goes to zero

$$I = \frac{dQ}{dt}$$


Current goes to zero twice during one cycle

LC Circuit 2: Question 5 (N = 87)

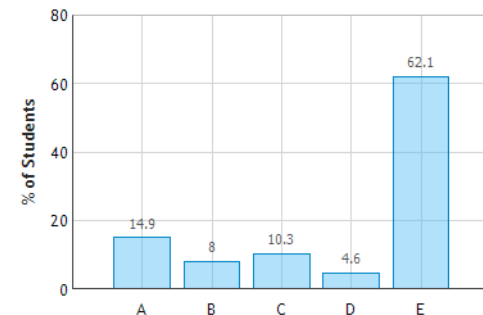

Add R: Damping

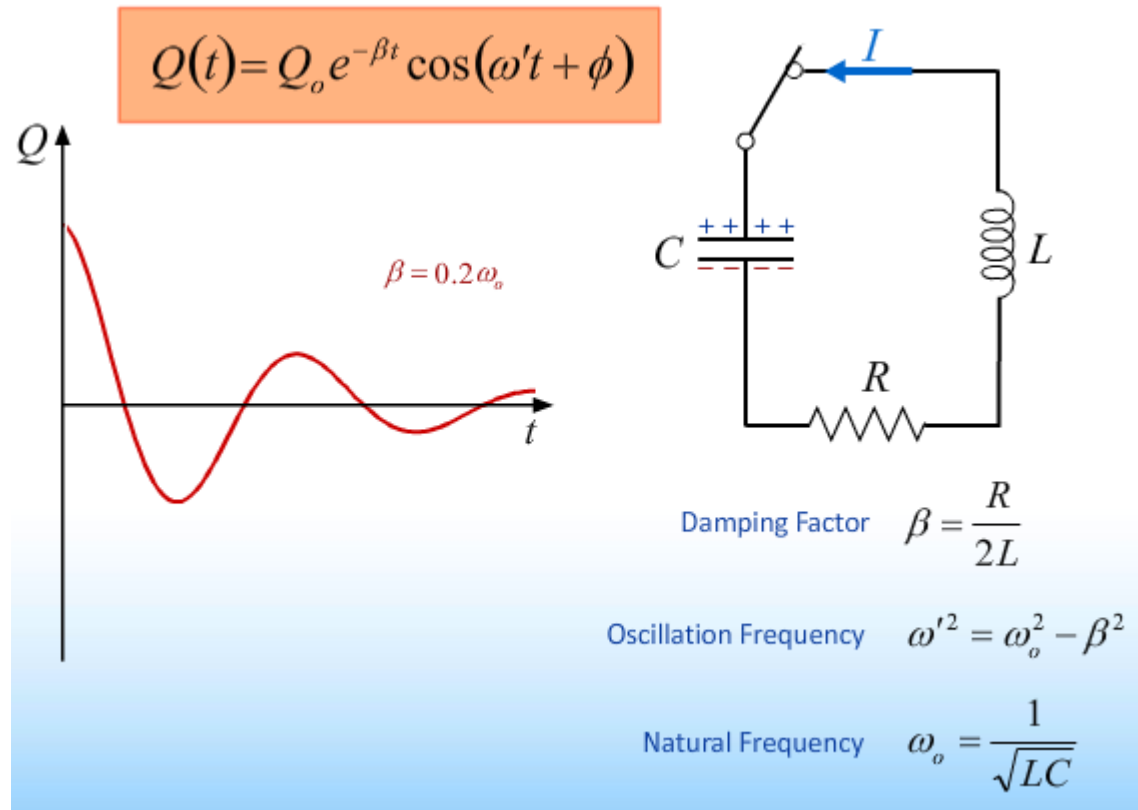Just like LC circuit but the oscillations get smaller because of R



Concept makes sense...

...but answer looks kind of complicated

Physics Truth #1:

Even though the answer sometimes looks complicated...


$$Q(t) = Q_o \cos(\omega t - \phi)$$

the physics under the hood is still very simple!

$$\frac{d^2 Q}{dt^2} = -\omega^2 Q$$

The elements of a circuit are very simple:

$$V_L = L \frac{dI}{dt}$$

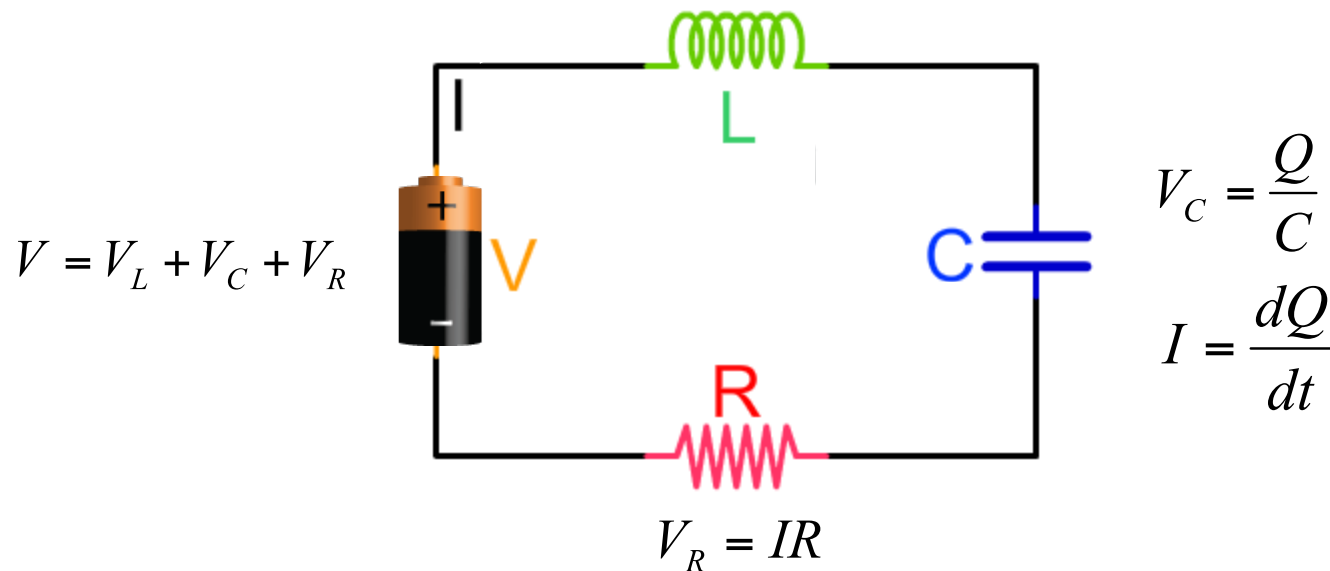


This is all we need to know to solve for anything!

A Different Approach

Start with some initial V , I , Q , V_L

Now take a tiny time step dt (1 ms)

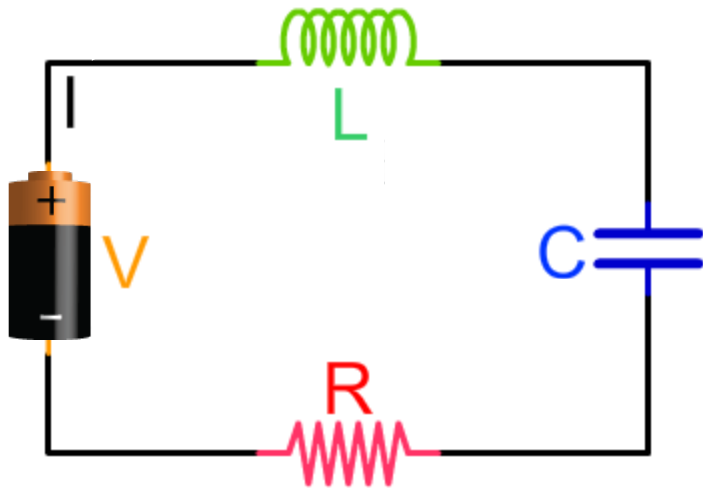

```
for (var t=0; t<tStepSec; t+=dt) {  
  I += Vind_last*dt/L;  
  Qcap += I*dt;  
  Vcap = Qcap/C;  
  Vres = I*R1;  
  Vind_last = Vind;  
  Vind = Va - Vres - Vcap;  
}
```

$$dI = \frac{V_L}{L} dt$$


$$dQ = Idt$$

$$V_C = \frac{Q}{C}$$

$$V_R = IR$$

$$V_L = V - V_R - V_C$$


Repeat...

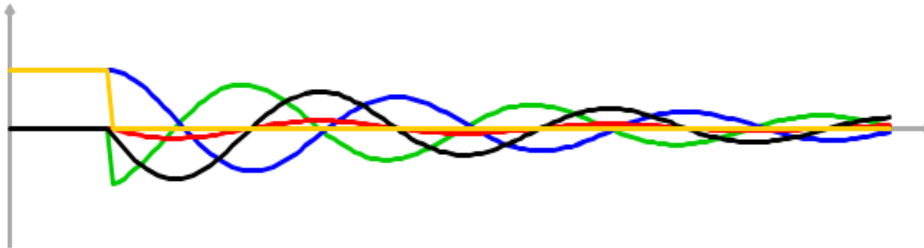

Calculation

The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

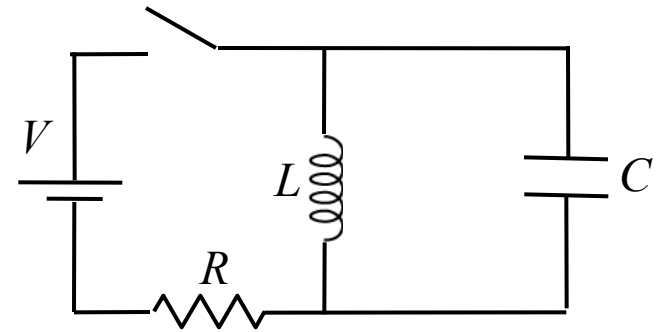What is Q_{MAX} , the maximum charge on the capacitor?



Conceptual Analysis


Once switch is opened, we have an LC circuit
Current will oscillate with natural frequency ω_0

Strategic Analysis

Determine initial current
Determine oscillation frequency ω_0
Find maximum charge on capacitor

Calculation

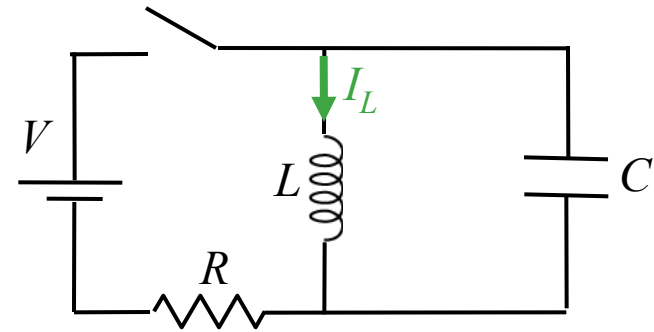The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is I_L , the current in the inductor, immediately **after** the switch is opened? Take positive direction as shown.

A) $I_L < 0$

B) $I_L = 0$

C) $I_L > 0$

Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened


before switch is opened:

all current goes through inductor in direction shown

Calculation



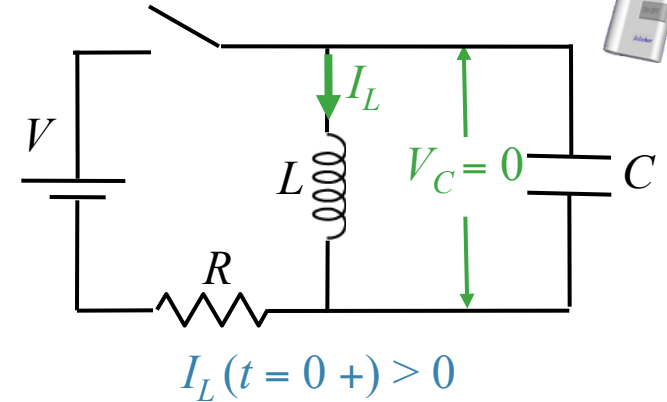The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



The energy stored in the capacitor immediately after the switch is opened is zero.

A) TRUE

B) FALSE

before switch is opened:

$$dI_L/dt \sim 0 \Rightarrow V_L = 0$$

BUT: $V_L = V_C$

since they are in parallel

$$\longrightarrow V_C = 0$$

after switch is opened:

V_C cannot change abruptly

$$\longrightarrow V_C = 0$$

$$\longrightarrow U_C = \frac{1}{2} CV_C^2 = 0 !$$


IMPORTANT: NOTE DIFFERENT CONSTRAINTS AFTER SWITCH OPENED

CURRENT through INDUCTOR cannot change abruptly

VOLTAGE across CAPACITOR cannot change abruptly

Calculation

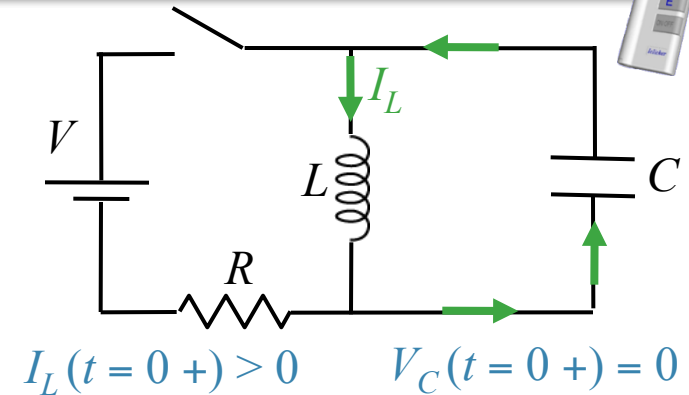The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is the direction of the current immediately after the switch is opened?

A) clockwise

B) counterclockwise

Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened


Before switch is opened: Current moves down through L

After switch is opened: Current continues to move down through L

Calculation



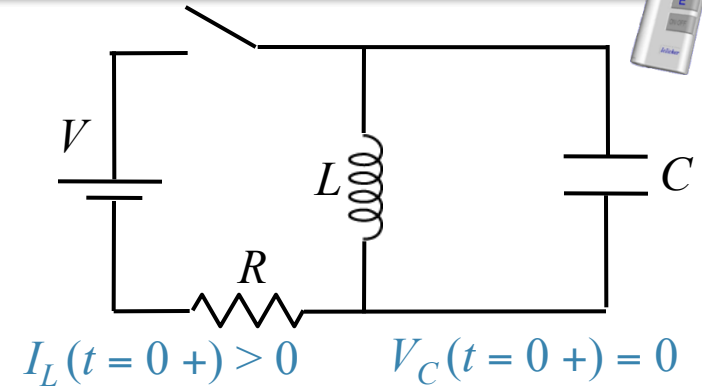The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is the magnitude of the current right after the switch is opened?

A) $I_o = V \sqrt{\frac{C}{L}}$


B) $I_o = \frac{V}{R^2} \sqrt{\frac{L}{C}}$

C) $I_o = \frac{V}{R}$

D) $I_o = \frac{V}{2R}$

Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened

Before switch is opened:

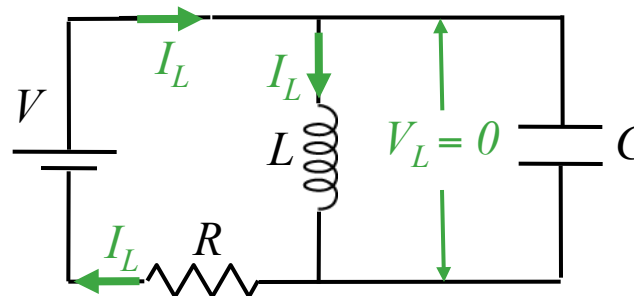


$$V_L = 0$$
$$\downarrow$$
$$V = I_L R$$

Calculation



The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

Hint: Energy is conserved

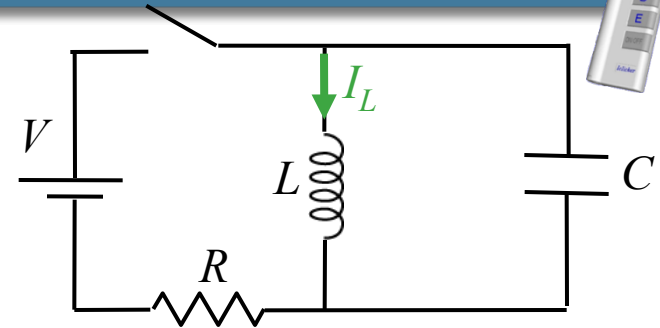

$$I_L(t = 0+) = V/R \quad V_C(t = 0+) = 0$$


What is Q_{\max} , the maximum charge on the capacitor during the oscillations?

A) $Q_{\max} = \frac{V}{R} \sqrt{LC}$

B) $Q_{\max} = \frac{1}{2} CV$


C) $Q_{\max} = CV$

D) $Q_{\max} = \frac{V}{R \sqrt{LC}}$

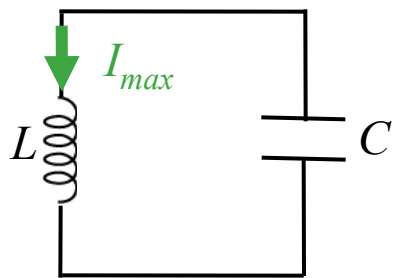

When I is *max*
(and Q is 0)

$$U = \frac{1}{2} LI^2$$

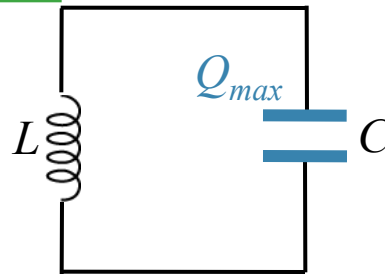

When Q is *max*
(and I is 0)

$$U = \frac{1}{2} \frac{Q_{\max}^2}{C}$$



$$\frac{1}{2} LI^2 = \frac{1}{2} \frac{Q_{\max}^2}{C}$$


$$Q_{\max} = I_{\max} \sqrt{LC} = \frac{V}{R} \sqrt{LC}$$

Follow-Up



The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

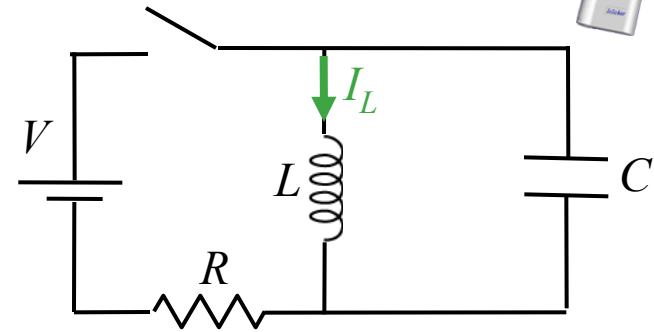Is it possible for the maximum voltage on the capacitor to be greater than V ?



A) YES

B) NO

$$I_{\max} = V/R$$

$$Q_{\max} = \frac{V}{R} \sqrt{LC}$$


$$Q_{\max} = \frac{V}{R} \sqrt{LC} \rightarrow V_{\max} = \frac{V}{R} \sqrt{\frac{L}{C}} \rightarrow V_{\max} \text{ can be greater than } V \text{ IF: } \sqrt{\frac{L}{C}} > R$$

We can rewrite this condition in terms of the resonant frequency:

$$\omega_0 L > R \quad \text{OR} \quad \frac{1}{\omega_0 C} > R$$

We will see these forms again when we study AC circuits!


FlipItPhysics Problem

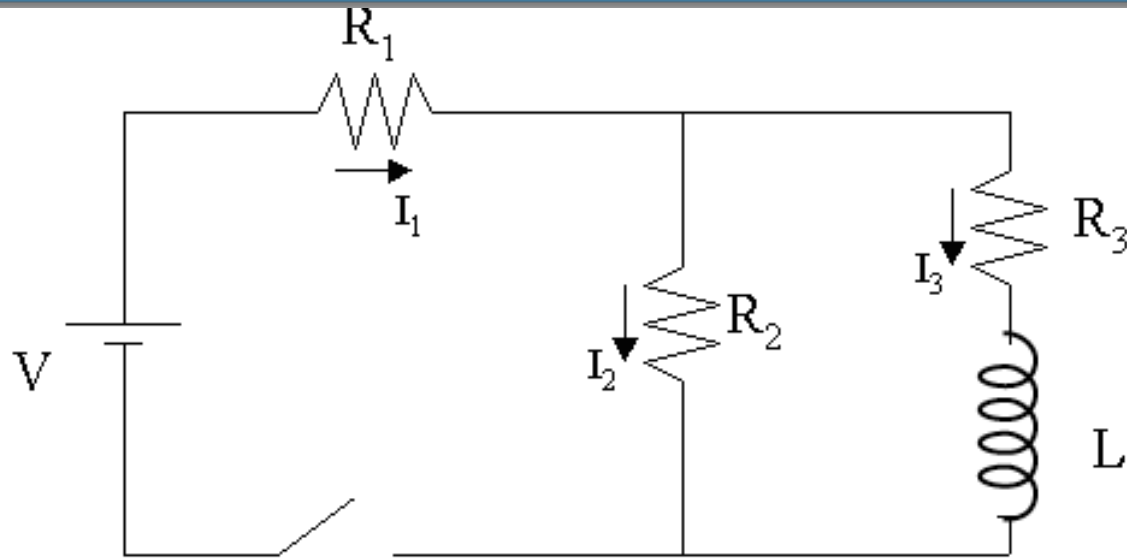

At what time, does the current through the inductor I_3 reach a value that is 63% of its maximum value?

Apply Kirchhoff's rules to (1) outer loop, (2) inner loop and (3) the junction.

FlipItPhysics Problem

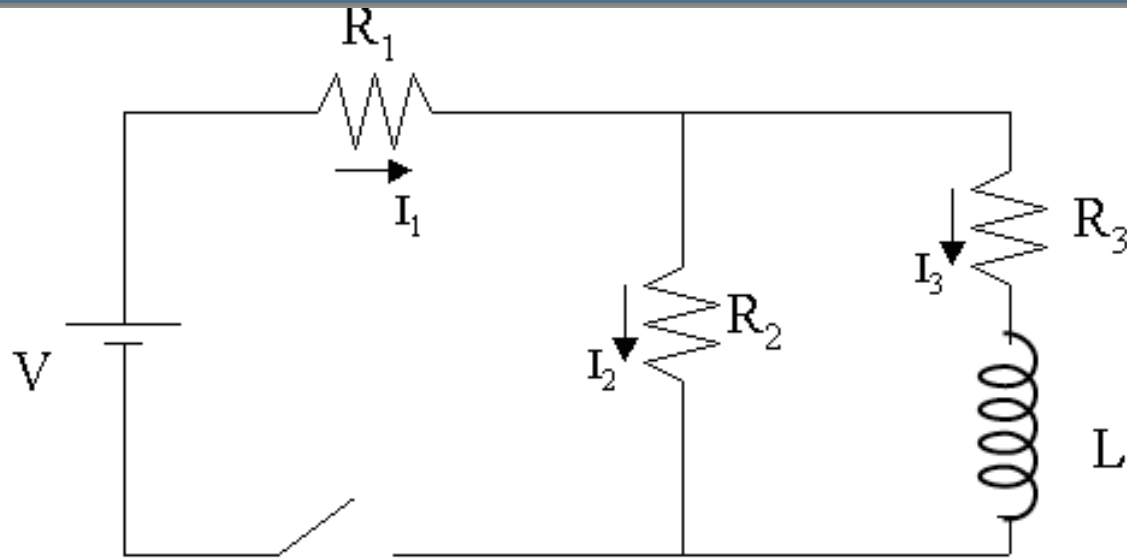

$$(1) V - I_1 R_1 - I_3 R_3 - L \frac{dI_3}{dt} = 0$$

$$(2) -I_3 R_3 - L \frac{dI_3}{dt} + I_2 R_2 = 0$$

$$(3) I_1 = I_2 + I_3$$

Eliminate I_1 and I_2 and find the equation for I_3 of the form

$$V - AI_3 - B \frac{dI_3}{dt} = 0$$

$$\tau = \frac{B}{A}$$