

Electricity & Magnetism

Lecture 8: Capacitors

Today's Concept:

Capacitors

(Capacitors in a circuits, Dielectrics, Energy in capacitors)

Stuff you asked about:

- “Capacitance: parallel and series” -- “Can we go over more on series vs parallel capacitor circuits?”
- “the formula for calculating capacitance in parallel and series are the opposite of the formula for resistance “
- “Please go over the Capacitors with and without a dielectric from checkpoint.”
- “this stuff is alot harder than what weve been doing before, one thing i dont understand is when you disconnect a battery from a capacitor what exactly happens, how come it still has a charge?? ”
- “I am very confused about the dielectric “

Capacitors, connected and unconnected


- ⑩ A capacitor that is unconnected to a battery has constant charge: $V = Q/C$ (V is determined by Q)
- ⑩ Capacitors in parallel have the same voltage. Charge may redistribute among them: $Q_1/C_1 = Q_2/C_2 = Q_2/C_2 \dots$
- ⑩ A capacitor connected to a battery has a constant voltage. $Q = CV$ (Q is determined by V)

Dielectric

- ⑩ Charged capacitor, not connected to battery
- ⑩ Dielectric makes ΔV smaller

air capacitor

$$\kappa = 1$$

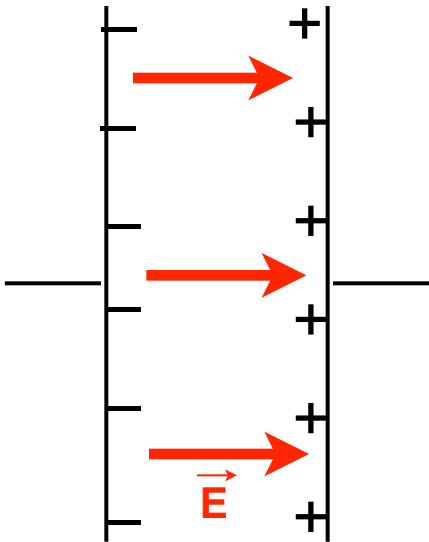


Dielectric

- ⑩ Charged capacitor, not connected to battery
- ⑩ Dielectric makes ΔV smaller

air capacitor

$$\kappa = 1$$

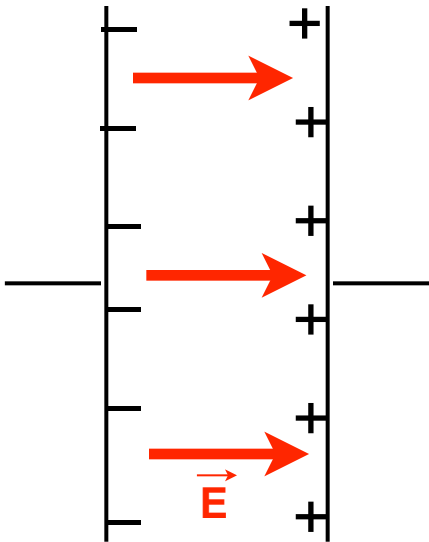


dielectric capacitor

Dielectric

- ⑩ Charged capacitor, not connected to battery
- ⑩ Dielectric makes ΔV smaller

air capacitor

$$\kappa = 1$$

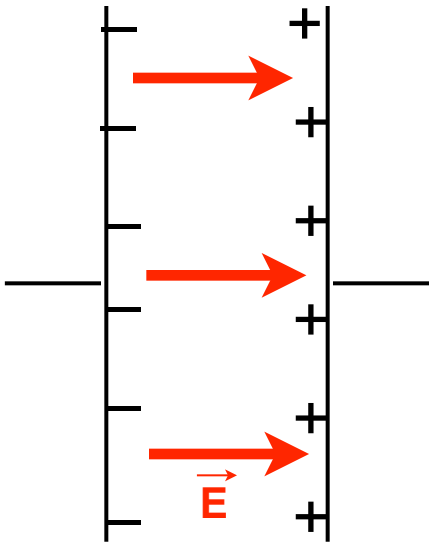

dielectric capacitor


$$\kappa > 1$$

Dielectric

- ⑩ Charged capacitor, not connected to battery
- ⑩ Dielectric makes ΔV smaller


air capacitor

$$\kappa = 1$$

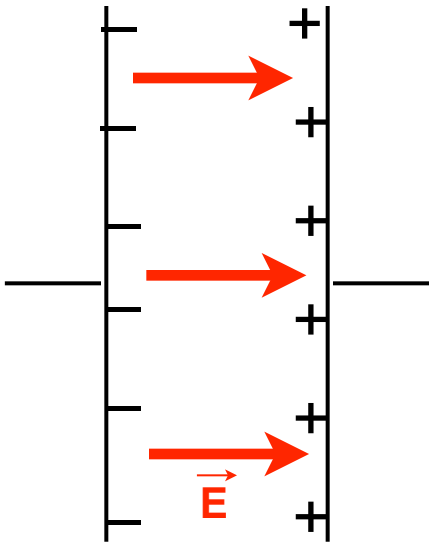

dielectric capacitor

$$\kappa > 1$$

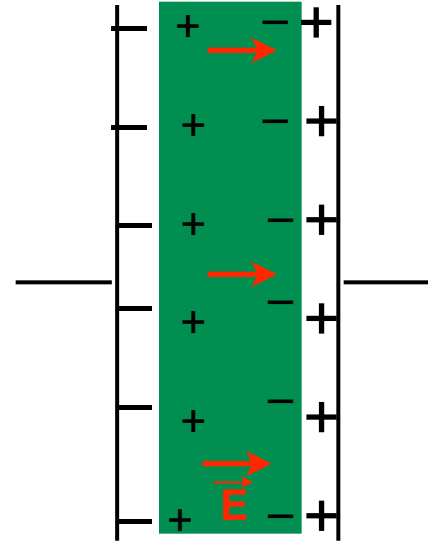


Dielectric

- ⑩ Charged capacitor, not connected to battery
- ⑩ Dielectric makes ΔV smaller


air capacitor

$$\kappa = 1$$

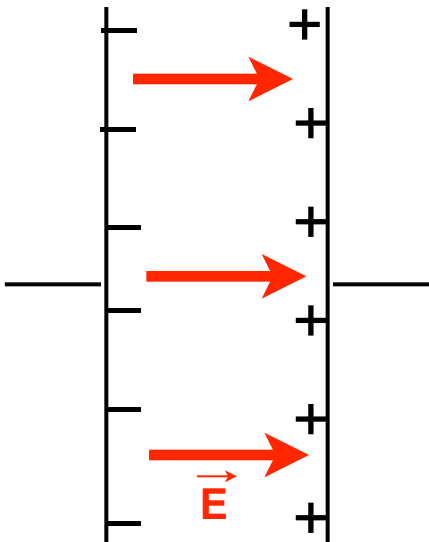

dielectric capacitor

$$\kappa > 1$$

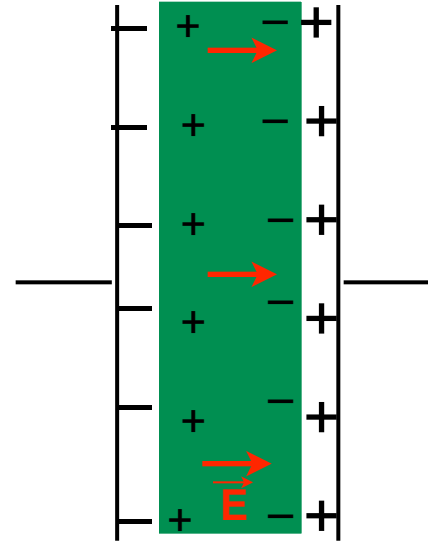


E inside dielectric is smaller than E outside.
The charge on the surface of the dielectric partially cancels the E field from the charge on the plates.
Therefore the ΔV between the plates is less.

Dielectric

- ⑩ Charged capacitor, not connected to battery
- ⑩ Dielectric makes ΔV smaller

air capacitor


$$\kappa = 1$$

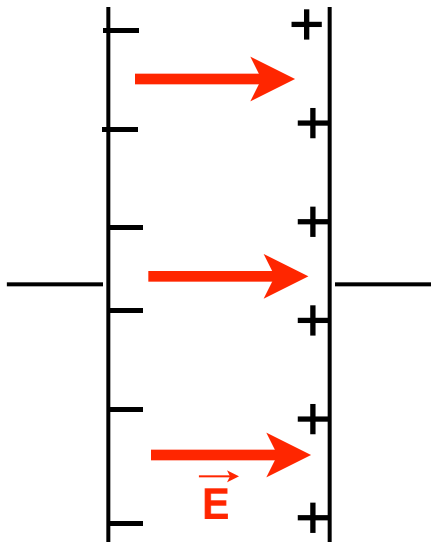

$$C = \epsilon_0 A/L$$

dielectric capacitor

$$\kappa > 1$$

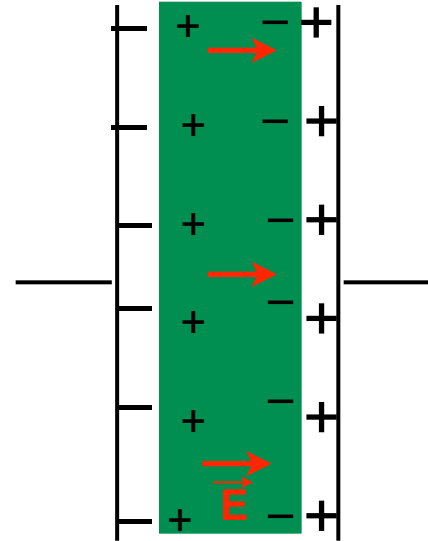


E inside dielectric is smaller than E outside.
The charge on the surface of the dielectric partially cancels the E field from the charge on the plates.
Therefore the ΔV between the plates is less.

Dielectric

- ⑩ Charged capacitor, not connected to battery
- ⑩ Dielectric makes ΔV smaller

air capacitor


$$\kappa = 1$$

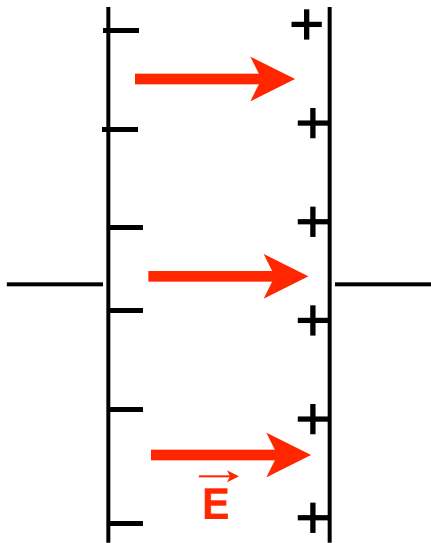

$$C = \epsilon_0 A/L$$

dielectric capacitor


$$\kappa > 1$$

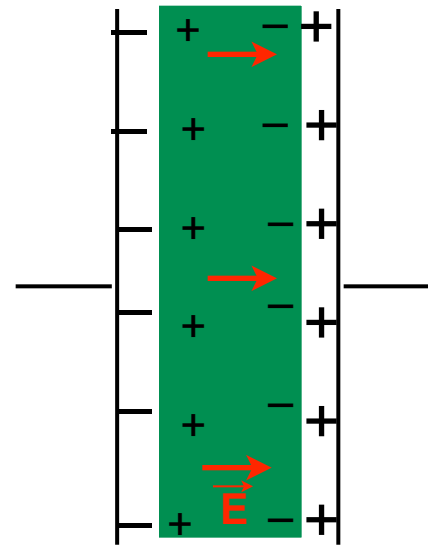


$$C = \kappa \epsilon_0 A/L$$

E inside dielectric is smaller than E outside.
The charge on the surface of the dielectric partially cancels the E field from the charge on the plates.
Therefore the ΔV between the plates is less.


Simple Capacitor Circuit

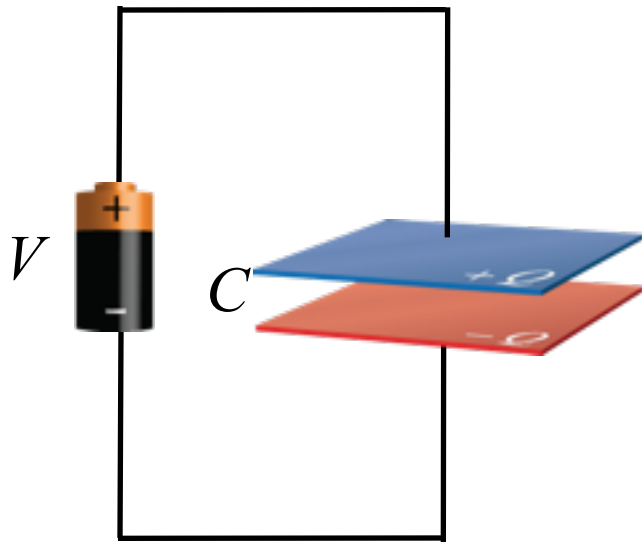


Simple Capacitor Circuit

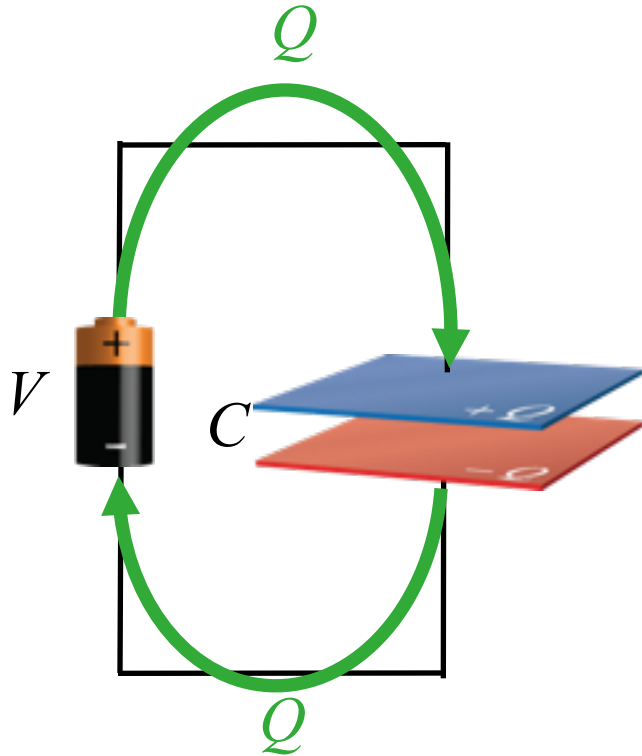

Simple Capacitor Circuit

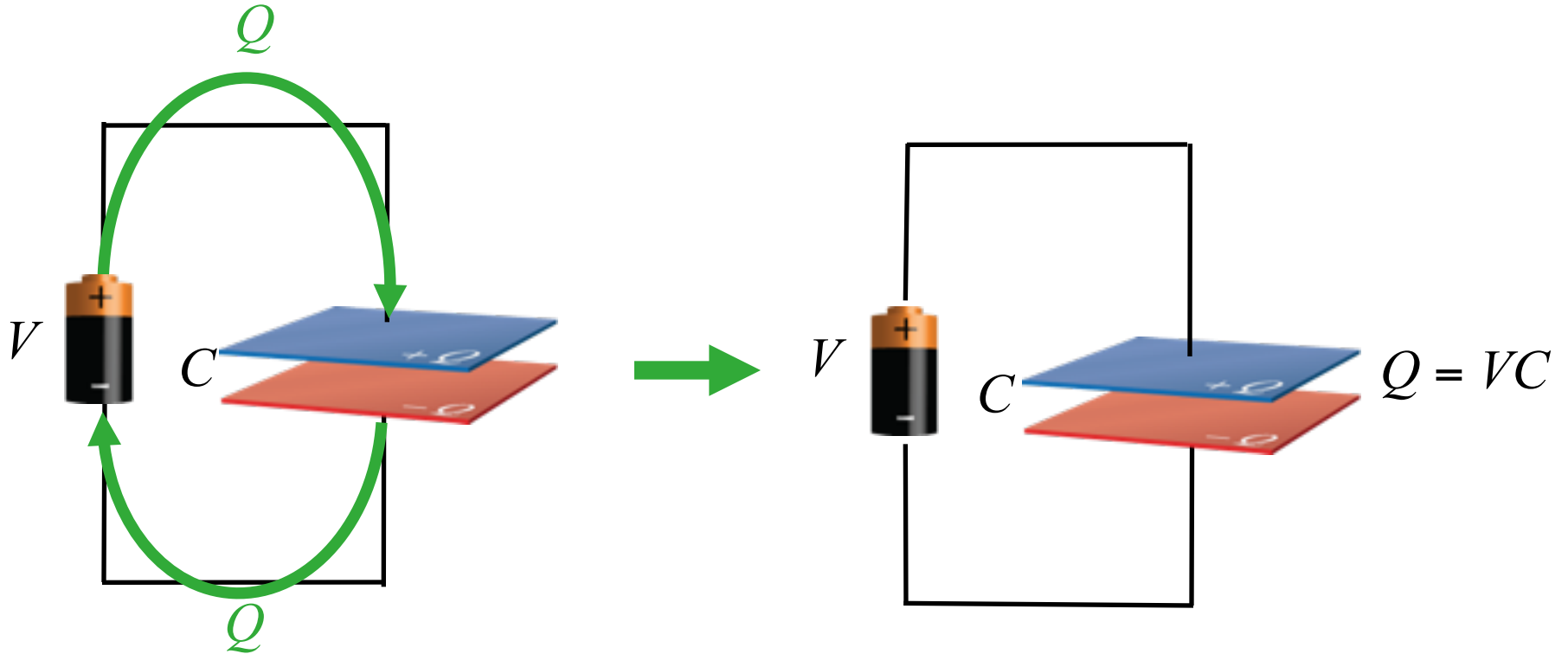


Simple Capacitor Circuit

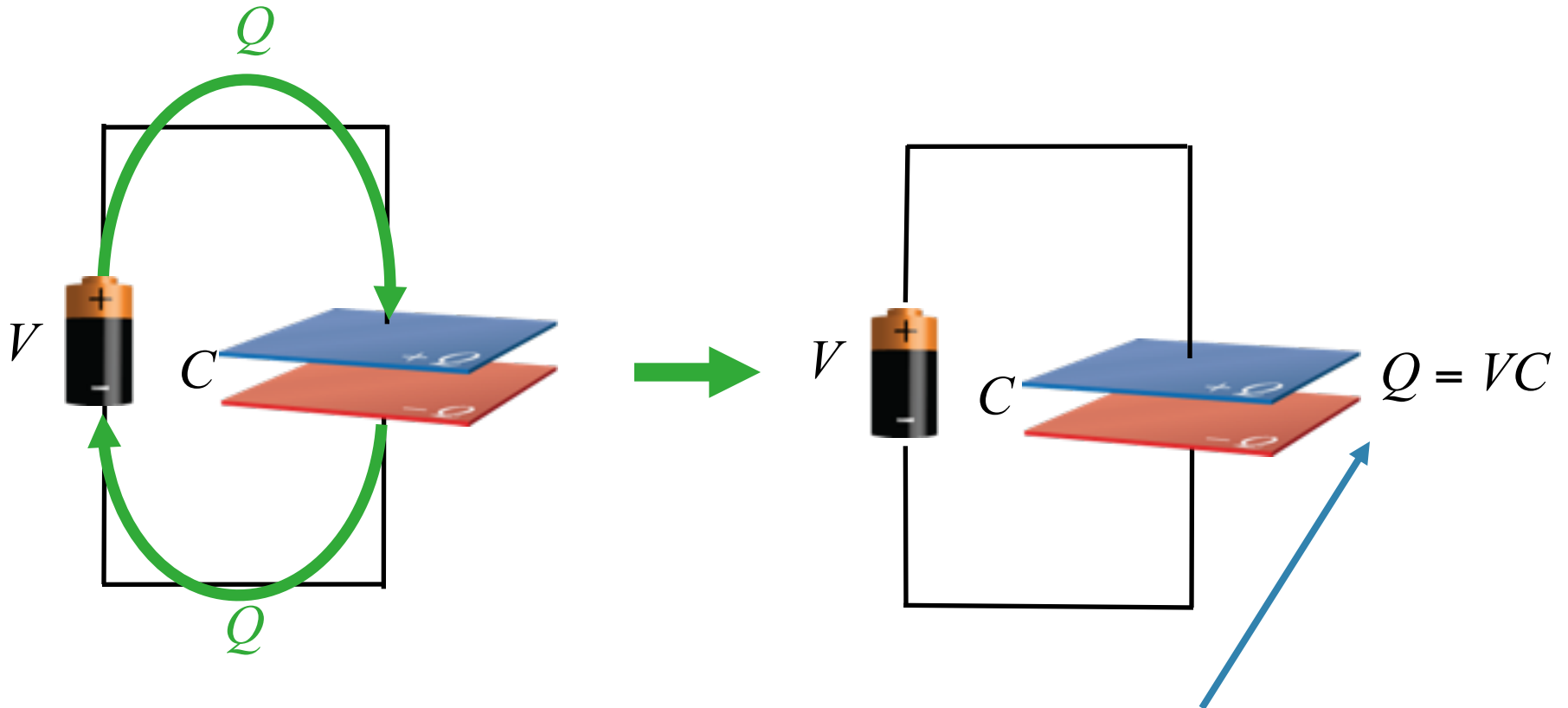


This “ Q ” really means that the battery has moved charge Q from one plate to the other, so that one plate holds $+Q$ and the other $-Q$.


Dielectrics

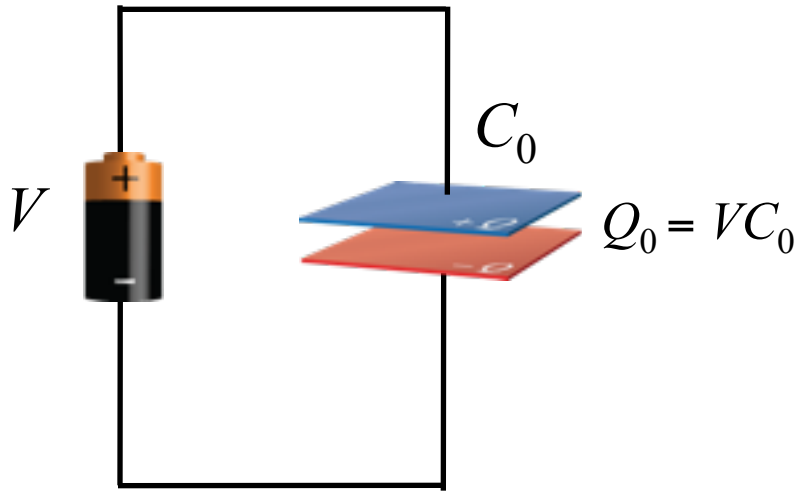

Dielectrics

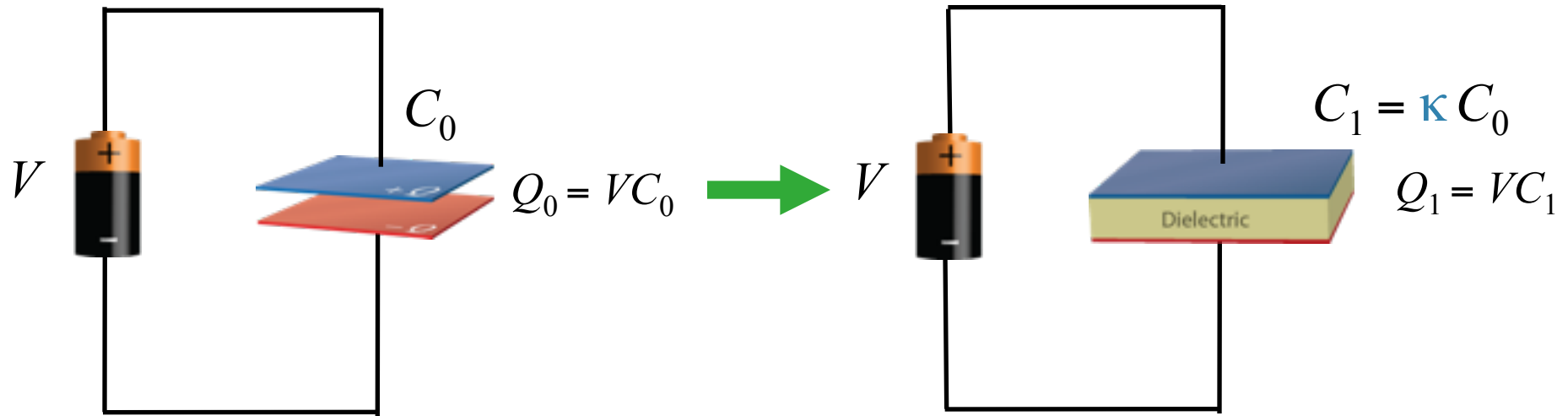


Dielectrics

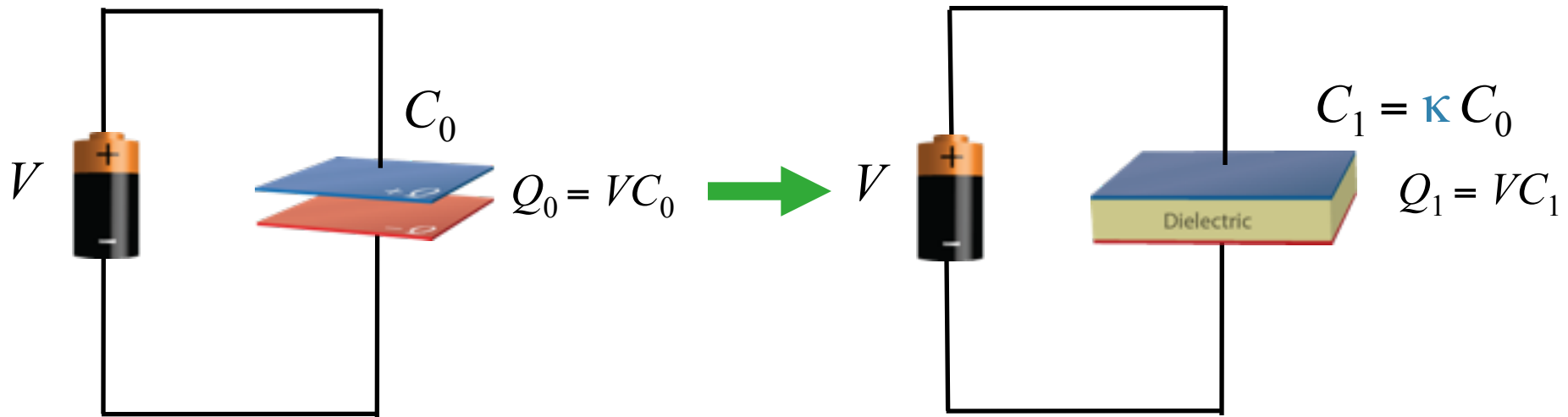


By adding a dielectric you are just making a new capacitor with larger capacitance (factor of κ)


Parallel Capacitor Circuit

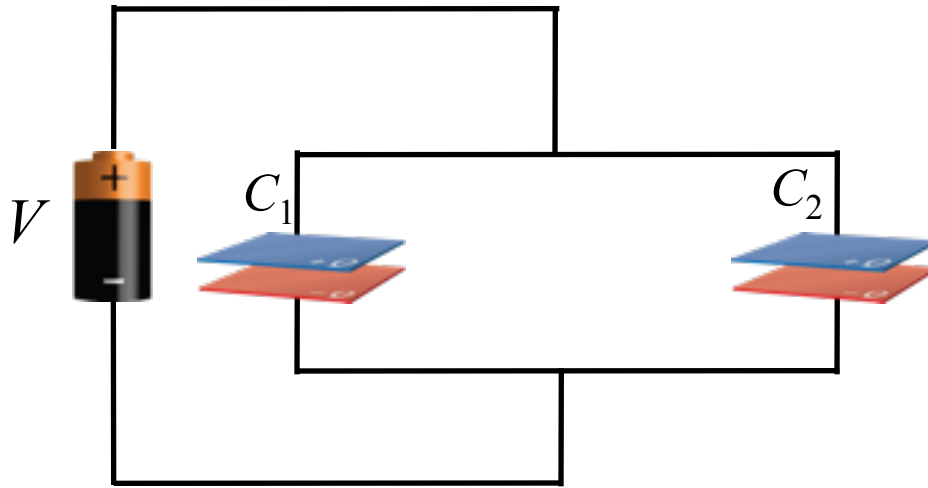


Parallel Capacitor Circuit

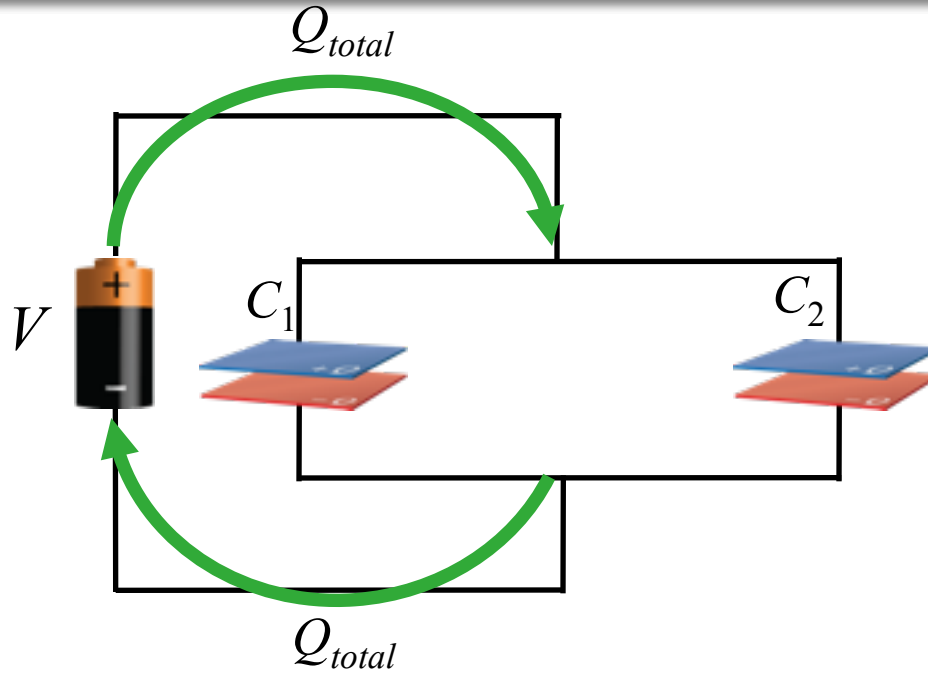

Parallel Capacitor Circuit

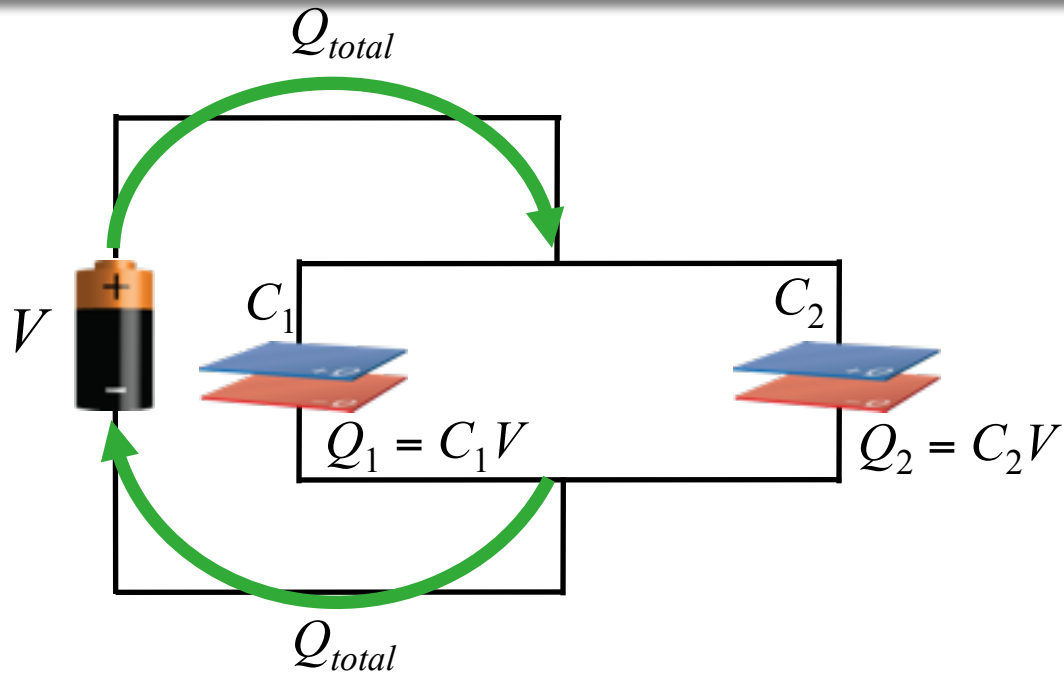


Parallel Capacitor Circuit

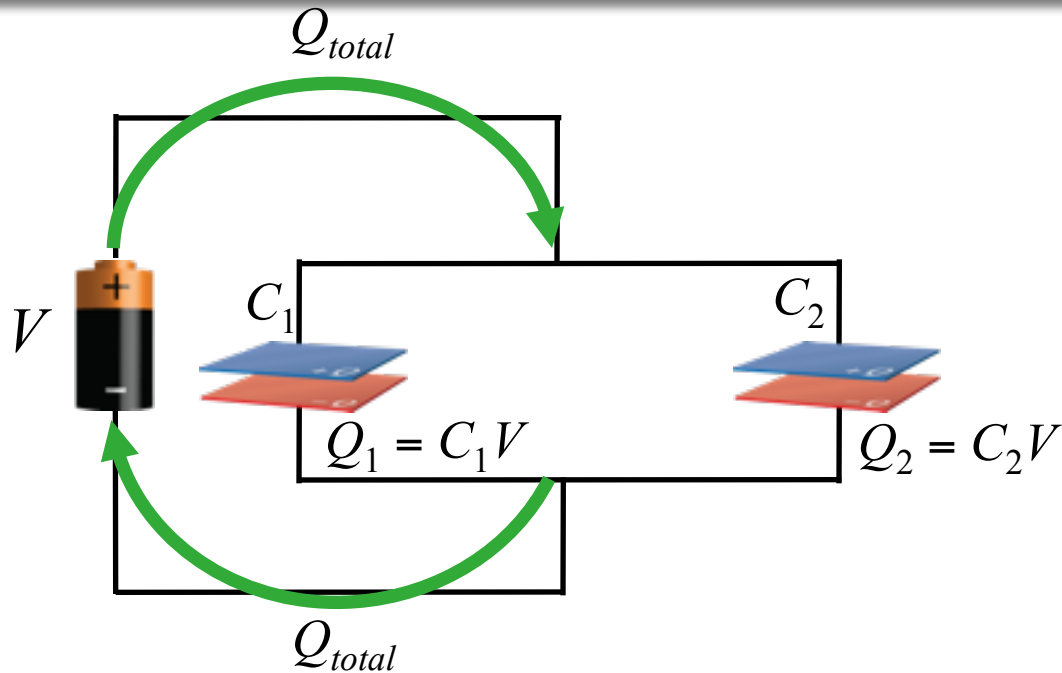

Key point: V is the same for both capacitors


Parallel Capacitor Circuit

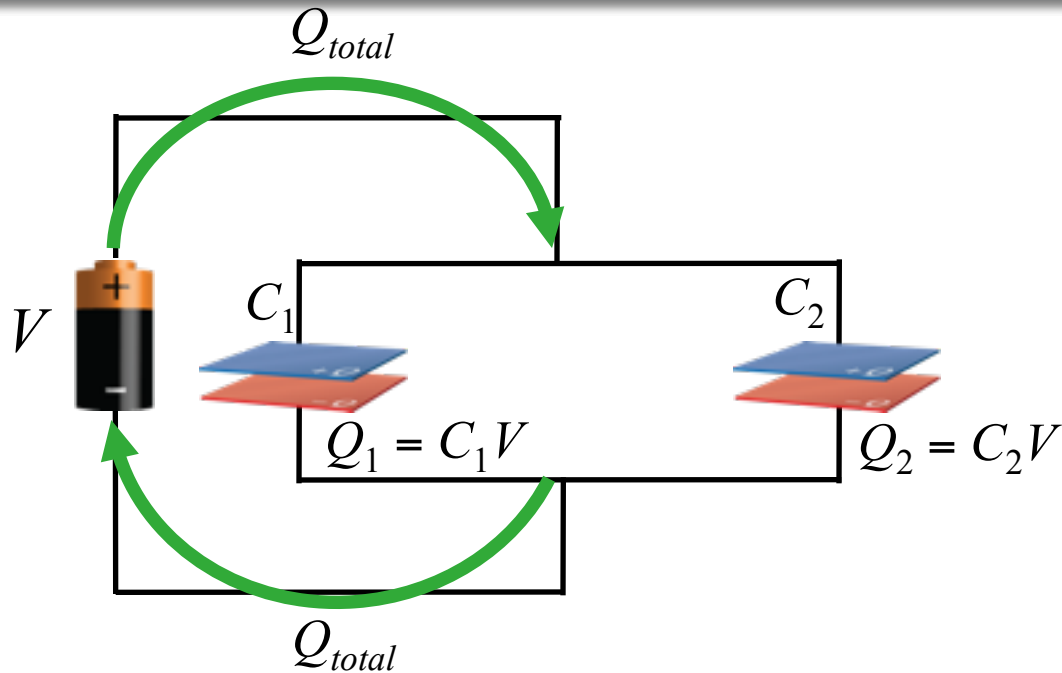

Key point: V is the same for both capacitors

Key Point: $Q_{total} = Q_1 + Q_2 = VC_1 + VC_2 = V(C_1 + C_2)$

Parallel Capacitor Circuit

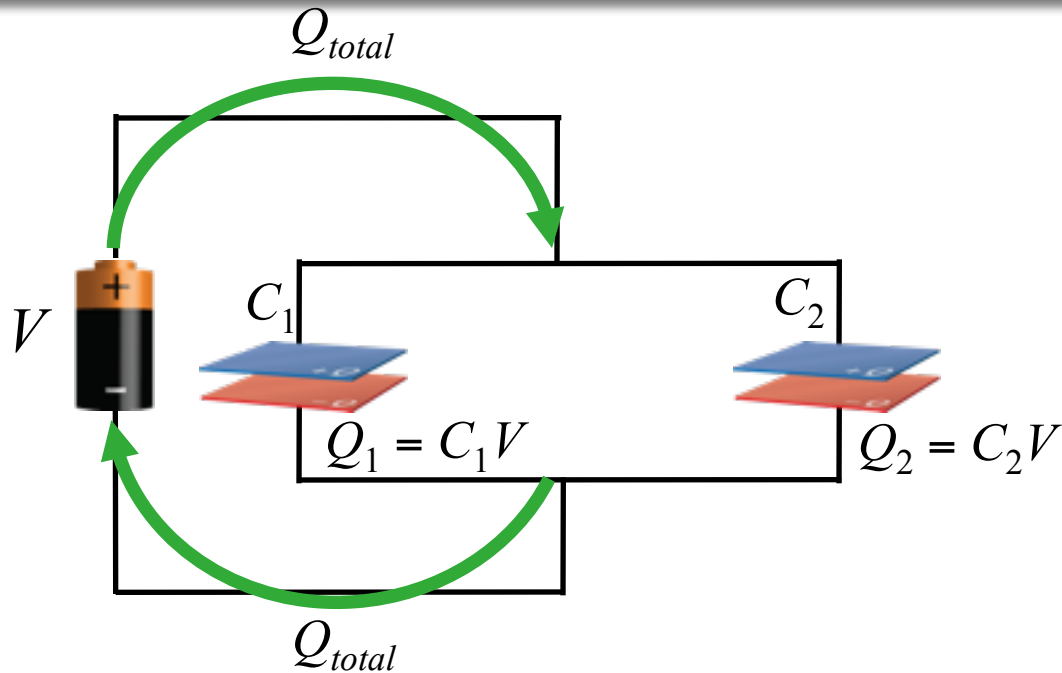


Key point: V is the same for both capacitors


Key Point: $Q_{total} = Q_1 + Q_2 = VC_1 + VC_2 = V(C_1 + C_2)$

$$C_{total} = C_1 + C_2$$


Series Capacitor Circuit

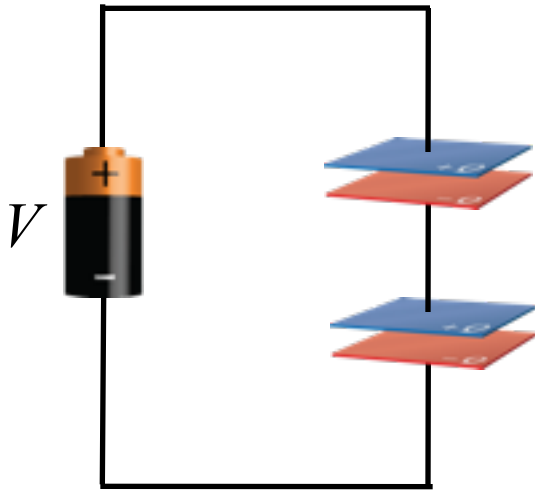


Series Capacitor Circuit

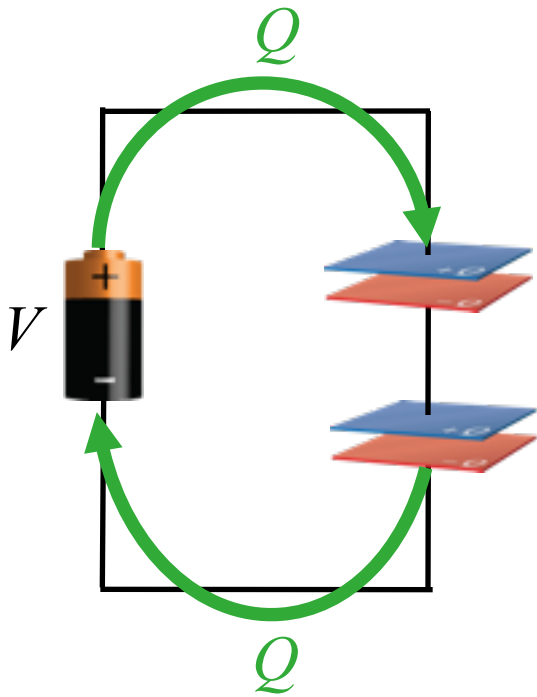


Series Capacitor Circuit

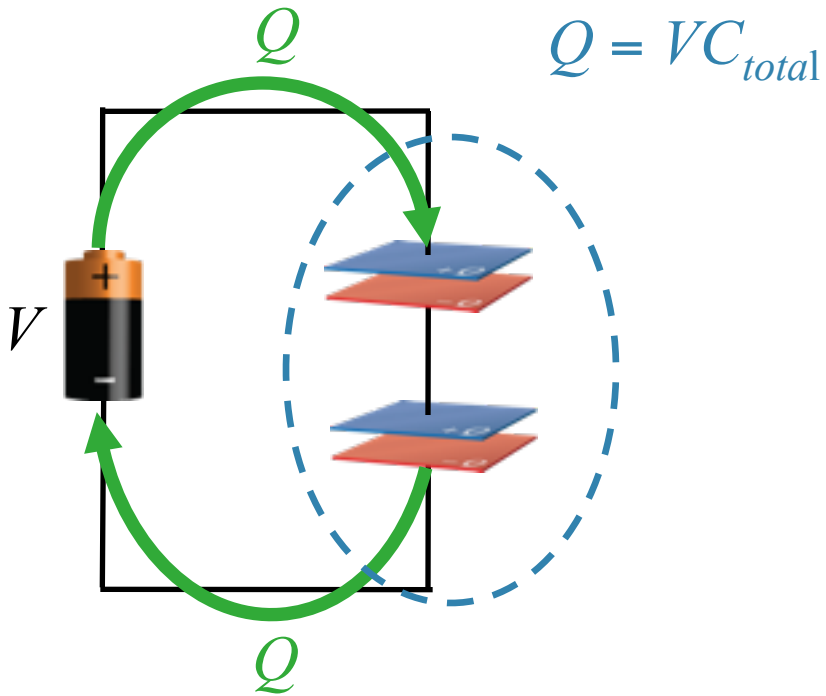


Series Capacitor Circuit

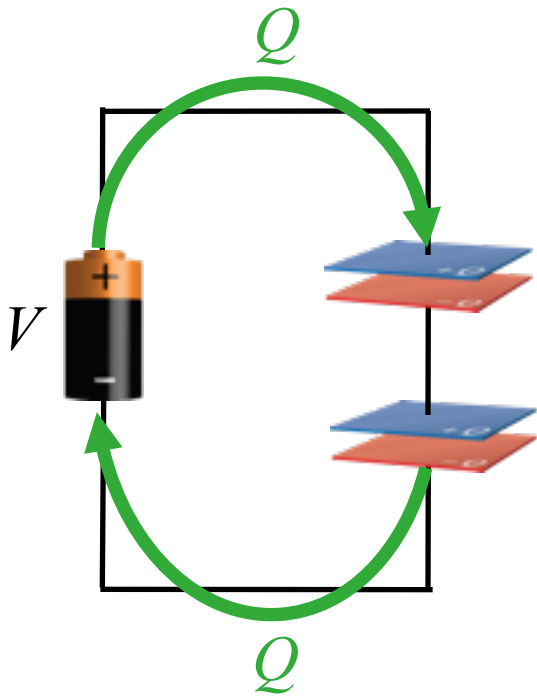


Series Capacitor Circuit

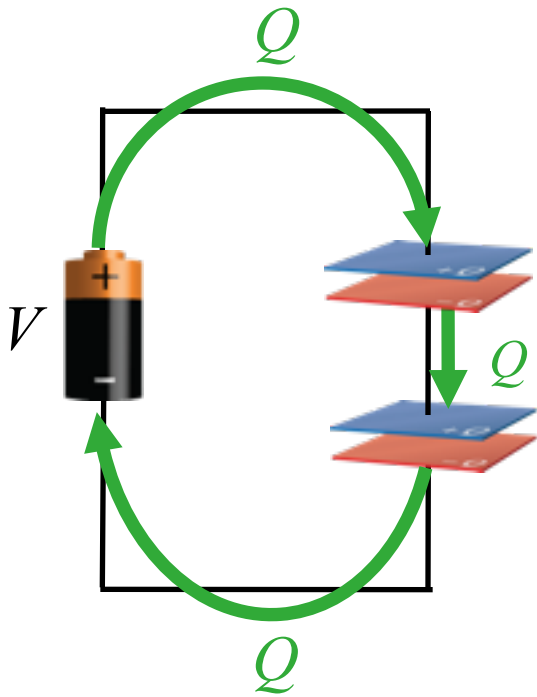

Series Capacitor Circuit

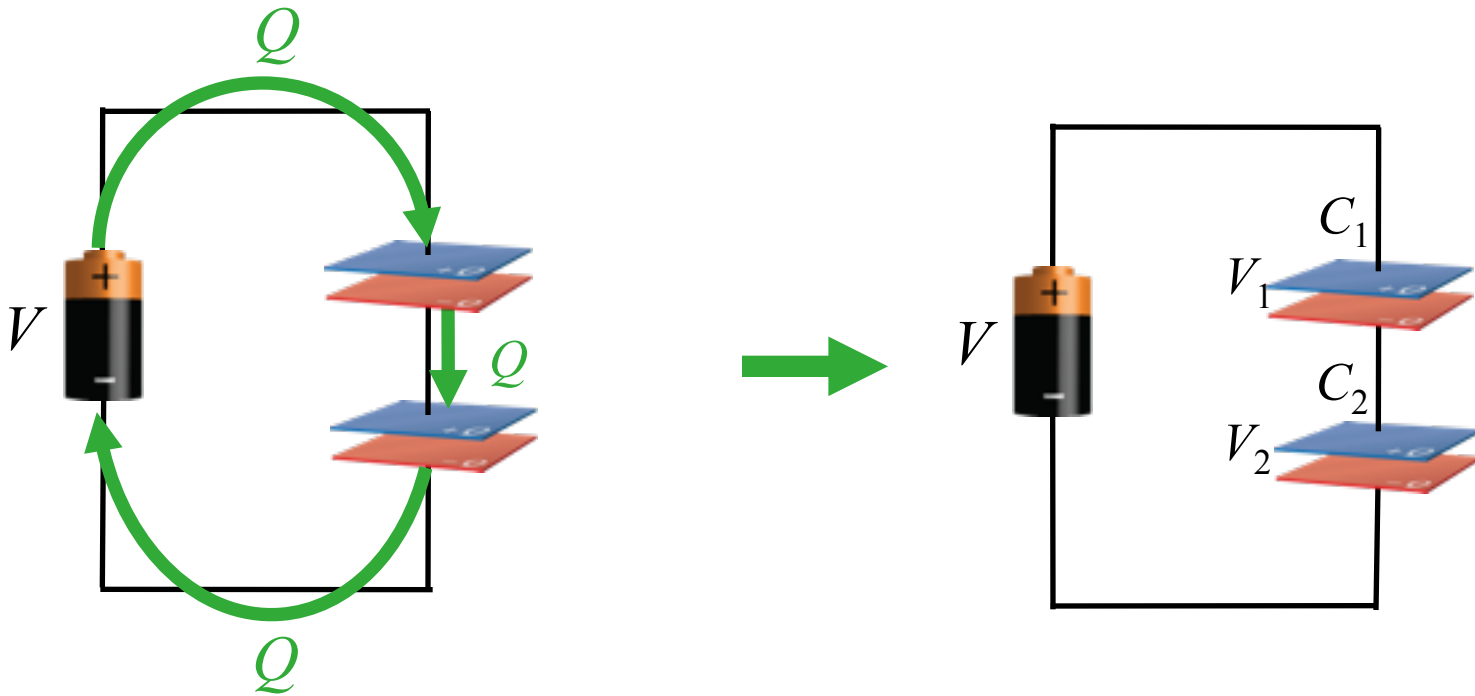


Series Capacitor Circuit

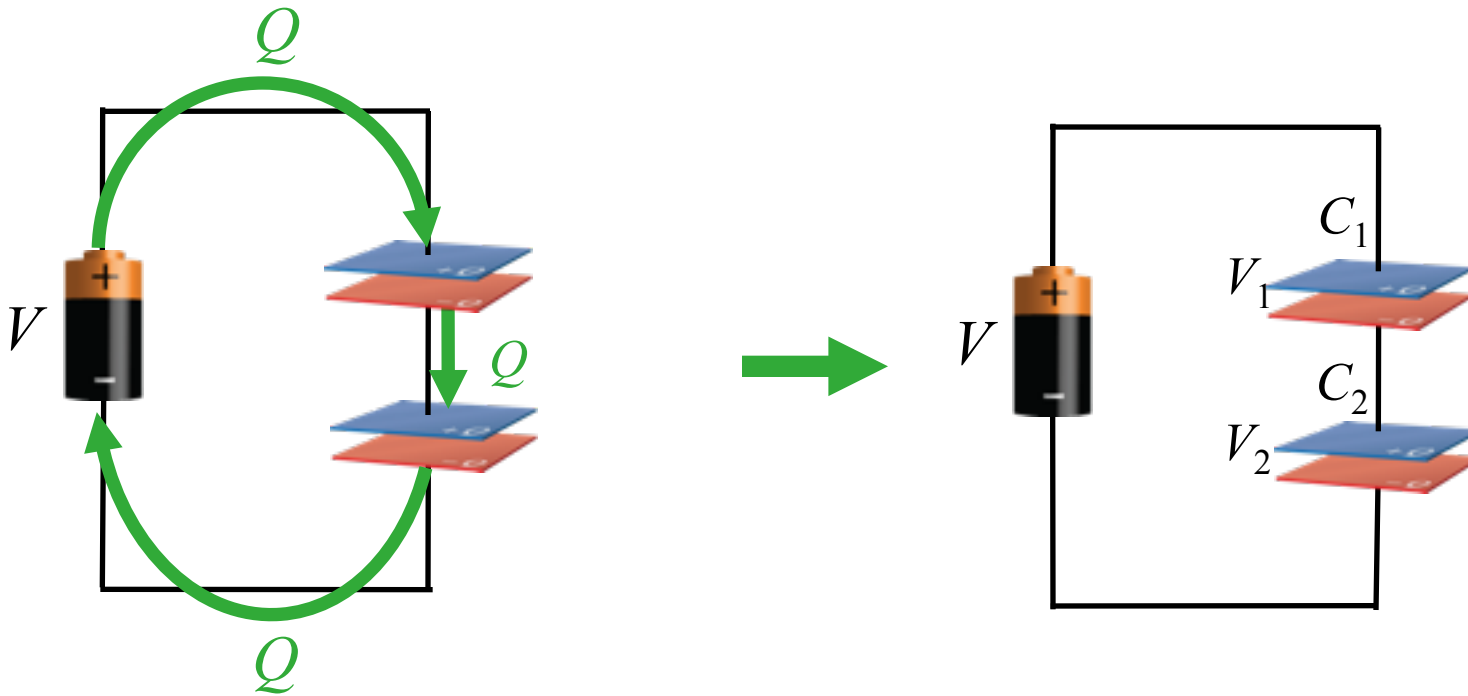

Key point: Q is the same for both capacitors


Series Capacitor Circuit

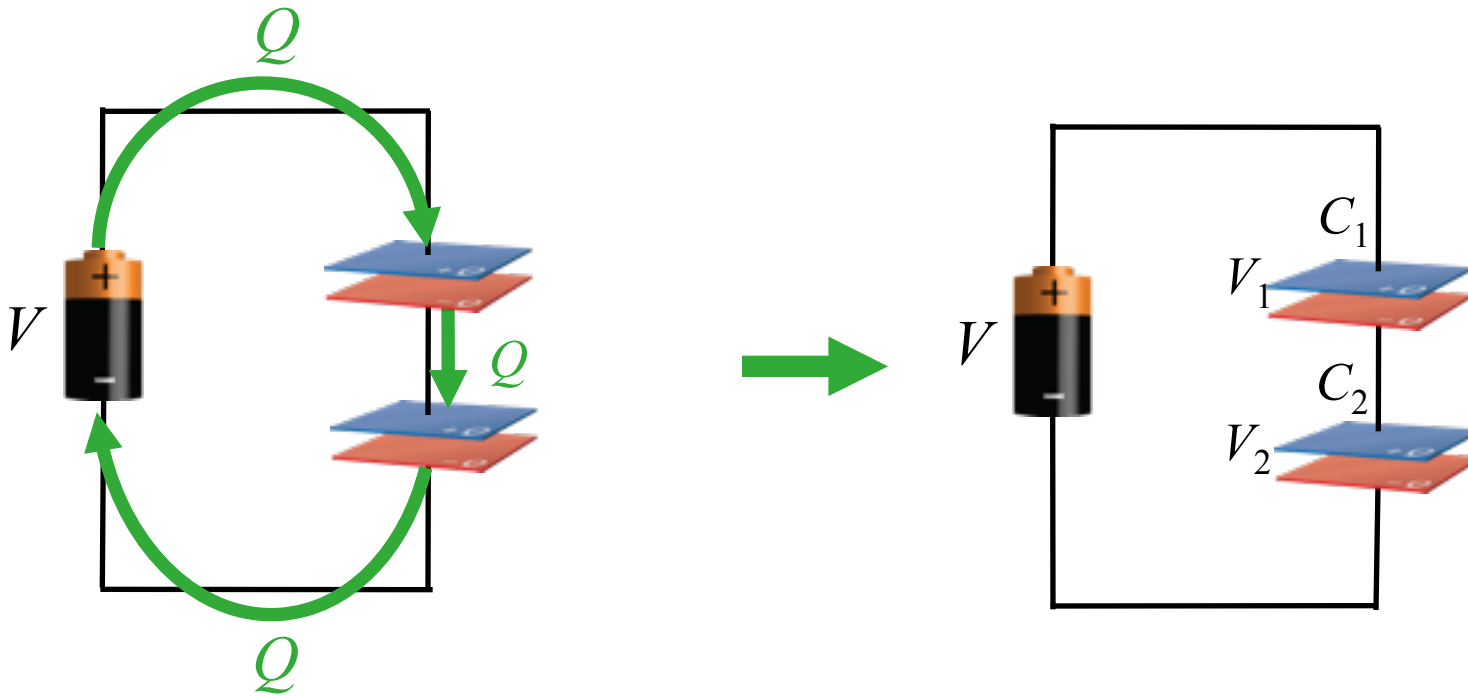

Key point: Q is the same for both capacitors

Key point: $Q = VC_{total} = V_1C_1 = V_2C_2$

Series Capacitor Circuit

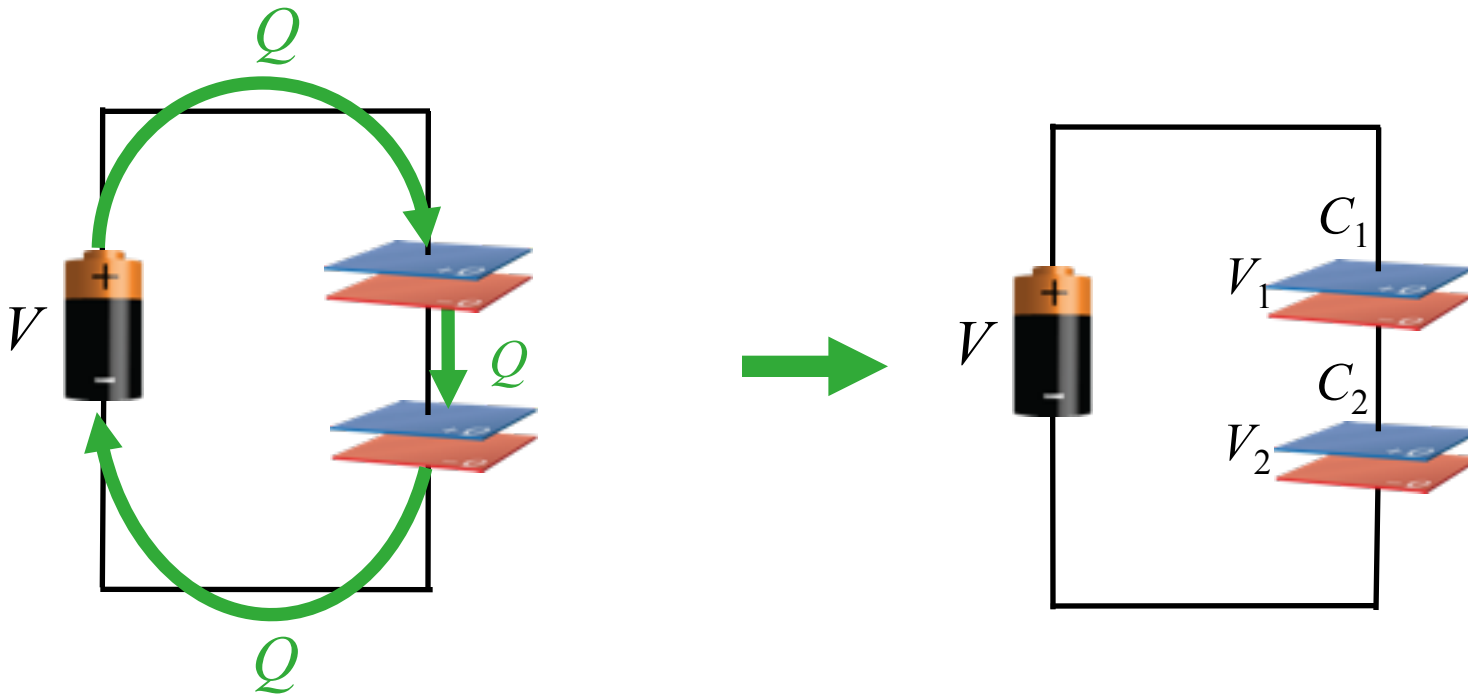


Key point: Q is the same for both capacitors

Key point: $Q = VC_{total} = V_1C_1 = V_2C_2$

Also: $V = V_1 + V_2$

Series Capacitor Circuit

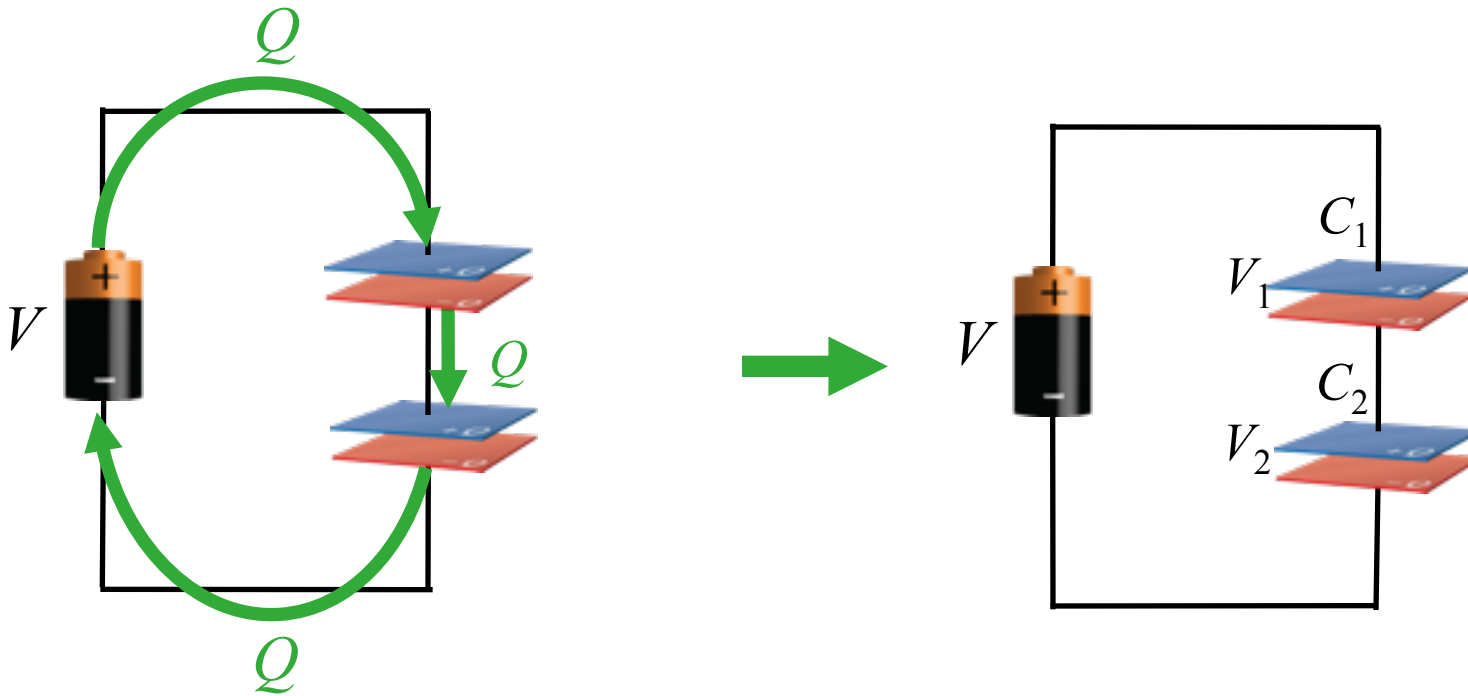


Key point: Q is the same for both capacitors

Key point: $Q = VC_{total} = V_1C_1 = V_2C_2$

Also: $V = V_1 + V_2 \quad \longrightarrow \quad Q/C_{total} = Q/C_1 + Q/C_2$

Series Capacitor Circuit

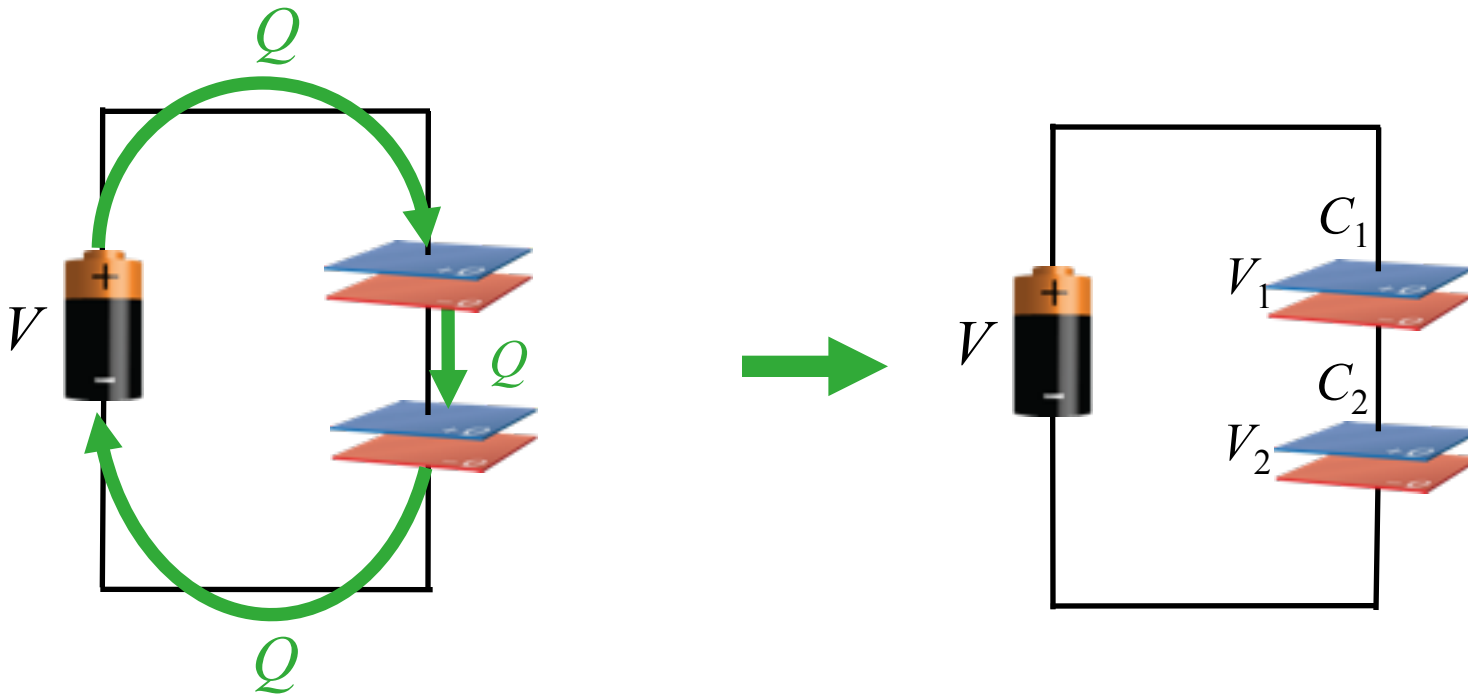

Key point: Q is the same for both capacitors




Key point: $Q = VC_{total} = V_1C_1 = V_2C_2$

Also: $V = V_1 + V_2 \quad \longrightarrow \quad Q/C_{total} = Q/C_1 + Q/C_2$

$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2}$$

CheckPoint: Three Capacitor Configurations

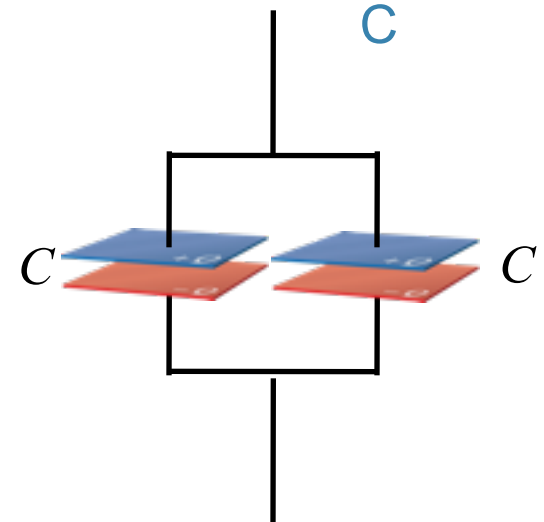
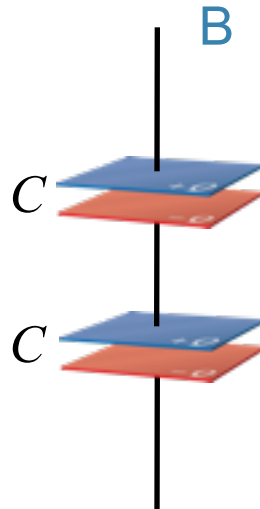
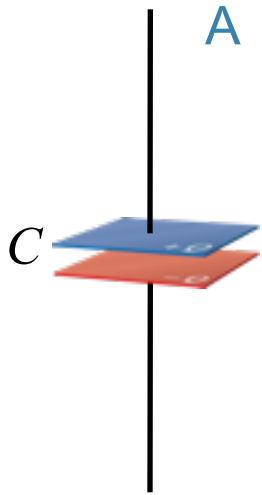
The three configurations shown below are constructed using identical capacitors. Which of these configurations has lowest total capacitance?



D: All 3 are the same

CheckPoint: Three Capacitor Configurations

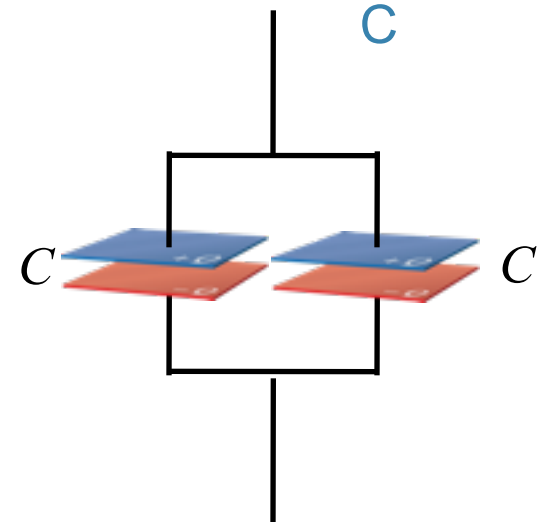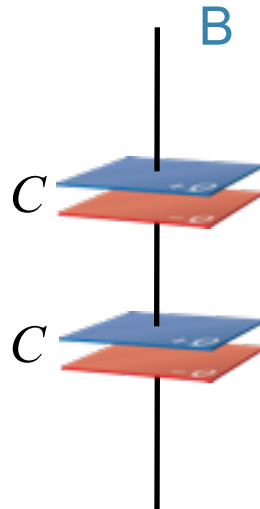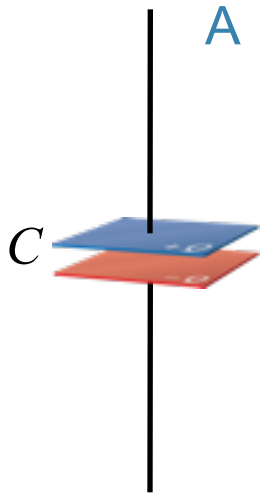The three configurations shown below are constructed using identical capacitors. Which of these configurations has lowest total capacitance?




$$\begin{aligned} 1/C_{total} &= 1/C + 1/C \\ &= 2/C \end{aligned}$$


D: All 3 are the same

CheckPoint: Three Capacitor Configurations

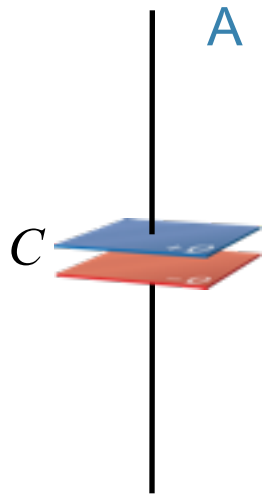
The three configurations shown below are constructed using identical capacitors. Which of these configurations has lowest total capacitance?



$$C_{total} = C$$

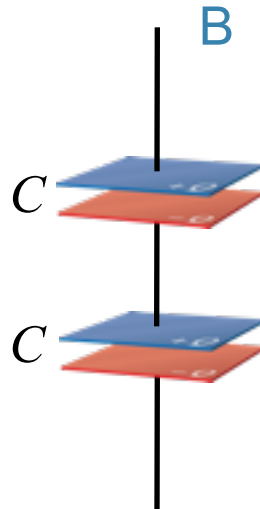

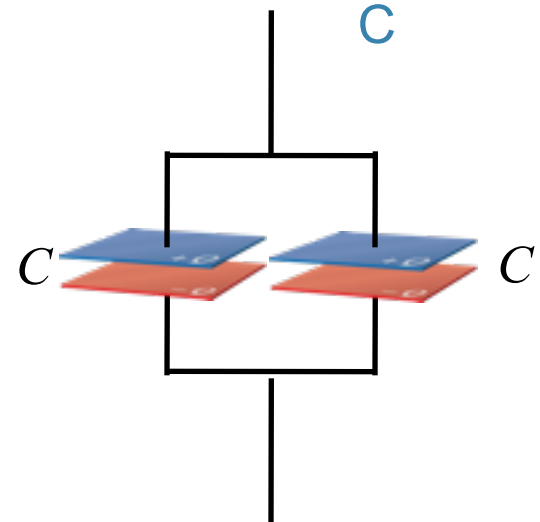
$$\begin{aligned} 1/C_{total} &= 1/C + 1/C \\ &= 2/C \end{aligned}$$




D: All 3 are the same

CheckPoint: Three Capacitor Configurations

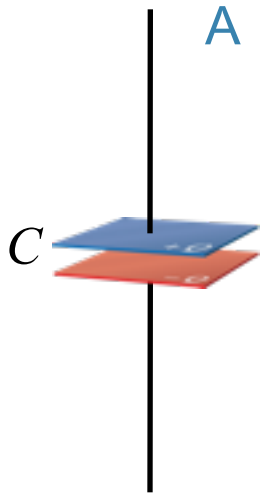The three configurations shown below are constructed using identical capacitors. Which of these configurations has lowest total capacitance?




$$C_{total} = C$$

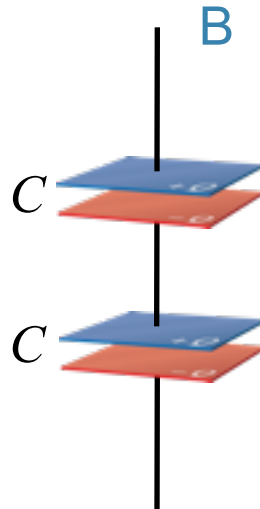

$$\begin{aligned} 1/C_{total} &= 1/C + 1/C \\ &= 2/C \end{aligned}$$



$$C_{total} = C/2$$

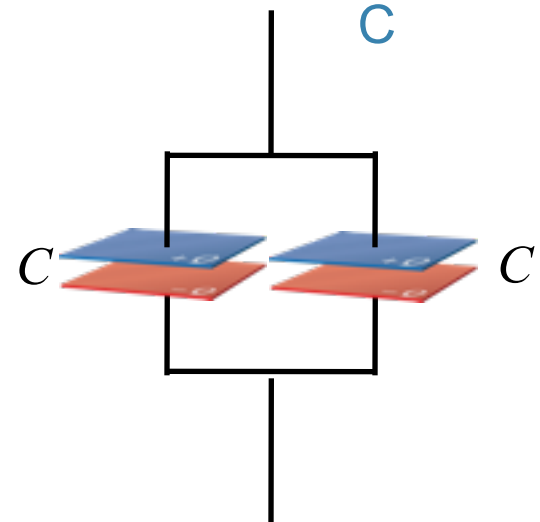

D: All 3 are the same


CheckPoint: Three Capacitor Configurations

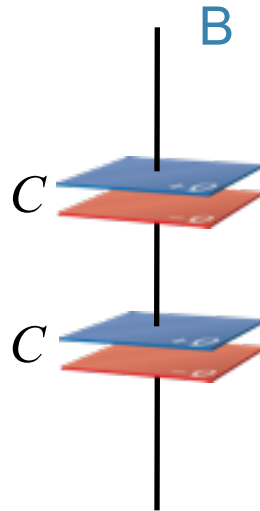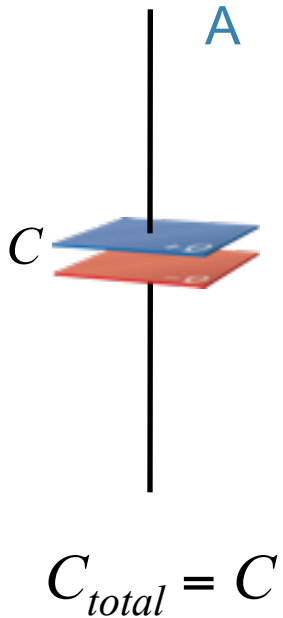The three configurations shown below are constructed using identical capacitors. Which of these configurations has lowest total capacitance?



$$\begin{aligned} \frac{1}{C_{total}} &= \frac{1}{C} + \frac{1}{C} \\ &= \frac{2}{C} \end{aligned}$$



$$C_{total} = C/2$$

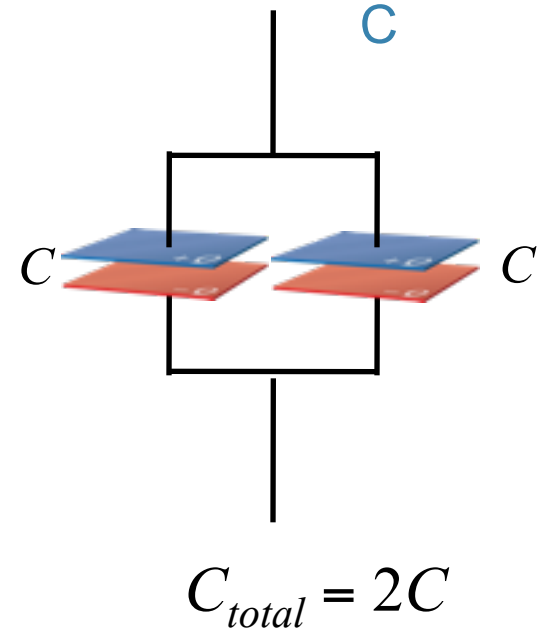

D: All 3 are the same


CheckPoint: Three Capacitor Configurations

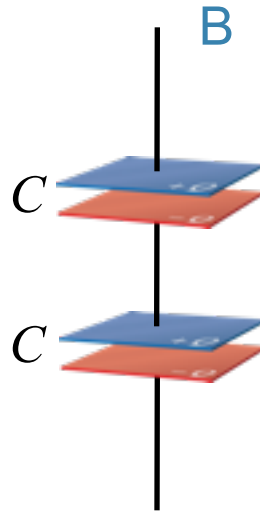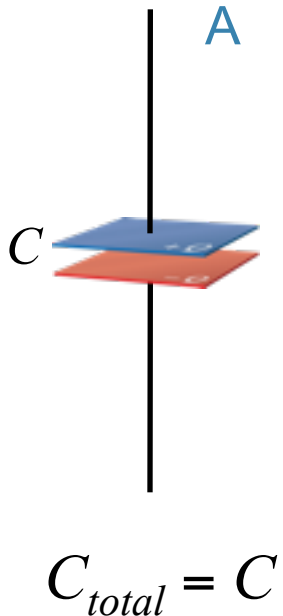The three configurations shown below are constructed using identical capacitors. Which of these configurations has lowest total capacitance?



$$\begin{aligned} \frac{1}{C_{total}} &= \frac{1}{C} + \frac{1}{C} \\ &= \frac{2}{C} \end{aligned}$$



$$C_{total} = C/2$$

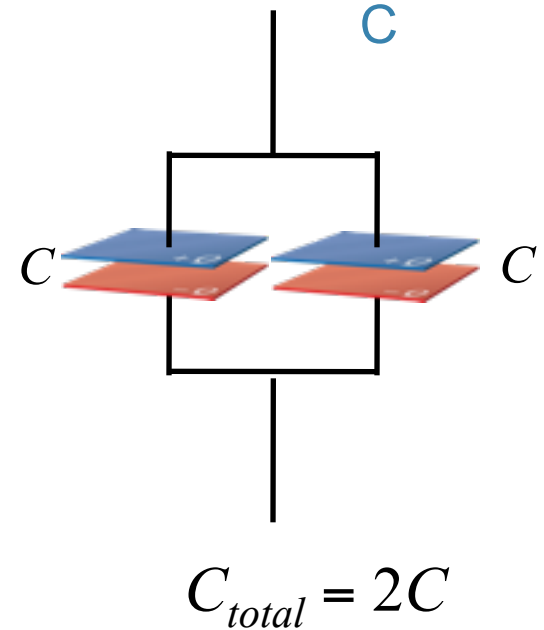

D: All 3 are the same


CheckPoint: Three Capacitor Configurations

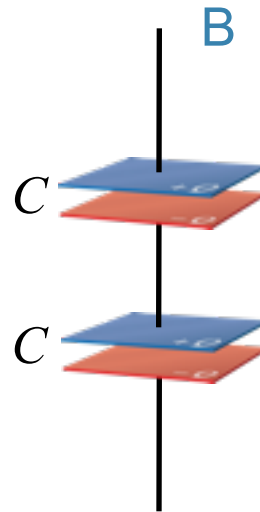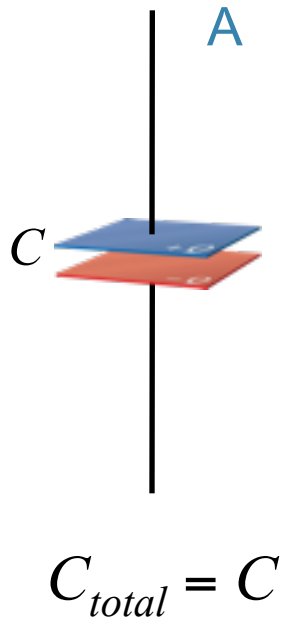The three configurations shown below are constructed using identical capacitors. Which of these configurations has lowest total capacitance?




$$\frac{1}{C_{total}} = \frac{1}{C} + \frac{1}{C}$$
$$= \frac{2}{C}$$

$$C_{total} = C/2$$

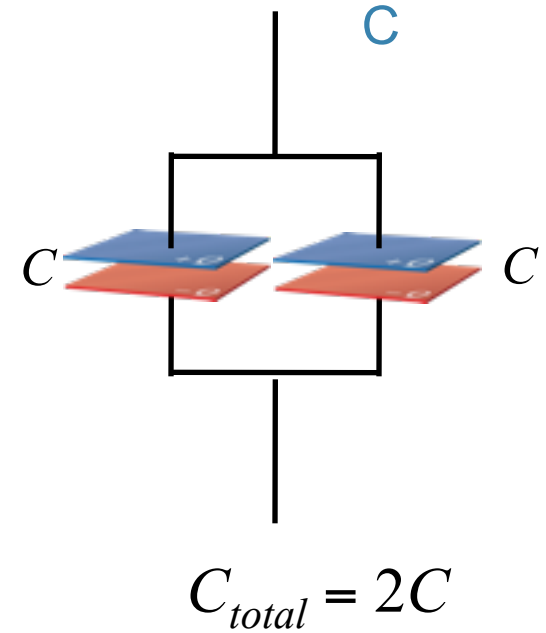


D: All 3 are the same

Answer Choice Distribution

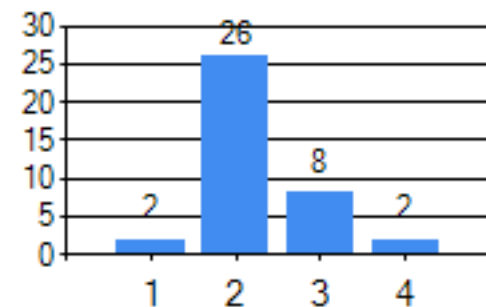

Checkpoint: Two Capacitor Configurations


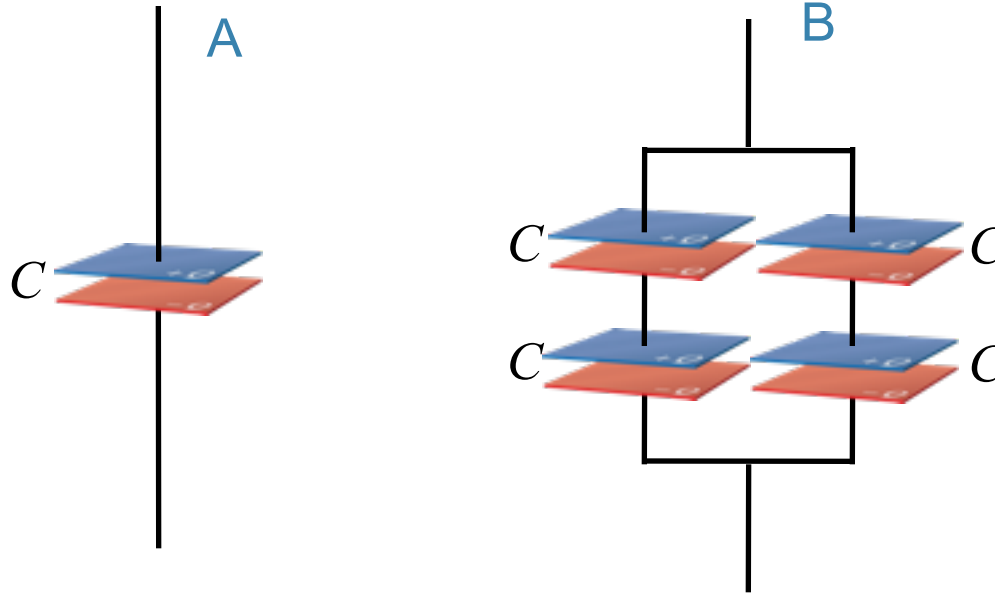
The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?



- ☐ A
- ☐ B
- ☐ Both configurations have the same capacitance

Checkpoint: Two Capacitor Configurations

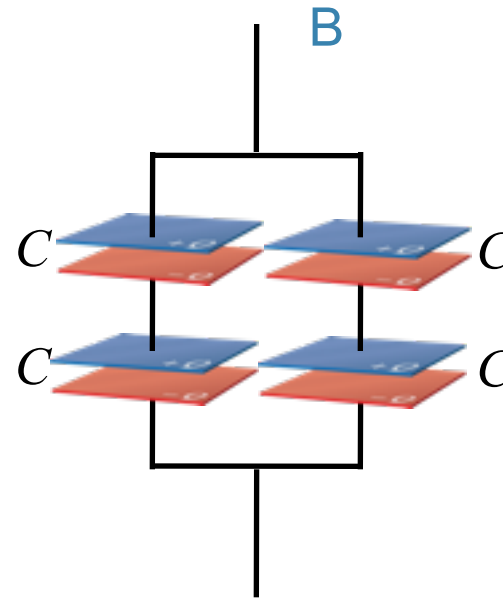
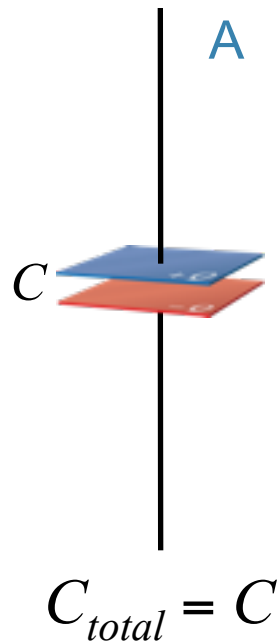
The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?



- ☐ A
- ☐ B
- ☐ Both configurations have the same capacitance

CheckPoint: Two Capacitor Configurations

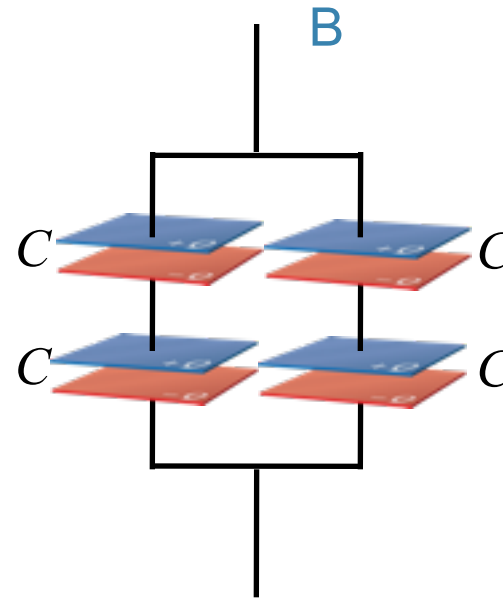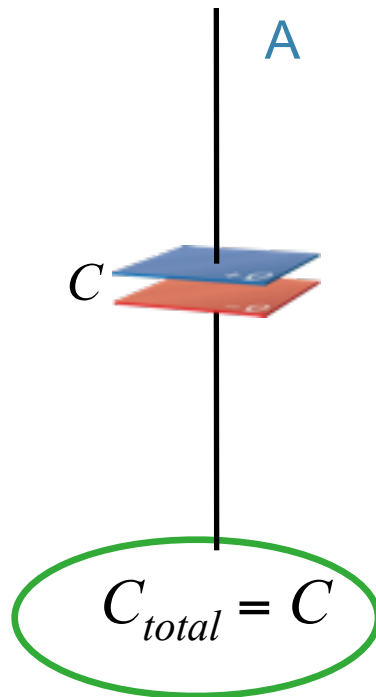
The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?



- ☐ A
- ☐ B
- ☐ Both configurations have the same capacitance

CheckPoint: Two Capacitor Configurations

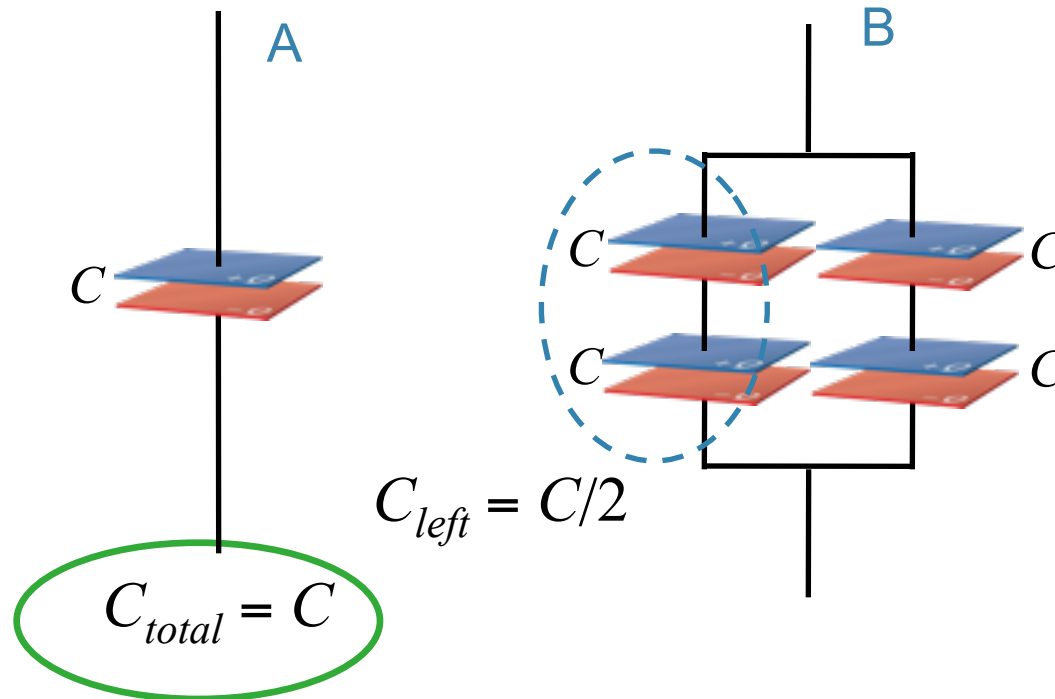
The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?



- ☐ A
- ☐ B
- ☐ Both configurations have the same capacitance

CheckPoint: Two Capacitor Configurations

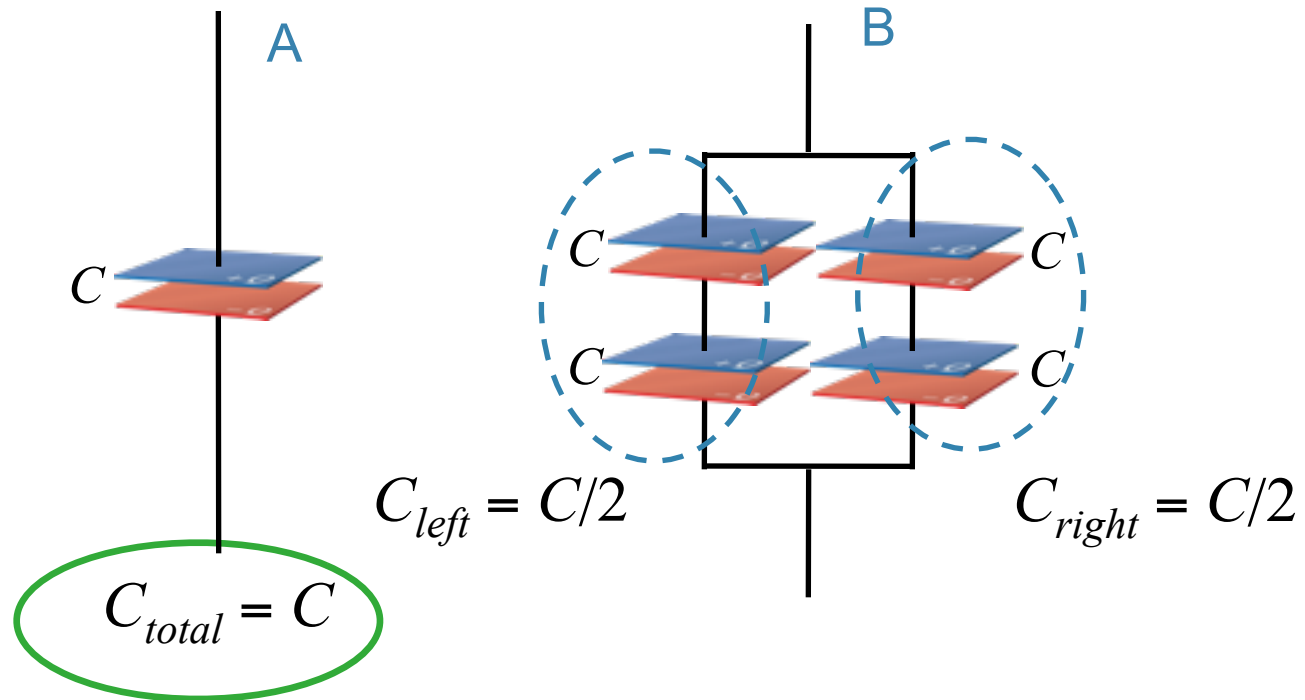
The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?



- ☐ A
- ☐ B
- ☐ Both configurations have the same capacitance

CheckPoint: Two Capacitor Configurations

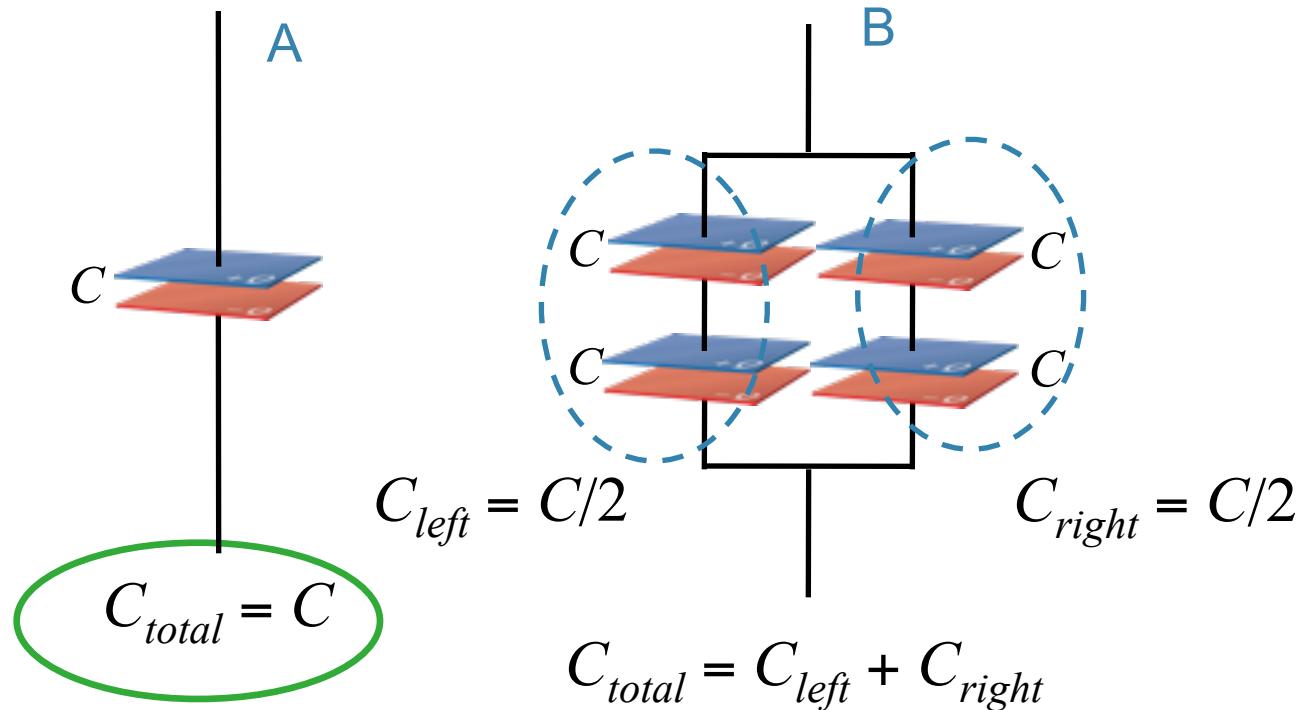
The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?



- ☐ A
- ☐ B
- ☐ Both configurations have the same capacitance

CheckPoint: Two Capacitor Configurations

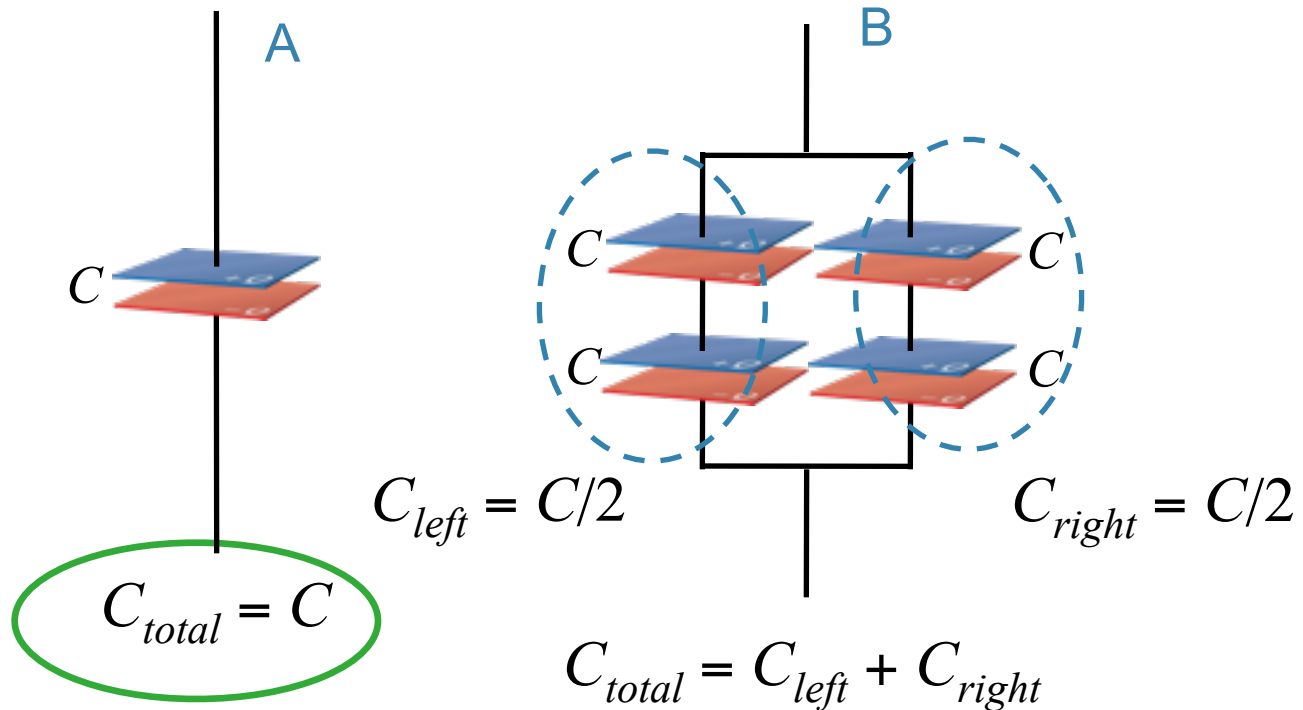The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?




$$C_{total} = C$$

- ☐ A
- ☐ B
- ☐ Both configurations have the same capacitance

CheckPoint: Two Capacitor Configurations

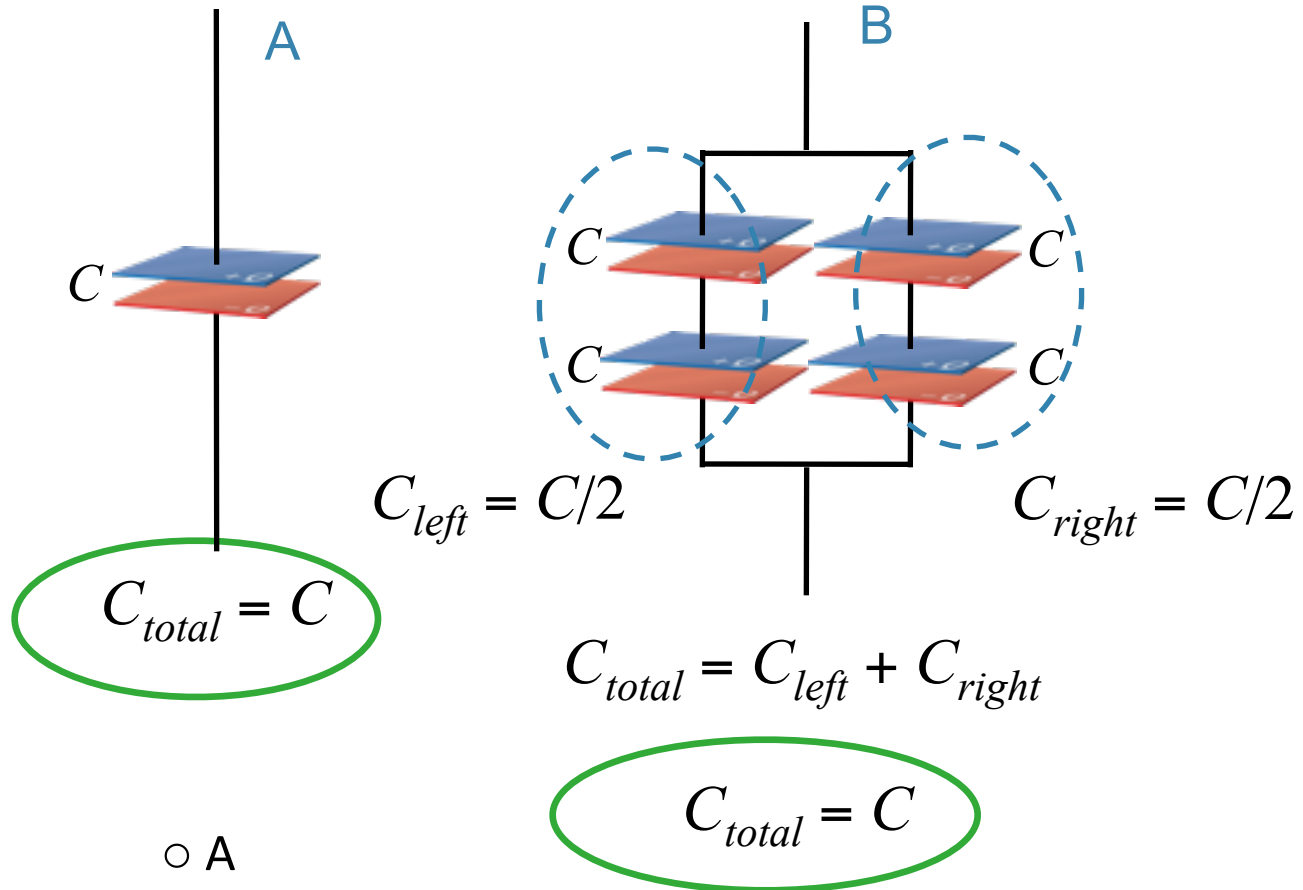
The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?



- ☐ A
- ☐ B
- ☐ Both configurations have the same capacitance

CheckPoint: Two Capacitor Configurations

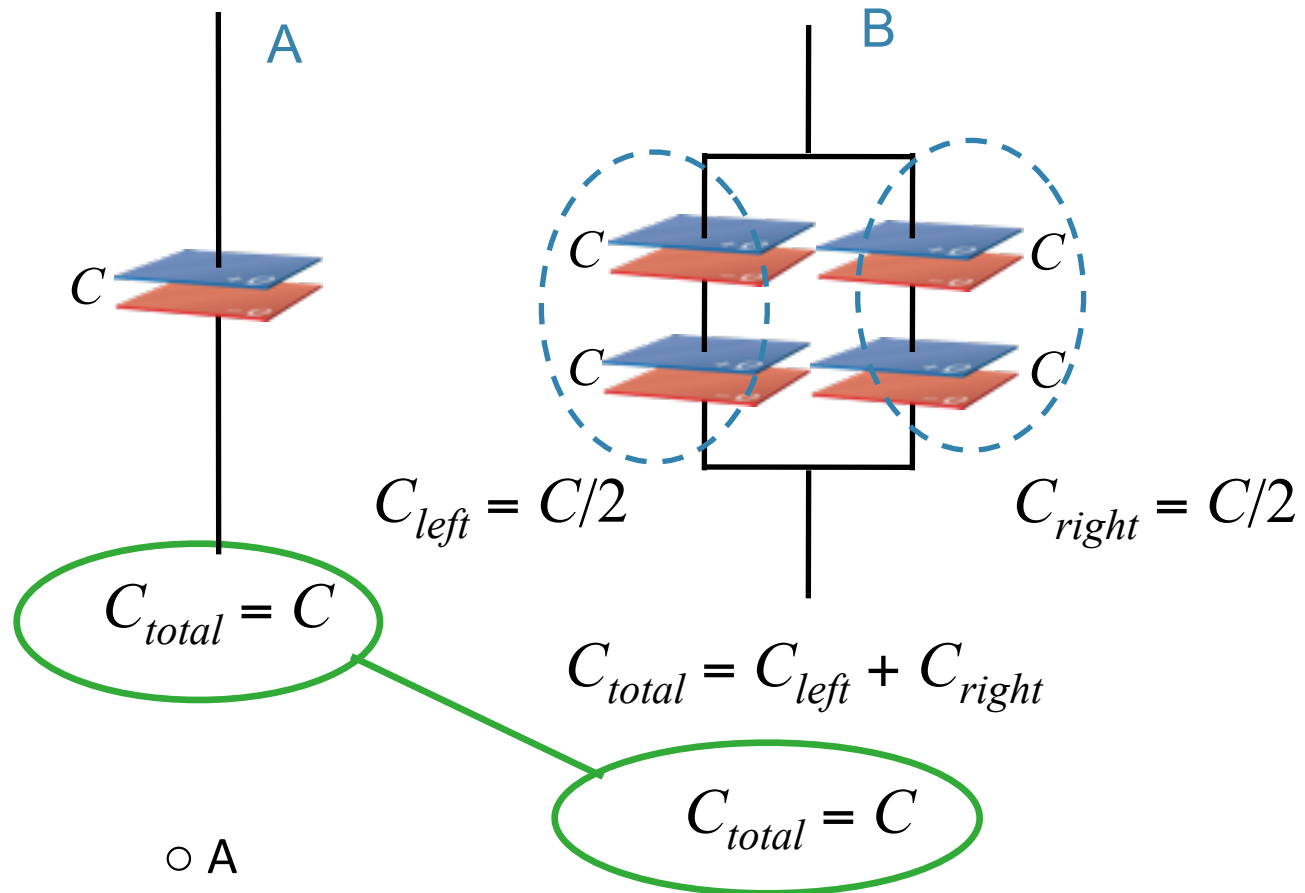
The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?



- ☐ A
- ☐ B
- ☐ Both configurations have the same capacitance

CheckPoint: Two Capacitor Configurations

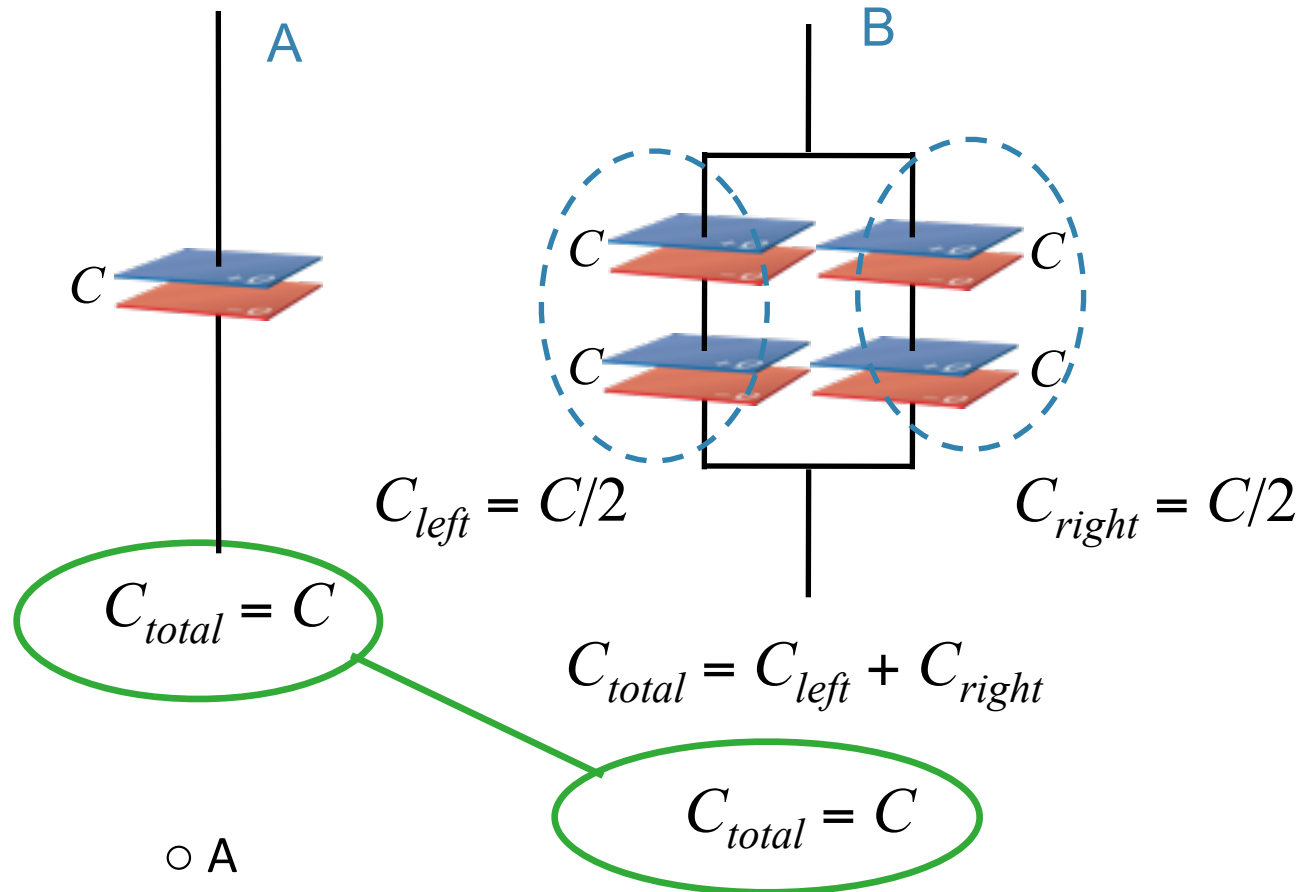The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?




☐ A

☐ B


☐ Both configurations have the same capacitance

CheckPoint: Two Capacitor Configurations

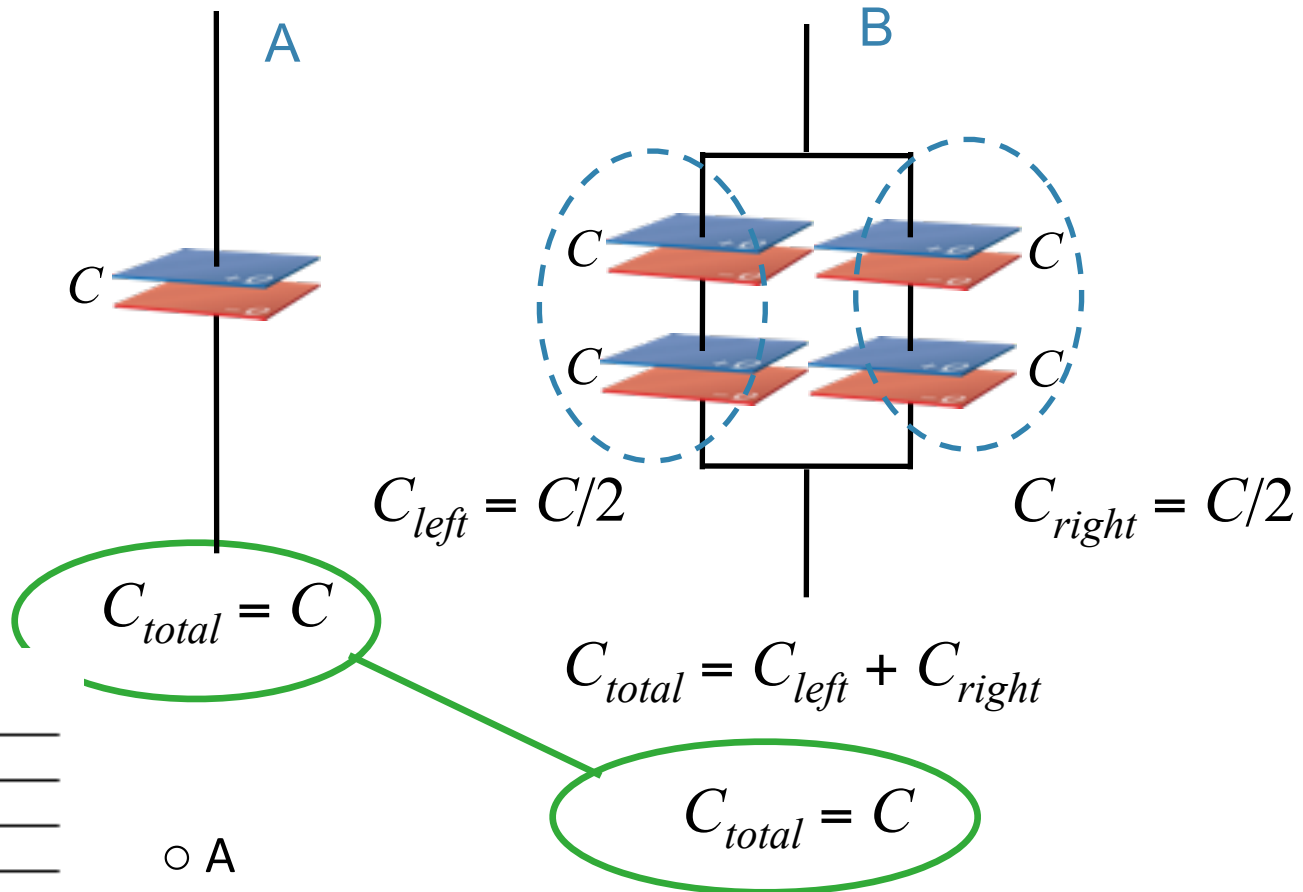The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?




Answer Choice Distribution

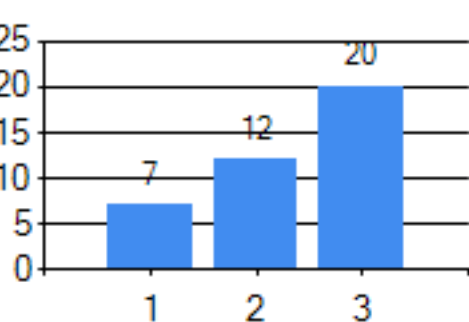


- ☐ A
- ☐ B
- ☐ Both configurations have the same capacitance


Clicker Question: Capacitor Network

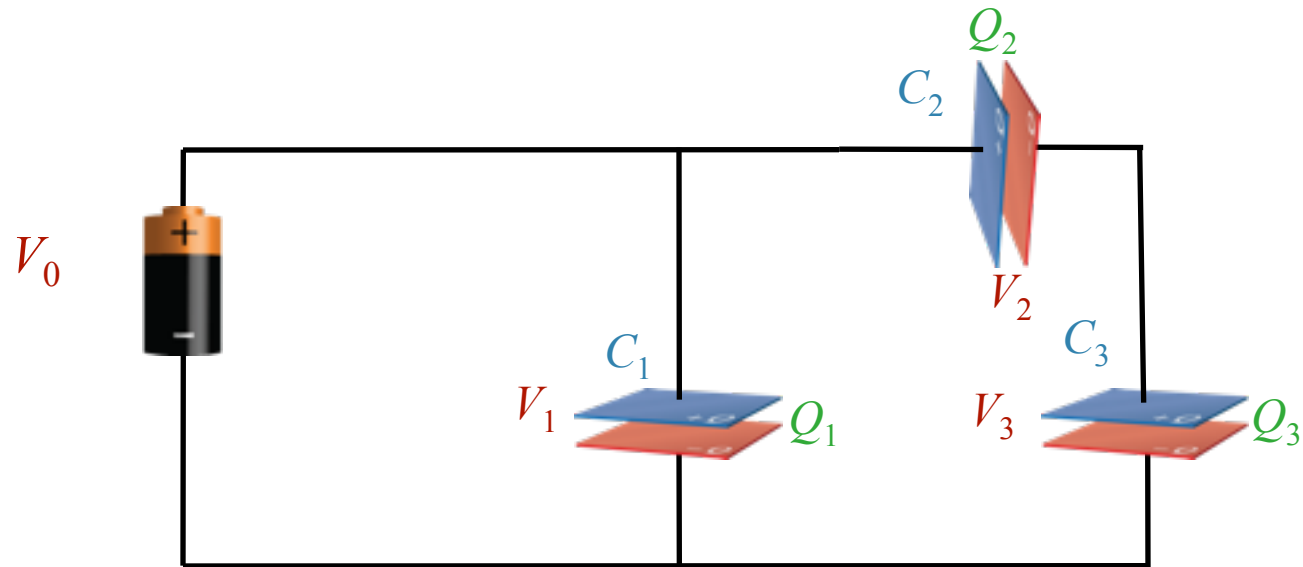

Clicker Question: Capacitor Network

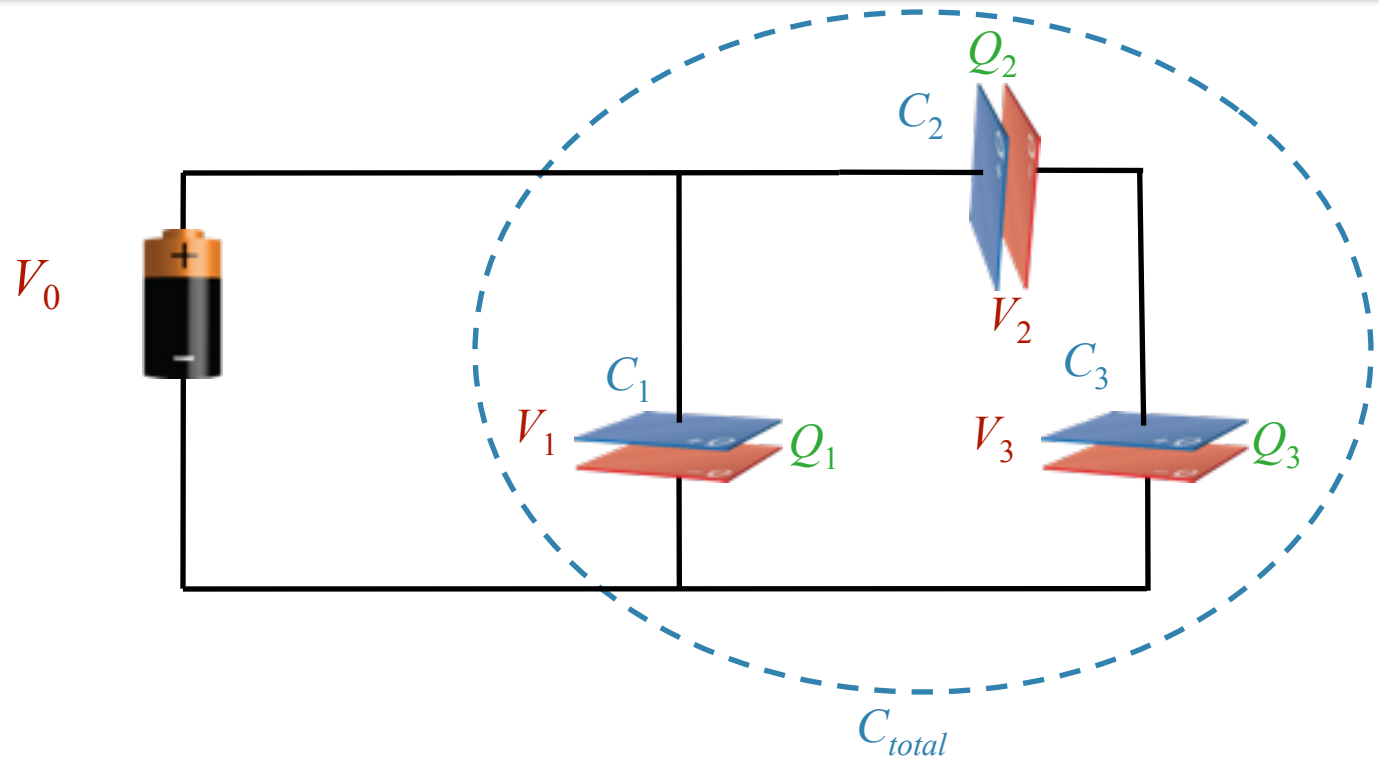


Clicker Question: Capacitor Network

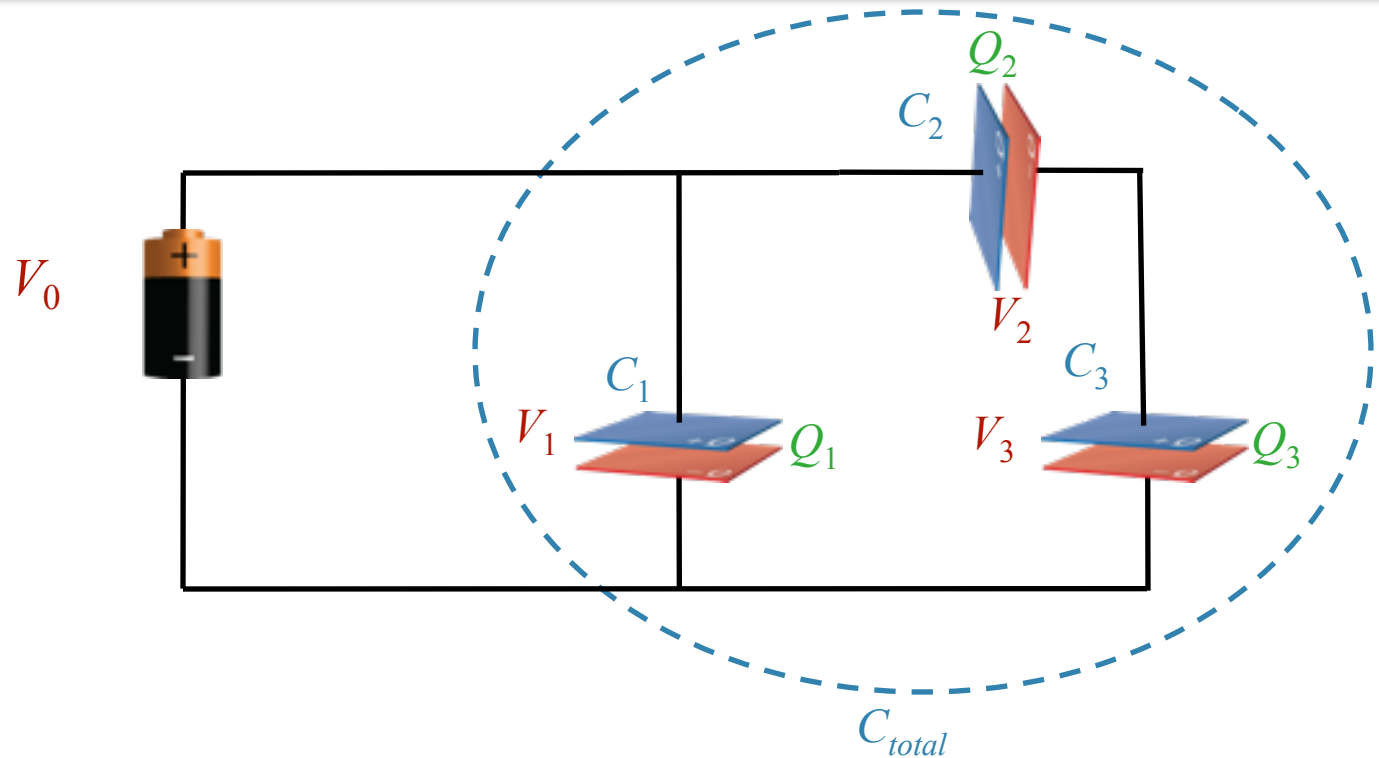

Which of the following is **NOT** necessarily true:

- A) $V_0 = V_1$
- B) $C_{total} > C_1$
- C) $V_2 = V_3$
- D) $Q_2 = Q_3$
- E) $V_1 = V_2 + V_3$

Clicker Question: Capacitor Network

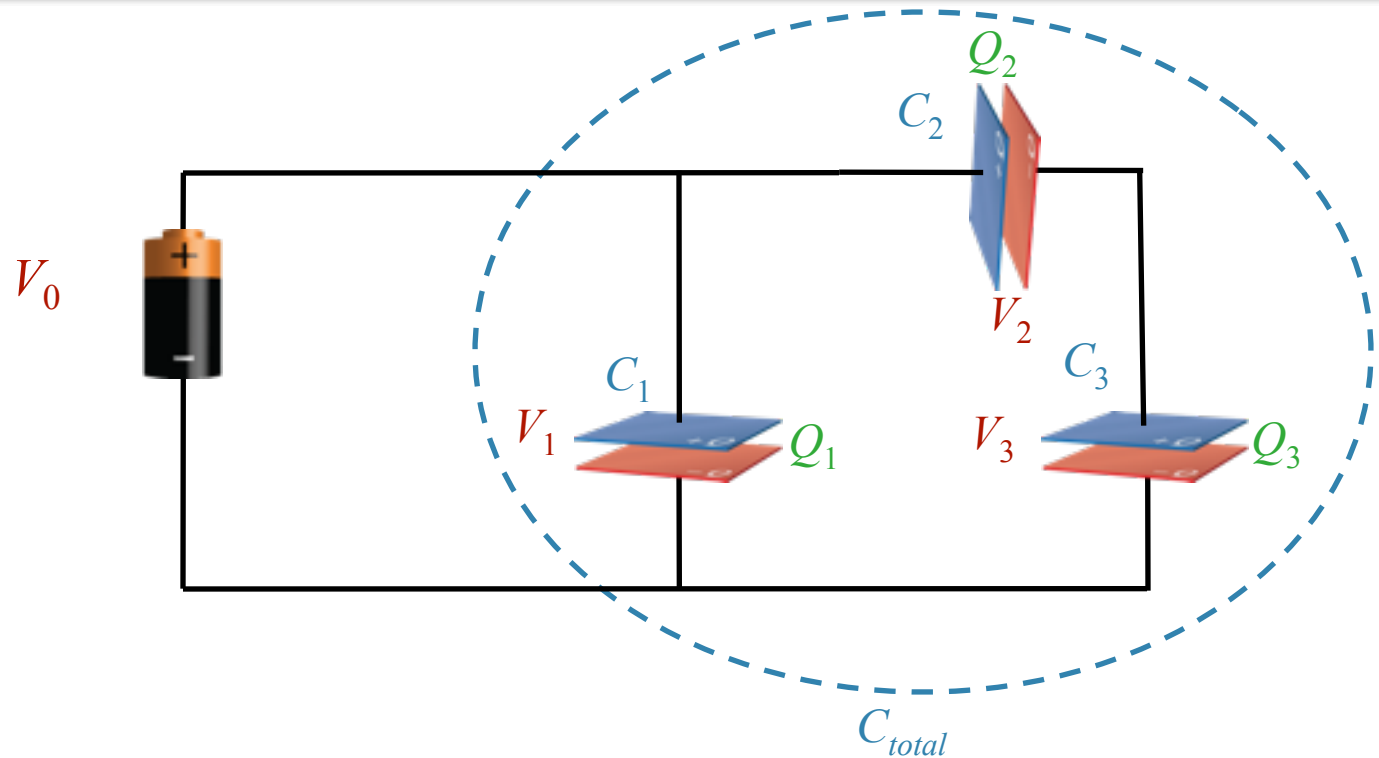


Which of the following is **NOT** necessarily true:

- A) $V_0 = V_1$
- B) $C_{total} > C_1$
- C) $V_2 = V_3$**
- D) $Q_2 = Q_3$
- E) $V_1 = V_2 + V_3$

Clicker Question: Capacitor Network



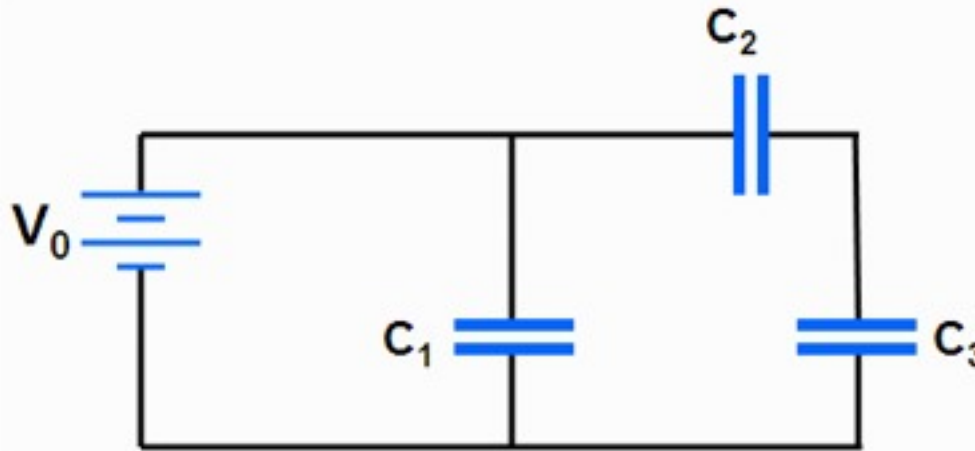7) A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitors obtain charges Q_1 , Q_2 , Q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.



To simplify,
Assume $C_1 = C_2 = C_3$

Check all of the following that apply in the general case for all values of the capacitors:

- ☐ $Q_1 = Q_2$
- ☐ $Q_2 = Q_3$
- ☐ $V_2 = V_3$
- ☐ $V_0 = V_1$
- ☐ $V_1 < V_2$
- ☐ $C_{eq} > C_1$

$$\begin{matrix} Q_1 = Q_2 \\ V_1 < V_2 \end{matrix}$$

(A)

$$\begin{matrix} Q_1 = Q_2 \\ V_1 \nless V_2 \end{matrix}$$

(B)

$$\begin{matrix} Q_1 \neq Q_2 \\ V_1 < V_2 \end{matrix}$$

(C)


$$\begin{matrix} Q_1 \neq Q_2 \\ V_1 \nless V_2 \end{matrix}$$

(D)

Clicker Question: Capacitor Network



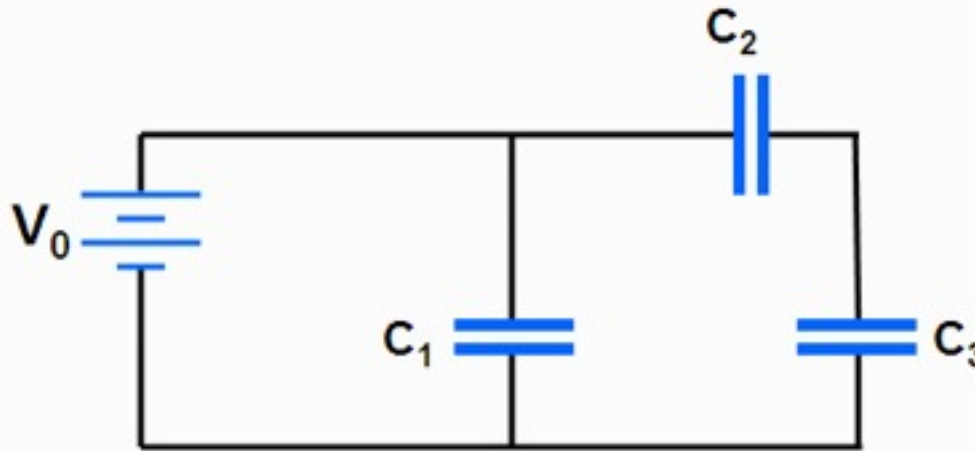7) A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitors obtain charges Q_1 , Q_2 , Q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.



To simplify,
Assume $C_1 = C_2 = C_3$

Check all of the following that apply in the general case for all values of the capacitors:

- ☐ $Q_1 = Q_2$
 - ☐ $Q_2 = Q_3$
 - ☐ $V_2 = V_3$
 - ☐ $V_0 = V_1$
 - ☐ $V_1 < V_2$
 - ☐ $C_{eq} > C_1$
- $V_1 = V_2 + V_3$

$$\begin{array}{l} Q_1 = Q_2 \\ V_1 < V_2 \end{array}$$

(A)

$$\begin{array}{l} Q_1 = Q_2 \\ V_1 \nless V_2 \end{array}$$

(B)

$$\begin{array}{l} Q_1 \neq Q_2 \\ V_1 < V_2 \end{array}$$

(C)


$$\begin{array}{l} Q_1 \neq Q_2 \\ V_1 \nless V_2 \end{array}$$

(D)

Clicker Question: Capacitor Network



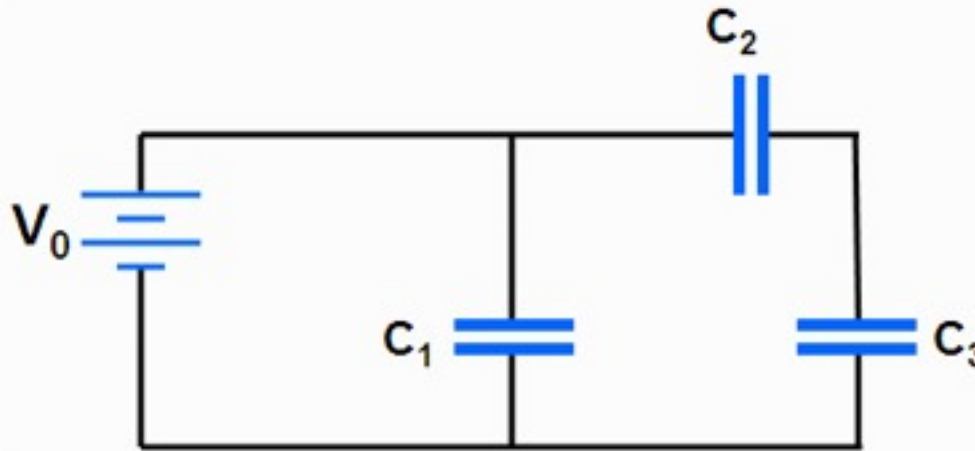7) A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitors obtain charges Q_1 , Q_2 , Q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.



To simplify,
Assume $C_1 = C_2 = C_3$

Check all of the following that apply in the general case for all values of the capacitors:

☐ $Q_1 = Q_2$
☐ $Q_2 = Q_3$
☐ $V_2 = V_3$
☐ $V_0 = V_1$
☐ $V_1 < V_2$
☐ $C_{eq} > C_1$

$V_1 = V_2 + V_3$
 $\rightarrow V_1 > V_2$

$Q_1 = Q_2$
 $V_1 < V_2$

(A)

$Q_1 = Q_2$
 $V_1 < V_2$

(B)

$Q_1 \neq Q_2$
 $V_1 < V_2$

(C)


$Q_1 \neq Q_2$
 $V_1 < V_2$

(D)

Clicker Question: Capacitor Network



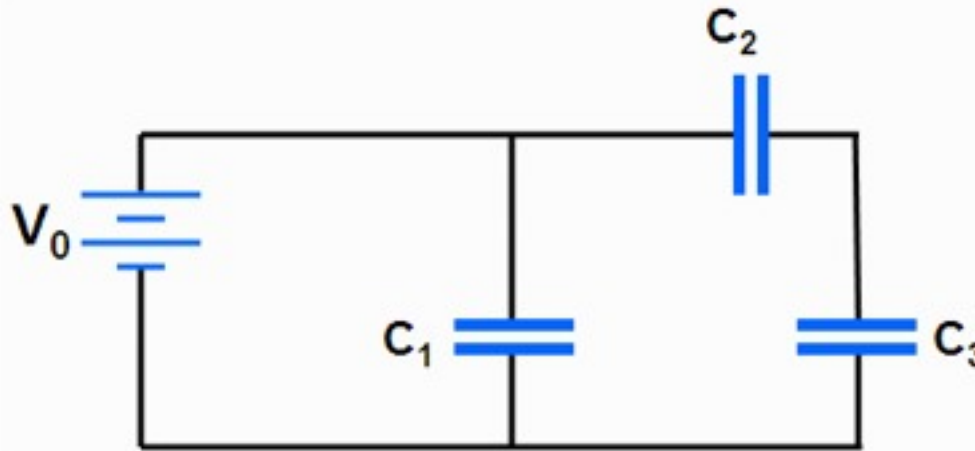7) A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitors obtain charges Q_1 , Q_2 , Q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.



To simplify,
Assume $C_1 = C_2 = C_3$

Check all of the following that apply in the general case for all values of the capacitors:

☐ $Q_1 = Q_2$

☐ $Q_2 = Q_3$

☐ $V_2 = V_3$

☐ $V_0 = V_1$

NO ☐ $V_1 < V_2$

☐ $C_{eq} > C_1$

$V_1 = V_2 + V_3$

$Q_2 = Q_3$

$\longrightarrow V_1 > V_2$

$Q_1 = Q_2$
 $V_1 < V_2$

(A)

$Q_1 = Q_2$
 $V_1 < V_2$

(B)

$Q_1 \neq Q_2$
 $V_1 < V_2$

(C)


$Q_1 \neq Q_2$
 $V_1 < V_2$

(D)

Clicker Question: Capacitor Network



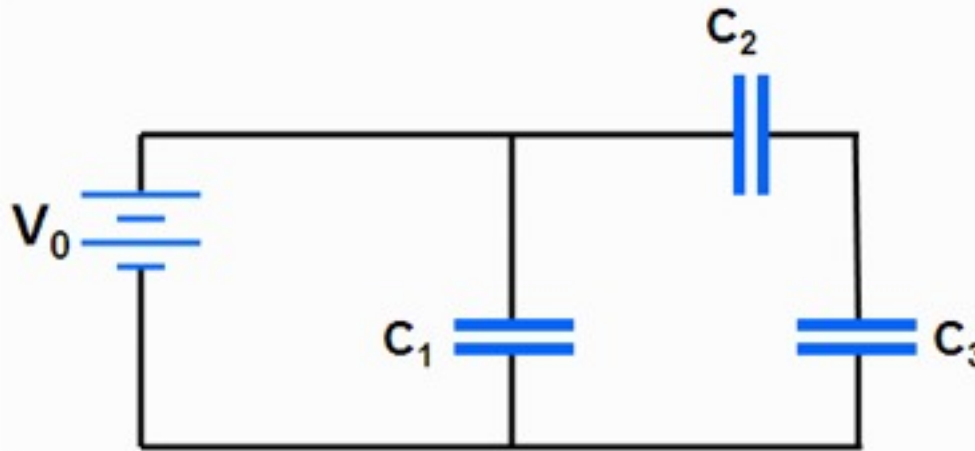7) A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitors obtain charges Q_1 , Q_2 , Q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.



To simplify,
Assume $C_1 = C_2 = C_3$

Check all of the following that apply in the general case for all values of the capacitors:

- ☐ $Q_1 = Q_2$
 - ☐ $Q_2 = Q_3$
 - ☐ $V_2 = V_3$
 - ☐ $V_0 = V_1$
 - ☒ $V_1 < V_2$
 - ☐ $C_{eq} > C_1$
- $V_1 = V_2 + V_3$
 $Q_2 = Q_3$
 $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} + \frac{Q_2}{C_3}$
 $Q_1 = Q_2$
 $V_1 < V_2$

(A)

$$Q_1 = Q_2$$

$$V_1 \neq V_2$$

(B)

$$Q_1 \neq Q_2$$

$$V_1 < V_2$$

(C)

$$Q_1 \neq Q_2$$


$$V_1 \neq V_2$$

(D)

Clicker Question: Capacitor Network



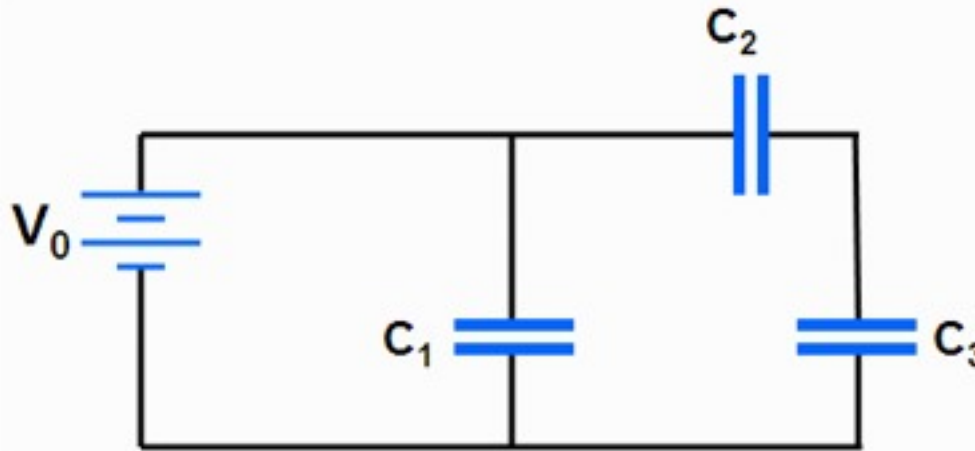7) A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitors obtain charges Q_1 , Q_2 , Q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.



To simplify,
Assume $C_1 = C_2 = C_3$

Check all of the following that apply in the general case for all values of the capacitors:

NO ☐ $Q_1 = Q_2$

☐ $Q_2 = Q_3$

☐ $V_2 = V_3$

☐ $V_0 = V_1$

NO ☐ $V_1 < V_2$

☐ $C_{eq} > C_1$

$$V_1 = V_2 + V_3$$

$$Q_2 = Q_3$$

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2} + \frac{Q_2}{C_3}$$

$$Q_1 = Q_2$$

$$V_1 < V_2$$

(A)

$$\longrightarrow V_1 > V_2$$

$$\longrightarrow Q_2 = \frac{C_2 C_3}{C_1 (C_2 + C_3)} Q_1$$

$$Q_1 = Q_2$$

$$V_1 < V_2$$

(B)

$$Q_1 \neq Q_2$$

$$V_1 < V_2$$

(C)

$$Q_1 \neq Q_2$$


$$V_1 < V_2$$

(D)

Clicker Question: Capacitor Network



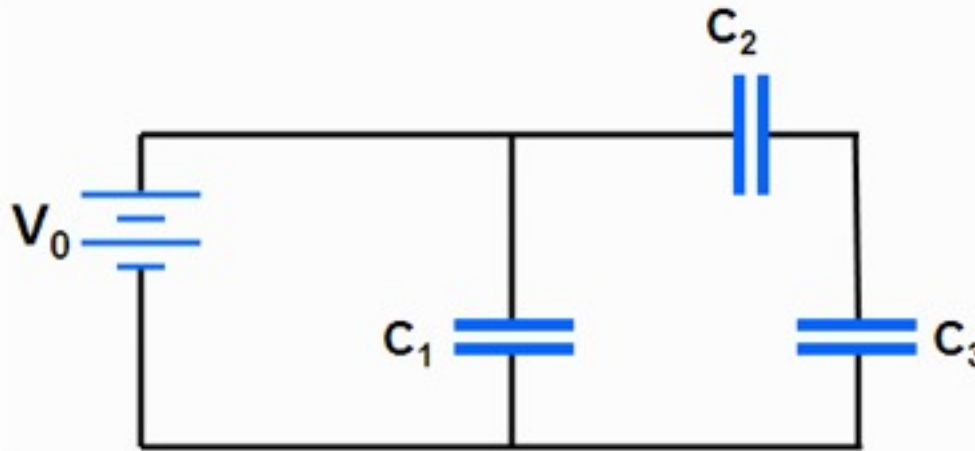7) A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitors obtain charges Q_1 , Q_2 , Q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.



To simplify,
Assume $C_1 = C_2 = C_3$

Check all of the following that apply in the general case for all values of the capacitors:

NO ☐ $Q_1 = Q_2$

☐ $Q_2 = Q_3$

☐ $V_2 = V_3$

☐ $V_0 = V_1$

NO ☐ $V_1 < V_2$

☐ $C_{eq} > C_1$

$$V_1 = V_2 + V_3$$

$$Q_2 = Q_3$$

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2} + \frac{Q_2}{C_3}$$

$$Q_1 = Q_2$$

$$V_1 < V_2$$

(A)

$$\longrightarrow V_1 > V_2$$

$$\longrightarrow Q_2 = \frac{C_2 C_3}{C_1 (C_2 + C_3)} Q_1$$

$$Q_1 = Q_2$$

$$V_1 \neq V_2$$

(B)

$$Q_1 \neq Q_2$$

$$V_1 < V_2$$

(C)

$$Q_1 \neq Q_2$$


$$V_1 \neq V_2$$

(D)

Clicker Question: Capacitor Network



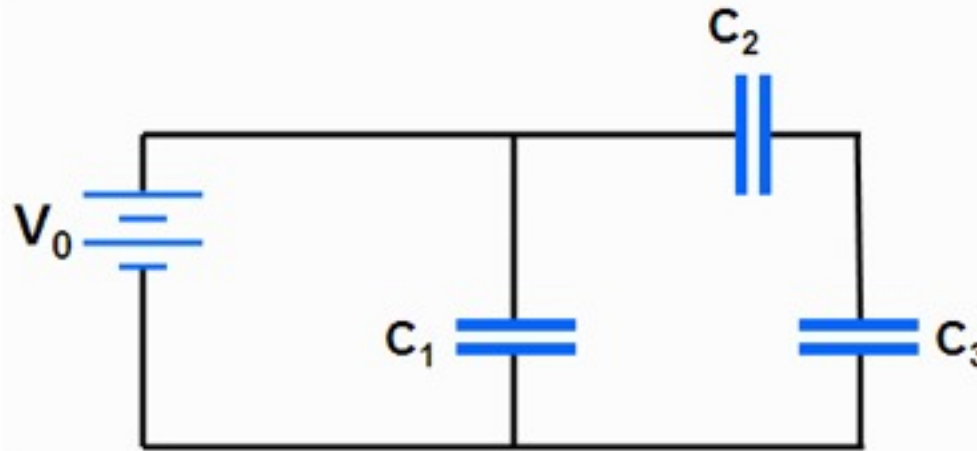7) A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitors obtain charges Q_1 , Q_2 , Q_3 , and have voltages across their plates V_1 , V_2 , and V_3 . C_{eq} is the equivalent capacitance of the circuit.



To simplify,
Assume $C_1 = C_2 = C_3$

Check all of the following that apply in the general case for all values of the capacitors:

NO ☐ $Q_1 = Q_2$

$$V_1 = V_2 + V_3$$

$$\longrightarrow V_1 > V_2$$

YES ☐ $Q_2 = Q_3$

$$Q_2 = Q_3$$



$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2} + \frac{Q_2}{C_3}$$

$$\longrightarrow Q_2 = \frac{C_2 C_3}{C_1 (C_2 + C_3)} Q_1$$

$$Q_1 = Q_2$$

$$V_1 < V_2$$

(A)

$$Q_1 = Q_2$$

$$V_1 \neq V_2$$

(B)

$$Q_1 \neq Q_2$$

$$V_1 < V_2$$

(C)

$$Q_1 \neq Q_2$$

$$V_1 \neq V_2$$

(D)

CheckPoint: Capacitor Network

A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitance of C_2 is twice that of C_1 . The capacitance of C_3 is three times that of C_1 . The capacitors obtain charges Q_1 , Q_2 , and Q_3 .

Compare Q_1 , Q_2 , and Q_3 .


A. $Q_1 > Q_3 > Q_2$

B. $Q_1 > Q_2 > Q_3$

C. $Q_1 > Q_2 = Q_3$

D. $Q_1 = Q_2 = Q_3$

E. $Q_1 < Q_2 = Q_3$

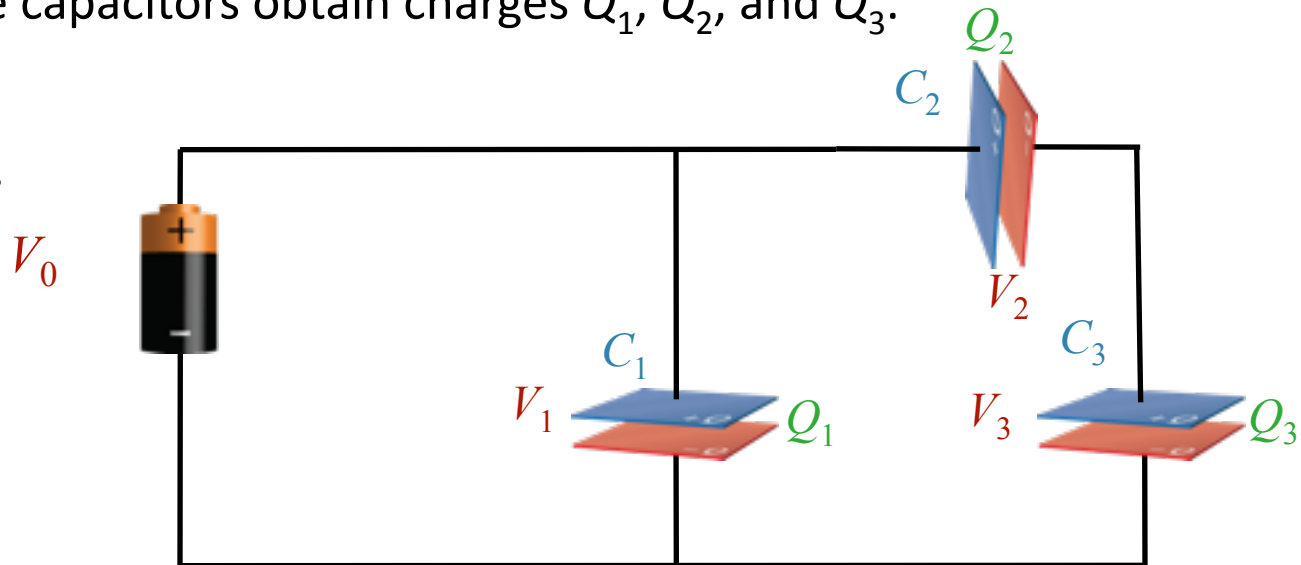

CheckPoint: Capacitor Network

A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitance of C_2 is twice that of C_1 . The capacitance of C_3 is three times that of C_1 . The capacitors obtain charges Q_1 , Q_2 , and Q_3 .

Compare Q_1 , Q_2 , and Q_3 .


A. $Q_1 > Q_3 > Q_2$

B. $Q_1 > Q_2 > Q_3$

C. $Q_1 > Q_2 = Q_3$

D. $Q_1 = Q_2 = Q_3$

E. $Q_1 < Q_2 = Q_3$

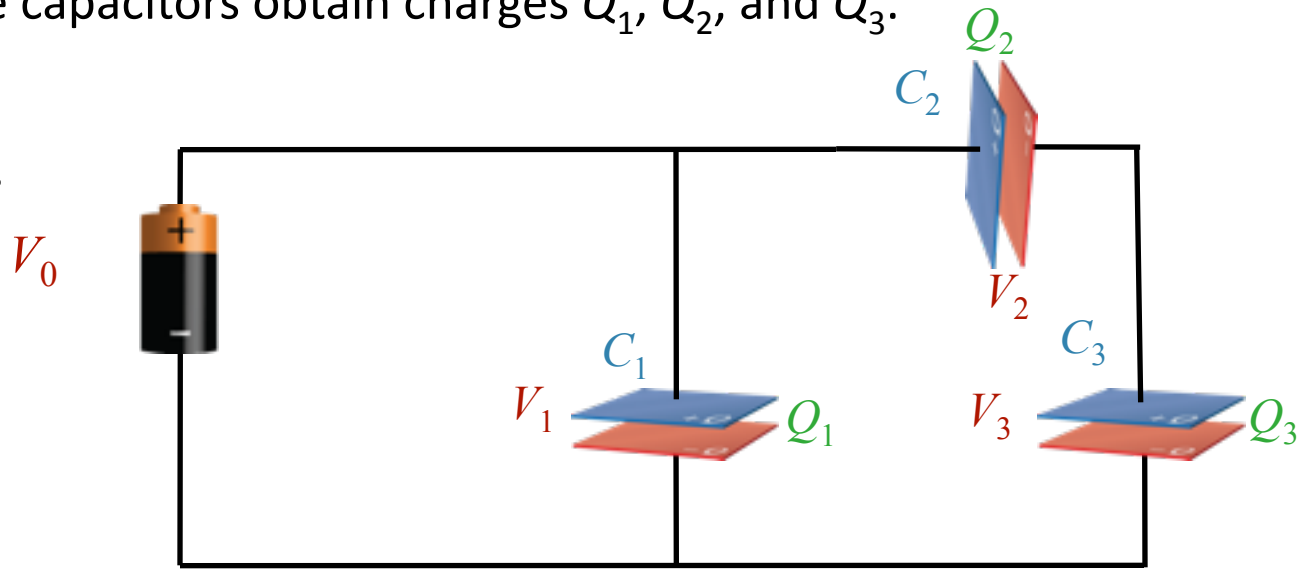

CheckPoint: Capacitor Network

A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitance of C_2 is twice that of C_1 . The capacitance of C_3 is three times that of C_1 . The capacitors obtain charges Q_1 , Q_2 , and Q_3 .

Compare Q_1 , Q_2 , and Q_3 .


A. $Q_1 > Q_3 > Q_2$

B. $Q_1 > Q_2 > Q_3$


C. $Q_1 > Q_2 = Q_3$

D. $Q_1 = Q_2 = Q_3$

E. $Q_1 < Q_2 = Q_3$

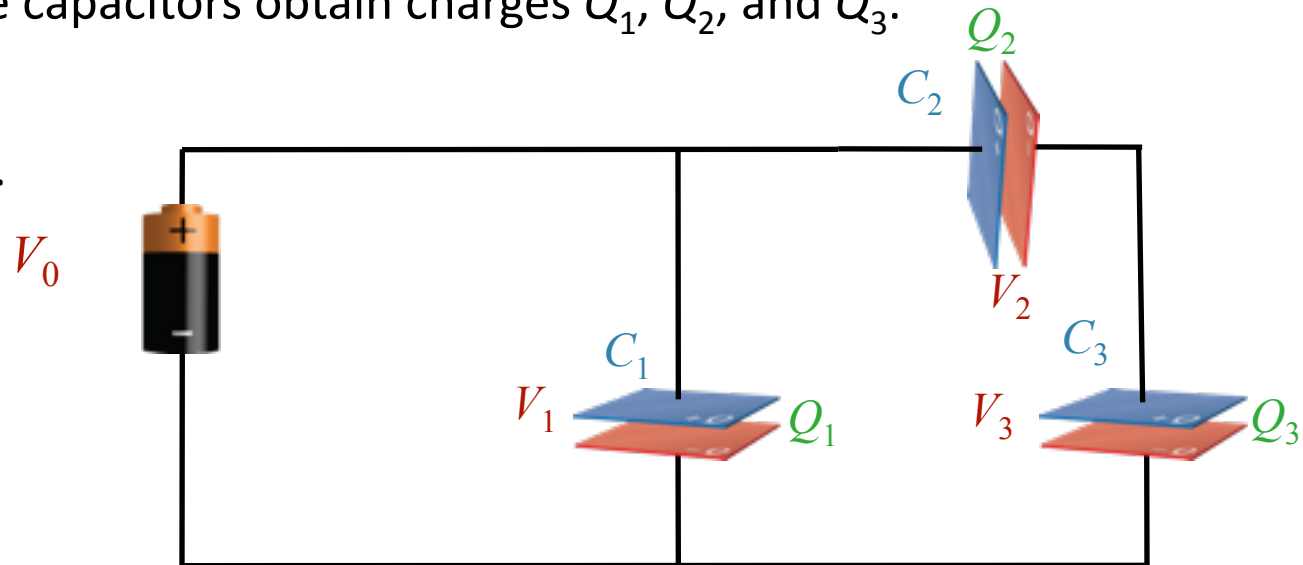


Answer Choice Distribution

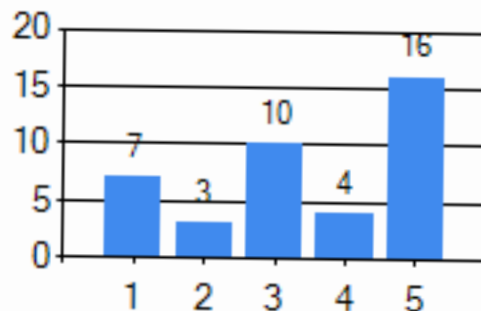

Energy in a Capacitor

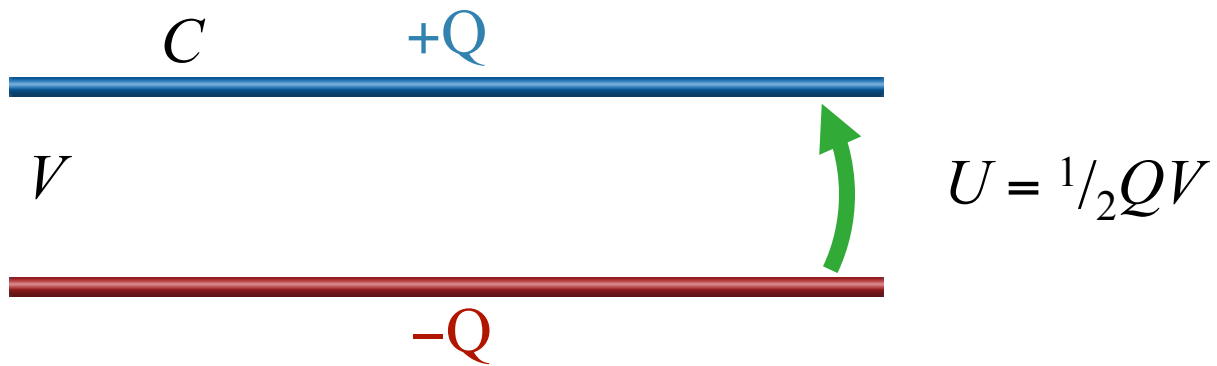
In Prelecture 7 we calculated the work done to move charge Q from one plate to another:



This is potential energy waiting to be used...

Energy in a Capacitor

In Prelecture 7 we calculated the work done to move charge Q from one plate to another:

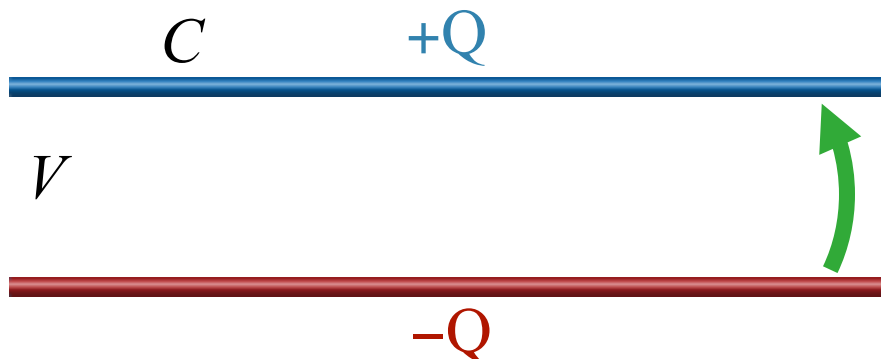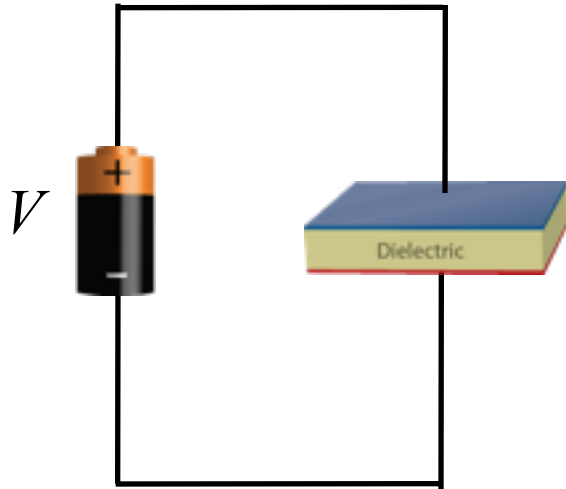

$$\begin{aligned} U &= \frac{1}{2}QV \\ &= \frac{1}{2}CV^2 \\ &= \frac{1}{2}Q^2/C \end{aligned} \quad \left. \vphantom{\begin{aligned} U &= \frac{1}{2}QV \\ &= \frac{1}{2}CV^2 \\ &= \frac{1}{2}Q^2/C \end{aligned}} \right\} \text{Since } Q = VC$$

This is potential energy waiting to be used...

Messing with Capacitors


Messing with Capacitors

If connected to a battery V stays constant




Messing with Capacitors

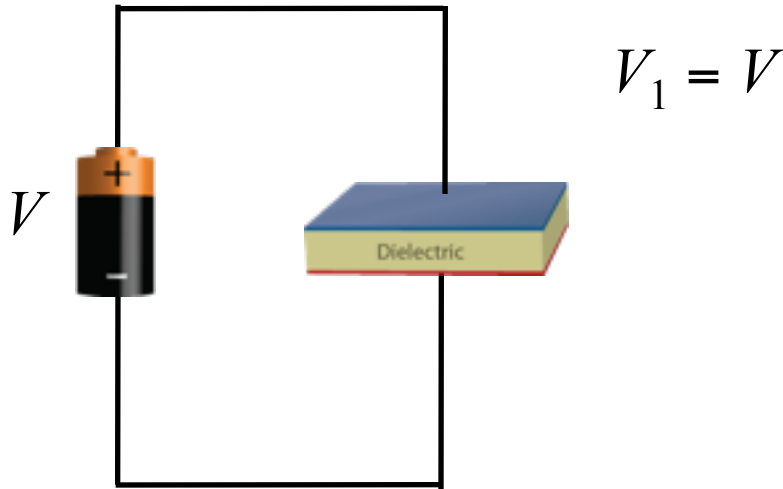If connected to a battery V stays constant



Messing with Capacitors

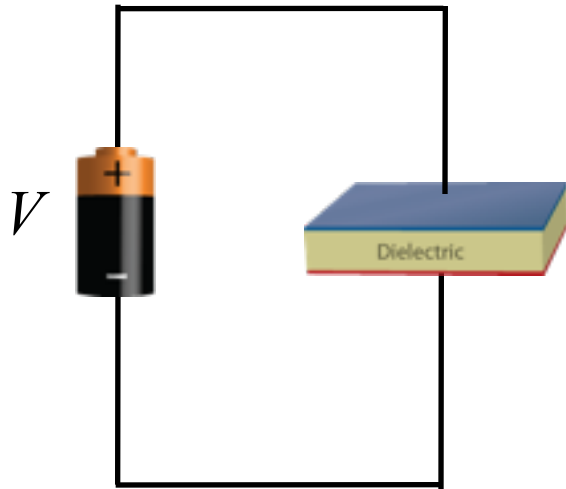If connected to a battery V stays constant




$$V_1 = V$$

$$C_1 = \kappa C$$

Messing with Capacitors

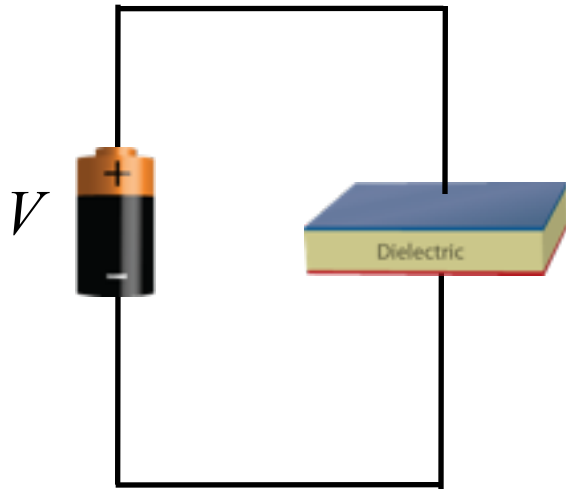If connected to a battery V stays constant




$$V_1 = V$$

$$C_1 = \kappa C$$

Messing with Capacitors

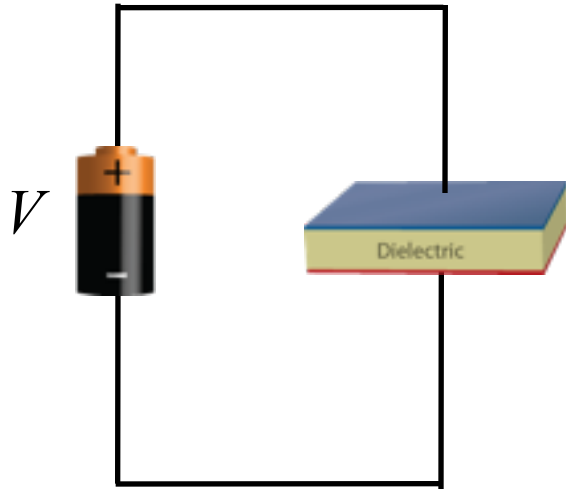If connected to a battery V stays constant




$$V_1 = V$$

$$C_1 = \kappa C$$

Messing with Capacitors

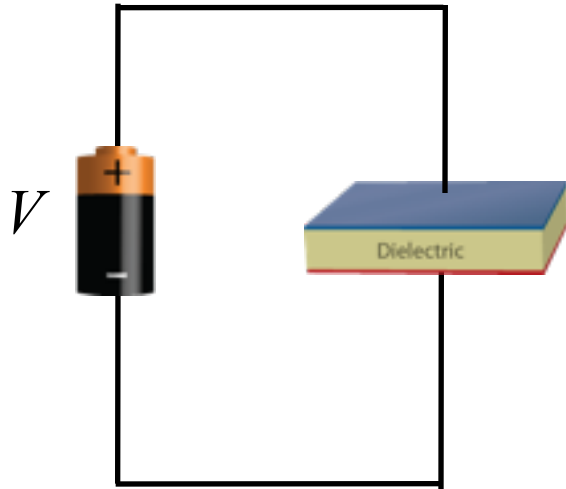If connected to a battery V stays constant




$$V_1 = V$$

$$C_1 = \kappa C$$

Messing with Capacitors

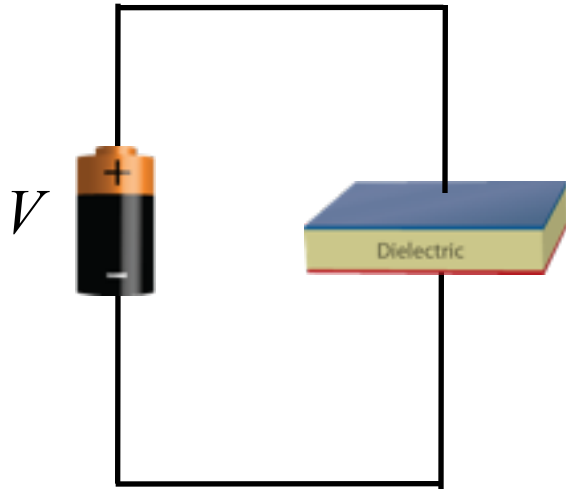If connected to a battery V stays constant




$$V_1 = V$$

$$C_1 = \kappa C$$

Messing with Capacitors

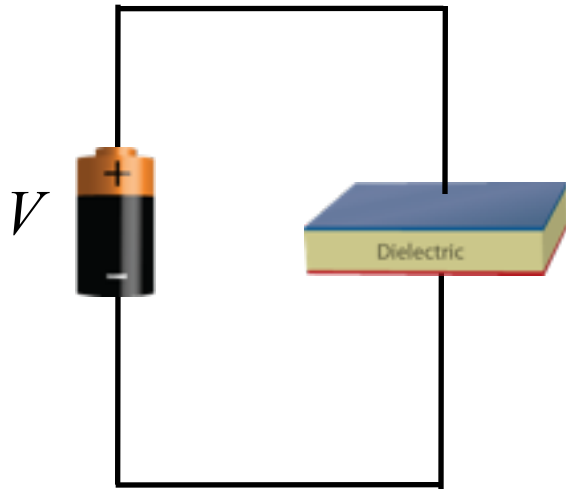If connected to a battery V stays constant




$$V_1 = V$$


$$C_1 = \kappa C$$

Messing with Capacitors

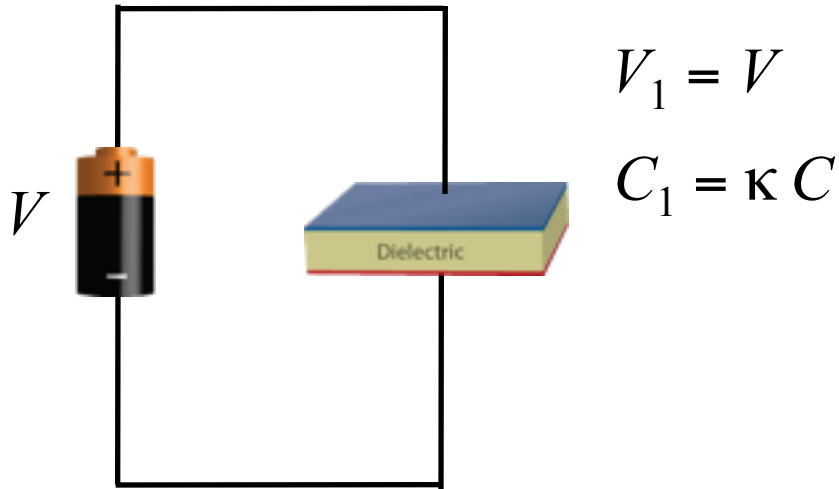If connected to a battery V stays constant




If isolated then total Q stays constant

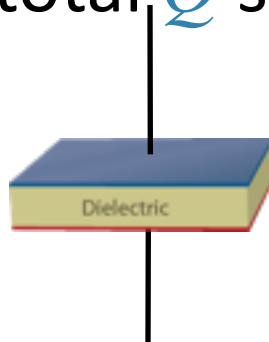


Messing with Capacitors

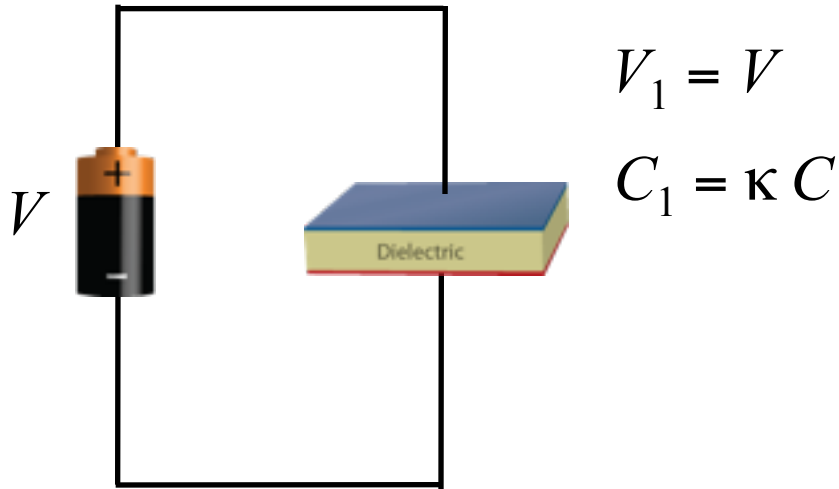If connected to a battery V stays constant




If isolated then total Q stays constant

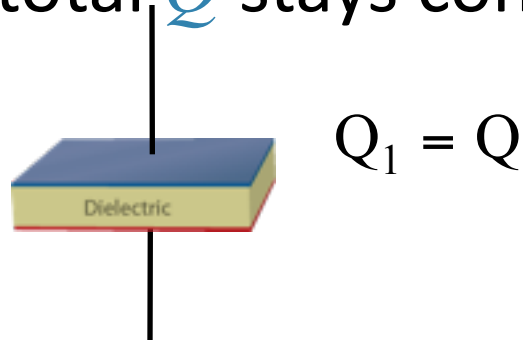


Messing with Capacitors

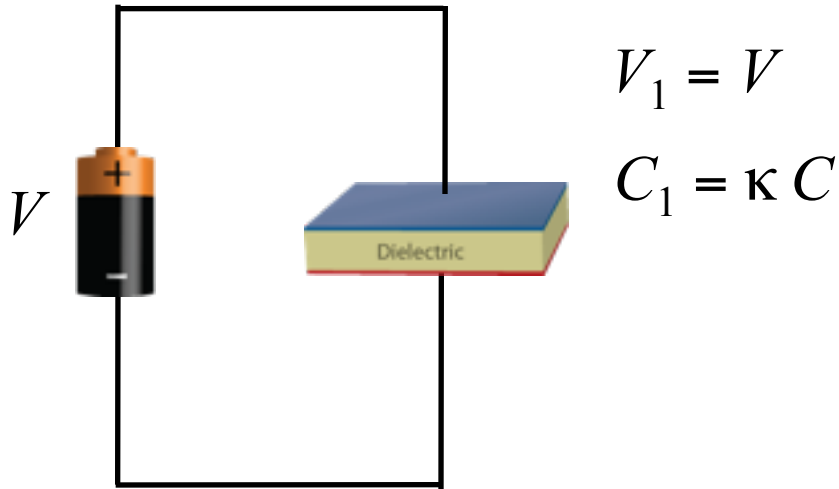If connected to a battery V stays constant




If isolated then total Q stays constant

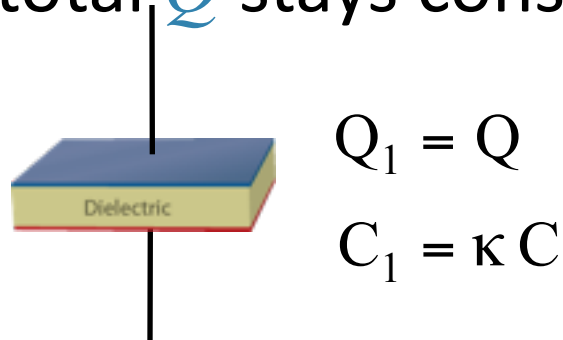

Messing with Capacitors

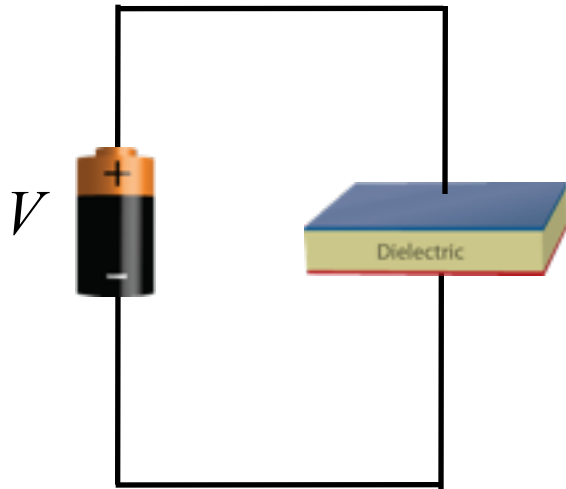If connected to a battery V stays constant



$$V_1 = V$$


$$C_1 = \kappa C$$



$$Q_1 = C_1 V_1$$

$$= \kappa C V = \kappa Q$$

If isolated then total Q stays constant

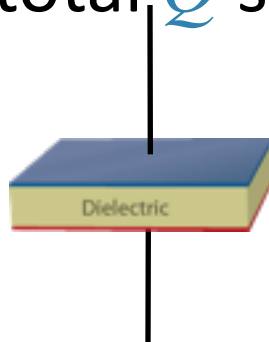


$$Q_1 = Q$$

$$C_1 = \kappa C$$


Messing with Capacitors

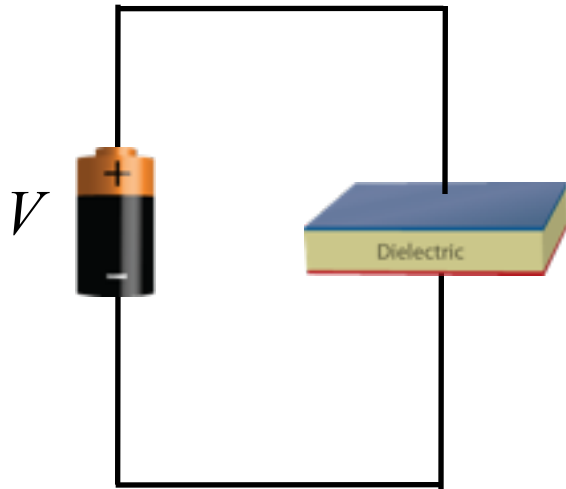If connected to a battery V stays constant



$$\begin{array}{l} V_1 = V \\ C_1 = \kappa C \end{array} \left. \vphantom{\begin{array}{l} V_1 = V \\ C_1 = \kappa C \end{array}} \right\} \rightarrow \begin{array}{l} Q_1 = C_1 V_1 \\ = \kappa C V = \kappa Q \end{array}$$

If isolated then total Q stays constant

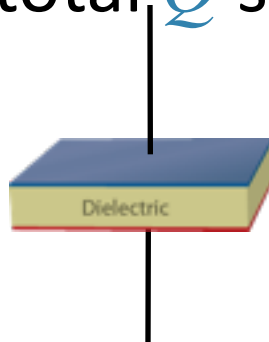


$$\begin{array}{l} Q_1 = Q \\ C_1 = \kappa C \end{array} \left. \vphantom{\begin{array}{l} Q_1 = Q \\ C_1 = \kappa C \end{array}} \right\} \rightarrow \begin{array}{l} V_1 = Q_1 / C_1 \\ = Q / \kappa C = V / \kappa \end{array}$$

CheckPoint: Capacitors and Dielectrics 1

Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric.


Compare the voltages of the two capacitors.

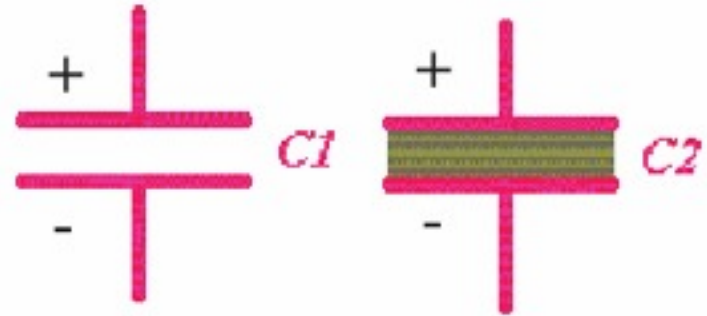- A. $V_1 > V_2$
- B. $V_1 = V_2$
- C. $V_1 < V_2$



CheckPoint: Capacitors and Dielectrics 1

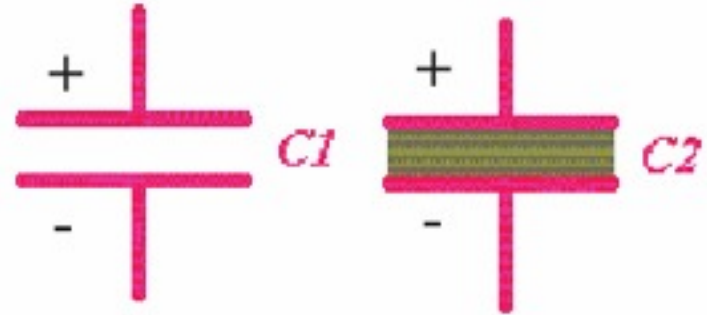Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric.



Compare the voltages of the two capacitors.

- A. $V_1 > V_2$
- B. $V_1 = V_2$
- C. $V_1 < V_2$

“The electric field decreases on the second due to the dielectric, so its voltage must decrease.”


“The little brown thing is stopping the pikachus from reaching the other side.”

“ Dielectrics don't change voltages. ”

“Capacitance lowers in case 2, meaning V increases in case 2. ”

CheckPoint: Capacitors and Dielectrics 1

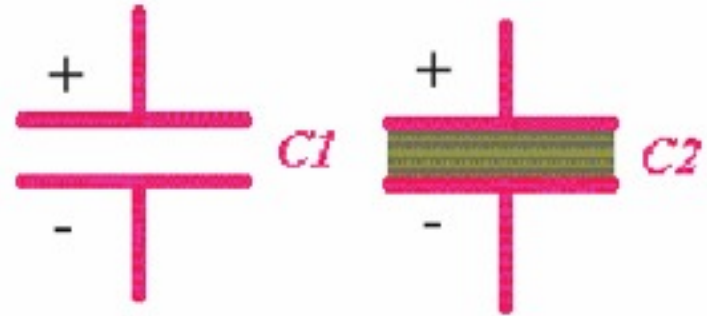Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric.



Compare the voltages of the two capacitors.


- A. $V_1 > V_2$
- B. $V_1 = V_2$
- C. $V_1 < V_2$

“The electric field decreases on the second due to the dielectric, so its voltage must decrease.”

“The little brown thing is stopping the pikachus from reaching the other side.”

“Dielectrics don't change voltages.”

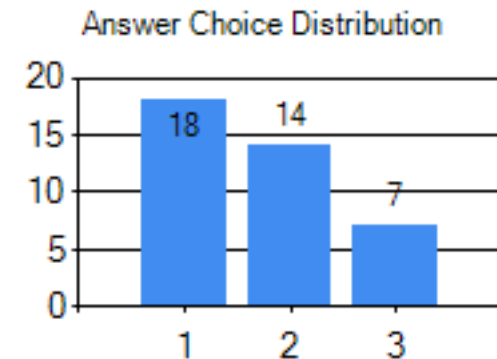
“Capacitance lowers in case 2, meaning V increases in case 2.”



CheckPoint: Capacitors and Dielectrics 1

Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric.

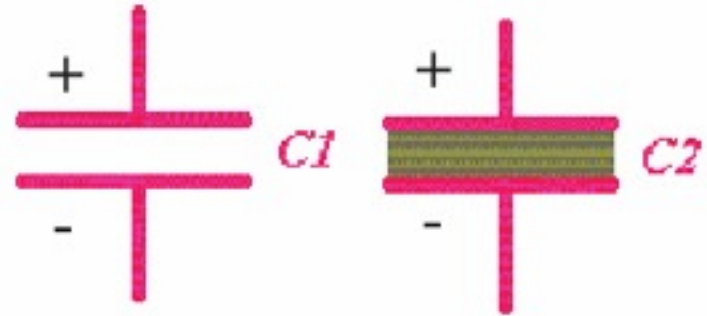Compare the voltages of the two capacitors.



A. $V_1 > V_2$

B. $V_1 = V_2$


C. $V_1 < V_2$

“The electric field decreases on the second due to the dielectric, so its voltage must decrease.”

“The little brown thing is stopping the pikachus from reaching the other side.”

“Dielectrics don't change voltages.”


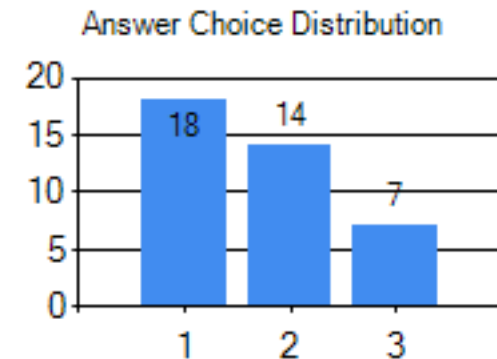
“Capacitance lowers in case 2, meaning V increases in case 2.”



Clicker Question: Messing with Capacitors



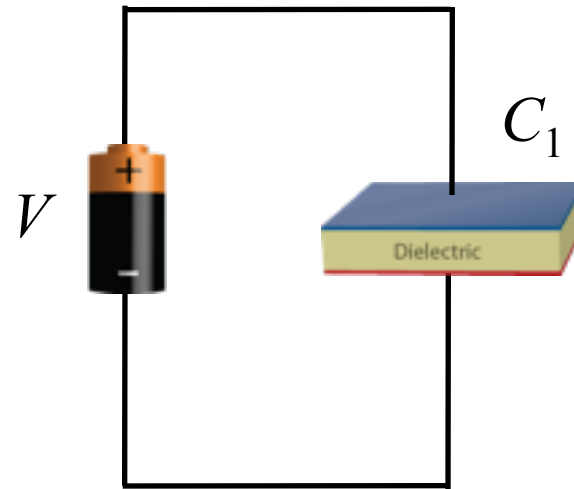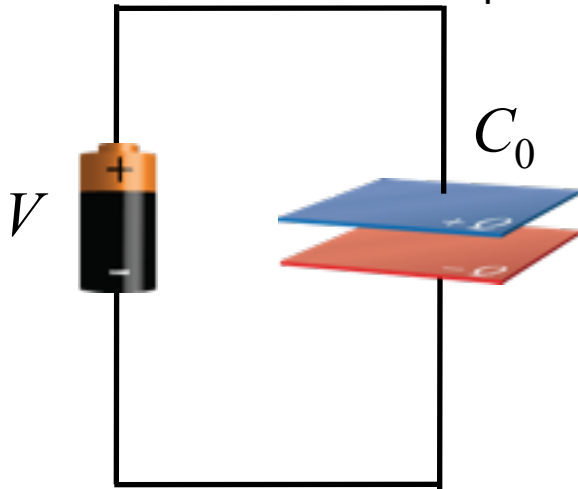Two identical parallel plate capacitors are connected to identical batteries. Then a dielectric is inserted between the plates of capacitor C_1 . Compare the energy stored in the two capacitors.



A) $U_1 < U_0$



B) $U_0 = U_1$

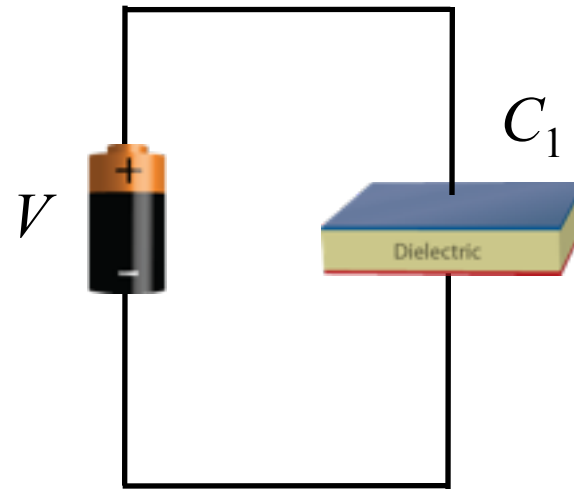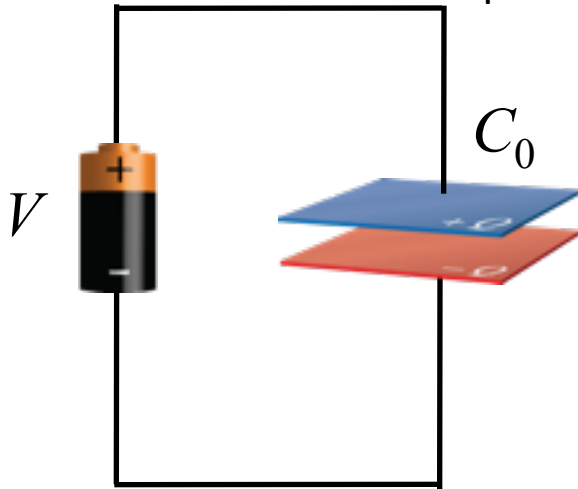C) $U_1 > U_0$

Clicker Question: Messing with Capacitors



Two identical parallel plate capacitors are connected to identical batteries. Then a dielectric is inserted between the plates of capacitor C_1 . Compare the energy stored in the two capacitors.



A) $U_1 < U_0$



B) $U_0 = U_1$

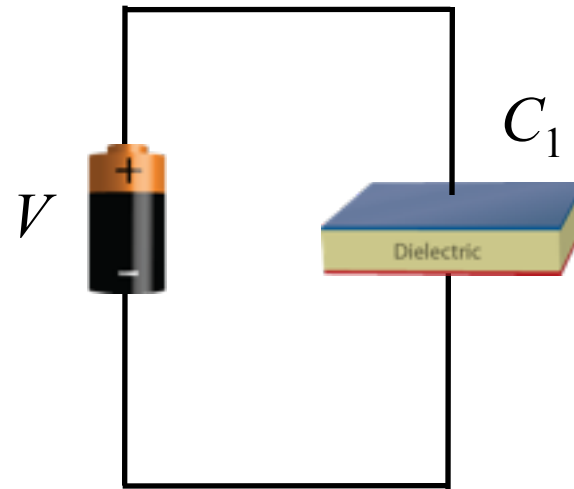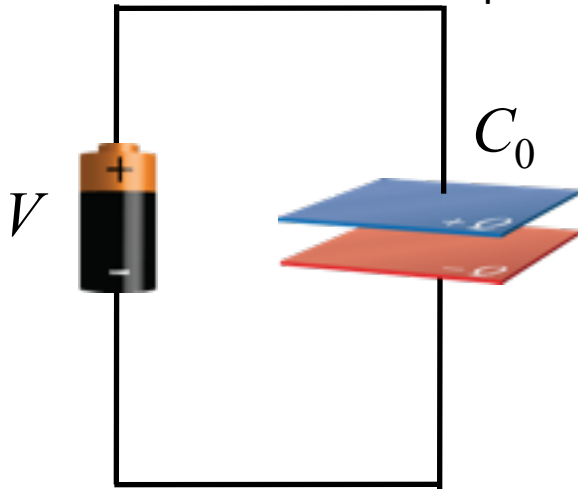C) $U_1 > U_0$

Clicker Question: Messing with Capacitors



Two identical parallel plate capacitors are connected to identical batteries. Then a dielectric is inserted between the plates of capacitor C_1 . Compare the energy stored in the two capacitors.



A) $U_1 < U_0$

B) $U_0 = U_1$



C) $U_1 > U_0$

Compare using $U = \frac{1}{2}CV^2$

Clicker Question: Messing with Capacitors



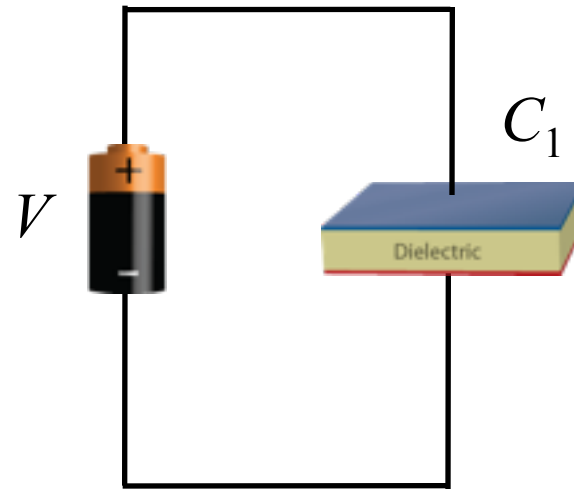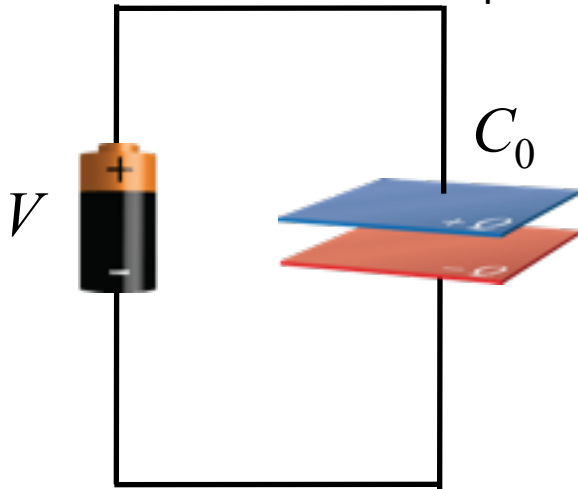Two identical parallel plate capacitors are connected to identical batteries. Then a dielectric is inserted between the plates of capacitor C_1 . Compare the energy stored in the two capacitors.



A) $U_1 < U_0$

B) $U_0 = U_1$

C) $U_1 > U_0$



Compare using $U = \frac{1}{2}CV^2$

$$U_1/U_0 = \kappa$$

Clicker Question: Messing with Capacitors



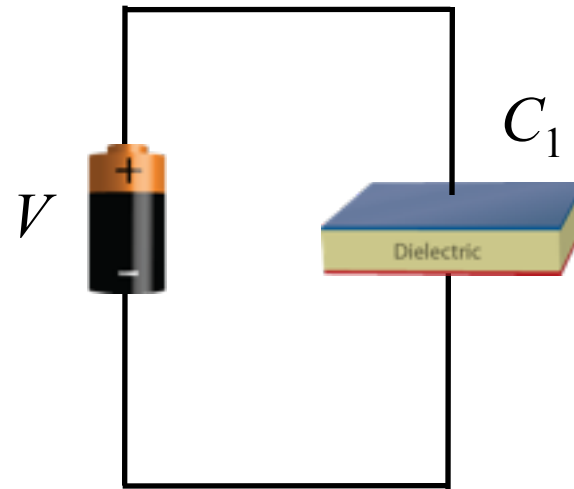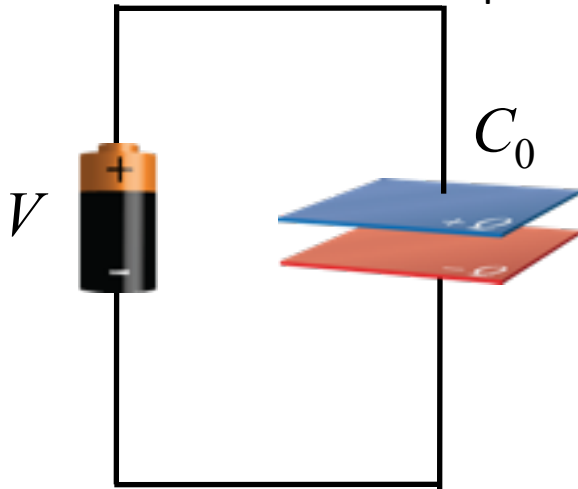Two identical parallel plate capacitors are connected to identical batteries. Then a dielectric is inserted between the plates of capacitor C_1 . Compare the energy stored in the two capacitors.



A) $U_1 < U_0$

B) $U_0 = U_1$

C) $U_1 > U_0$

Compare using $U = \frac{1}{2}CV^2$

$$U_1/U_0 = \kappa$$


→ Potential Energy goes UP

CheckPoint: Capacitors and Dielectrics 2

Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric.

Compare the potential energy stored by the two capacitors.

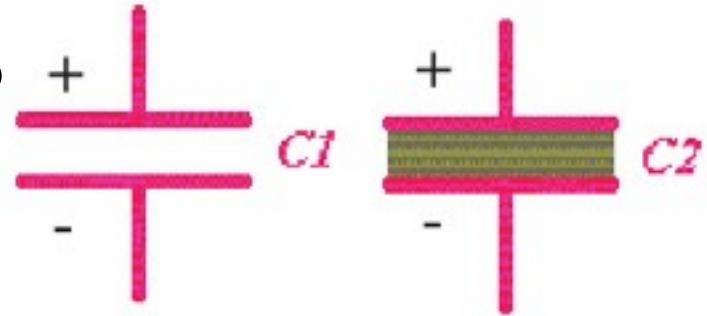- A. $U_1 > U_2$
- B. $U_1 = U_2$
- C. $U_1 < U_2$



CheckPoint: Capacitors and Dielectrics 2


Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric.

Compare the potential energy stored by the two capacitors.

A. $U_1 > U_2$

B. $U_1 = U_2$

C. $U_1 < U_2$

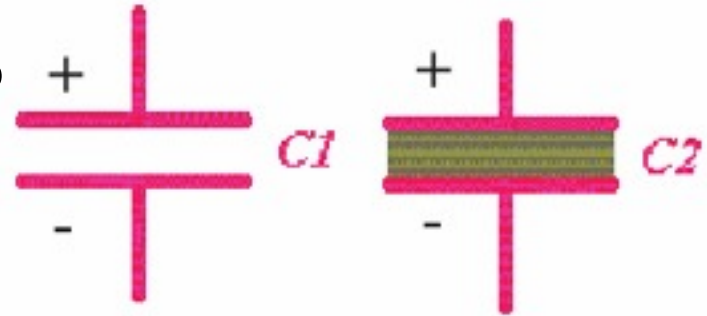

CheckPoint: Capacitors and Dielectrics 2


Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric.

Compare the potential energy stored by the two capacitors.

A. $U_1 > U_2$

B. $U_1 = U_2$

C. $U_1 < U_2$

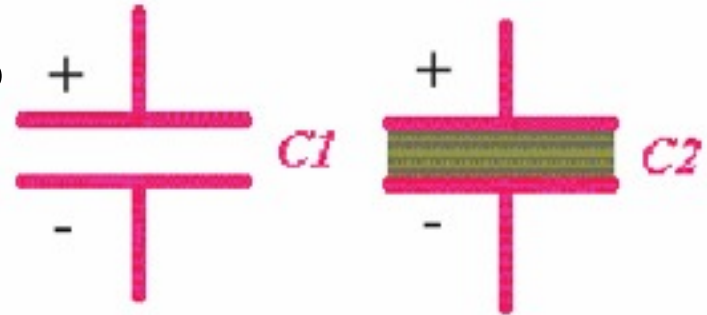

“If the electric field goes down, then so does the potential energy of the second system..”

“Dielectrics don't affect potential.”

“ $U = QV$. Since voltage remains constant and charge increases, potential energy must also increase.”

CheckPoint: Capacitors and Dielectrics 2


Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric.

Compare the potential energy stored by the two capacitors.

A. $U_1 > U_2$

B. $U_1 = U_2$


C. $U_1 < U_2$

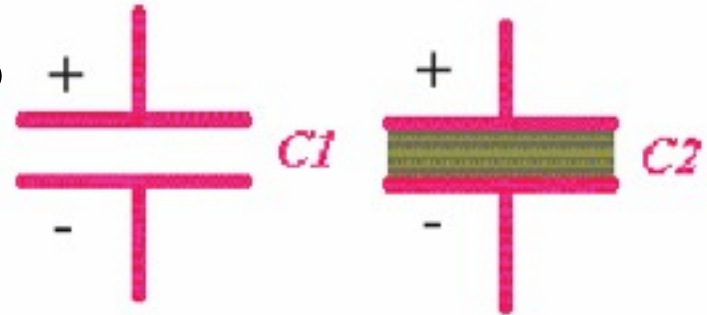

“If the electric field goes down, then so does the potential energy of the second system..”


“Dielectrics don't affect potential.”

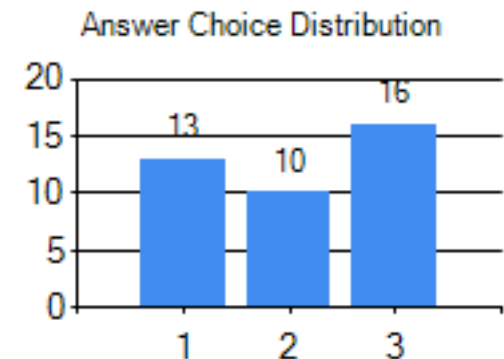“ $U = QV$. Since voltage remains constant and charge increases, potential energy must also increase.”



CheckPoint: Capacitors and Dielectrics 3

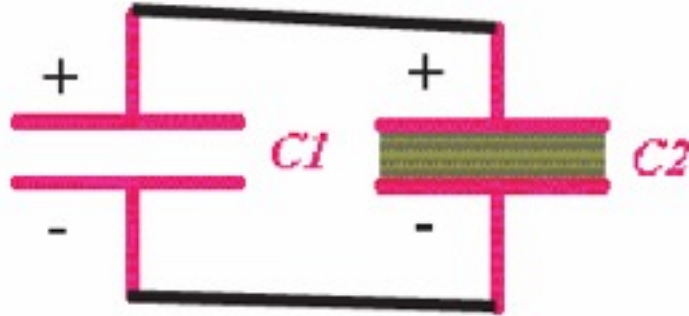
The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?




- The charges will flow so that the charge on C1 will become equal to the charge on C2.
- The charges will flow so that the energy stored in C1 will become equal to the energy stored in C2
- The charges will flow so that the potential difference across C1 will become the same as the potential difference across C2.
- No charges will flow. The charge on the capacitors will remain what it was before they were connected.

CheckPoint: Capacitors and Dielectrics 3

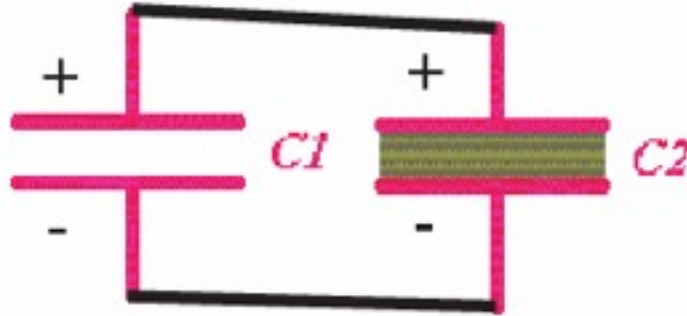The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?




- The charges will flow so that the charge on C1 will become equal to the charge on C2.
- The charges will flow so that the energy stored in C1 will become equal to the energy stored in C2
- The charges will flow so that the potential difference across C1 will become the same as the potential difference across C2.
- No charges will flow. The charge on the capacitors will remain what it was before they were connected.

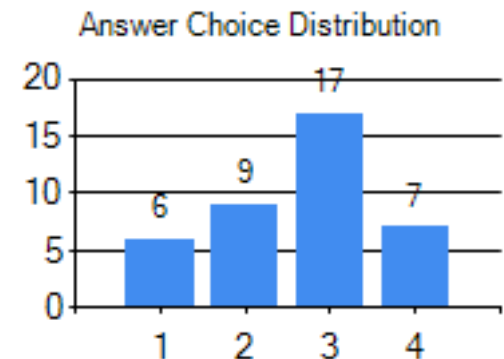


CheckPoint: Capacitors and Dielectrics 3

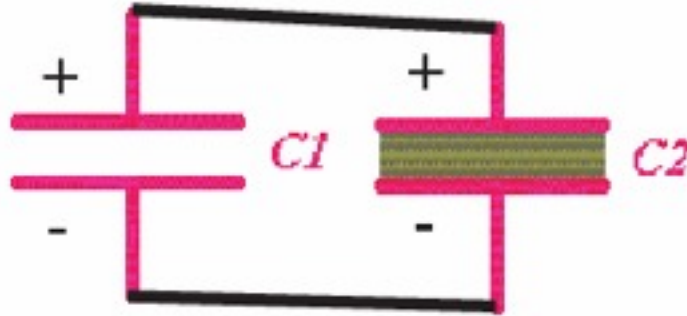The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?




- The charges will flow so that the charge on C1 will become equal to the charge on C2.
- The charges will flow so that the energy stored in C1 will become equal to the energy stored in C2
- The charges will flow so that the potential difference across C1 will become the same as the potential difference across C2.
- No charges will flow. The charge on the capacitors will remain what it was before they were connected.

Q:
$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

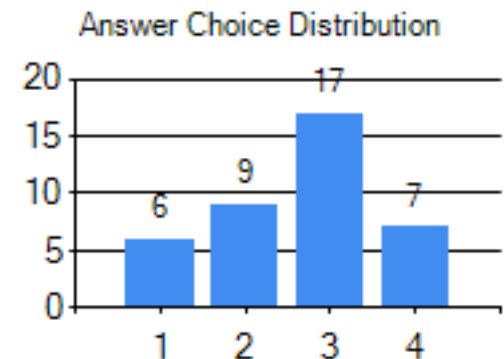


CheckPoint: Capacitors and Dielectrics 3

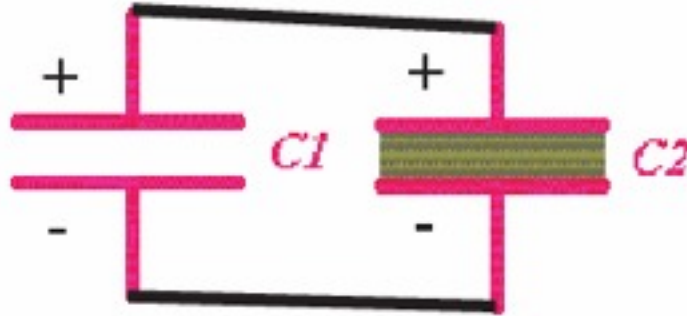The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?




- The charges will flow so that the charge on C1 will become equal to the charge on C2.
- The charges will flow so that the energy stored in C1 will become equal to the energy stored in C2
- The charges will flow so that the potential difference across C1 will become the same as the potential difference across C2.
- No charges will flow. The charge on the capacitors will remain what it was before they were connected.

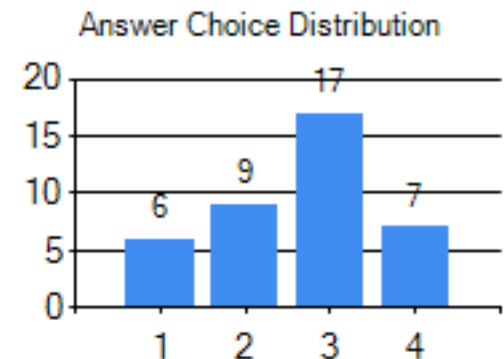Q: $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \rightarrow Q_1 = \frac{C_1}{C_2} Q_2$



CheckPoint: Capacitors and Dielectrics 3

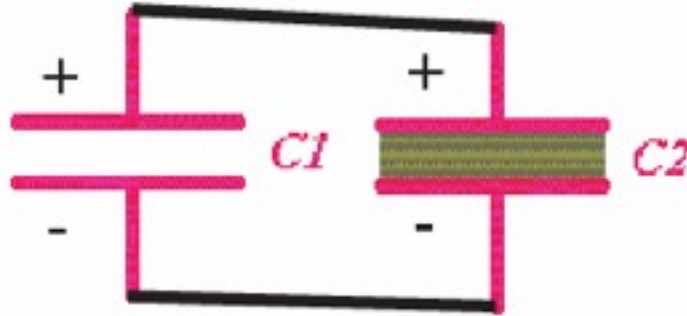
The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?



- The charges will flow so that the charge on C1 will become equal to the charge on C2.
- The charges will flow so that the energy stored in C1 will become equal to the energy stored in C2
- The charges will flow so that the potential difference across C1 will become the same as the potential difference across C2.
- No charges will flow. The charge on the capacitors will remain what it was before they were connected.


Q: $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \rightarrow Q_1 = \frac{C_1}{C_2} Q_2$

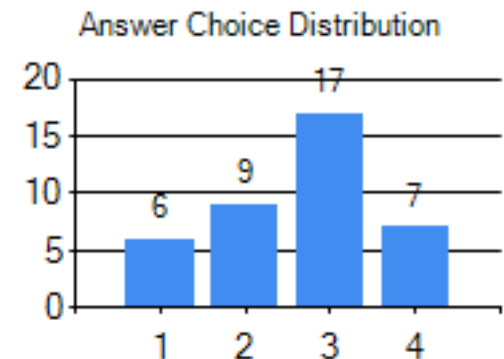U: $U_1 = \frac{1}{2} C_1 V^2$
 $U_2 = \frac{1}{2} C_2 V^2$



CheckPoint: Capacitors and Dielectrics 3

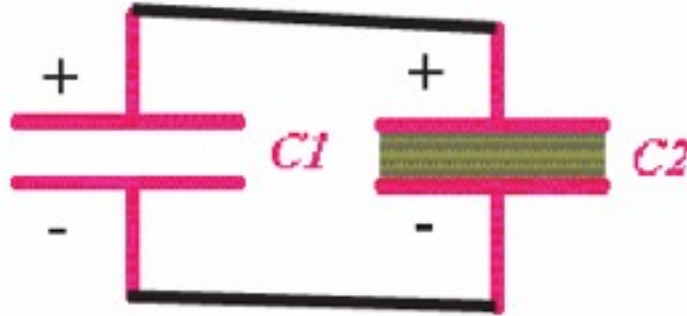
The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?



- The charges will flow so that the charge on C1 will become equal to the charge on C2.
- The charges will flow so that the energy stored in C1 will become equal to the energy stored in C2
- The charges will flow so that the potential difference across C1 will become the same as the potential difference across C2.
- No charges will flow. The charge on the capacitors will remain what it was before they were connected.


Q: $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \rightarrow Q_1 = \frac{C_1}{C_2} Q_2$

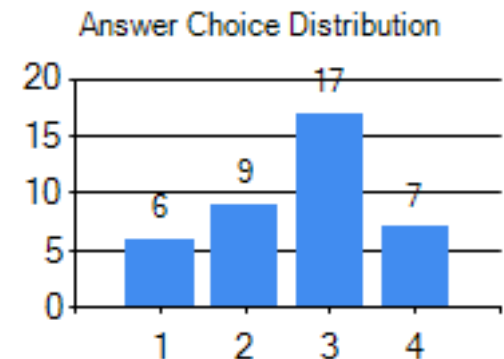U: $U_1 = \frac{1}{2} C_1 V^2$
 $U_2 = \frac{1}{2} C_2 V^2 \rightarrow U_1 = \frac{C_1}{C_2} U_2$



CheckPoint: Capacitors and Dielectrics 3

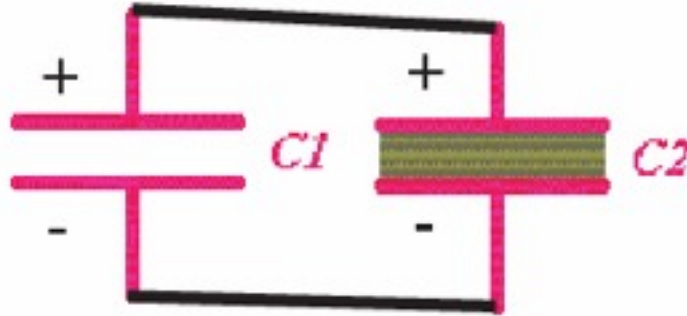The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?




V must be the same !

- The charges will flow so that the charge on C1 will become equal to the charge on C2.
- The charges will flow so that the energy stored in C1 will become equal to the energy stored in C2
- The charges will flow so that the potential difference across C1 will become the same as the potential difference across C2.
- No charges will flow. The charge on the capacitors will remain what it was before they were connected.


$$\text{Q: } \frac{Q_1}{C_1} = \frac{Q_2}{C_2} \quad \longrightarrow \quad Q_1 = \frac{C_1}{C_2} Q_2$$
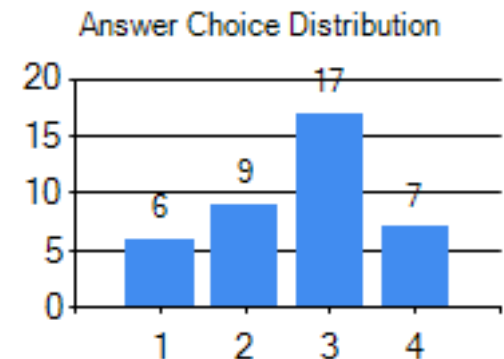
$$\text{U: } \begin{aligned} U_1 &= \frac{1}{2} C_1 V^2 \\ U_2 &= \frac{1}{2} C_2 V^2 \end{aligned} \quad \longrightarrow \quad U_1 = \frac{C_1}{C_2} U_2$$



CheckPoint: Capacitors and Dielectrics 3

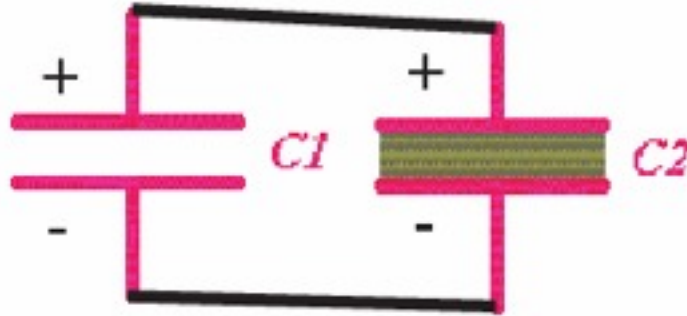The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?




V must be the same !


- The charges will flow so that the charge on C1 will become equal to the charge on C2.
- The charges will flow so that the energy stored in C1 will become equal to the energy stored in C2
- The charges will flow so that the potential difference across C1 will become the same as the potential difference across C2.
- No charges will flow. The charge on the capacitors will remain what it was before they were connected.

Q: $\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \rightarrow Q_1 = \frac{C_1}{C_2} Q_2$

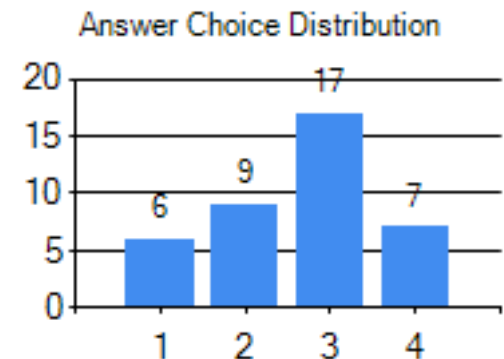U: $U_1 = \frac{1}{2} C_1 V^2$
 $U_2 = \frac{1}{2} C_2 V^2 \rightarrow U_1 = \frac{C_1}{C_2} U_2$



Calculation

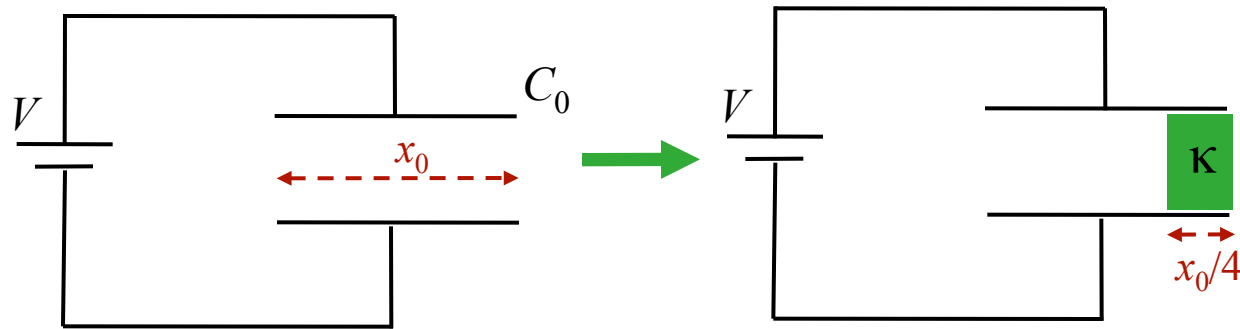


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Conceptual Analysis:

What is Q_f , the final charge on the capacitor?

Calculation

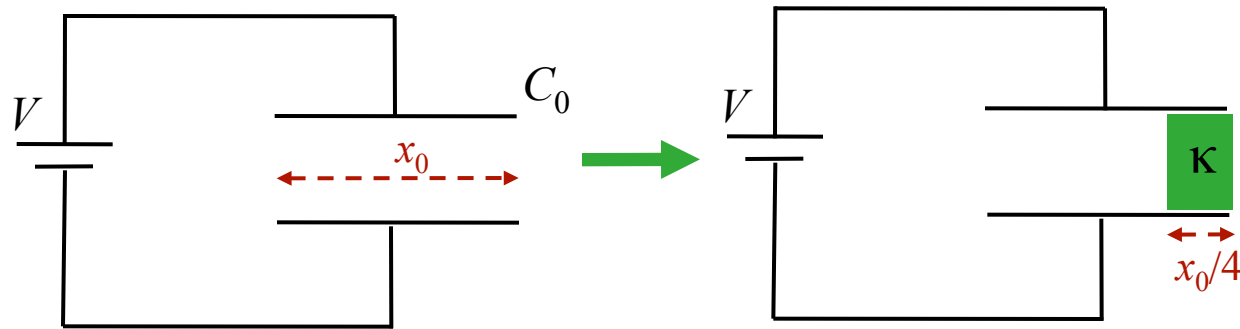

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .


A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Conceptual Analysis:

$$C \equiv \frac{Q}{V}$$

What is Q_f , the final charge on the capacitor?

Calculation

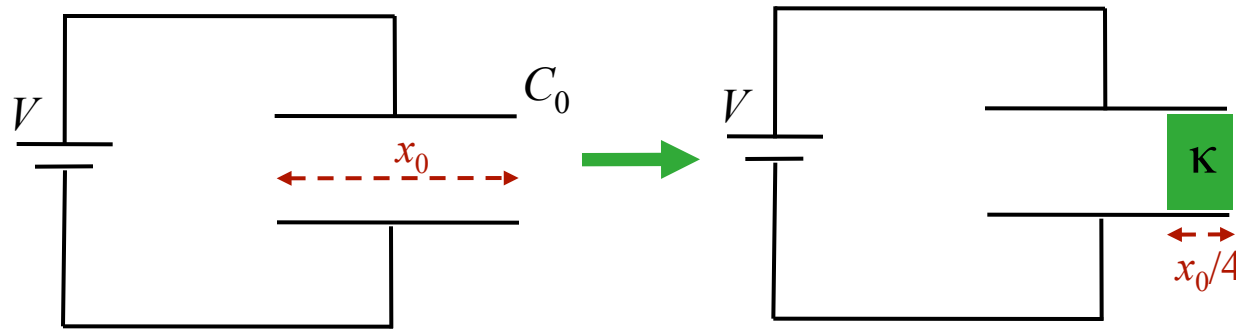

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Conceptual Analysis:


$$C \equiv \frac{Q}{V}$$

What changes when the dielectric added?

What is Q_f , the final charge on the capacitor?

- A) Only C B) only Q C) only V D) C and Q E) V and Q

Calculation

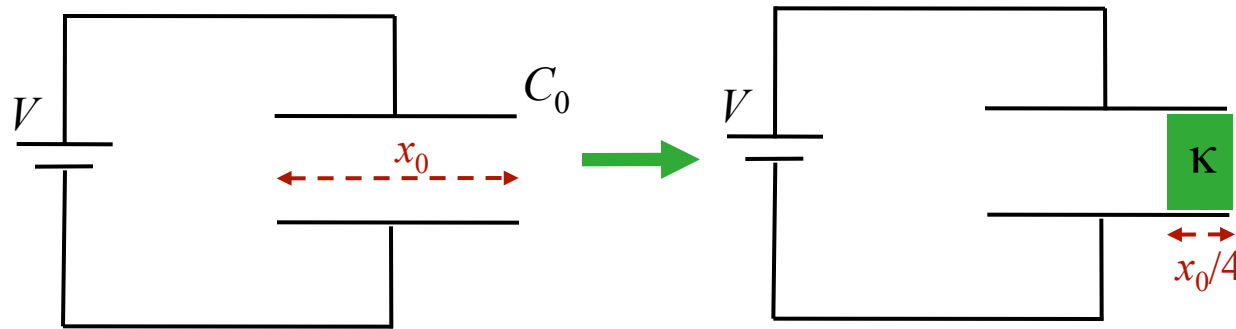

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Conceptual Analysis:


$$C \equiv \frac{Q}{V}$$

What changes when the dielectric added?

- A) Only C B) only Q C) only V **D) C and Q** E) V and Q

What is Q_f , the final charge on the capacitor?

Calculation

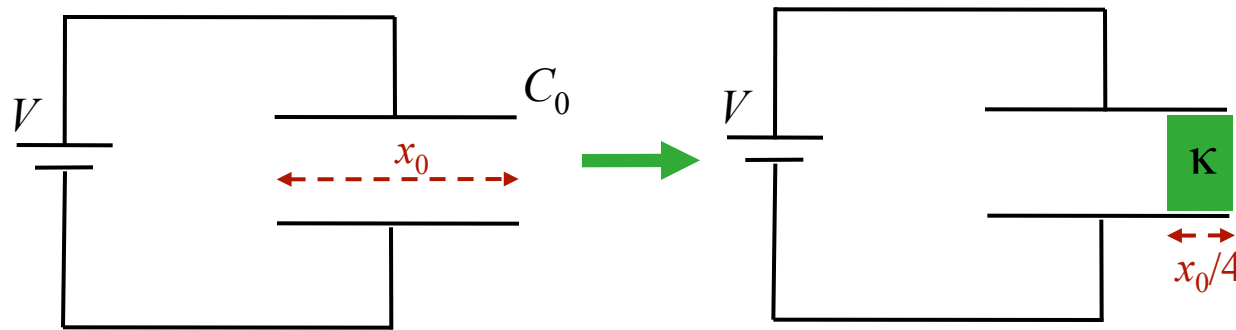

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Conceptual Analysis:

$$C \equiv \frac{Q}{V}$$

What changes when the dielectric added?

- A) Only C B) only Q C) only V **D) C and Q** E) V and Q


What is Q_f , the final charge on the capacitor?

Adding dielectric changes the physical capacitor



C changes

Calculation

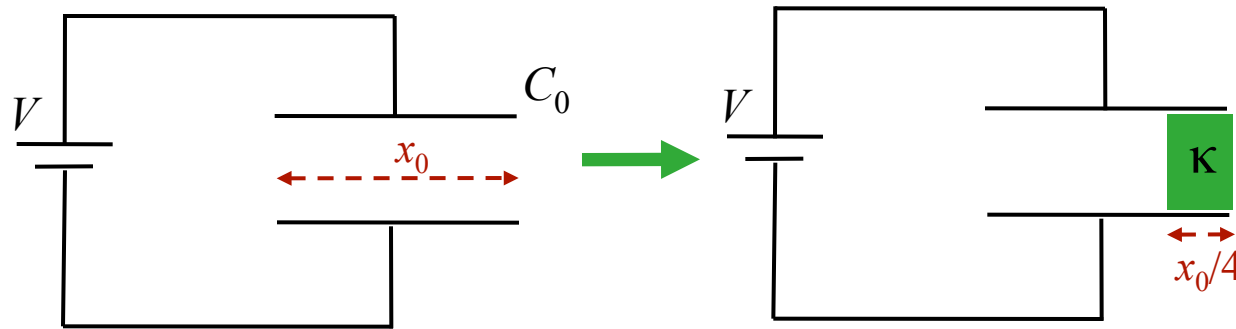

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Conceptual Analysis:

$$C \equiv \frac{Q}{V}$$

What changes when the dielectric added?

- A) Only C B) only Q C) only V **D) C and Q** E) V and Q

Adding dielectric changes the physical capacitor




C changes

V does not change and C changes



Q changes

Calculation

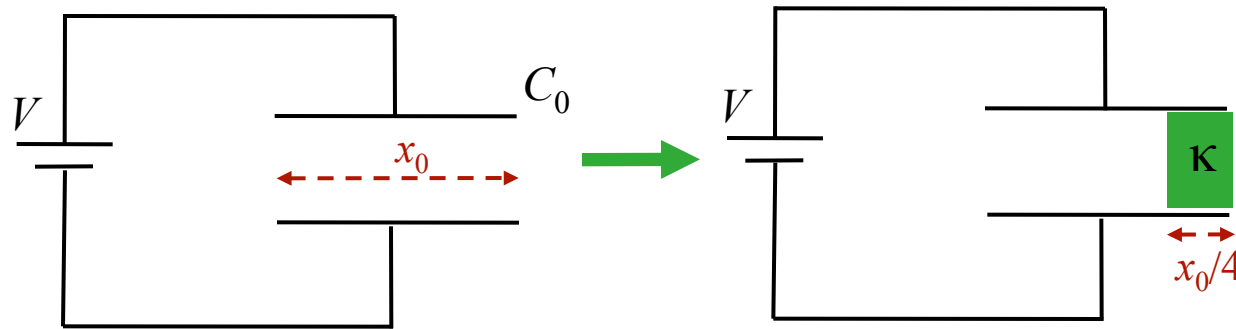


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

Calculation

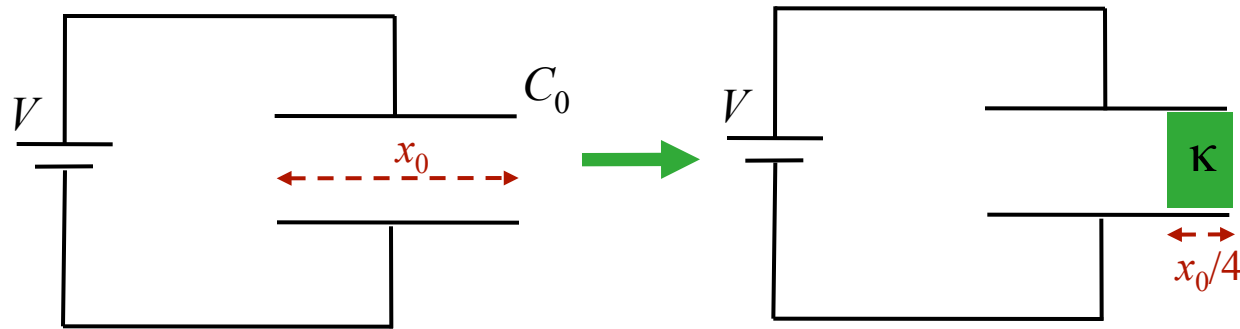


Strategic Analysis:

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

Calculation

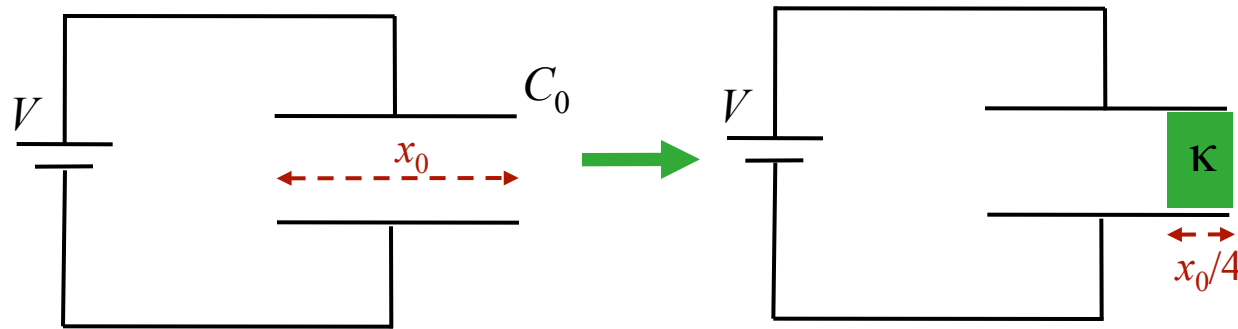

Strategic Analysis:


- Calculate new capacitance C

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

Calculation

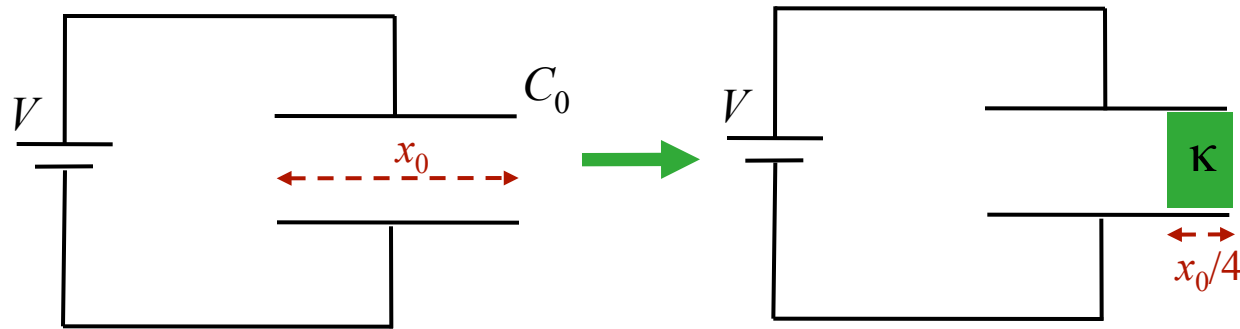

Strategic Analysis:


- Calculate new capacitance C
- Apply definition of capacitance to determine Q

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

Calculation

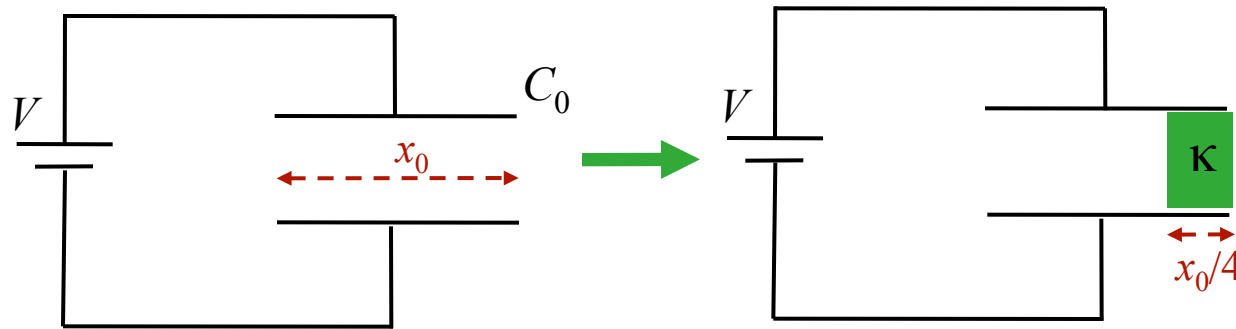

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Strategic Analysis:


- Calculate new capacitance C
- Apply definition of capacitance to determine Q

To calculate C , let's first look at:



What is Q_f , the final charge on the capacitor?

Calculation

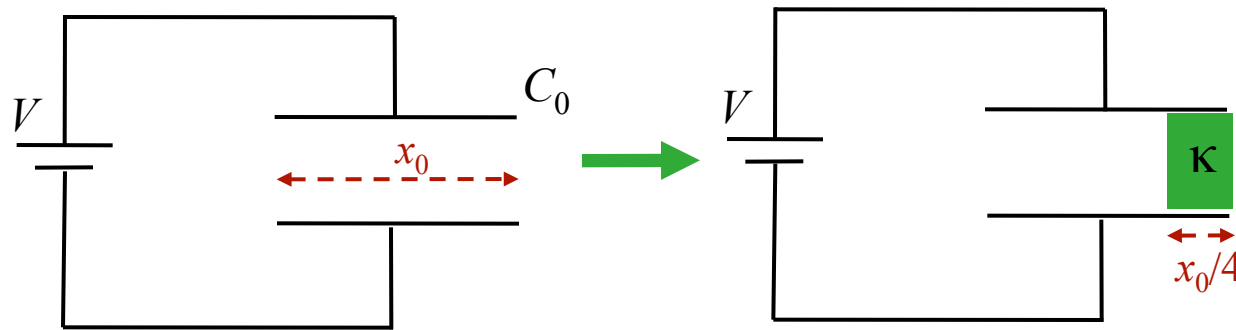

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Strategic Analysis:

- Calculate new capacitance C
- Apply definition of capacitance to determine Q


To calculate C , let's first look at:



- A) $V_{left} < V_{right}$ B) $V_{left} = V_{right}$ C) $V_{left} > V_{right}$

What is Q_f , the final charge on the capacitor?

Calculation

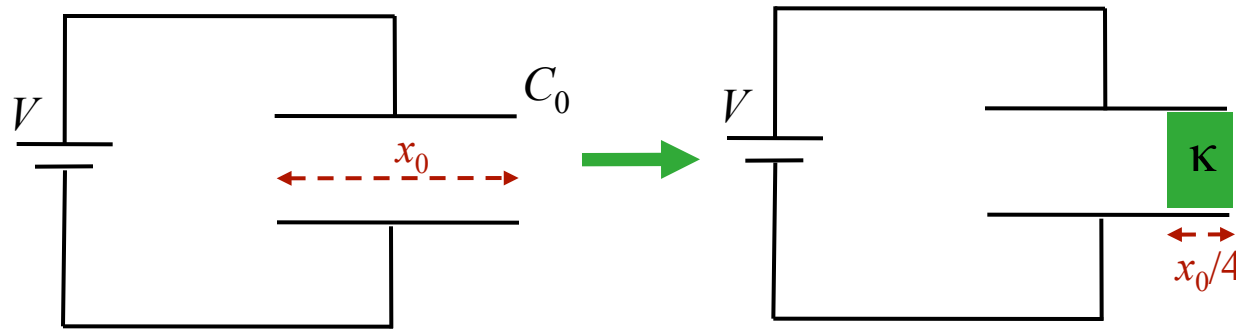

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Strategic Analysis:

- Calculate new capacitance C
- Apply definition of capacitance to determine Q

To calculate C , let's first look at:




A) $V_{left} < V_{right}$

B) $V_{left} = V_{right}$

C) $V_{left} > V_{right}$

What is Q_f , the final charge on the capacitor?

Calculation

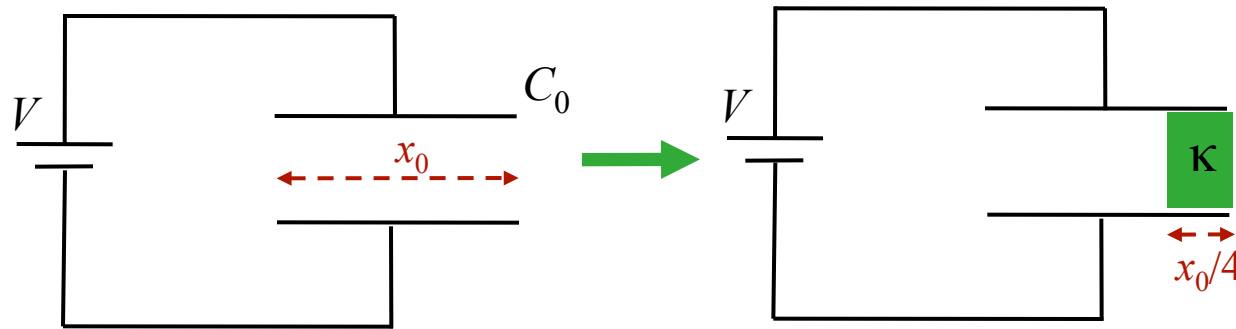

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Strategic Analysis:

- Calculate new capacitance C
- Apply definition of capacitance to determine Q

To calculate C , let's first look at:



A) $V_{left} < V_{right}$


B) $V_{left} = V_{right}$

C) $V_{left} > V_{right}$

What is Q_f , the final charge on the capacitor?

The conducting plate is an equipotential !

Calculation

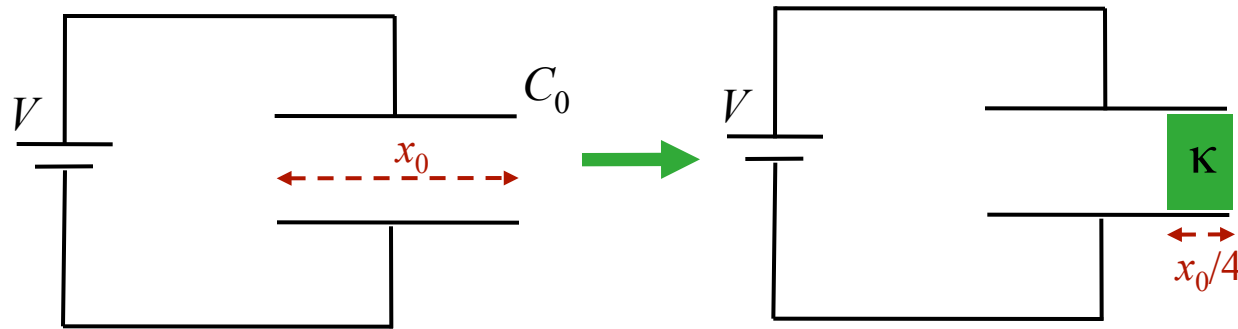


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

Calculation

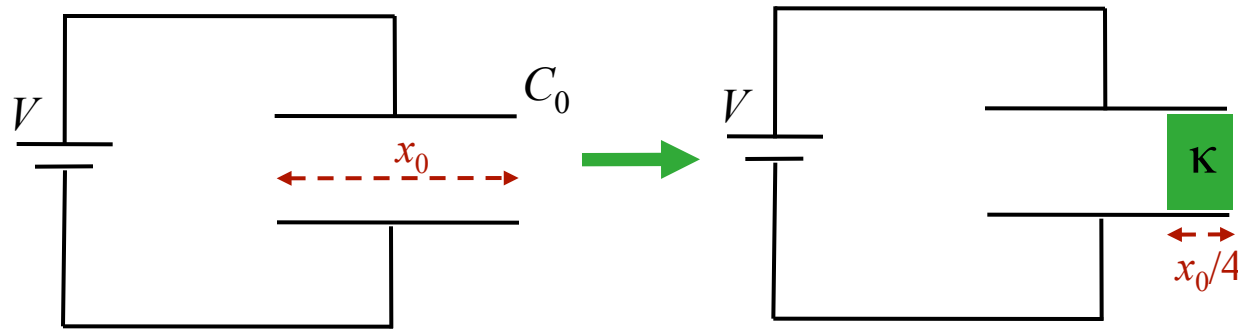


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel

What is Q_f , the final charge on the capacitor?

Calculation

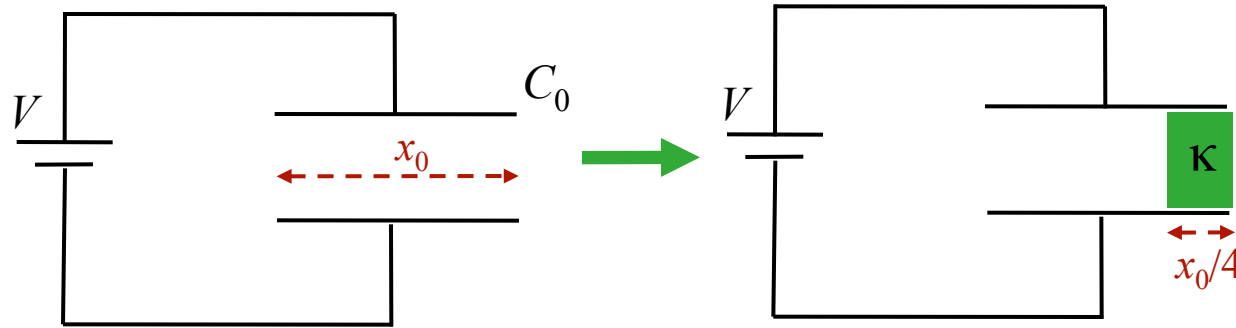


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .


A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel

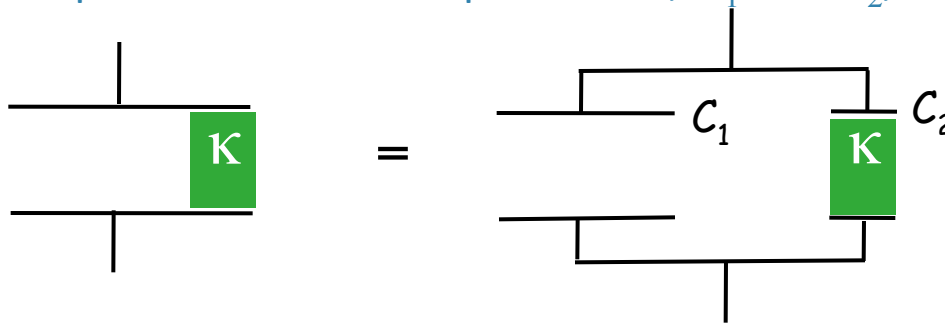What is Q_f , the final charge on the capacitor?



Calculation

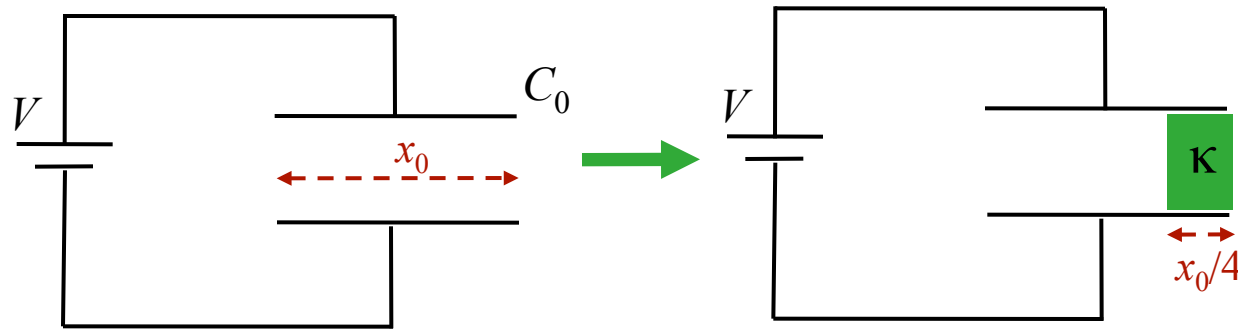


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel

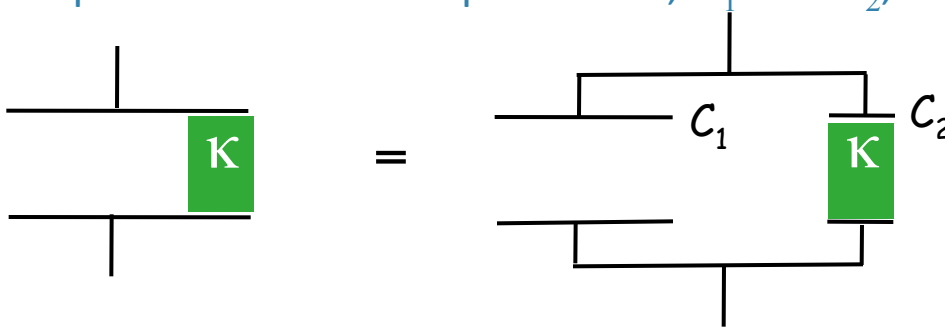
What is Q_f , the final charge on the capacitor?



What is C_1 ?

- A) $C_1 = C_0$ B) $C_1 = \frac{3}{4}C_0$ C) $C_1 = \frac{4}{3}C_0$ D) $C_1 = \frac{1}{4}C_0$

Calculation

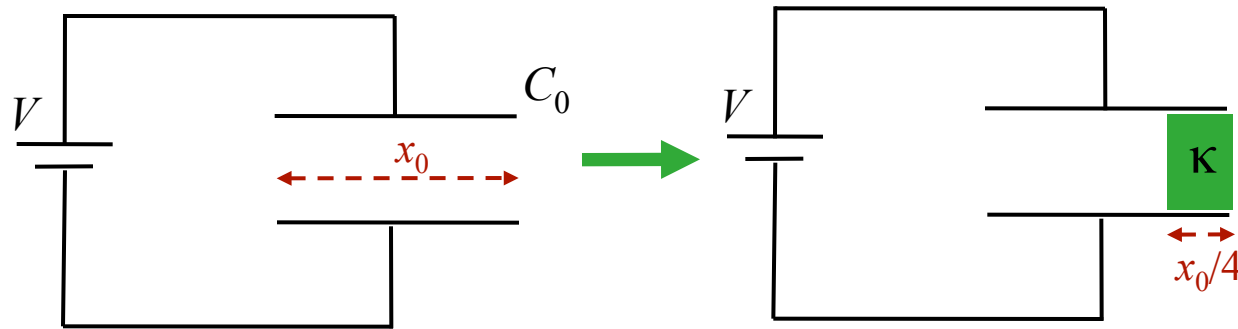


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel

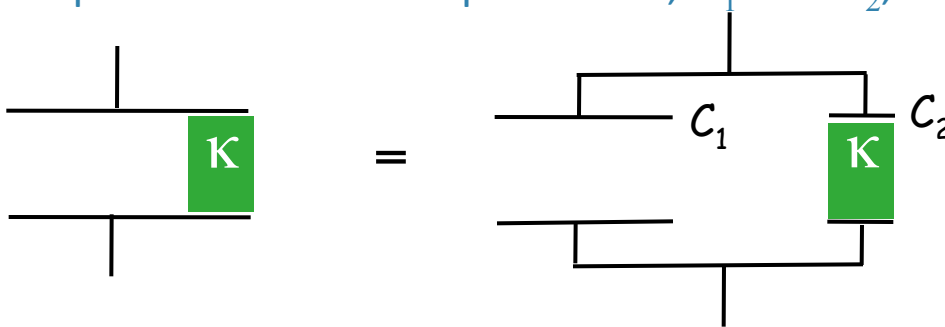
What is Q_f , the final charge on the capacitor?



What is C_1 ?

- A) $C_1 = C_0$ B) $C_1 = \frac{3}{4}C_0$ C) $C_1 = \frac{4}{3}C_0$ D) $C_1 = \frac{1}{4}C_0$

Calculation

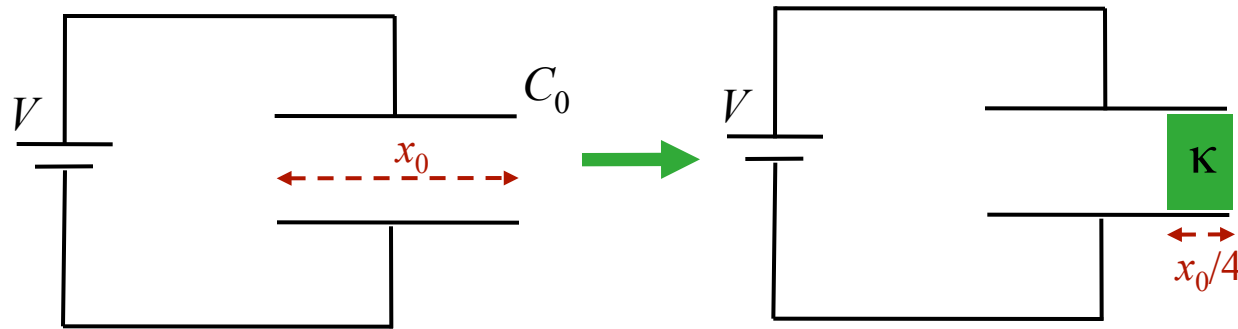


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel

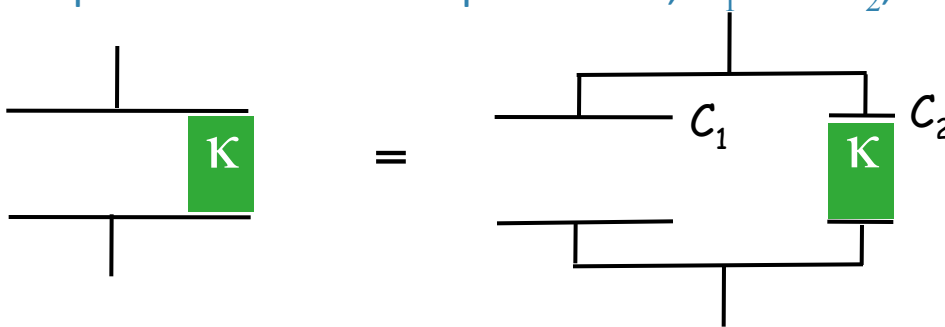What is Q_f , the final charge on the capacitor?




What is C_1 ?

- A) $C_1 = C_0$ B) $C_1 = \frac{3}{4}C_0$ C) $C_1 = \frac{4}{3}C_0$ D) $C_1 = \frac{1}{4}C_0$

In general. For parallel plate capacitor: $C = \epsilon_0 A/d$

Calculation

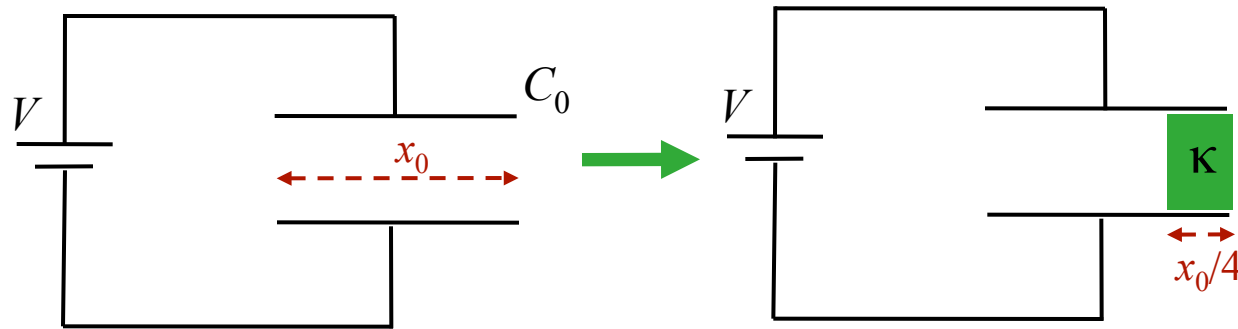


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel

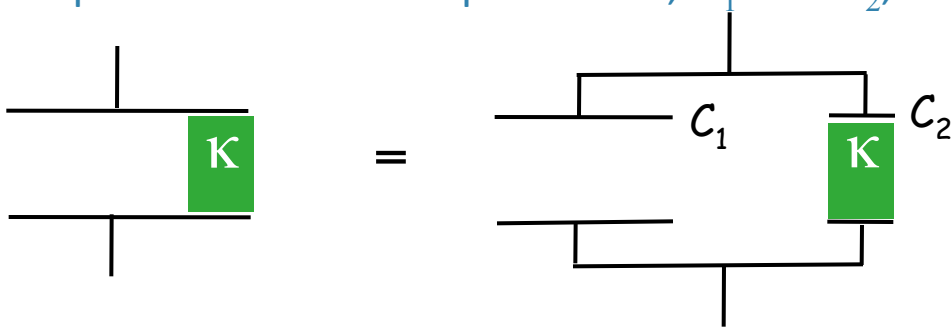What is Q_f , the final charge on the capacitor?



What is C_1 ?


- A) $C_1 = C_0$ B) $C_1 = \frac{3}{4}C_0$ C) $C_1 = \frac{4}{3}C_0$ D) $C_1 = \frac{1}{4}C_0$

In general. For parallel plate capacitor: $C = \epsilon_0 A/d$

$$A = \frac{3}{4}A_0$$

$$d = d_0$$

Calculation

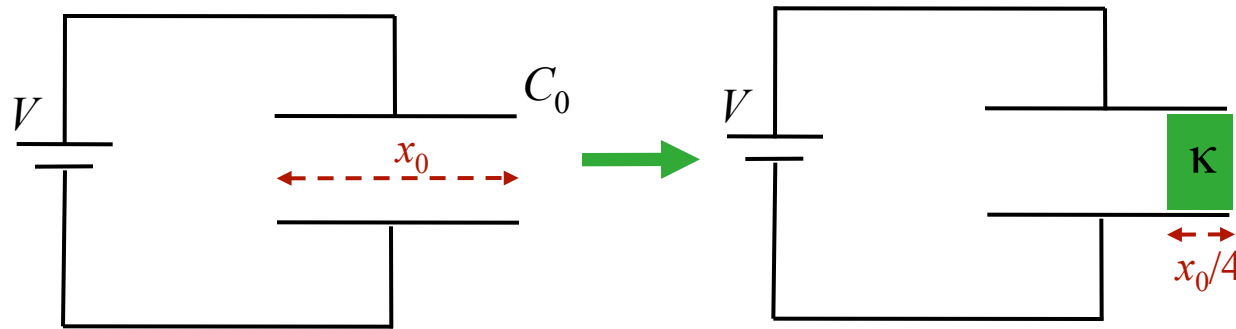


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel

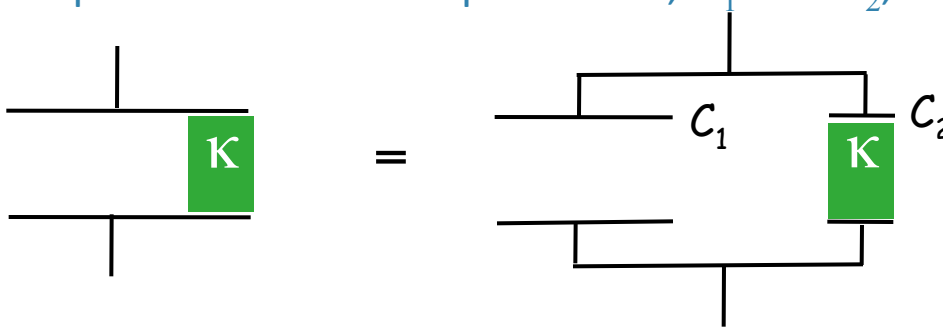What is Q_f , the final charge on the capacitor?




What is C_1 ?

- A) $C_1 = C_0$ B) $C_1 = \frac{3}{4}C_0$ C) $C_1 = \frac{4}{3}C_0$ D) $C_1 = \frac{1}{4}C_0$

In general. For parallel plate capacitor: $C = \epsilon_0 A/d$

$$\begin{matrix} A = \frac{3}{4}A_0 \\ d = d_0 \end{matrix} \quad \rightarrow \quad C_1 = \frac{3}{4}(\epsilon_0 A_0/d_0)$$

Calculation

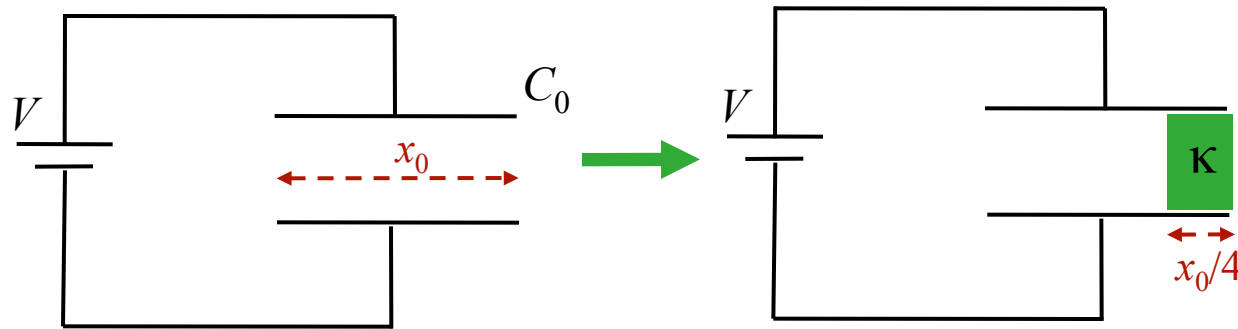


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel

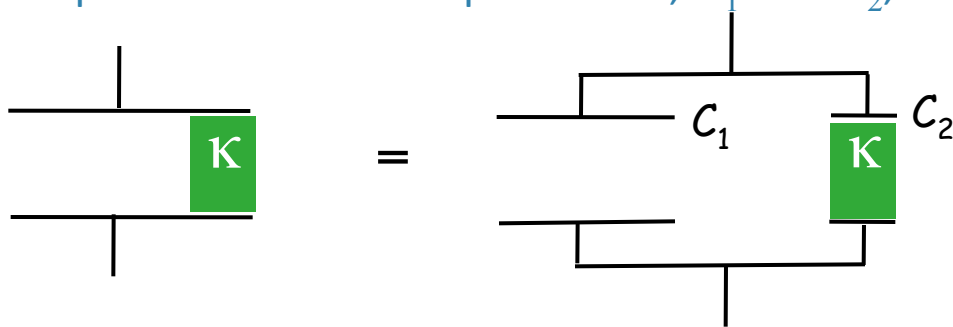What is Q_f , the final charge on the capacitor?




What is C_1 ?

- A) $C_1 = C_0$ B) $C_1 = \frac{3}{4}C_0$ C) $C_1 = \frac{4}{3}C_0$ D) $C_1 = \frac{1}{4}C_0$

In general. For parallel plate capacitor: $C = \epsilon_0 A/d$

$$\begin{array}{l} A = \frac{3}{4}A_0 \\ d = d_0 \end{array} \quad \rightarrow \quad C_1 = \frac{3}{4}(\epsilon_0 A_0/d_0) \quad \rightarrow \quad C_1 = \frac{3}{4}C_0$$

Calculation

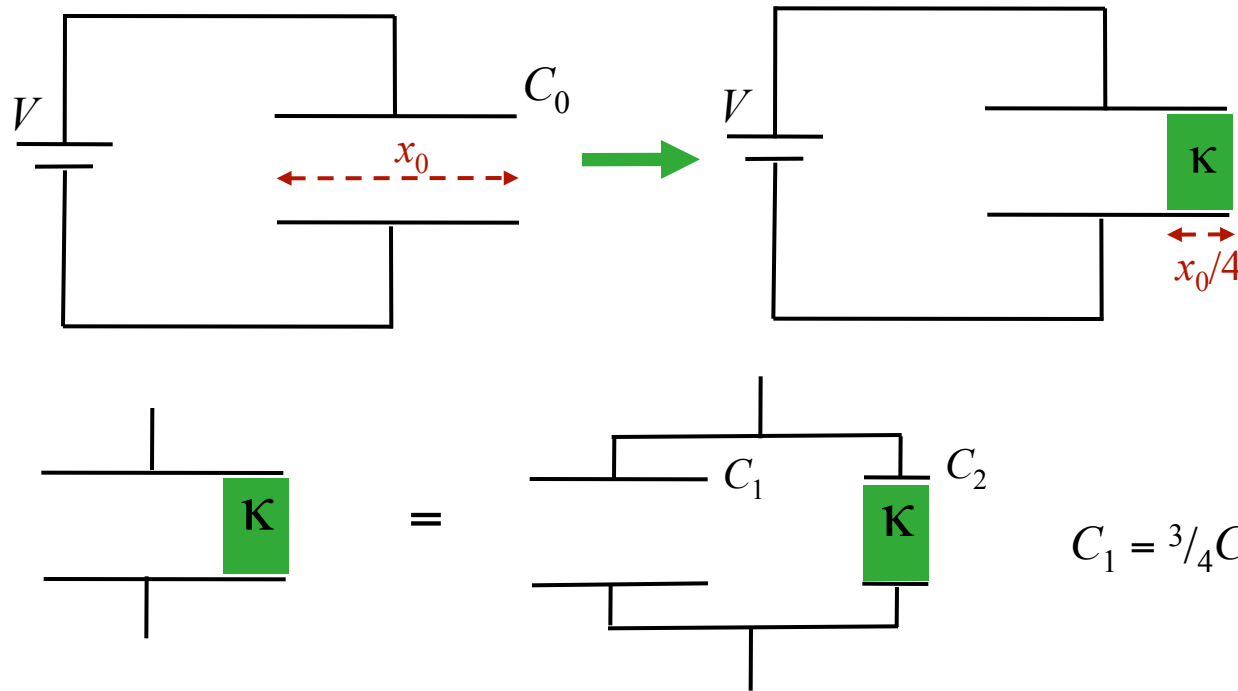


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

Calculation

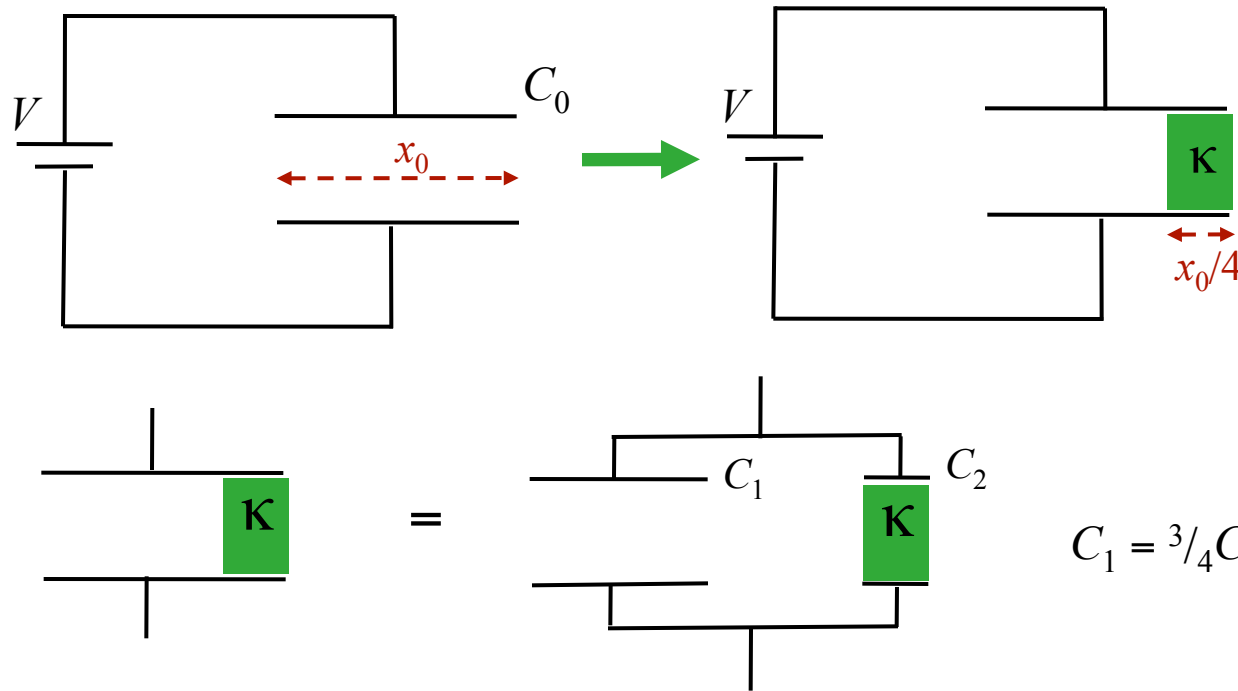

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

What is C_2 ?


A) $C_2 = \kappa C_0$

B) $C_2 = \frac{3}{4} \kappa C_0$

C) $C_2 = \frac{4}{3} \kappa C_0$

D) $C_2 = \frac{1}{4} \kappa C_0$

Calculation

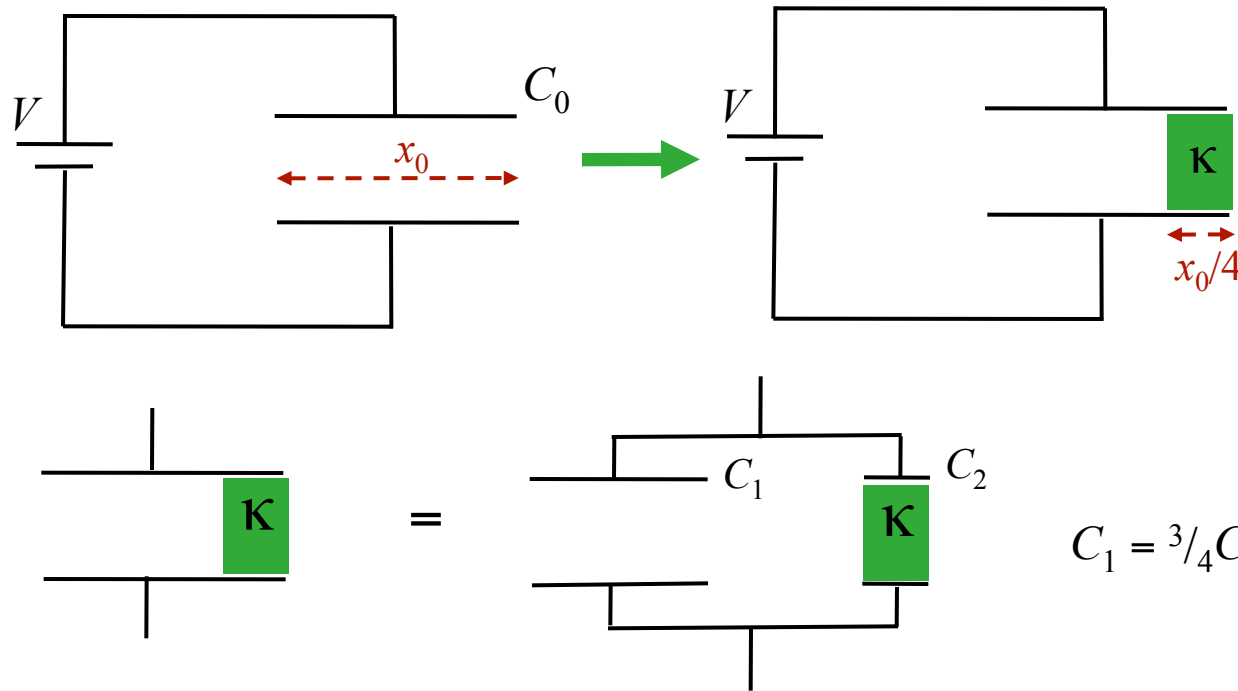

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

What is C_2 ?


A) $C_2 = \kappa C_0$

B) $C_2 = \frac{3}{4} \kappa C_0$

C) $C_2 = \frac{4}{3} \kappa C_0$

D) $C_2 = \frac{1}{4} \kappa C_0$

Calculation

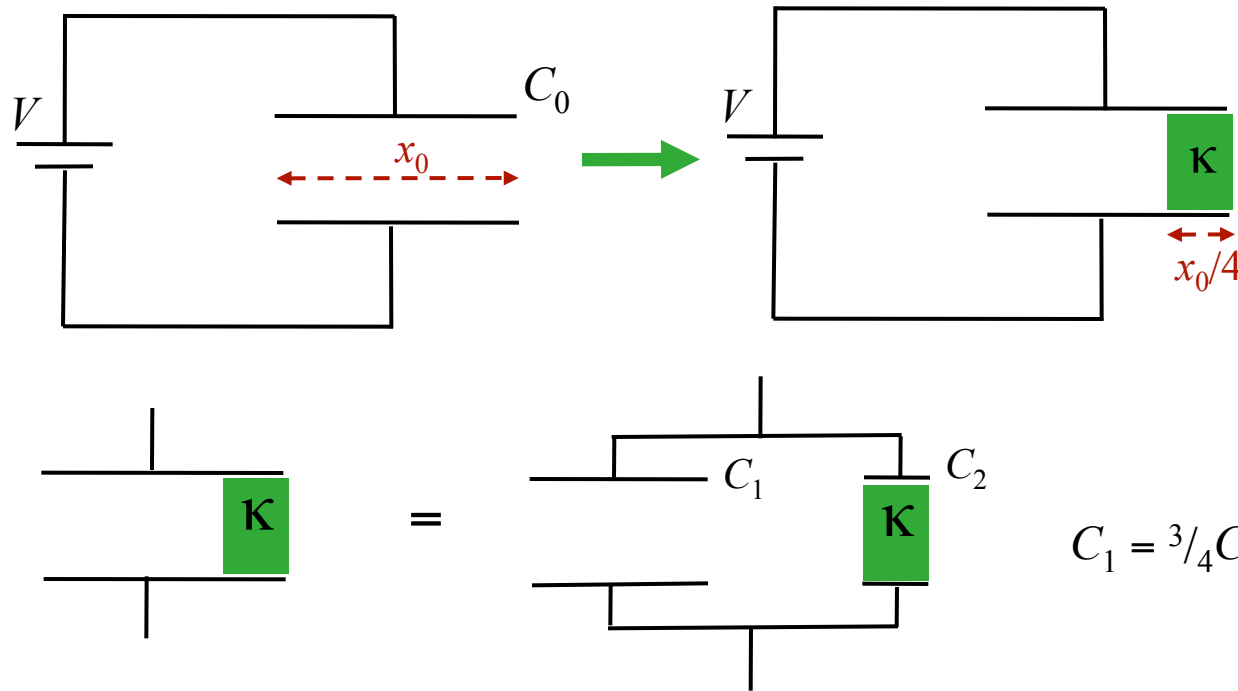

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

What is C_2 ?

A) $C_2 = \kappa C_0$


B) $C_2 = \frac{3}{4} \kappa C_0$

C) $C_2 = \frac{4}{3} \kappa C_0$

D) $C_2 = \frac{1}{4} \kappa C_0$

In general. For parallel plate capacitor filled with dielectric: $C = \kappa \epsilon_0 A/d$

Calculation

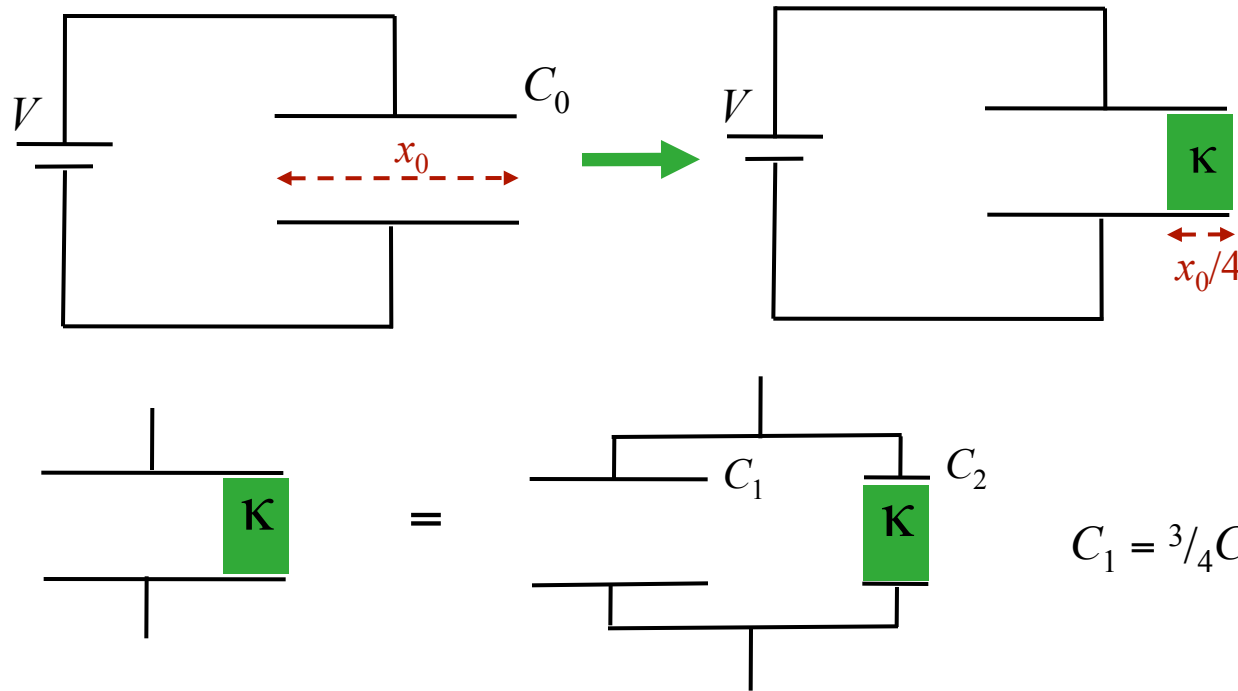

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

What is C_2 ?

A) $C_2 = \kappa C_0$

B) $C_2 = \frac{3}{4} \kappa C_0$


C) $C_2 = \frac{4}{3} \kappa C_0$

D) $C_2 = \frac{1}{4} \kappa C_0$

In general. For parallel plate capacitor filled with dielectric: $C = \kappa \epsilon_0 A/d$

$$\begin{matrix} A = \frac{1}{4}A_0 \\ d = d_0 \end{matrix} \quad \rightarrow \quad C = \frac{1}{4}(\kappa \epsilon_0 A_0/d_0) \quad \rightarrow \quad C_2 = \frac{1}{4} \kappa C_0$$

Calculation

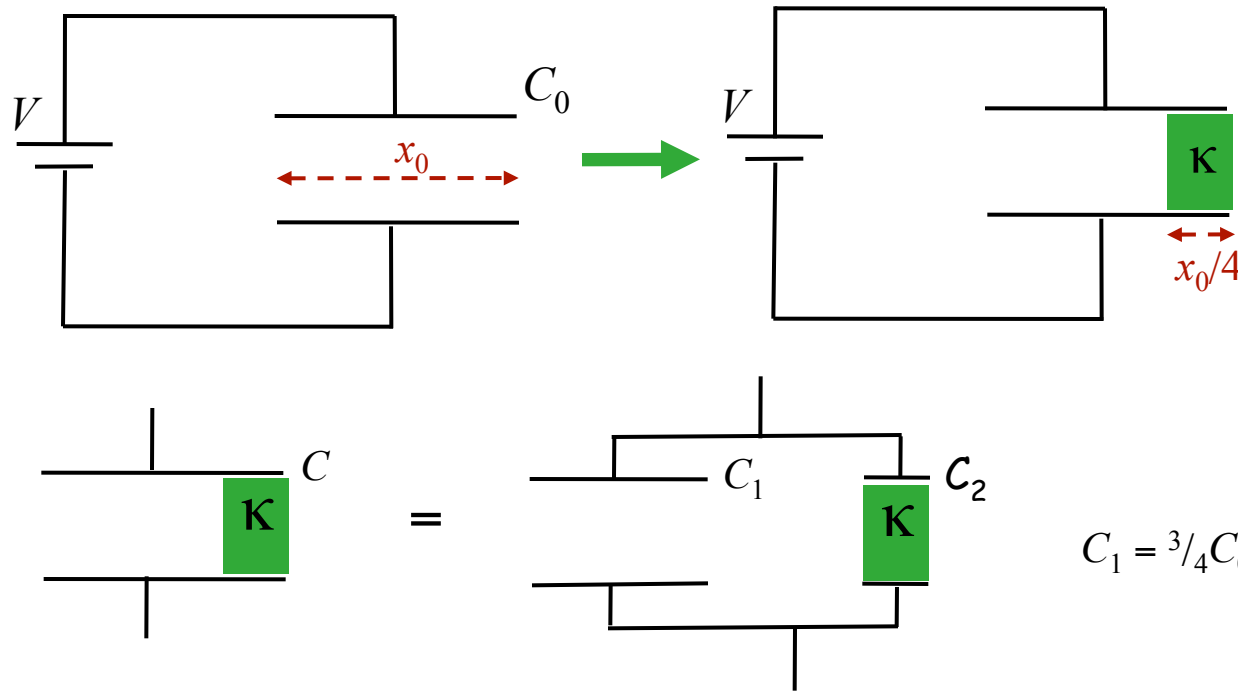

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .


A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}C_0$$

Calculation

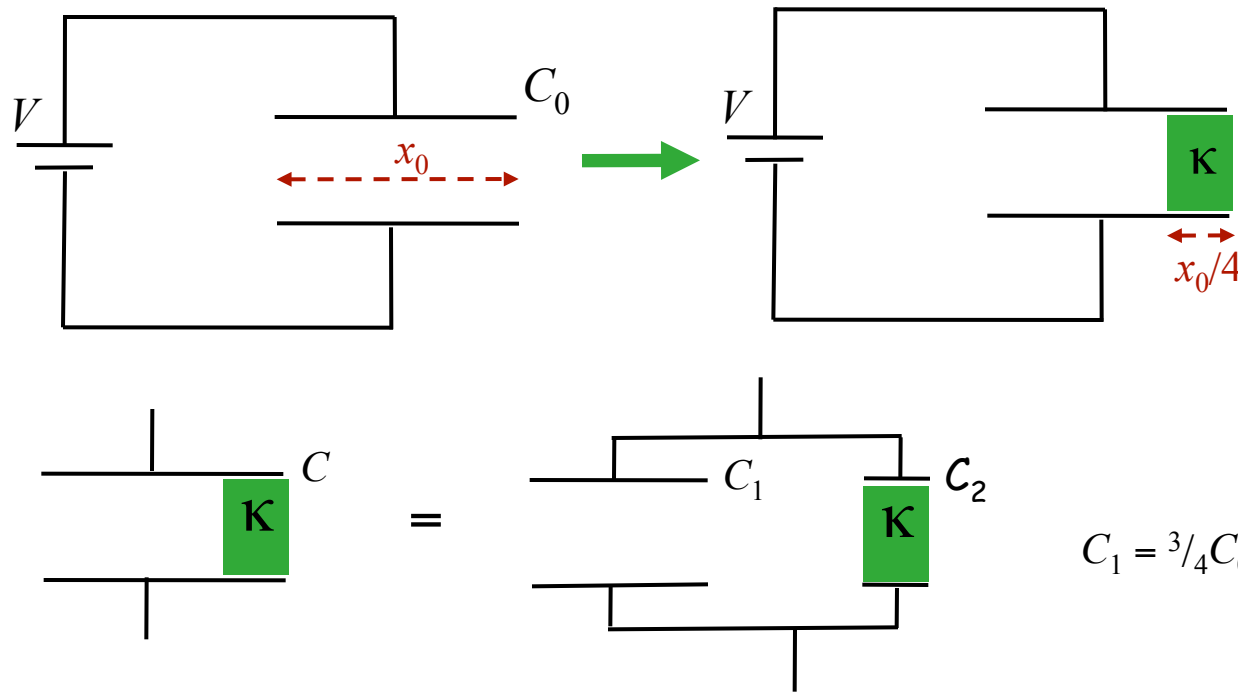

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$


What is C ?

A) $C = C_1 + C_2$

B) $C = C_1 + \kappa C_2$


C) $C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

Calculation

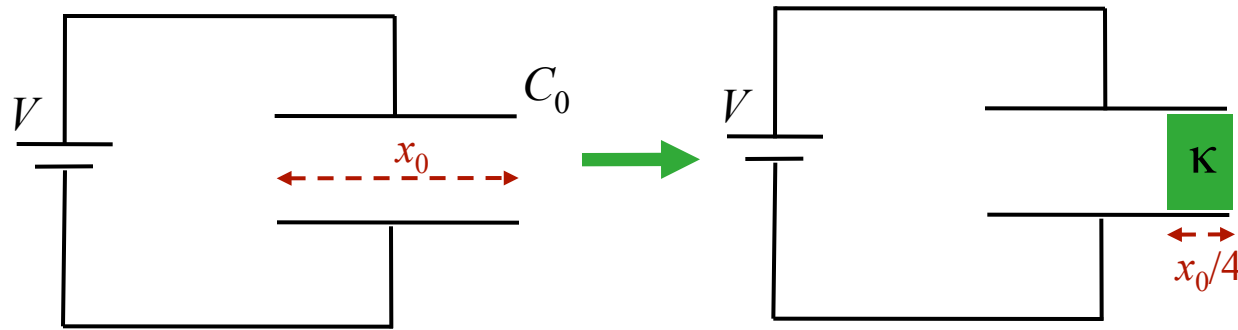

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

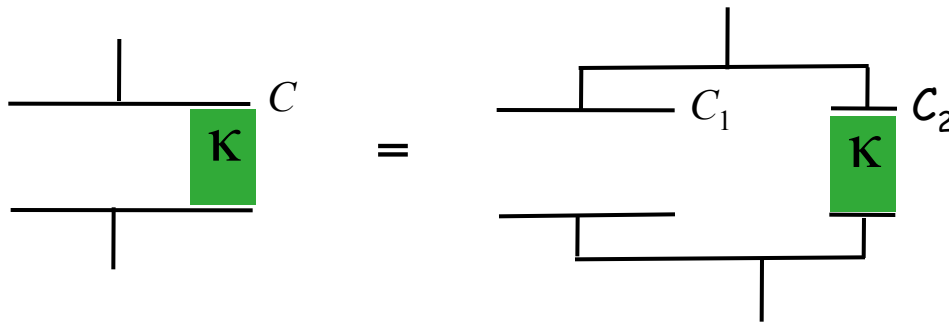A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.



What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$


What is C ?

A) $C = C_1 + C_2$

B) $C = C_1 + \kappa C_2$

C) $C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

Calculation

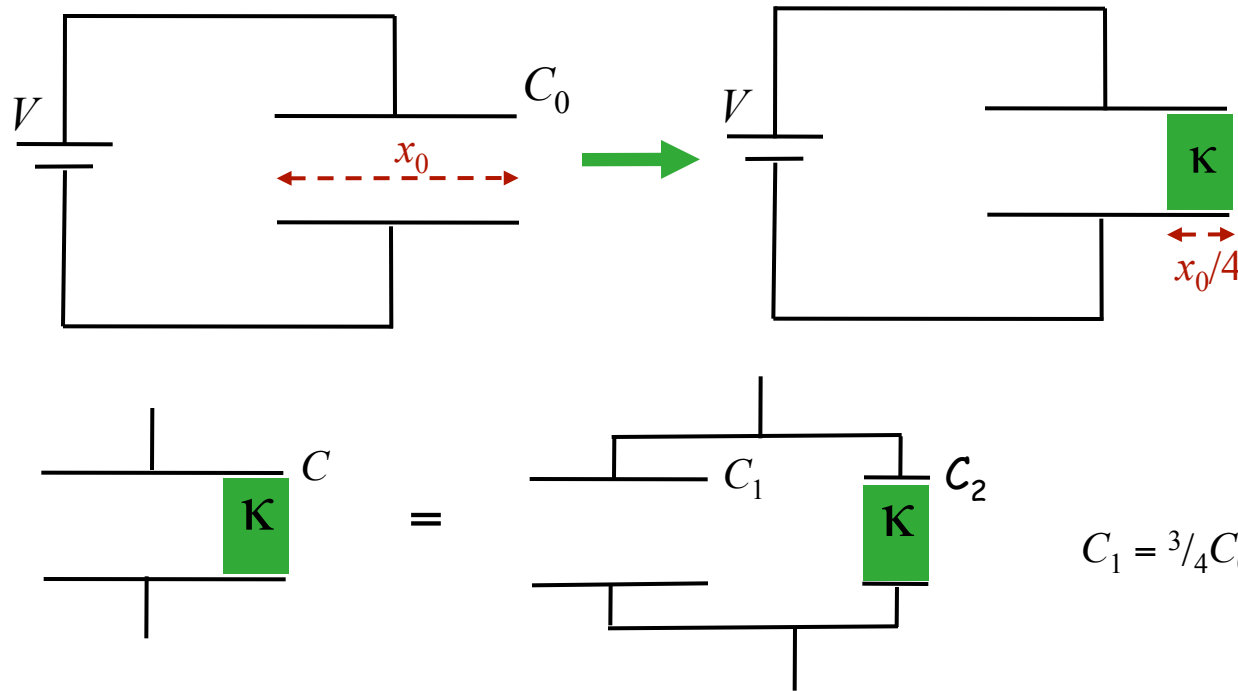

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

What is C ?


A) $C = C_1 + C_2$

B) $C = C_1 + \kappa C_2$

C) $C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

C = parallel combination of C_1 and C_2 : $C = C_1 + C_2$

Calculation

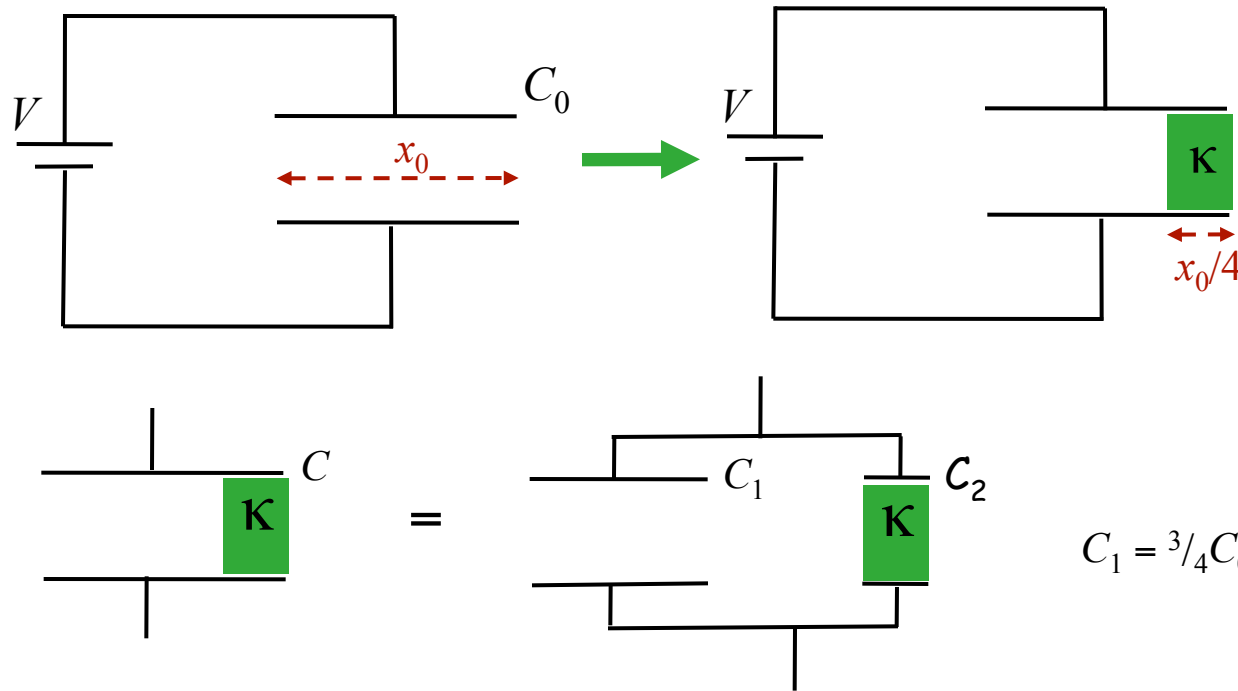

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$

What is C ?

A) $C = C_1 + C_2$


B) $C = C_1 + \kappa C_2$

C) $C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

C = parallel combination of C_1 and C_2 : $C = C_1 + C_2$

$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$

Calculation

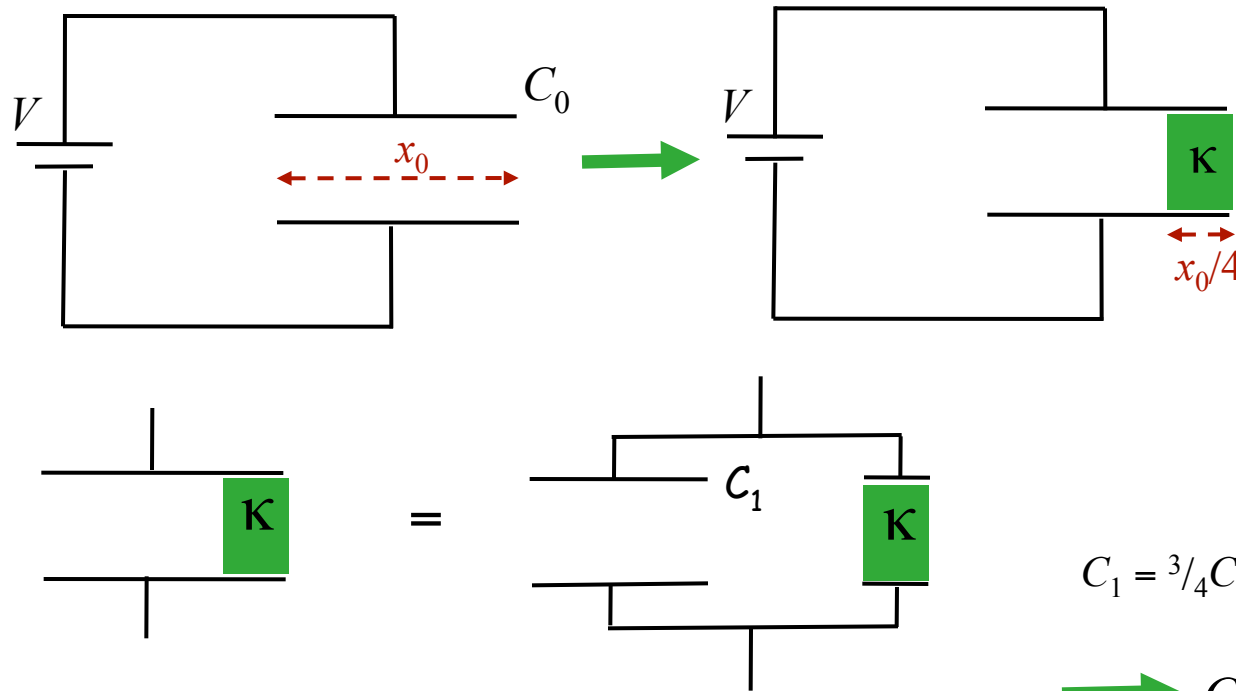

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.


What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$


$$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$$

Calculation

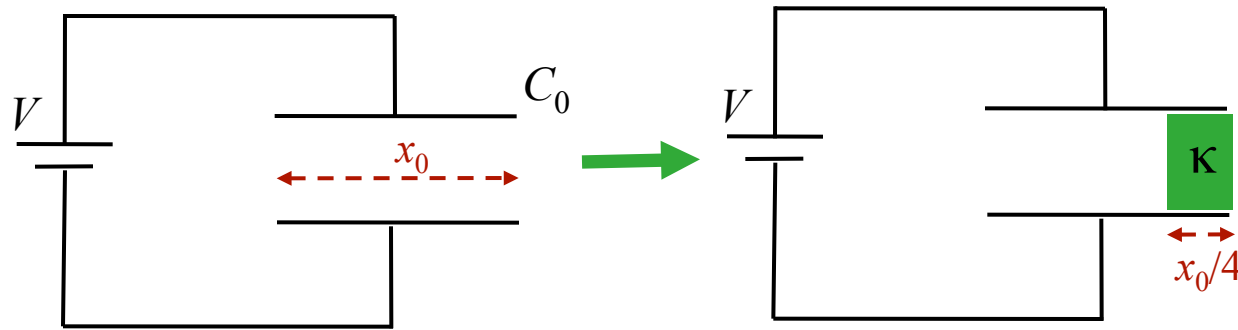

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

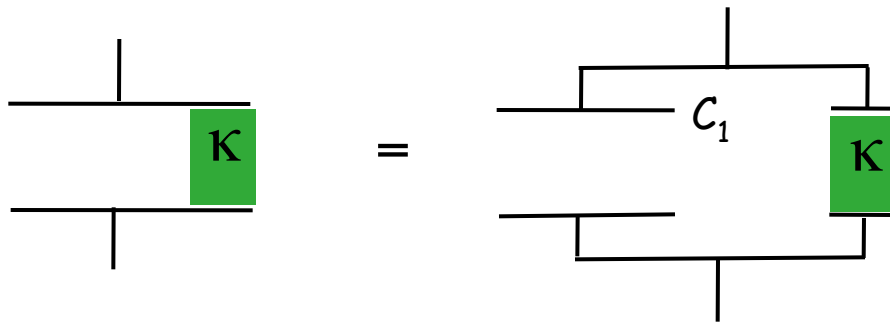A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.



What is Q_f , the final charge on the capacitor?


$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$

$$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$$


What is Q ?

Calculation

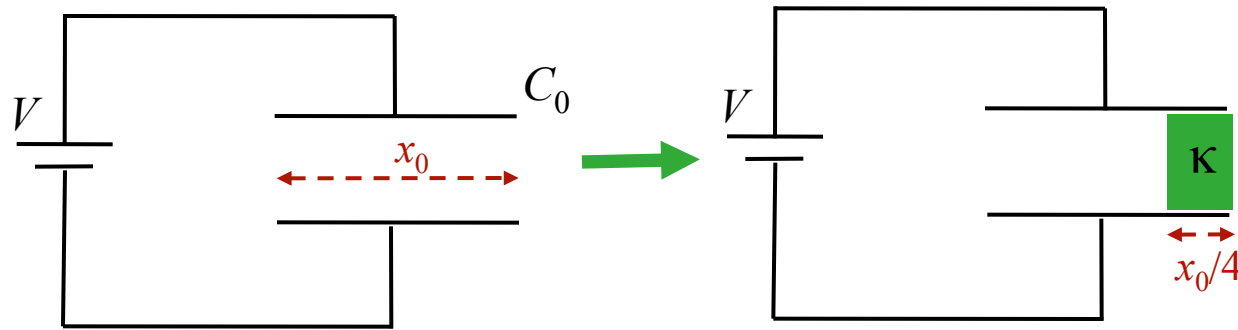

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

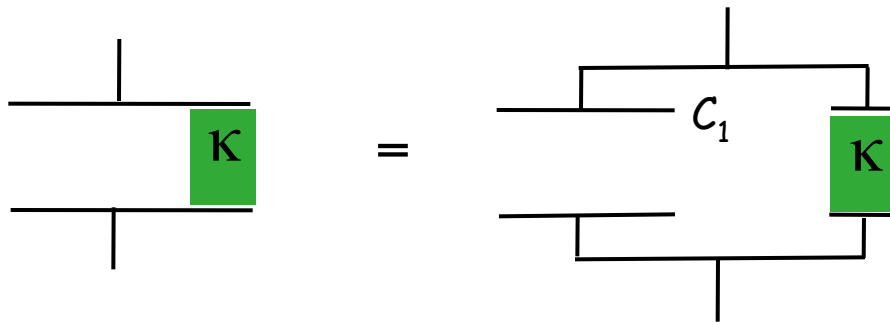A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.



What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$


$$C_2 = \frac{1}{4}\kappa C_0$$

$$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$$

What is Q ?


$$C \equiv \frac{Q}{V}$$

Calculation

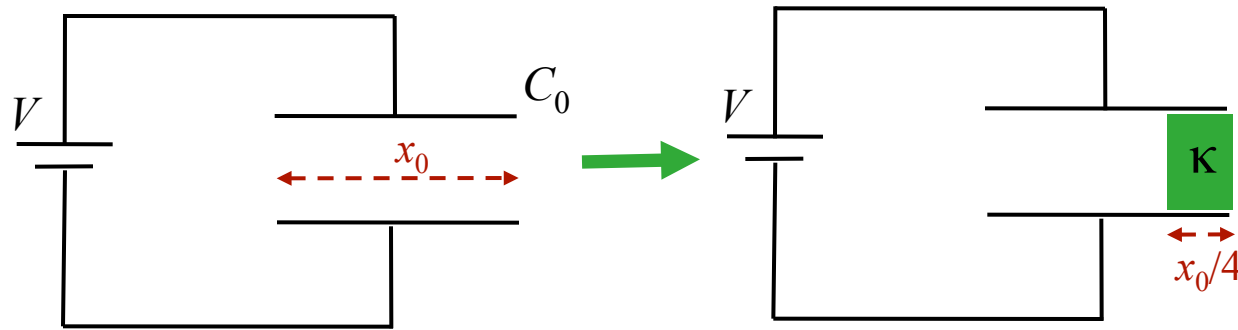

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

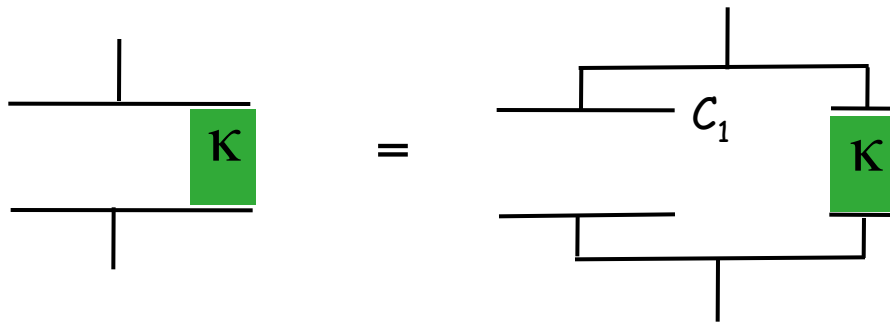A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.



What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$


$$C_2 = \frac{1}{4}\kappa C_0$$

$$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$$

What is Q ?


$$C \equiv \frac{Q}{V} \rightarrow Q = VC$$

Calculation

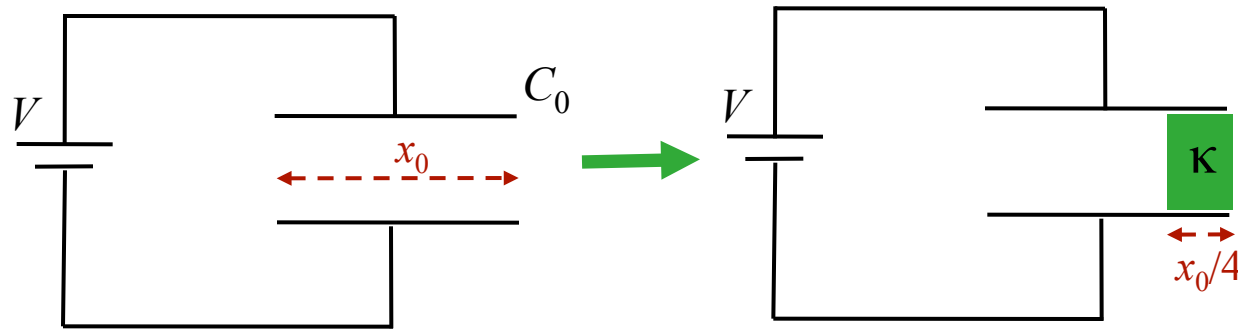

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

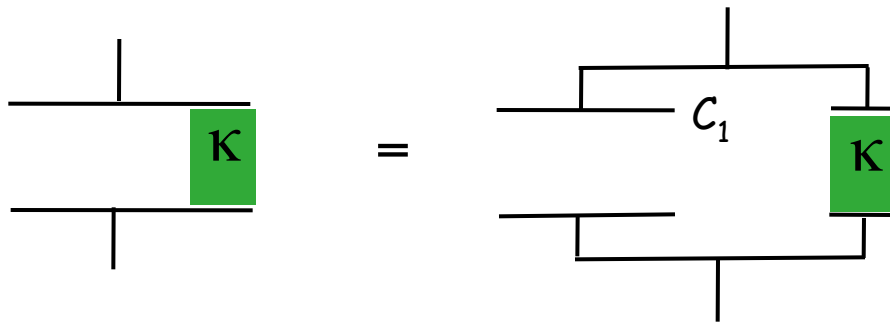A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.



What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$


$$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$$

What is Q ?

$$C \equiv \frac{Q}{V} \rightarrow Q = VC$$

$$Q_f = VC_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$$

Different Problem

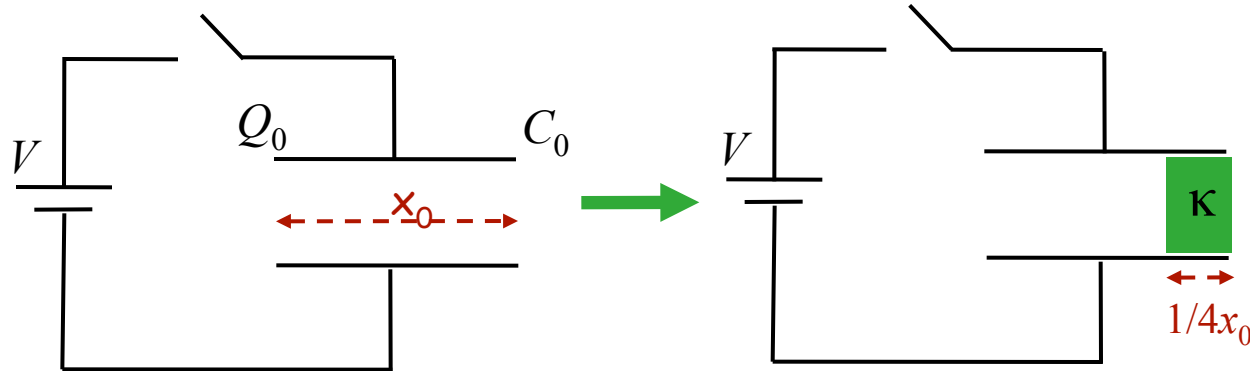


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?

Different Problem

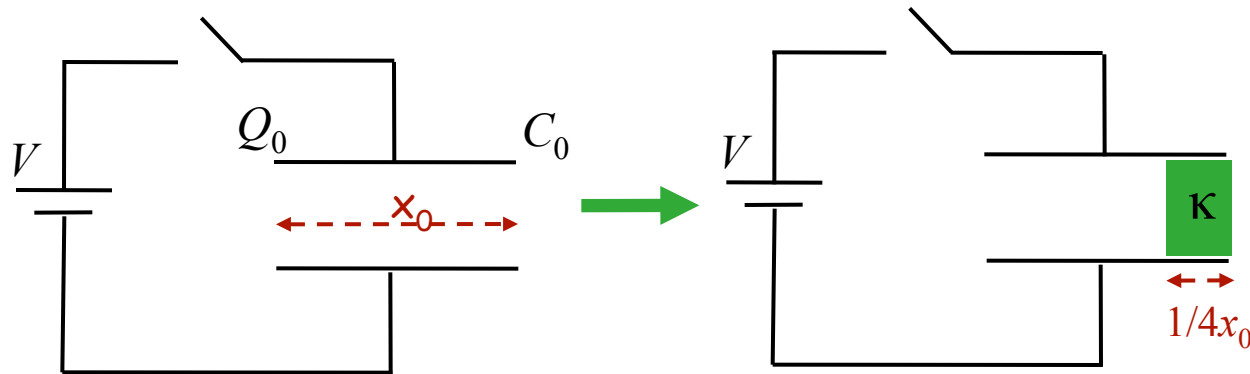

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.


What is V_f , the final voltage on the capacitor?

A) $V_f < V$

B) $V_f = V$

C) $V_f > V$

Different Problem

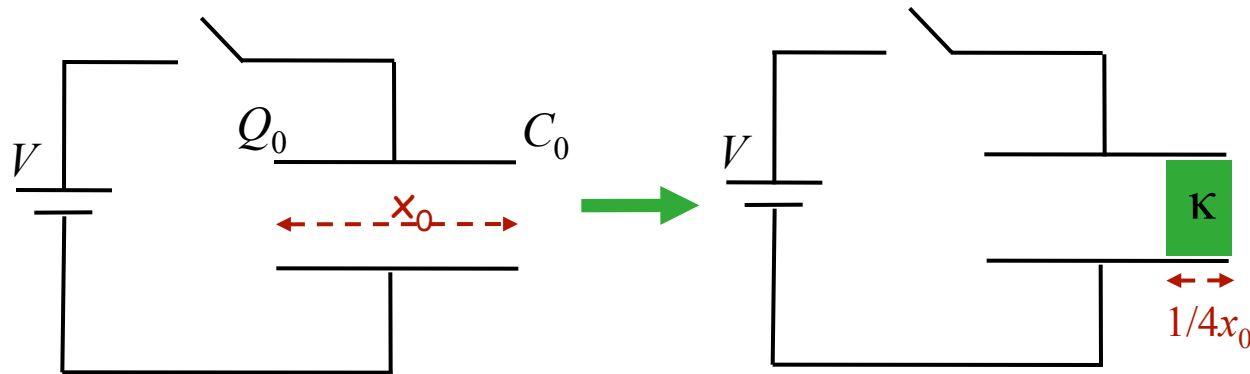

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.


What is V_f , the final voltage on the capacitor?

A) $V_f < V$

B) $V_f = V$

C) $V_f > V$

Different Problem

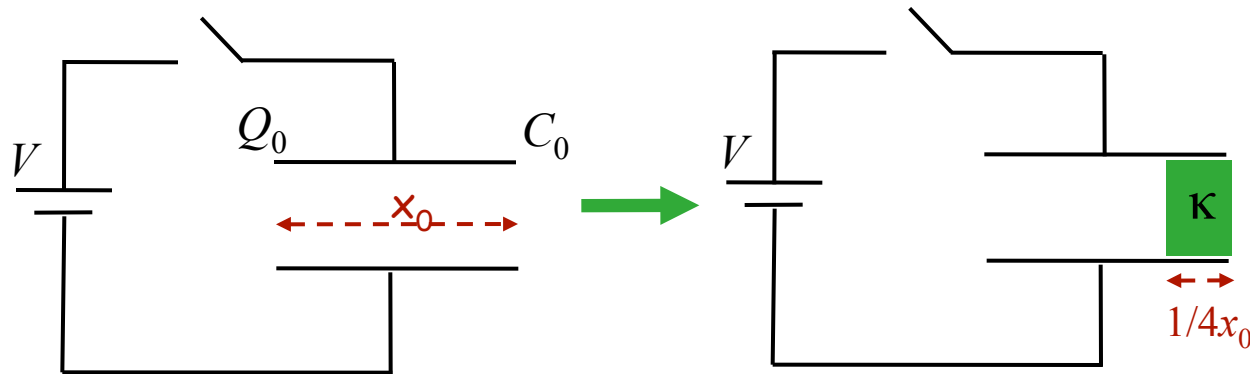

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?


A) $V_f < V$

B) $V_f = V$

C) $V_f > V$

Q stays same: no way to add or subtract

Different Problem

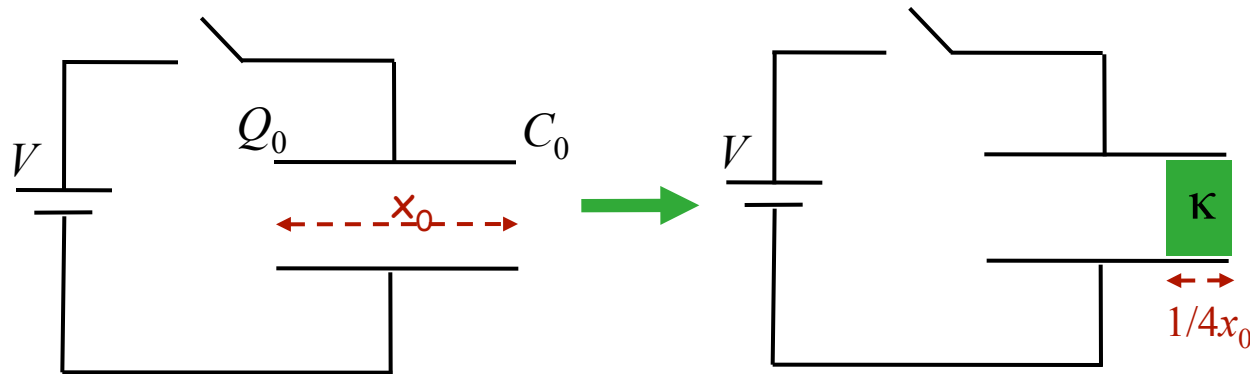

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4 x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?

A) $V_f < V$

B) $V_f = V$


C) $V_f > V$

Q stays same: no way to add or subtract



$$Q = Q_0 = C_0 V$$

Different Problem

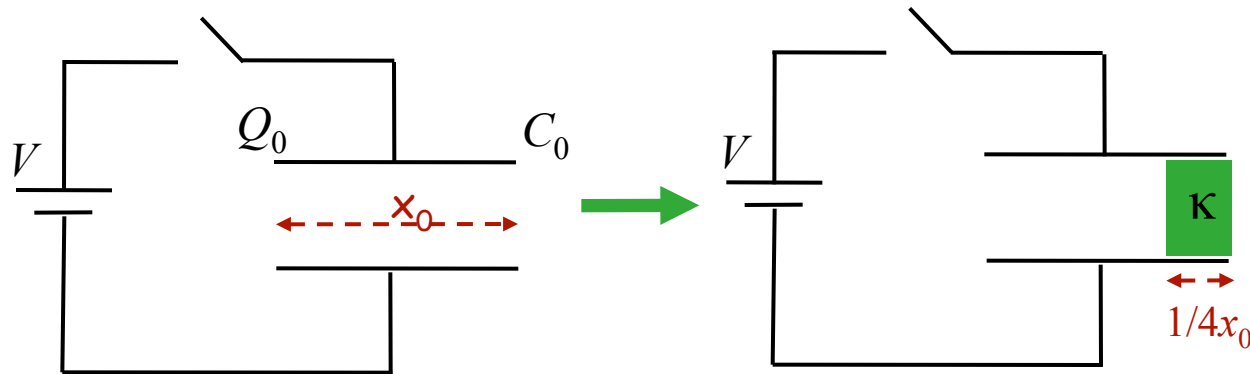

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4 x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?

A) $V_f < V$

B) $V_f = V$

C) $V_f > V$


Q stays same: no way to add or subtract



$$Q = Q_0 = C_0 V$$

We know C : (property of capacitor)

Different Problem

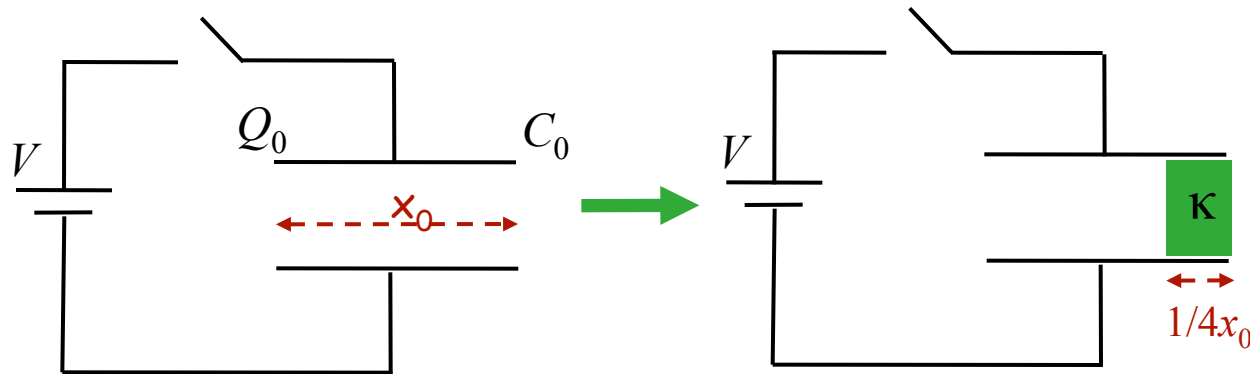

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4 x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?

A) $V_f < V$

B) $V_f = V$

C) $V_f > V$

Q stays same: no way to add or subtract




$$Q = Q_0 = C_0 V$$

We know C : (property of capacitor)



$$C = C_0 \left(\frac{3}{4} + \frac{1}{4} \kappa \right)$$

Different Problem

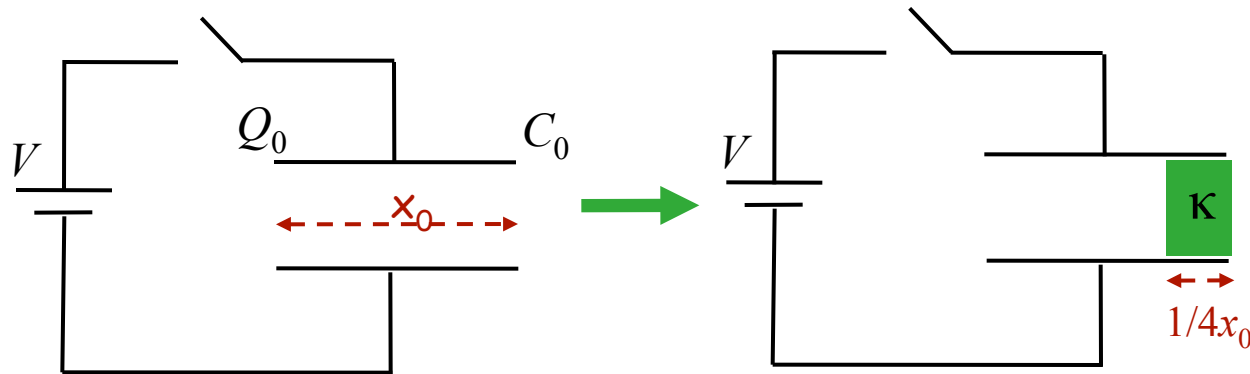

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4 x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?

A) $V_f < V$

B) $V_f = V$

C) $V_f > V$

Q stays same: no way to add or subtract


$\rightarrow Q = Q_0 = C_0 V$

We know C : (property of capacitor)

$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4} \kappa \right)$

$\rightarrow V_f = Q/C = V / \left(\frac{3}{4} + \frac{1}{4} \kappa \right)$

Different Problem

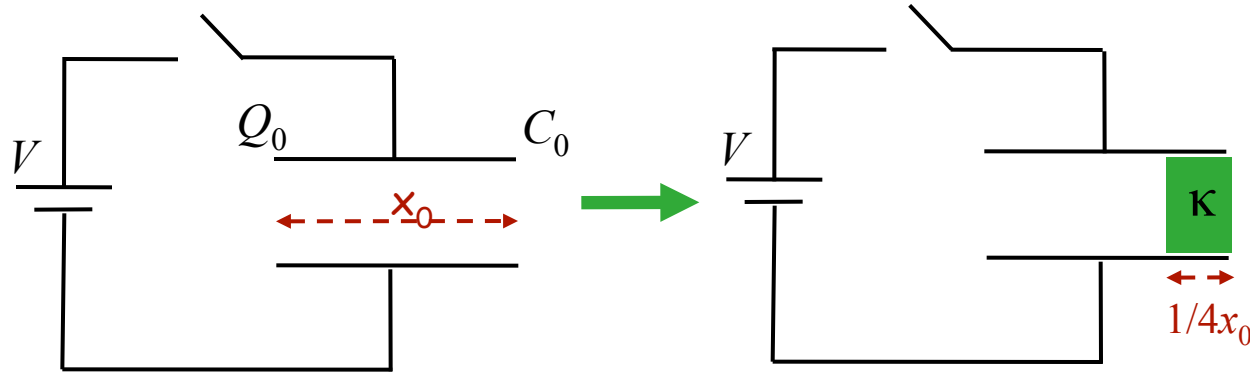


$$V_f = Q/C = V/(3/4 + 1/4 \kappa)$$

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4 x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?

Different Problem

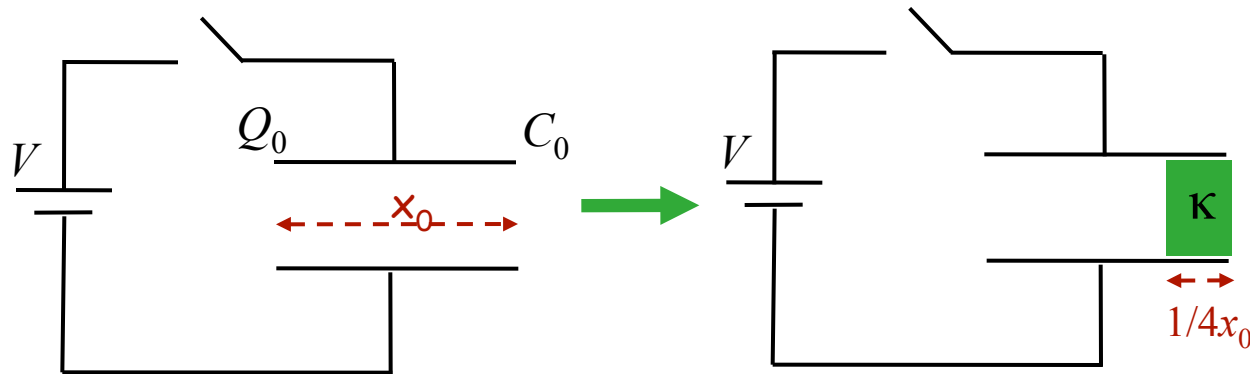

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.


A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.

$$V_f = Q/C = V/(3/4 + 1/4 \kappa)$$

How did energy stored in capacitor change when dielectric inserted?

What is V_f , the final voltage on the capacitor?

Different Problem

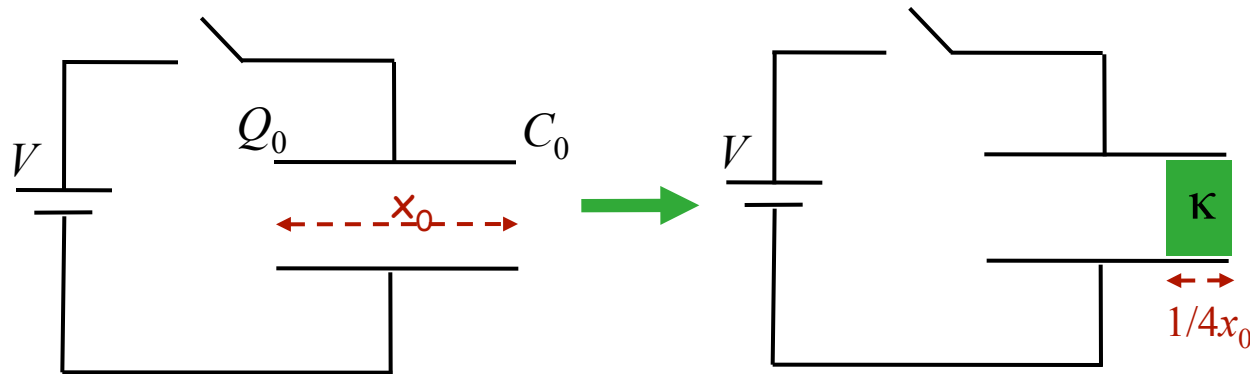

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4 x_0$ is inserted into the gap as shown.


$$V_f = Q/C = V/(3/4 + 1/4 \kappa)$$

How did energy stored in capacitor change when dielectric inserted?

What is V_f , the final voltage on the capacitor?

A) U increased B) U stayed same C) U decreased

Different Problem

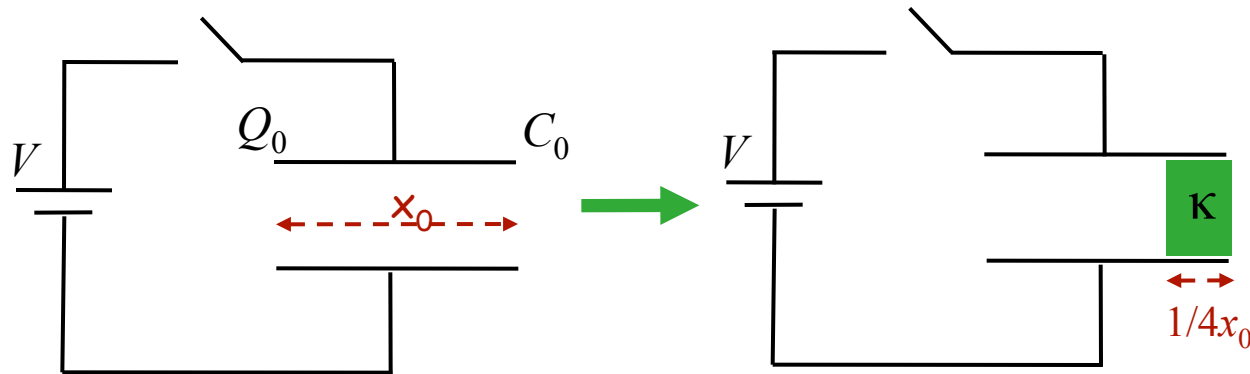

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.


$$V_f = Q/C = V/(3/4 + 1/4 \kappa)$$

How did energy stored in capacitor change when dielectric inserted?

What is V_f , the final voltage on the capacitor?

- A) U increased B) U stayed same C) U decreased

Different Problem

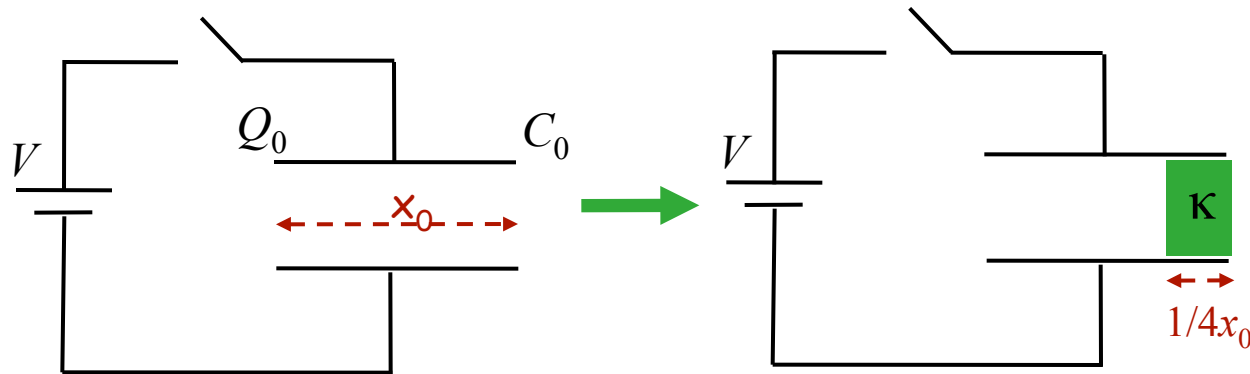

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?


$$V_f = Q/C = V/(3/4 + 1/4 \kappa)$$

How did energy stored in capacitor change when dielectric inserted?

A) U increased B) U stayed same C) U decreased

$$U = \frac{1}{2} Q^2/C$$

Different Problem

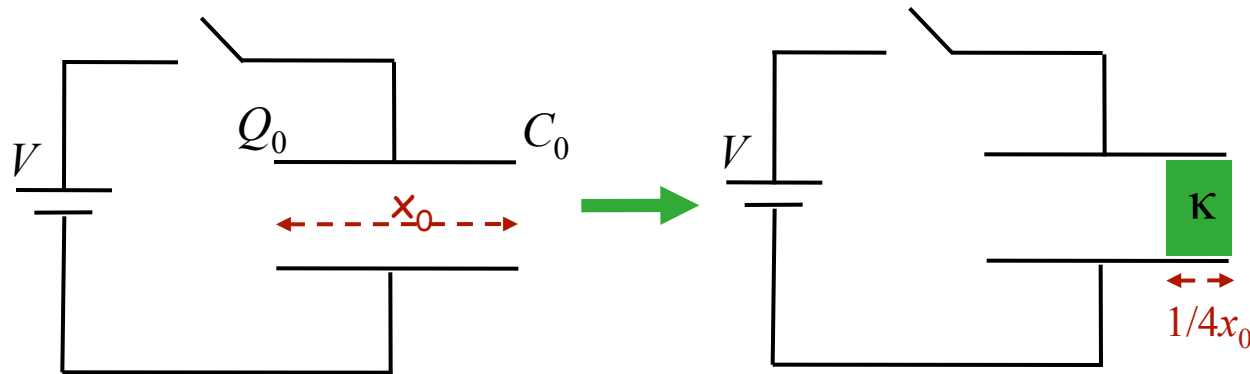

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?

$$V_f = Q/C = V/(3/4 + 1/4 \kappa)$$


How did energy stored in capacitor change when dielectric inserted?

- A) U increased B) U stayed same C) U decreased

$$U = \frac{1}{2} Q^2/C$$

Q remained same

Different Problem

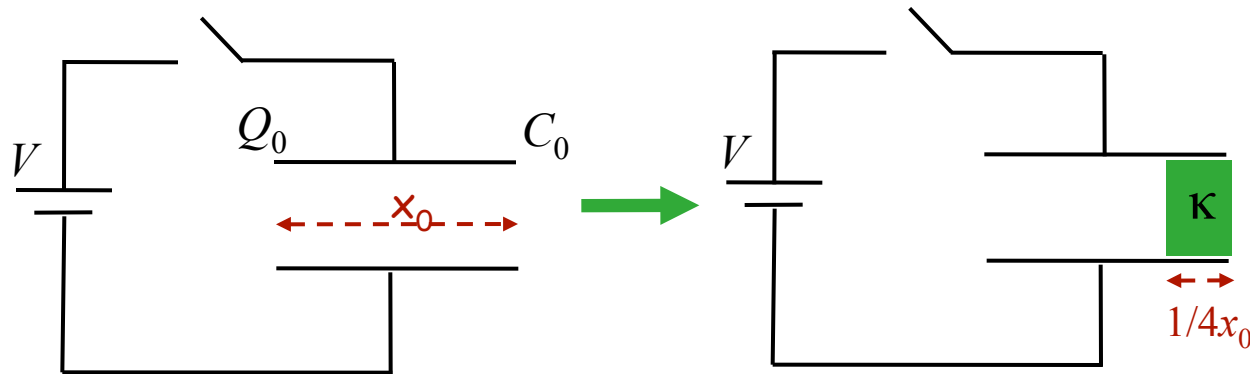

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?

$$V_f = Q/C = V/(3/4 + 1/4 \kappa)$$

How did energy stored in capacitor change when dielectric inserted?


- A) U increased B) U stayed same C) U decreased

$$U = \frac{1}{2} Q^2/C$$

Q remained same

C increased

Different Problem

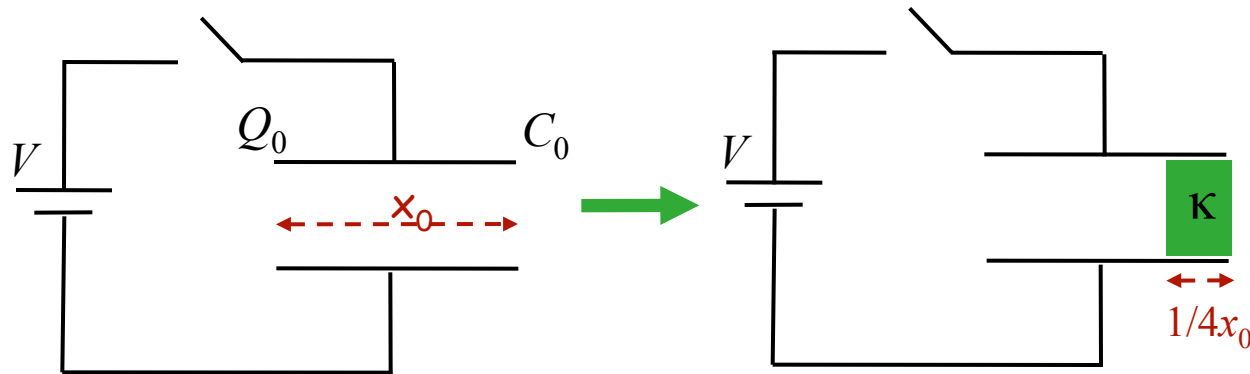

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.

$$V_f = Q/C = V/(3/4 + 1/4 \kappa)$$

How did energy stored in capacitor change when dielectric inserted?

What is V_f , the final voltage on the capacitor?

A) U increased B) U stayed same **C) U decreased**

$$U = \frac{1}{2} Q^2/C$$

Q remained same

C increased



U decreased