

Electricity & Magnetism

Lecture 9: Electric Current

Today's Concept:
Electric Current

- “So simple i thought i did something wrong.”
- “current density”
- “Since $R = \rho L/A$, the greater the cross sectional area, the smaller the resistance, but the greater the length the higher the resistance. Is that why long cables have to be very thick?”

A Big Idea Review

Coulomb's Law

Force law between point charges

$$\vec{F}_{1,2} = \frac{kq_1q_2}{r_{1,2}^2} \hat{r}_{1,2}$$



Electric Field

Force per unit charge

$$\vec{E} \equiv \frac{\vec{F}}{q}$$

Electric Field
Property of Space
Created by Charges
Superposition

Gauss' Law

Flux through closed surface is always proportional to charge enclosed

$$\oint_{\text{surface}} \vec{E} \cdot \vec{A} = \frac{Q_{\text{enclosed}}}{\epsilon_0}$$

Gauss' Law
Can be used to determine E field

Spheres
Cylinders
Infinite Planes

Electric Potential

Potential energy per unit charge

$$\Delta V_{a \rightarrow b} \equiv \frac{\Delta U_{a \rightarrow b}}{q} = - \int_a^b \vec{E} \cdot d\vec{l}$$

Electric Potential

Scalar Function that can be used to determine E

$$\vec{E} = -\vec{\nabla}V$$

Capacitance

Relates charge and potential for two conductor system

$$C \equiv \frac{Q}{V}$$

Applications of Big Ideas

Conductors
Charges free to move



What Determines
How They Move?



They move until
 $E = 0$!




$E = 0$ in conductor
determines charge
densities on surfaces

Spheres
Cylinders
Infinite Planes



Field Lines &
Equipotentials

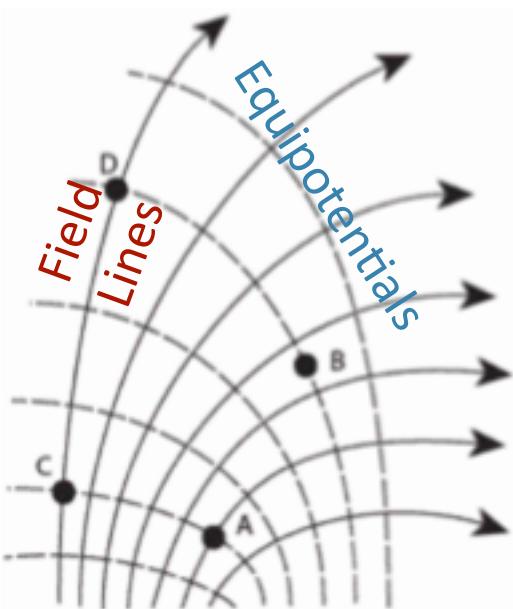


Work Done By E Field

$$W_{a \rightarrow b} = \int_a^b \vec{F} \cdot d\vec{l} = \int_a^b q \vec{E} \cdot d\vec{l}$$

Change in Potential Energy

$$\Delta V_{a \rightarrow b} \equiv \frac{\Delta U_{a \rightarrow b}}{q} = - \int_a^b \vec{E} \cdot d\vec{l}$$

Capacitor Networks

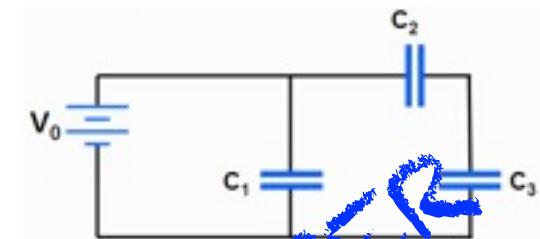

Series: $(1/C_{23}) = (1/C_2) + (1/C_3)$

Parallel


$$C_{123} = C_1 + C_{23}$$

Key Concepts:

- 1) How resistance depends on A, L, σ, ρ σ is **conductivity** here (not surface charge density)
 ρ is **resistivity** here (not volume charge density).
- 2) How to combine resistors in series and parallel
- 3) Understanding resistors in circuits

Today's Plan:

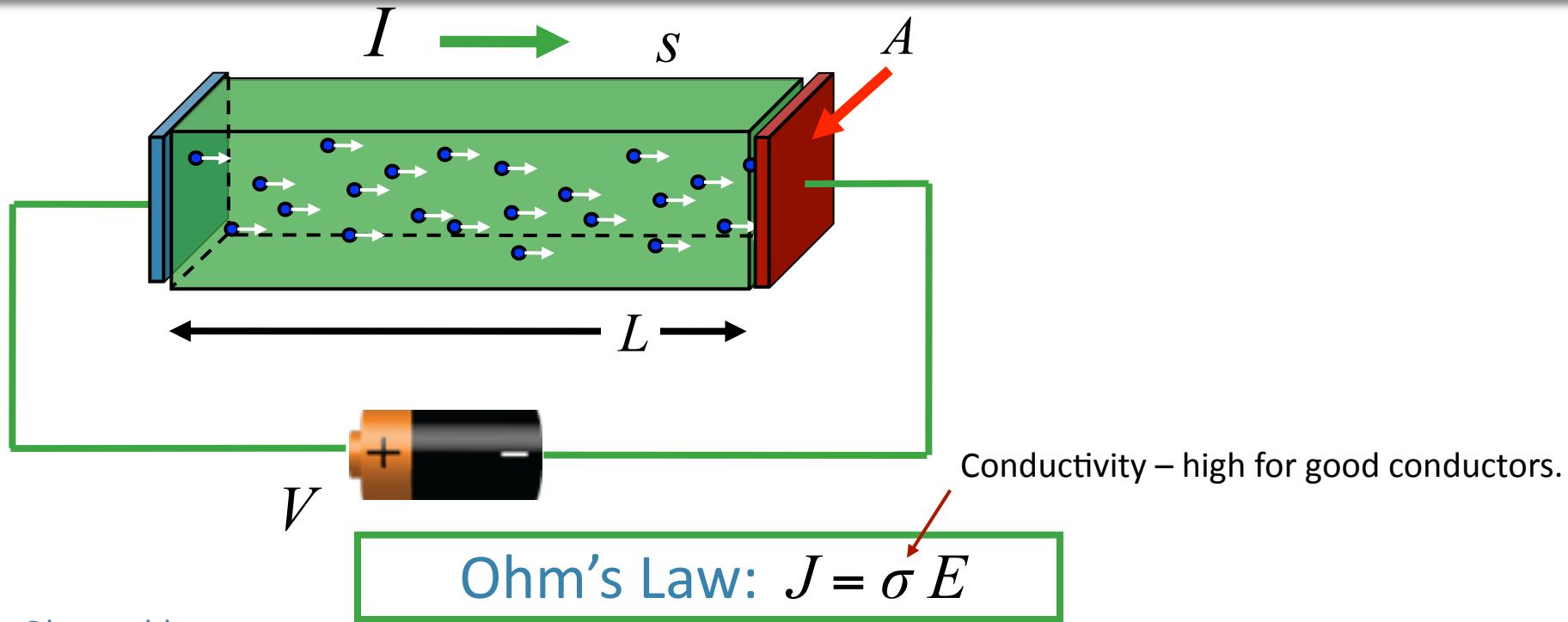- 1) Review of resistance & preflights
- 2) Work out a circuit problem in detail



$$V = EL$$

$$I = JA$$



$$I/A = \sigma V/L$$



$$I = V/(L/\sigma A)$$



$$R = \text{Resistance}$$

$$\rho = 1/\sigma$$

$I = V/R$



$$R = \frac{L}{\sigma A}$$

This is just like Plumbing!

I is like flow rate of water

V is like pressure

R is how hard it is for water to flow in a pipe


$$R = \frac{L}{\sigma A}$$

To make *R* big, make *L* long or *A* small



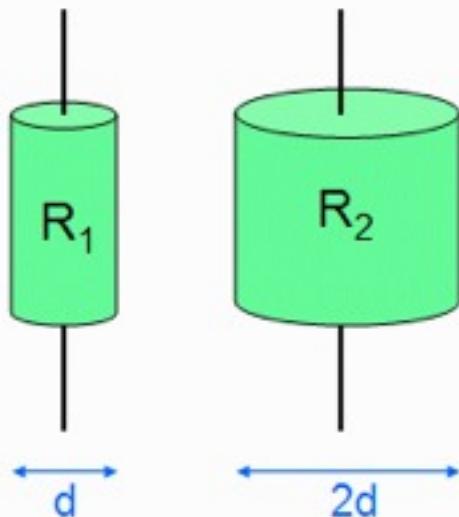To make *R* small, make *L* short or *A* big






A $V_1 > V_2$ B $V_1 = V_2$ C $V_1 < V_2$

Same current through both resistors


Compare voltages across resistors

$$R \propto \frac{L}{A}$$

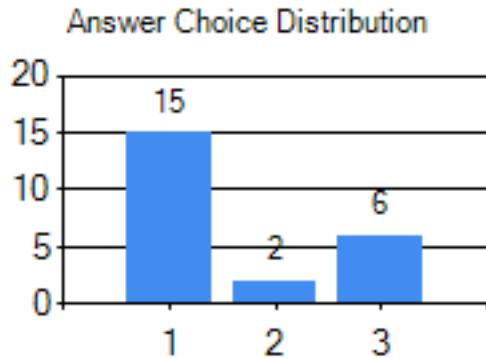A $V_1 > V_2$ B $V_1 = V_2$ C $V_1 < V_2$



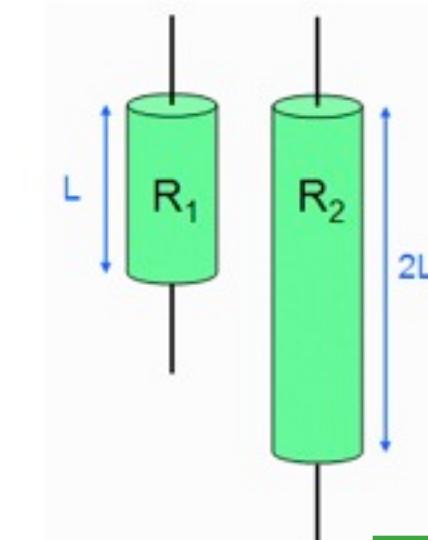
$$A_2 = 4A_1 \Rightarrow V_2 = \frac{1}{4}V_1$$



A $V_1 > V_2$ B $V_1 = V_2$ C $V_1 < V_2$


$$V = IR \propto \frac{L}{A}$$

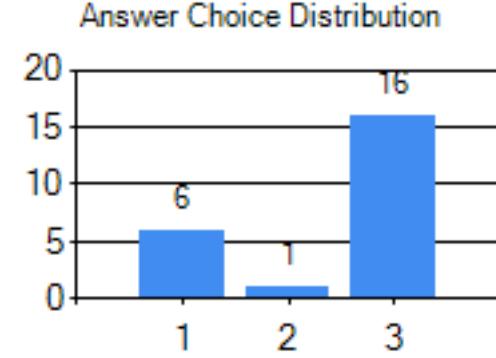


$$L_2 = 2L_1 \Rightarrow V_2 = 2V_1$$

CheckPoint: Current Density


The SAME amount of current I passes through three different resistors. R_2 has twice the cross-sectional area and the same length as R_1 , and R_3 is three times as long as R_1 but has the same cross-sectional area as R_1 . In which case is the CURRENT DENSITY through the resistor the smallest?

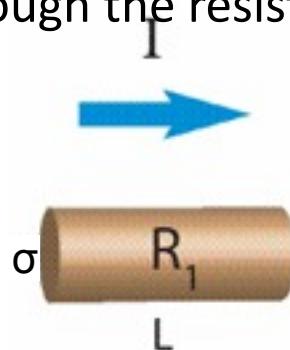

Case 1

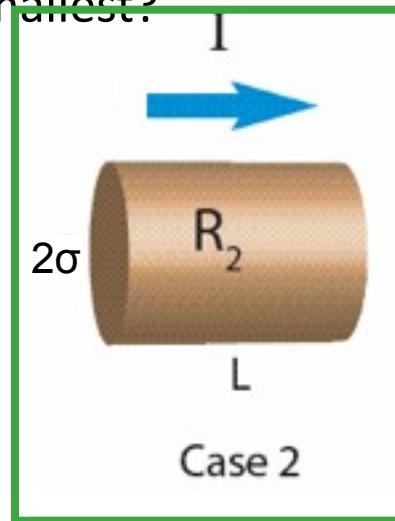

Case 2

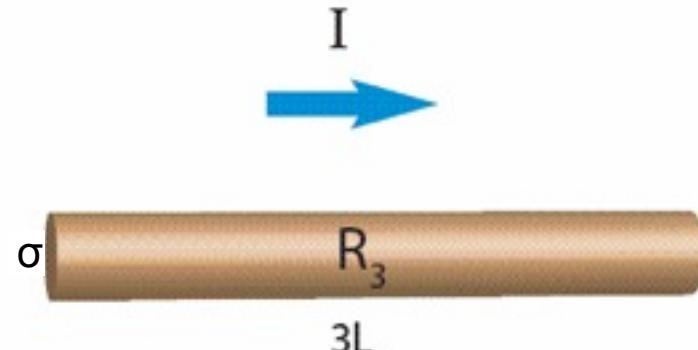


Case 3

$$J \equiv \frac{I}{A} \rightarrow J_1 = J_3 = 2J_2$$

Same Current $\rightarrow J \propto \frac{1}{A}$

Answer Choice Distribution

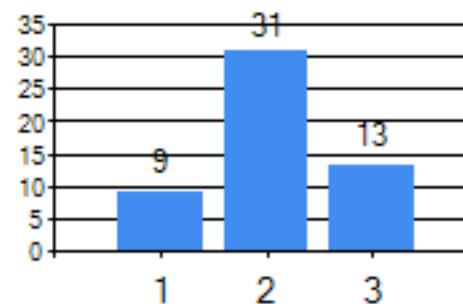

Resistor Summary

Wiring

Voltage

Current

Resistance

Series



Each resistor on the same wire.

Different for each resistor.

$$V_{total} = V_1 + V_2$$

Voltage Divider


Same for each resistor

$$I_{total} = I_1 = I_2$$

Increases

$$R_{eq} = R_1 + R_2$$

Parallel

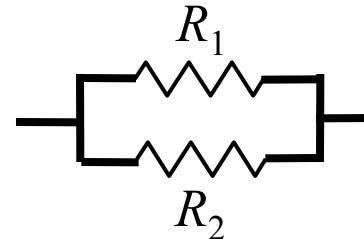

Each resistor on a different wire.

Same for each resistor.

$$V_{total} = V_1 = V_2$$

Different for each resistor

$$I_{total} = I_1 + I_2$$

Current Divider

Decreases


$$1/R_{eq} = 1/R_1 + 1/R_2$$

CheckPoint: Resistor Network 1


Three resistors are connected to a battery with emf V as shown. The resistances of the resistors are all the same, i.e. $R_1 = R_2 = R_3 = R$.

Compare the current through R_2 with the current through R_3 :

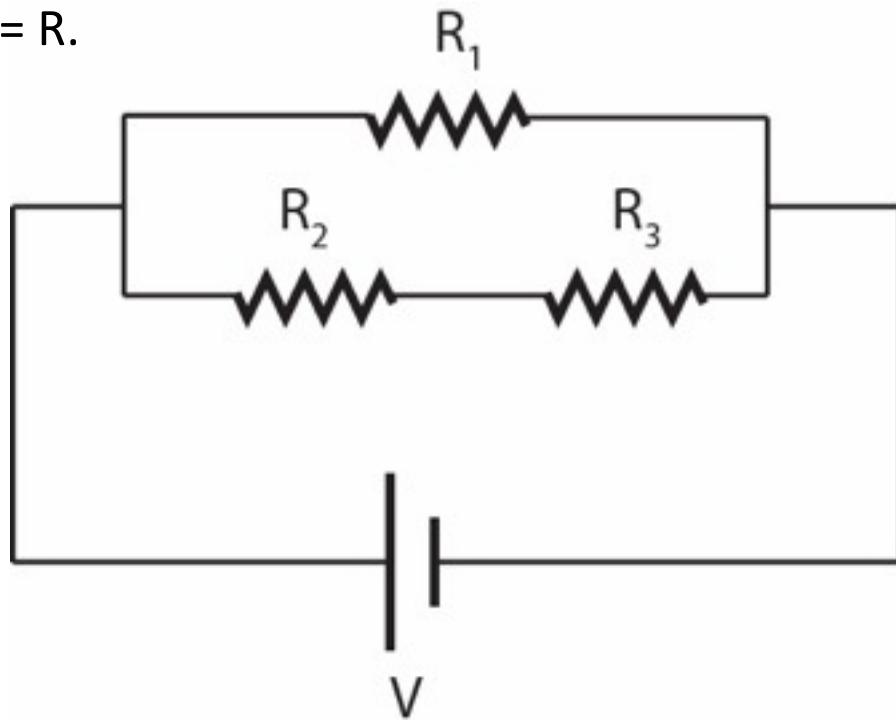- A. $I_2 > I_3$
- B. $I_2 = I_3$
- C. $I_2 < I_3$



Answer Choice Distribution

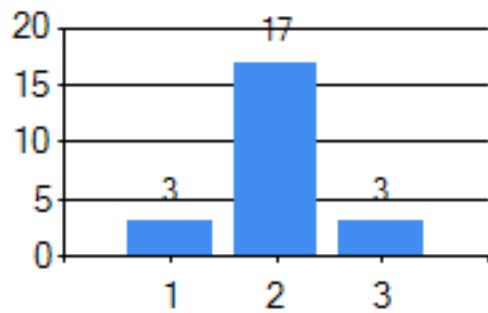


R_2 in series with R_3



Current through R_2 and R_3 is the same

$$I_{23} = \frac{V}{R_2 + R_3}$$

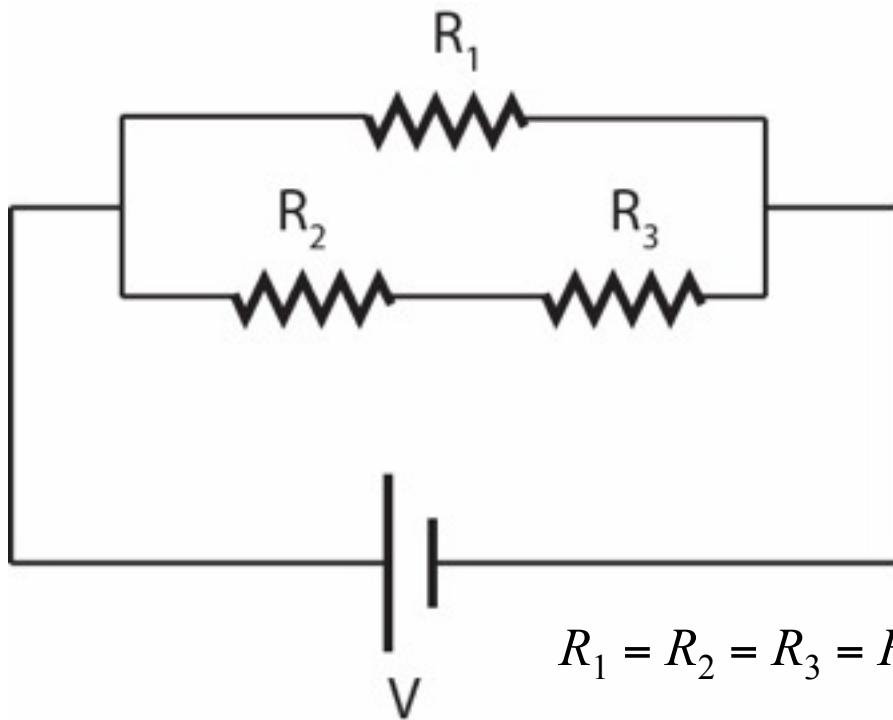

CheckPoint 2

Compare the current through R_1 with the current through R_2

$$I_1 \longleftrightarrow I_2$$

CheckPoint 3

Compare the voltage across R_2 with the voltage across R_3

$$V_2 \longleftrightarrow V_3$$


CheckPoint 4

Compare the voltage across R_1 with the voltage across R_2

$$V_1 \longleftrightarrow V_2$$

CheckPoint: Resistor Network 2

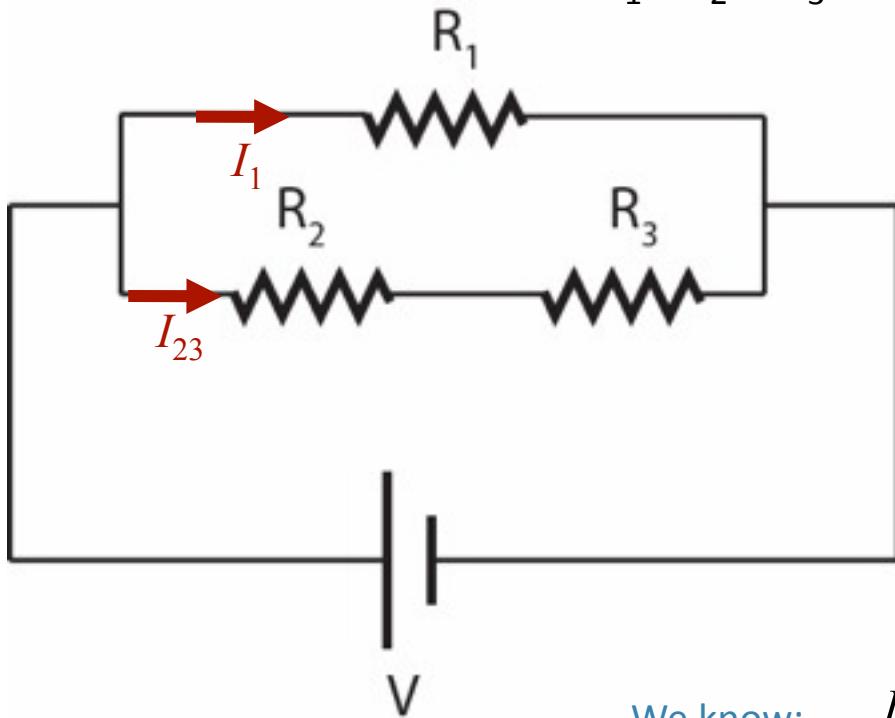Three resistors are connected to a battery with emf V as shown. The resistances of the resistors are all the same, i.e. $R_1 = R_2 = R_3 = R$.



Compare the current through R_1 with the current through R_2 :

- A. $I_1/I_{23} = 1/2$
- B. $I_1/I_{23} = 1/3$
- C. $I_1 = I_{23}$
- D. $I_1/I_{23} = 2$
- E. $I_1/I_{23} = 3$

We know: $I_{23} = \frac{V}{R_2 + R_3}$


$$I_1 = I_{23} \frac{R_2 + R_3}{R_1}$$

Similarly:

$$I_1 = \frac{V}{R_1}$$


$$\frac{I_1}{I_{23}} = \frac{R_2 + R_3}{R_1} = 2$$

Answer Choice Distribution

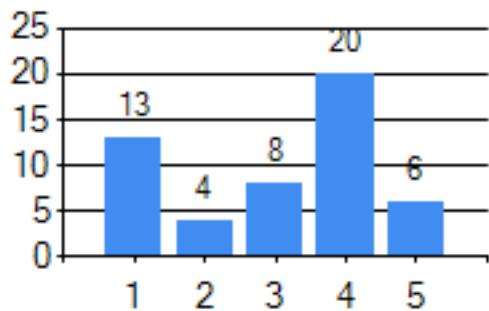

CheckPoint: Resistor Network 3

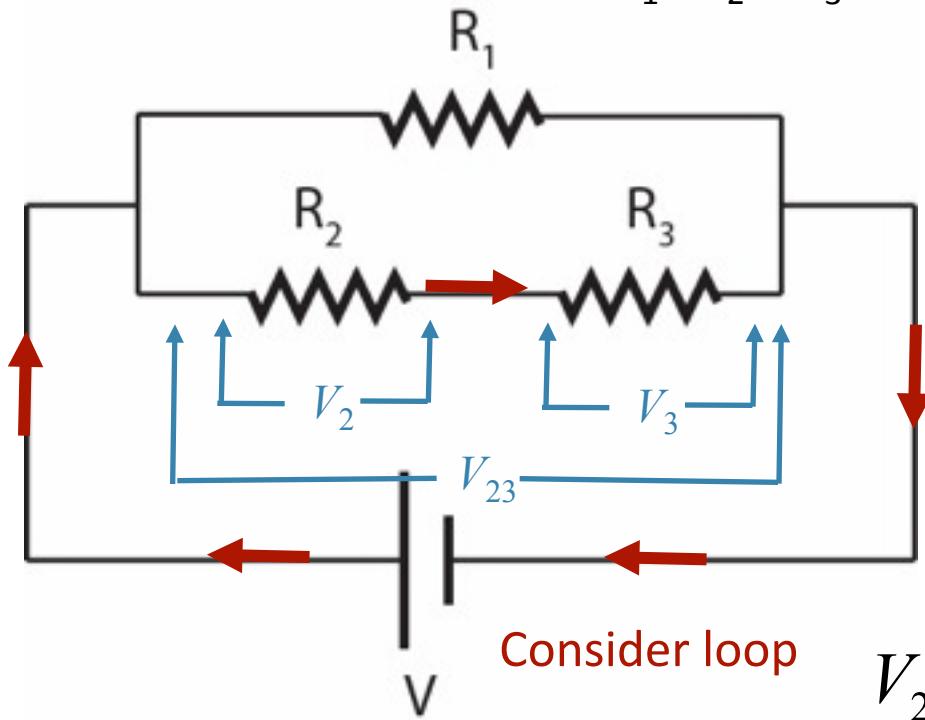Three resistors are connected to a battery with emf V as shown. The resistances of the resistors are all the same, i.e. $R_1 = R_2 = R_3 = R$.



Compare the voltage across R_2 with the voltage across R_3 :


- A. $V_2 > V_3$
- B. $V_2 = V_3 = V$
- C. $V_2 = V_3 < V$
- D. $V_2 < V_3$

$$V_{23} = V$$

$$V_{23} = V_2 + V_3 \quad \longrightarrow \quad V_2 = V_3 = \frac{V}{2}$$


$$R_2 = R_3 \Rightarrow V_2 = V_3$$

Answer Choice Distribution

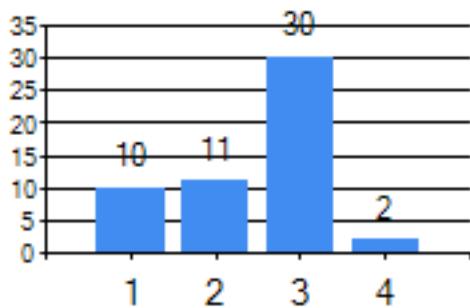

CheckPoint: Resistor Network 4

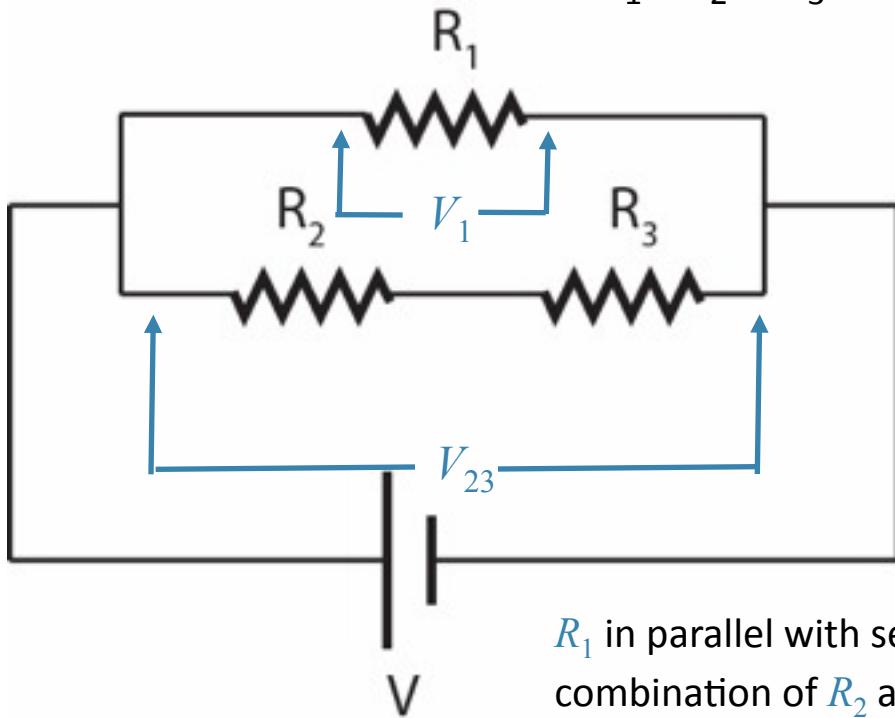Three resistors are connected to a battery with emf V as shown. The resistances of the resistors are all the same, i.e. $R_1 = R_2 = R_3 = R$.




Compare the voltage across R_1 with the voltage across R_2 .

- A. $V_1 = V_2 = V$
- B. $V_1 = 1/2 V_2 = V$
- C. $V_1 = 2V_2 = V$
- D. $V_1 = 1/2 V_2 = 1/5 V$
- E. $V_1 = 1/2 V_2 = 1/2 V$

R_1 in parallel with series combination of R_2 and R_3

Answer Choice Distribution

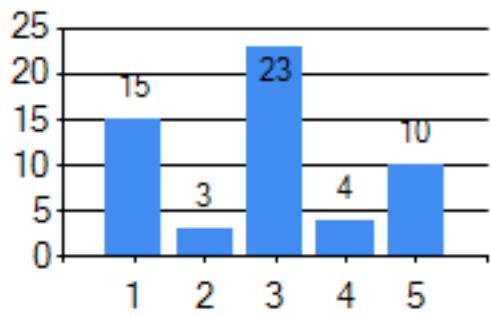


$$V_1 = V_{23}$$

$$R_2 = R_3 \Rightarrow V_2 = V_3 \rightarrow V_1 = 2V_2 = V$$

$$V_{23} = V_2 + V_3 = 2V_2$$

Calculation

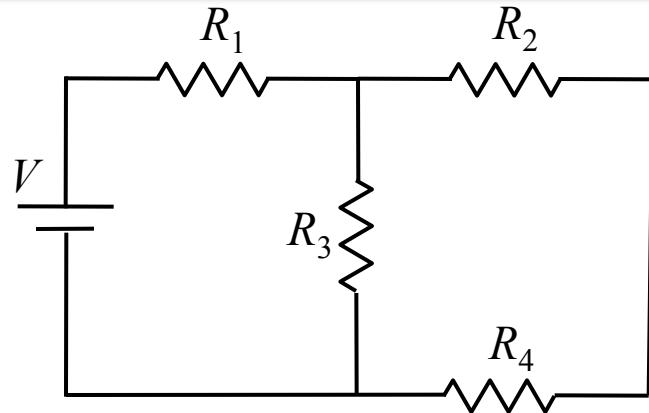

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?

Conceptual Analysis:

Ohm's Law: when current I flows through resistance R , the potential drop V is given by:
 $V = IR$.

Resistances are combined in series and parallel combinations

$$R_{series} = R_a + R_b$$

$$(1/R_{parallel}) = (1/R_a) + (1/R_b)$$


Strategic Analysis:

Combine resistances to form equivalent resistances

Evaluate voltages or currents from Ohm's Law

Expand circuit back using knowledge of voltages and currents

Calculation

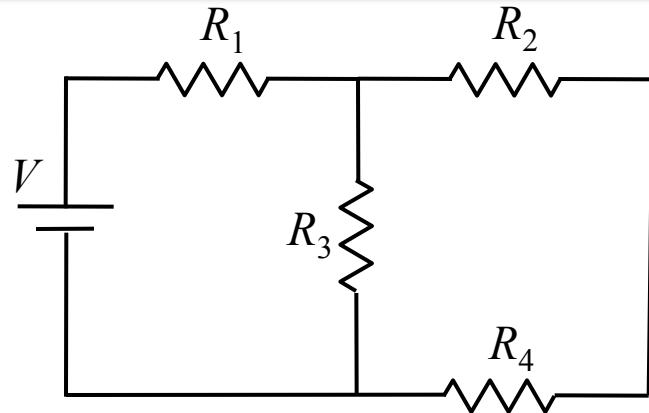

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?


Combine Resistances:

R_1 and R_2 are connected:

A) in series B) in parallel

C) neither in series nor in parallel

Parallel Combination

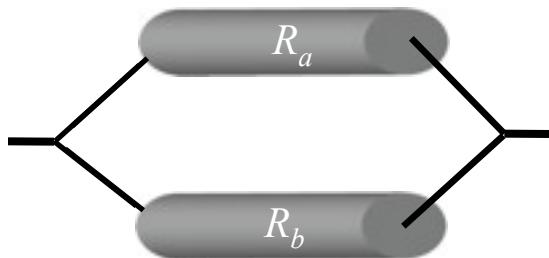


Parallel: Can make a loop that contains only those two resistors

Series Combination



Series : Every loop with resistor 1 also has resistor 2.

Calculation

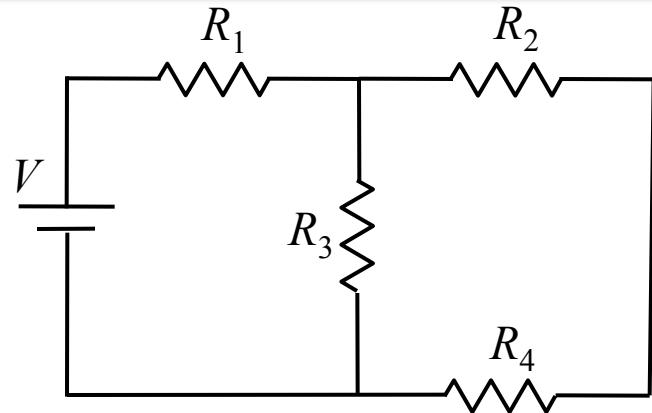

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.


What is V_2 , the voltage across R_2 ?

We first will combine resistances $R_2 + R_3 + R_4$:

Which of the following is true?

- A) R_2 , R_3 and R_4 are connected in series
- B) R_2 , R_3 , and R_4 are connected in parallel
- C) R_3 and R_4 are connected in series (R_{34}) which is connected in parallel with R_2
- D) R_2 and R_4 are connected in series (R_{24}) which is connected in parallel with R_3
- E) R_2 and R_4 are connected in parallel (R_{24}) which is connected in parallel with R_3

Calculation

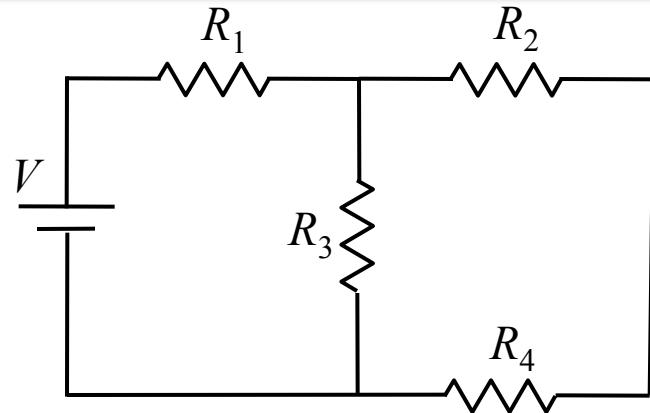


In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.


What is V_2 , the voltage across R_2 ?

R_2 and R_4 are connected in series (R_{24}) which is connected in parallel with R_3 .

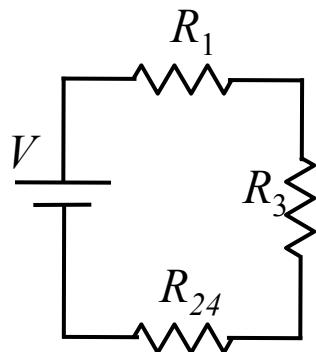
Redraw the circuit using the equivalent resistor R_{24} = series combination of R_2 and R_4 .



(A)

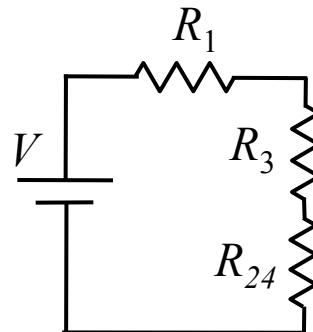


(B)

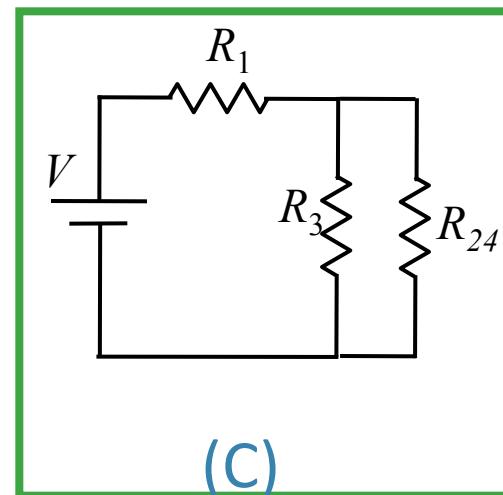

(C)

Calculation

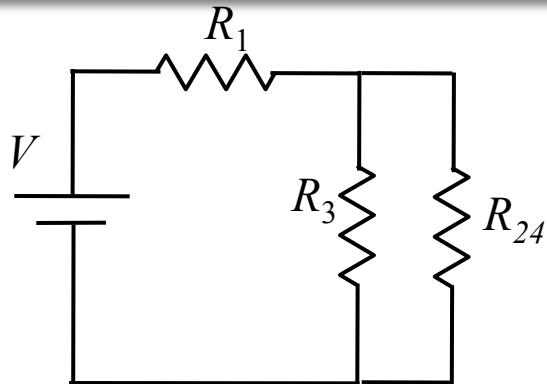

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.

What is V_2 , the voltage across R_2 ?

Combine Resistances:

R_2 and R_4 are connected in series = R_{24}

R_3 and R_{24} are connected in parallel = R_{234}


What is the value of R_{234} ?

A) $R_{234} = 1\ \Omega$ B) $R_{234} = 2\ \Omega$ C) $R_{234} = 4\ \Omega$ D) $R_{234} = 6\ \Omega$

R_2 and R_4 in series $R_{24} = R_2 + R_4 = 2\Omega + 4\Omega = 6\Omega$

$(1/R_{parallel}) = (1/R_a) + (1/R_b)$ $1/R_{234} = (1/3) + (1/6) = (3/6)\ \Omega^{-1}$ $R_{234} = 2\ \Omega$

Calculation

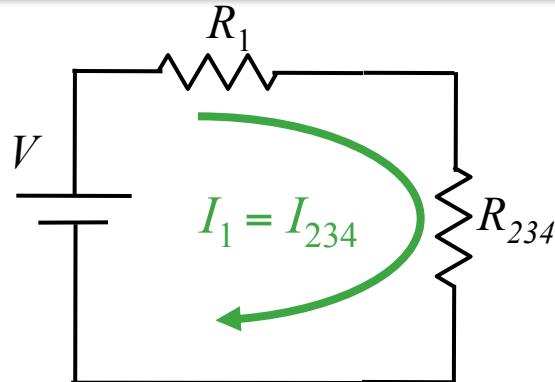


In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.
 $R_{24} = 6\Omega$ $R_{234} = 2\Omega$

What is V_2 , the voltage across R_2 ?




R_1 and R_{234} are in series. $R_{1234} = 1 + 2 = 3 \Omega$

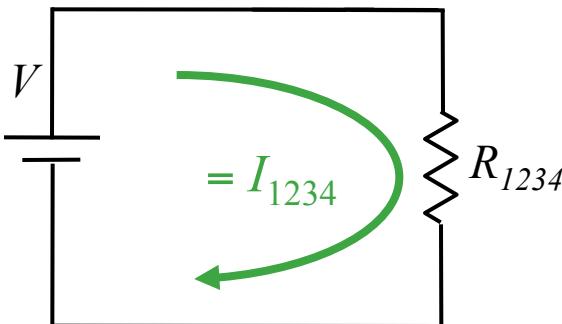Our next task is to calculate the total current in the circuit




Ohm's Law tells us: $I_{1234} = V/R_{1234}$
 $= 18 / 3$
 $= 6$ Amps

Calculation

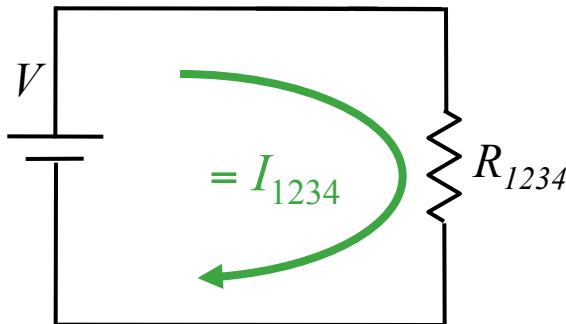

In the circuit shown: $V = 18V$,
 $R_1 = 1\Omega$, $R_2 = 2\Omega$, $R_3 = 3\Omega$, and $R_4 = 4\Omega$.
 $R_{24} = 6\Omega$ $R_{234} = 2\Omega$ $I_{1234} = 6 A$

What is V_2 , the voltage across R_2 ?

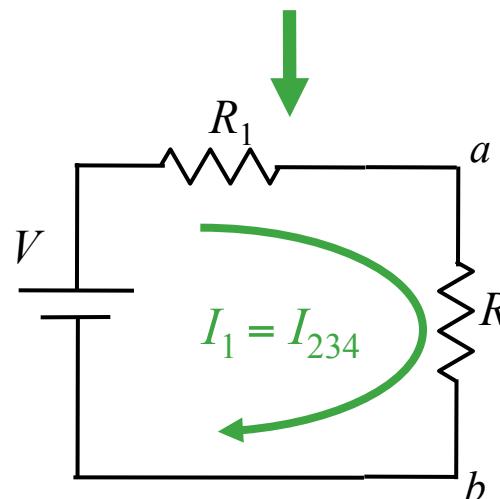



$I_{234} = I_{1234}$ Since R_1 in series with R_{234}

$$\begin{aligned}V_{234} &= I_{234} R_{234} \\&= 6 \times 2 \\&= 12 \text{ Volts}\end{aligned}$$

What is V_{ab} , the voltage across R_{234} ?

A) $V_{ab} = 1 V$ B) $V_{ab} = 2 V$ C) $V_{ab} = 9 V$ D) $V_{ab} = 12 V$ E) $V_{ab} = 16 V$

Calculation

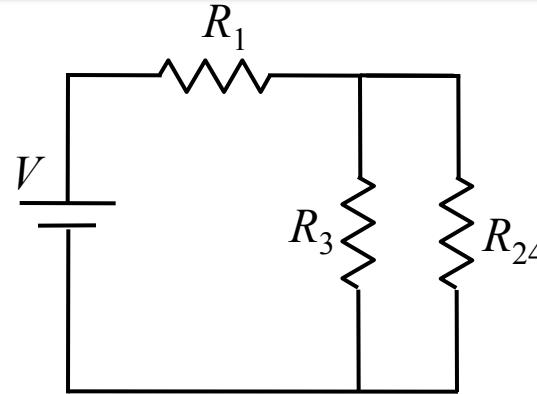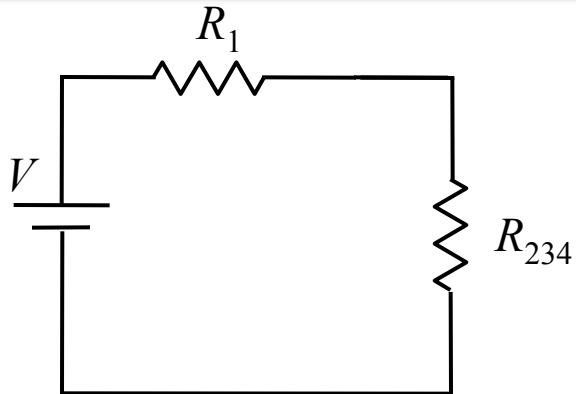

Which of the following are true?

A) $V_{234} = V_{24}$

B) $I_{234} = I_{24}$

C) Both A+B

D) None

R_3 and R_{24} were combined in parallel to get R_{234}



Voltages are same! What is V_2 ?

$$V = 18V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$R_4 = 4\Omega$$

$$R_{24} = 6\Omega$$

$$R_{234} = 2\Omega$$

$$I_{1234} = 6 \text{ Amps}$$

$$I_{234} = 6 \text{ Amps}$$

$$V_{234} = 12V$$



Ohm's Law

$$I_{24} = V_{24} / R_{24}$$

$$= 12 / 6$$

$$= 2 \text{ Amps}$$

Calculation

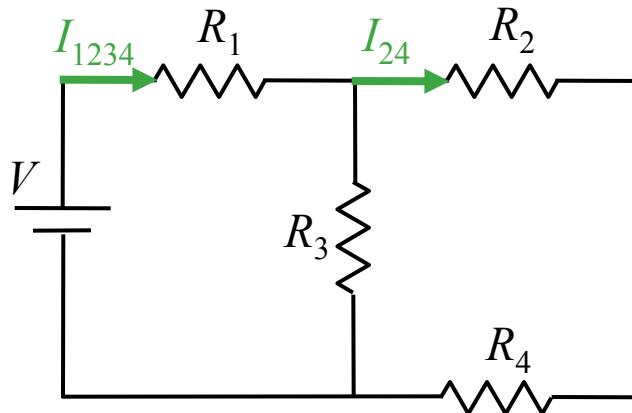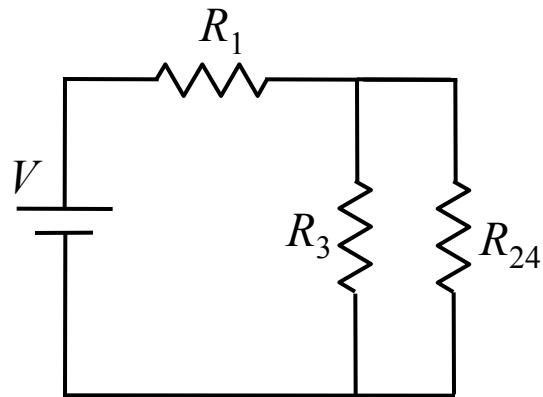

Which of the following are true?

A) $V_{24} = V_2$ B) $I_{24} = I_2$ C) Both A+B D) None

R_2 and R_4 are combined in series to get R_{24} → Currents are same!

Ohm's Law

$$\begin{aligned}
 V_2 &= I_2 \cdot R_2 \\
 &= 2 \times 2 \\
 &= 4 \text{ Volts!}
 \end{aligned}$$

The Problem Can Now Be Solved!

$$V = 18V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 3\Omega$$

$$R_4 = 4\Omega$$

$$R_{24} = 6\Omega$$

$$R_{234} = 2\Omega$$

$$I_{1234} = 6 \text{ Amps}$$

$$I_{234} = 6 \text{ Amps}$$



$$V_{234} = 12V$$

$$V_{24} = 12V$$

$$I_{24} = 2 \text{ Amps}$$

What is V_2 ?

Quick Follow-Ups

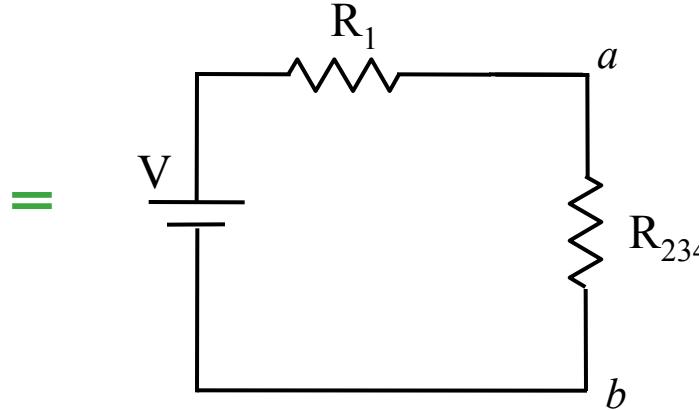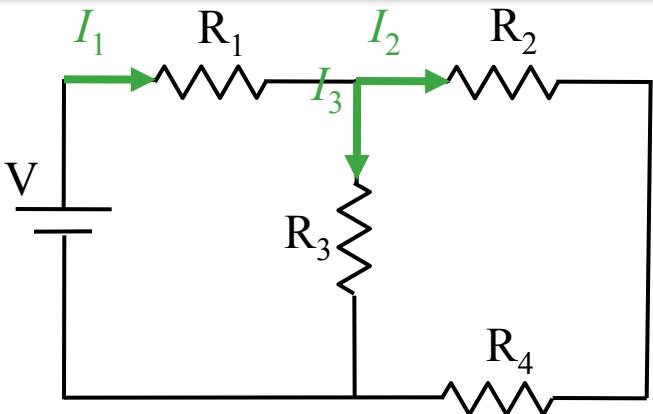

What is I_3 ?

A) $I_3 = 2 A$ B) $I_3 = 3 A$

C) $I_3 = 4 A$

$$V_3 = V_{234} = 12V \rightarrow I_3 = V_3/R_3 = 12V/3\Omega = 4A$$

$V = 18V$
 $R_1 = 1\Omega$
 $R_2 = 2\Omega$
 $R_3 = 3\Omega$
 $R_4 = 4\Omega$
 $R_{24} = 6\Omega$
 $R_{234} = 2\Omega$
 $V_{234} = 12V$
 $V_2 = 4V$
 $I_{1234} = 6 \text{ Amps}$

What is I_1 ?

We know $I_1 = I_{1234} = 6 A$

NOTE: $I_2 = V_2/R_2 = 4/2 = 2 A$ $\rightarrow I_1 = I_2 + I_3$ Make Sense?