


# Electricity & Magnetism

## Lecture 18


### Today's Concepts:

- A) Induction
- B) RL Circuits

#### INDUCTION and RL CIRCUITS

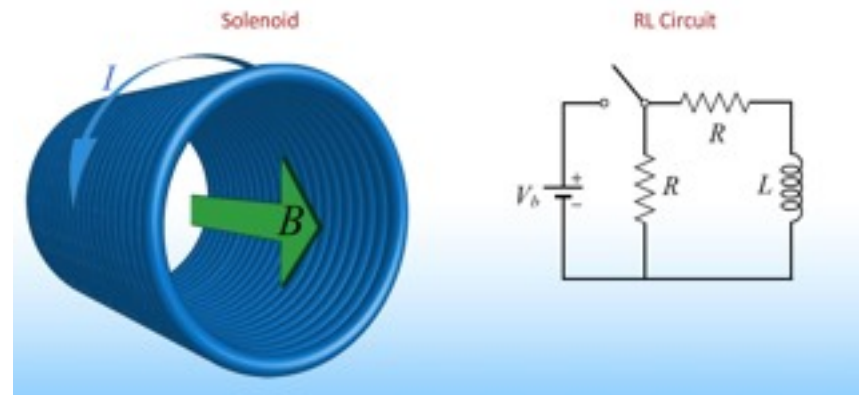

# From the Prelecture: Self Inductance

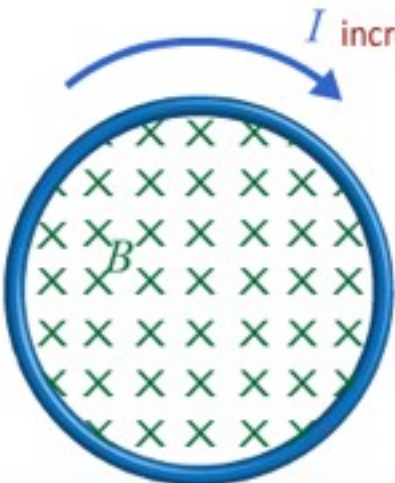

$I$  increases

Faraday's Law

$$\mathcal{E} = -\frac{d\Phi_B}{dt} = -\frac{d(LI)}{dt} = -L \frac{dI}{dt}$$


Self-Inductance

$$L \equiv \frac{\Phi_B}{I}$$

SI Unit

$$H = T \cdot m^2 / A$$

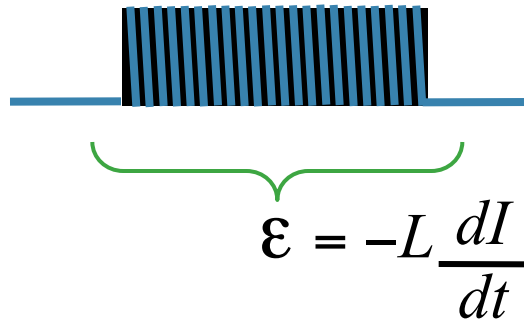
Wrap a wire into a coil to make an “inductor”...



# What this really means:

*emf* induced across  $L$  tries to keep  $I$  constant.

$$\mathcal{E}_L = -L \frac{dI}{dt}$$

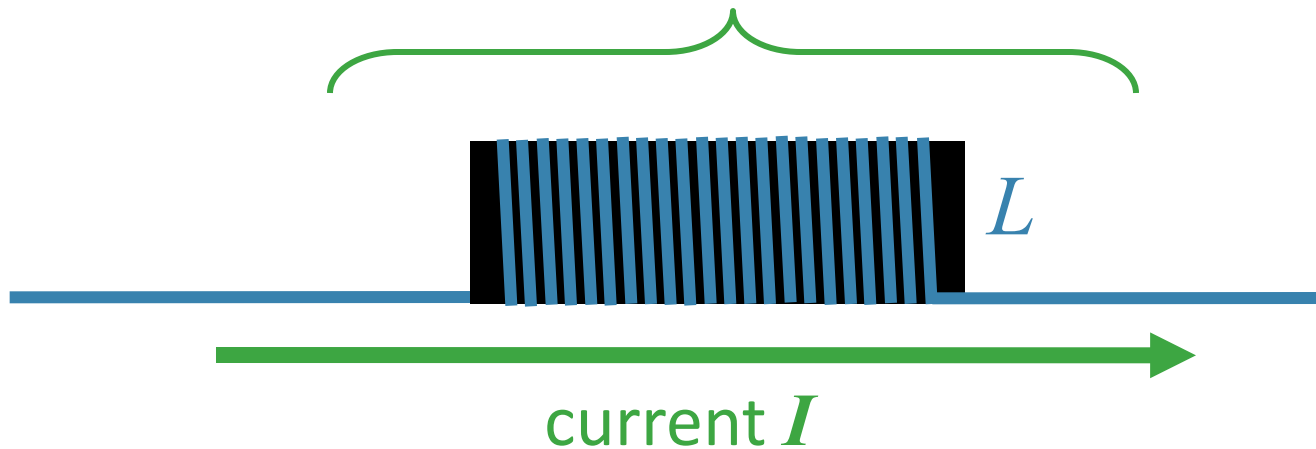

Inductors prevent discontinuous current changes!



It's like inertia!

## CheckPoint 2

Two solenoids are made with the same cross sectional area and total number of turns. Inductor *B* is twice as long as inductor *A*

$$L_B = \mu_0 n^2 \pi r^2 z$$

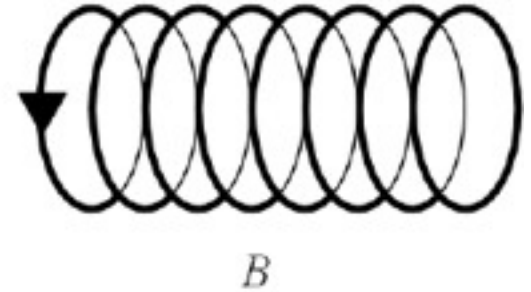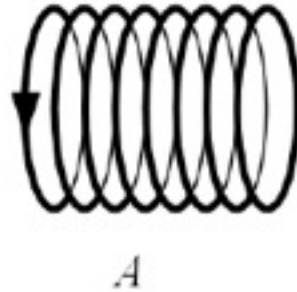$\uparrow$                        $\uparrow$   
 $(1/2)^2$                   2




→  $L_B = \frac{1}{2} L_A$

Compare the inductance of the two solenoids

- A)  $L_A = 4 L_B$
- B)  $L_A = 2 L_B$
- C)  $L_A = L_B$
- D)  $L_A = (1/2) L_B$
- E)  $L_A = (1/4) L_B$

# How to think about RL circuits Episode 1:

When no current is flowing initially:

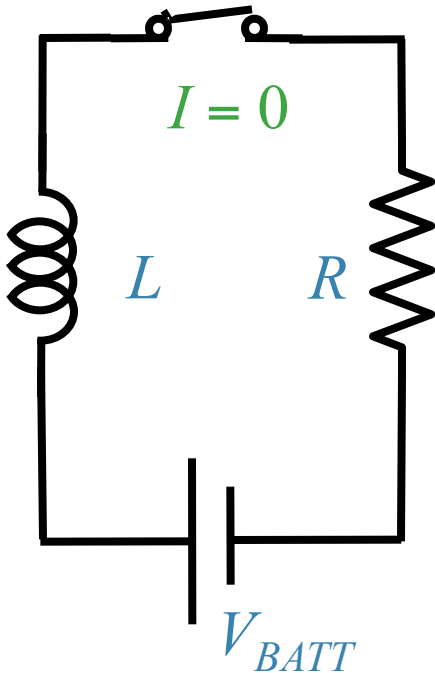


At  $t = 0$ :

$$I = 0$$

$$V_L = V_{BATT}$$

$$V_R = 0$$

( $L$  is like a giant resistor)

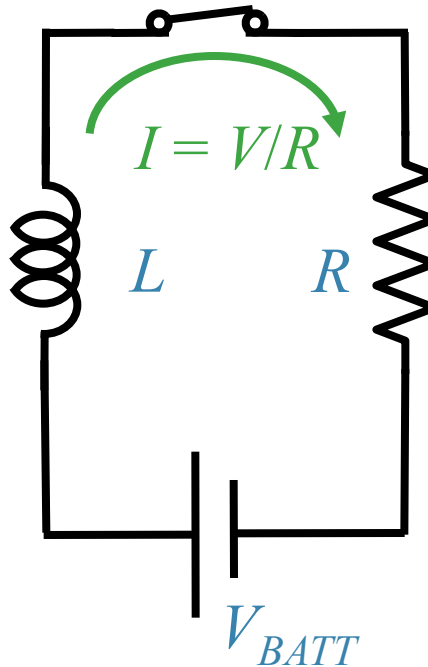


At  $t \gg L/R$ :

$$V_L = 0$$

$$V_R = V_{BATT}$$

$$I = V_{BATT}/R$$

( $L$  is like a short circuit)

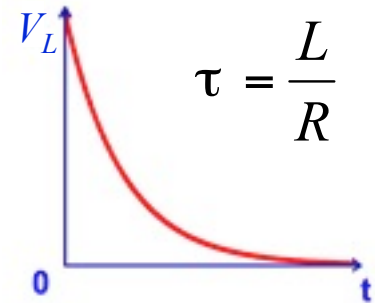


# CheckPoint 4



In the circuit, the switch has been open for a long time, and the current is zero everywhere.

At time  $t = 0$  the switch is closed.

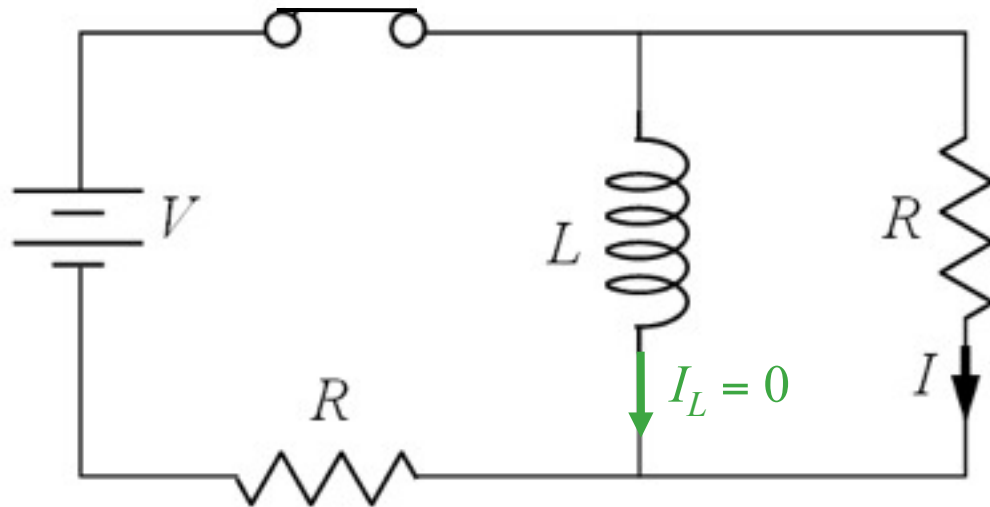What is the current  $I$  through the vertical resistor immediately after the switch is closed?



(+ is in the direction of the arrow)

- A)  $I = V/R$
- B)  $I = V/2R$
- C)  $I = 0$
- D)  $I = -V/2R$
- E)  $I = -V/R$


# RL Circuit (Long Time)



What is the current  $I$  through the vertical resistor after the switch has been closed for a long time?





(+ is in the direction of the arrow)

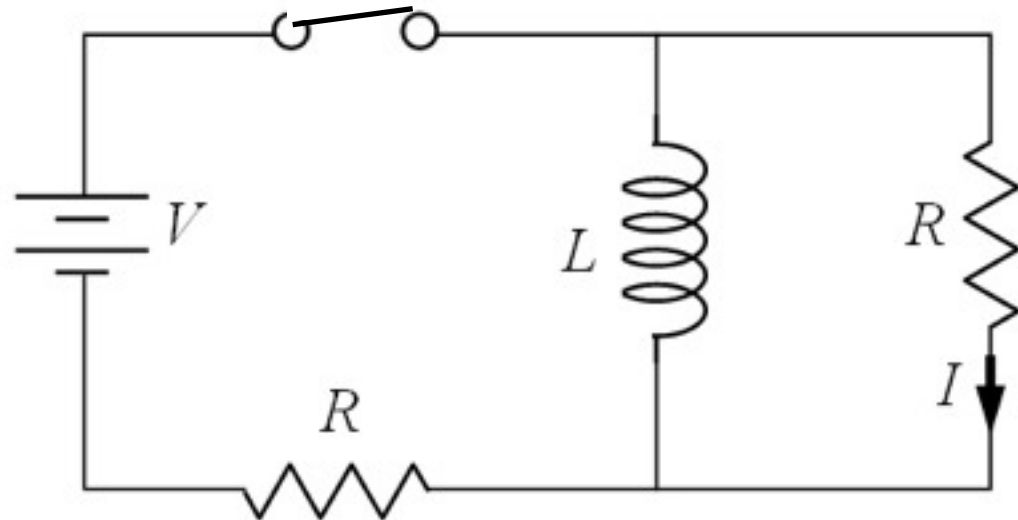- A)  $I = V/R$
- B)  $I = V/2R$
- C)  $I = 0$
- D)  $I = -V/2R$
- E)  $I = -V/R$


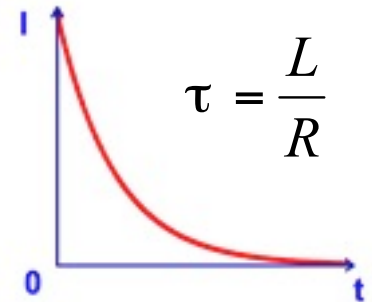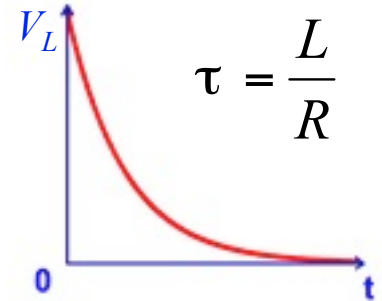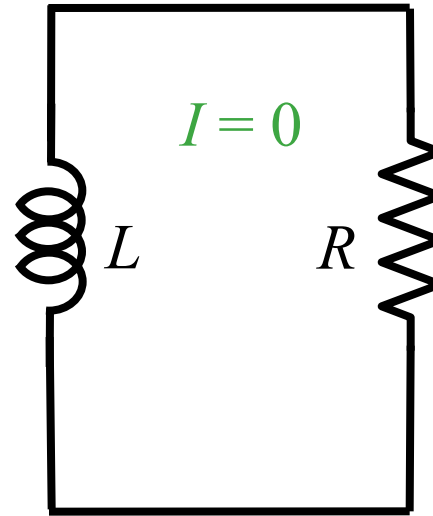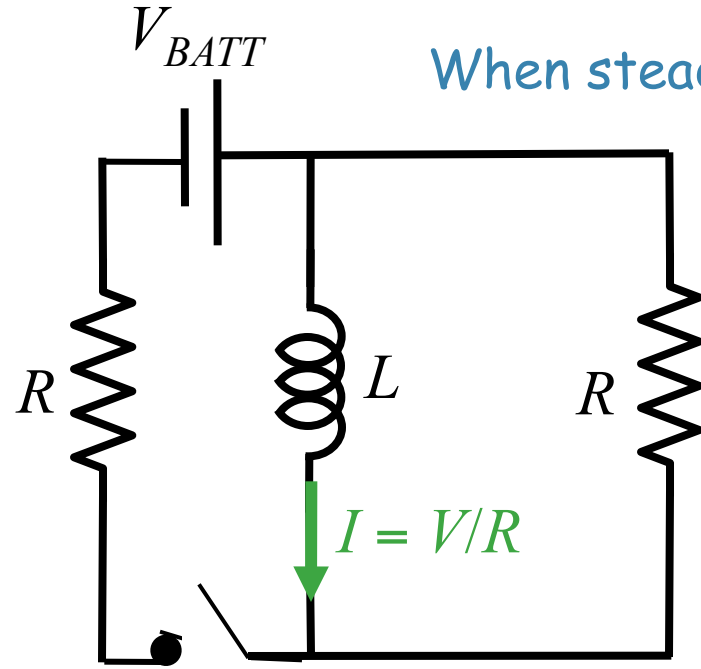
# How to Think about RL Circuits Episode 2:

When steady current is flowing initially:



At  $t = 0$ :

$$\begin{aligned} I &= V_{BATT}/R \\ V_R &= IR \\ V_L &= V_R \end{aligned}$$

At  $t \gg L/R$ :

$$\begin{aligned} I &= 0 \\ V_L &= 0 \\ V_R &= 0 \end{aligned}$$




# CheckPoint 6



After a long time, the switch is opened, abruptly disconnecting the battery from the circuit.


What is the current  $I$  through the vertical resistor immediately after the switch is opened?

(+ is in the direction of the arrow)

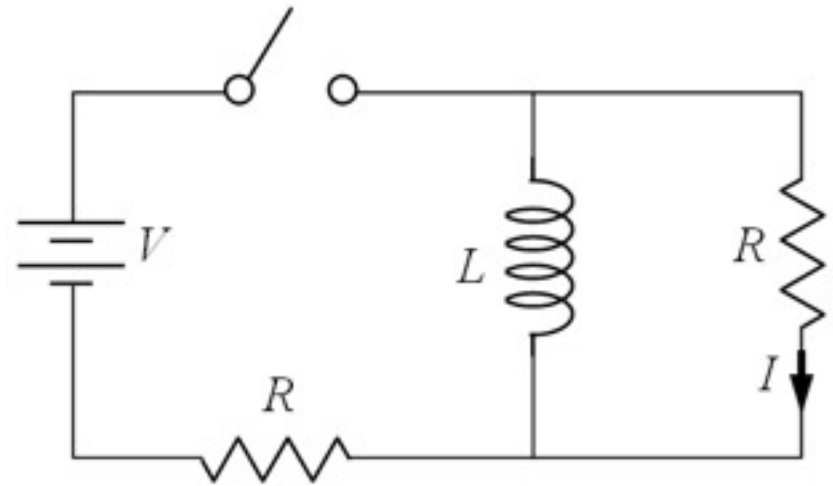

- A)  $I = V/R$
- B)  $I = V/2R$
- C)  $I = 0$
- D)  $I = -V/2R$
- E)  $I = -V/R$



# Why is there Exponential Behavior?


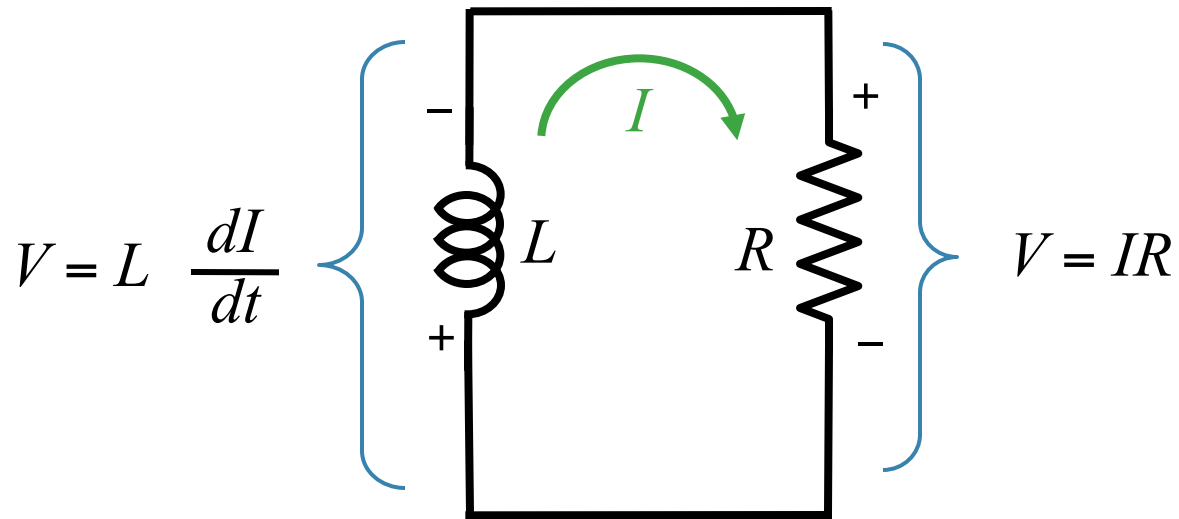


$$L \frac{dI}{dt} + IR = 0$$

$$I(t) = I_0 e^{-tR/L} = I_0 e^{-t/\tau}$$



where  $\tau = \frac{L}{R}$

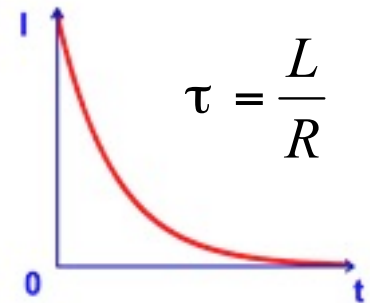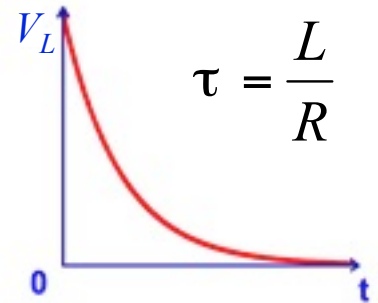

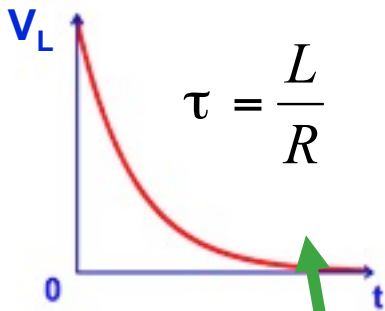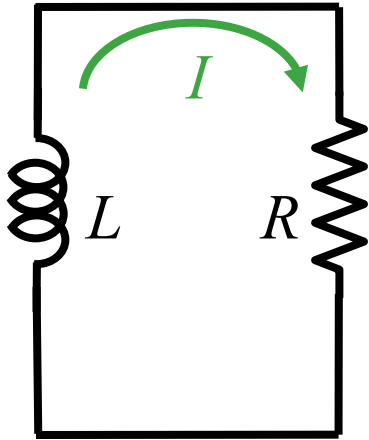


Lecture:

Time Constant  $\tau = \frac{L}{2R}$

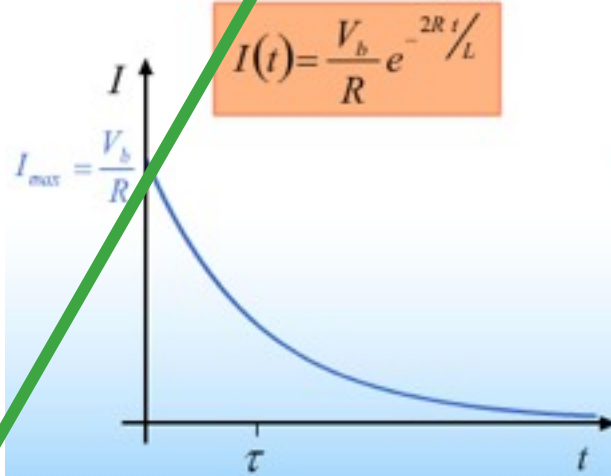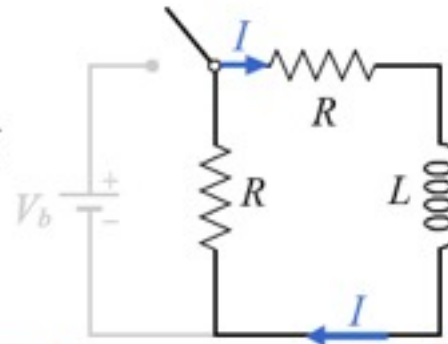

Prelecture:

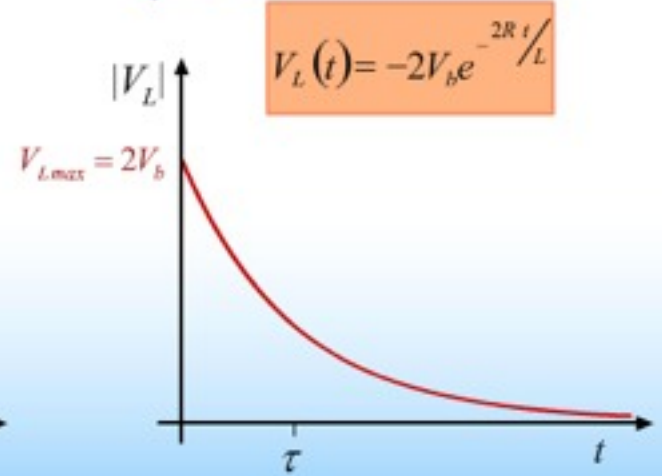


Did we mess up?

No: The resistance is simply twice as big in one case.

# CheckPoint 8




After long time at 0, moved to 1

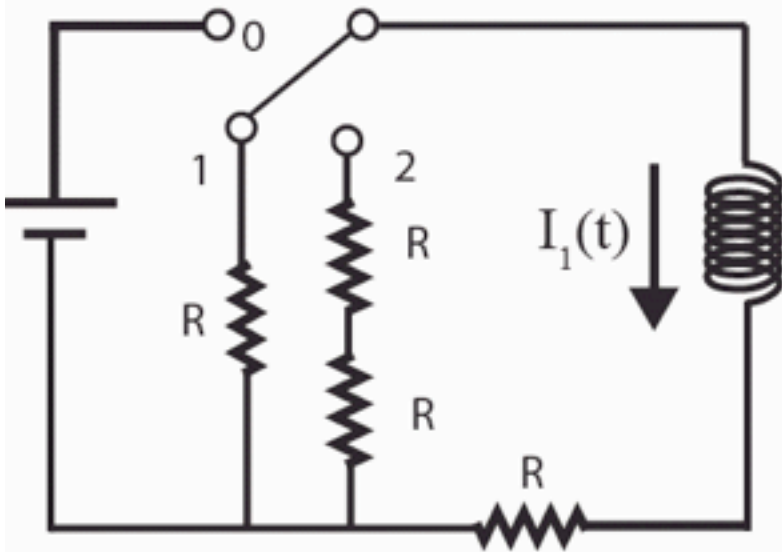

Case 1

After long time at 0, moved to 2

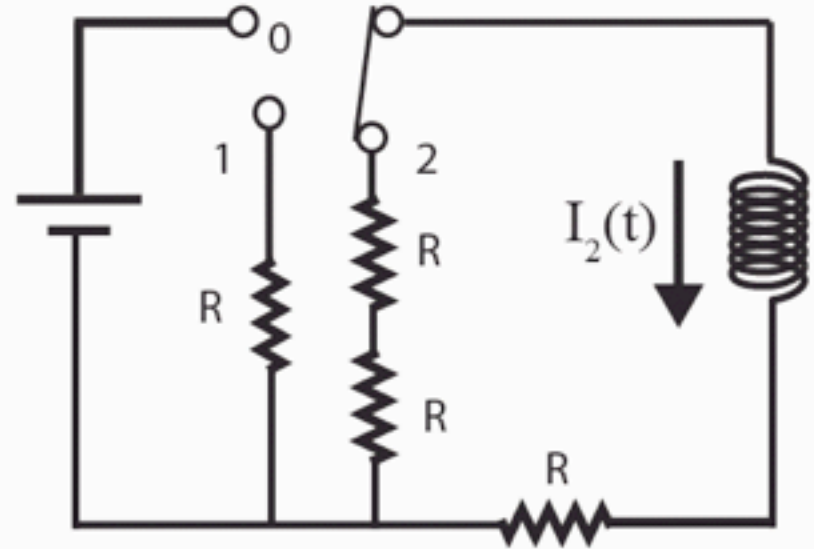

Case 2


After switch moved, which case has larger time constant?

- A) Case 1
- B) Case 2
- C) The same

# CheckPoint 10




After long time at 0, moved to 1

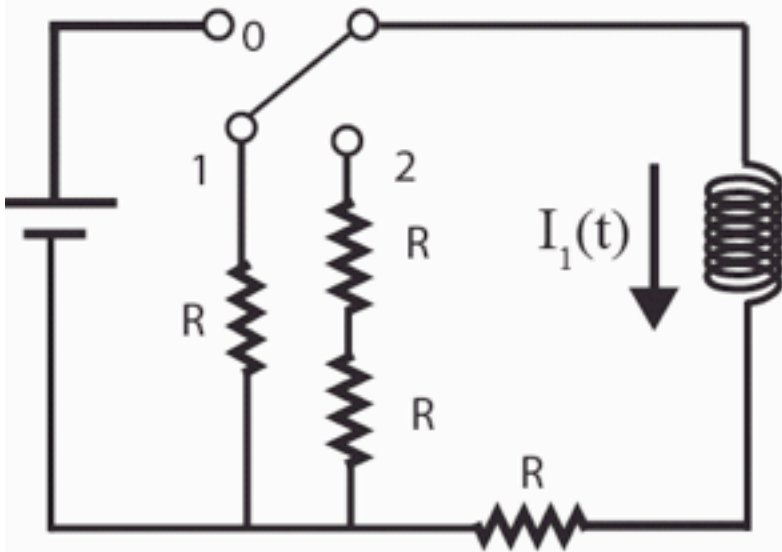

Case 1

After long time at 0, moved to 2

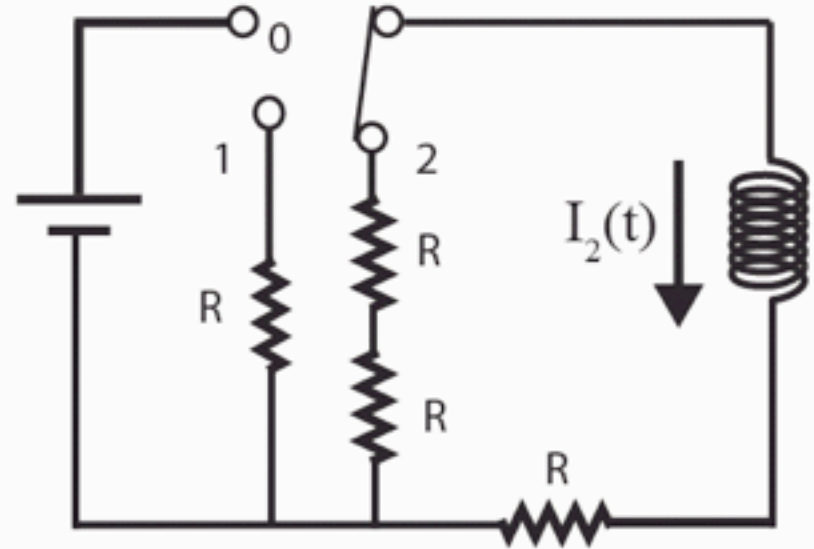

Case 2


Immediately after switch moved,  
in which case is the voltage across  
the inductor larger?

- A) Case 1
- B) Case 2
- C) The same

# CheckPoint 12




After long time at 0, moved to 1

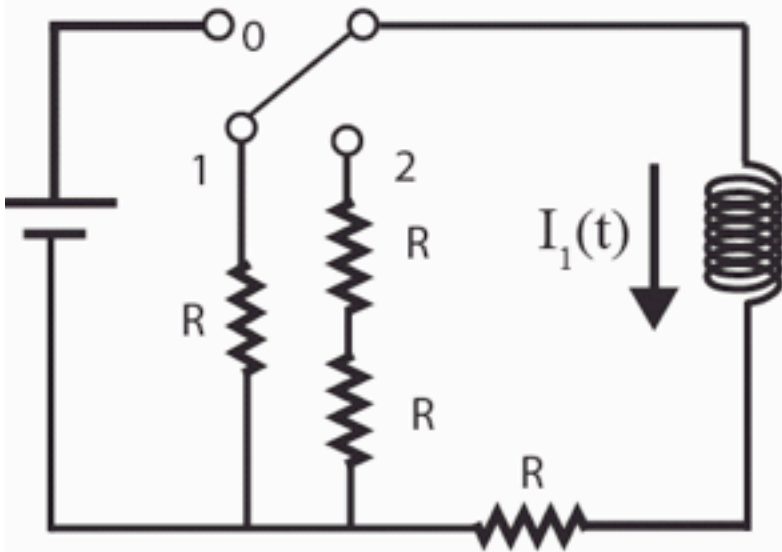

Case 1

After long time at 0, moved to 2

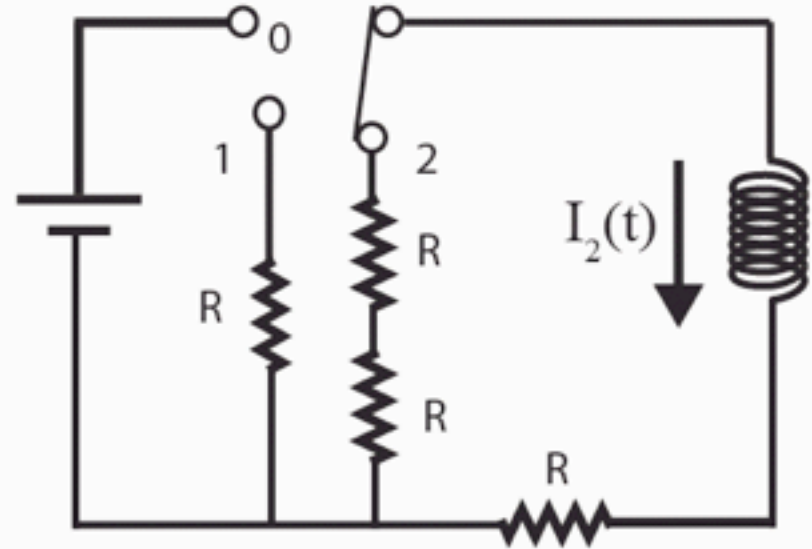


Case 2

After switch moved for finite time, in which case is the current through the inductor larger?

- A) Case 1
- B) Case 2
- C) The same
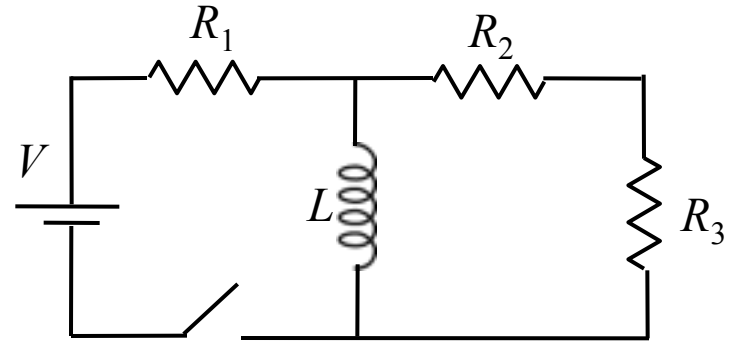
# Calculation

The switch in the circuit shown has been open for a long time. At  $t = 0$ , the switch is closed.



What is  $dI_L/dt$ , the time rate of change of the current through the inductor immediately after switch is closed

## Conceptual Analysis

Once switch is closed, currents will flow through this 2-loop circuit.

$KVR$  and  $KCR$  can be used to determine currents as a function of time.

## Strategic Analysis

Determine currents immediately after switch is closed.


Determine voltage across inductor immediately after switch is closed.

Determine  $dI_L/dt$  immediately after switch is closed.
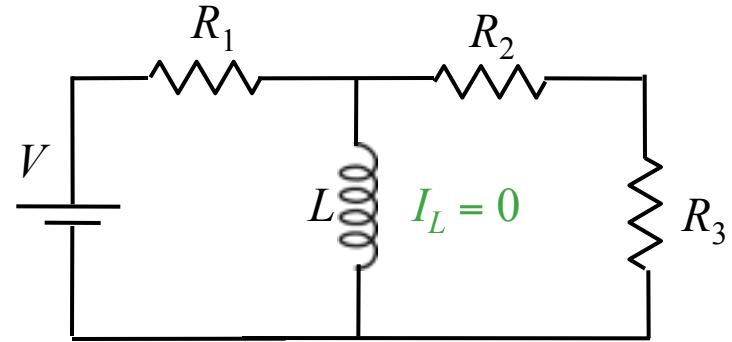
# Calculation



The switch in the circuit shown has been open for a long time. At  $t = 0$ , the switch is closed.



What is  $I_L$ , the current in the inductor, immediately after the switch is closed?


- A)  $I_L = V/R_1$  up      B)  $I_L = V/R_1$  down      C)  $I_L = 0$


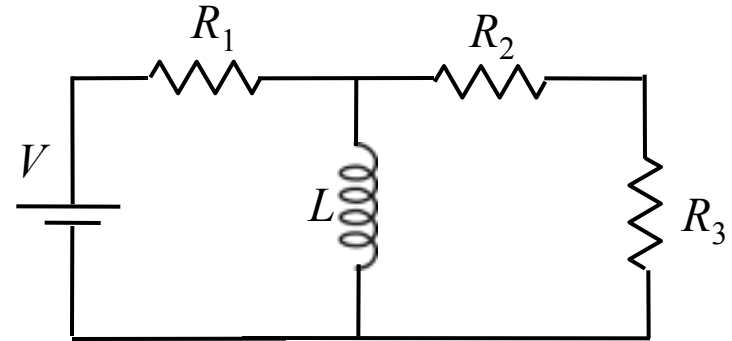
# Calculation



The switch in the circuit shown has been open for a long time. At  $t = 0$ , the switch is closed.



$$I_L(t = 0+) = 0$$


What is the magnitude of  $I_2$ , the current in  $R_2$ , immediately after the switch is closed?

A)  $I_2 = \frac{V}{R_1}$       B)  $I_2 = \frac{V}{R_2 + R_3}$       C)  $I_2 = \frac{V}{R_1 + R_2 + R_3}$       D)  $I_2 = \frac{VR_2R_3}{R_2 + R_3}$
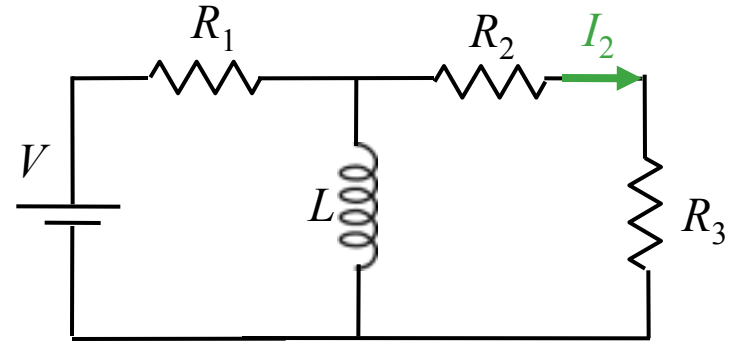
# Calculation



The switch in the circuit shown has been open for a long time. At  $t = 0$ , the switch is closed.



$$I_L(t = 0+) = 0 \quad I_2(t = 0+) = V/(R_1 + R_2 + R_3)$$

What is the magnitude of  $V_L$ , the voltage across the inductor, immediately after the switch is closed?


- A)**  $V_L = V \frac{R_2 R_3}{R_1}$       **B)**  $V_L = V$       **C)**  $V_L = 0$       **D)**  $V_L = V \frac{R_2 R_3}{R_1 (R_2 + R_3)}$       **E)**  $V_L = V \frac{R_2 + R_3}{R_1 + R_2 + R_3}$
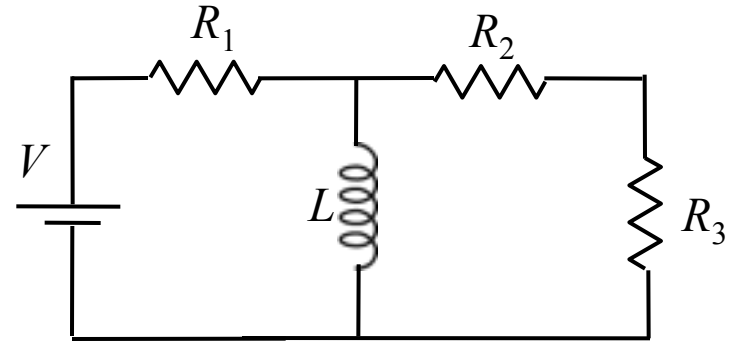
# Calculation



The switch in the circuit shown has been open for a long time. At  $t = 0$ , the switch is closed.

What is  $dI_L/dt$ , the time rate of change of the current through the inductor immediately after switch is closed



$$V_L(t = 0+) = V(R_2 + R_3)/(R_1 + R_2 + R_3)$$

A)  $\frac{dI_L}{dt} = \frac{V}{L} \frac{R_2 + R_3}{R_1}$

B)  $\frac{dI_L}{dt} = 0$

C)  $\frac{dI_L}{dt} = \frac{V}{L} \frac{R_2 + R_3}{R_1 + R_2 + R_3}$

D)  $\frac{dI_L}{dt} = \frac{V}{L}$


# Follow Up



The switch in the circuit shown has been closed for a long time.

What is  $I_2$ , the current through  $R_2$ ?

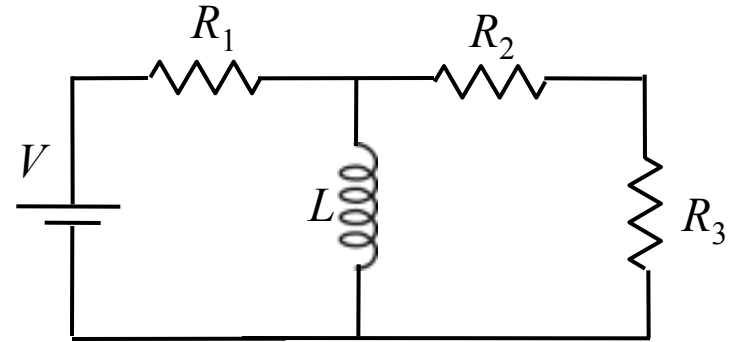(Positive values indicate current flows to the right)



- A)  $I_2 = +\frac{V}{R_2 + R_3}$     B)  $I_2 = +\frac{V(R_2 R_3)}{R_1 + R_2 + R_3}$     C)  $I_2 = 0$     D)  $I_2 = -\frac{V}{R_2 + R_3}$


## Follow Up 2



The switch in the circuit shown has been closed for a long time at which point, the switch is opened.

What is  $I_2$ , the current through  $R_2$  immediately after switch is opened ?

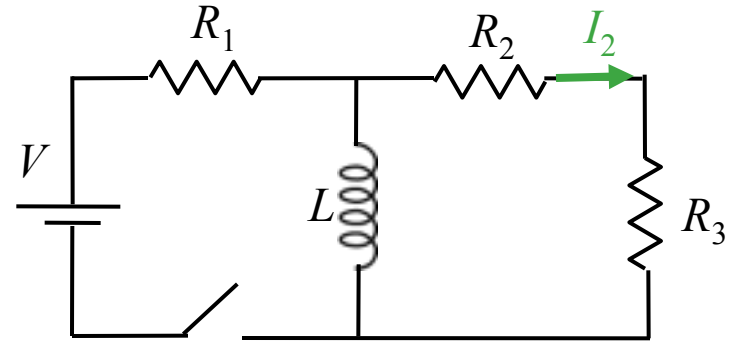(Positive values indicate current flows to the right)



A)  $I_2 = +\frac{V}{R_1 + R_2 + R_3}$

B)  $I_2 = +\frac{V}{R_1}$

C)  $I_2 = 0$

D)  $I_2 = -\frac{V}{R_1}$

E)  $I_2 = -\frac{V}{R_1 + R_2 + R_3}$