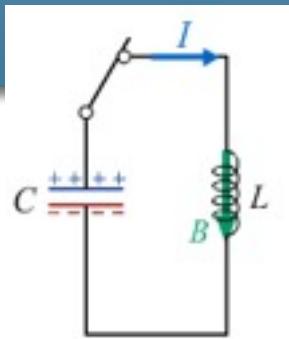





Electricity & Magnetism

Lecture 19



Today's Concepts:

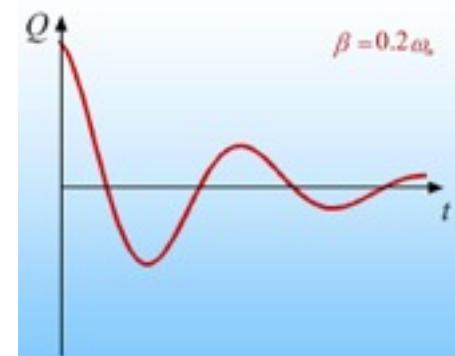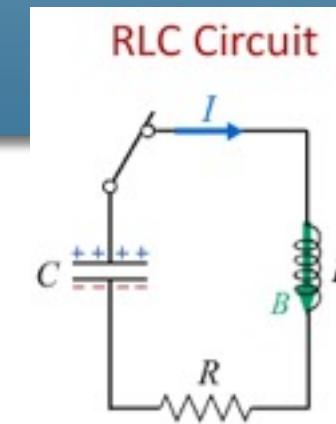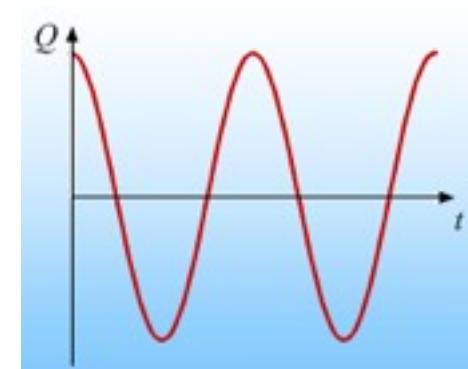- A) Oscillation Frequency
- B) Energy
- C) Damping





I am ...

- A. Confused
- B. Somewhat Confused
- C. So-so
- D. Somewhat Confident
- E. Confident

Your Comments

“All of this stuff, I wish we could go slower but I know we cant.”

TOO TRUE: Hang in there, we'll do our best to work on the issues....


“Differential equations have taken over my life. I'm not sure I approve.”

“How did yawl derive the differential equations?”


“Why do capacitors start off with a charge of zero when the switch is opened? shouldn't they start off with charge? “

It all depends on how the circuit was started. You have to determine the initial conditions from the problem statement

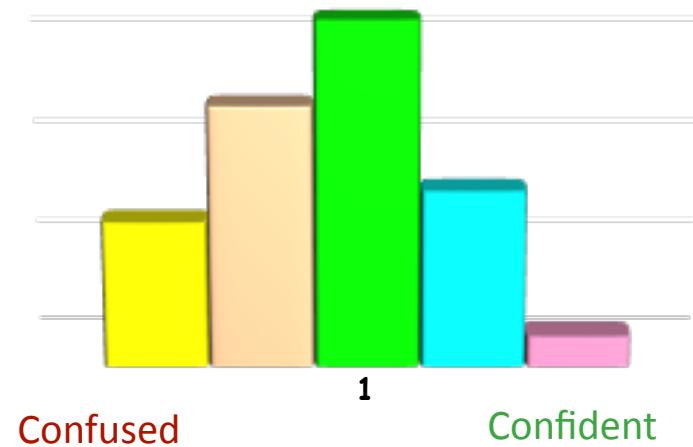Differential Equations Do Determine Much Behavior in Physics. We will show corresponding equations in mechanics today



LC Circuit

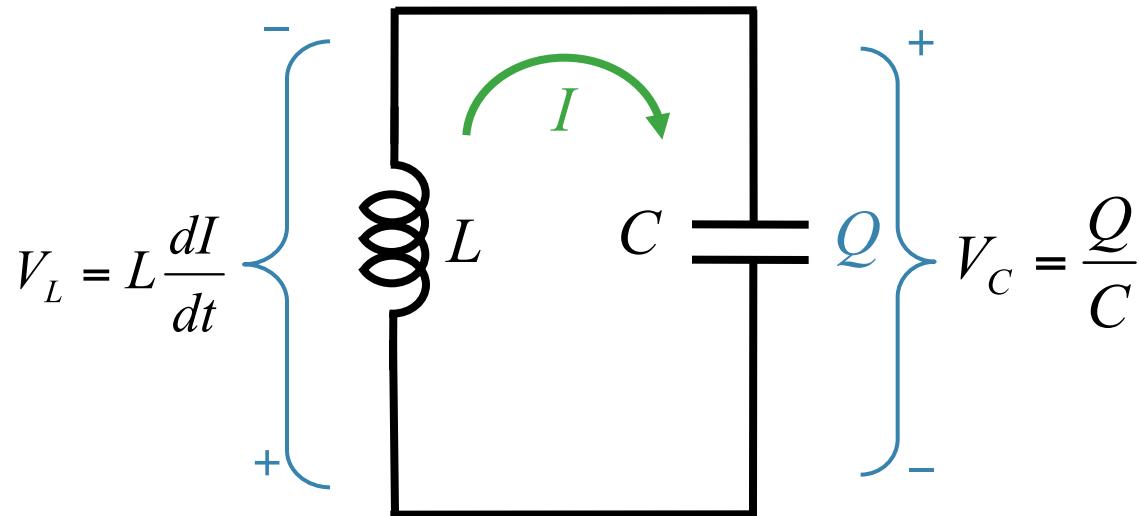

Circuit Equation: $\frac{Q}{C} + L \frac{dI}{dt} = 0$

$$I = \frac{dQ}{dt} \rightarrow \frac{d^2Q}{dt^2} = -\frac{Q}{LC} \rightarrow \frac{d^2Q}{dt^2} = -\omega^2 Q$$


where

$$\omega = \frac{1}{\sqrt{LC}}$$

$$m \leftrightarrow L$$


$$\frac{d^2Q}{dt^2} = -\omega^2 Q$$

$$\omega = \frac{1}{\sqrt{LC}}$$

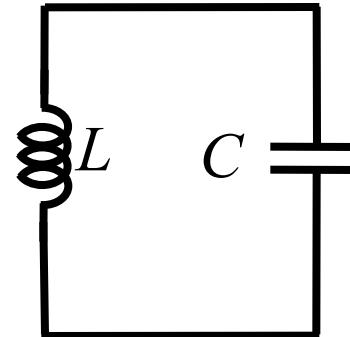

$$\frac{d^2x}{dt^2} = -\omega^2 x$$

$$\omega = \sqrt{\frac{k}{m}}$$

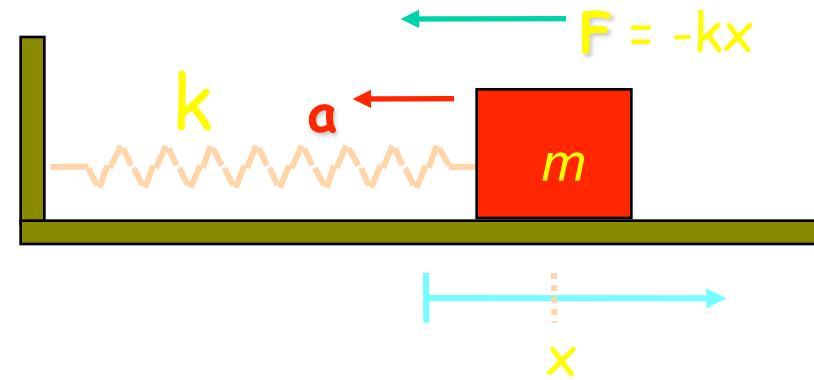



Same thing if we notice that

$$k \leftrightarrow \frac{1}{C}$$

and


$$m \leftrightarrow L$$

Time Dependence

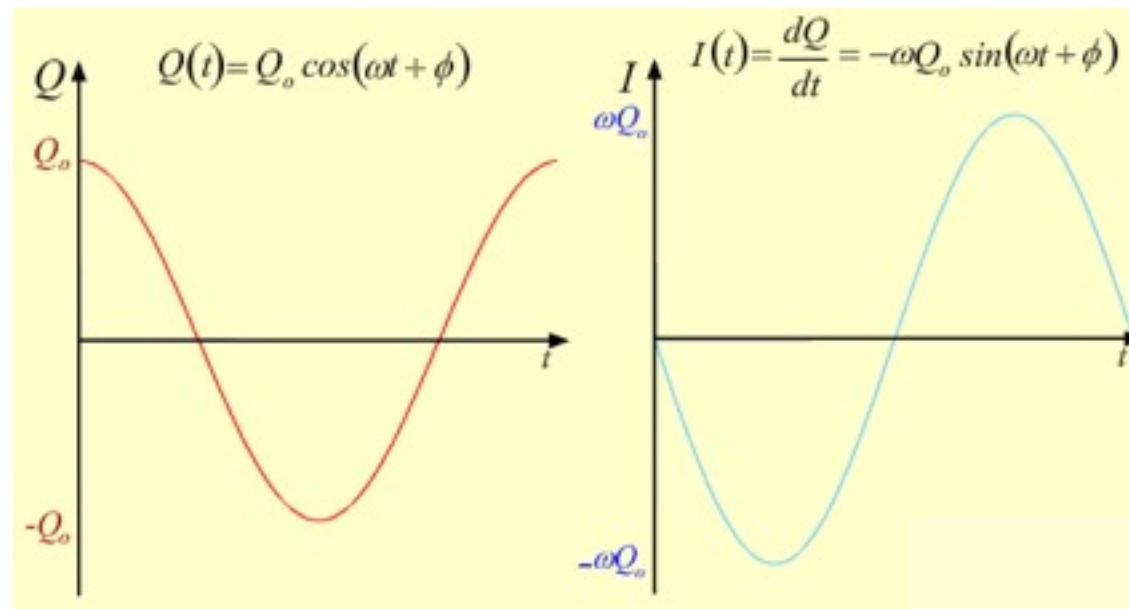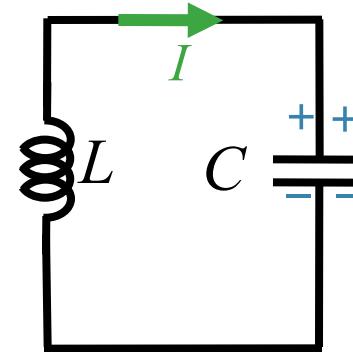

CheckPoint 2

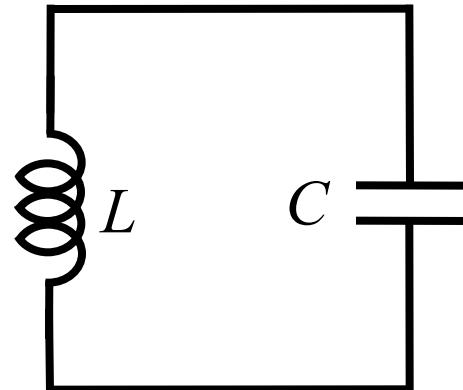At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.




What is the potential difference across the inductor at $t = 0$?

- A) $V_L = 0$
- B) $V_L = Q_{max}/C$ since $V_L = V_C$
- C) $V_L = Q_{max}/2C$


The voltage across the capacitor is Q_{max}/C Kirchhoff's Voltage Rule implies that must also be equal to the voltage across the inductor

Pendulum.

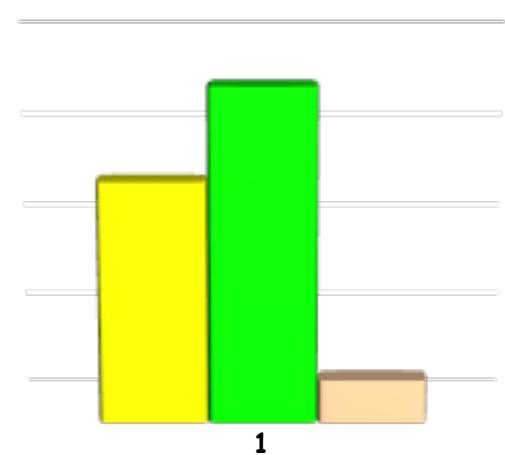

CheckPoint 4

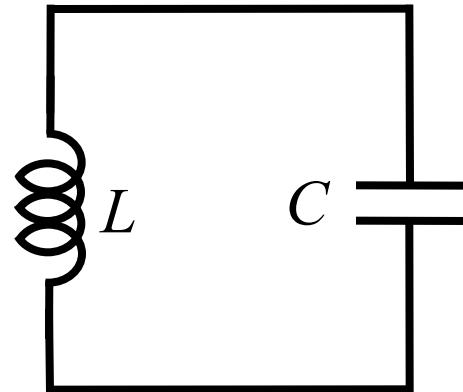
At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.



What is the potential difference across the inductor when the current is maximum?


- A) $V_L = 0$
- B) $V_L = Q_{max}/C$
- C) $V_L = Q_{max}/2C$

dI/dt is zero when current is maximum

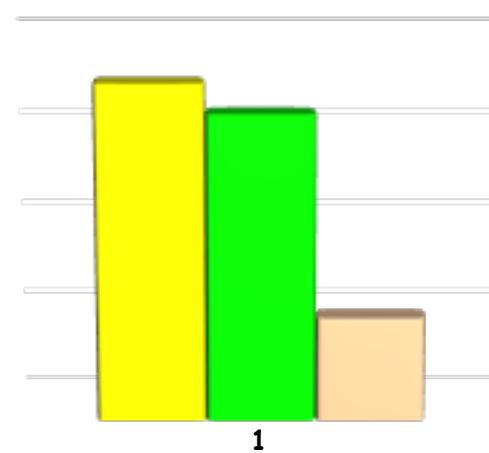

CheckPoint 6

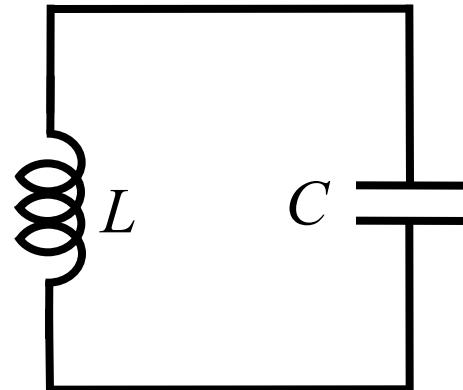At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.



How much energy is stored in the capacitor when the current is a maximum ?


- A) $U = Q_{max}^2/(2C)$
- B) $U = Q_{max}^2/(4C)$
- C) $U = 0$

Total Energy is constant!

$$U_{Lmax} = \frac{1}{2} L I_{max}^2$$

$$U_{Cmax} = Q_{max}^2/2C$$


$I = \text{max}$ when $Q = 0$

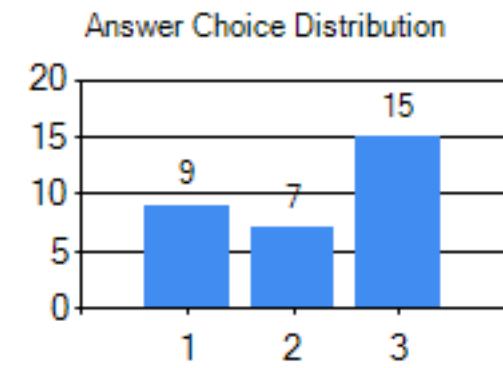

CheckPoint 8

The capacitor is charged such that the top plate has a charge $+Q_0$ and the bottom plate $-Q_0$. At time $t = 0$, the switch is closed and the circuit oscillates with frequency $\omega = 500$ radians/s.

What is the value of the capacitor C ?

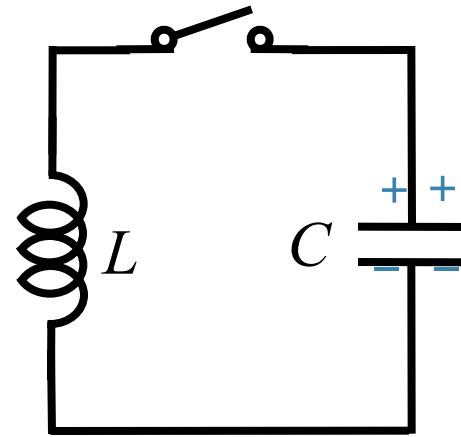


$$L = 4 \times 10^{-3} \text{ H}$$
$$\omega = 500 \text{ rad/s}$$

A) $C = 1 \times 10^{-3} \text{ F}$



B) $C = 2 \times 10^{-3} \text{ F}$

C) $C = 4 \times 10^{-3} \text{ F}$

$$\omega = \frac{1}{\sqrt{LC}} \rightarrow C = \frac{1}{\omega^2 L} = \frac{1}{(25 \times 10^4)(4 \times 10^{-3})} = 10^{-3}$$

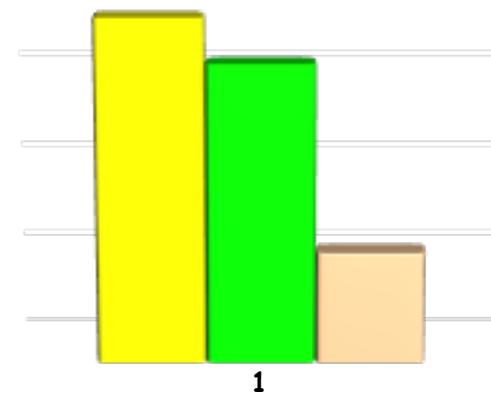

CheckPoint 10

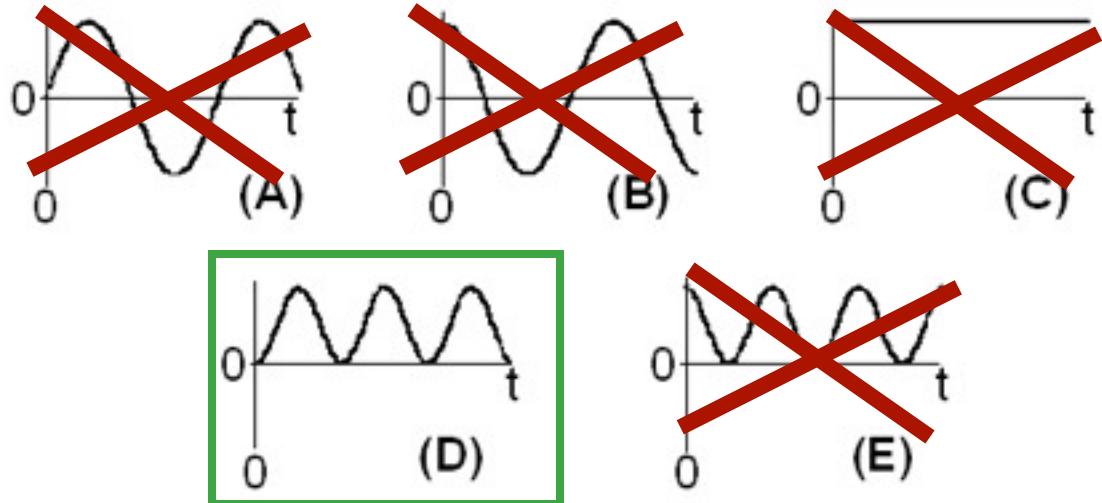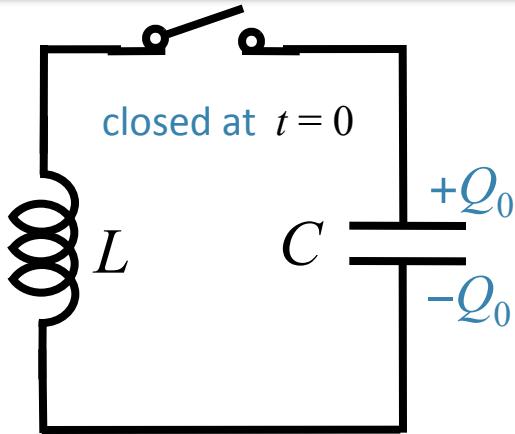


Which plot best represents the energy in the inductor as a function of time starting just after the switch is closed?

$$U_L = \frac{1}{2} L I^2$$

Energy proportional to $I^2 \Rightarrow C$ cannot be negative


Current is changing $\Rightarrow U_L$ is not constant

Initial current is zero

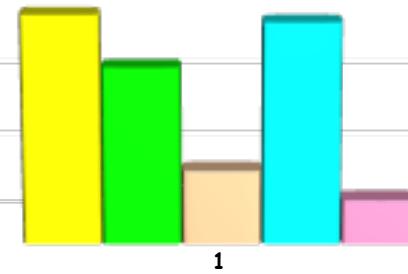


CheckPoint 12

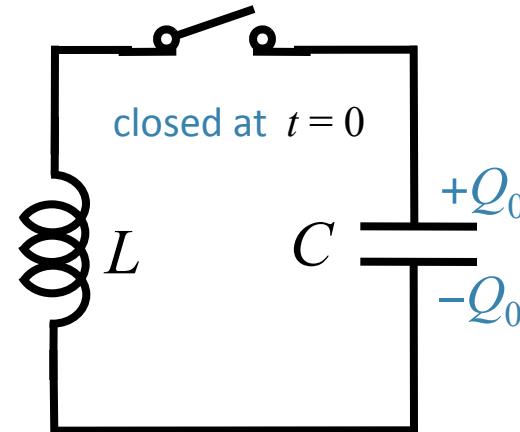When the energy stored in the capacitor reaches its maximum again for the **first time after $t = 0$** , how much charge is stored on the top plate of the capacitor?



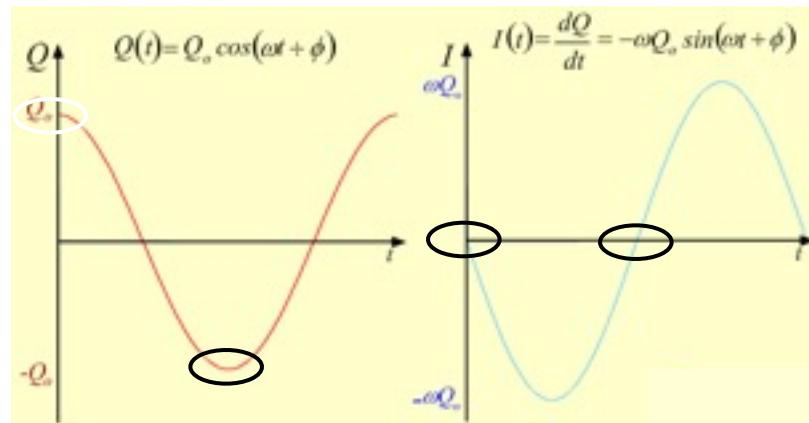
- A) $+Q_0$
- B) $+Q_0/2$
- C) 0
- D) $-Q_0/2$
- E) $-Q_0$



Q is maximum when current goes to zero


$$I = \frac{dQ}{dt}$$

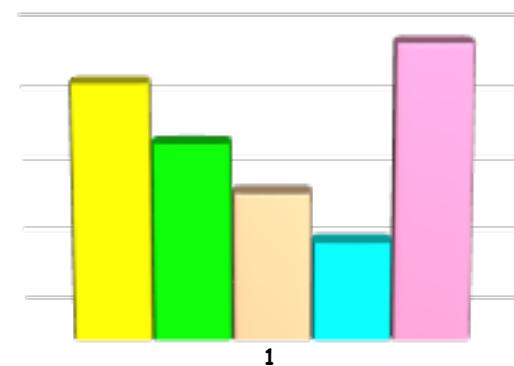Current goes to zero twice during one cycle



Add R : Damping

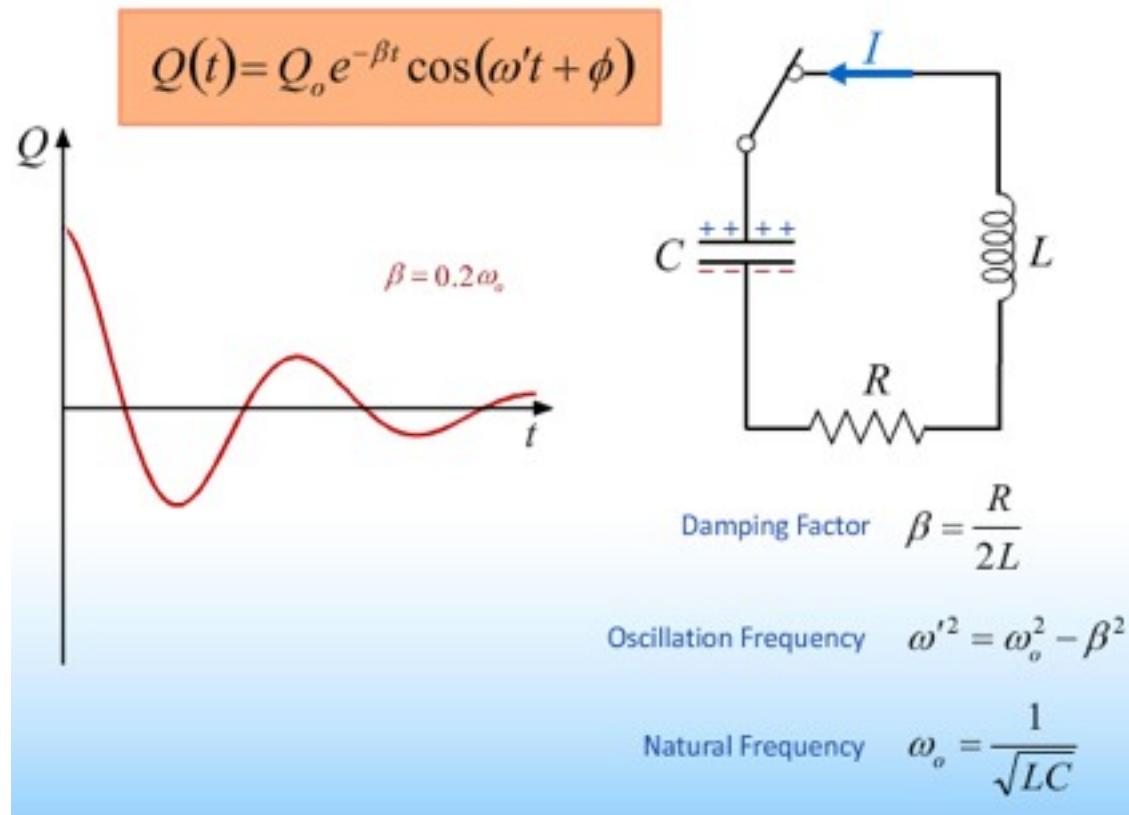Just like LC circuit but the oscillations get smaller because of R



Concept makes sense...

...but answer looks kind of complicated

Physics Truth #1:

Even though the answer sometimes looks complicated...

$$Q(t) = Q_o \cos(\omega t - \phi)$$


the physics under the hood is still very simple!

$$\frac{d^2Q}{dt^2} = -\omega^2 Q$$

The elements of a circuit are very simple:

$$V_L = L \frac{dI}{dt}$$

$$V = V_L + V_C + V_R$$

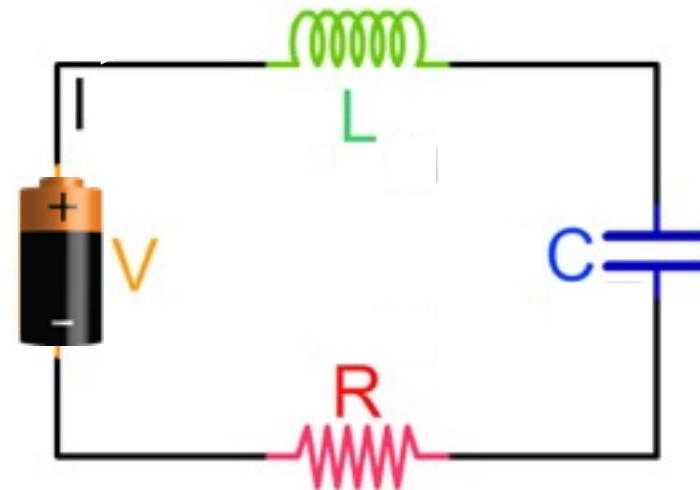


$$V_R = IR$$

$$V_C = \frac{Q}{C}$$

$$I = \frac{dQ}{dt}$$

This is all we need to know to solve for anything!

A Different Approach

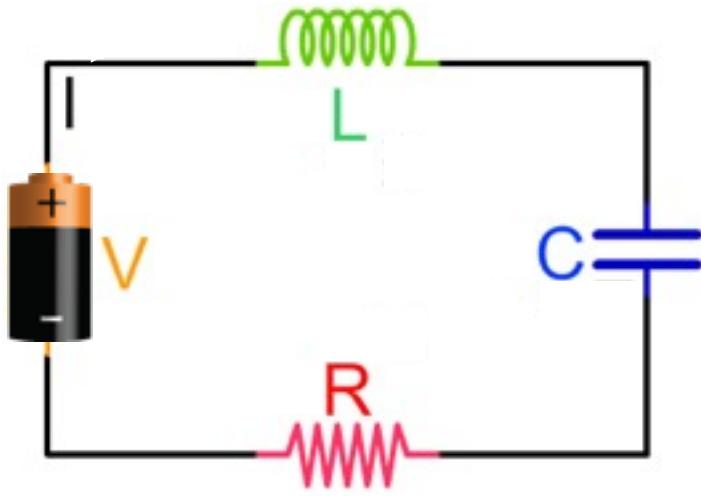


Start with some initial V, I, Q, V_L

Now take a tiny time step dt (1 ms)

```
for (var t=0; t<tStepSec; t+=dt) {  
    I += Vind_last*dt/L;  
    Qcap += I*dt;  
    Vcap = Qcap/C;  
    Vres = I*R1;  
    Vind_last = Vind;  
    Vind = Va - Vres - Vcap;  
}
```

$$\begin{aligned} dI &= \frac{V_L}{L} dt \\ dQ &= Idt \\ V_C &= \frac{Q}{C} \\ V_R &= IR \\ V_L &= V - V_R - V_C \end{aligned}$$


Repeat...

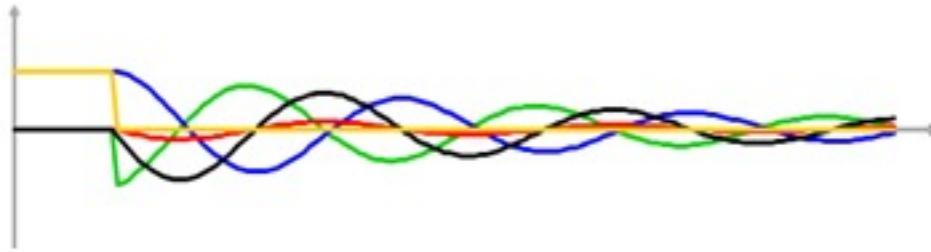

Calculation

The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

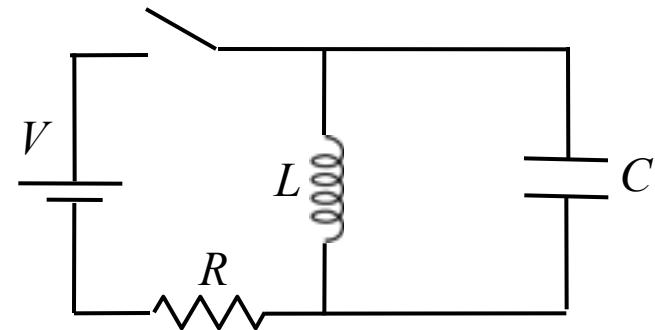What is Q_{MAX} , the maximum charge on the capacitor?



Conceptual Analysis

Once switch is opened, we have an LC circuit

Current will oscillate with natural frequency ω_0

Strategic Analysis


Determine initial current

Determine oscillation frequency ω_0

Find maximum charge on capacitor

Calculation

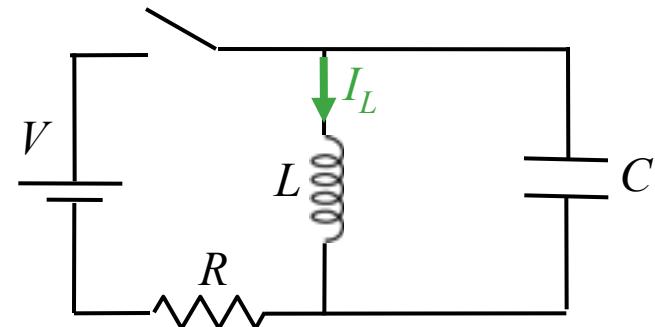The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is I_L , the current in the inductor, immediately **after** the switch is opened? Take positive direction as shown.

A) $I_L < 0$

B) $I_L = 0$

C) $I_L > 0$


Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened

before switch is opened:

all current goes through inductor in direction shown

Calculation

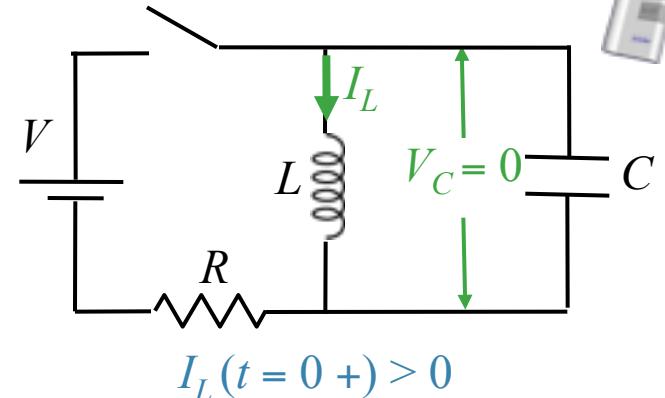The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



The energy stored in the capacitor immediately after the switch is opened is zero.

A) TRUE

B) FALSE

before switch is opened:

$$dI_L/dt \sim 0 \Rightarrow V_L = 0$$

BUT: $V_L = V_C$

since they are in parallel

$$\rightarrow V_C = 0$$

after switch is opened:

V_C cannot change abruptly

$$\rightarrow V_C = 0$$

$$\rightarrow U_C = \frac{1}{2} CV_C^2 = 0 !$$


IMPORTANT: NOTE DIFFERENT CONSTRAINTS AFTER SWITCH OPENED

CURRENT through INDUCTOR cannot change abruptly

VOLTAGE across CAPACITOR cannot change abruptly

Calculation

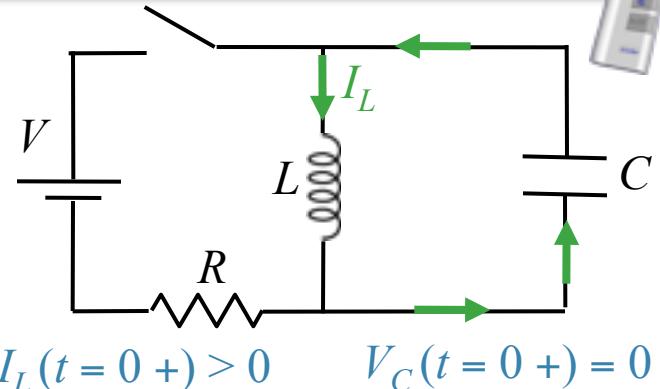The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is the direction of the current immediately after the switch is opened?

A) clockwise

B) counterclockwise

Current through inductor immediately **after** switch is opened
is the same as


the current through inductor immediately **before** switch is opened

Before switch is opened: Current moves down through ***L***

After switch is opened: Current continues to move down through ***L***

Calculation

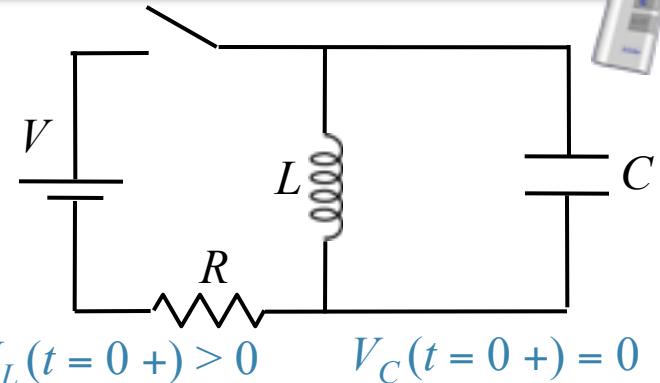The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is the magnitude of the current right after the switch is opened?

$$A) \quad I_o = V \sqrt{\frac{C}{L}}$$


$$B) \quad I_o = \frac{V}{R^2} \sqrt{\frac{L}{C}}$$

$$C) \quad I_o = \frac{V}{R}$$

$$D) \quad I_o = \frac{V}{2R}$$

Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened


Before switch is opened:

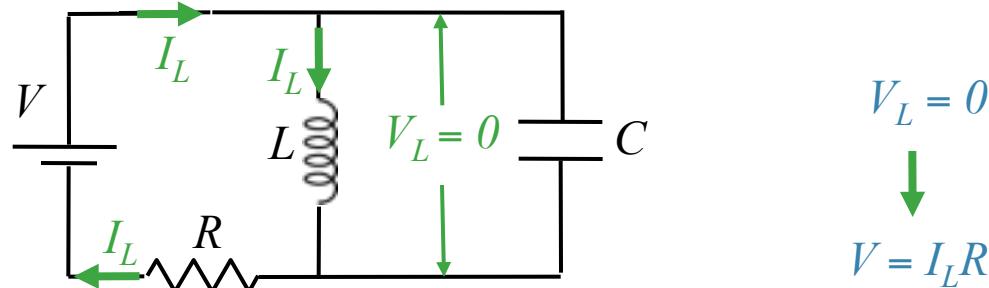

Calculation

The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

Hint: Energy is conserved

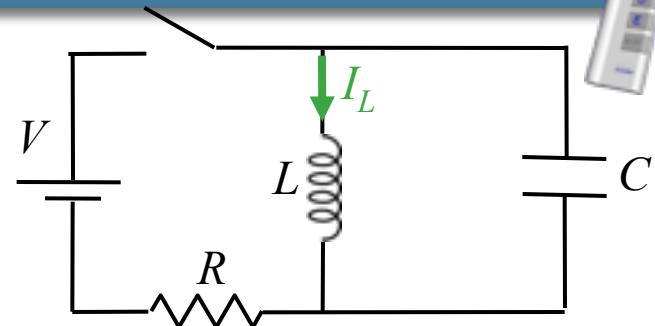

$$I_L(t = 0+) = V/R \quad V_C(t = 0+) = 0$$


What is Q_{max} , the maximum charge on the capacitor during the oscillations?

A) $Q_{max} = \frac{V}{R} \sqrt{LC}$

B) $Q_{max} = \frac{1}{2} CV$


C) $Q_{max} = CV$

D) $Q_{max} = \frac{V}{R \sqrt{LC}}$

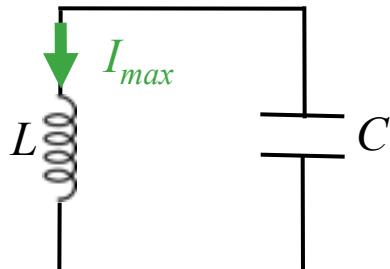

When I is **max**
(and Q is **0**)

$$U = \frac{1}{2} LI^2$$

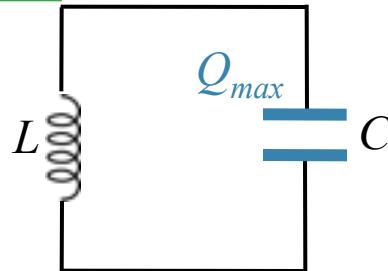

When Q is **max**
(and I is **0**)

$$U = \frac{1}{2} \frac{Q_{max}^2}{C}$$



$$\frac{1}{2} LI^2 = \frac{1}{2} \frac{Q_{max}^2}{C}$$

$$Q_{max} = I_{max} \sqrt{LC} = \frac{V}{R} \sqrt{LC}$$


Follow-Up

The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

Is it possible for the maximum voltage on the capacitor to be greater than V ?

A) YES

B) NO

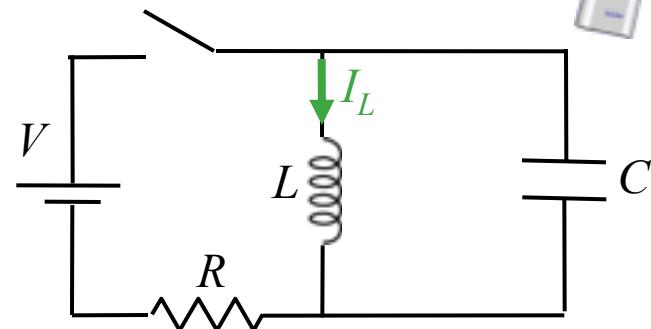

$$I_{max} = V/R$$

$$Q_{max} = \frac{V}{R} \sqrt{LC}$$

$$Q_{max} = \frac{V}{R} \sqrt{LC} \rightarrow V_{max} = \frac{V}{R} \sqrt{\frac{L}{C}} \rightarrow V_{max} \text{ can be greater than } V \text{ IF: } \sqrt{\frac{L}{C}} > R$$

We can rewrite this condition in terms of the resonant frequency:

$$\omega_0 L > R \quad \text{OR} \quad \frac{1}{\omega_0 C} > R$$

We will see these forms again when we study *AC* circuits!