

Electricity & Magnetism


Lecture 20

Today's Concept:


AC Circuits

Maximum currents & voltages


Phasors: A Simple Tool

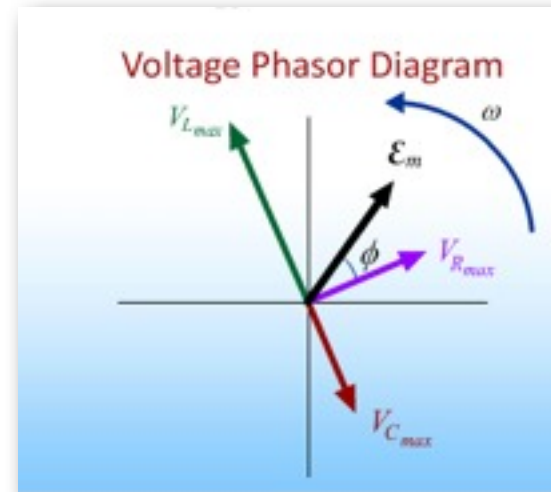


Resistors

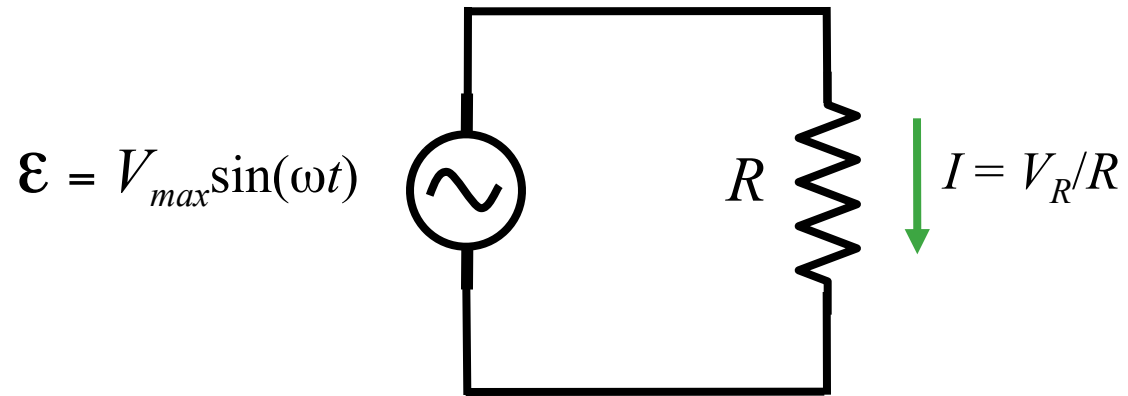



Resistors

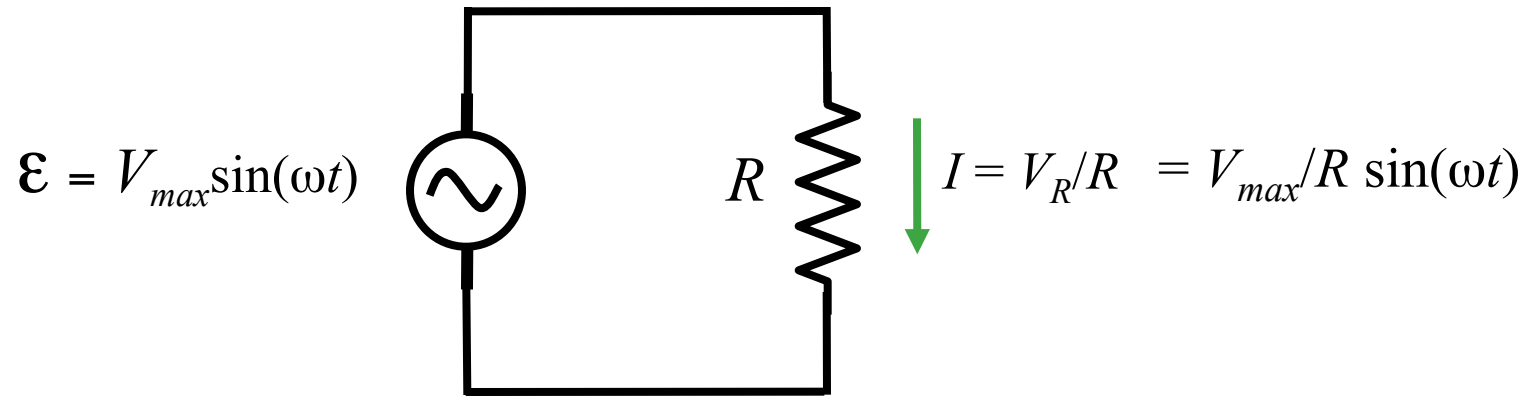

Resistors

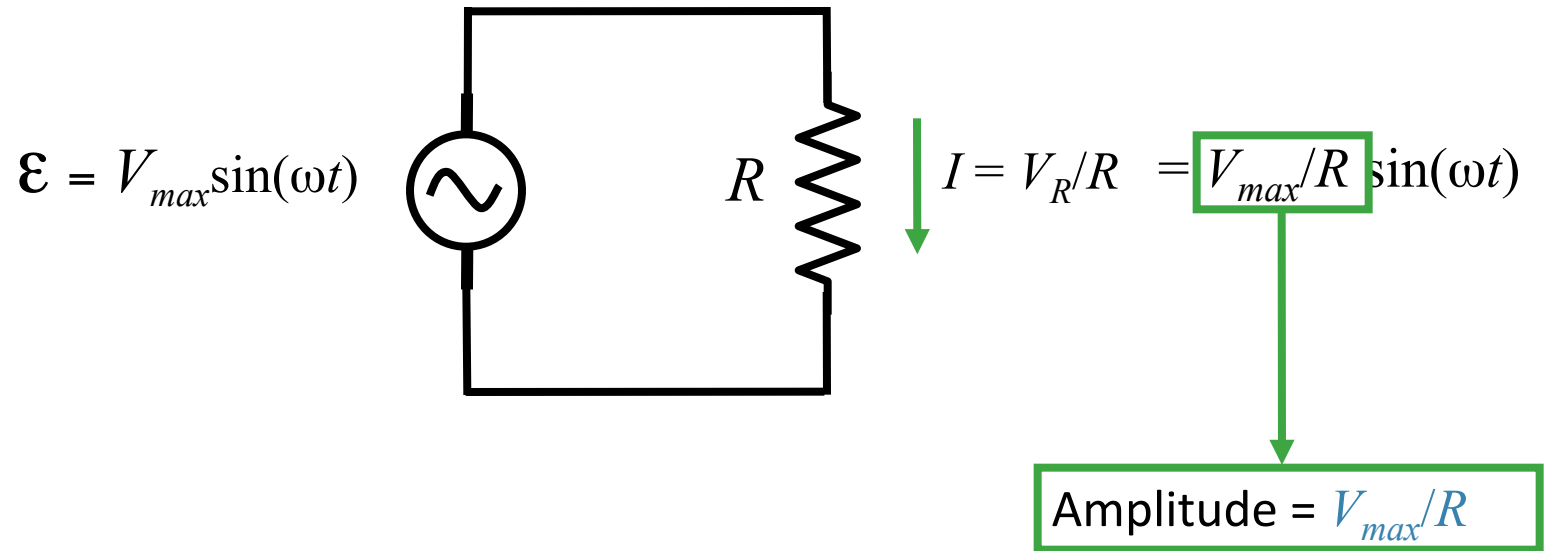


Resistors

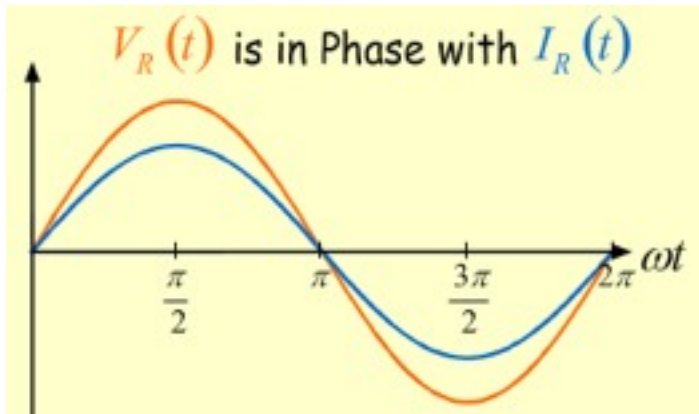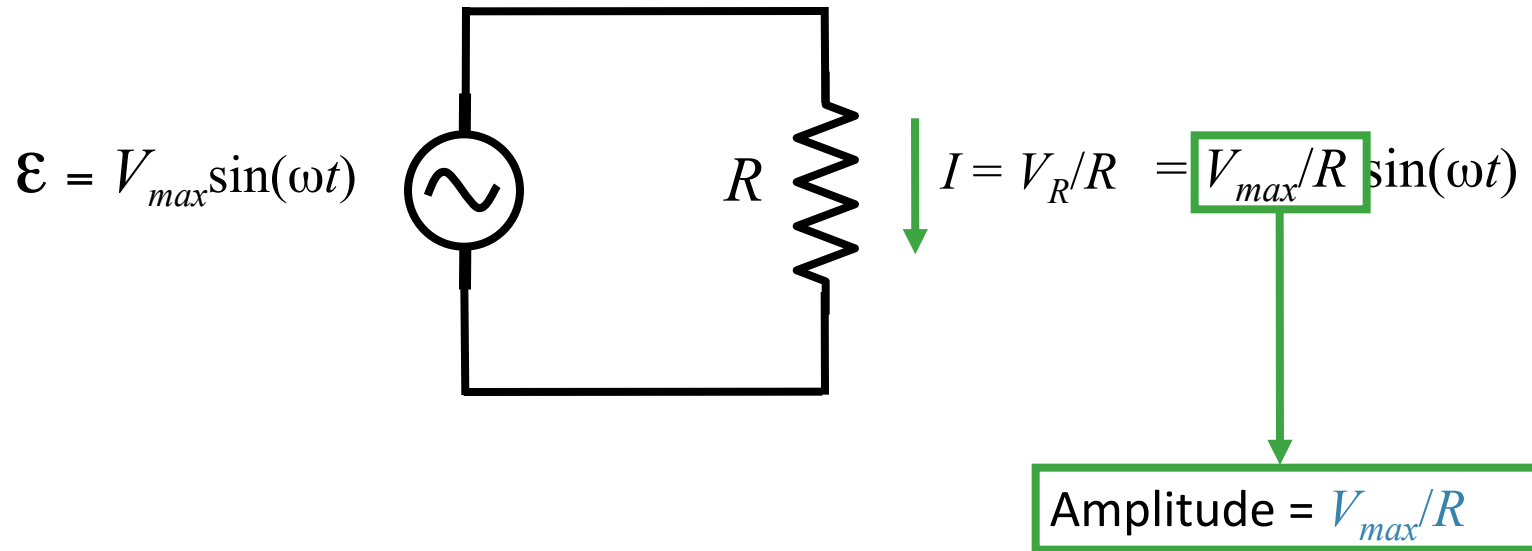

Capacitors

$$\mathcal{E} = V_{max} \sin(\omega t)$$

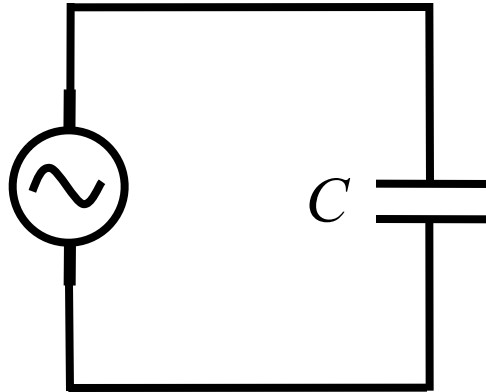

$$Q = CV = CV_{max} \sin(\omega t)$$


$$I = dQ/dt$$

$$I = V_{max} \omega C \cos(\omega t)$$



Capacitors
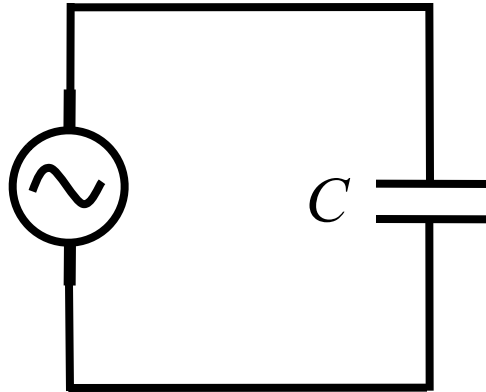
$$\mathcal{E} = V_{\max} \sin(\omega t)$$



$$Q = CV = CV_{\max} \sin(\omega t)$$


$$I = dQ/dt$$

$$I = V_{\max} \omega C \cos(\omega t)$$

$$\text{Amplitude} = V_{\max} / X_C$$

Capacitors
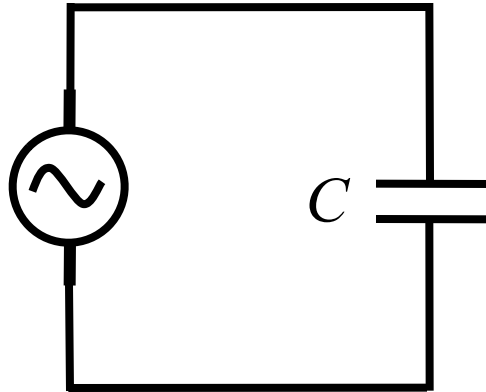
$$\mathcal{E} = V_{\max} \sin(\omega t)$$



$$Q = CV = CV_{\max} \sin(\omega t)$$

$$I = dQ/dt$$


$$I = V_{\max} \omega C \cos(\omega t)$$

$$\text{Amplitude} = V_{\max} / X_C$$

where $X_C = 1/\omega C$
is like the “resistance”
of the capacitor
 X_C depends on ω

Capacitors
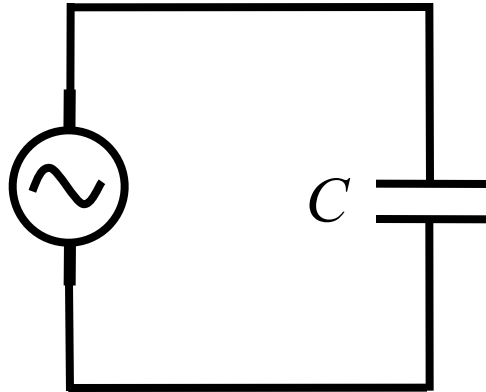
$$\mathcal{E} = V_{\max} \sin(\omega t)$$




$$Q = CV = CV_{\max} \sin(\omega t)$$

$$I = dQ/dt$$


$$I = V_{\max} \omega C \cos(\omega t)$$

$$\text{Amplitude} = V_{\max} / X_C$$

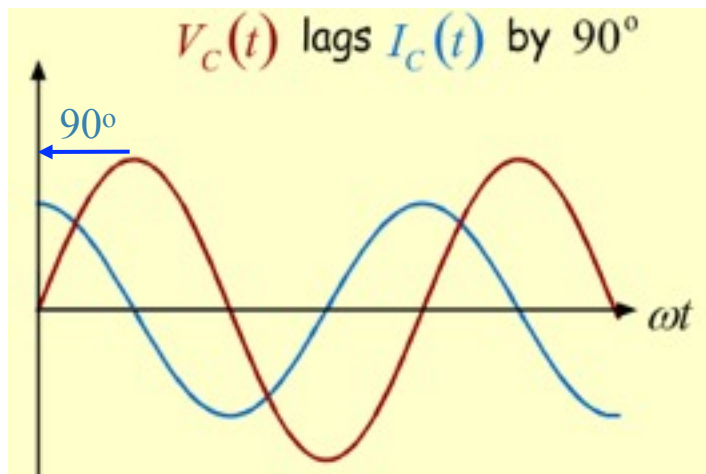where $X_C = 1/\omega C$
is like the “resistance”
of the capacitor
 X_C depends on ω




Inductors

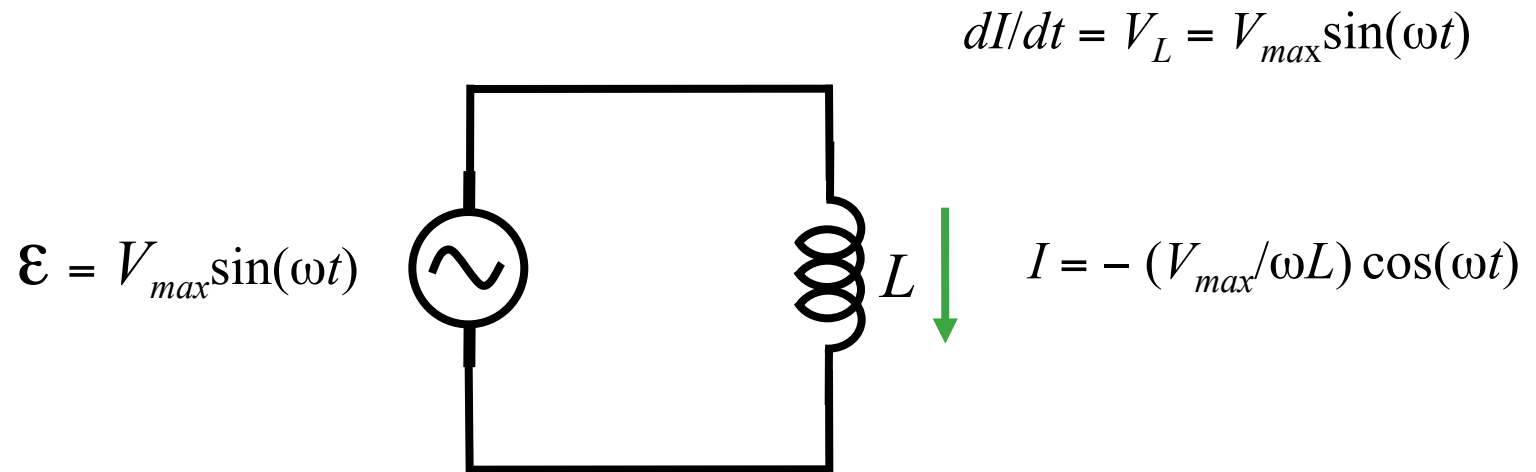

Inductors
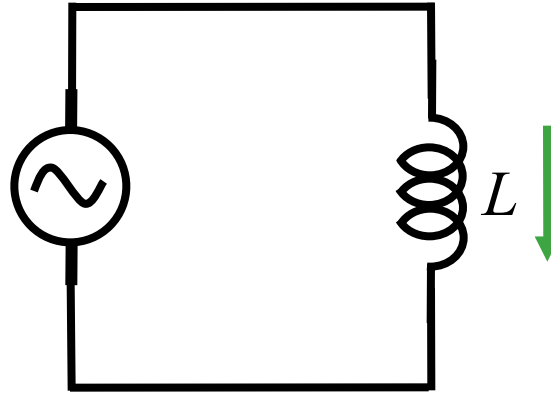
$$\mathcal{E} = V_{\max} \sin(\omega t)$$




$$dI/dt = V_L = V_{\max} \sin(\omega t)$$

$$I = -\boxed{(V_{\max}/\omega L)} \cos(\omega t)$$

Amplitude = $\boxed{V_{\max}/X_L}$

Inductors
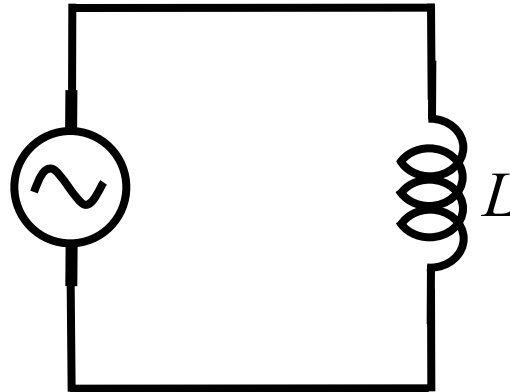
$$\mathcal{E} = V_{\max} \sin(\omega t)$$



$$dI/dt = V_L = V_{\max} \sin(\omega t)$$

$$I = -\boxed{(V_{\max}/\omega L)} \cos(\omega t)$$

Amplitude = $\boxed{V_{\max}/X_L}$


where $X_L = \omega L$

is like the “resistance”
of the inductor

X_L depends on ω

Inductors

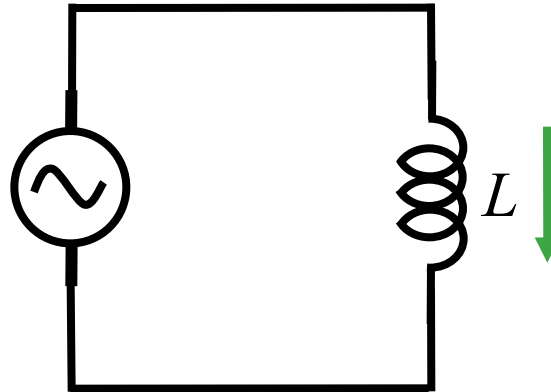
$$\mathcal{E} = V_{\max} \sin(\omega t)$$



$$dI/dt = V_L = V_{\max} \sin(\omega t)$$

$$I = -\left(V_{\max}/\omega L\right) \cos(\omega t)$$

$$\text{Amplitude} = V_{\max}/X_L$$

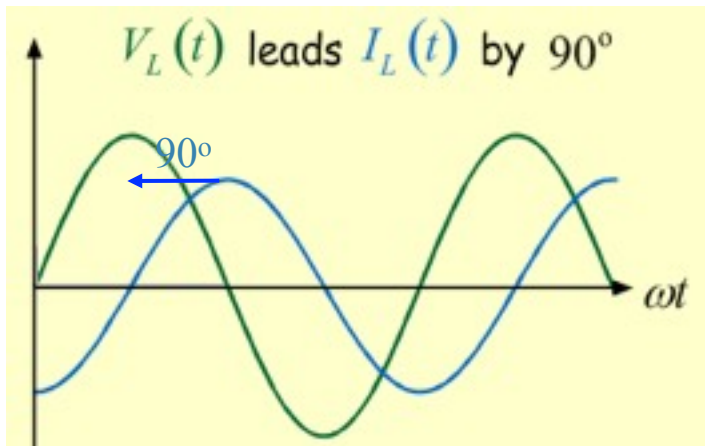


where $X_L = \omega L$
is like the “resistance”
of the inductor
 X_L depends on ω

RL Clicker Question



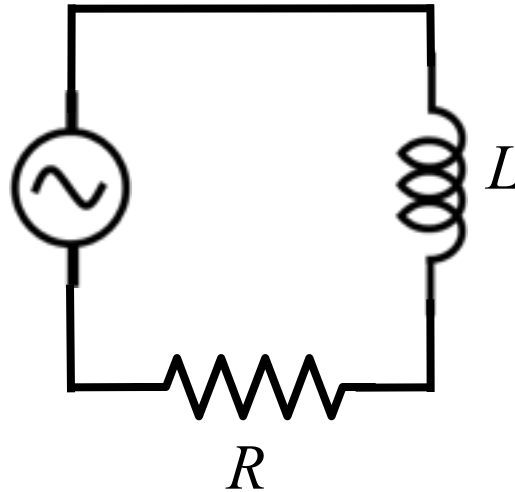An RL circuit is driven by an AC generator as shown in the figure.




For what driving frequency ω of the generator will the current through the resistor be largest

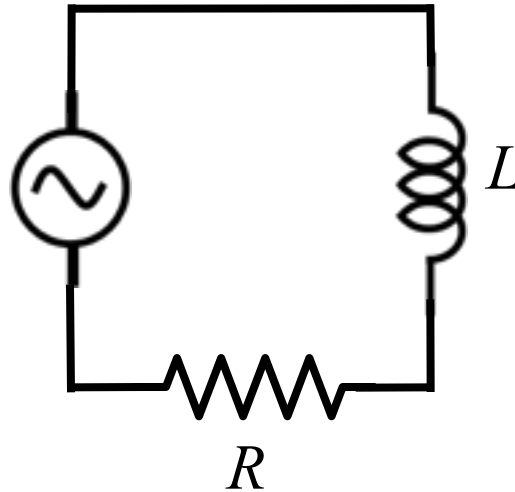- A) ω large
- B) Current through R doesn't depend on ω
- C) ω small

RL Clicker Question



An RL circuit is driven by an *AC* generator as shown in the figure.



$$X_L = \omega L$$


For what driving frequency ω of the generator will the current through the resistor be largest

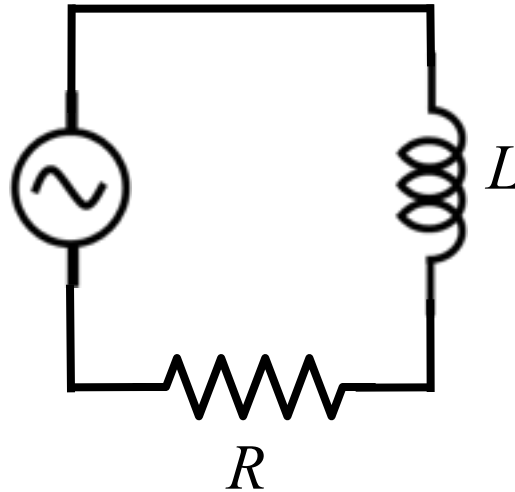- A) ω large
- B) Current through R doesn't depend on ω
- C) ω small

RL Clicker Question



An RL circuit is driven by an *AC* generator as shown in the figure.



$$X_L = \omega L$$

As $\omega \rightarrow 0$, so does X_L


For what driving frequency ω of the generator will the current through the resistor be largest

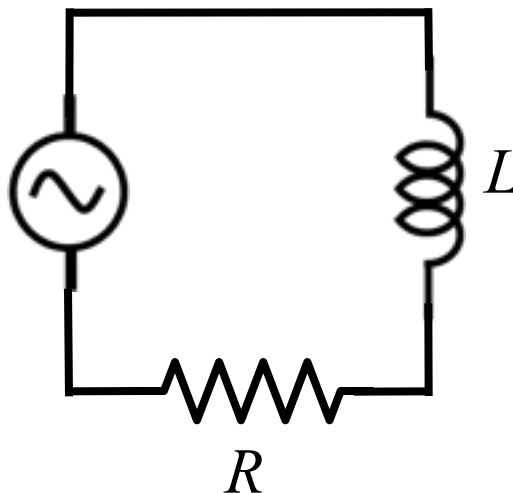- A) ω large
- B) Current through R doesn't depend on ω
- C) ω small

RL Clicker Question



An RL circuit is driven by an *AC* generator as shown in the figure.



$$X_L = \omega L$$

As $\omega \rightarrow 0$, so does X_L



As $\omega \rightarrow 0$,
resistance of circuit $\rightarrow R$
current gets bigger


For what driving frequency ω of the generator will the current through the resistor be largest

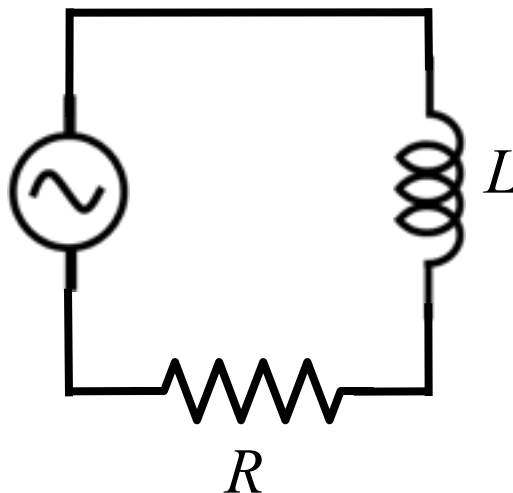- A) ω large
- B) Current through R doesn't depend on ω
- C) ω small

RL Clicker Question



An RL circuit is driven by an *AC* generator as shown in the figure.



$$X_L = \omega L$$

As $\omega \rightarrow 0$, so does X_L



As $\omega \rightarrow 0$,
resistance of circuit $\rightarrow R$
current gets bigger


For what driving frequency ω of the generator will the current through the resistor be largest

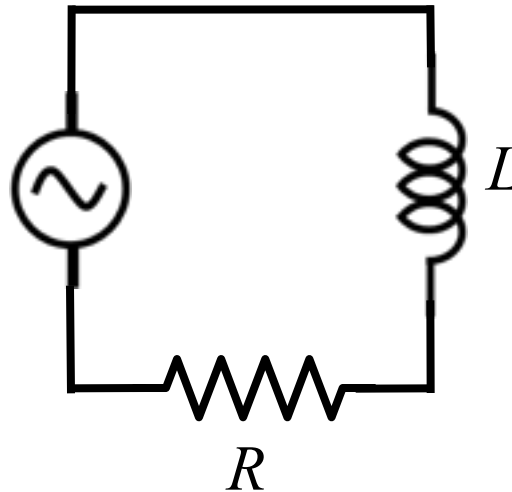- A) ω large
- B) Current through R doesn't depend on ω
- C) ω small

RL Clicker Question



An RL circuit is driven by an *AC* generator as shown in the figure.



$$X_L = \omega L$$

As $\omega \rightarrow 0$, so does X_L



As $\omega \rightarrow 0$,
impedance resistance of circuit $\rightarrow R$
current gets bigger


For what driving frequency ω of the generator will the current through the resistor be largest

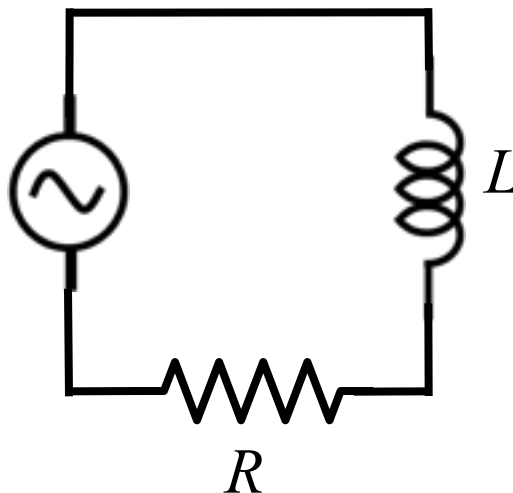- A) ω large
- B) Current through R doesn't depend on ω
- C) ω small

RL Clicker Question



An RL circuit is driven by an *AC* generator as shown in the figure.



$$X_L = \omega L$$

As $\omega \rightarrow 0$, so does X_L




As $\omega \rightarrow 0$,
impedance resistance of circuit $\rightarrow R$
current gets bigger

For what driving frequency ω of the generator will the current through the resistor be largest

- A) ω large
- B) Current through R doesn't depend on ω
- C) ω small


Summary

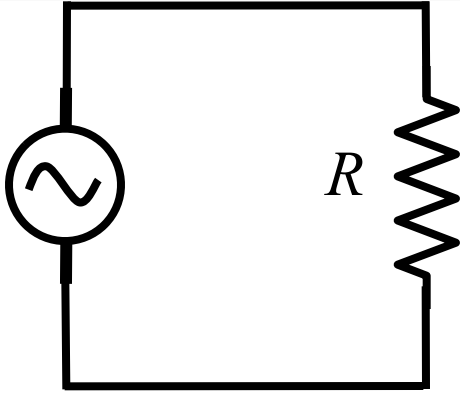

$$I_{max} = V_{max}/R$$


V_R in phase with I

Summary

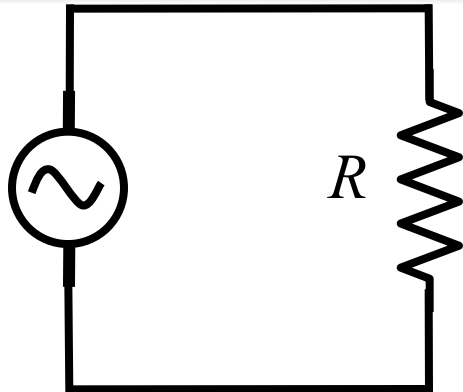

$$I_{max} = V_{max}/R$$

V_R in phase with I

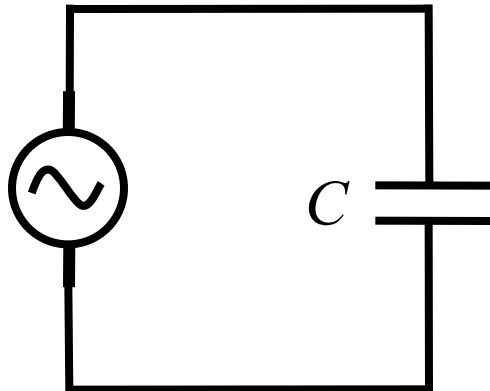


$$I_{max} = V_{max}/X_C$$

$$X_C = 1/\omega C$$


V_C 90° behind I

Summary

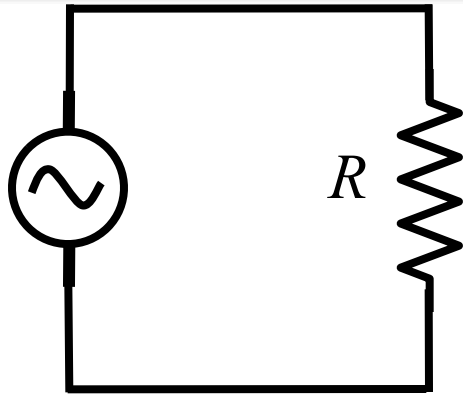

$$I_{max} = V_{max}/R$$


V_R in phase with I

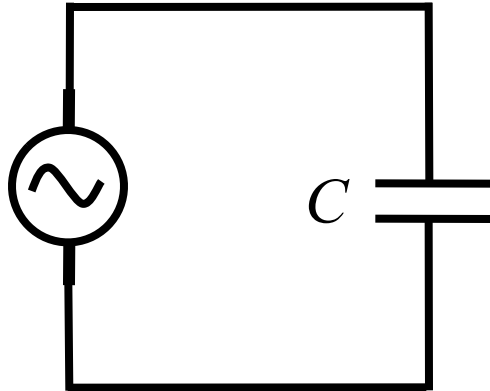

$$I_{max} = V_{max}/X_C$$

$$X_C = 1/\omega C$$

V_C 90° behind I

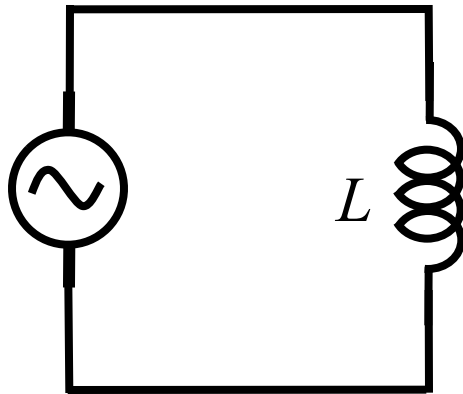


$$I_{max} = V_{max}/X_L$$

$$X_L = \omega L$$


V_L 90° ahead of I

Summary

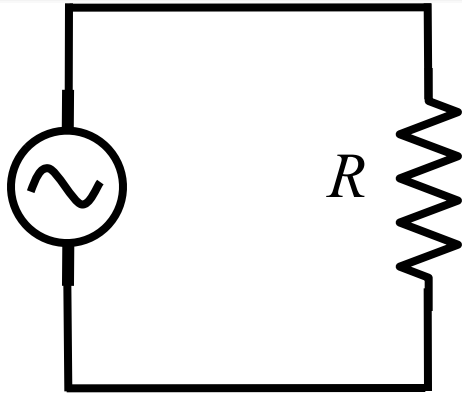

$$I_{max} = V_{max}/R$$

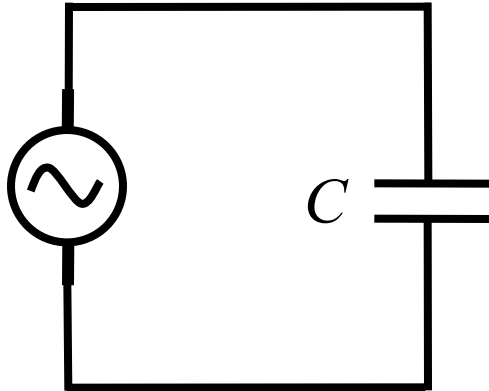
V_R in phase with I
Because resistors are simple



$$I_{max} = V_{max}/X_C$$

$$X_C = 1/\omega C$$

V_C 90° behind I

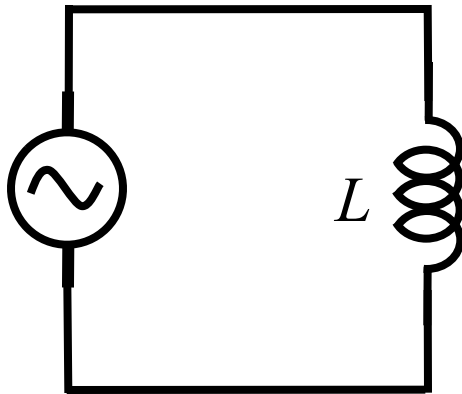


$$I_{max} = V_{max}/X_L$$

$$X_L = \omega L$$


V_L 90° ahead of I

Summary

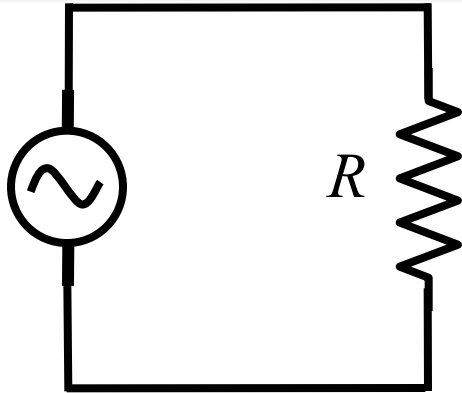

$$I_{max} = V_{max}/R$$

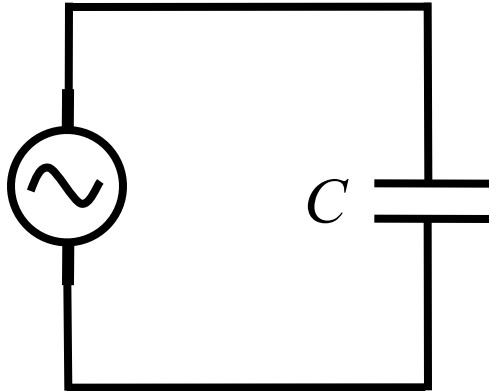
V_R in phase with I
Because resistors are simple



$$I_{max} = V_{max}/X_C$$

$$X_C = 1/\omega C$$

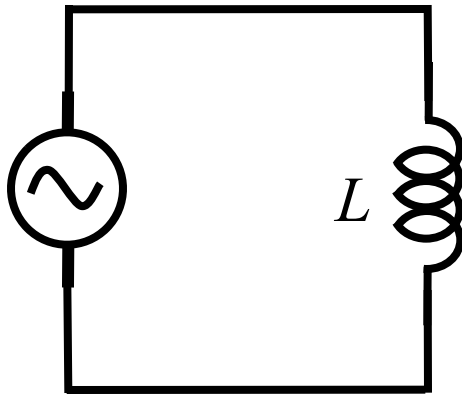V_C 90° behind I
Current comes first since it
charges capacitor




$$I_{max} = V_{max}/X_L$$

$$X_L = \omega L$$


V_L 90° ahead of I

Summary

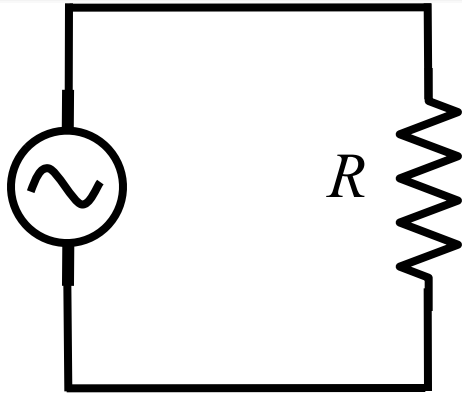

$$I_{max} = V_{max}/R$$

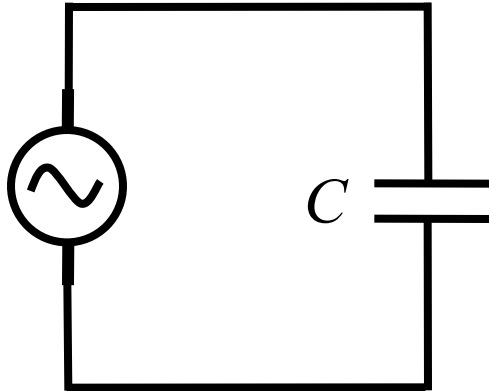
V_R in phase with I
Because resistors are simple



$$I_{max} = V_{max}/X_C$$

$$X_C = 1/\omega C$$

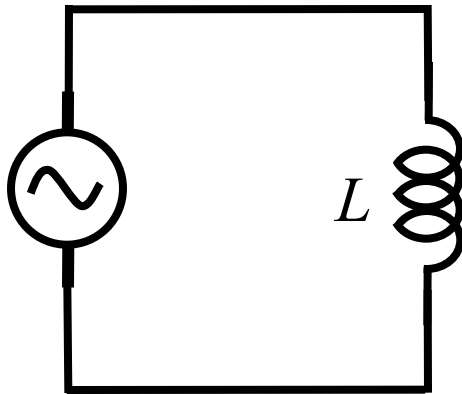V_C 90° behind I
Current comes first since it
charges capacitor




$$I_{max} = V_{max}/X_L$$

$$X_L = \omega L$$


V_L 90° ahead of I
Opposite of capacitor

Summary

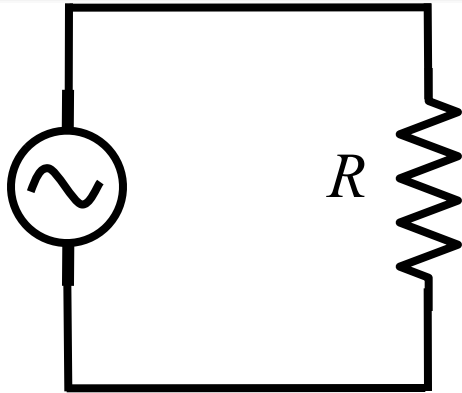

$$I_{max} = V_{max}/R$$

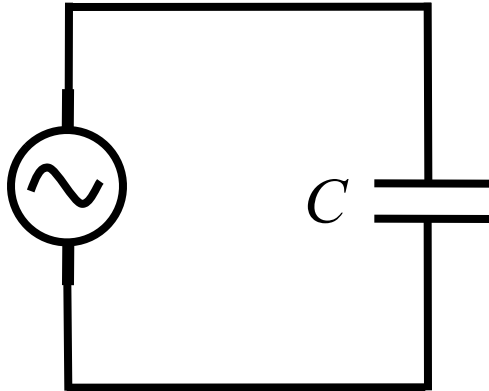
V_R in phase with I
Because resistors are simple



$$I_{max} = V_{max}/X_C$$

$$X_C = 1/\omega C$$

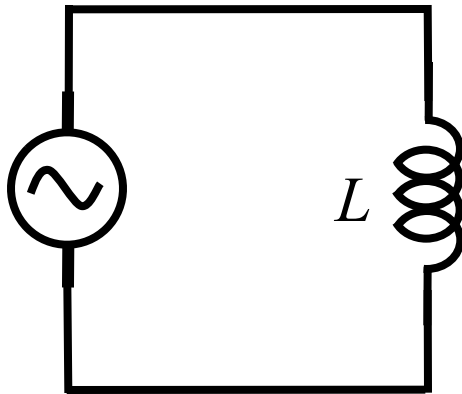V_C 90° behind I
Current comes first since it
charges capacitor
Like a wire at high ω




$$I_{max} = V_{max}/X_L$$

$$X_L = \omega L$$


V_L 90° ahead of I
Opposite of capacitor

Summary

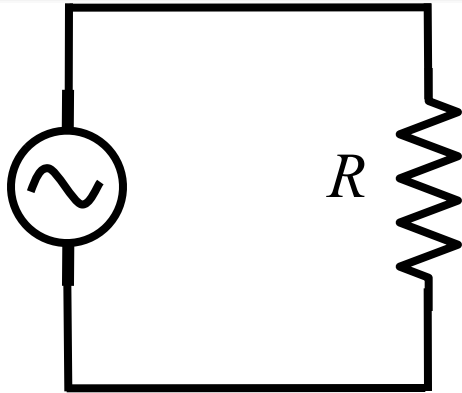

$$I_{max} = V_{max}/R$$

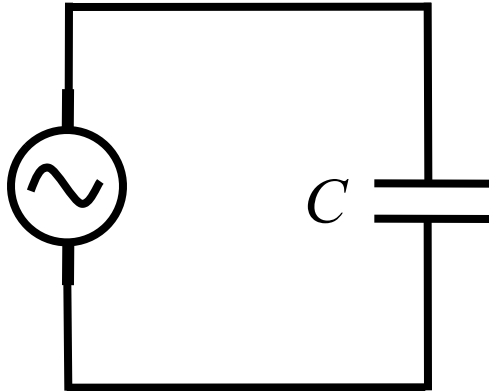
V_R in phase with I
Because resistors are simple



$$I_{max} = V_{max}/X_C$$

$$X_C = 1/\omega C$$

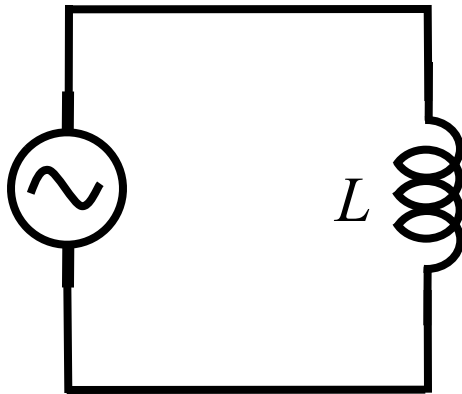V_C 90° behind I
Current comes first since it
charges capacitor
Like a wire at high ω



$$I_{max} = V_{max}/X_L$$


$$X_L = \omega L$$

V_L 90° ahead of I
Opposite of capacitor
Like a wire at low ω

Makes sense to write everything in terms of I since this is the same everywhere in a one-loop circuit:

$$V_{max} = I_{max} X_C$$

V 90° behind I

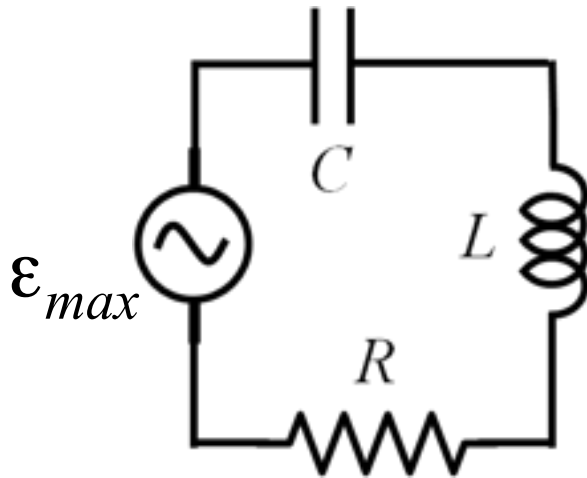

$$V_{max} = I_{max} X_L$$

V 90° ahead of I


$$V_{max} = I_{max} R$$

V in phase with I

Makes sense to write everything in terms of I since this is the same everywhere in a one-loop circuit:

$$V_{max} = I_{max} X_C$$

V 90° behind I

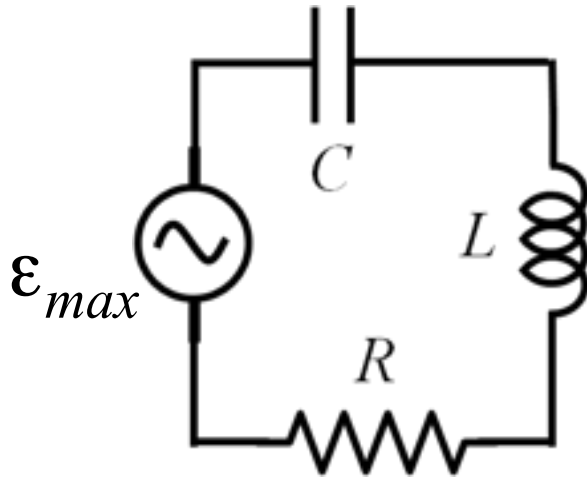


$$V_{max} = I_{max} X_L$$

V 90° ahead of I

$$V_{max} = I_{max} R$$

V in phase with I


Phasors make this simple to see

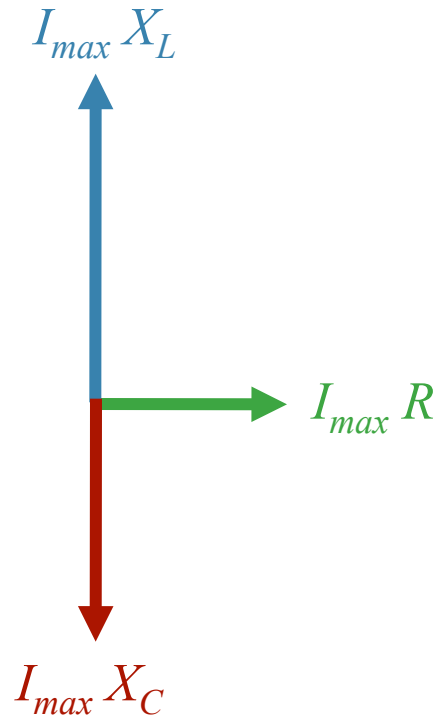

Makes sense to write everything in terms of I since this is the same everywhere in a one-loop circuit:

$$V_{max} = I_{max} X_C$$

V 90° behind I

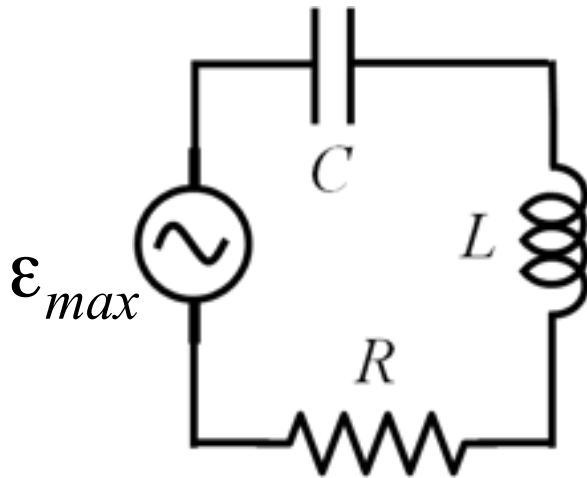


$$V_{max} = I_{max} X_L$$

V 90° ahead of I

$$V_{max} = I_{max} R$$

V in phase with I

Phasors make this simple to see

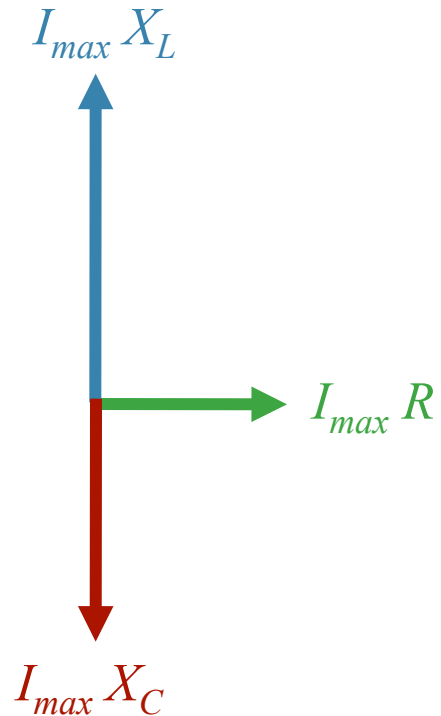


Always looks the same.
Only the lengths will change

Makes sense to write everything in terms of I since this is the same everywhere in a one-loop circuit:

$$V_{max} = I_{max} X_C$$

V 90° behind I

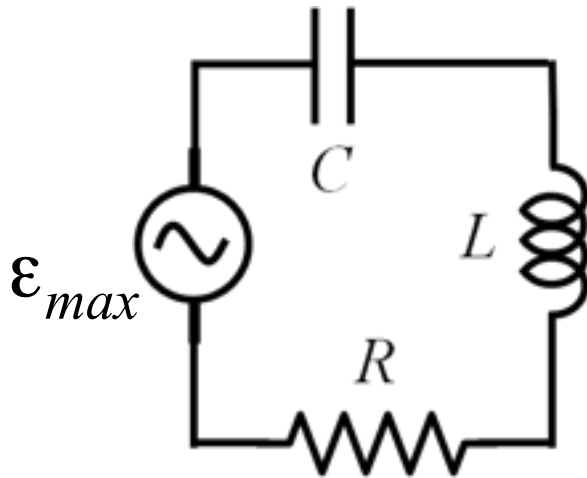

$$V_{max} = I_{max} X_L$$


V 90° ahead of I

$$V_{max} = I_{max} R$$

V in phase with I

“Do you have any fancy-schmancy simulations for to show me?”



Phasors make this simple to see

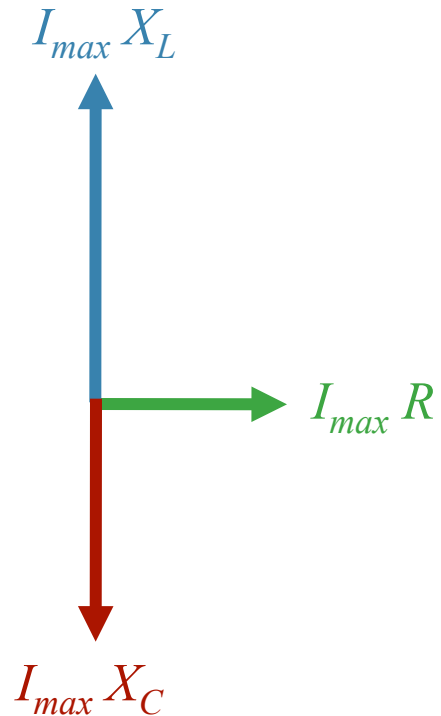

Always looks the same.
Only the lengths will change




The Voltages still Add Up

But now we are adding vectors:

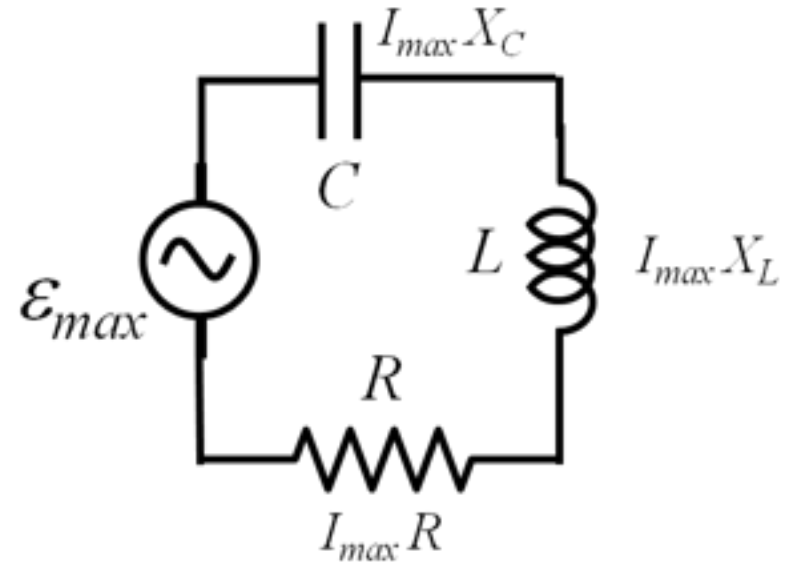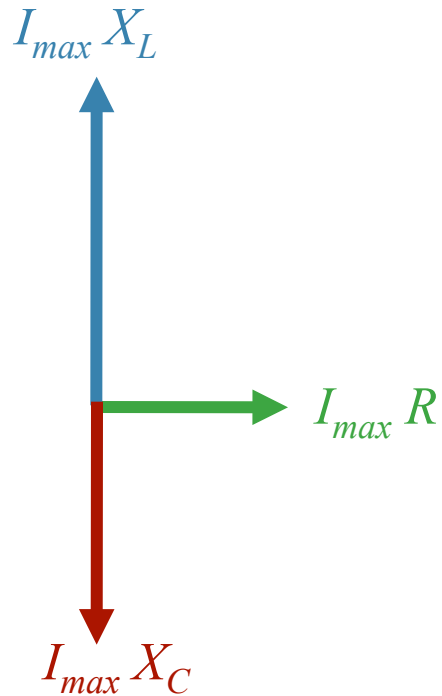




The Voltages still Add Up

But now we are adding vectors:

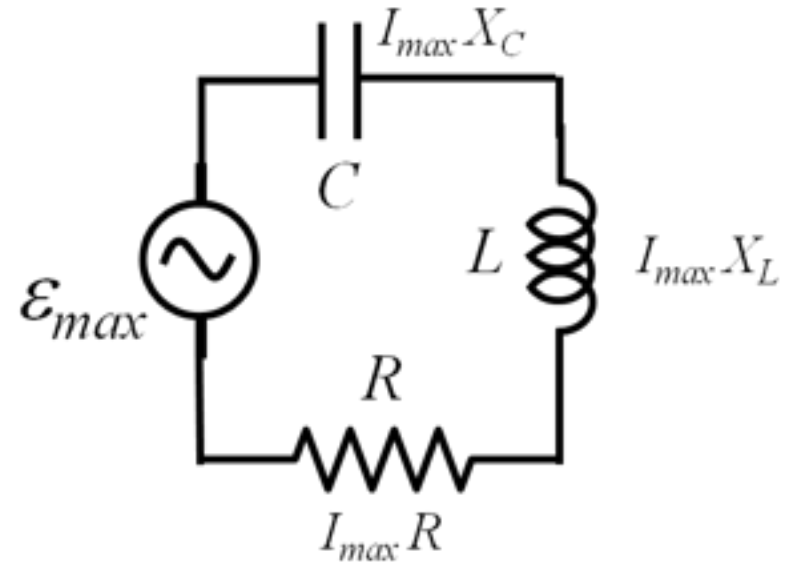
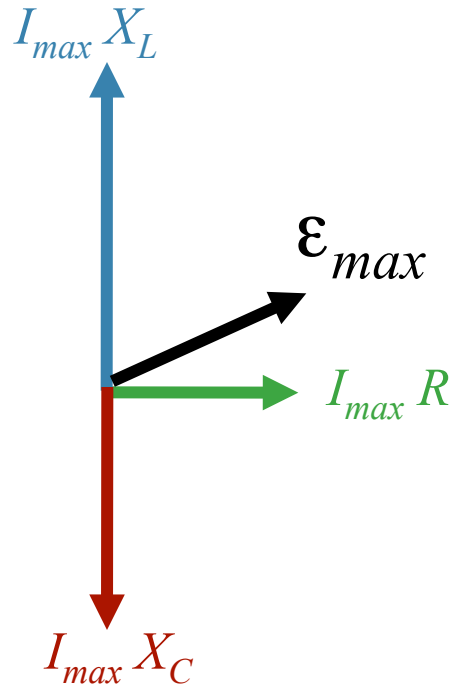
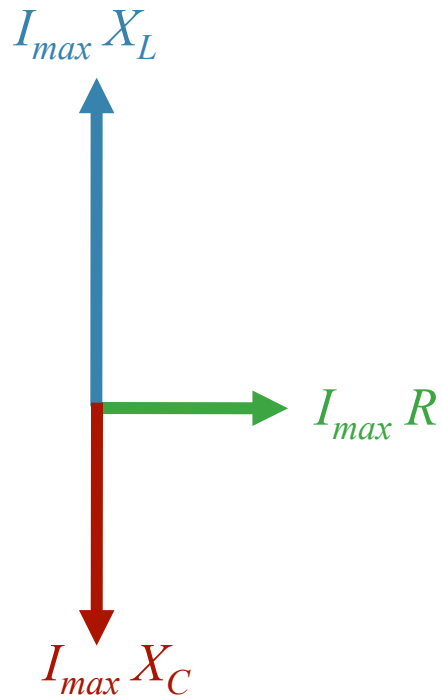


The Voltages still Add Up




But now we are adding vectors:

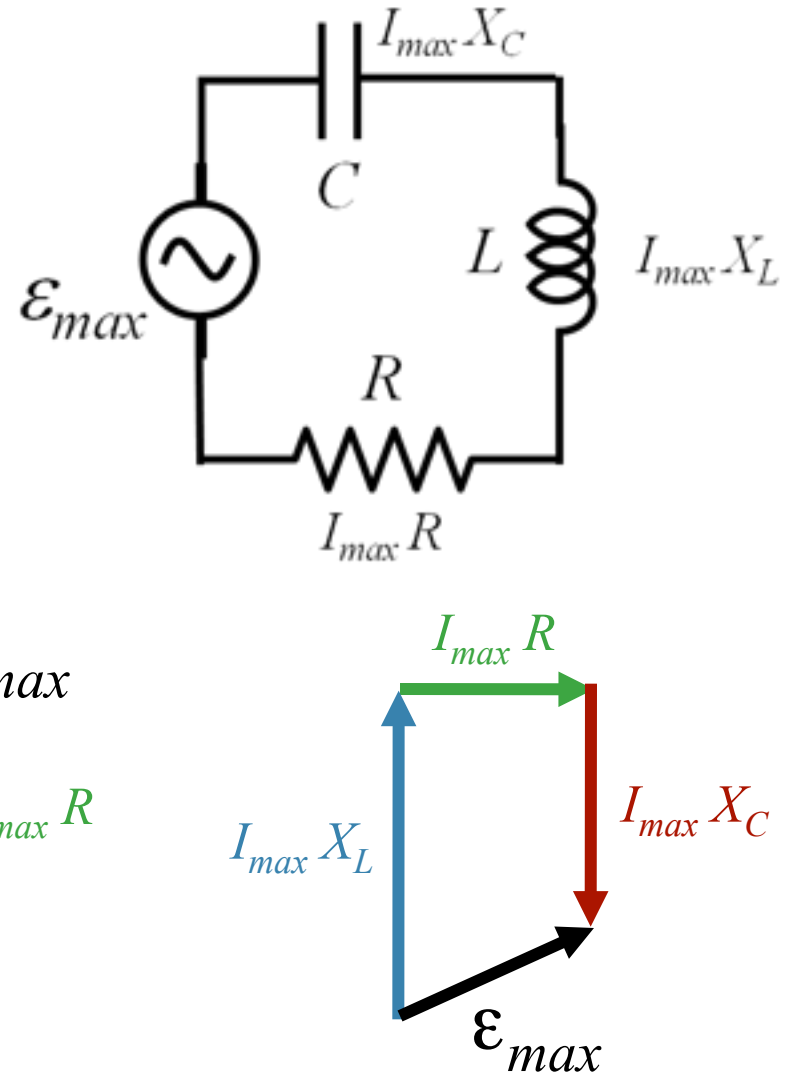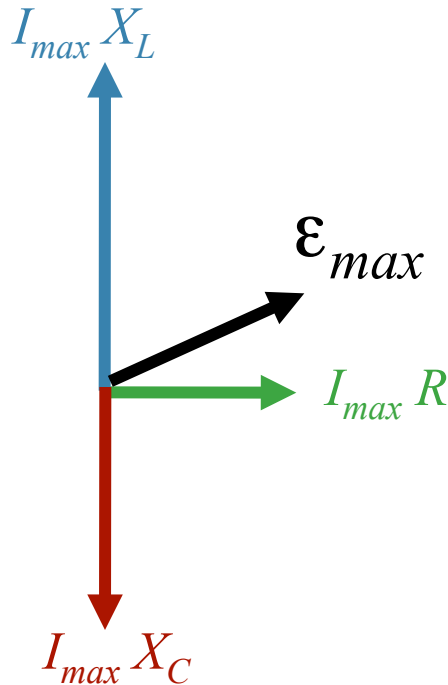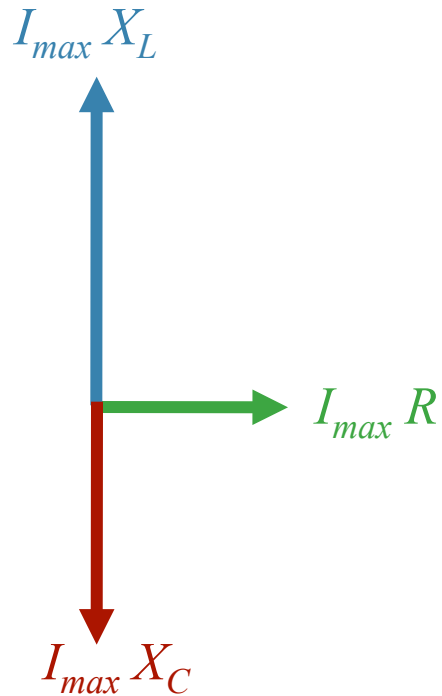




Make this Simpler

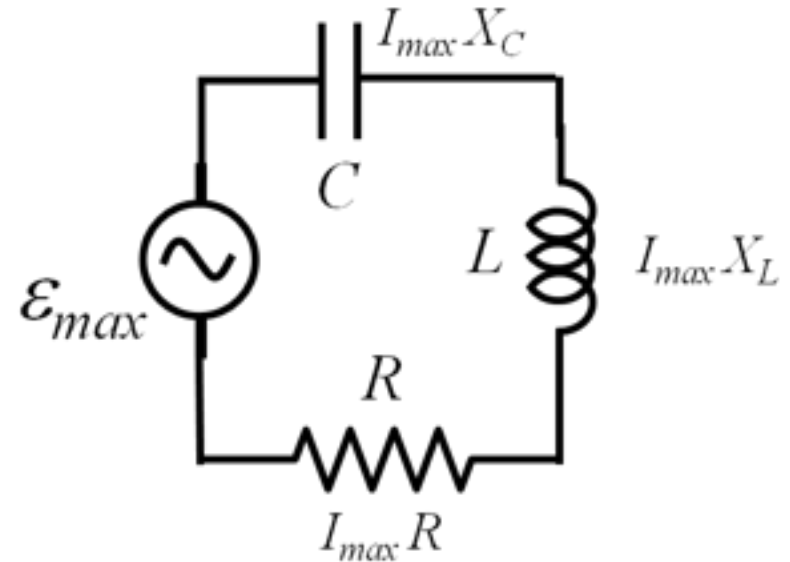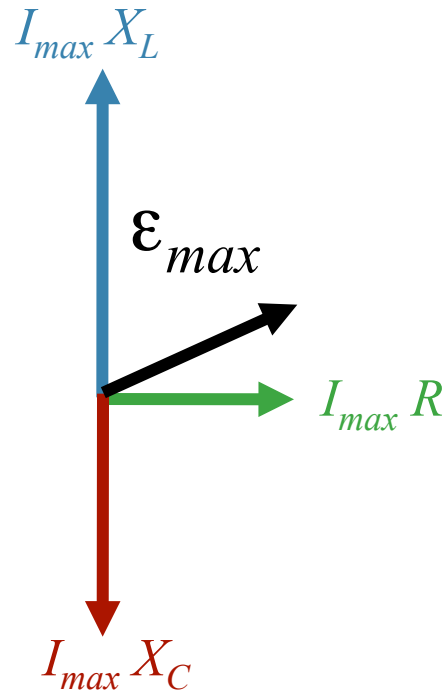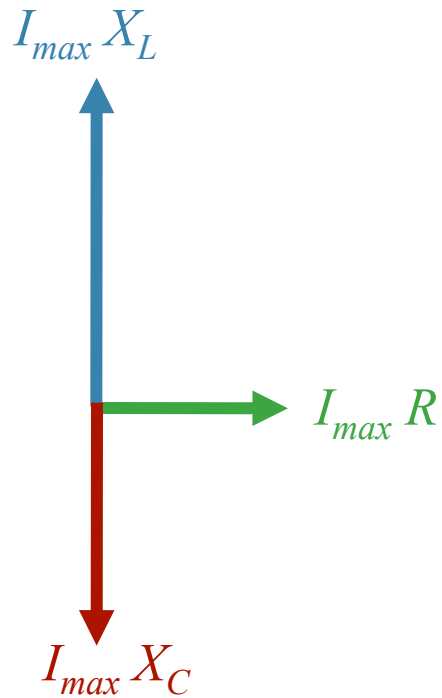


Make this Simpler

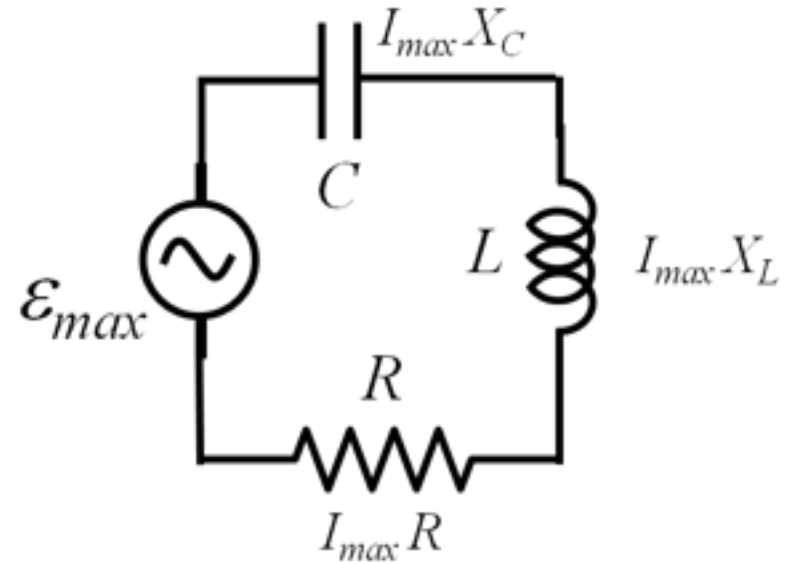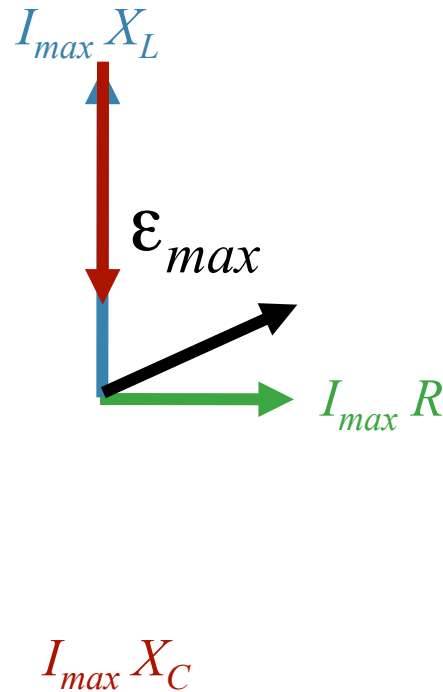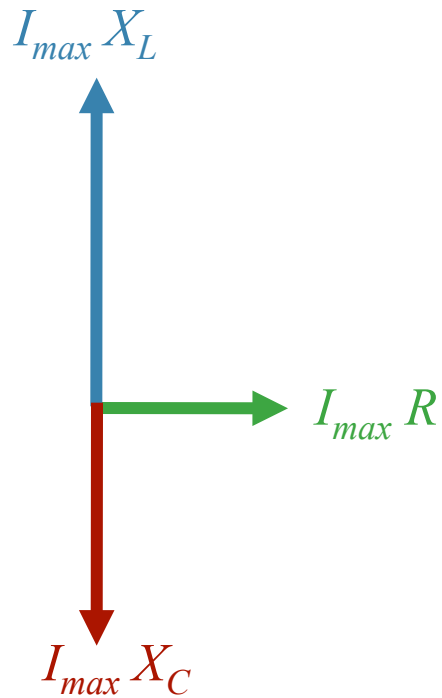


Make this Simpler

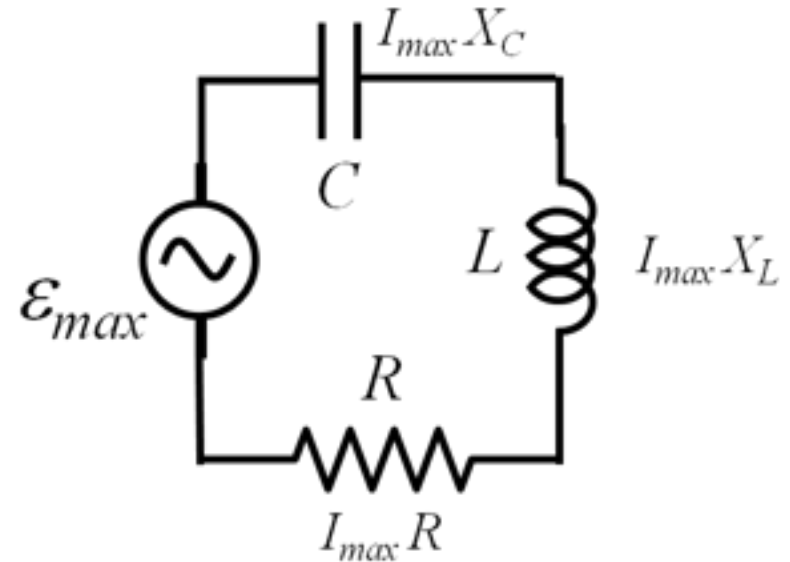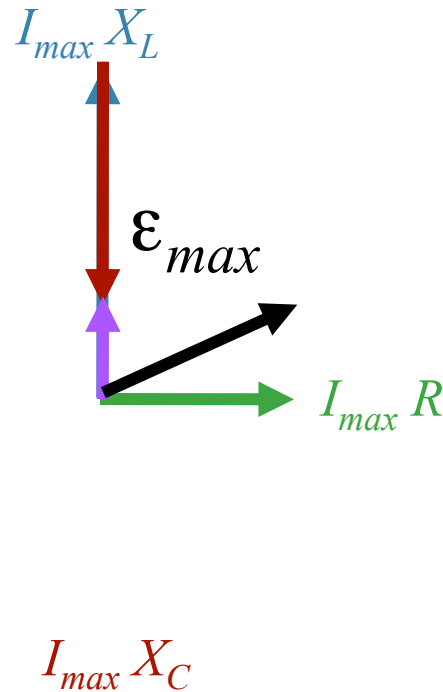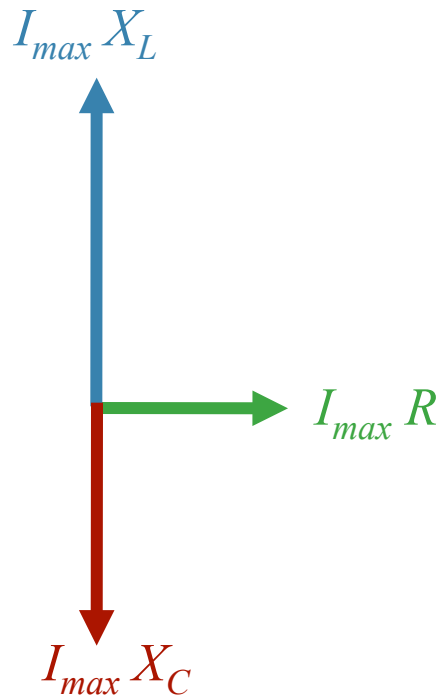


Make this Simpler

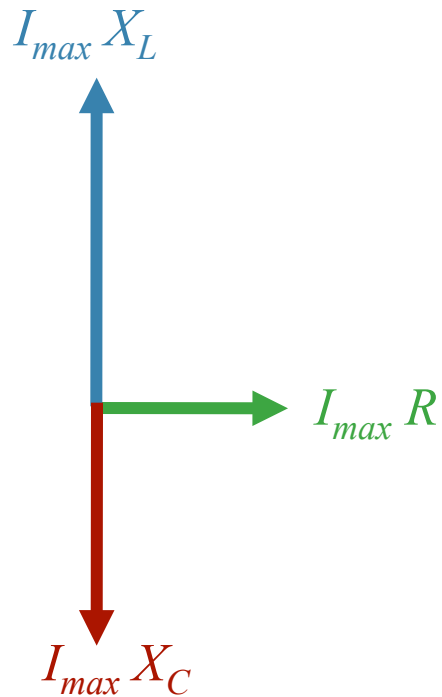

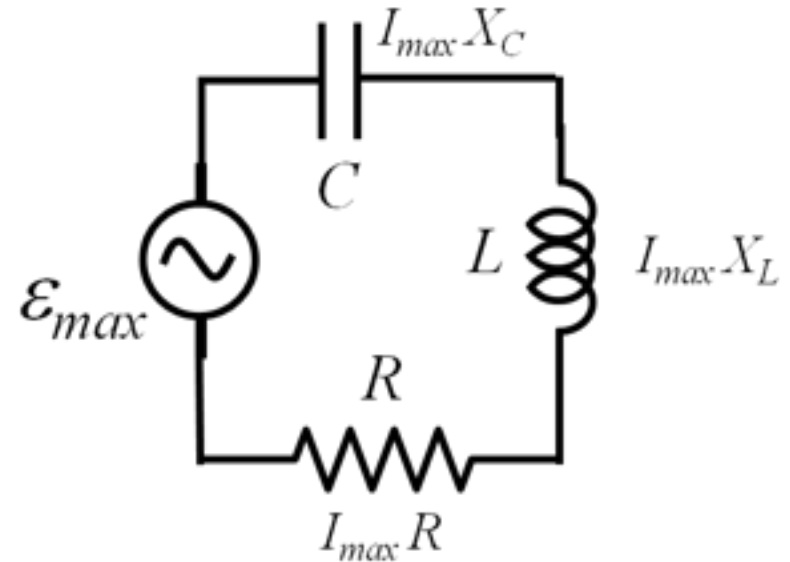
A phasor diagram showing the total voltage ϵ_{max} as the resultant of the voltage drops. A black vector labeled $\epsilon_{max} = I_{max} Z$ is the hypotenuse of a right triangle formed by a green vector labeled $I_{max} R$ (horizontal) and a purple vector (vertical).




Make this Simpler

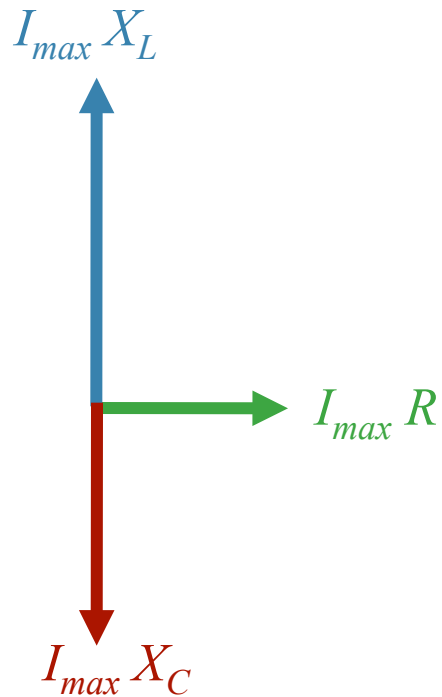

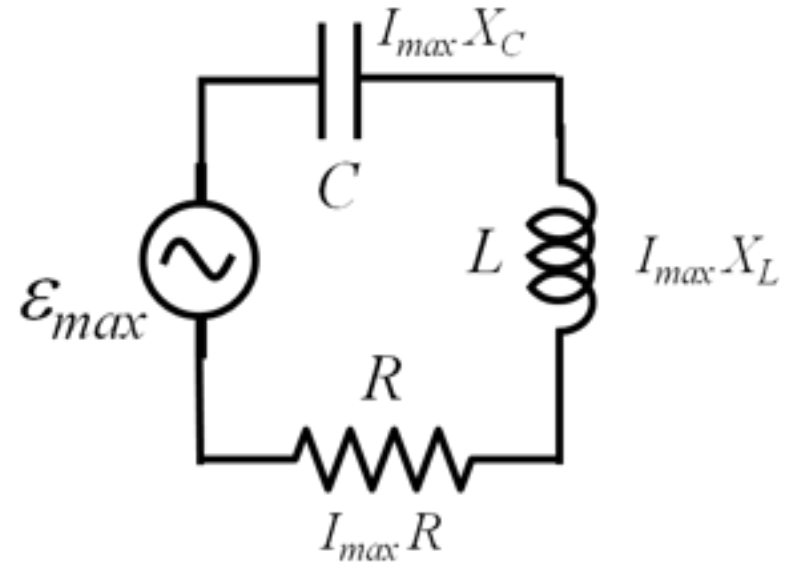A phasor diagram showing the total voltage drop ϵ_{max} as the vector sum of the individual voltage drops. A black vector labeled $\epsilon_{max} = I_{max} Z$ is the hypotenuse of a right triangle formed by a green vector labeled $I_{max} R$ (horizontal) and a purple vector (vertical). The purple vector's length is equal to the net reactance voltage drop.




Make this Simpler



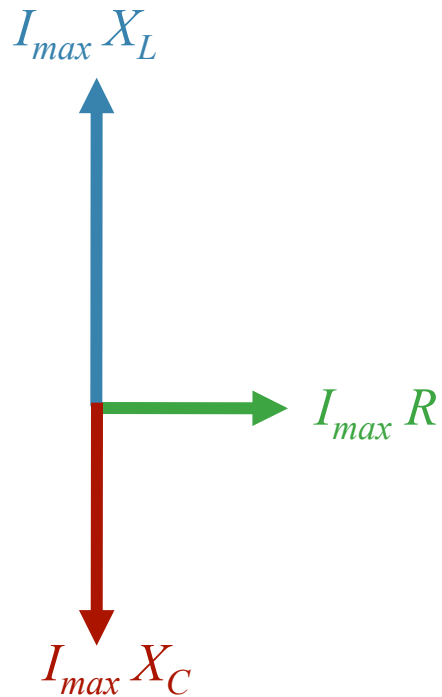


$$\epsilon_{max} = I_{max} Z$$

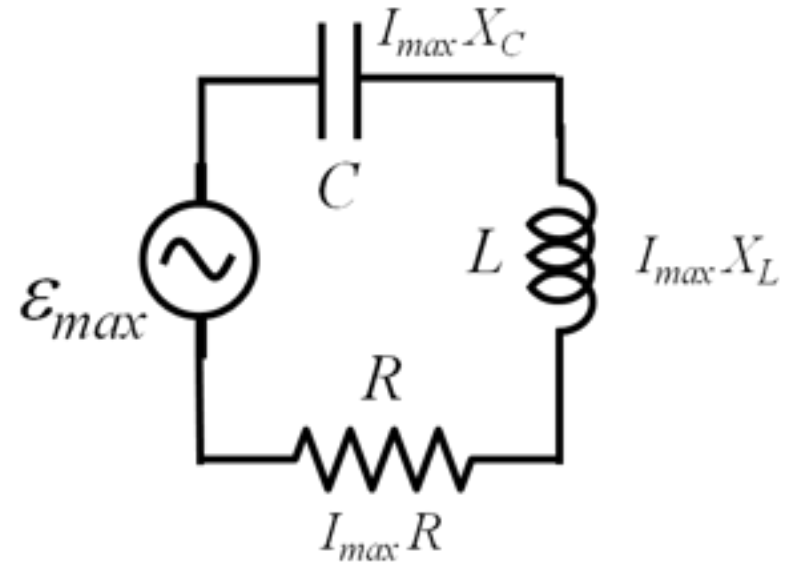
A phasor diagram showing the total voltage drop. It includes a green vector pointing horizontally to the right labeled $I_{max} R$, a purple vector pointing vertically upwards, and a black vector (the hypotenuse) pointing from the origin to the tip of the purple vector, labeled $\epsilon_{max} = I_{max} Z$.



Make this Simpler

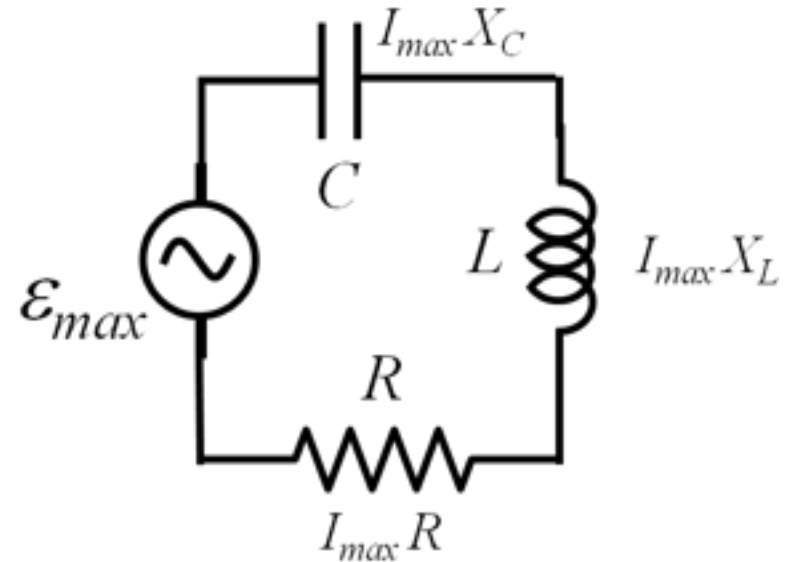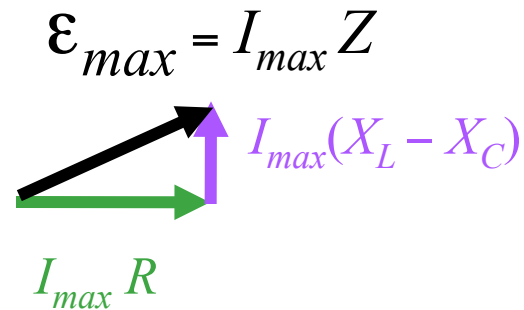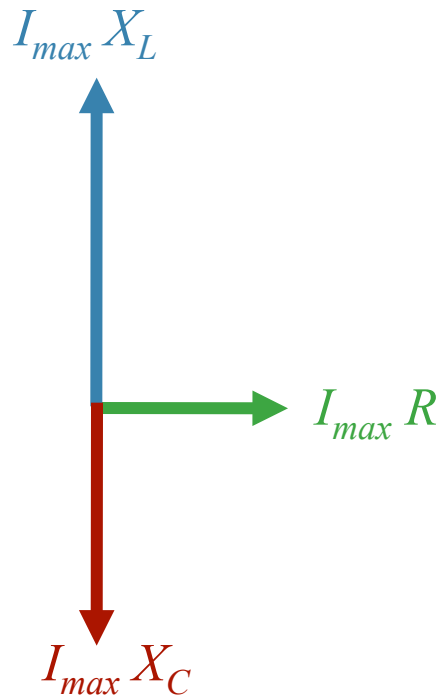

Make this Simpler

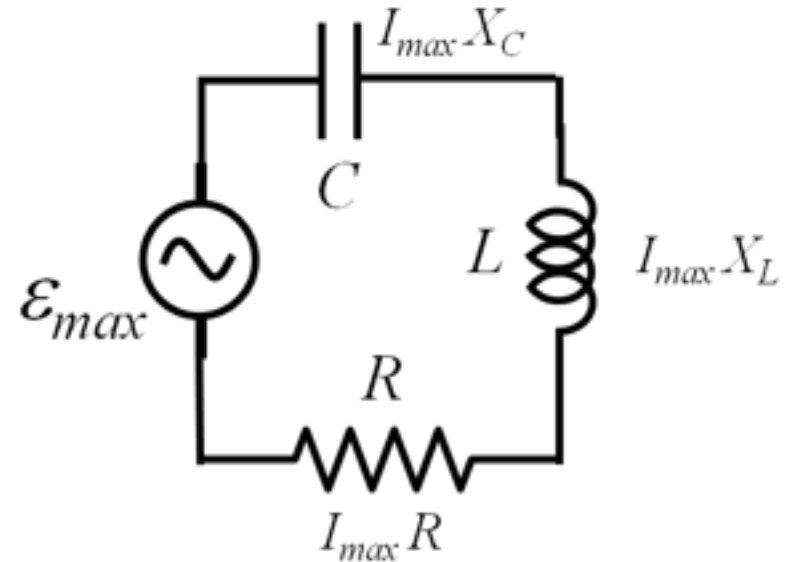

$$\mathcal{E}_{max} = I_{max} Z$$

A phasor diagram illustrating the relationship between the maximum EMF and the maximum current. It shows a black vector representing \mathcal{E}_{max} as the hypotenuse of a right-angled triangle. The horizontal leg is a green vector labeled $I_{max}R$. The vertical leg is a purple vector labeled $I_{max}(X_L - X_C)$.

Make this Simpler






$$\epsilon_{max} = I_{max} Z$$


Diagram illustrating the phasor relationship in an AC circuit. The total EMF ϵ_{max} is the resultant of the voltage drops across the resistor $I_{max} R$ and the net reactance $I_{max}(X_L - X_C)$.






Make this Simpler

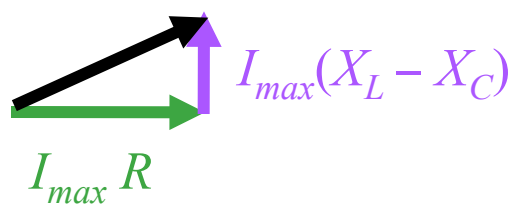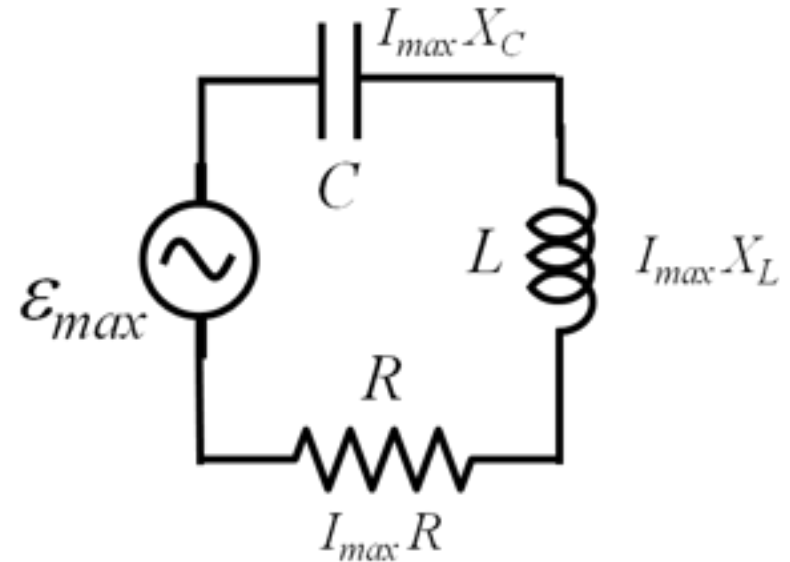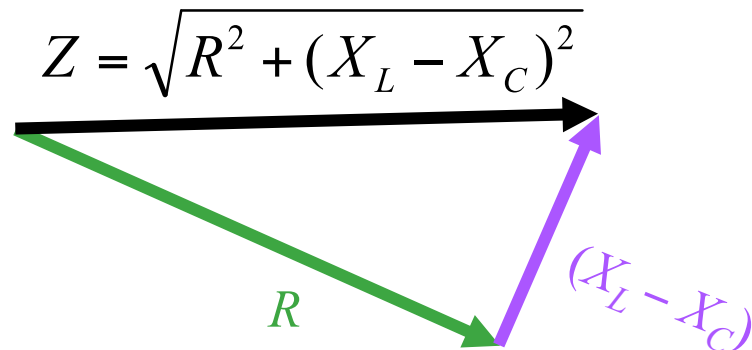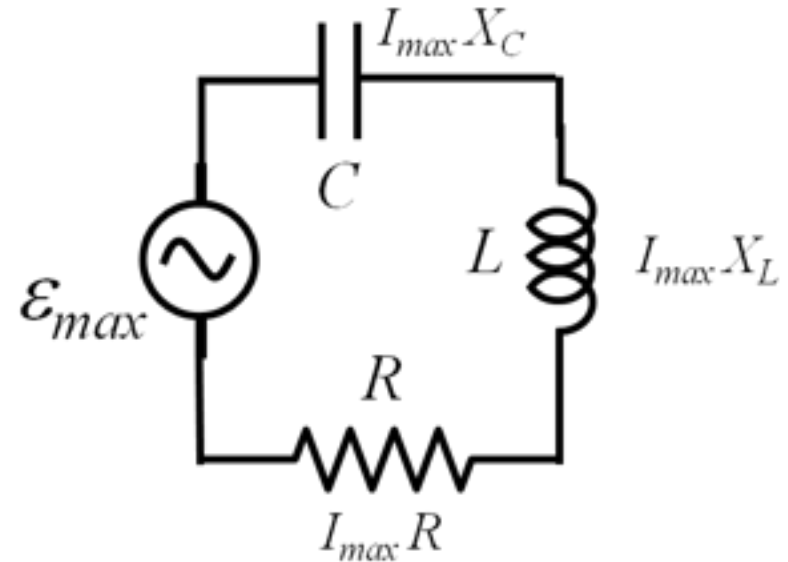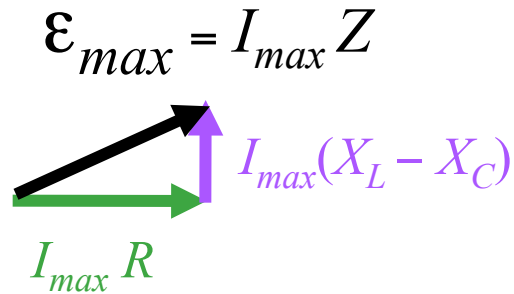




$$\tan(\phi) = \frac{X_L - X_C}{R}$$

Make this Simpler

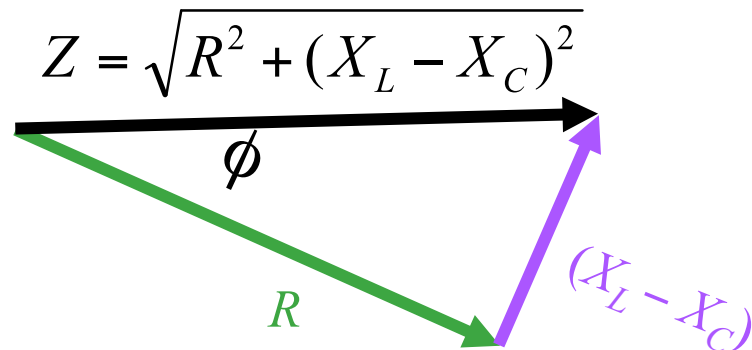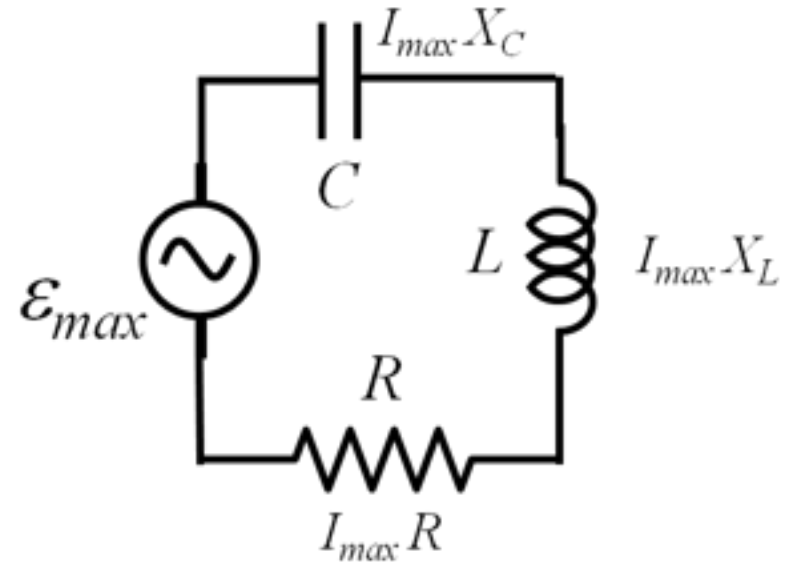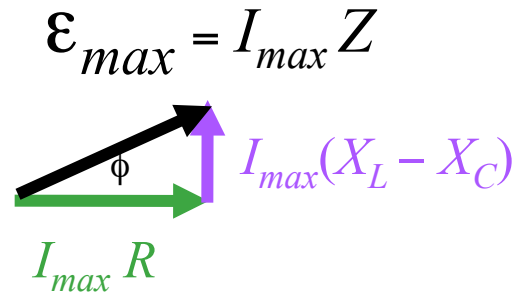

$$\tan(\phi) = \frac{X_L - X_C}{R}$$

Make this Simpler

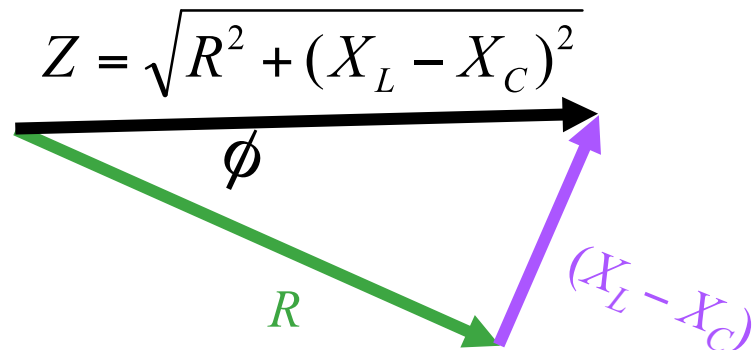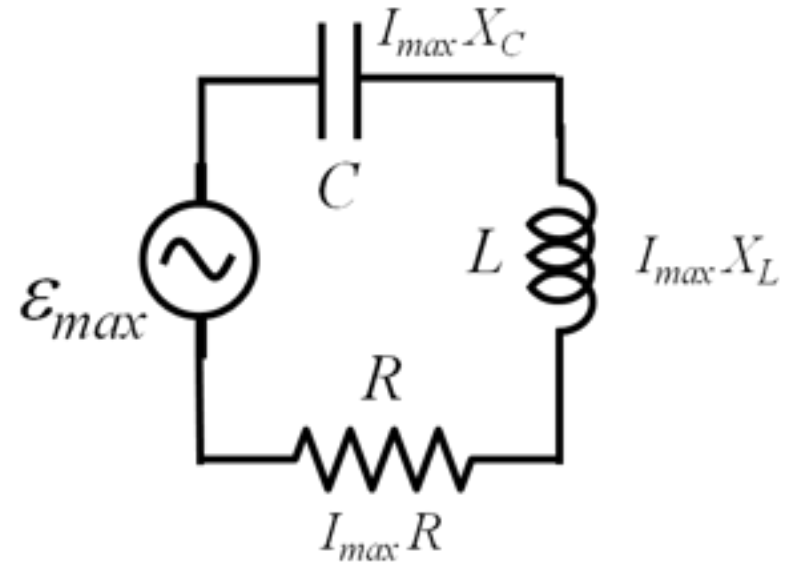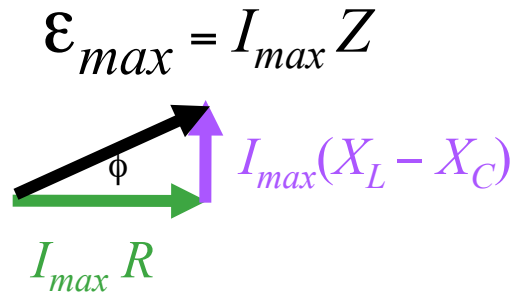

Impedance Triangle

$$\tan(\phi) = \frac{X_L - X_C}{R}$$

Summary

$$V_{Cmax} = I_{max} X_C$$

$$V_{Lmax} = I_{max} X_L$$



$$V_{Rmax} = I_{max} R$$

$$\mathcal{E}_{max} = I_{max} Z$$



$$I_{max} = \mathcal{E}_{max} / Z$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$



$$\tan(\phi) = \frac{X_L - X_C}{R}$$

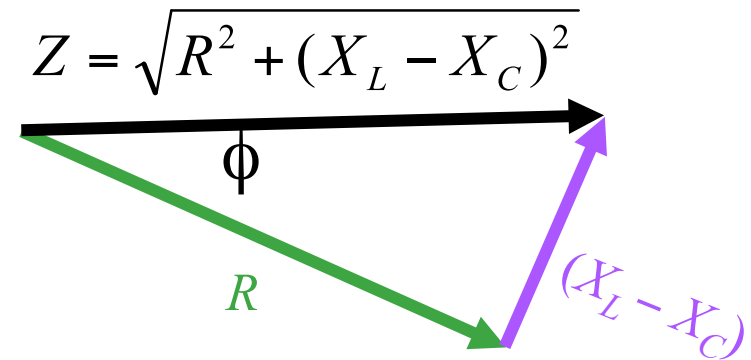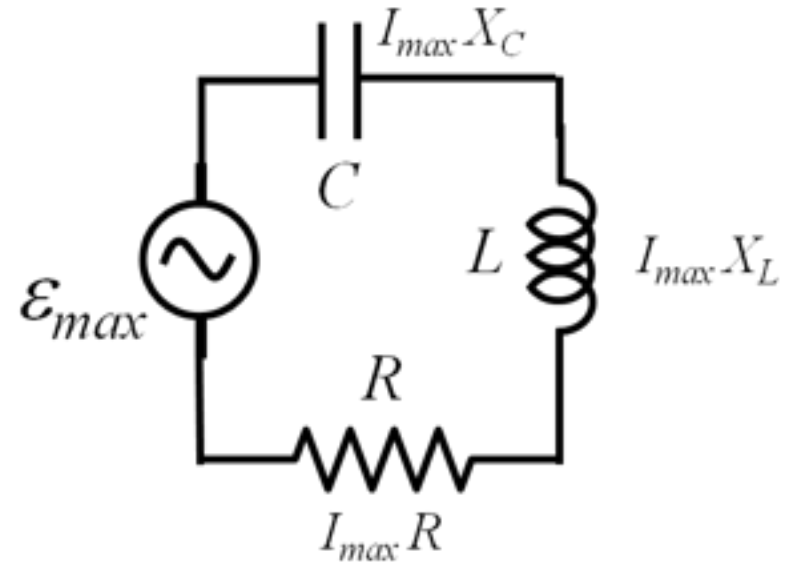

Example: RL Circuit $X_c = 0$

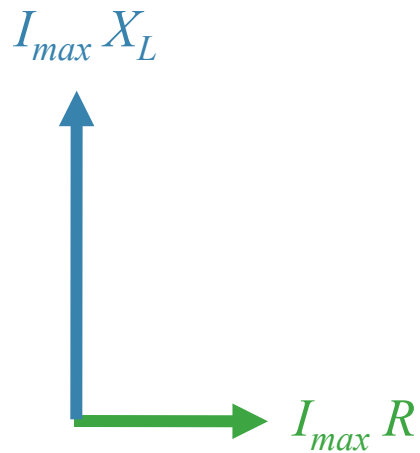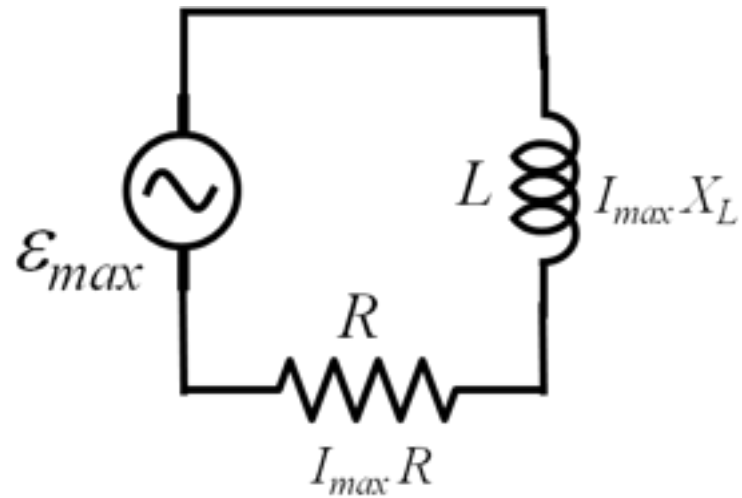


Example: RL Circuit $X_c = 0$

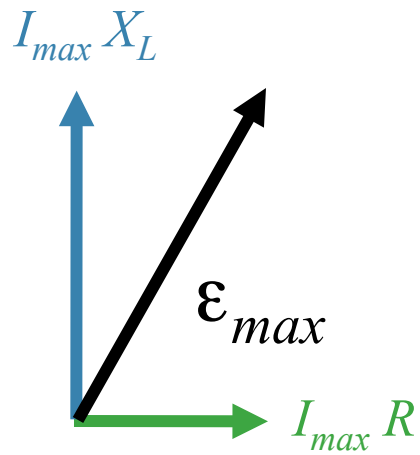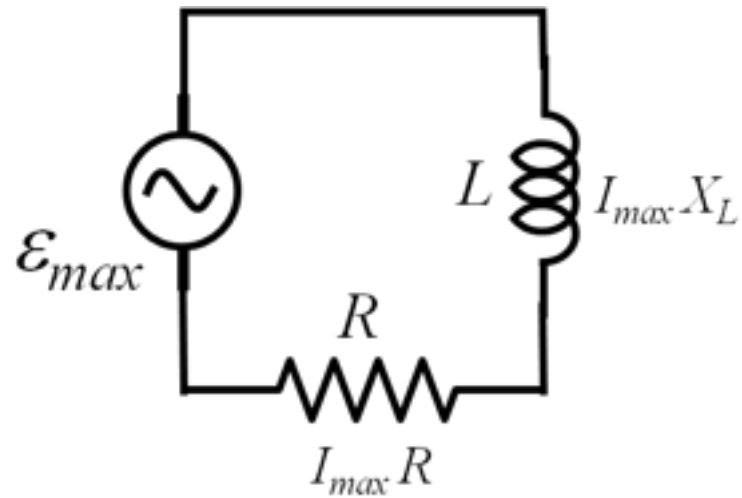

CheckPoint 2



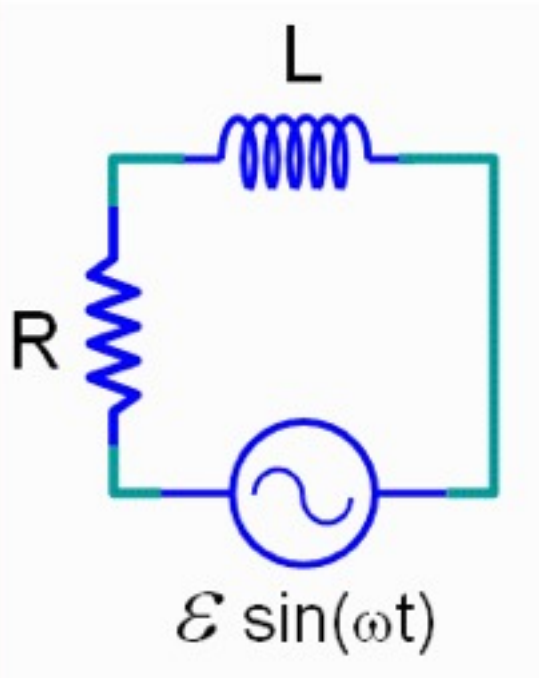2) A RL circuit is driven by an AC generator as shown in the figure.




The voltages across the resistor and generator are _____.

- A ☐ always out of phase
- B ☐ always in phase
- C ☐ sometimes in phase and sometimes out of phase

CheckPoint 2




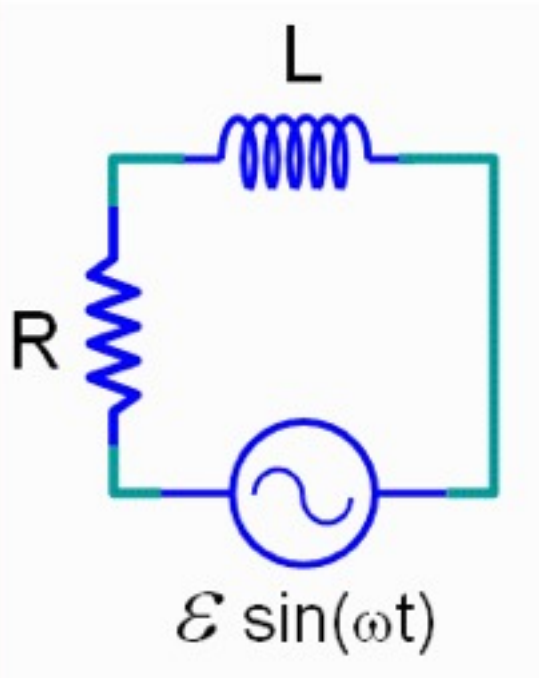2) A RL circuit is driven by an AC generator as shown in the figure.



The voltages across the resistor and generator are _____.


- A ☐ always out of phase
- B ☐ always in phase
- C ☐ sometimes in phase and sometimes out of phase

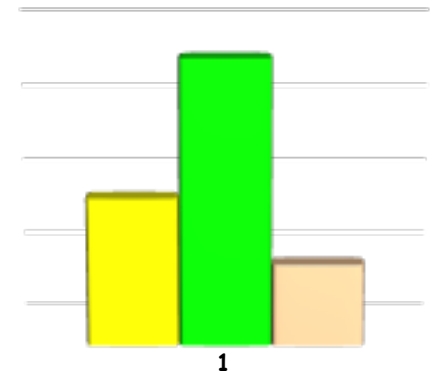

CheckPoint 2



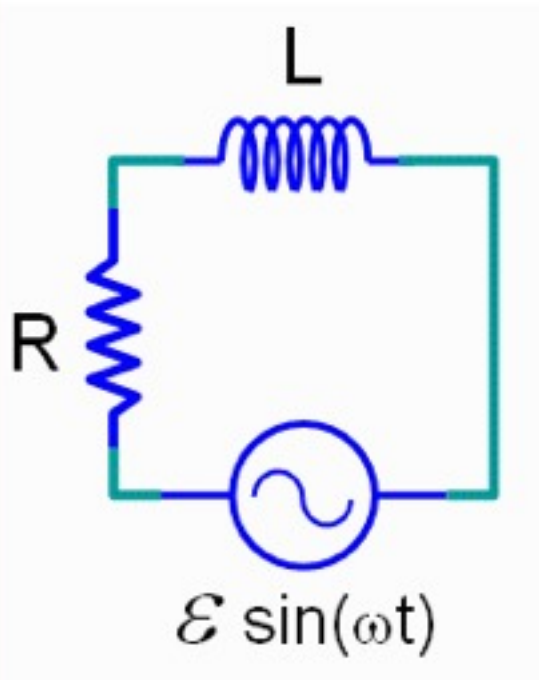
2) A RL circuit is driven by an AC generator as shown in the figure.



Draw Voltage Phasors

The voltages across the resistor and generator are _____.


- A ☐ always out of phase
- B ☐ always in phase
- C ☐ sometimes in phase and sometimes out of phase

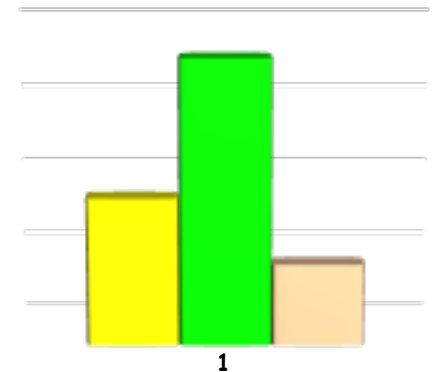

CheckPoint 2




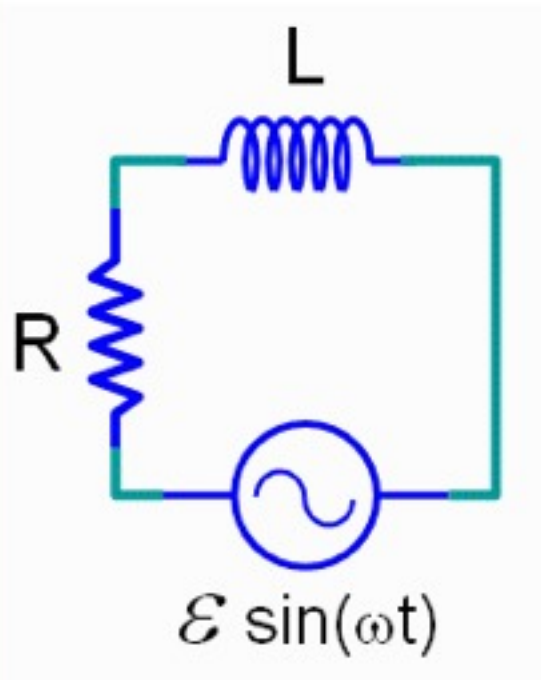
2) A RL circuit is driven by an AC generator as shown in the figure.



The voltages across the resistor and generator are _____.

- A ☐ always out of phase
- B ☐ always in phase
- C ☐ sometimes in phase and sometimes out of phase


Draw Voltage Phasors

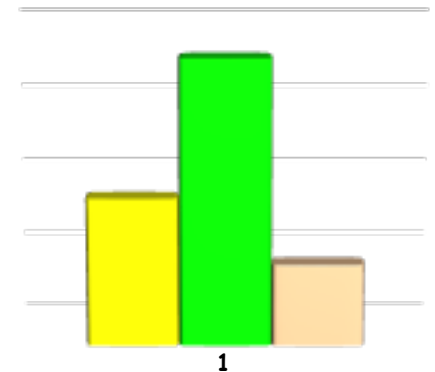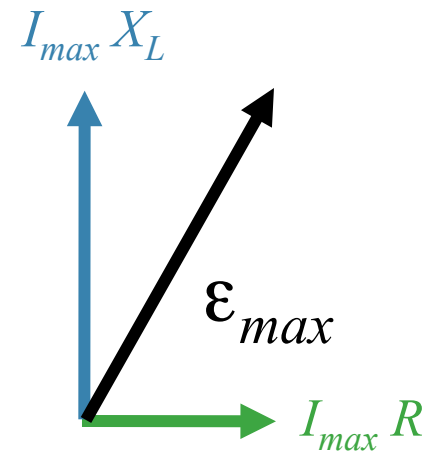


CheckPoint 2



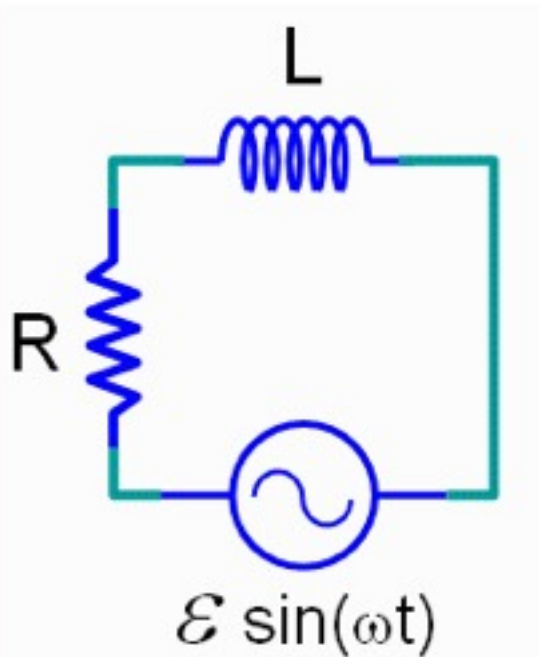2) A RL circuit is driven by an AC generator as shown in the figure.




Draw Voltage Phasors

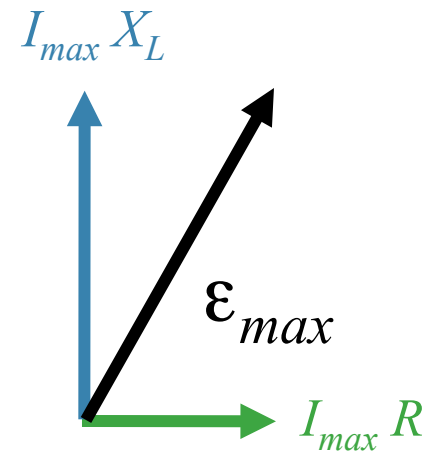

The voltages across the resistor and generator are _____.


- A ☒ always out of phase
- B ☐ always in phase
- C ☐ sometimes in phase and sometimes out of phase

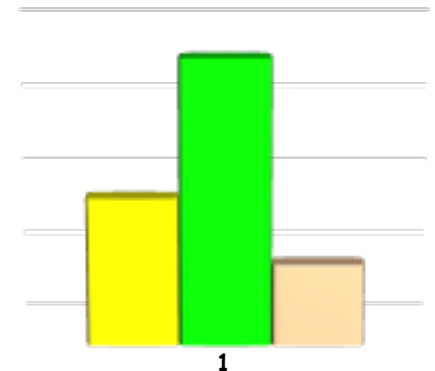

CheckPoint 4



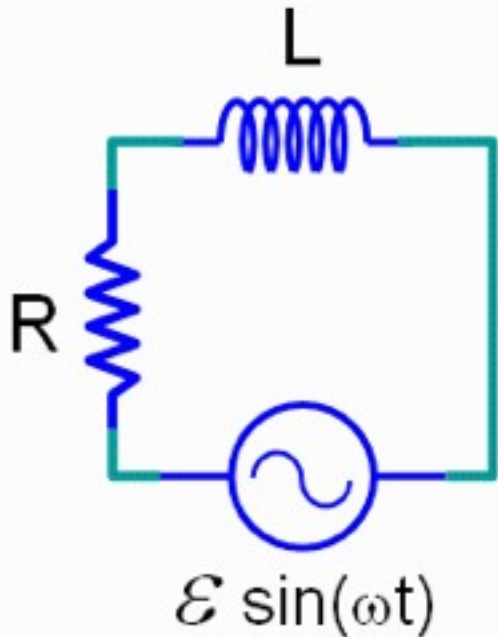A RL circuit is driven by an AC generator as shown in the figure.




The voltages across the resistor and the inductor are _____.

- A ☐ always out of phase
- B ☐ always in phase
- C ☐ sometimes in phase and sometimes out of phase

CheckPoint 4




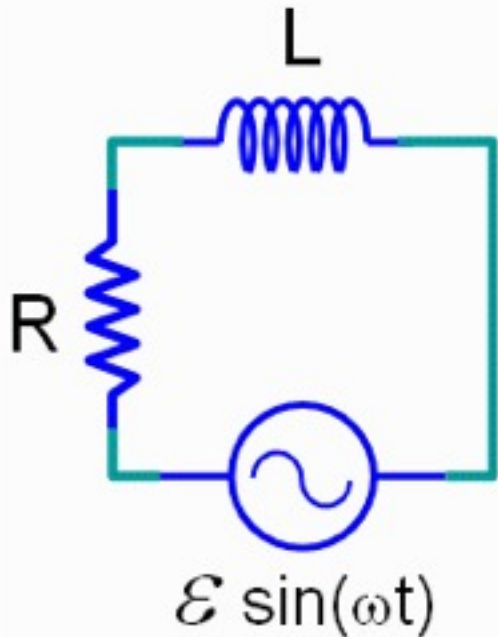A RL circuit is driven by an AC generator as shown in the figure.



The voltages across the resistor and the inductor are _____.


- A ☐ always out of phase
- B ☐ always in phase
- C ☐ sometimes in phase and sometimes out of phase

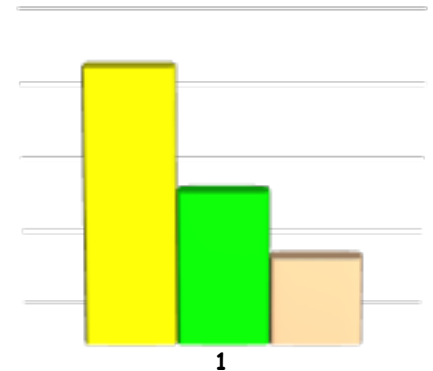

CheckPoint 4



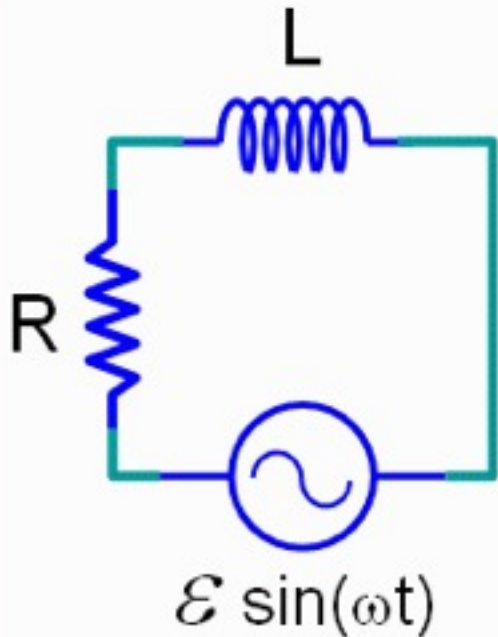
A RL circuit is driven by an AC generator as shown in the figure.



Draw Voltage Phasors

The voltages across the resistor and the inductor are _____.


- A ☐ always out of phase
- B ☐ always in phase
- C ☐ sometimes in phase and sometimes out of phase

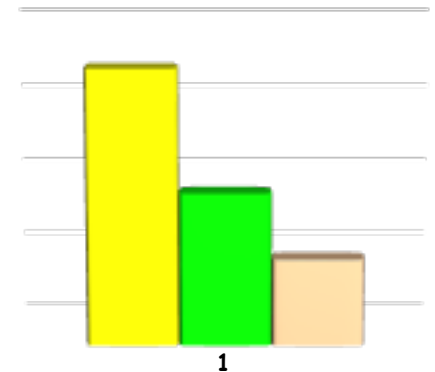


CheckPoint 4



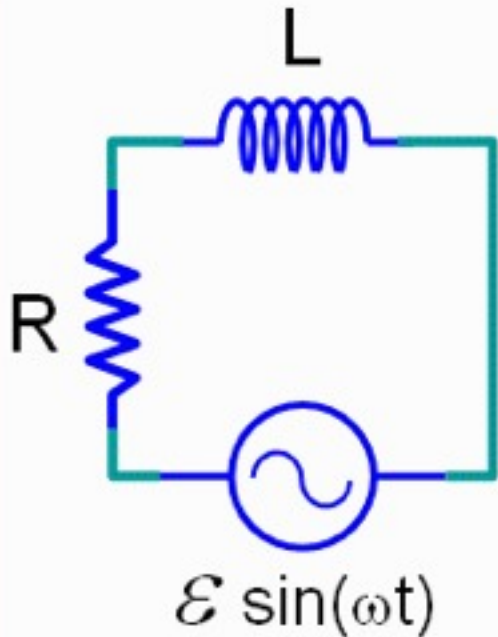A RL circuit is driven by an AC generator as shown in the figure.




Draw Voltage Phasors

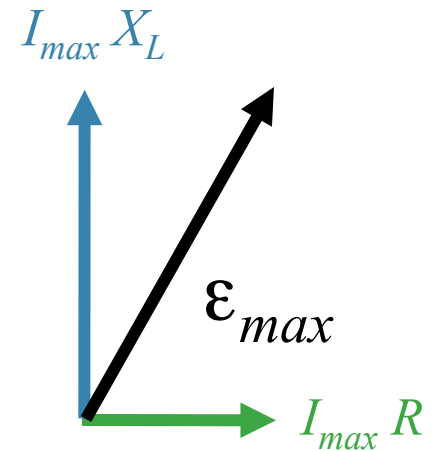

The voltages across the resistor and the inductor are _____.


- A ☐ always out of phase
- B ☐ always in phase
- C ☐ sometimes in phase and sometimes out of phase

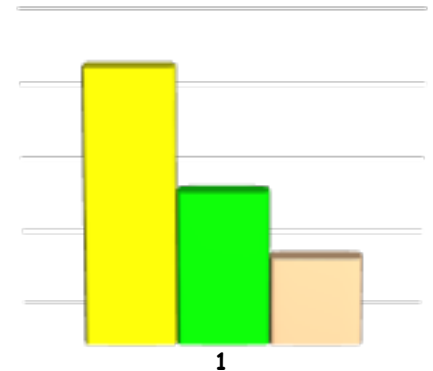


CheckPoint 4



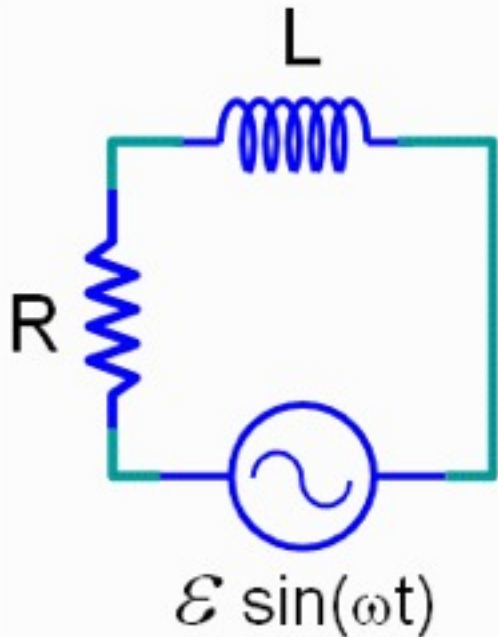A RL circuit is driven by an AC generator as shown in the figure.




Draw Voltage Phasors

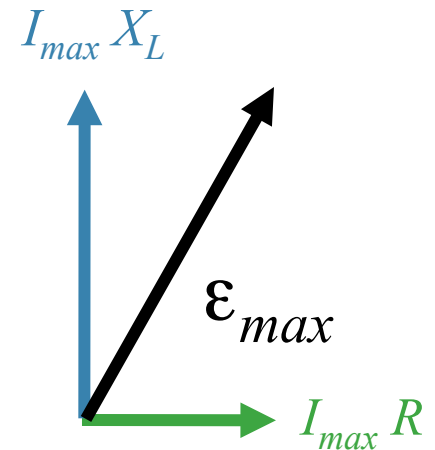

The voltages across the resistor and the inductor are _____.


- A ☒ always out of phase
- B ☐ always in phase
- C ☐ sometimes in phase and sometimes out of phase

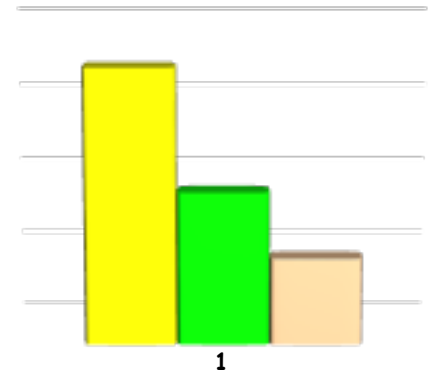

CheckPoint 6



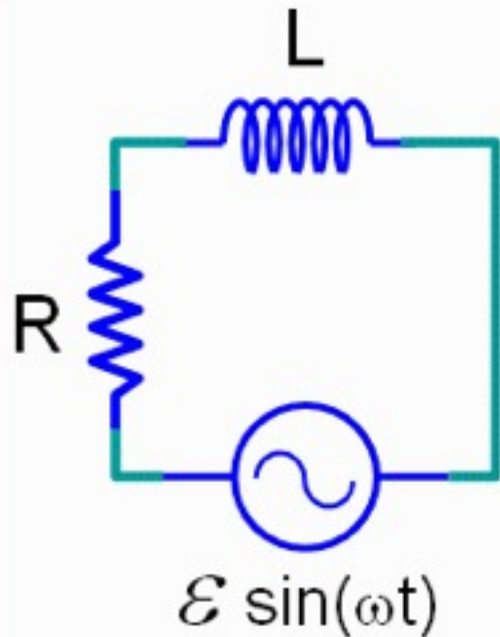A RL circuit is driven by an AC generator as shown in the figure.




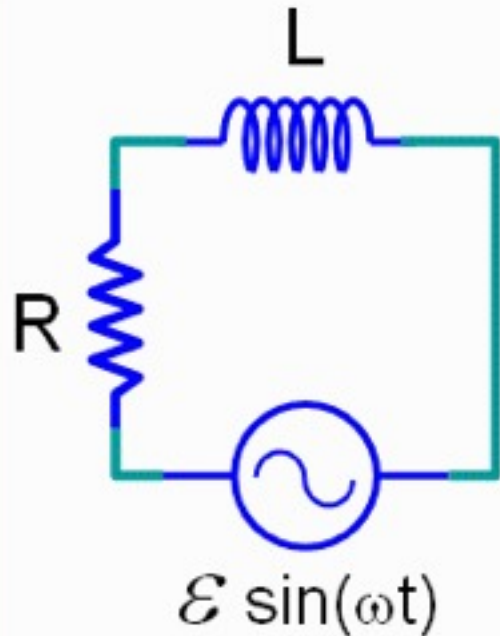- 6) The phase difference between the CURRENT through the resistor and inductor ____
- A ☐ is always zero
 - B ☐ is always 90°
 - C ☐ depends on the value of L and R
 - D ☐ depends on L , R and the generator voltage

CheckPoint 6




A RL circuit is driven by an AC generator as shown in the figure.



6) The phase difference between the CURRENT through the resistor and inductor ____

- A ☐ is always zero
- B ☐ is always 90°
- C ☐ depends on the value of L and R
- D ☐ depends on L , R and the generator voltage

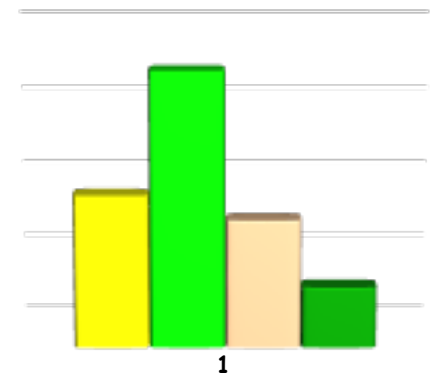


CheckPoint 6




A RL circuit is driven by an AC generator as shown in the figure.

The CURRENT is THE CURRENT

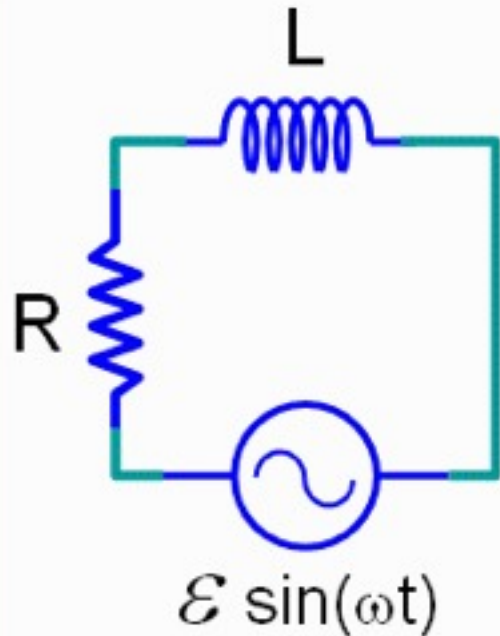

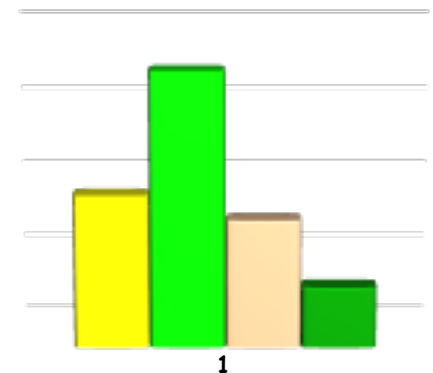6) The phase difference between the CURRENT through the resistor and inductor ____

- A ☐ is always zero
- B ☐ is always 90°
- C ☐ depends on the value of L and R
- D ☐ depends on L, R and the generator voltage




1


CheckPoint 6



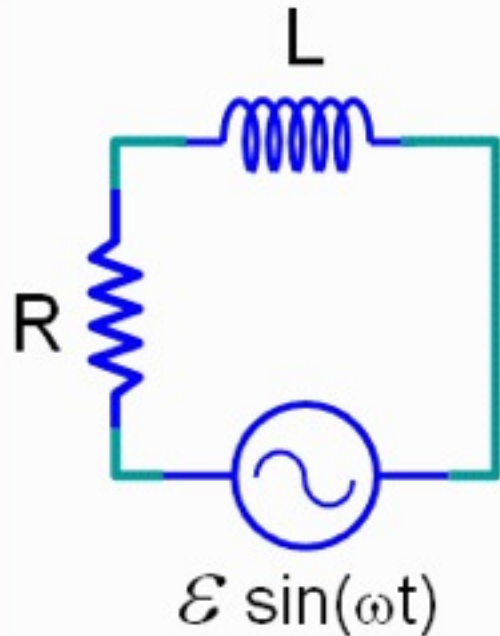A RL circuit is driven by an AC generator as shown in the figure.




The CURRENT is THE CURRENT

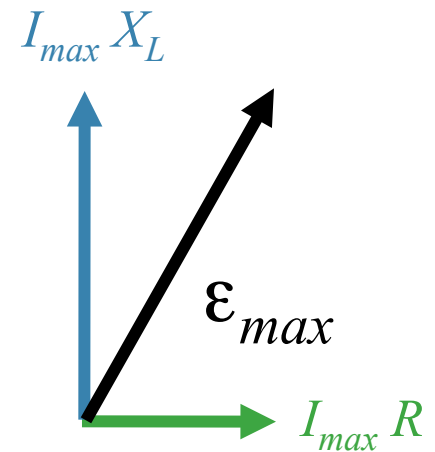

6) The phase difference between the CURRENT through the resistor and inductor ____


- A ☐ is always zero
- B ☐ is always 90°
- C ☐ depends on the value of L and R
- D ☐ depends on L, R and the generator voltage

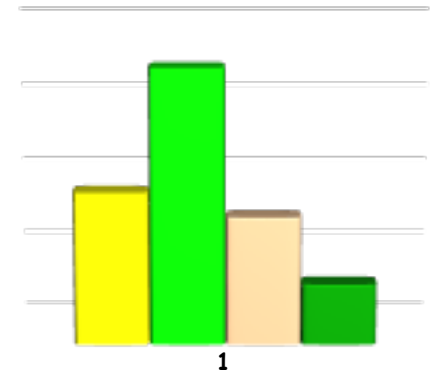


CheckPoint 6



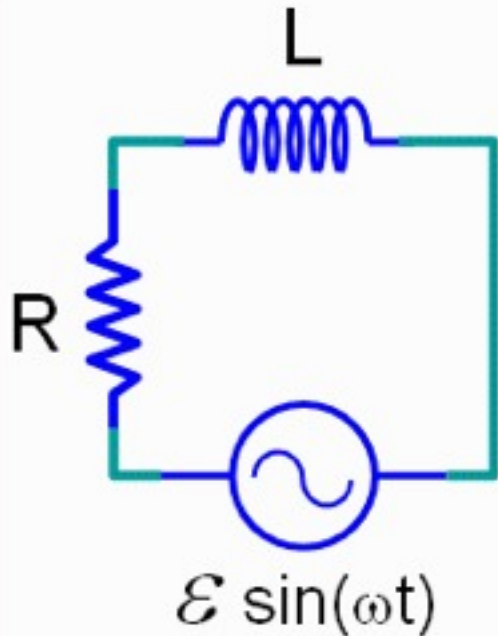A RL circuit is driven by an AC generator as shown in the figure.




The CURRENT is THE CURRENT

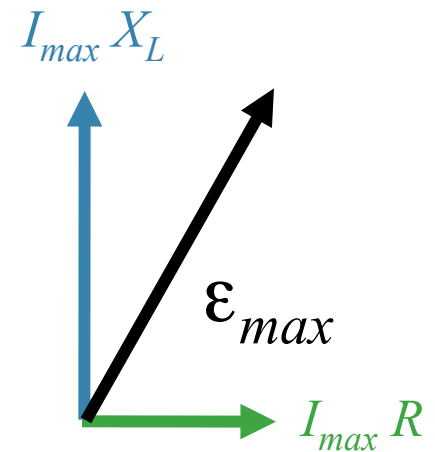

ϕ is the phase between generator and current

6) The phase difference between the CURRENT through the resistor and inductor ____


- A ☐ is always zero
- B ☐ is always 90°
- C ☐ depends on the value of L and R
- D ☐ depends on L, R and the generator voltage

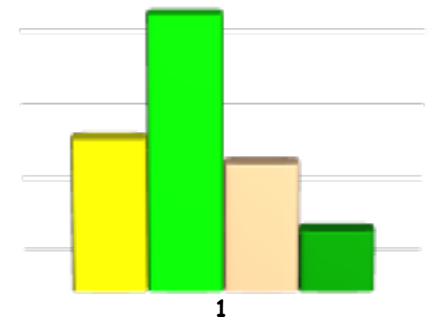


CheckPoint 6



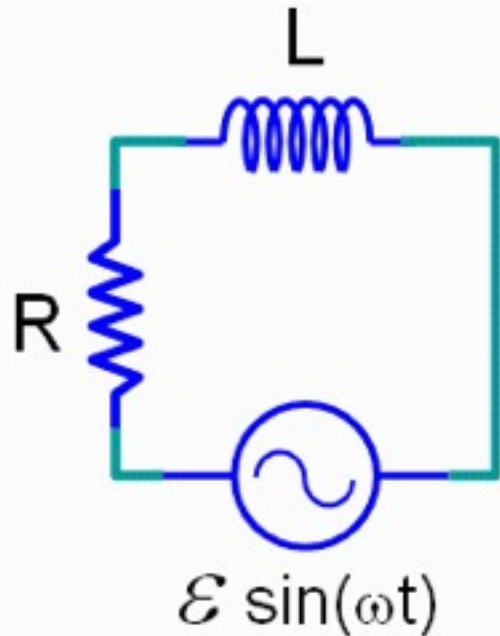A RL circuit is driven by an AC generator as shown in the figure.




The CURRENT is THE CURRENT

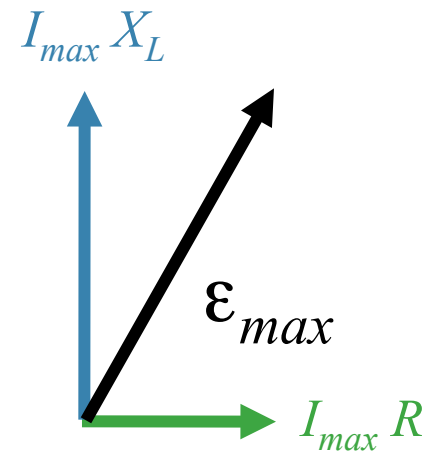

ϕ is the phase between generator and current

6) The phase difference between the CURRENT through the resistor and inductor ____



- A ☒ is always zero
- B ☐ is always 90°
- C ☐ depends on the value of L and R
- D ☐ depends on L, R and the generator voltage

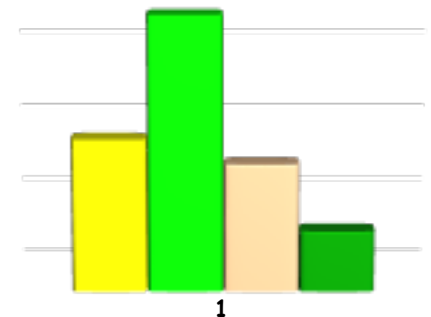

CheckPoint 8



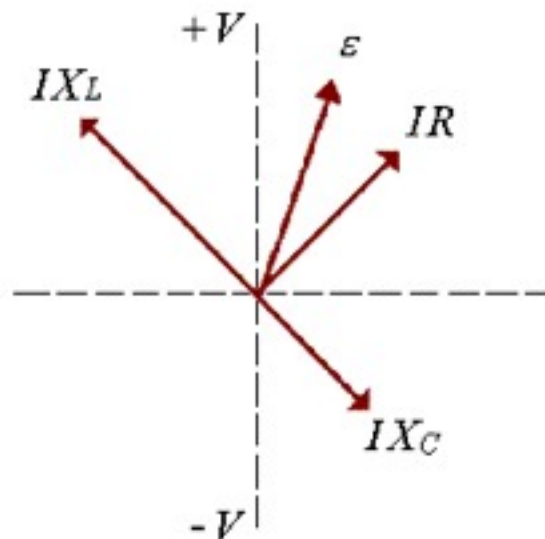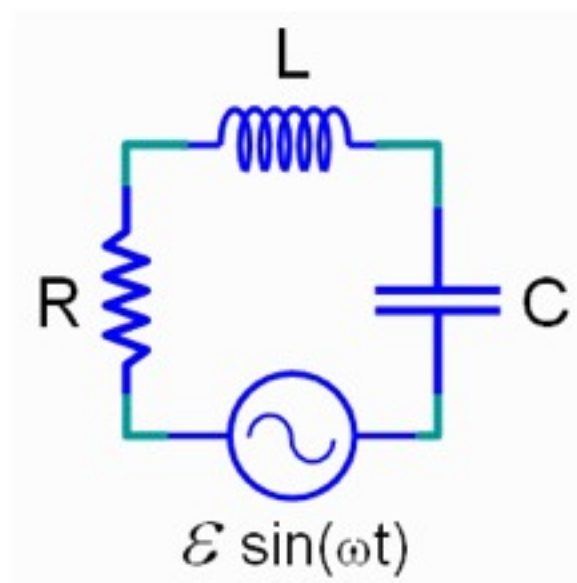A driven RLC circuit is represented by the phasor diagram below.





The vertical axis of the phasor diagram represents voltage. When the current through the circuit is maximum, what is the potential difference across the inductor?

- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}/2$
- C ☐ $V_L = V_{Lmax}$

CheckPoint 8



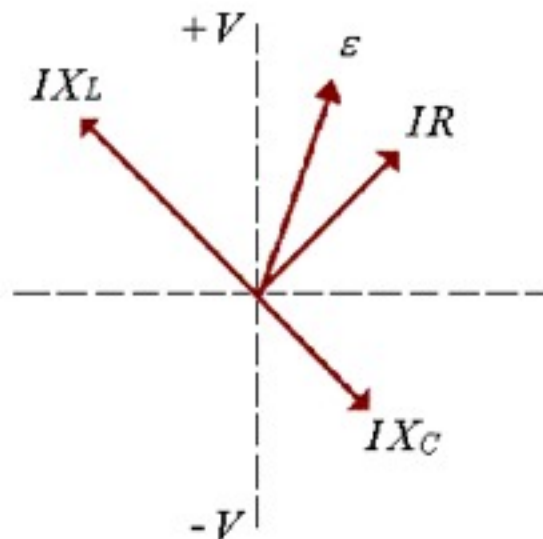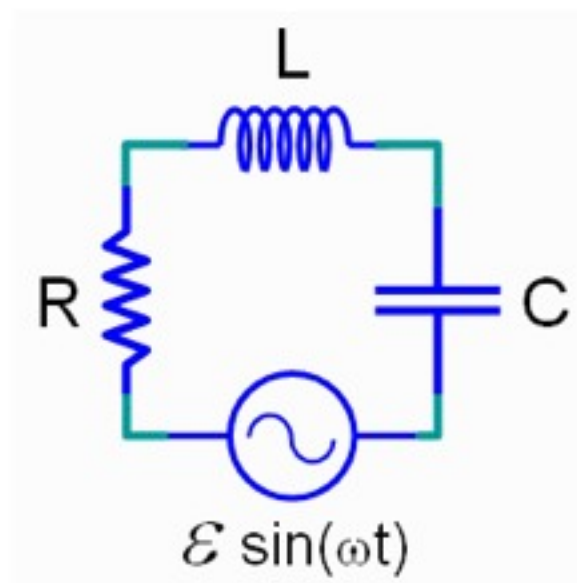A driven RLC circuit is represented by the phasor diagram below.





The vertical axis of the phasor diagram represents voltage. When the current through the circuit is maximum, what is the potential difference across the inductor?

- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}/2$
- C ☐ $V_L = V_{Lmax}$

CheckPoint 8



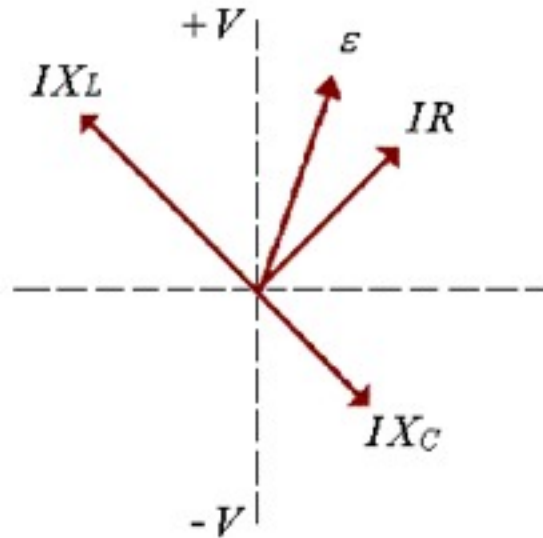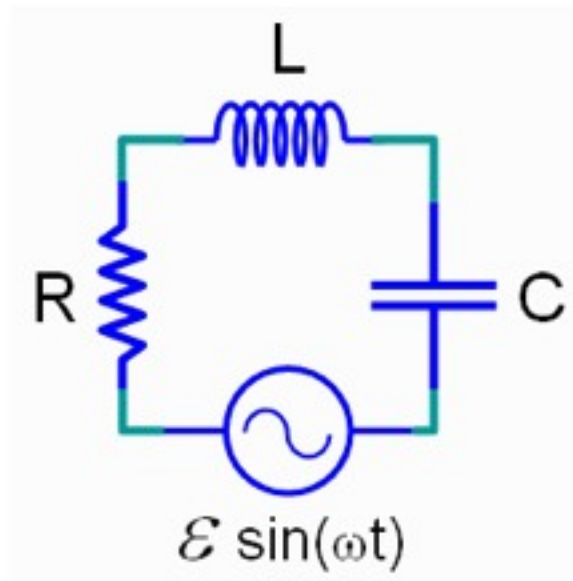
A driven RLC circuit is represented by the phasor diagram below.



The vertical axis of the phasor diagram represents voltage. When the current through the circuit is maximum, what is the potential difference across the inductor?

- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}/2$
- C ☐ $V_L = V_{Lmax}$



What does the voltage phasor diagram look like when the current is a maximum?

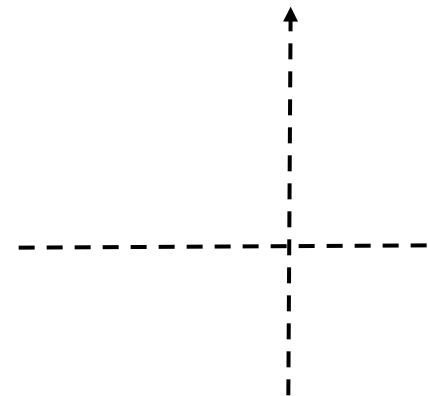

CheckPoint 8



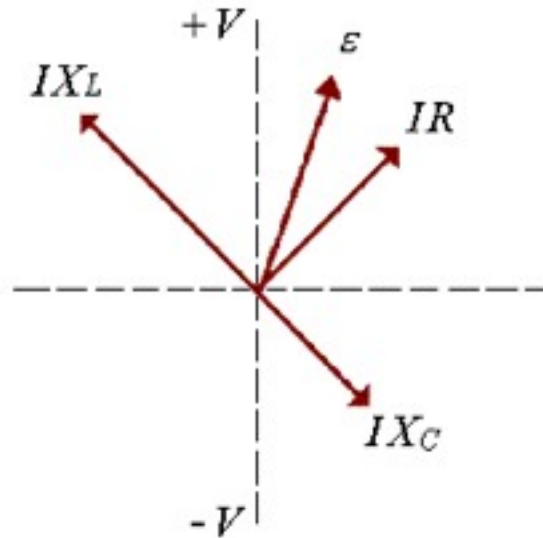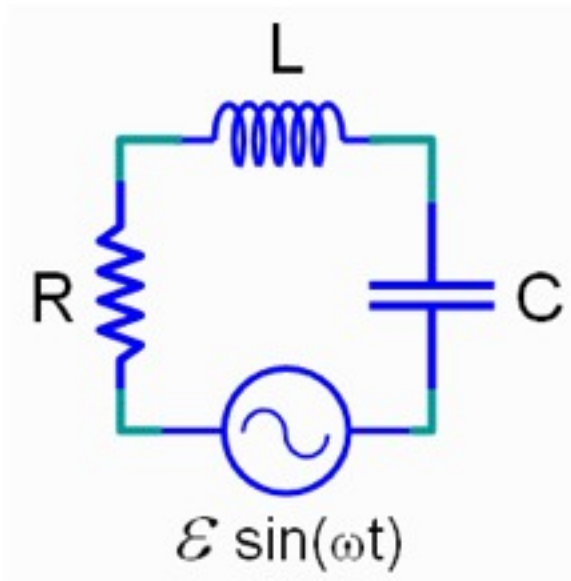
A driven RLC circuit is represented by the phasor diagram below.



The vertical axis of the phasor diagram represents voltage. When the current through the circuit is maximum, what is the potential difference across the inductor?

- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}/2$
- C ☐ $V_L = V_{Lmax}$



What does the voltage phasor diagram look like when the current is a maximum?

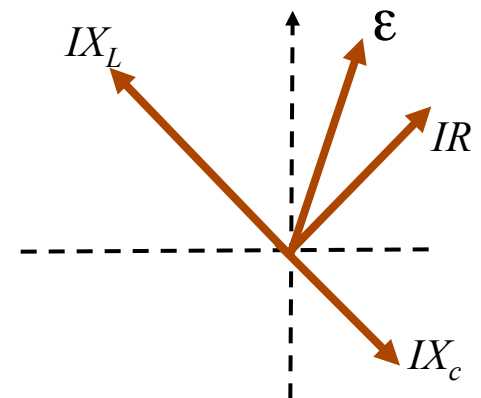

CheckPoint 8



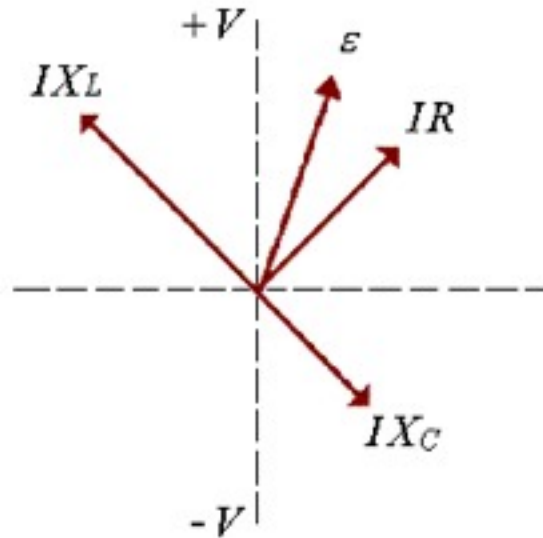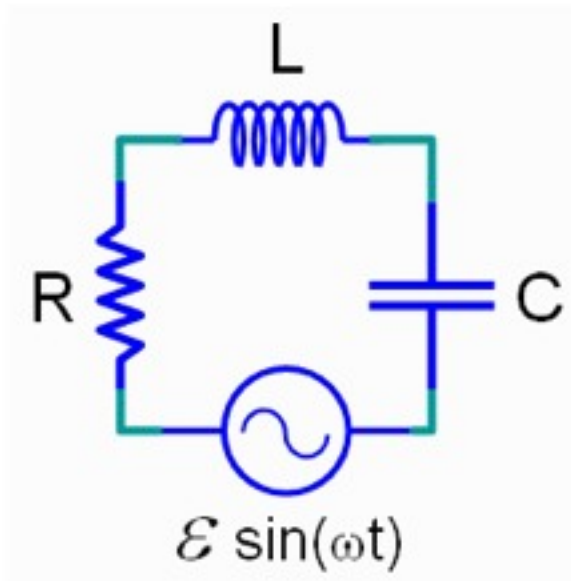
- A driven RLC circuit is represented by the phasor diagram below.



The vertical axis of the phasor diagram represents voltage. When the current through the circuit is maximum, what is the potential difference across the inductor?

- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}/2$
- C ☐ $V_L = V_{Lmax}$



What does the voltage phasor diagram look like when the current is a maximum?

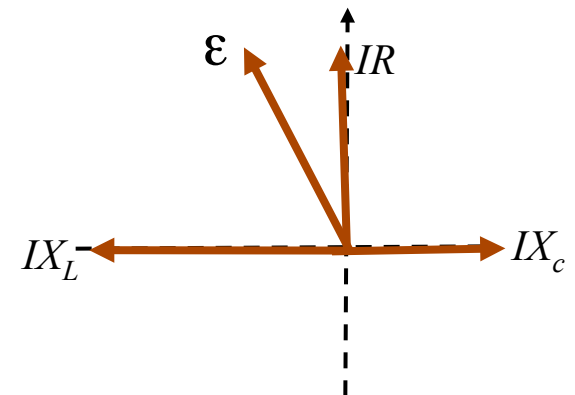

CheckPoint 8




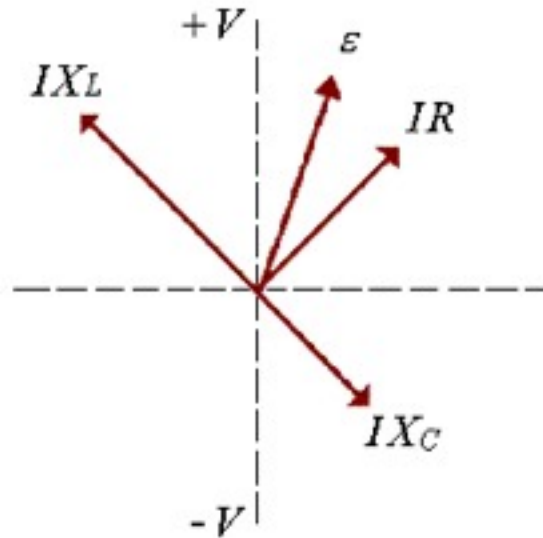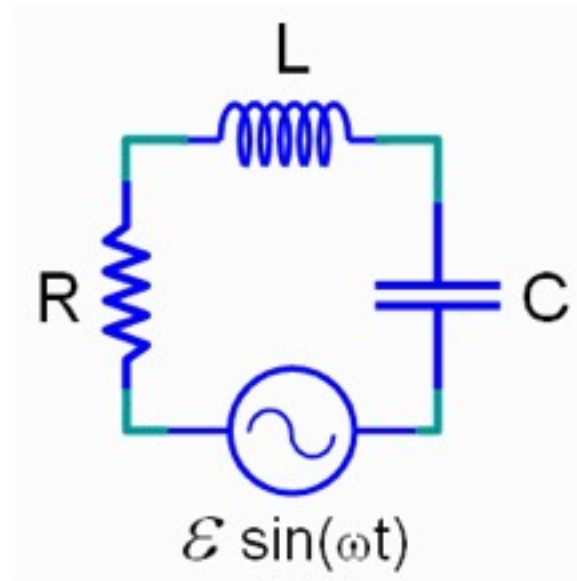- A driven RLC circuit is represented by the phasor diagram below.



The vertical axis of the phasor diagram represents voltage. When the current through the circuit is maximum, what is the potential difference across the inductor?

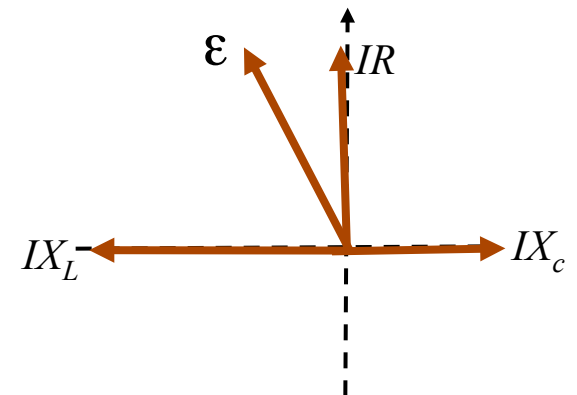- ☒ A $V_L = 0$
- ☐ B $V_L = V_{Lmax}/2$
- ☐ C $V_L = V_{Lmax}$





What does the voltage phasor diagram look like when the current is a maximum?

CheckPoint 10



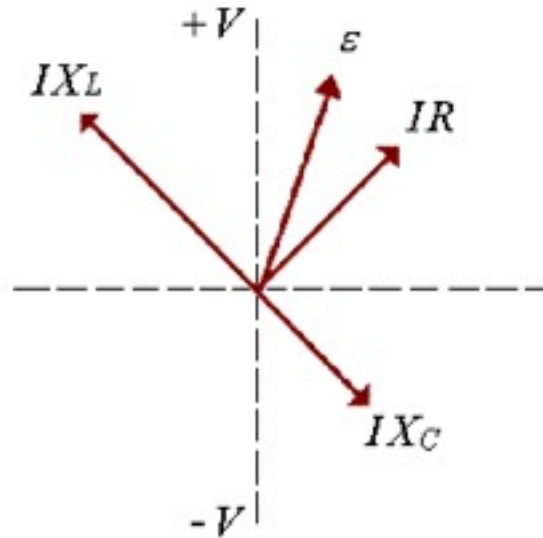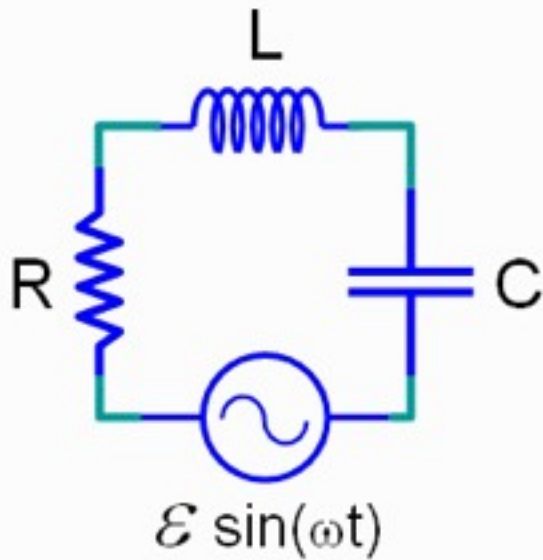A driven RLC circuit is represented by the phasor diagram below.





- When the capacitor is fully charged, what is the magnitude of the voltage across the inductor?
- A ☐ $V_L = 0$
 - B ☐ $V_L = V_{Lmax}/2$
 - C ☐ $V_L = V_{Lmax}$

CheckPoint 10



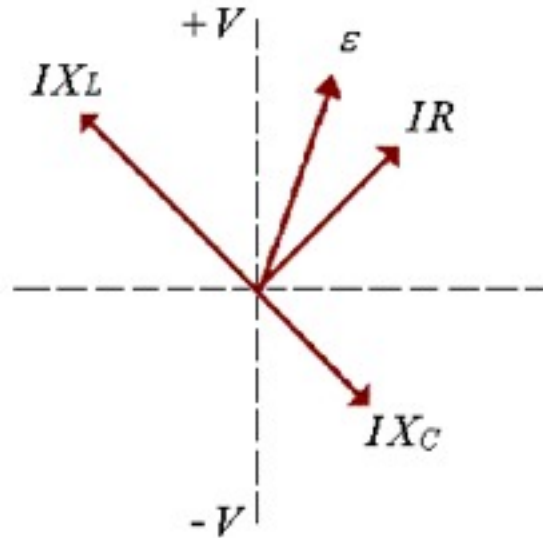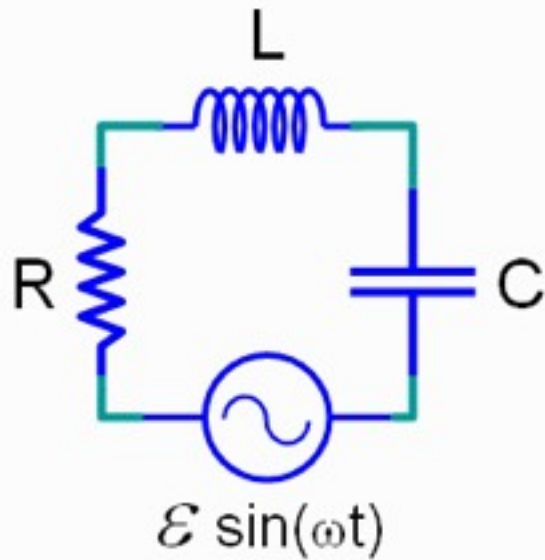A driven RLC circuit is represented by the phasor diagram below.





- When the capacitor is fully charged, what is the magnitude of the voltage across the inductor?
- A ☐ $V_L = 0$
 - B ☐ $V_L = V_{Lmax}/2$
 - C ☐ $V_L = V_{Lmax}$

CheckPoint 10



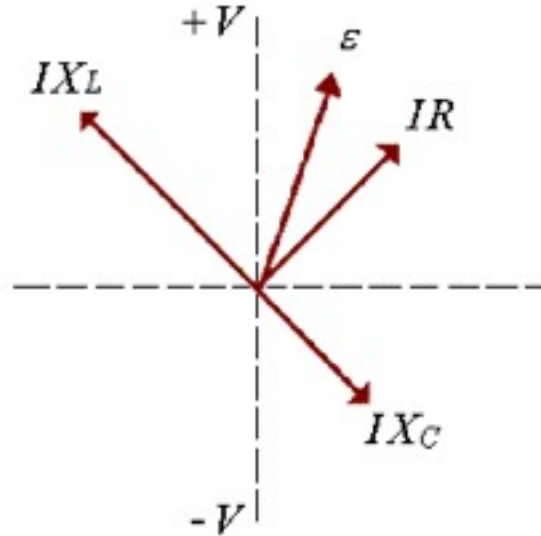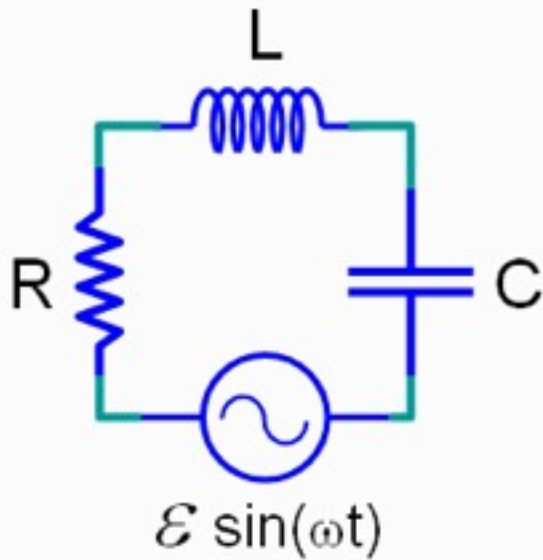A driven RLC circuit is represented by the phasor diagram below.






- When the capacitor is fully charged, what is the magnitude of the voltage across the inductor?
- A ☐ $V_L = 0$
 - B ☐ $V_L = V_{Lmax}/2$
 - C ☐ $V_L = V_{Lmax}$

What does the voltage phasor diagram look like when the capacitor is fully charged?

CheckPoint 10

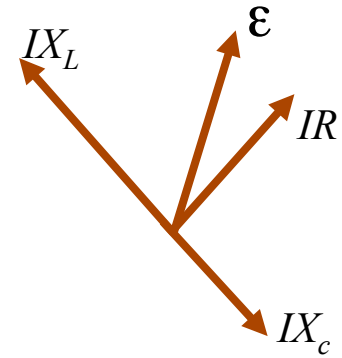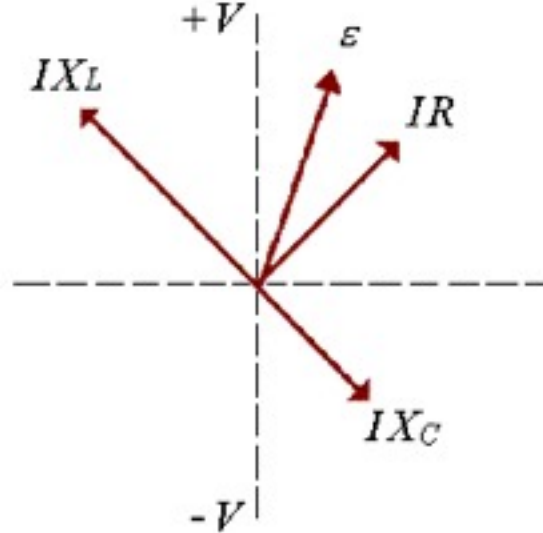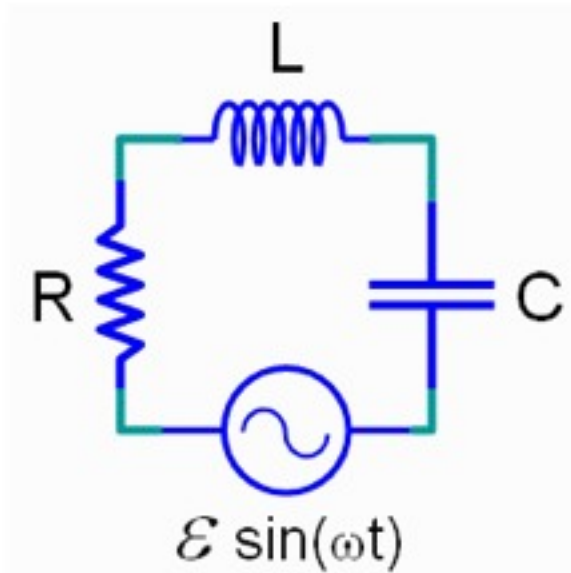A driven RLC circuit is represented by the phasor diagram below.



When the capacitor is fully charged, what is the magnitude of the voltage across the inductor?




- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}/2$
- C ☐ $V_L = V_{Lmax}$

What does the voltage phasor diagram look like when the capacitor is fully charged?

CheckPoint 10



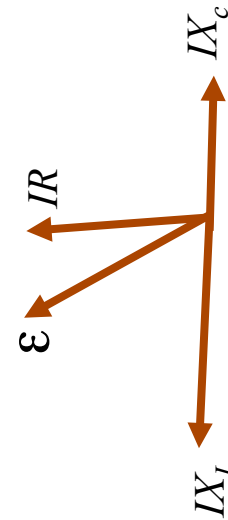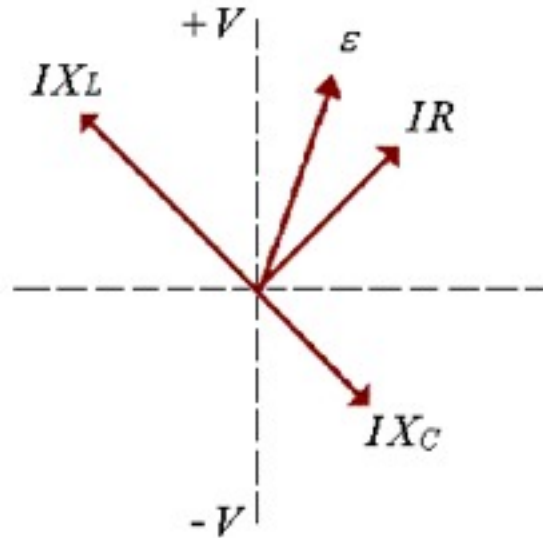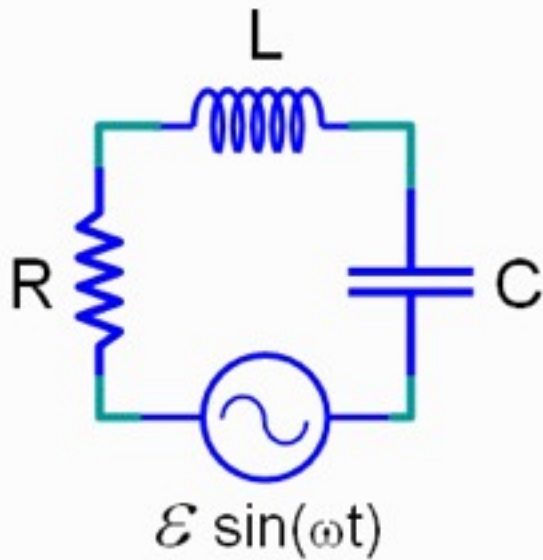A driven RLC circuit is represented by the phasor diagram below.






- When the capacitor is fully charged, what is the magnitude of the voltage across the inductor?
- A ☐ $V_L = 0$
 - B ☐ $V_L = V_{Lmax}/2$
 - C ☐ $V_L = V_{Lmax}$

What does the voltage phasor diagram look like when the capacitor is fully charged?

CheckPoint 10



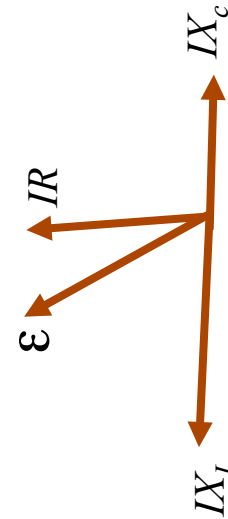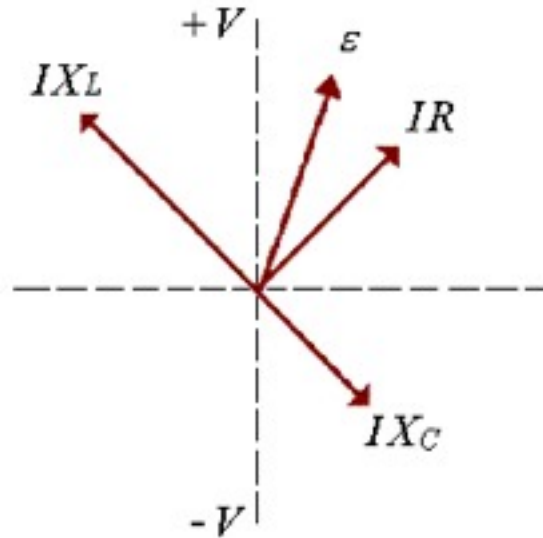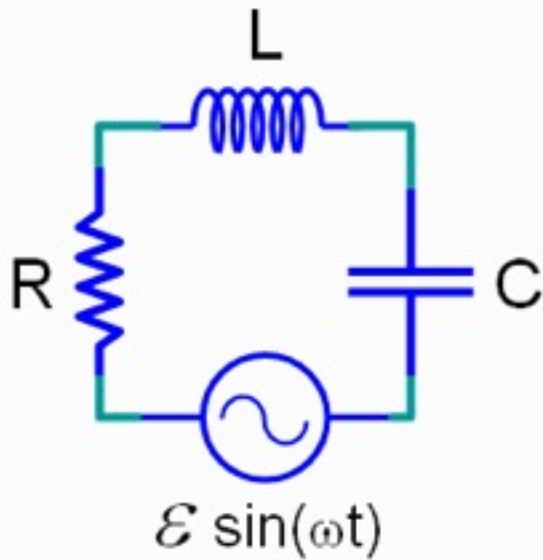A driven RLC circuit is represented by the phasor diagram below.



When the capacitor is fully charged, what is the magnitude of the voltage across the inductor?




- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}/2$
- C ☒ $V_L = V_{Lmax}$

What does the voltage phasor diagram look like when the capacitor is fully charged?

CheckPoint 12



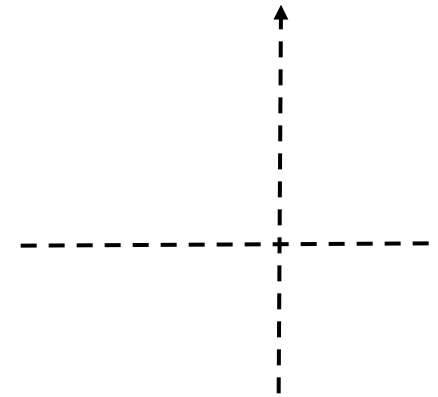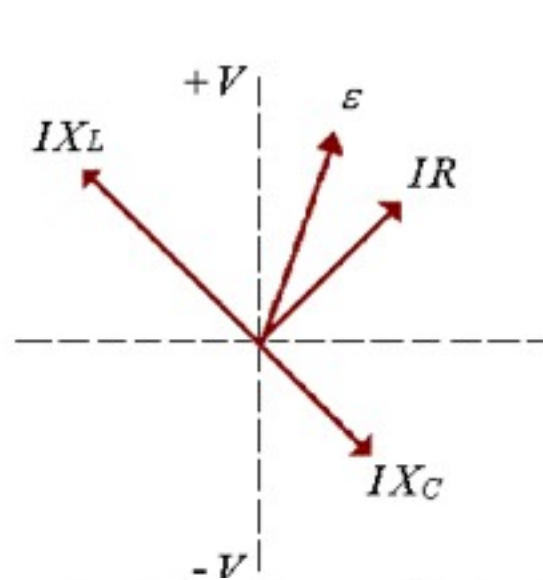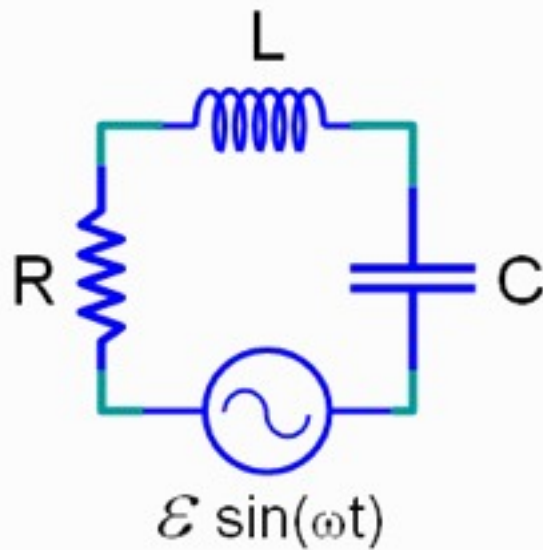A driven RLC circuit is represented by the phasor diagram below.






12) When the voltage across the capacitor is at its positive maximum, $V_C = +V_{Cmax}$, what is the voltage across the inductor?

- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}$
- C ☐ $V_L = -V_{Lmax}$

CheckPoint 12

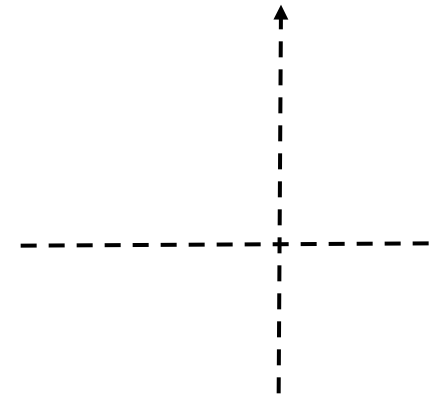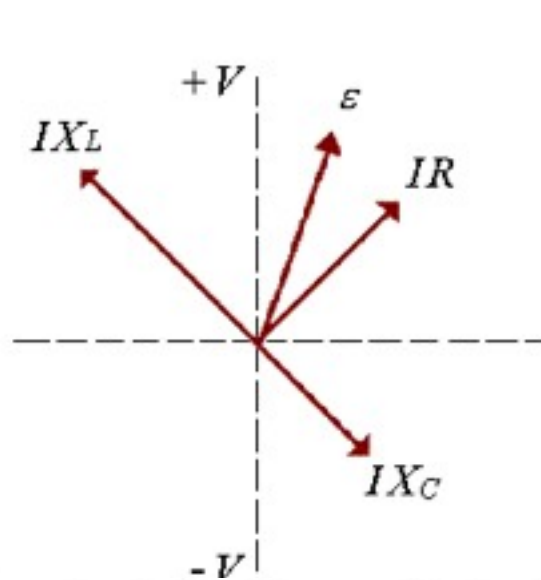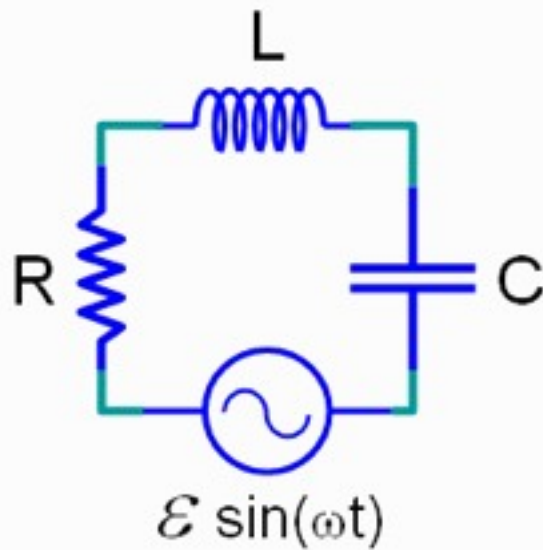A driven RLC circuit is represented by the phasor diagram below.



12) When the voltage across the capacitor is at its positive maximum, $V_C = +V_{Cmax}$, what is the voltage across the inductor?




- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}$
- C ☐ $V_L = -V_{Lmax}$

1

CheckPoint 12



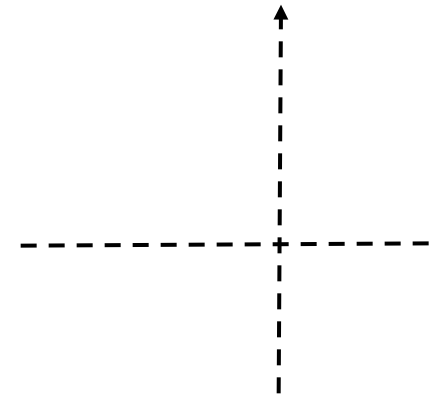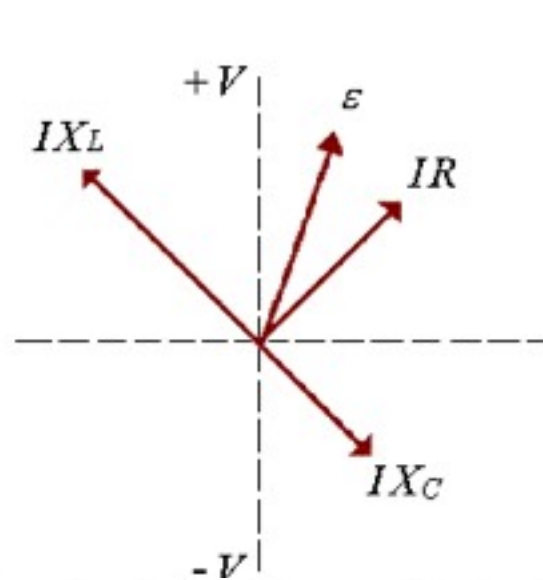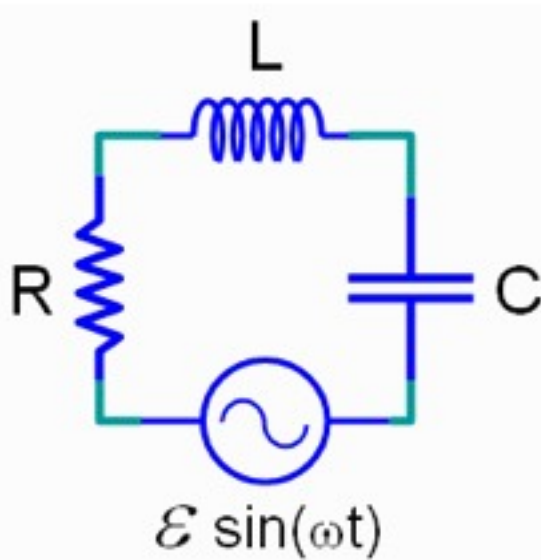A driven RLC circuit is represented by the phasor diagram below.



12) When the voltage across the capacitor is at its positive maximum, $V_C = +V_{Cmax}$, what is the voltage across the inductor?




- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}$
- C ☐ $V_L = -V_{Lmax}$

1

What does the voltage phasor diagram look like when the voltage across capacitor is at its positive maximum?

CheckPoint 12

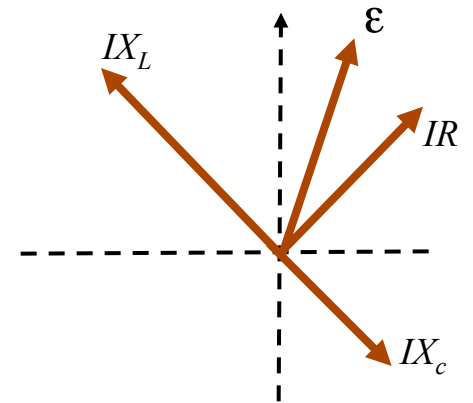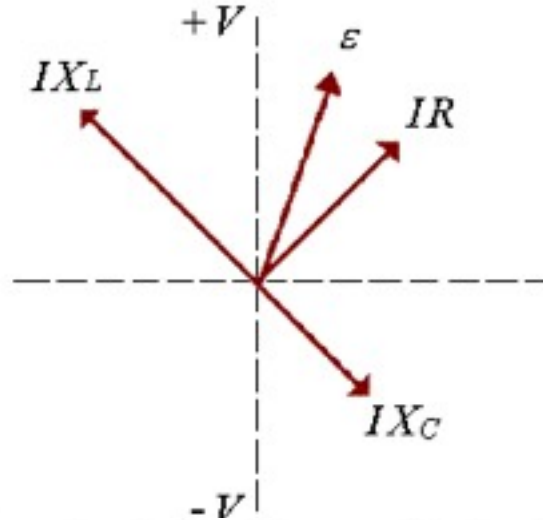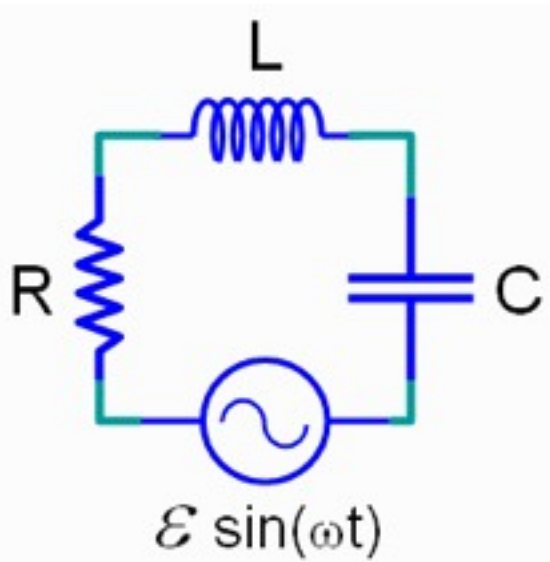A driven RLC circuit is represented by the phasor diagram below.



12) When the voltage across the capacitor is at its positive maximum, $V_C = +V_{Cmax}$, what is the voltage across the inductor?




- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}$
- C ☐ $V_L = -V_{Lmax}$

1

What does the voltage phasor diagram look like when the voltage across capacitor is at its positive maximum?

CheckPoint 12

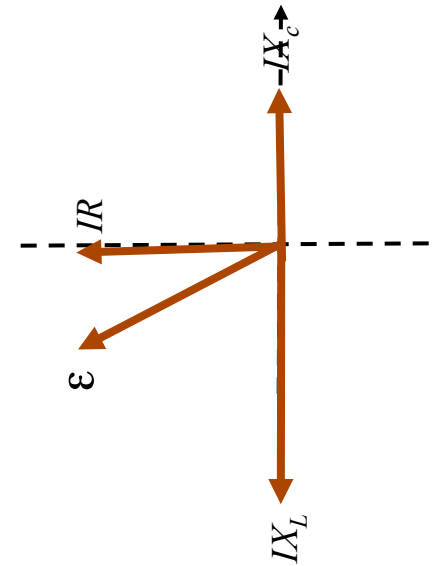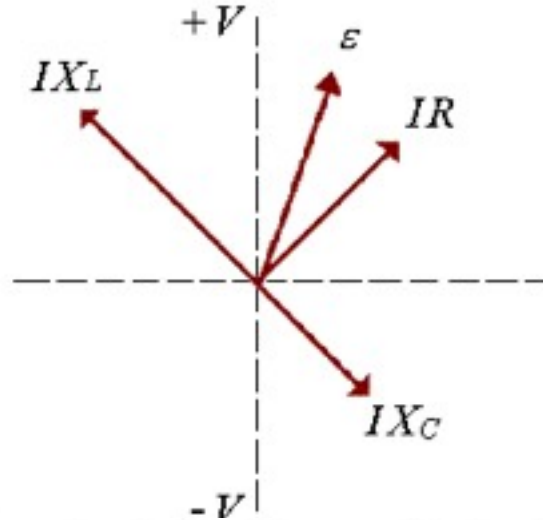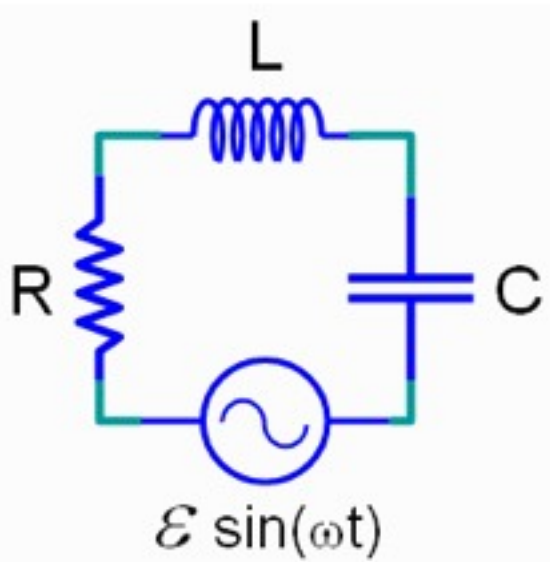A driven RLC circuit is represented by the phasor diagram below.



12) When the voltage across the capacitor is at its positive maximum, $V_C = +V_{Cmax}$, what is the voltage across the inductor?




- A ☐ $V_L = 0$
- B ☐ $V_L = V_{Lmax}$
- C ☐ $V_L = -V_{Lmax}$

1

What does the voltage phasor diagram look like when the voltage across capacitor is at its positive maximum?

CheckPoint 12

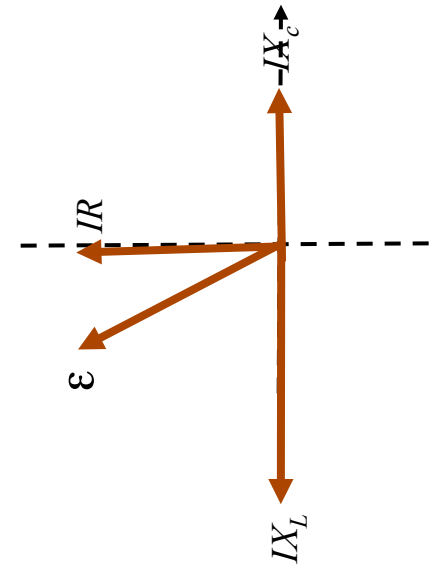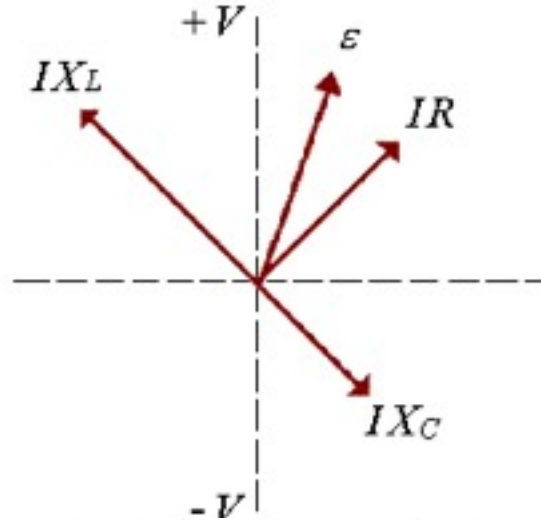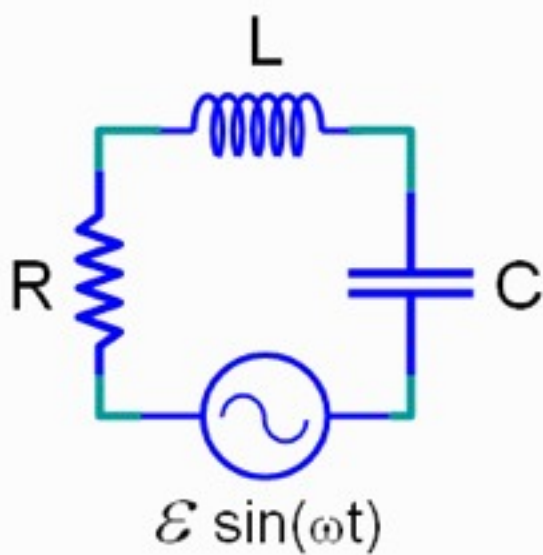A driven RLC circuit is represented by the phasor diagram below.



12) When the voltage across the capacitor is at its positive maximum, $V_C = +V_{Cmax}$, what is the voltage across the inductor?

A ☐ $V_L = 0$

B ☐ $V_L = V_{Lmax}$

C ☒ $V_L = -V_{Lmax}$

1

What does the voltage phasor diagram look like when the voltage across capacitor is at its positive maximum?

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

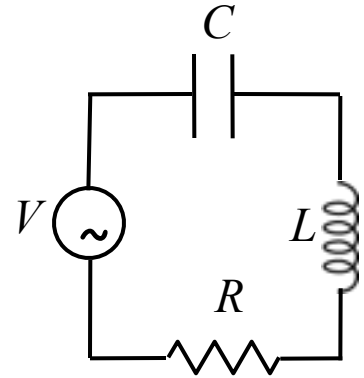What is X_L , the reactance of the inductor, at this frequency?



Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

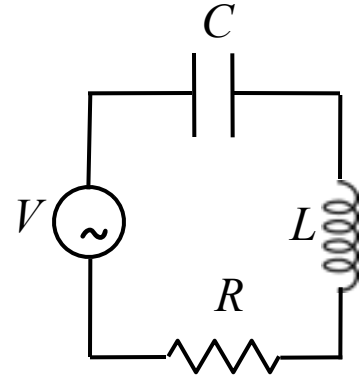What is X_L , the reactance of the inductor, at this frequency?



Conceptual Analysis

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

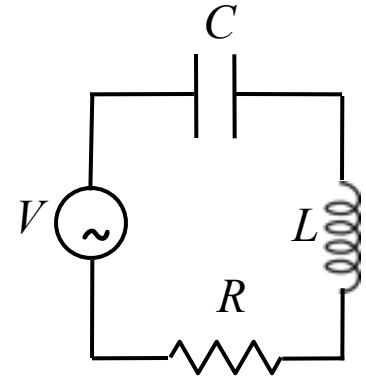What is X_L , the reactance of the inductor, at this frequency?



Conceptual Analysis

The maximum voltage for each component is related to its reactance and to the maximum current.

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

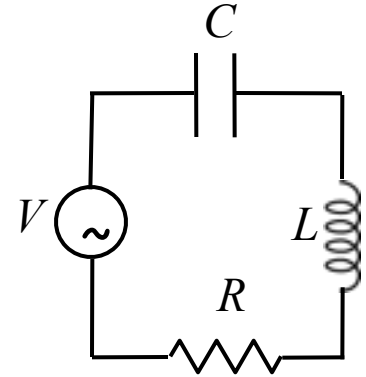What is X_L , the reactance of the inductor, at this frequency?



Conceptual Analysis

The maximum voltage for each component is related to its reactance and to the maximum current.

The impedance triangle determines the relationship between the maximum voltages for the components

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

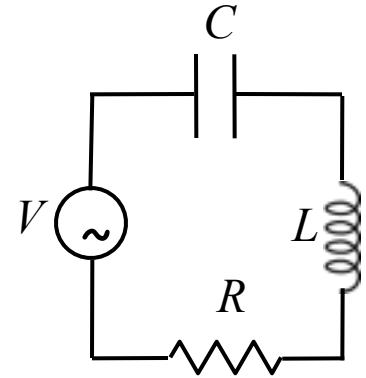What is X_L , the reactance of the inductor, at this frequency?



Conceptual Analysis

The maximum voltage for each component is related to its reactance and to the maximum current.

The impedance triangle determines the relationship between the maximum voltages for the components

Strategic Analysis

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

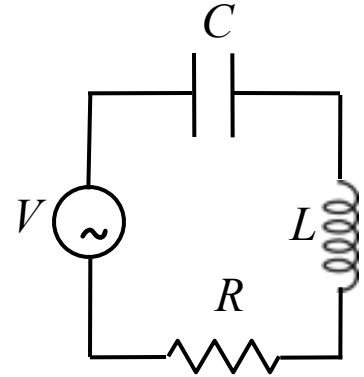What is X_L , the reactance of the inductor, at this frequency?



Conceptual Analysis

The maximum voltage for each component is related to its reactance and to the maximum current.

The impedance triangle determines the relationship between the maximum voltages for the components

Strategic Analysis

Use V_{max} and I_{max} to determine Z

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

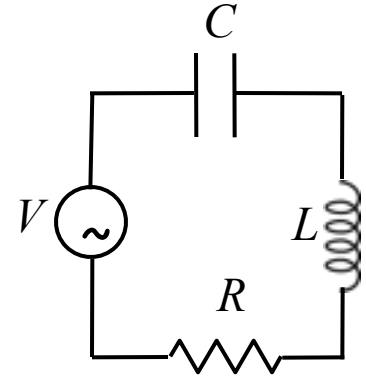What is X_L , the reactance of the inductor, at this frequency?



Conceptual Analysis

The maximum voltage for each component is related to its reactance and to the maximum current.

The impedance triangle determines the relationship between the maximum voltages for the components

Strategic Analysis

Use V_{max} and I_{max} to determine Z

Use impedance triangle to determine R

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

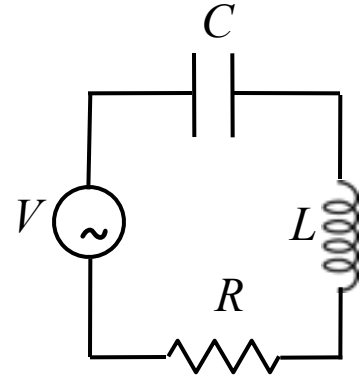What is X_L , the reactance of the inductor, at this frequency?



Conceptual Analysis

The maximum voltage for each component is related to its reactance and to the maximum current.

The impedance triangle determines the relationship between the maximum voltages for the components

Strategic Analysis

Use V_{max} and I_{max} to determine Z

Use impedance triangle to determine R

Use V_{Cmax} and impedance triangle to determine X_L

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$


The current leads generator voltage by 45°

L and R are unknown.

What is X_L , the reactance of the inductor, at this frequency?

Compare X_L and X_C at this frequency:

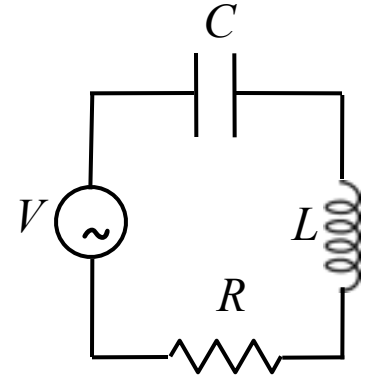- A) $X_L < X_C$ B) $X_L = X_C$ C) $X_L > X_C$ D) Not enough information



Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°


L and R are unknown.

What is X_L , the reactance of the inductor, at this frequency?

Compare X_L and X_C at this frequency:

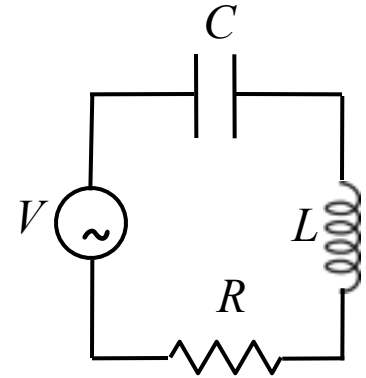- A) $X_L < X_C$ B) $X_L = X_C$ C) $X_L > X_C$ D) Not enough information

This information is determined from the phase



Calculation



Consider the harmonically driven series LCR circuit shown.


$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

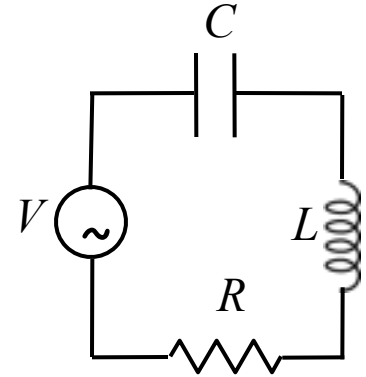

What is X_L , the reactance of the inductor, at this frequency?

Compare X_L and X_C at this frequency:

- A) $X_L < X_C$ B) $X_L = X_C$ C) $X_L > X_C$ D) Not enough information

This information is determined from the phase
Current leads voltage

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°



L and R are unknown.

What is X_L , the reactance of the inductor, at this frequency?

Compare X_L and X_C at this frequency:

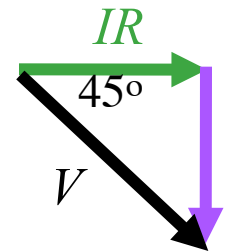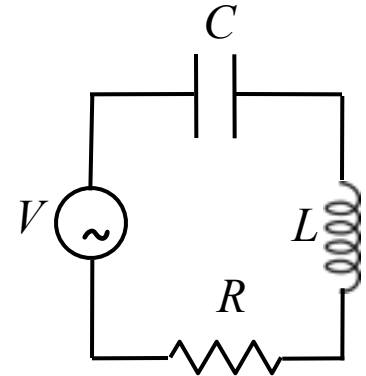- A) $X_L < X_C$ B) $X_L = X_C$ C) $X_L > X_C$ D) Not enough information

This information is determined from the phase
Current leads voltage



Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.




What is X_L , the reactance of the inductor, at this frequency?

Compare X_L and X_C at this frequency:

- A) $X_L < X_C$ B) $X_L = X_C$ C) $X_L > X_C$ D) Not enough information

This information is determined from the phase

Current leads voltage

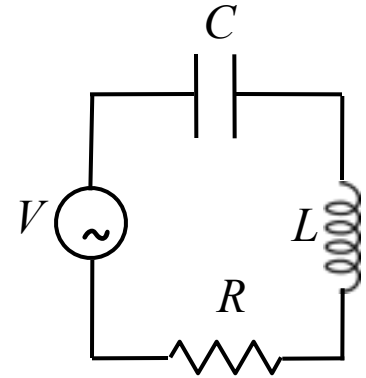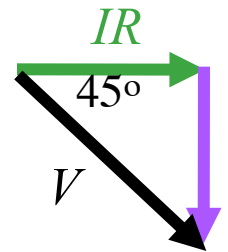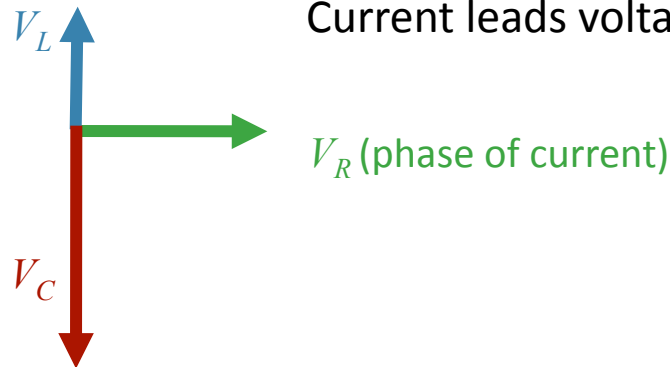

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.




What is X_L , the reactance of the inductor, at this frequency?

Compare X_L and X_C at this frequency:

- A) $X_L < X_C$ B) $X_L = X_C$ C) $X_L > X_C$ D) Not enough information

This information is determined from the phase

Current leads voltage

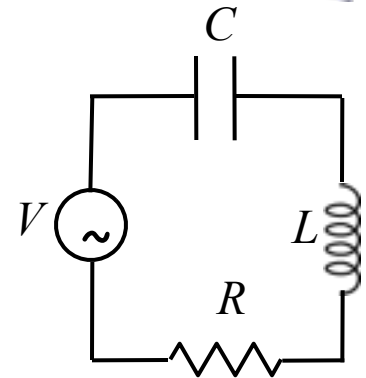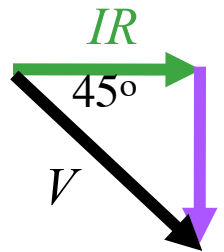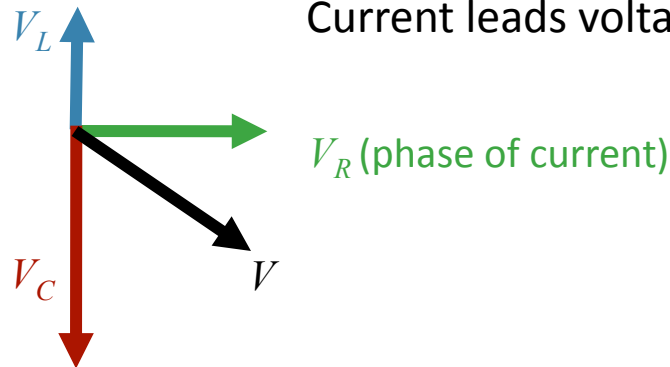

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.




What is X_L , the reactance of the inductor, at this frequency?

Compare X_L and X_C at this frequency:

- A) $X_L < X_C$ B) $X_L = X_C$ C) $X_L > X_C$ D) Not enough information

This information is determined from the phase

Current leads voltage

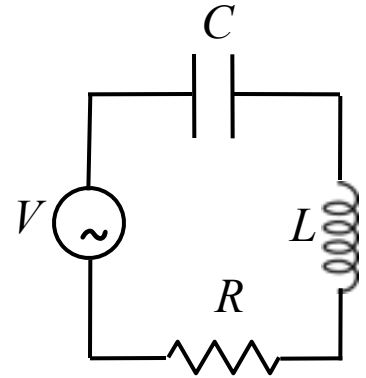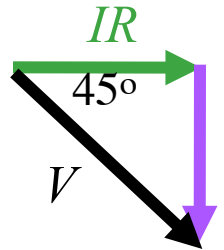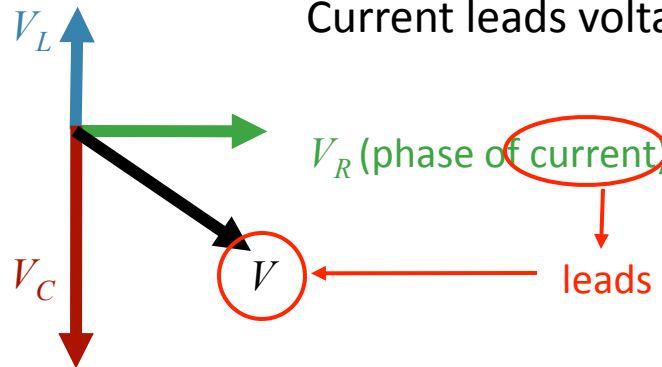

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{\max} = 100 \text{ V}$$

$$I_{\max} = 2 \text{ mA}$$

$$V_{C\max} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.


What is X_L , the reactance of the inductor, at this frequency?

Compare X_L and X_C at this frequency:

- A) $X_L < X_C$ B) $X_L = X_C$ C) $X_L > X_C$ D) Not enough information



This information is determined from the phase

Current leads voltage

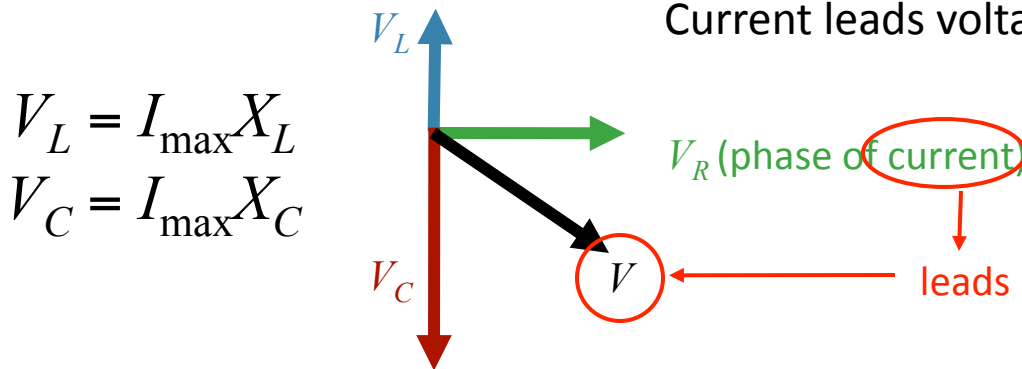

$$V_L = I_{\max} X_L$$

$$V_C = I_{\max} X_C$$

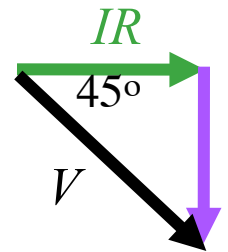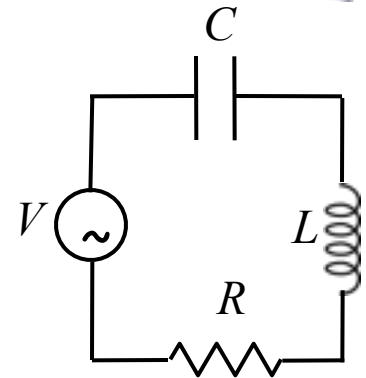

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{\max} = 100 \text{ V}$$

$$I_{\max} = 2 \text{ mA}$$

$$V_{C\max} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

What is X_L , the reactance of the inductor, at this frequency?


Compare X_L and X_C at this frequency:

A) $X_L < X_C$

B) $X_L = X_C$

C) $X_L > X_C$

D) Not enough information


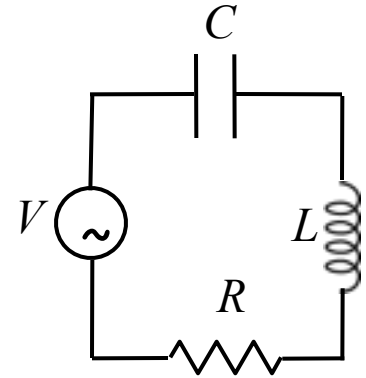


This information is determined from the phase

Current leads voltage

$$V_L = I_{\max} X_L$$

$$V_C = I_{\max} X_C$$

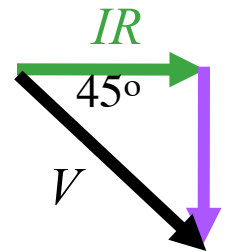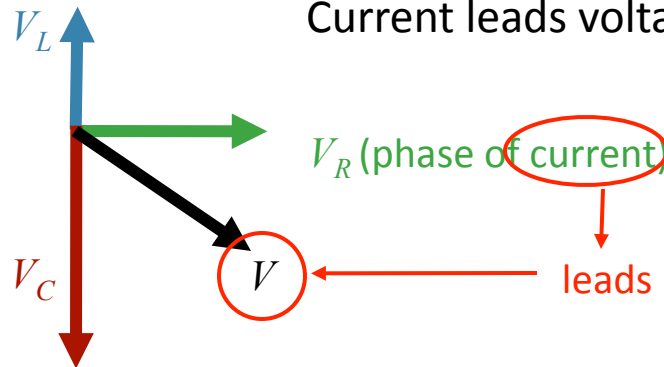

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$


$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

What is X_L , the reactance of the inductor, at this frequency?

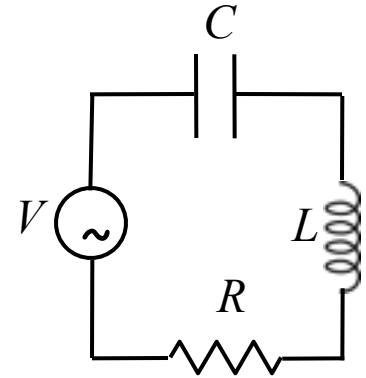What is Z , the total impedance of the circuit?



- A) 70.7 k Ω B) 50 k Ω C) 35.4 k Ω D) 21.1 k Ω

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{\max} = 100 \text{ V}$$

$$I_{\max} = 2 \text{ mA}$$


$$V_{C\max} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

What is X_L , the reactance of the inductor, at this frequency?

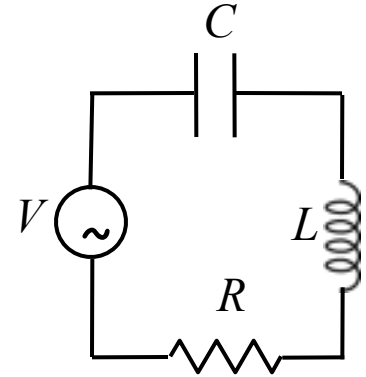What is Z , the total impedance of the circuit?



- A) 70.7 k Ω B) 50 k Ω C) 35.4 k Ω D) 21.1 k Ω

$$Z = \frac{V_{\max}}{I_{\max}} = \frac{100V}{2mA} = 50k\Omega$$

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{\max} = 100 \text{ V}$$

$$I_{\max} = 2 \text{ mA}$$


$$V_{C\max} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

What is X_L , the reactance of the inductor, at this frequency?

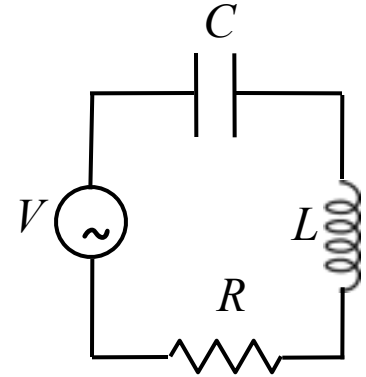What is Z , the total impedance of the circuit?



A) 70.7 k Ω

B) 50 k Ω

C) 35.4 k Ω

D) 21.1 k Ω

$$Z = \frac{V_{\max}}{I_{\max}} = \frac{100V}{2mA} = 50k\Omega$$

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$


The current leads generator voltage by 45°

L and R are unknown.

What is X_L , the reactance of the inductor, at this frequency?

What is R ?

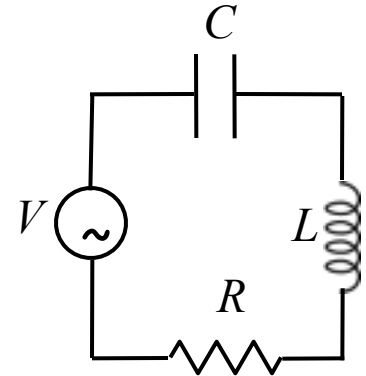- A) $70.7 \text{ k}\Omega$ B) $50 \text{ k}\Omega$ C) $35.4 \text{ k}\Omega$ D) $21.1 \text{ k}\Omega$



$$Z = 50 \text{ k}\Omega$$

$$\sin(45^\circ) = 0.707$$

$$\cos(45^\circ) = 0.707$$

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°



L and R are unknown.

What is X_L , the reactance of the inductor, at this frequency?

What is R ?

- A) 70.7 k Ω B) 50 k Ω C) 35.4 k Ω D) 21.1 k Ω

Determined from impedance triangle

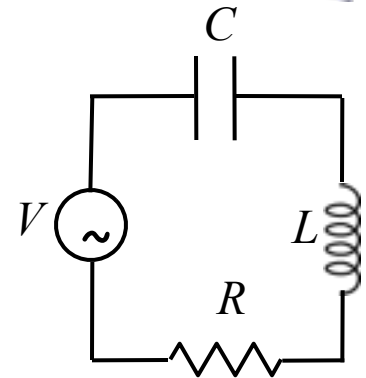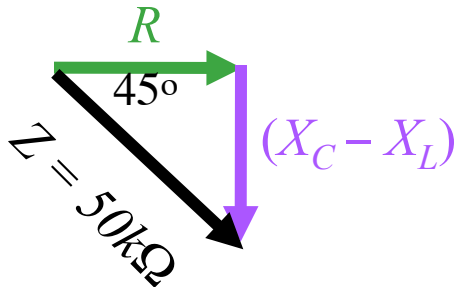

$$Z = 50 \text{ k}\Omega$$

$$\sin(45^\circ) = 0.707$$

$$\cos(45^\circ) = 0.707$$

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°


L and *R* are unknown.

What is X_L , the reactance of the inductor, at this frequency?


What is *R*?

- A) 70.7 k Ω B) 50 k Ω C) 35.4 k Ω D) 21.1 k Ω

Determined from impedance triangle

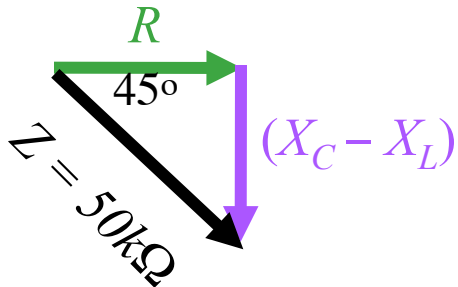

$$\cos(45) = \frac{R}{Z}$$

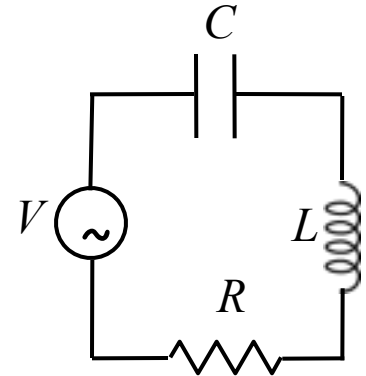

$$Z = 50 \text{ k}\Omega$$

$$\sin(45^\circ) = 0.707$$

$$\cos(45^\circ) = 0.707$$

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°


L and R are unknown.

What is X_L , the reactance of the inductor, at this frequency?


What is R ?

- A) 70.7 k Ω B) 50 k Ω C) 35.4 k Ω D) 21.1 k Ω

Determined from impedance triangle

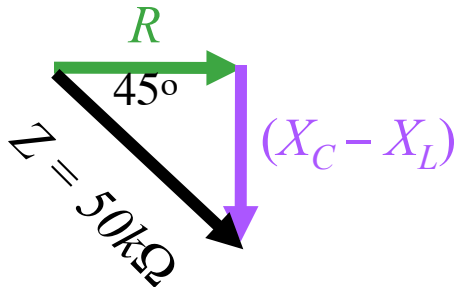
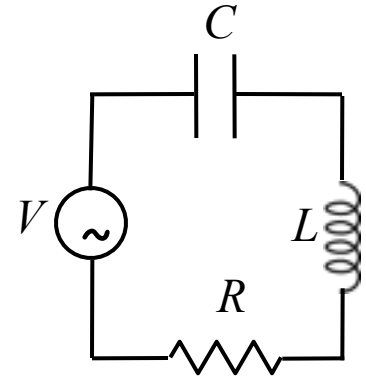
$$\cos(45) = \frac{R}{Z} \quad \longrightarrow \quad R = Z \cos(45^\circ)$$



$$Z = 50 \text{ k}\Omega$$

$$\sin(45^\circ) = 0.707$$

$$\cos(45^\circ) = 0.707$$

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$


The current leads generator voltage by 45°

L and *R* are unknown.

What is X_L , the reactance of the inductor, at this frequency?

What is *R*?

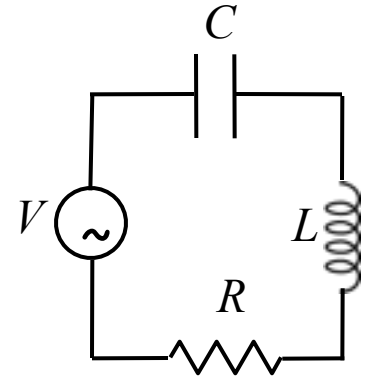- A) 70.7 k Ω B) 50 k Ω C) 35.4 k Ω D) 21.1 k Ω




$$Z = 50 \text{ k}\Omega$$

$$\sin(45^\circ) = 0.707$$

$$\cos(45^\circ) = 0.707$$

Determined from impedance triangle

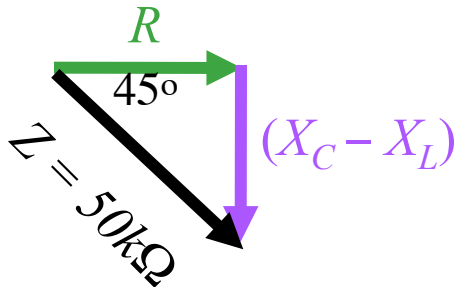

$$\begin{aligned} \cos(45) &= \frac{R}{Z} \quad \longrightarrow \quad R = Z \cos(45^\circ) \\ &= 50 \text{ k}\Omega \times 0.707 \\ &= 35.4 \text{ k}\Omega \end{aligned}$$

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

What is X_L , the reactance of the inductor, at this frequency?


What is R ?

A) 70.7 k Ω

B) 50 k Ω

C) 35.4 k Ω

D) 21.1 k Ω

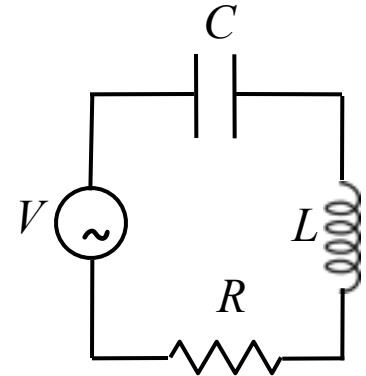


$$Z = 50 \text{ k}\Omega$$

$$\sin(45^\circ) = 0.707$$

$$\cos(45^\circ) = 0.707$$

Determined from impedance triangle

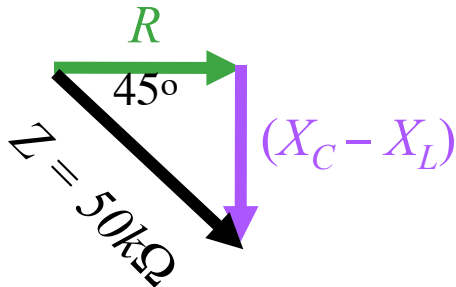

$$\begin{aligned} \cos(45) &= \frac{R}{Z} \quad \longrightarrow \quad R = Z \cos(45^\circ) \\ &= 50 \text{ k}\Omega \times 0.707 \\ &= 35.4 \text{ k}\Omega \end{aligned}$$

Calculation

Consider the harmonically driven series LCR circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

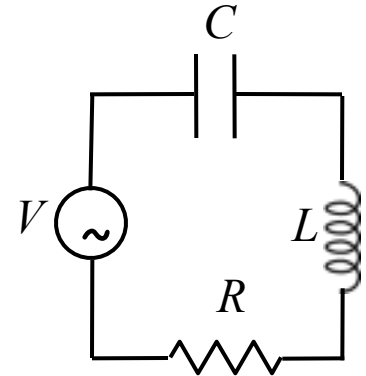What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$R = 35.4 \text{ k}\Omega$$

A) $70.7 \text{ k}\Omega$

B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

D) $21.1 \text{ k}\Omega$

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

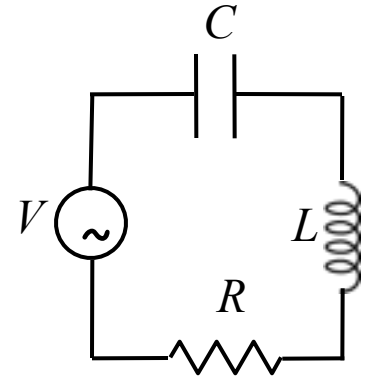What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$R = 35.4 \text{ k}\Omega$$


A) $70.7 \text{ k}\Omega$

B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

D) $21.1 \text{ k}\Omega$

We start with the
impedance triangle:

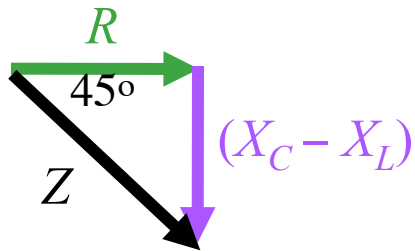

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

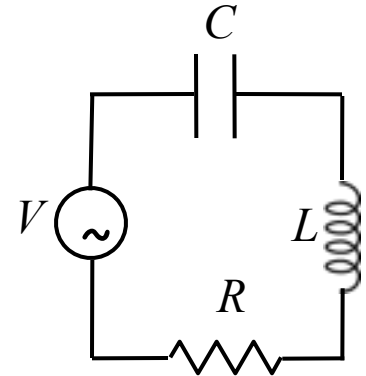What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$R = 35.4 \text{ k}\Omega$$

A) $70.7 \text{ k}\Omega$


B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

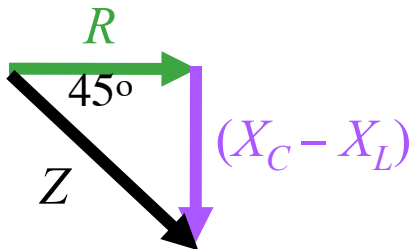D) $21.1 \text{ k}\Omega$

We start with the impedance triangle:

$$\frac{X_C - X_L}{R} = \tan 45^\circ = 1$$



Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

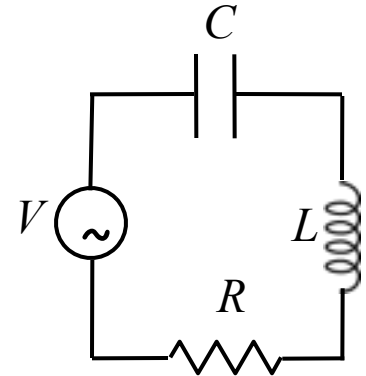What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$R = 35.4 \text{ k}\Omega$$

A) $70.7 \text{ k}\Omega$


B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

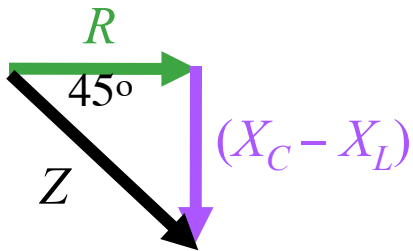D) $21.1 \text{ k}\Omega$

We start with the impedance triangle:

$$\frac{X_C - X_L}{R} = \tan 45^\circ = 1 \quad \longrightarrow \quad X_L = X_C - R$$



Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

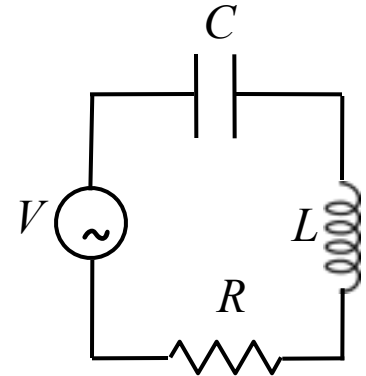What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$R = 35.4 \text{ k}\Omega$$

A) $70.7 \text{ k}\Omega$

B) $50 \text{ k}\Omega$


C) $35.4 \text{ k}\Omega$

D) $21.1 \text{ k}\Omega$

We start with the impedance triangle:

$$\frac{X_C - X_L}{R} = \tan 45^\circ = 1 \quad \longrightarrow \quad X_L = X_C - R$$

What is X_C ?

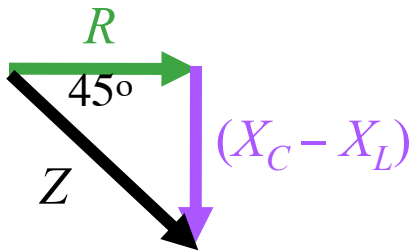

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

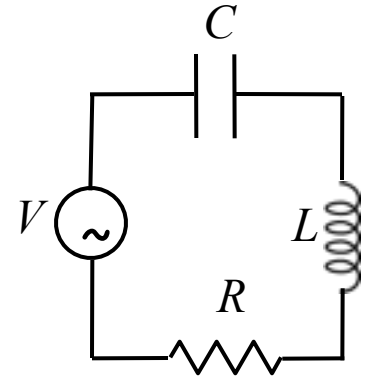What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$R = 35.4 \text{ k}\Omega$$


A) $70.7 \text{ k}\Omega$

B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

D) $21.1 \text{ k}\Omega$

We start with the impedance triangle:

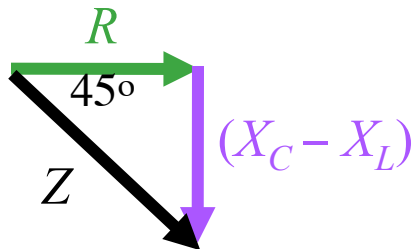

$$\frac{X_C - X_L}{R} = \tan 45^\circ = 1 \quad \longrightarrow \quad X_L = X_C - R$$

What is X_C ?

$$V_{Cmax} = I_{max} X_C$$

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

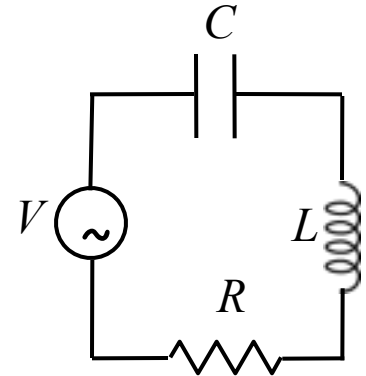What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$R = 35.4 \text{ k}\Omega$$


A) $70.7 \text{ k}\Omega$

B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

D) $21.1 \text{ k}\Omega$

We start with the impedance triangle:

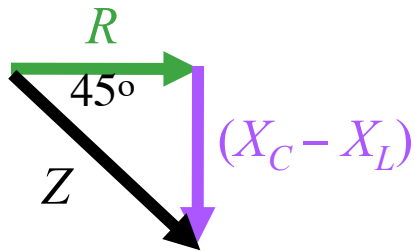

$$\frac{X_C - X_L}{R} = \tan 45^\circ = 1 \quad \rightarrow \quad X_L = X_C - R$$

What is X_C ?

$$V_{Cmax} = I_{max} X_C$$

$$X_C = \frac{113}{2} = 56.5 \text{ k}\Omega$$

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

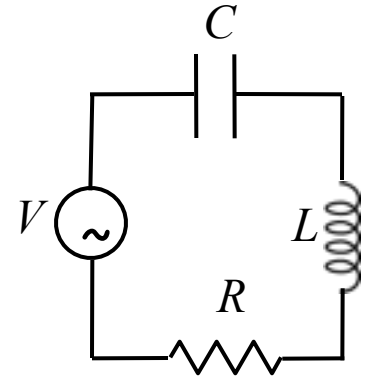What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$R = 35.4 \text{ k}\Omega$$


A) $70.7 \text{ k}\Omega$

B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

D) $21.1 \text{ k}\Omega$

We start with the impedance triangle:

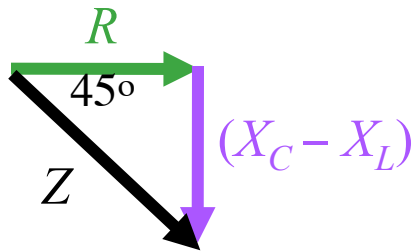

$$\frac{X_C - X_L}{R} = \tan 45^\circ = 1 \quad \rightarrow \quad X_L = X_C - R$$

What is X_C ?

$$V_{Cmax} = I_{max} X_C$$

$$X_C = \frac{113}{2} = 56.5 \text{ k}\Omega$$

$$X_L = 56.5 \text{ k}\Omega - 35.4 \text{ k}\Omega$$

Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and R are unknown.

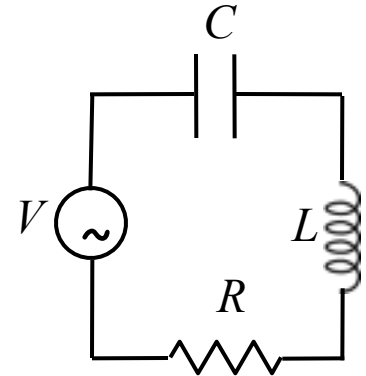What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$R = 35.4 \text{ k}\Omega$$


A) $70.7 \text{ k}\Omega$

B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

D) $21.1 \text{ k}\Omega$

We start with the impedance triangle:

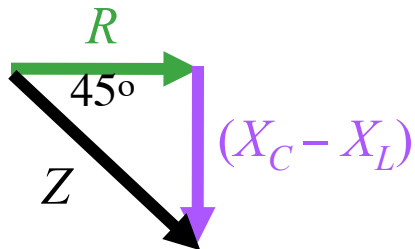

$$\frac{X_C - X_L}{R} = \tan 45^\circ = 1 \quad \rightarrow \quad X_L = X_C - R$$

What is X_C ?

$$V_{Cmax} = I_{max} X_C$$

$$X_C = \frac{113}{2} = 56.5 \text{ k}\Omega$$

$$X_L = 56.5 \text{ k}\Omega - 35.4 \text{ k}\Omega$$