
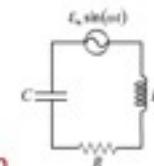


# Electricity & Magnetism

## Lecture 21

Voltage Phasor Diagram

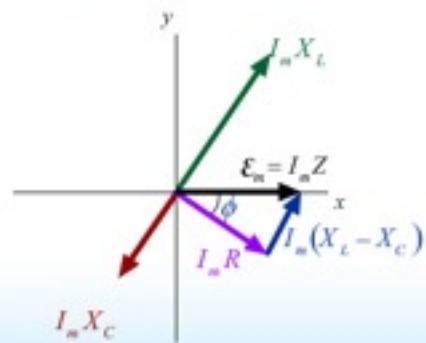

Phase Relation

$$\tan \phi = \frac{X_L - X_C}{R}$$

Impedance

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


Maximum Current

$$I_m = \frac{\mathcal{E}_m}{Z}$$


PHASORS ARE THE KEY !  
FORMULAS ARE NOT !

START WITH PHASOR DIAGRAM



DEVELOP FORMULAS FROM THE  
DIAGRAM !!

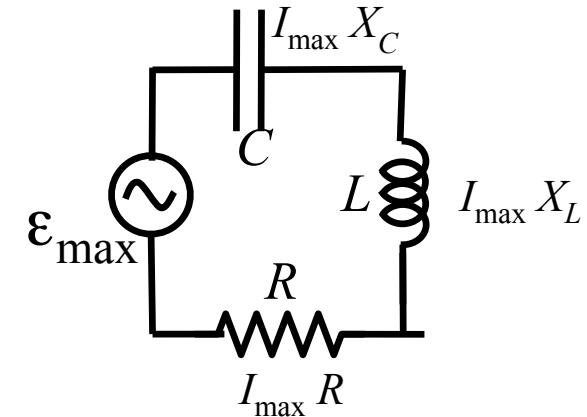

$V$  = Projection along Vertical

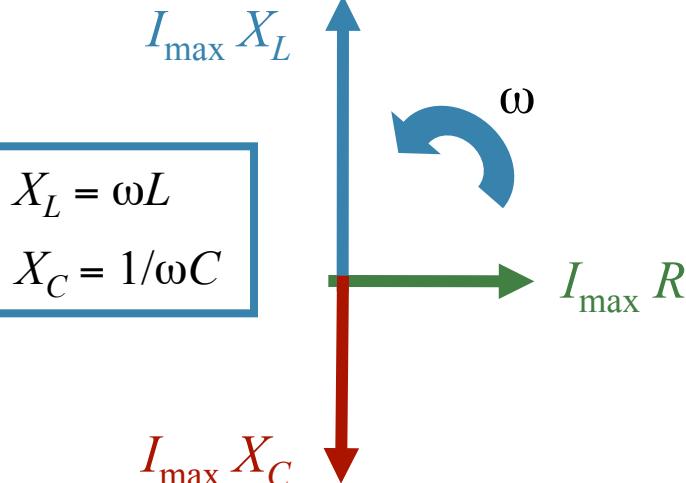

$$\epsilon_{\max} = I_{\max} Z$$

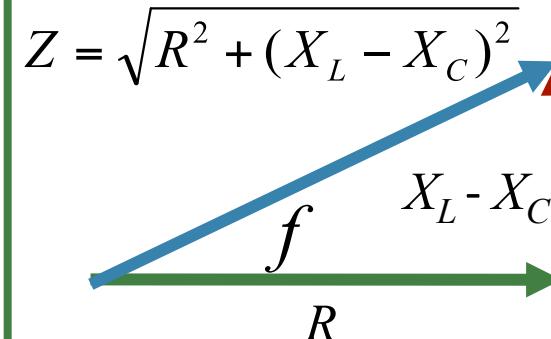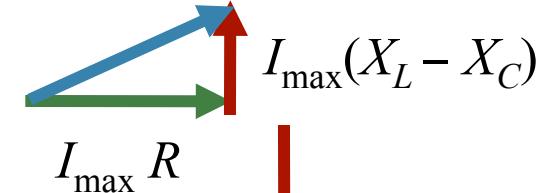

# Peak AC Problems

“Ohms” Law for each element

NOTE: Good for PEAK values only)

$$V_{gen} = I_{\max} Z$$

$$V_{Resistor} = I_{\max} R$$


$$V_{inductor} = I_{\max} X_L$$

$$V_{Capacitor} = I_{\max} X_C$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

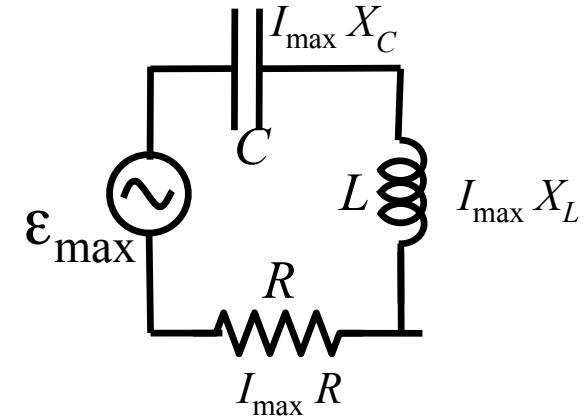

## Typical Problem


A generator with peak voltage 15 volts and angular frequency 25 rad/sec is connected in series with an 8 Henry inductor, a 0.4 mF capacitor and a 50 ohm resistor. What is the peak current through the circuit?

$$X_L = \omega L = 200 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 122 \Omega$$

$$X_C = \frac{1}{\omega C} = 100 \Omega$$
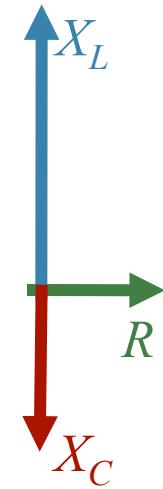
$$I_{\max} = \frac{V_{gen}}{Z} = 0.13 A$$



# Peak AC Problems

“Ohms” Law for each element

NOTE: Good for PEAK values only)

$$V_{gen} = I_{max} Z$$

$$V_{Resistor} = I_{max} R$$


$$V_{inductor} = I_{max} X_L$$

$$V_{Capacitor} = I_{max} X_C$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

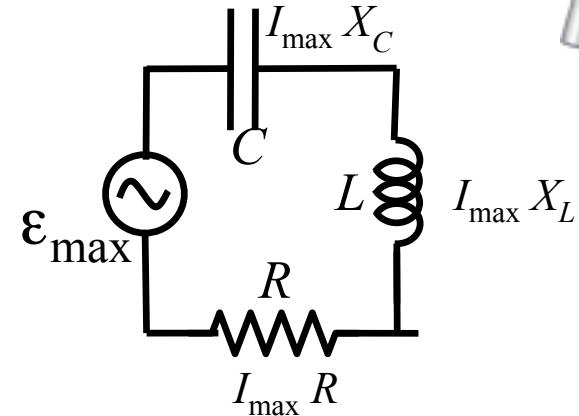

## Typical Problem

A generator with peak voltage 15 volts and angular frequency 25 rad/sec is connected in series with an 8 Henry inductor, a 0.4 mF capacitor and a 50 ohm resistor. What is the peak current through the circuit?

Which element has the largest peak voltage across it?

- A) Generator
- B) Inductor**
- C) Resistor
- D) Capacitor

- E) All the same.

$$V_{max} = I_{max} X$$

$$X_L = \omega L = 200 \Omega$$

$$X_C = \frac{1}{\omega C} = 100 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 122 \Omega$$

$$I_{max} = \frac{V_{gen}}{Z} = 0.13A$$

# Peak AC Problems

“Ohms” Law for each element

NOTE: Good for PEAK values only

$$V_{gen} = I_{\max} Z$$

$$V_{Resistor} = I_{\max} R$$


$$V_{inductor} = I_{\max} X_L$$

$$V_{Capacitor} = I_{\max} X_C$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

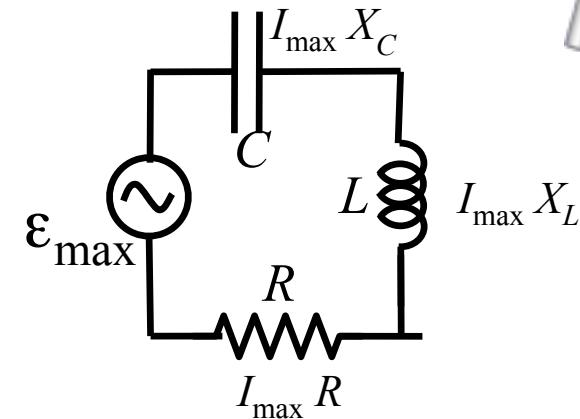


## Typical Problem

A generator with peak voltage 15 volts and angular frequency 25 rad/sec is connected in series with an 8 Henry inductor, a 0.4 mF capacitor and a 50 ohm resistor. What is the peak current through the circuit?



What happens to the impedance if we decrease the angular frequency to 20 rad/sec?

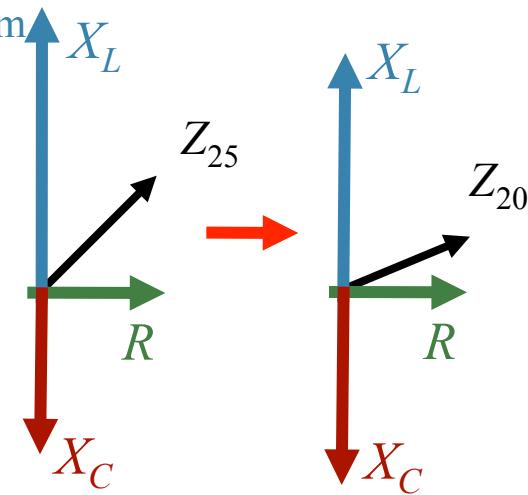- A)  $Z$  increases
- B)  $Z$  remains the same
- C)  $Z$  decreases**

$$(X_L - X_C) : (200 - 100) \rightarrow (160 - 125)$$



# Resonance

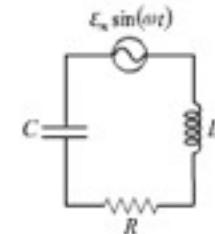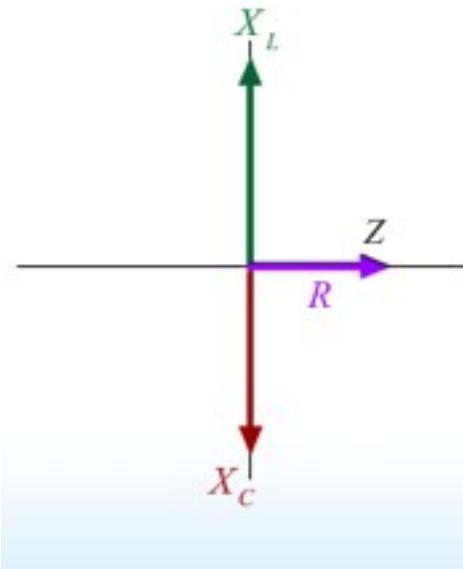

## Resonance

$$I_m \text{ is a maximum} \longrightarrow I_m = \frac{E_m}{R}$$

$$\omega = \omega_o$$

$$Z \text{ minimized} \longrightarrow X_L = X_C$$

$$\phi = 0^\circ$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

## Light-bulb Demo

# Resonance in AC circuits

$\omega_0$ : Frequency at which voltage across inductor and capacitor cancel

$R$  is independent of  $\omega$

$X_L$  increases with  $\omega$

$$X_L = \omega L$$


$X_C$  increases with  $1/\omega$

$$X_C = \frac{1}{\omega C}$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

is minimum at resonance

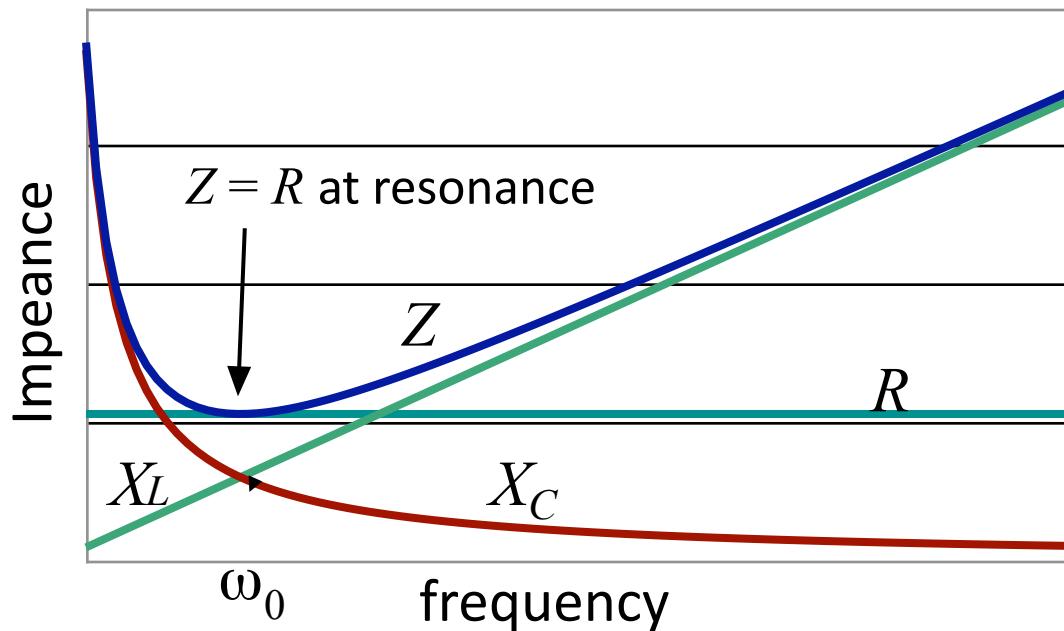Resonance:  $X_L = X_C$     $\omega_0 = \frac{1}{\sqrt{LC}}$




# Off Resonance

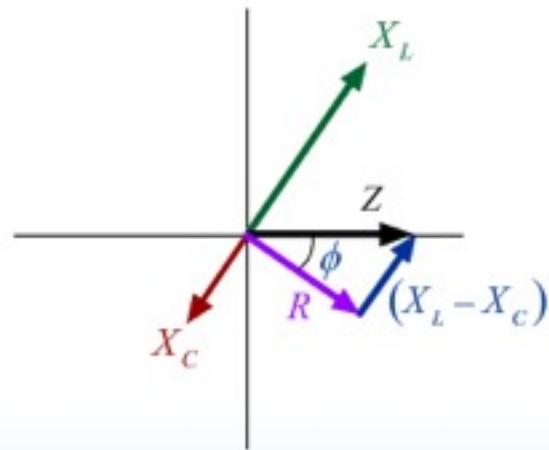

$$I_m = \frac{\mathcal{E}_m}{Z}$$

$$I_m = \frac{\mathcal{E}_m}{R} \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

**Z**

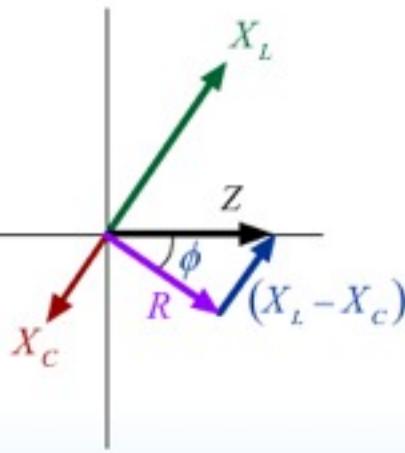

$$x \equiv \frac{\omega}{\omega_o}$$

$$Q^2 \equiv \frac{L}{R^2 C}$$


$$Q \equiv 2\pi \frac{U_{\max}}{\Delta U}$$

$$I_m = \frac{\mathcal{E}_m}{R} \frac{1}{\sqrt{1 + Q^2 \frac{(x^2 - 1)^2}{x^2}}}$$

$U_{\max}$  = max energy stored



$\Delta U$  = energy dissipated  
in one cycle at resonance

# Off Resonance

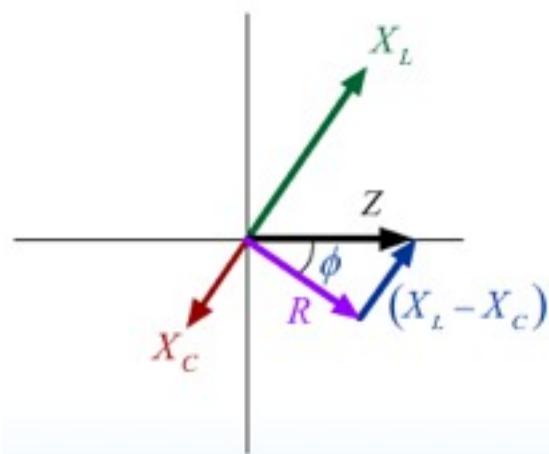


$$x \equiv \frac{\omega}{\omega_o} \quad Q^2 \equiv \frac{L}{R^2 C}$$
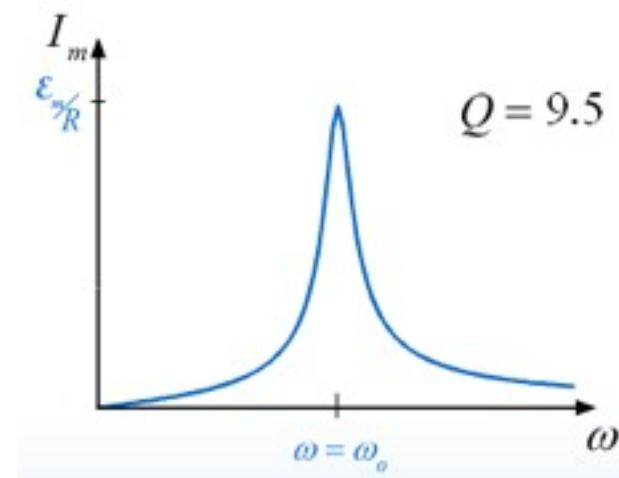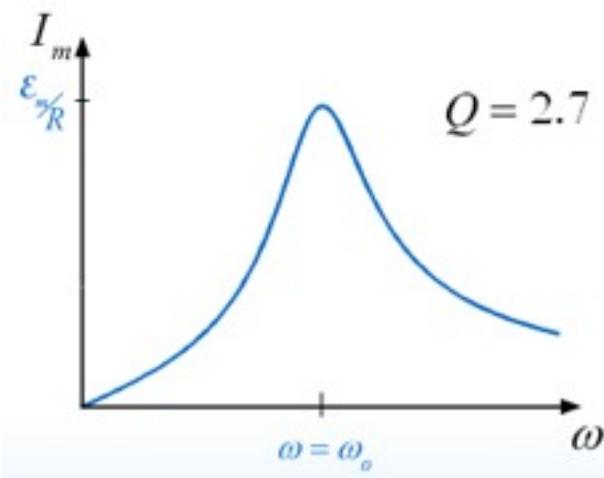
$$I_m = \frac{\mathcal{E}_m}{R} \frac{1}{\sqrt{1 + Q^2 \left( \frac{x^2 - 1}{x^2} \right)^2}}$$




# CheckPoint 2

Circuit I

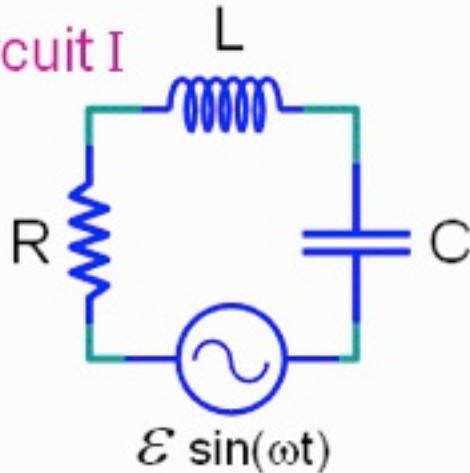

Circuit II

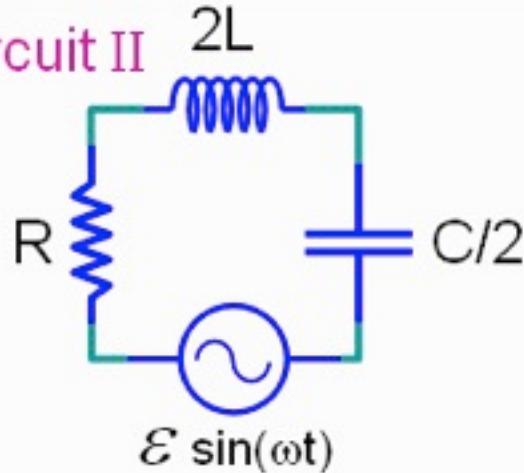

Consider two RLC circuits with identical generators and resistors. Both circuits are driven at the resonant frequency. Circuit II has twice the inductance and 1/2 the capacitance of circuit I as shown above.


Compare the peak voltage across the resistor in the two circuits

- $V_I > V_{II}$
- $V_I = V_{II}$
- $V_I < V_{II}$



$$\text{Resonance: } X_L = X_C$$

$$Z = R$$

Same since  $R$  doesn't change

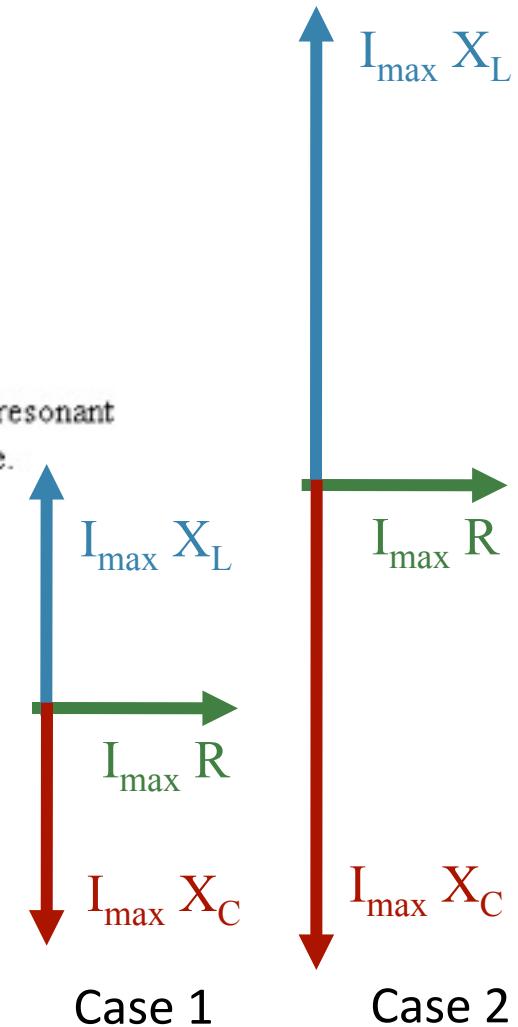

# CheckPoint 4

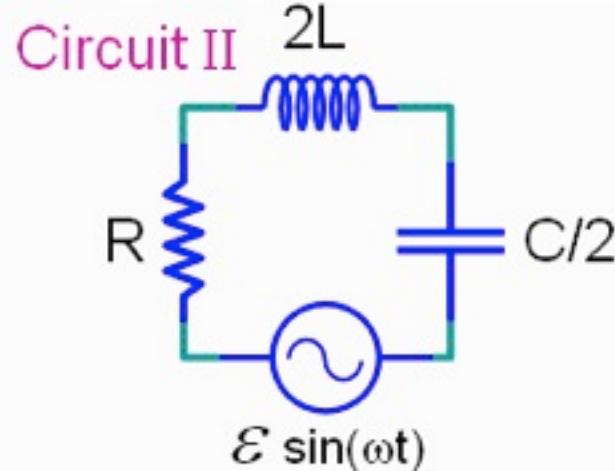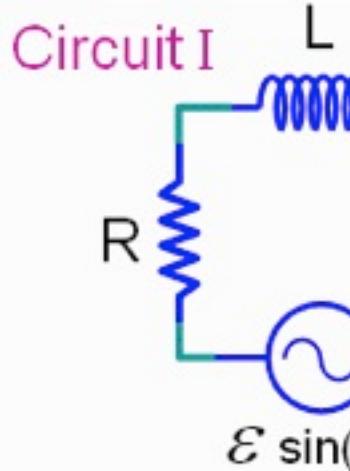


Consider two RLC circuits with identical generators and resistors. Both circuits are driven at the resonant frequency. Circuit II has twice the inductance and 1/2 the capacitance of circuit I as shown above.



Compare the peak voltage across the inductor in the two circuits

- $V_I > V_{II}$
- $V_I = V_{II}$
- $V_I < V_{II}$

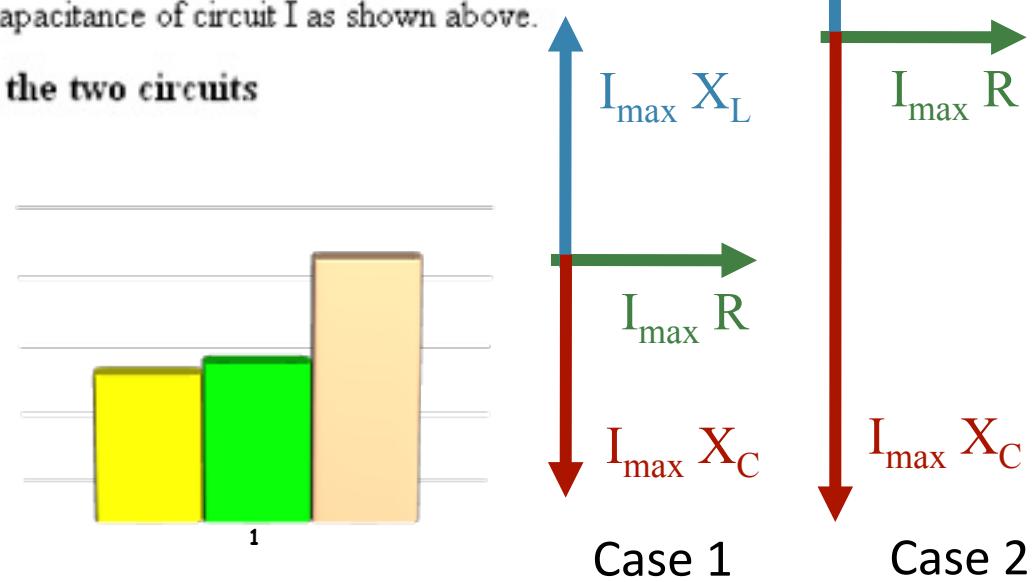Voltage in second circuit will be twice that of the first because of the  $2L$  compared to  $L$ .



# CheckPoint 6

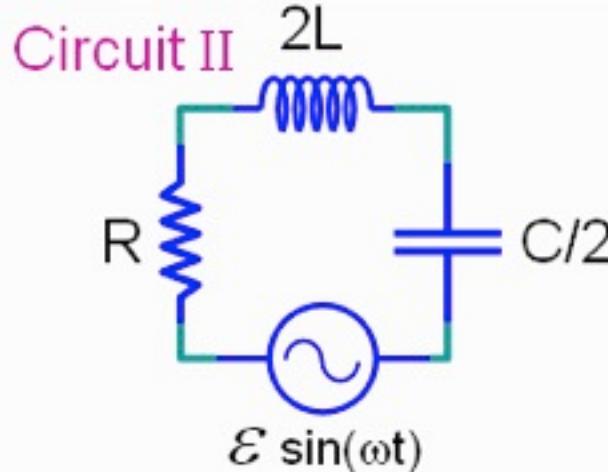
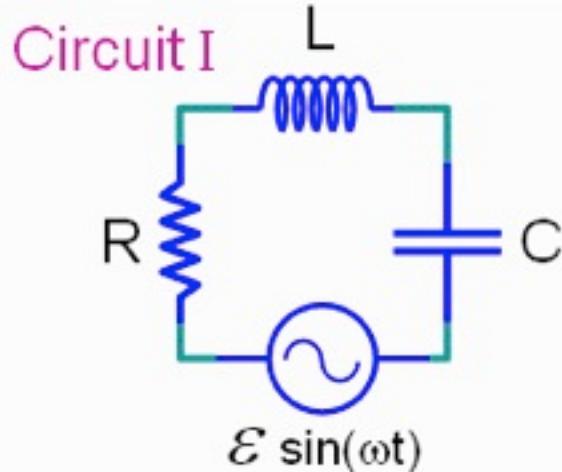


Consider two RLC circuits with identical generators and resistors. Both circuits are driven at the resonant frequency. Circuit II has twice the inductance and 1/2 the capacitance of circuit I as shown above.



Compare the peak voltage across the capacitor in the two circuits

- $V_I > V_{II}$
- $V_I = V_{II}$
- $V_I < V_{II}$

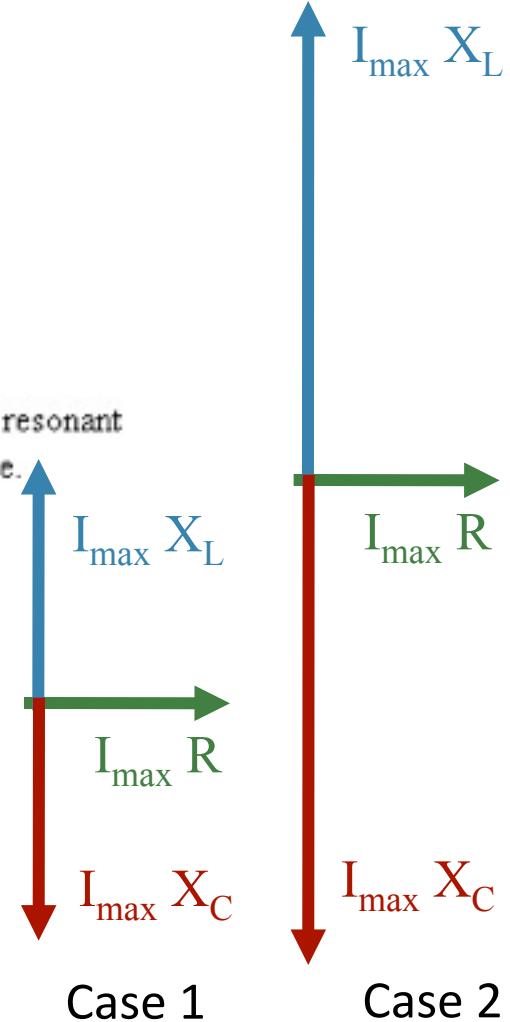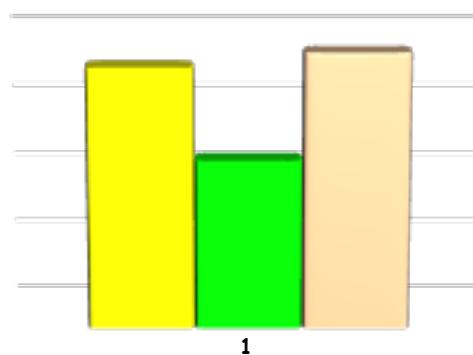The peak voltage will be greater in circuit 2 because the value of  $X_C$  doubles.



# CheckPoint 8

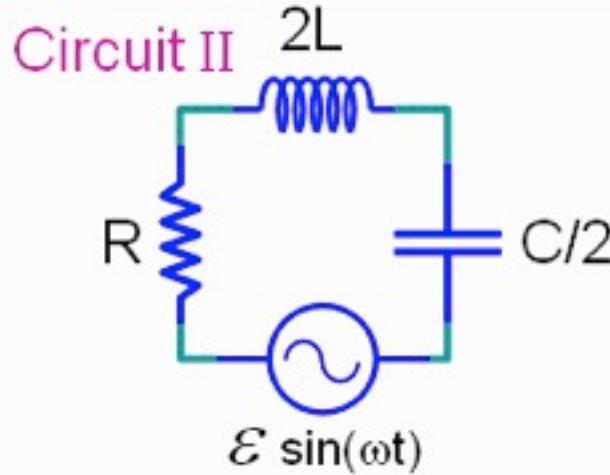
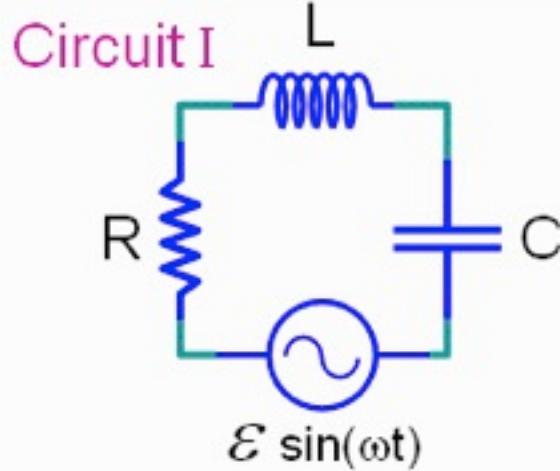


Consider two RLC circuits with identical generators and resistors. Both circuits are driven at the resonant frequency. Circuit II has twice the inductance and 1/2 the capacitance of circuit I as shown above.

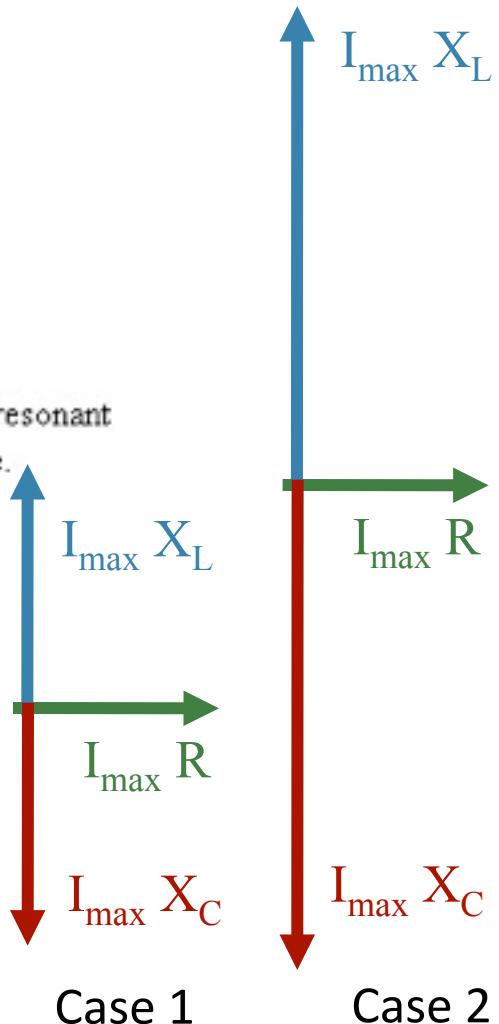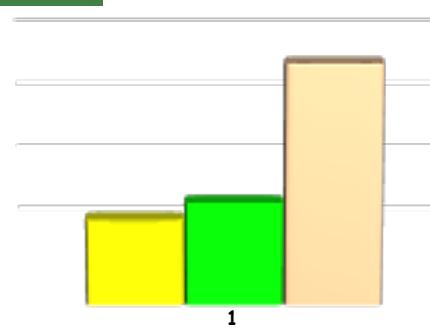**At the resonant frequency, which of the following is true?**

- current leads voltage across the generator
- current lags voltage across the generator
- current is in phase with the voltage across the generator

The voltage across the inductor and the capacitor are equal when at resonant frequency, so there is no lag or lead.



# Power

$$P = IV \text{ instantaneous always true}$$

- Difficult for Generator, Inductor and Capacitor because of phase
- Resistor  $I, V$  are always in phase!



$$\begin{aligned} P &= IV \\ &= I^2 R \end{aligned}$$

## Average Power

$$\text{Inductor and Capacitor} = 0 \quad (\langle \sin \omega t \cos \omega t \rangle = 0)$$

Resistor
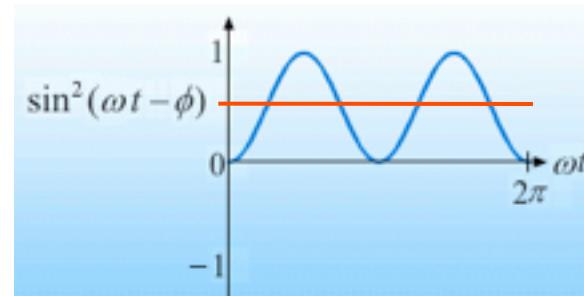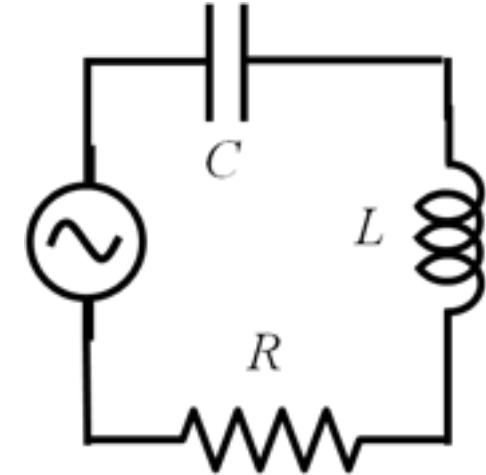
$$\langle I^2 R \rangle = \langle I^2 \rangle R = \frac{1}{2} I_{\text{peak}}^2 R$$



RMS = Root Mean Square

$$I_{\text{peak}} = I_{\text{rms}} \sqrt{2}$$



$$\langle I^2 R \rangle = I_{\text{rms}}^2 R$$

# Power Line Calculation

If you want to deliver 1500 Watts at 100 Volts over transmission lines w/ resistance of 5 Ohms. How much power is lost in the lines?

- Current Delivered:  $I = P/V = 15$  Amps
- Loss =  $IV$  (on line) =  $I^2 R = 15 \times 15 \times 5 = 1125$  Watts!

If you deliver 1,500 Watts at 10,000 Volts over the same transmission lines. How much power is lost?

- Current Delivered:  $I = P/V = .15$  Amps
- Loss =  $IV$  (on line) =  $I^2 R = 0.125$  Watts


DEMO

# Transformers

## Application of Faraday's Law

- › Changing EMF in Primary creates changing flux
- › Changing flux, creates EMF in secondary

$$\frac{V_p}{N_p} = \frac{V_s}{N_s}$$

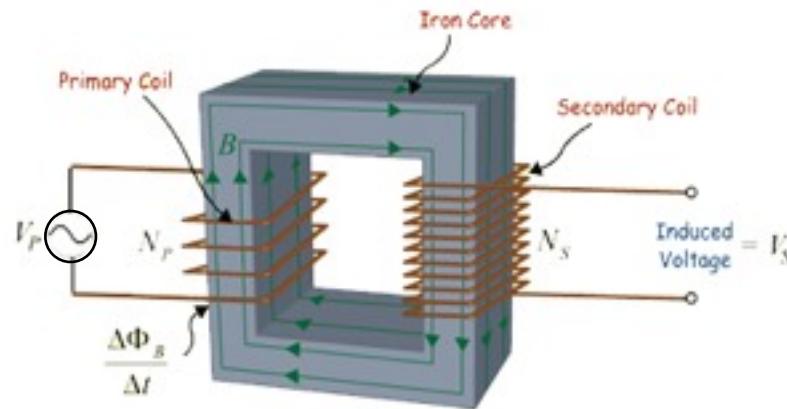

Efficient method to change voltage for AC.

Power Transmission Loss =  $I^2R$

Power electronics

Demo

# Follow-Up from Last Lecture

Consider the harmonically driven series **LCR** circuit shown.


$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V} (= 80 \sqrt{2})$$



The current leads generator voltage by  $45^\circ$  ( $\cos = \sin = 1/\sqrt{2}$ )

**L** and **R** are unknown.

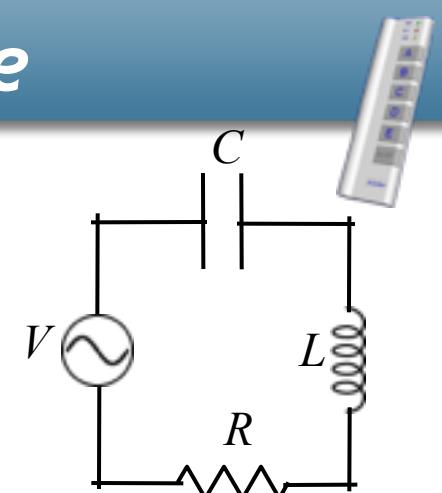

How should we change  $\omega$  to bring circuit to resonance?

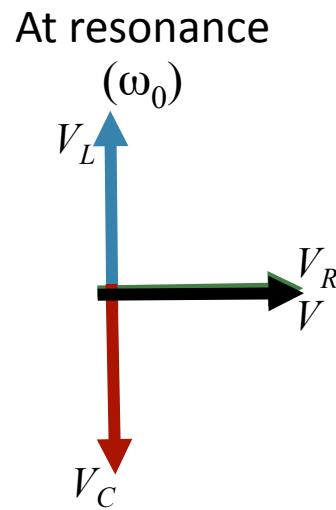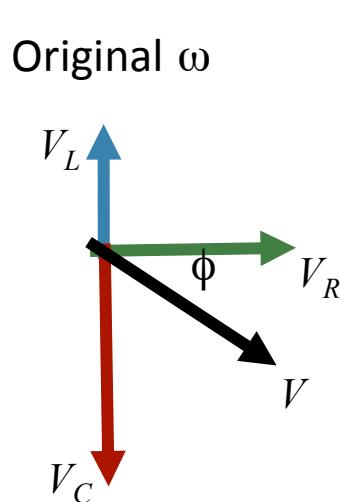- A) decrease  $\omega$
- B) increase  $\omega$**
- C) Not enough info



At resonance  
 $(\omega_0)$

$X_L = X_C$

$X_L$  increases  
 $X_C$  decreases

$\omega$  increases

# More Follow-Up

Consider the harmonically driven series **LCR** circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V} (= 80 \sqrt{2})$$

The current leads generator voltage by  $45^\circ$  ( $\cos = \sin = 1/\sqrt{2}$ )

**L** and **R** are unknown.

By what factor should we increase  $\omega$  to bring circuit to resonance? i.e.

if  $\omega_0 = f\omega$ , what is  $f$ ?

A)  $f = \sqrt{2}$

B)  $f = 2\sqrt{2}$

C)  $f = \sqrt{\frac{8}{3}}$

D)  $f = \sqrt{\frac{8}{5}}$

If  $\omega$  is increased by a factor of  $f$ :

$X_L$  increases by factor of  $f$

$X_C$  decreases by factor of  $f$




$X_L \circledR f \times 15\sqrt{2}$

$X_C \circledR (1/f) \times 40\sqrt{2}$

At resonance

$$X_L = X_C$$
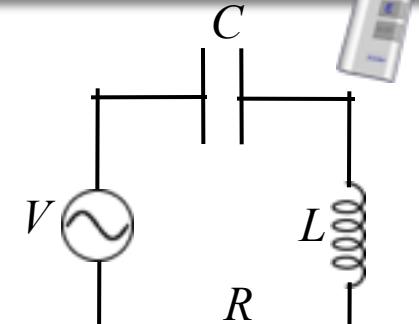
$$\rightarrow 15f = \frac{40}{f} \rightarrow f^2 = \frac{40}{15} \rightarrow f = \sqrt{\frac{8}{3}}$$



$$R = 25\sqrt{2} \text{ k}\Omega$$

$$X_L = 15\sqrt{2} \text{ k}\Omega$$

# Current Follow-Up

Consider the harmonically driven series *LCR* circuit shown.

$$V_{\max} = 100 \text{ V}$$

$$I_{\max} = 2 \text{ mA}$$

$$V_{C\max} = 113 \text{ V} (= 80 \sqrt{2})$$

The current leads generator voltage by  $45^\circ$  ( $\cos = \sin = 1/\sqrt{2}$ )

*L* and *R* are unknown.

What is the maximum current at resonance

A)  $I_{\max}(\omega_0) = \sqrt{2} \text{ mA}$

B)  $I_{\max}(\omega_0) = 2\sqrt{2} \text{ mA}$


C)  $I_{\max}(\omega_0) = \sqrt{\frac{8}{3}} \text{ mA}$

At resonance

$$X_L = X_C$$

$$\rightarrow Z = R$$
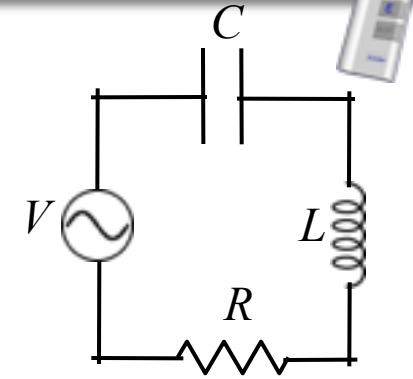
$$\rightarrow I_{\max}(\omega_0) = \frac{V_{\max}}{R} = \frac{100}{25\sqrt{2}} = 2\sqrt{2} \text{ mA}$$



$$R = 25\sqrt{2} \text{ k}\Omega$$

$$X_L = 15\sqrt{2} \text{ k}\Omega$$

$$\omega_0 = \sqrt{\frac{8}{3}}\omega$$

# Phasor Follow-Up

Consider the harmonically driven series  $LCR$  circuit shown.

$$V_{max} = 100 \text{ V}$$






$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V} (= 80\sqrt{2})$$

The current leads generator voltage by  $45^\circ$  ( $\cos = \sin = 1/\sqrt{2}$ )

$L$  and  $R$  are unknown.

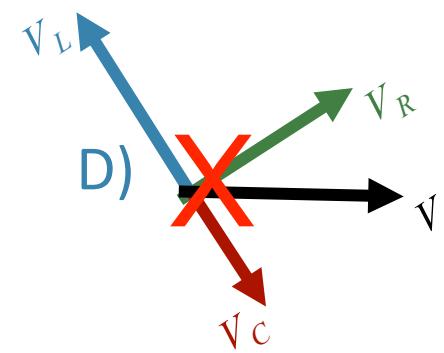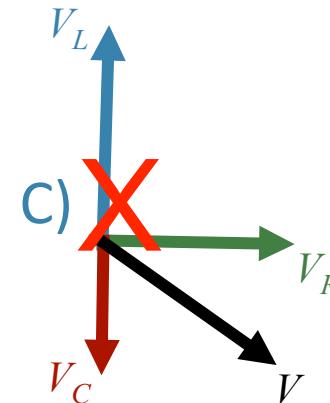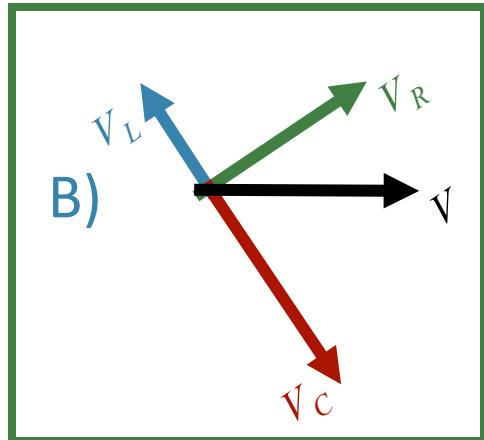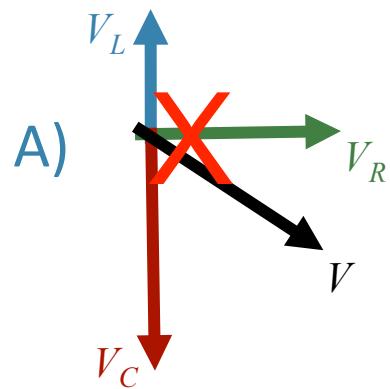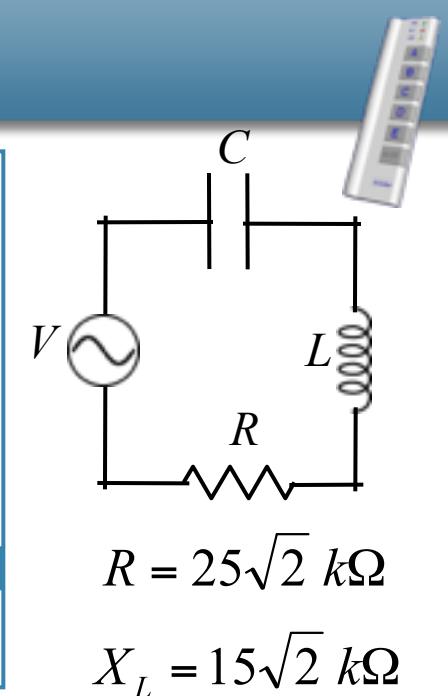What does the phasor diagram look like at  $t = 0$ ? (assume  $V = V_{max}\sin(\omega t)$ )



$$V = V_{max} \sin(\omega t) \Rightarrow V \text{ is horizontal at } t = 0 \quad (V = 0)$$

$$\vec{V} = \vec{V}_L + \vec{V}_C + \vec{V}_R \quad \rightarrow \quad V_L < V_C \text{ if current leads generator voltage}$$