


Electricity & Magnetism

Lecture 18

INDUCTION and RL CIRCUITS

Today's Concepts:

- A) Induction
- B) RL Circuits

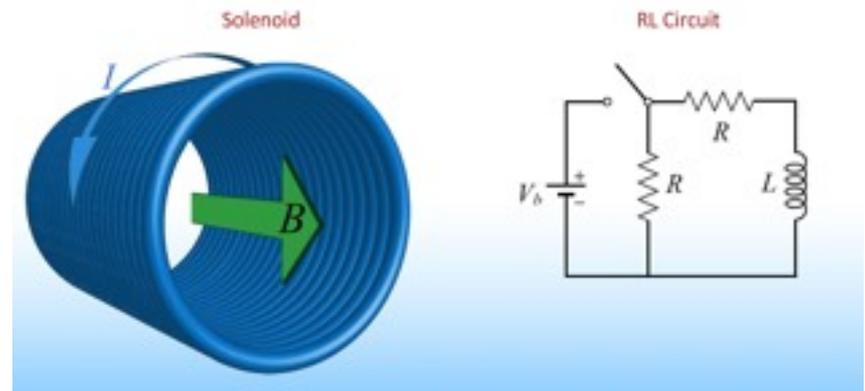

Stuff you said..

Will there be more lab activities involving oscilloscopes?

Unlike lab activities involving magnets, the oscilloscopes are foreign, new, and curiously interesting to play/learn with due to the above?


<http://www.sfu.ca/phys/141/1134/Schedule141.pdf>

What are the exact differences between the Capacitor and Inductor. In which situation would I use the Capacitor instead of the Inductor or vice versa?




Capacitors are yin — Inductors are yang

Time Spent Viewing Prelecture (N = 21)

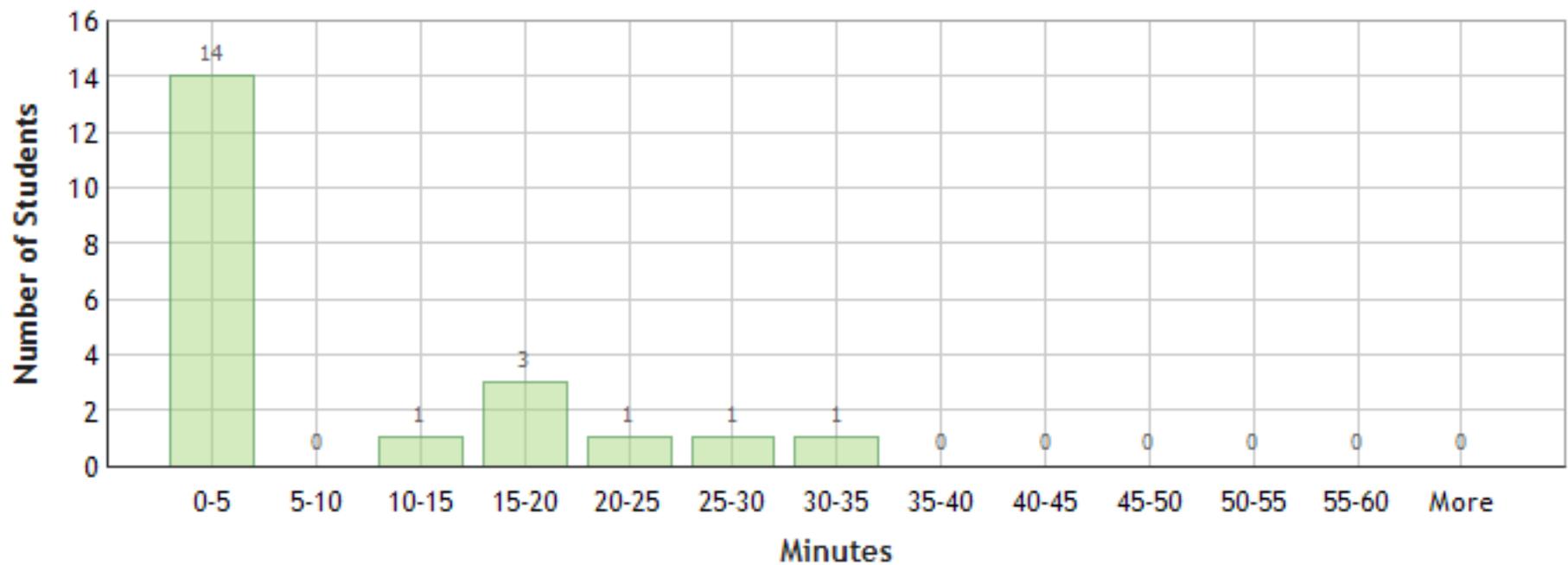

From the Prelecture: Self Inductance

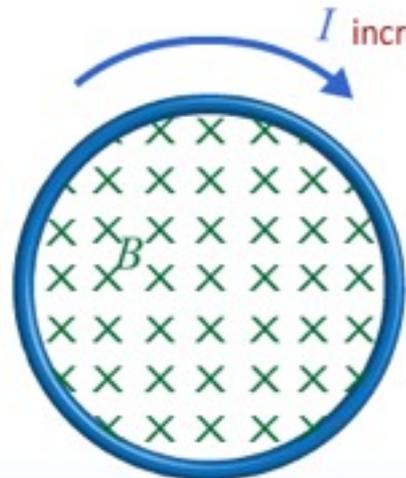

I increases

Faraday's Law

$$\mathcal{E} = -\frac{d\Phi_B}{dt} = -\frac{d(LI)}{dt} = -L\frac{dI}{dt}$$


Self-Inductance

$$L \equiv \frac{\Phi_B}{I}$$

SI Unit

$$H = T \cdot m^2 / A$$

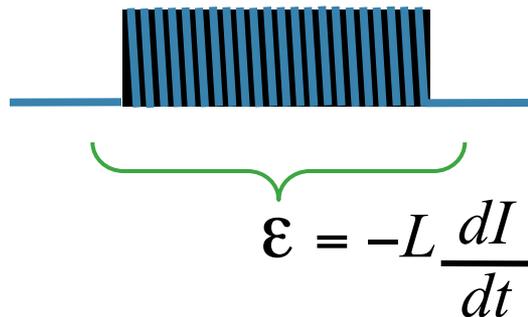
Wrap a wire into a coil to make an “inductor”...



What this really means:

emf induced across L tries to keep I constant.

$$\mathcal{E}_L = -L \frac{dI}{dt}$$

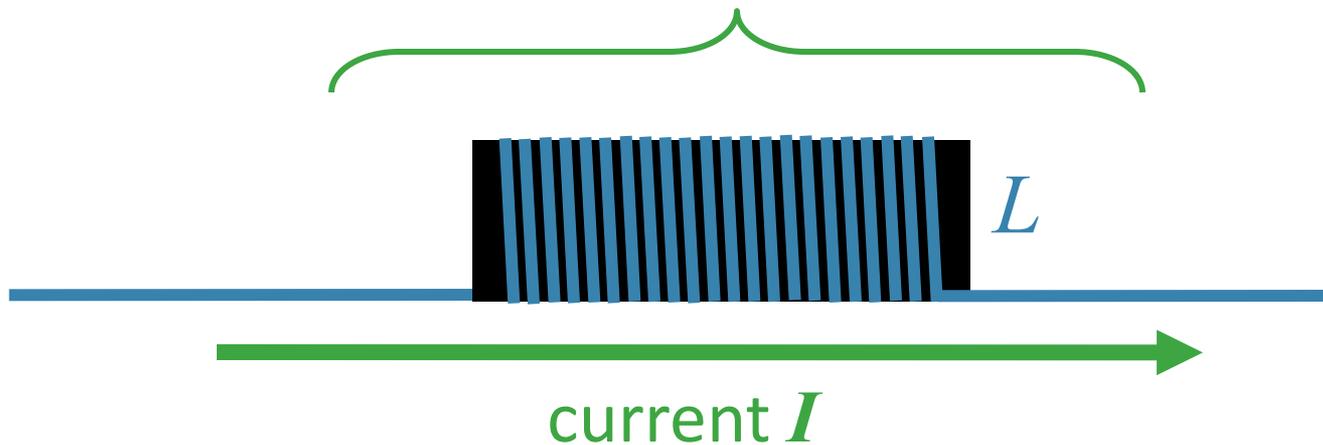

Inductors prevent discontinuous current changes!



It's like inertia!

Checkpoint 2

Two solenoids are made with the same cross sectional area and total number of turns. Inductor B is twice as long as inductor A

$$L_B = \mu_0 n^2 \pi r^2 z$$

\uparrow \uparrow
 $(1/2)^2$ 2

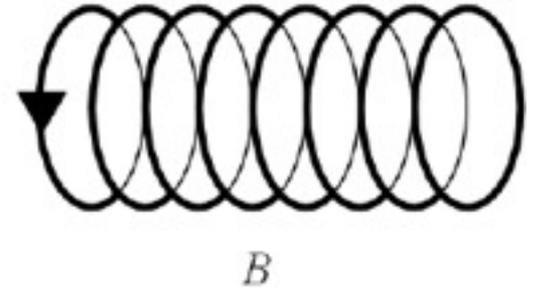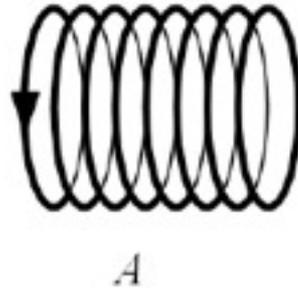


→ $L_B = \frac{1}{2} L_A$

Compare the inductance of the two solenoids

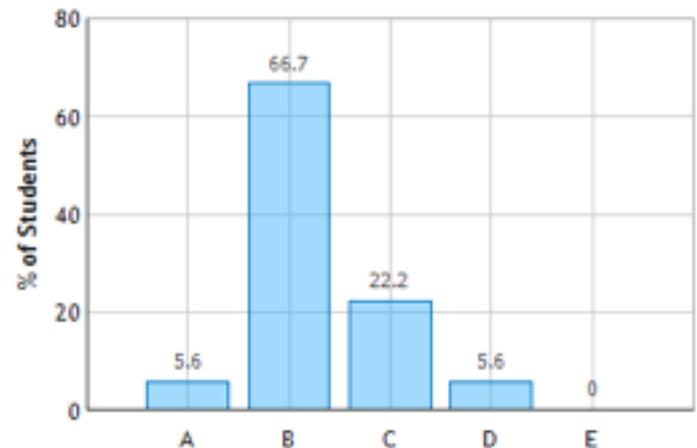
- A) $L_A = 4 L_B$
- B) $L_A = 2 L_B$**
- C) $L_A = L_B$
- D) $L_A = (1/2) L_B$
- E) $L_A = (1/4) L_B$

Inductance of Solenoids: Question 1 (N = 18)



How to think about RL circuits Episode 1:

When no current is flowing initially:

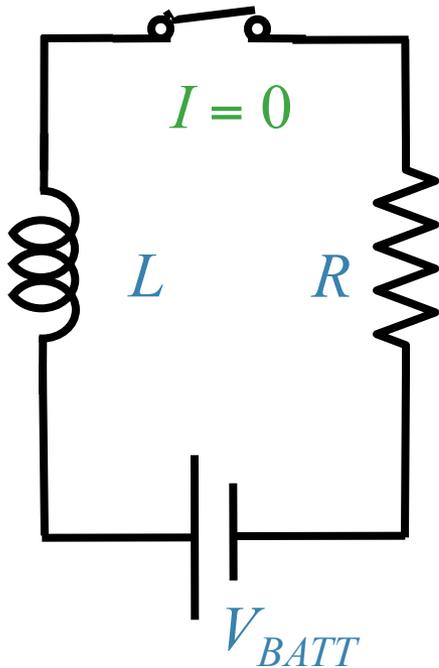


At $t = 0$:

$$I = 0$$

$$V_L = V_{BATT}$$

$$V_R = 0$$

(L is like a giant resistor)

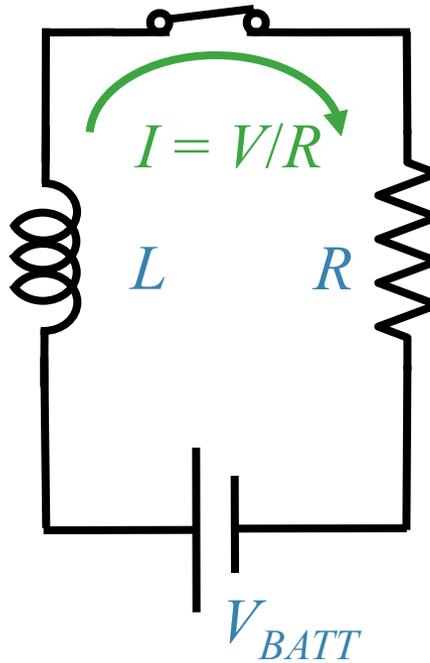


At $t \gg L/R$:

$$V_L = 0$$

$$V_R = V_{BATT}$$

$$I = V_{BATT}/R$$

(L is like a short circuit)

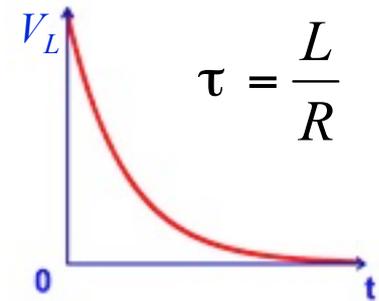

Checkpoint 4




In the circuit, the switch has been open for a long time, and the current is zero everywhere.

At time $t = 0$ the switch is closed.

What is the current I through the vertical resistor immediately after the switch is closed?

(+ is in the direction of the arrow)

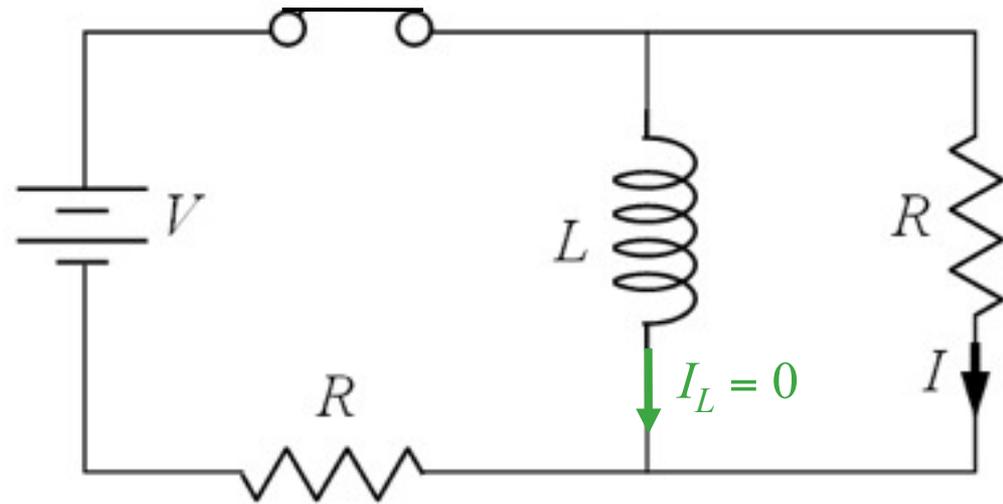

A) $I = V/R$


B) $I = V/2R$

C) $I = 0$

D) $I = -V/2R$

E) $I = -V/R$

RL Circuit: Question 1 (N = 17)

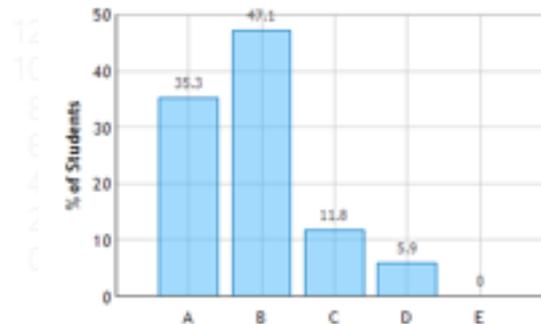


RL Circuit (Long Time)



What is the current I through the vertical resistor after the switch has been closed for a long time?





(+ is in the direction of the arrow)

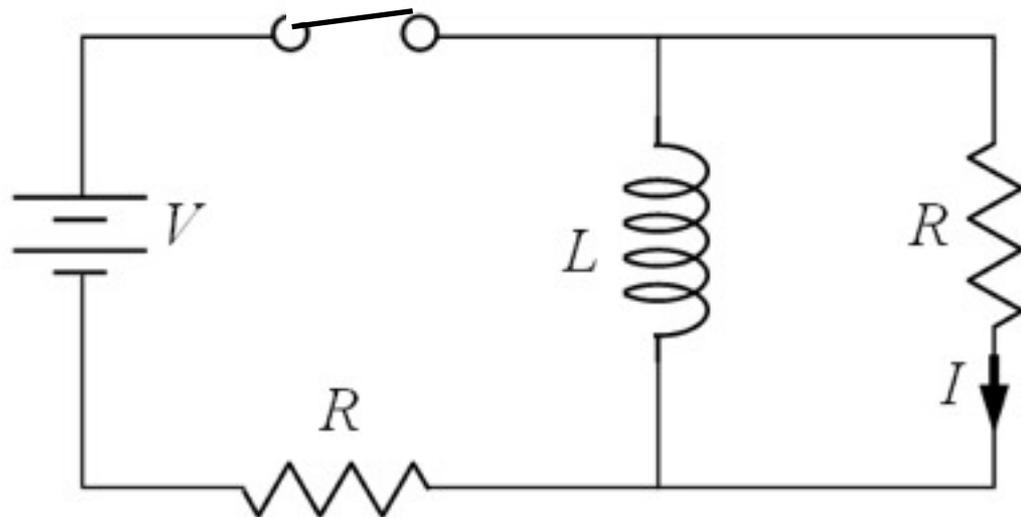- A) $I = V/R$
- B) $I = V/2R$
- C) $I = 0$
- D) $I = -V/2R$
- E) $I = -V/R$



How to Think about RL Circuits Episode 2:

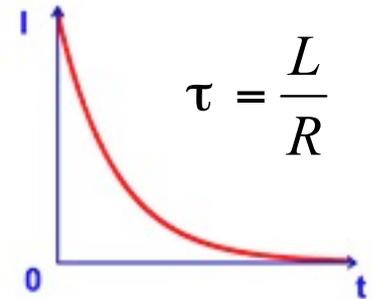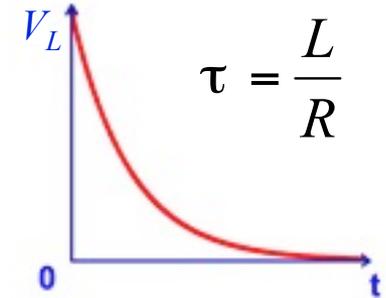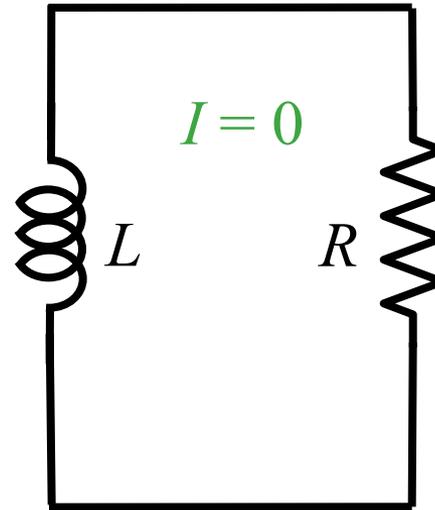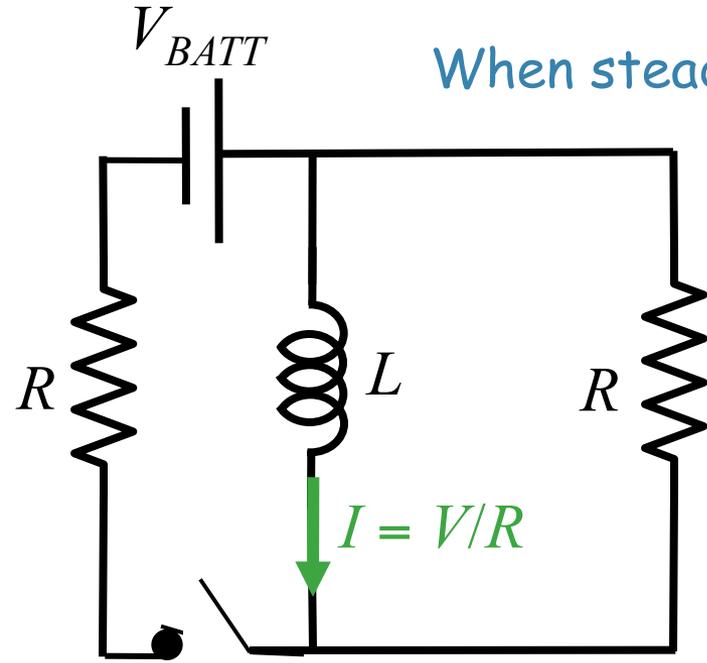When steady current is flowing initially:



At $t = 0$:

$$I = V_{BATT}/R$$
$$V_R = IR$$
$$V_L = V_R$$

At $t \gg L/R$:


$$I = 0$$
$$V_L = 0$$
$$V_R = 0$$

CheckPoint 6

After a long time, the switch is opened, abruptly disconnecting the battery from the circuit.


What is the current I through the vertical resistor immediately after the switch is opened?

(+ is in the direction of the arrow)

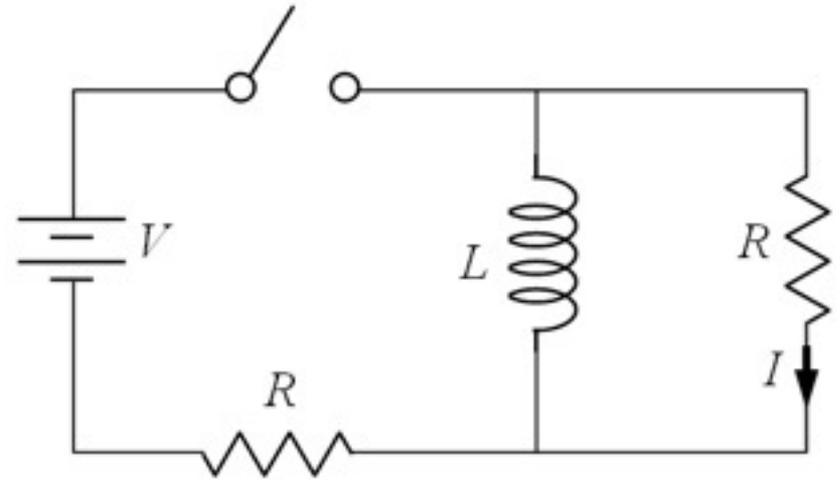


- A) $I = V/R$
- B) $I = V/2R$
- C) $I = 0$
- D) $I = -V/2R$
- E) $I = -V/R$

RL Circuit: Question 3 (N = 17)

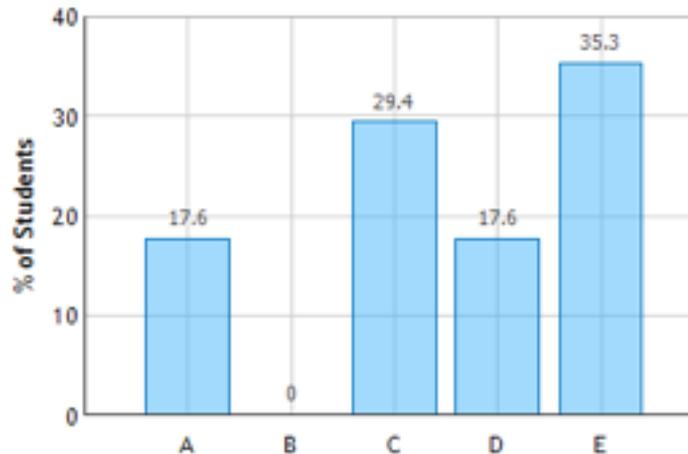

Why is there Exponential Behavior?

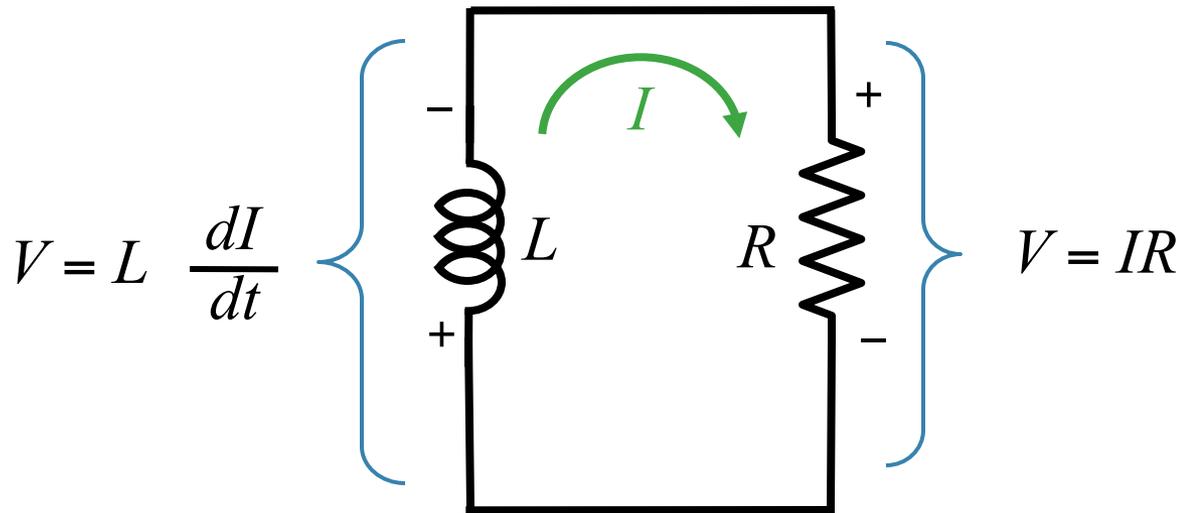



$$V = L \frac{dI}{dt}$$



$$V = IR$$

$$L \frac{dI}{dt} + IR = 0$$

$$I(t) = I_0 e^{-tR/L} = I_0 e^{-t/\tau}$$

where $\tau = \frac{L}{R}$

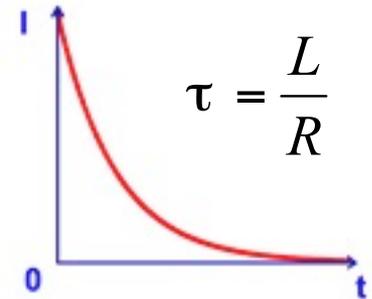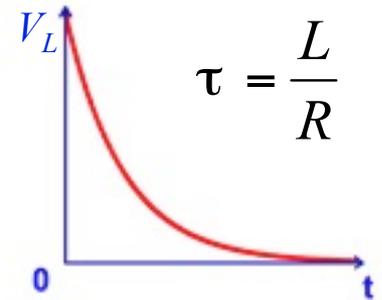

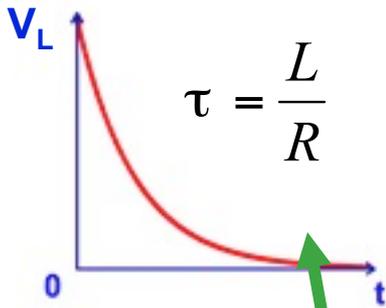
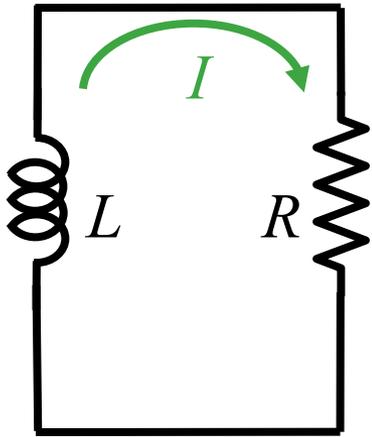


Lecture:


Did we mess up?

No: The resistance is simply twice as big in one case.

Time Constant $\tau = \frac{L}{2R}$

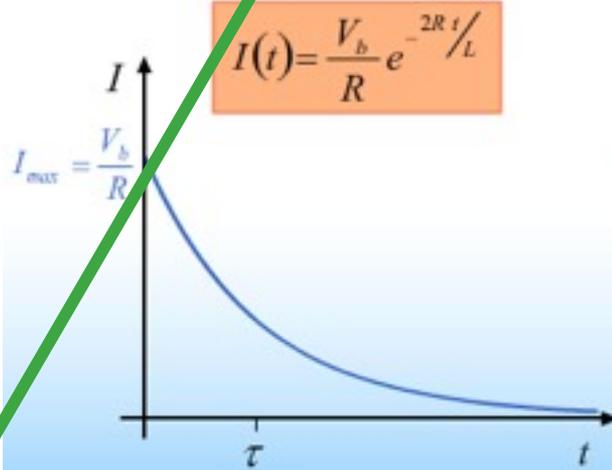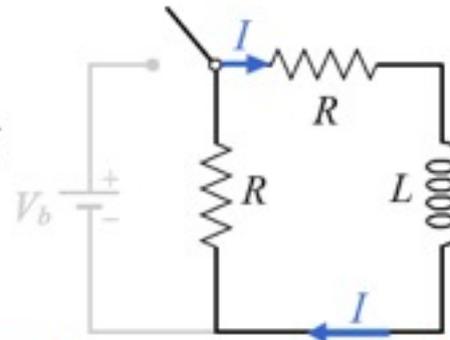


Prelecture:

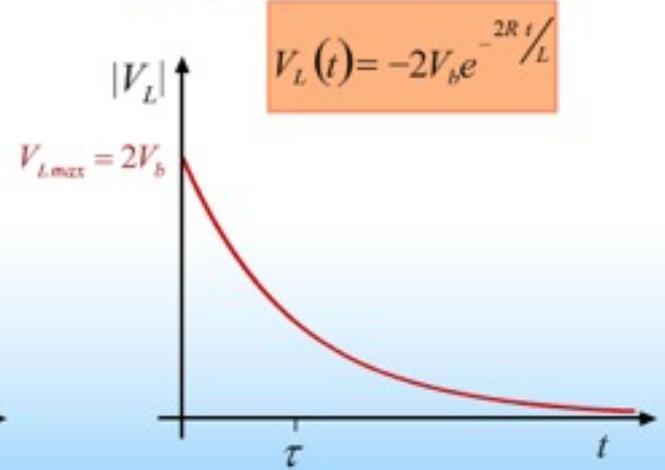

Checkpoint 8




After long time at 0, moved to 1

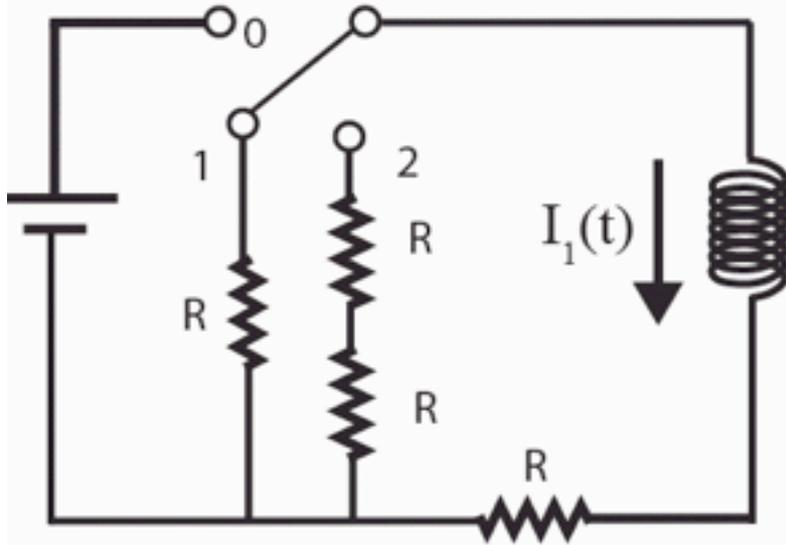

Case 1

After long time at 0, moved to 2

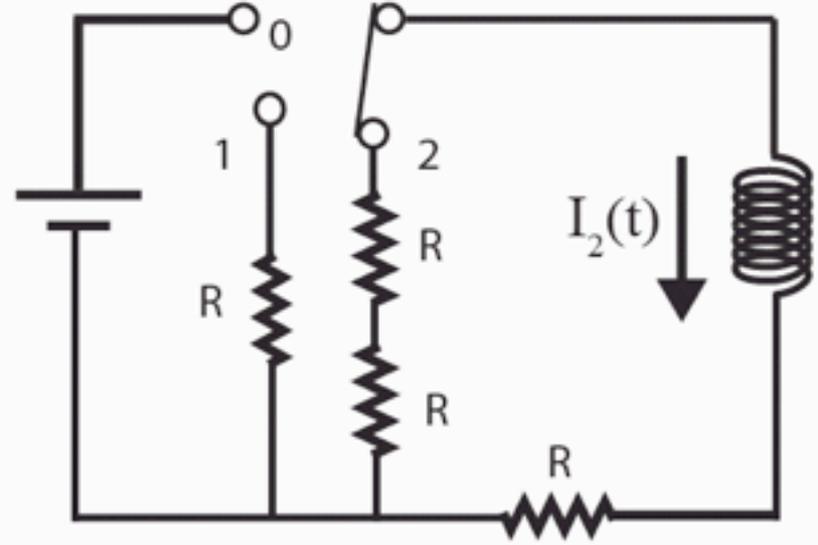

Case 2


After switch moved, which case has larger time constant?

- A) Case 1
- B) Case 2
- C) The same

CheckPoint 10




After long time at 0, moved to 1

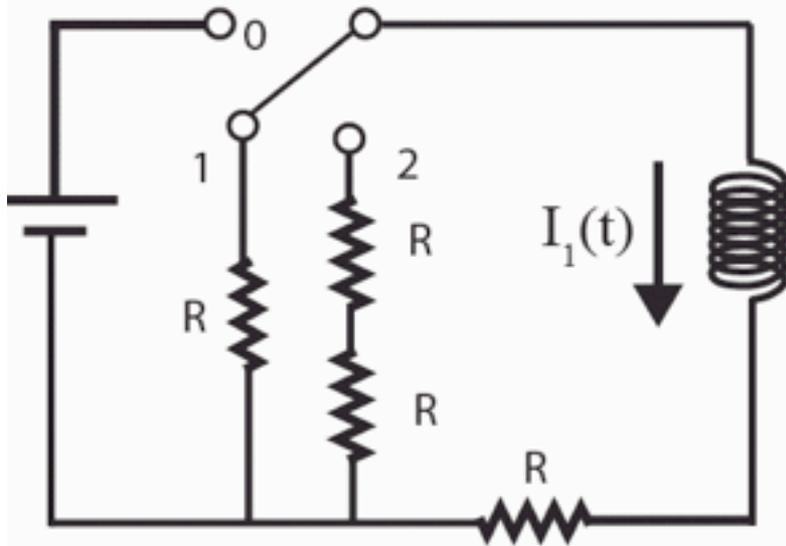

Case 1

After long time at 0, moved to 2

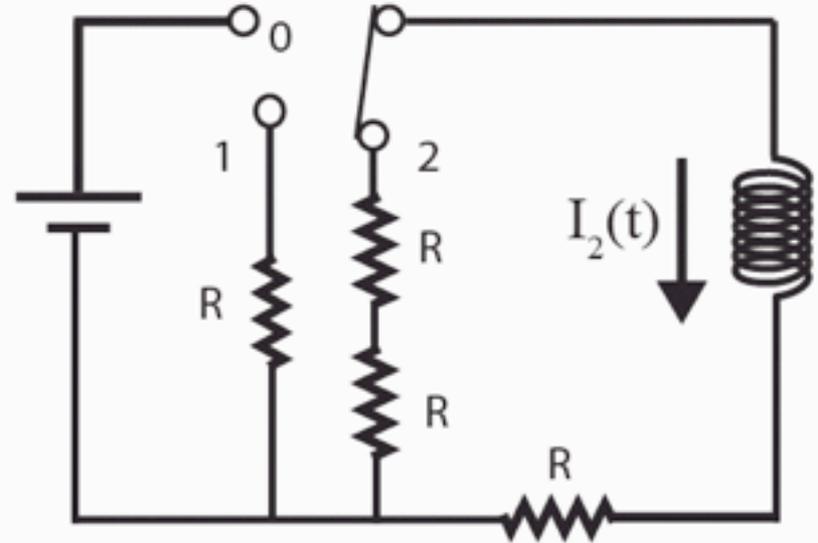

Case 2

Immediately after switch moved,
in which case is the voltage across
the inductor larger?

I_0 is V/R in both cases

- A) Case 1
- B) Case 2**
- C) The same


A) $V_L(0) = I_0 * 2R$

B) $V_L(0) = I_0 * 3R$

CheckPoint 12




After long time at 0, moved to 1

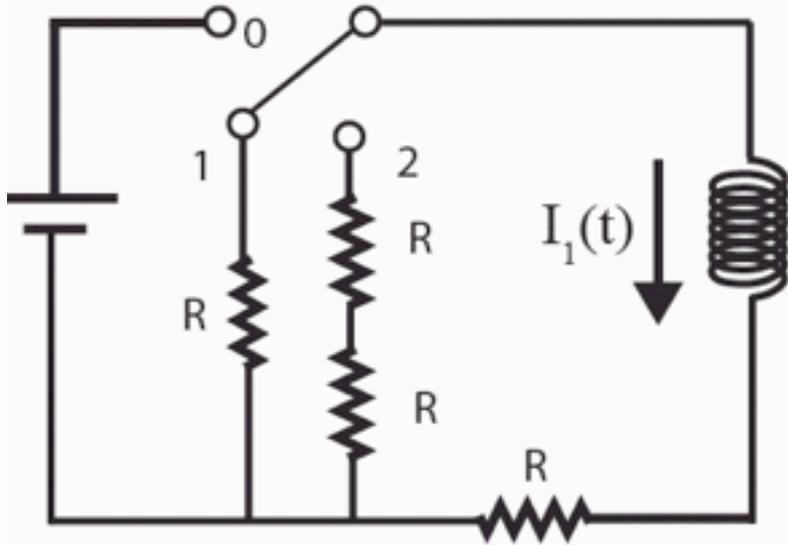

Case 1

After long time at 0, moved to 2

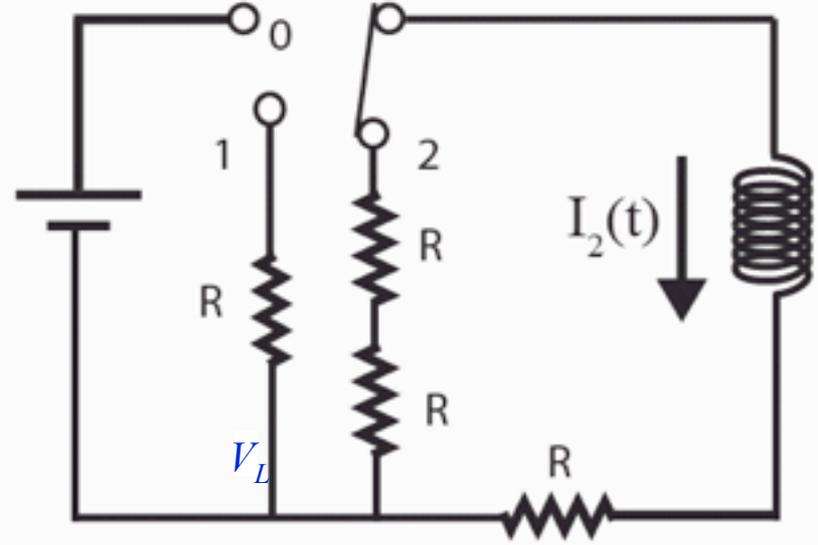


Case 2

After switch moved for finite time, in which case is the current through the inductor larger?

- A) Case 1
- B) Case 2
- C) The same

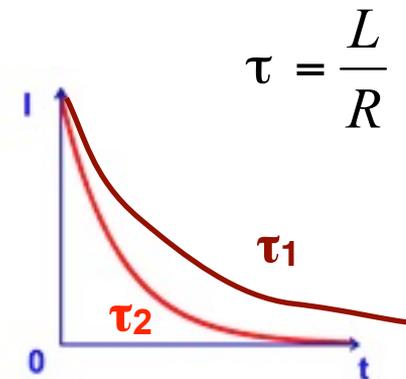
- A) $\tau_1 = L/2R$
- B) $\tau_2 = L/3R$



Calculation

The switch in the circuit shown has been open for a long time. At $t = 0$, the switch is closed.

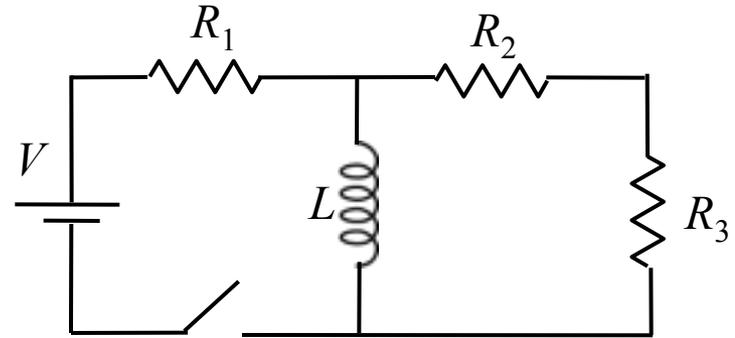What is dI_L/dt , the time rate of change of the current through the inductor immediately after switch is closed



Conceptual Analysis

Once switch is closed, currents will flow through this 2-loop circuit.

KVR and KCR can be used to determine currents as a function of time.

Strategic Analysis


Determine currents immediately after switch is closed.

Determine voltage across inductor immediately after switch is closed.

Determine dI_L/dt immediately after switch is closed.

Calculation

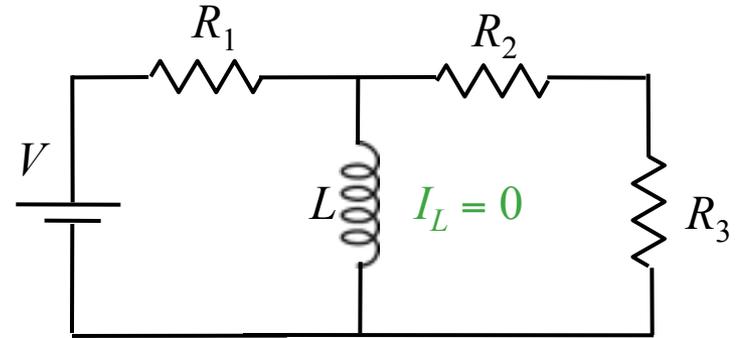The switch in the circuit shown has been open for a long time. At $t = 0$, the switch is closed.



What is I_L , the current in the inductor, immediately after the switch is closed?


A) $I_L = V/R_1$ up

B) $I_L = V/R_1$ down

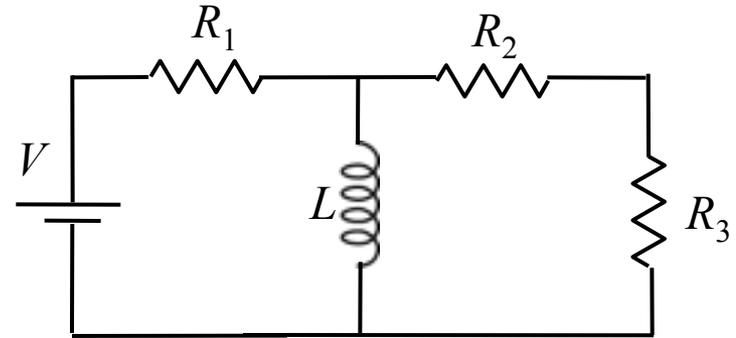C) $I_L = 0$

Calculation

The switch in the circuit shown has been open for a long time. At $t = 0$, the switch is closed.



$$I_L(t = 0+) = 0$$

What is the magnitude of I_2 , the current in R_2 , immediately after the switch is closed?

A) $I_2 = \frac{V}{R_1}$


B) $I_2 = \frac{V}{R_2 + R_3}$

C) $I_2 = \frac{V}{R_1 + R_2 + R_3}$

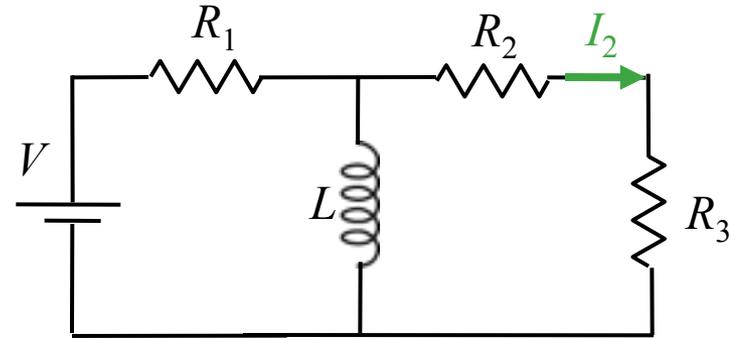D) $I_2 = \frac{VR_2R_3}{R_2 + R_3}$

Calculation

The switch in the circuit shown has been open for a long time. At $t = 0$, the switch is closed.



$$I_L(t = 0+) = 0 \quad I_2(t = 0+) = V/(R_1 + R_2 + R_3)$$

What is the magnitude of V_L , the voltage across the inductor, immediately after the switch is closed?

A) $V_L = V \frac{R_2 R_3}{R_1}$

B) $V_L = V$

C) $V_L = 0$


D) $V_L = V \frac{R_2 R_3}{R_1 (R_2 + R_3)}$

E) $V_L = V \frac{R_2 + R_3}{R_1 + R_2 + R_3}$

Calculation

The switch in the circuit shown has been open for a long time. At $t = 0$, the switch is closed.

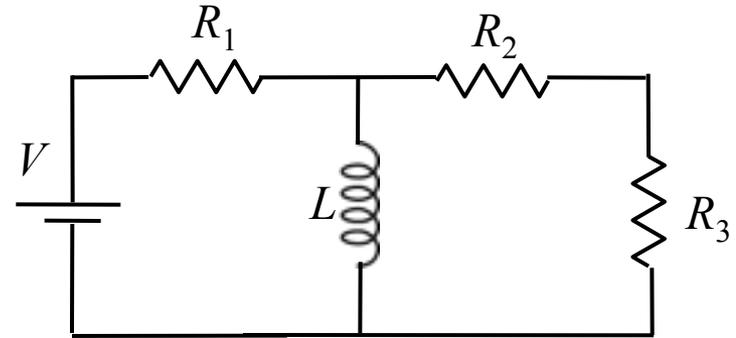What is dI_L/dt , the time rate of change of the current through the inductor immediately after switch is closed



$$V_L(t = 0+) = V(R_2 + R_3)/(R_1 + R_2 + R_3)$$

A) $\frac{dI_L}{dt} = \frac{V}{L} \frac{R_2 + R_3}{R_1}$

B) $\frac{dI_L}{dt} = 0$

C) $\frac{dI_L}{dt} = \frac{V}{L} \frac{R_2 + R_3}{R_1 + R_2 + R_3}$


D) $\frac{dI_L}{dt} = \frac{V}{L}$

Follow Up

The switch in the circuit shown has been closed for a long time.

What is I_2 , the current through R_2 ?

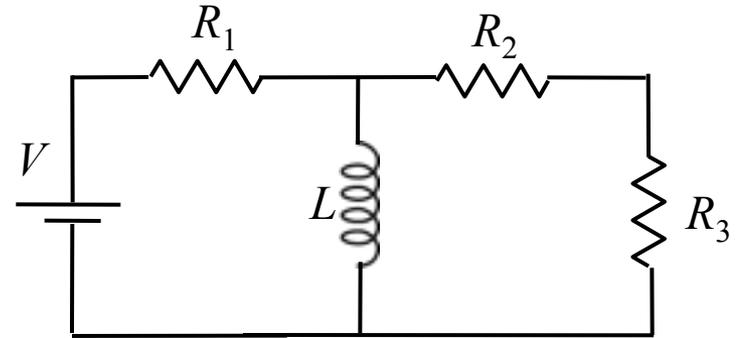(Positive values indicate current flows to the right)



A) $I_2 = +\frac{V}{R_2 + R_3}$

B) $I_2 = +\frac{V(R_2 R_3)}{R_1 + R_2 + R_3}$

C) $I_2 = 0$

D) $I_2 = -\frac{V}{R_2 + R_3}$


Follow Up 2



The switch in the circuit shown has been closed for a long time at which point, the switch is opened.

What is I_2 , the current through R_2 immediately after switch is opened?

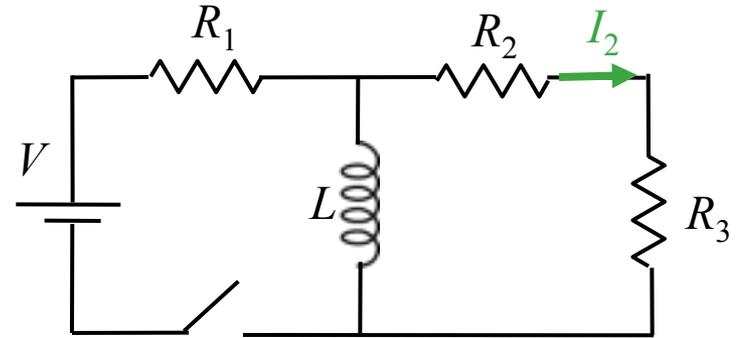(Positive values indicate current flows to the right)



A) $I_2 = +\frac{V}{R_1 + R_2 + R_3}$

B) $I_2 = +\frac{V}{R_1}$

C) $I_2 = 0$

D) $I_2 = -\frac{V}{R_1}$ E) $I_2 = -\frac{V}{R_1 + R_2 + R_3}$