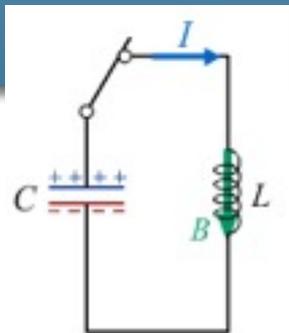





# Electricity & Magnetism

## Lecture 19



Today's Concepts:

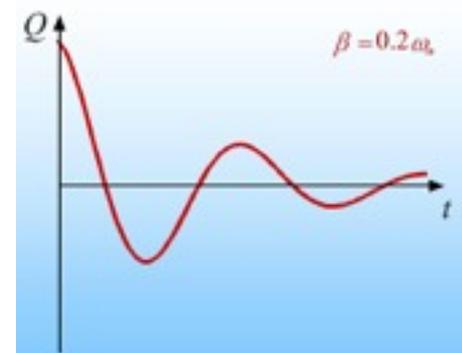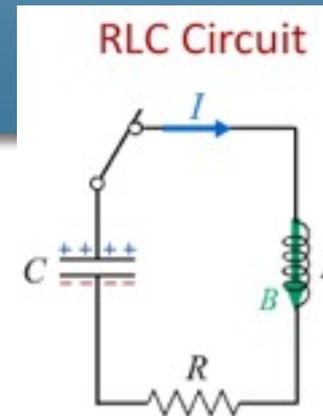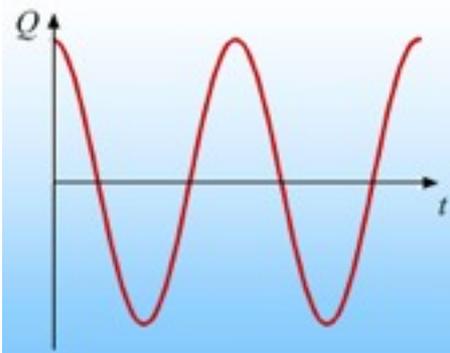- A) Oscillation Frequency
- B) Energy
- C) Damping



# Confused — Confident



I am ...

- A. Confused
- B. Somewhat Confused
- C. So-so
- D. Somewhat Confident
- E. Confident

# Your Comments

“All of this stuff, I wish we could go slower but I know we cant.”

TOO TRUE: Hang in there, we'll do our best to work on the issues....

“Differential equations have taken over my life. I'm not sure I approve.”

“There are a lot of formulas in this section”

“Please explain the meaning of  $\cos(\omega t + x)$ ”

Differential Equations Do Determine Much Behaviour in Physics. We will show corresponding equations in mechanics today

“Why do capacitors start off with a charge of zero when the switch is opened? shouldn't they start off with charge? “

Walking home from the mechanics final last semester I thought I was done with oscillatory motion for life. Never have I been so wrong...

It all depends on how the circuit was started. You have to determine the initial conditions from the problem statement


That's right!

# Some Practical Test Stuff

Practical Test is on Friday, July 5

- We will have 2 practise sessions: Friday and Next Wednesday
- Covers DC Circuits and the Oscilloscope (LC or RC Circuit)
- 50 min each — We will divide class into two halves.
  - (those who don't have class after this should sign up for the later one.)
- smartPhysics will continue Fri and Wed covering these topics theoretically
- Practise exam is [here](#):
- You may also practise on circuits of your own (eg. LCR circuits and resonance)

# LC Circuit

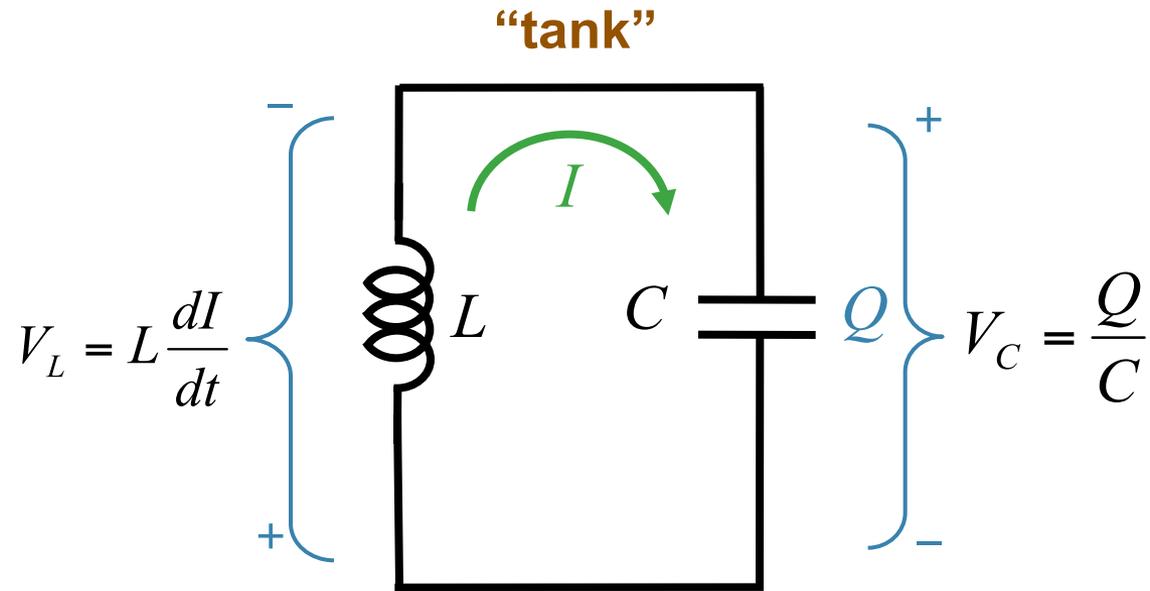

Circuit Equation:  $\frac{Q}{C} + L \frac{dI}{dt} = 0$

$$I = \frac{dQ}{dt} \longrightarrow \frac{d^2Q}{dt^2} = -\frac{Q}{LC} \longrightarrow \frac{d^2Q}{dt^2} = -\omega^2 Q$$


where

$$\omega = \frac{1}{\sqrt{LC}}$$

$$m \leftrightarrow L$$


$$\frac{d^2 Q}{dt^2} = -\omega^2 Q$$

$$\omega = \frac{1}{\sqrt{LC}}$$

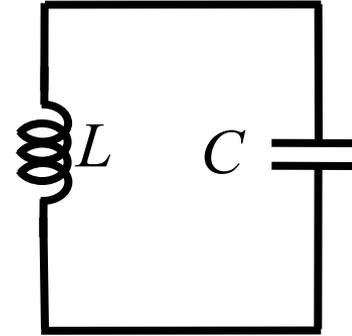

$$\frac{d^2 x}{dt^2} = -\omega^2 x$$

$$\omega = \sqrt{\frac{k}{m}}$$

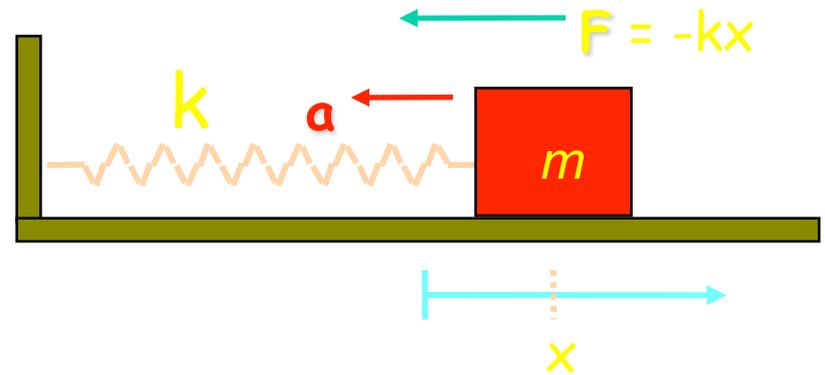



Same thing if we notice that

$$k \leftrightarrow \frac{1}{C}$$

and


$$m \leftrightarrow L$$

# Time Dependence

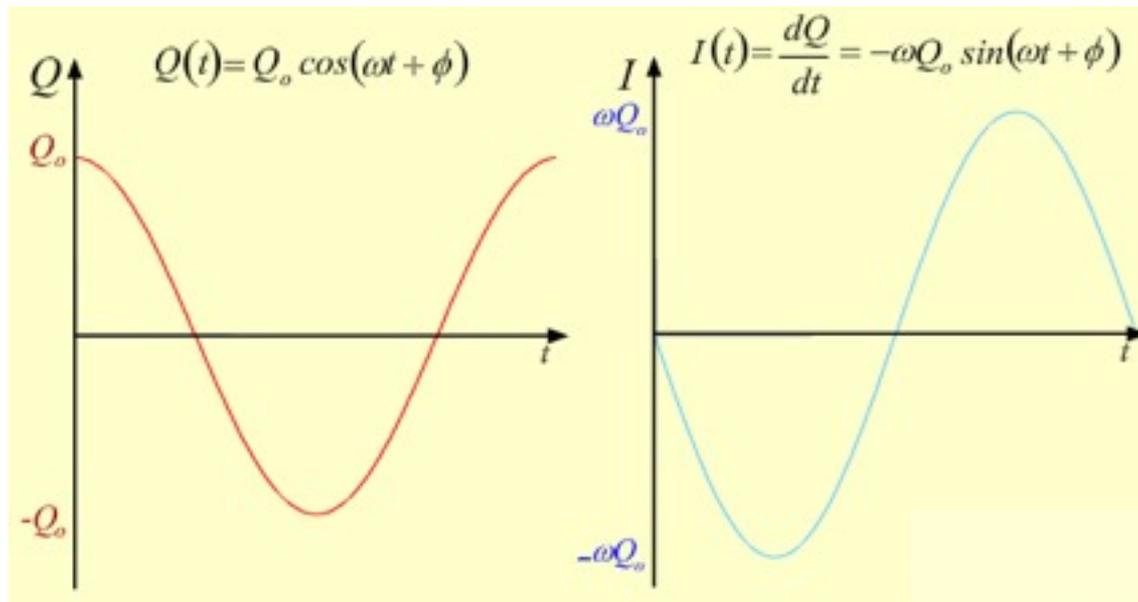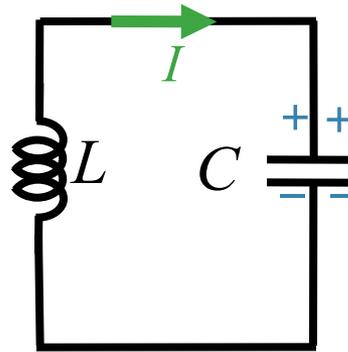

# Wikipedia Animation


## “LC Circuit”

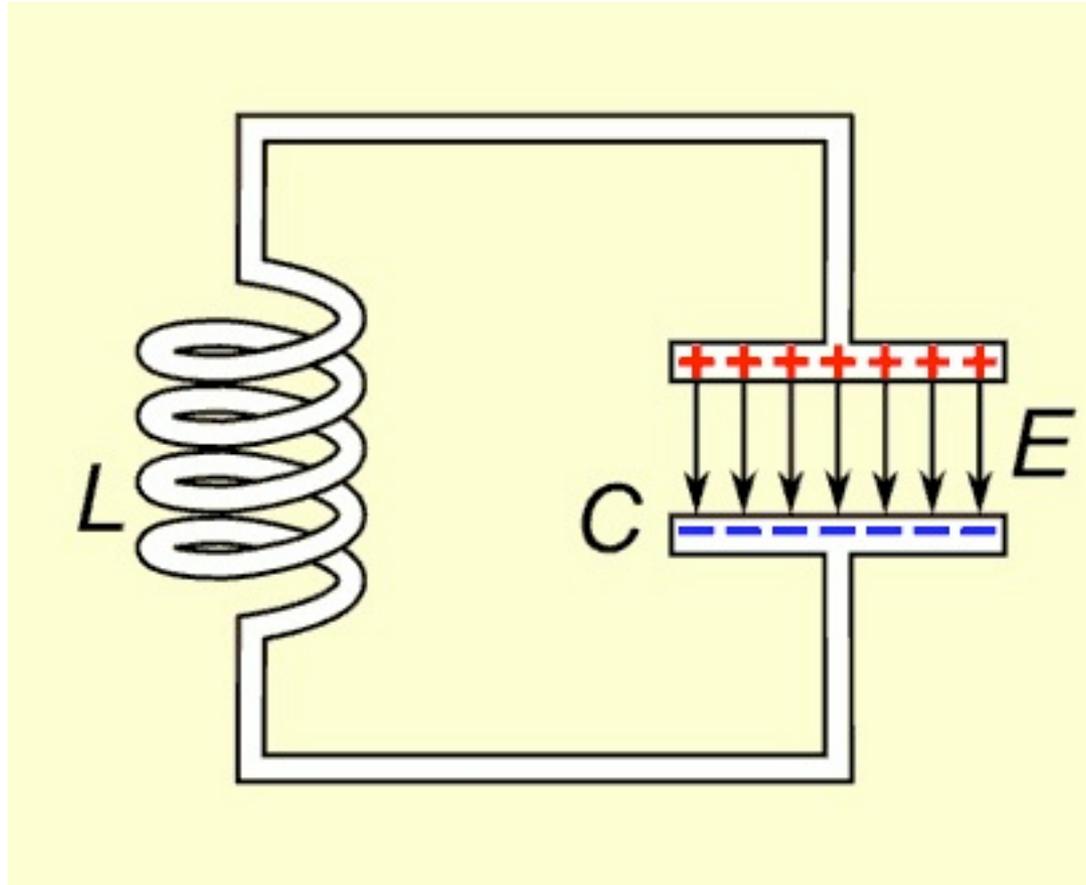
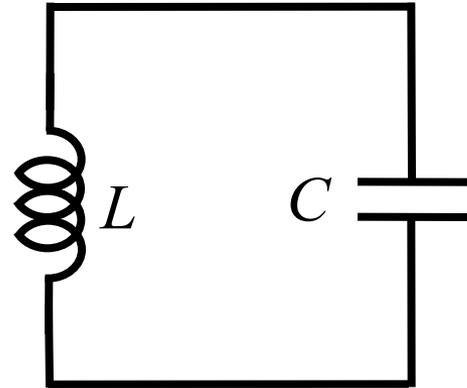
# CheckPoint 2



At time  $t = 0$  the capacitor is fully charged with  $Q_{max}$  and the current through the circuit is 0.



What is the potential difference across the inductor at  $t = 0$ ?

A)  $V_L = 0$


**B)  $V_L = Q_{max}/C$**

C)  $V_L = Q_{max}/2C$

since  $V_L = V_C$

The voltage across the capacitor is  $Q_{max}/C$ . Kirchhoff's Voltage Rule implies that must also be equal to the voltage across the inductor


Pendulum.

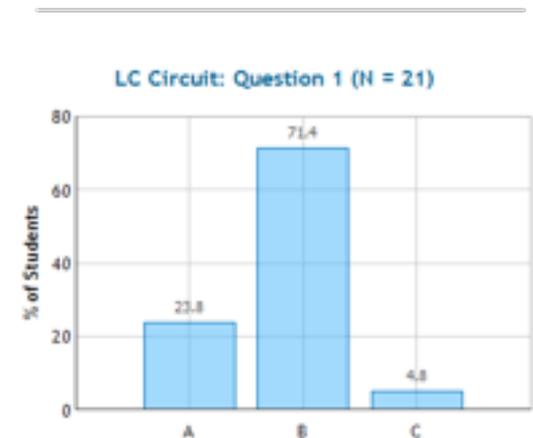
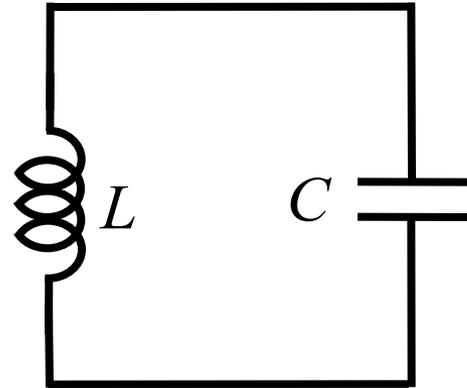
# Checkpoint 4



At time  $t = 0$  the capacitor is fully charged with  $Q_{max}$  and the current through the circuit is 0.



What is the potential difference across the inductor when the current is maximum?


A)  $V_L = 0$

B)  $V_L = Q_{max}/C$

C)  $V_L = Q_{max}/2C$

$dI/dt$  is zero when current is maximum


LC Circuit: Question 3 (N = 10)

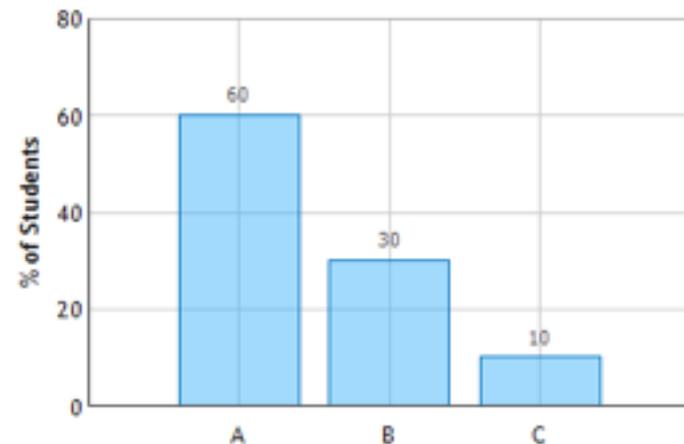
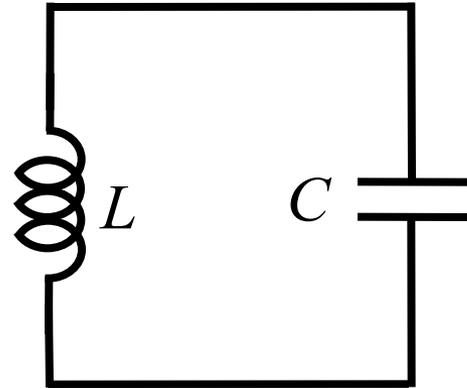
# Checkpoint 6



At time  $t = 0$  the capacitor is fully charged with  $Q_{max}$  and the current through the circuit is 0.



How much energy is stored in the capacitor when the current is a maximum ?

A)  $U = Q_{max}^2 / (2C)$

B)  $U = Q_{max}^2 / (4C)$

C)  $U = 0$


**Total Energy is constant!**

$$U_{Lmax} = \frac{1}{2} L I_{max}^2$$

$$U_{Cmax} = Q_{max}^2 / 2C$$

$$I = \text{max when } Q = 0$$


LC Circuit: Question 3 (N = 21)

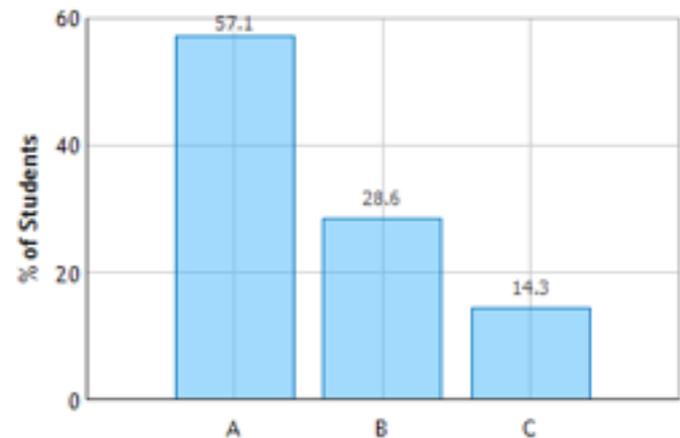
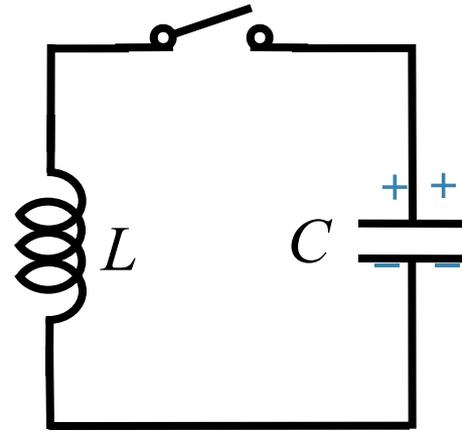
# Checkpoint 8



The capacitor is charged such that the top plate has a charge  $+Q_0$  and the bottom plate  $-Q_0$ . At time  $t = 0$ , the switch is closed and the circuit oscillates with frequency  $\omega = 500$  radians/s.



$$L = 4 \times 10^{-3} \text{ H}$$
$$\omega = 500 \text{ rad/s}$$

What is the value of the capacitor  $C$ ?


**A)  $C = 1 \times 10^{-3} \text{ F}$**

B)  $C = 2 \times 10^{-3} \text{ F}$







C)  $C = 4 \times 10^{-3} \text{ F}$

$$\omega = \frac{1}{\sqrt{LC}} \longrightarrow C = \frac{1}{\omega^2 L} = \frac{1}{(25 \times 10^4)(4 \times 10^{-3})} = 10^{-3}$$

LC Circuit 2: Question 1 (N = 10)

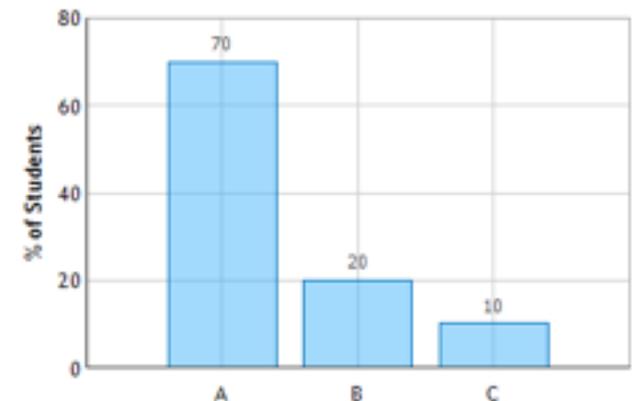

# CheckPoint 10

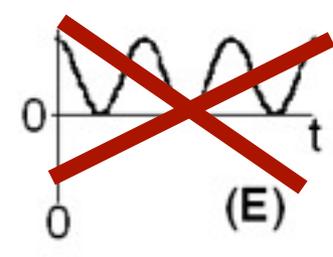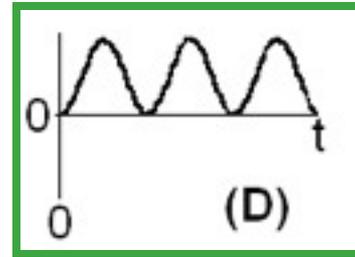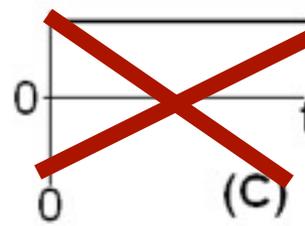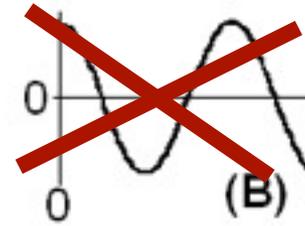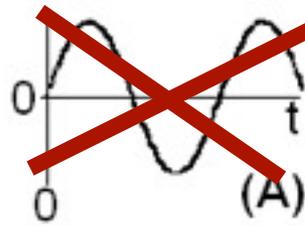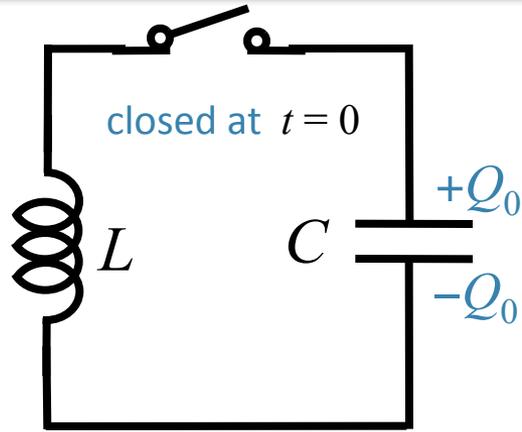

Which plot best represents the energy in the inductor as a function of time starting just after the switch is closed?


$$U_L = \frac{1}{2} LI^2$$

Energy proportional to  $I^2 \Rightarrow C$  cannot be negative

Current is changing  $\Rightarrow U_L$  is not constant


Initial current is zero

LC Circuit 2: Question 3 (N = 10)

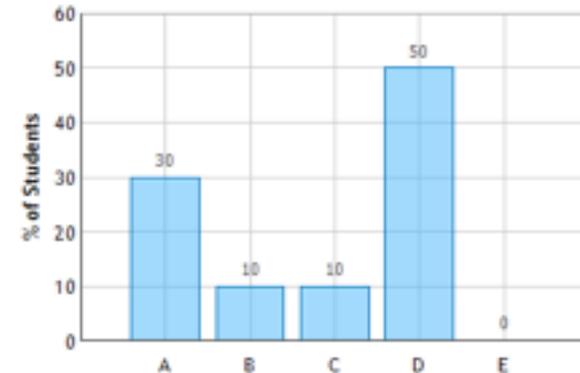

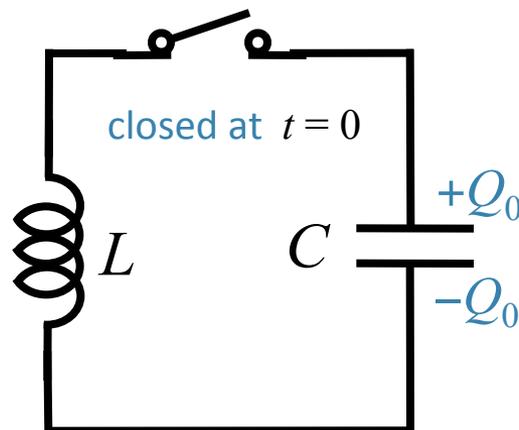
# CheckPoint 12

When the energy stored in the capacitor reaches its maximum again for the first time after  $t = 0$ , how much charge is stored on the top plate of the capacitor?



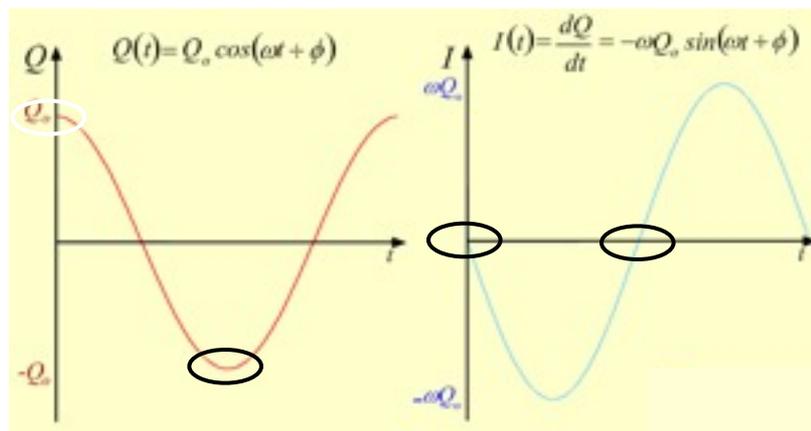- A)  $+Q_0$
- B)  $+Q_0/2$
- C) 0
- D)  $-Q_0/2$
- E)  $-Q_0$**




$Q$  is maximum when current goes to zero

$$I = \frac{dQ}{dt}$$


Current goes to zero twice during one cycle

LC Circuit 2: Question 5 (N = 10)

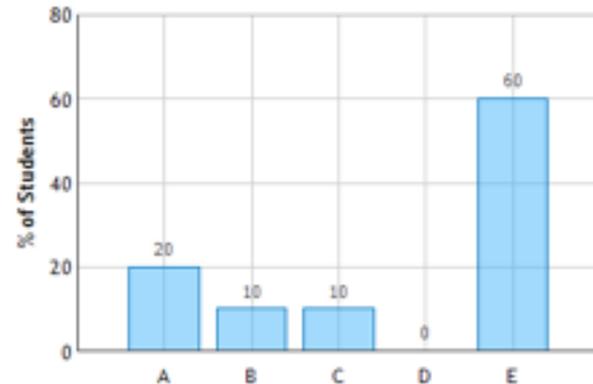
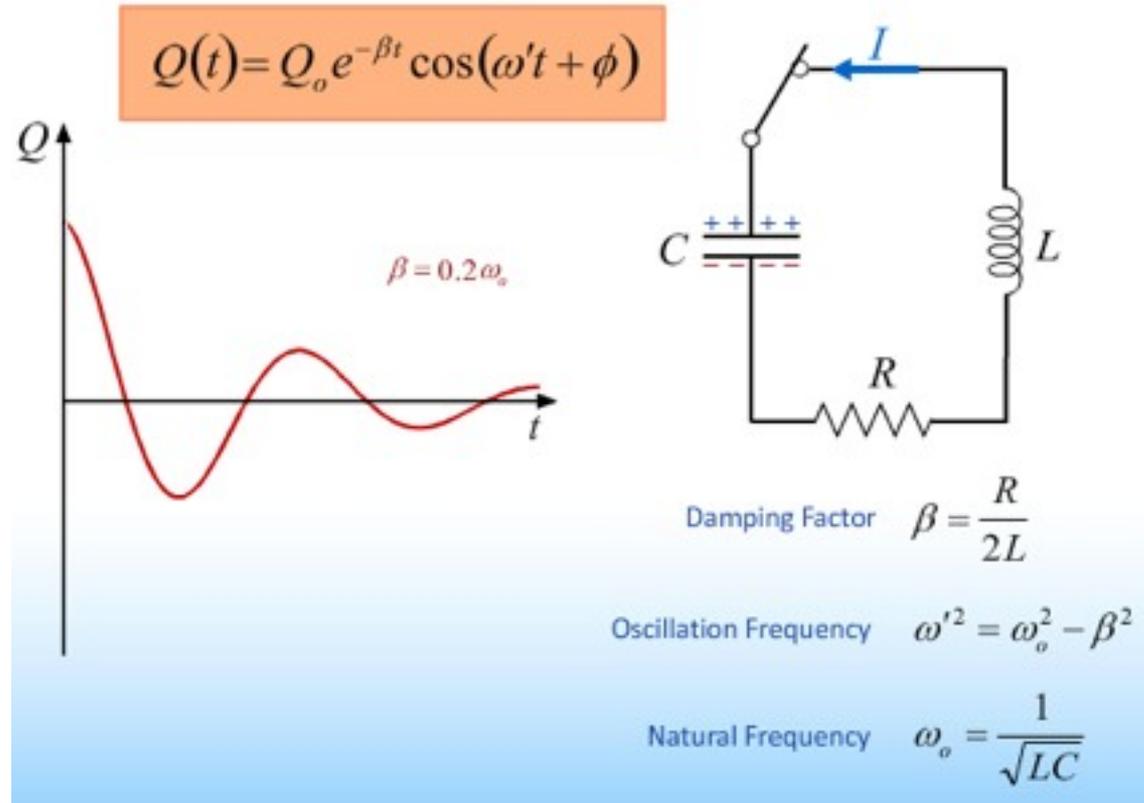
# Add R: Damping

Just like  $LC$  circuit but the oscillations get smaller because of  $R$



Concept makes sense...

...but answer looks kind of complicated

# Physics Truth #1:

Even though the answer sometimes looks complicated...

$$Q(t) = Q_o \cos(\omega t - \phi)$$


the physics under the hood is still very simple!

$$\frac{d^2 Q}{dt^2} = -\omega^2 Q$$

The elements of a circuit are very simple:

$$V_L = L \frac{dI}{dt}$$

$$V = V_L + V_C + V_R$$

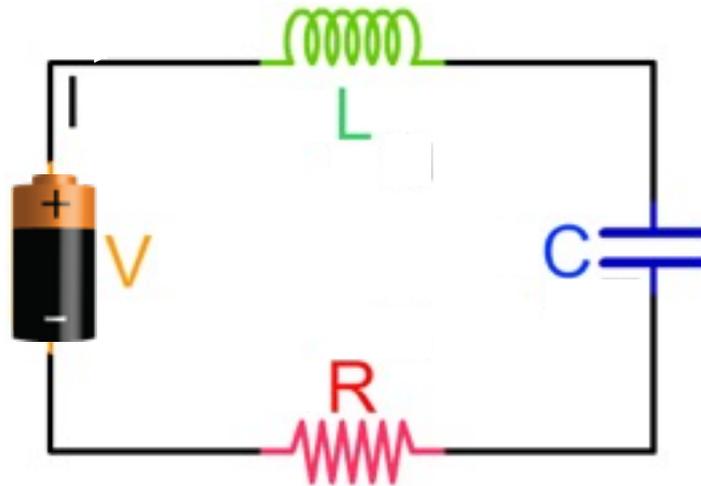

$$V_C = \frac{Q}{C}$$
$$I = \frac{dQ}{dt}$$


$$V_R = IR$$

This is all we need to know to solve for anything!

# A Different Approach

Start with some initial  $V, I, Q, V_L$

Now take a tiny time step  $dt$  (1 ms)

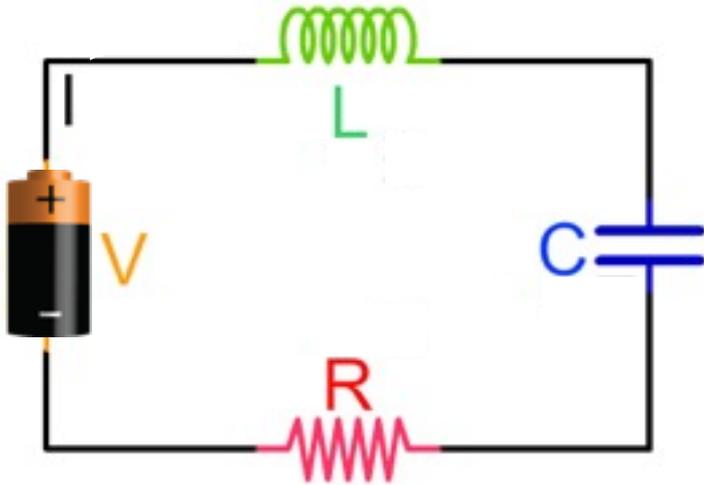

```
for (var t=0; t<tStepSec; t+=dt) {  
  I += Vind_last*dt/L;  
  Qcap += I*dt;  
  Vcap = Qcap/C;  
  Vres = I*R1;  
  Vind_last = Vind;  
  Vind = Va - Vres - Vcap;  
}
```

$$dI = \frac{V_L}{L} dt$$


$$dQ = Idt$$

$$V_C = \frac{Q}{C}$$

$$V_R = IR$$

$$V_L = V - V_R - V_C$$


Repeat...

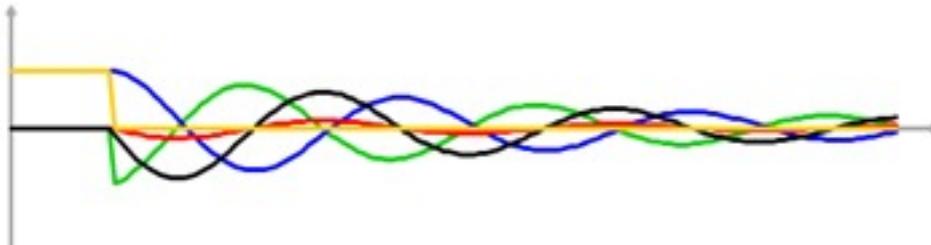
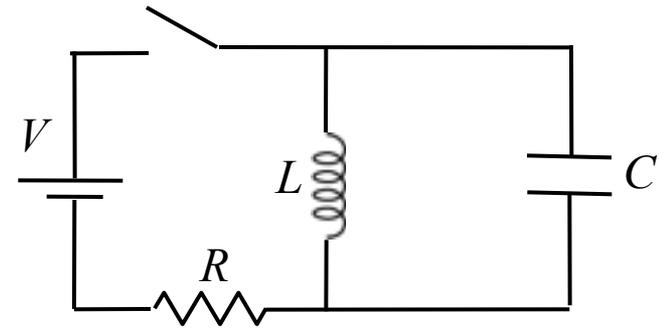
# Calculation

The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.

What is  $Q_{MAX}$ , the maximum charge on the capacitor?



## Conceptual Analysis


Once switch is opened, we have an  $LC$  circuit  
Current will oscillate with natural frequency  $\omega_0$

## Strategic Analysis

- Determine initial current
- Determine oscillation frequency  $\omega_0$
- Find maximum charge on capacitor
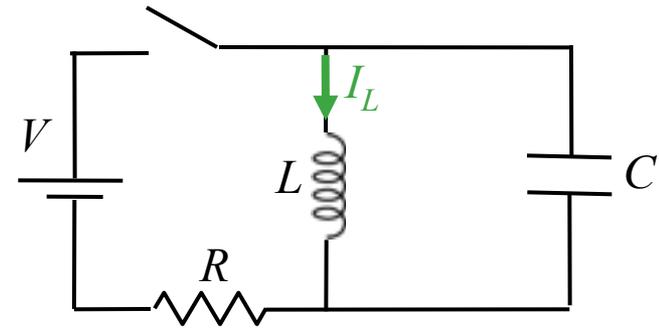
# Calculation

The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.



What is  $I_L$ , the current in the inductor, immediately **after** the switch is opened? Take positive direction as shown.

A)  $I_L < 0$

B)  $I_L = 0$

C)  $I_L > 0$


Current through inductor immediately **after** switch is opened  
**is the same as**  
the current through inductor immediately **before** switch is opened

**before switch is opened:**

all current goes through inductor in direction shown
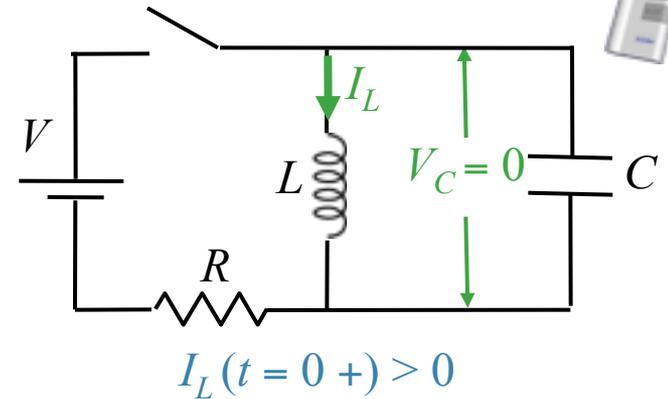
# Calculation

The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.



The energy stored in the capacitor immediately after the switch is opened is zero.

A) TRUE

B) FALSE

before switch is opened:

$$dI_L/dt \sim 0 \Rightarrow V_L = 0$$

BUT:  $V_L = V_C$

since they are in parallel

$$\longrightarrow V_C = 0$$

after switch is opened:

$V_C$  cannot change abruptly

$$\longrightarrow V_C = 0$$

$$\longrightarrow U_C = \frac{1}{2} CV_C^2 = 0!$$


**IMPORTANT:** NOTE DIFFERENT CONSTRAINTS AFTER SWITCH OPENED

CURRENT through INDUCTOR cannot change abruptly

VOLTAGE across CAPACITOR cannot change abruptly
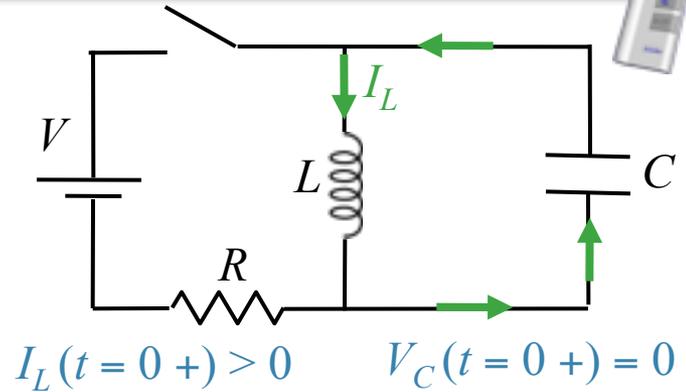
# Calculation

The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.



What is the direction of the current immediately after the switch is opened?

A) clockwise

B) counterclockwise


Current through inductor immediately **after** switch is opened  
**is the same as**  
the current through inductor immediately **before** switch is opened

**Before** switch is opened: Current moves down through  $L$

**After** switch is opened: Current continues to move down through  $L$
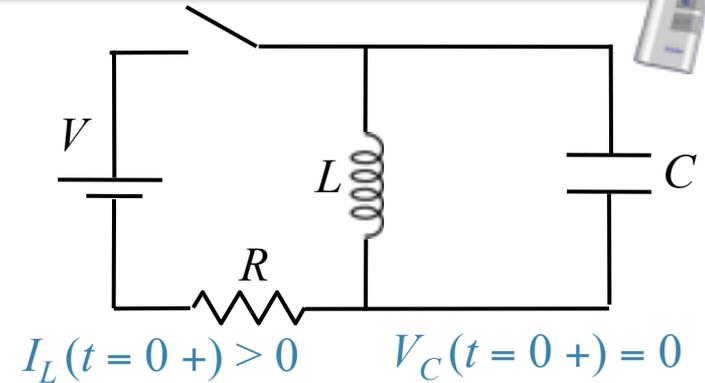
# Calculation


The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.



What is the magnitude of the current right after the switch is opened?

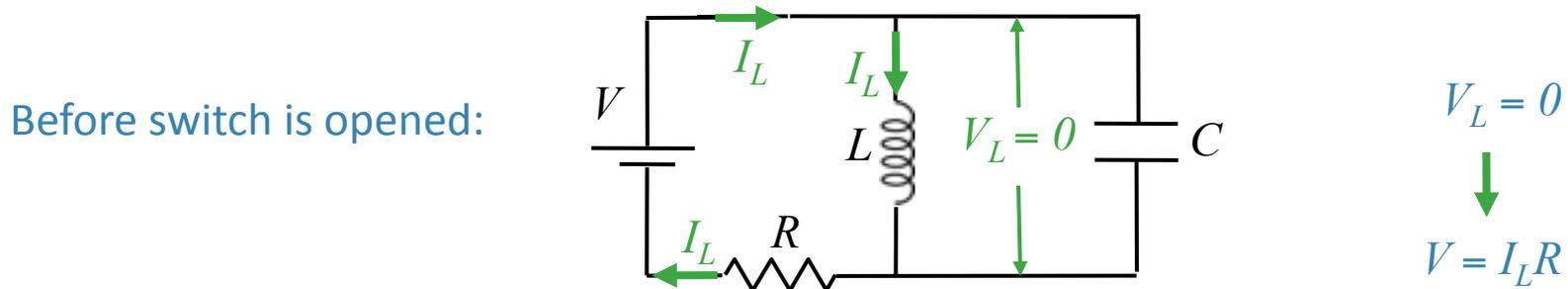- A)  $I_o = V \sqrt{\frac{C}{L}}$       B)  $I_o = \frac{V}{R^2} \sqrt{\frac{L}{C}}$       **C)  $I_o = \frac{V}{R}$**       D)  $I_o = \frac{V}{2R}$


Current through inductor immediately **after** switch is opened  
**is the same as**  
the current through inductor immediately **before** switch is opened



# Calculation

The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.

**Hint:** Energy is conserved

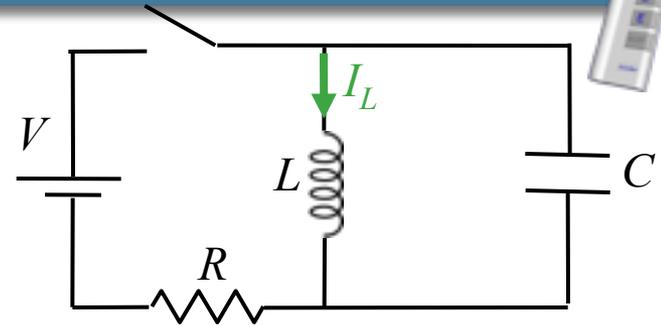

$$I_L(t = 0+) = V/R \quad V_C(t = 0+) = 0$$


What is  $Q_{\max}$ , the maximum charge on the capacitor during the oscillations?

$$\text{A) } Q_{\max} = \frac{V}{R} \sqrt{LC}$$

$$\text{B) } Q_{\max} = \frac{1}{2} CV$$


$$\text{C) } Q_{\max} = CV$$
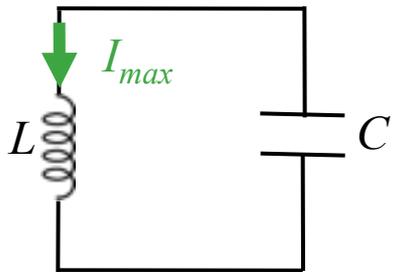
$$\text{D) } Q_{\max} = \frac{V}{R\sqrt{LC}}$$



When  $I$  is *max*  
(and  $Q$  is 0)

$$U = \frac{1}{2} LI^2$$

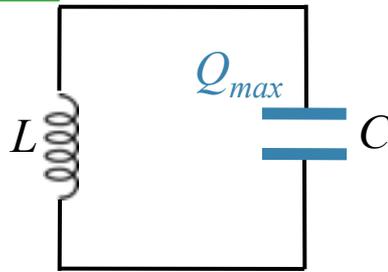

When  $Q$  is *max*  
(and  $I$  is 0)

$$U = \frac{1}{2} \frac{Q_{\max}^2}{C}$$




$$\frac{1}{2} LI^2 = \frac{1}{2} \frac{Q_{\max}^2}{C}$$

$$Q_{\max} = I_{\max} \sqrt{LC} = \frac{V}{R} \sqrt{LC}$$
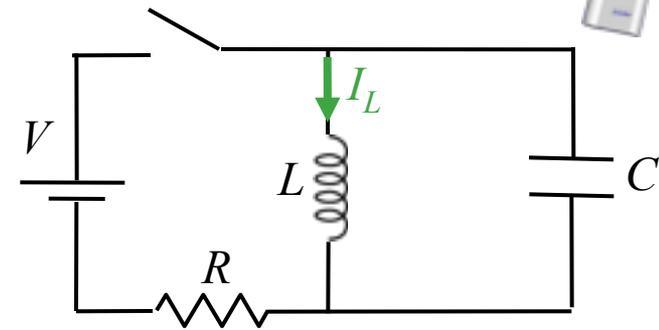
# Follow-Up

The switch in the circuit shown has been closed for a long time. At  $t = 0$ , the switch is opened.

Is it possible for the maximum voltage on the capacitor to be greater than  $V$ ?



**A) YES**

B) NO

$$I_{\max} = V/R$$

$$Q_{\max} = \frac{V}{R} \sqrt{LC}$$

$$Q_{\max} = \frac{V}{R} \sqrt{LC} \rightarrow V_{\max} = \frac{V}{R} \sqrt{\frac{L}{C}} \rightarrow V_{\max} \text{ can be greater than } V \text{ IF: } \sqrt{\frac{L}{C}} > R$$

We can rewrite this condition in terms of the resonant frequency:

$$\omega_0 L > R \quad \text{OR} \quad \frac{1}{\omega_0 C} > R$$

We will see these forms again when we study  $AC$  circuits!