

Unit 22 - Homework Solution

$$\frac{26 - 19}{}$$

$$\Delta V = 120 \text{ V}$$

$$R = 14 \Omega$$

$$a) P = \frac{(\Delta V)^2}{R} = \frac{120^2}{14} = 1029 \text{ J/s} = 1029 \text{ W}$$

$$b) \text{ Energy} = P \Delta t = (1029 \frac{\text{W}}{\text{s}})(5 \text{ h}) = (1.029 \text{ kW})(5 \text{ h}) \\ = 5.145 \text{ kW.h}$$

$$\text{Cost} = (5.145 \text{ kW.h})(5.0 \text{ ¢/kW.h}) \\ = 26 \text{ ¢}$$

$$\frac{26 - 26}{}$$

$$P = 100 \text{ W}$$

$$\Delta V = 120 \text{ V}$$

$$a) E = P \Delta t = (100 \text{ W})(30 \times 24 \text{ h}) = 72 \text{ kW.h}$$

$$\text{Cost} = (12 \text{ ¢/kW.h})(72 \text{ kW.h}) = 864 \text{ ¢}$$

$$b) P = (\Delta V)^2 / R \Rightarrow R = \frac{(\Delta V)^2}{P} = \frac{120^2}{100} = 144 \Omega$$

$$c) P = (\Delta V) I \Rightarrow I = \frac{P}{\Delta V} = \frac{100}{120} = 0.83 \text{ A}$$

d) Yes, resistance of the bulb depends on the current passing through it.