


27-5

$R_1 = 12\ \Omega$

$\Delta V_B = 15\text{ V}$

$R_2 = 15\ \Omega$

$R_3 = 25\ \Omega$

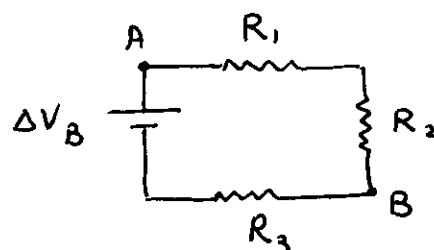

$$R_{tot} = R_1 + R_2 + R_3 = 52\ \Omega$$

$$I_{tot} = \frac{\Delta V_B}{R_{tot}} = \frac{15\text{ V}}{52\ \Omega} = 0.29\text{ A}$$

$$I_{tot} = I_1 = I_2 = I_3$$

$$\Rightarrow \Delta V_1 = R_1 I_1 = (12\ \Omega)(0.29\text{ A}) = 3.48\text{ V}$$

$$\Delta V_2 = R_2 I_2 = (15\ \Omega)(0.29\text{ A}) = 4.35\text{ V}$$

$$\Delta V_3 = R_3 I_3 = (25\ \Omega)(0.29\text{ A}) = 7.25\text{ V}$$

$$\Delta V_1 + \Delta V_2 + \Delta V_3 = 15\text{ V} \checkmark$$

$$= \Delta V_B$$

27-11 R_2, R_3, R_4 are parallel. R_1 is in series with R_{234} .

$$a) \frac{1}{R_{234}} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{50} + \frac{1}{50} + \frac{1}{75} \Rightarrow R_{234} = 18.75\ \Omega$$

$$R_{tot} = R_1 + R_{234} = 100 + 18.75 = 118.75\ \Omega = 119\ \Omega$$

$$b) I_{tot} = \frac{\Delta V_B}{R_{tot}} = \frac{6}{119} = 0.05\text{ A}$$

$$I_{tot} = I_1 = I_{234} \Rightarrow \boxed{I_1 = 0.05\text{ A}}$$

$$\Delta V_1 = R_1 I_1 = (100)(0.05) = 5\text{ V} \Rightarrow \Delta V_2 = \Delta V_3 = \Delta V_4 = \Delta V_B - \Delta V_1$$

$$= 1.0\text{ V}$$

$$I_2 = \frac{\Delta V_2}{R_2} = \frac{1}{50} = 0.02 \text{ A}$$

$$I_3 = \frac{\Delta V_3}{R_3} = \frac{1}{50} = 0.02 \text{ A}$$

$$I_4 = \frac{\Delta V_4}{R_4} = \frac{1}{75} = 0.01 \text{ A}$$

$$I_2 + I_3 + I_4 = 0.05$$

$$= I_1 \quad \checkmark$$

27-24 Similar to 24-11 !


$$R_{tot} = R_1 + R_{234} = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)^{-1}$$

$$= 100 + \left(\frac{1}{50} + \frac{1}{50} + \frac{1}{75} \right)^{-1} \dots$$

27-4

$$\Delta V_{QP} = V_P - V_Q$$

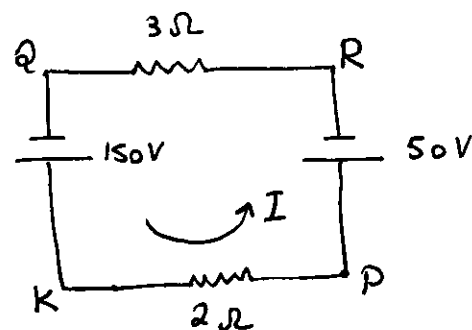Kirchhoff's law : starting from point Q and moving in counter clockwise direction



$$\Delta V_{QK} + \Delta V_{PK} + \Delta V_{RP} + \Delta V_{QR} = 0$$

$$+150 - 2I - 50 - 3I = 0 \Rightarrow I = 20 \text{ A}$$

$$\Delta V_{QP} = \Delta V_{QK} + \Delta V_{KP} = +150 - 2I = 150 - 40 = 110$$

$$\Delta V_{QP} = V_P - V_Q = 100 - V_Q = 110 \Rightarrow V_Q = -10 \text{ V}$$

— 27-19

4

loop ① (moving in counter clockwise direction):

$$\Delta V_{B1} - \Delta V_{B2} - \Delta V_{B3} - R_2 I_2 = 0$$


loop ②: $\Delta V_{B2} - R_1 I_1 = 0$

Point a: $I_2 = I_1 + I_3$


$$\Rightarrow 6 - 5 - 4 - 50 I_2 = 0 \Rightarrow I_2 = -\frac{3}{50} \text{ A} = -0.06 \text{ A}$$

$$5 - 100 I_1 = 0 \Rightarrow I_1 = 0.05 \text{ A}$$
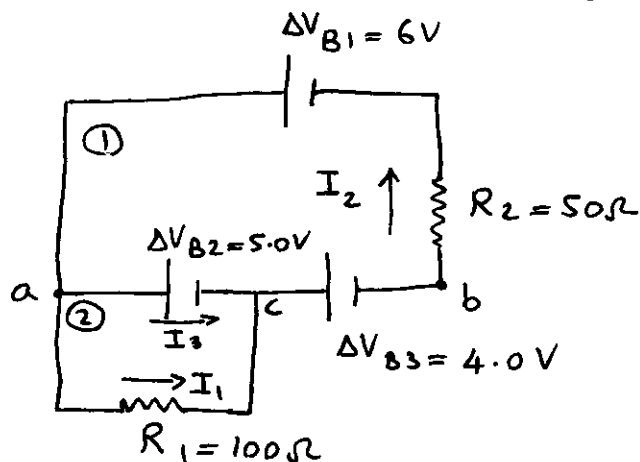
$$I_3 = I_2 - I_1 = -0.06 - 0.05 = -0.11 \text{ A} \quad I_3 = -0.11 \text{ A}$$



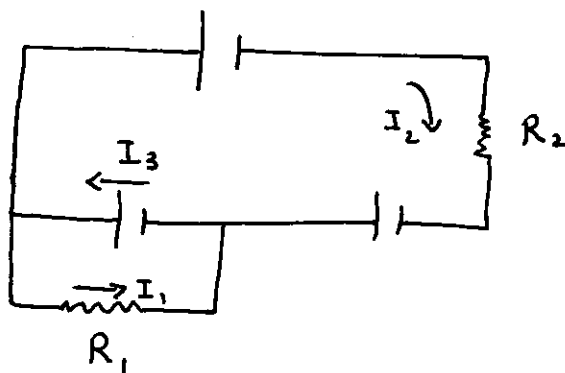the predicted direction
for I_2 was not
right.




$$V_a - V_b = (V_a - V_c) + (V_c - V_b) = 5 + 4 = 9.0 \text{ V}$$

27-9

$$R_1 = R_2 = R_3 = 4.0 \Omega$$

First assign a direction for currents through each resistor.

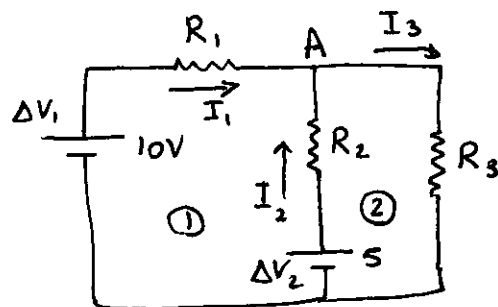(Don't worry about finding the right direction for currents at this step.)



Using Kirchhoff's laws:

loop #1 : (moving in clockwise direction)

$$\Delta V_1 - R_1 I_1 + R_2 I_2 - \Delta V_2 = 0$$

loop #2 :

$$\Delta V_2 - R_2 I_2 - R_3 I_3 = 0$$

for point A: $I_1 + I_2 = I_3$

$$\Rightarrow \begin{cases} +10 - 4I_1 + 4I_2 - 5 = 0 \\ +5 - 4I_2 - 4I_3 = 0 \\ I_1 + I_2 = I_3 \end{cases} \Rightarrow \begin{cases} 5 - 4I_1 + 4I_2 = 0 \Rightarrow I_1 = \frac{5 + 4I_2}{4} \\ 5 - 4I_2 - 4I_3 = 0 \Rightarrow I_3 = \frac{5 - 4I_2}{4} \\ I_1 + I_2 = I_3 \end{cases}$$

$$\Rightarrow \left(\frac{5}{4} + I_2 \right) + I_2 = \frac{5}{4} - I_2 \Rightarrow \boxed{I_2 = 0 \text{ A}}$$

$$\boxed{I_1 = \frac{5}{4} = 1.25 \text{ A}}$$

$$\boxed{I_3 = 1.25 \text{ A}}$$

Predicted directions were correct!