

33 - 9

$$u^{\text{mag}} = u^{\text{elec}} \Rightarrow \frac{1}{2} \frac{B^2}{\mu_0} = \frac{1}{2} \epsilon_0 E^2$$

$$\Rightarrow E = \frac{1}{\sqrt{\epsilon_0 \mu_0}} B = 3 \times 10^8 \times 0.50 = 1.50 \times 10^8 \text{ (V/m)}$$

33 - 12

$$a) B = \frac{\mu_0 I}{2R} = \frac{4\pi \times 10^{-7} \times 100}{2 \times 0.05} = 4\pi \times 10^{-4} \text{ T}$$

$$b) u^{\text{mag}} = \frac{1}{2} \mu_0^{-1} B^2 = \frac{1}{2} \times \frac{1}{4\pi \times 10^{-7}} \times (4\pi \times 10^{-4})^2 = 2\pi \times 10^{-1} \text{ J}$$

$$= 0.2 \pi \text{ (J)}$$

33 - 47

$$\mathcal{E} = \mathcal{E}^{\text{max}} \sin(\omega t - \frac{\pi}{4}) = 30 \sin(350t - \frac{\pi}{4})$$

$$i(t) = (620 \text{ mA}) \sin(\omega t - \frac{3\pi}{4}) = (620 \text{ mA}) \sin(350t - \frac{3\pi}{4})$$

$$a) \mathcal{E} = \mathcal{E}^{\text{max}} \Rightarrow \sin(\omega t - \frac{\pi}{4}) = 1 \Rightarrow \omega t - \frac{\pi}{4} = \frac{\pi}{2}$$

$$\Rightarrow \omega t = \frac{3\pi}{4} \Rightarrow t = \frac{3\pi}{4\omega} = \frac{3\pi}{4 \times 350} = 6.73 \times 10^{-3} \text{ (s)}$$

$$= 0.00673$$

$$b) I = I^{\text{max}} \Rightarrow \sin(\omega t - \frac{3\pi}{4}) = 1 \Rightarrow \omega t - \frac{3\pi}{4} = \frac{\pi}{2}$$

$$\Rightarrow t = \frac{1}{\omega} \frac{5\pi}{4} = \frac{1}{350} \frac{5\pi}{4} = 0.011 \text{ s}$$

c) From parts (a) and (b), you can see that I becomes maximum later than $\mathcal{E}$. In other words, $\mathcal{E}$ leads I . This happens when you have an inductor.

$$d) I^{max} = \frac{\mathcal{E}^{max}}{X_L} = \frac{\mathcal{E}^{max}}{L\omega} \Rightarrow 0.620 = \frac{30.0}{L(350)}$$

$$\Rightarrow L = 0.138 \text{ H} = 138 \text{ mH}$$

33 - 50

a) $R = 200 \Omega$, $C = 15.0 \mu\text{F}$, $f = 60.0 \text{ Hz}$, $\mathcal{E}^{max} = 36.0 \text{ V}$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{R^2 + \left(\frac{1}{C\omega}\right)^2} = \sqrt{200^2 + \left(\frac{1}{15 \times 10^{-6} \times 2\pi \times 60}\right)^2} = 267 \Omega$$


$$\tan \phi = \frac{-X_C}{R} = -\frac{1}{C\omega R} = -\frac{1}{15 \times 10^{-6} \times 2\pi \times 60 \times 200} \Rightarrow \phi = -41.5^\circ = 0.724 \text{ (rad)}$$

$$I = I^{max} \sin(\omega t - \phi) = \frac{\mathcal{E}^{max}}{Z} \sin(\omega t - \phi)$$

$$I = \frac{36}{267} \sin(2\pi \times 60 t + 0.724) = (0.135 \text{ A}) \sin(120\pi t + 0.724)$$

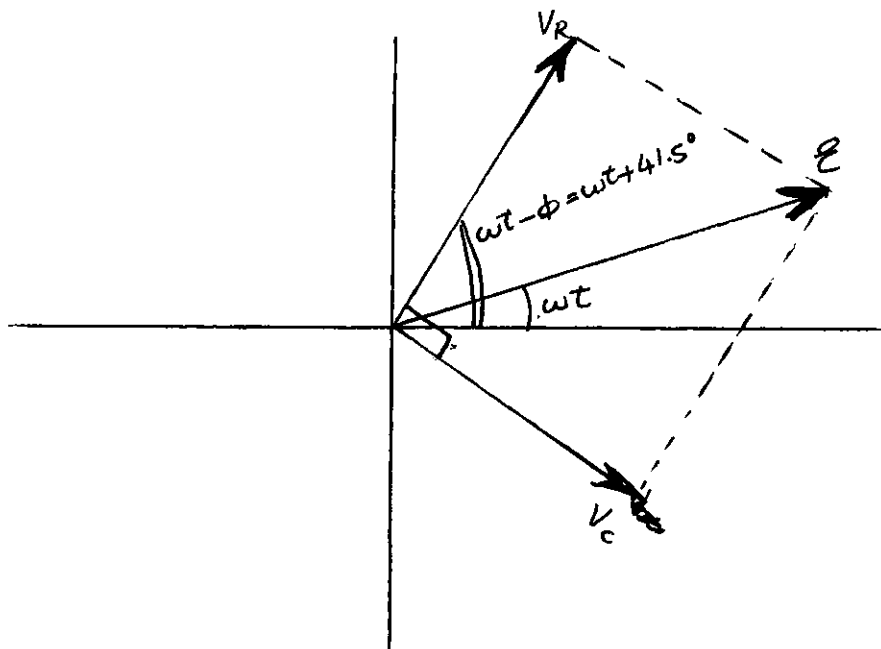b) $V_R^{max} = R I^{max} = 200 \times 0.135 = 27 \text{ V}$

$$V_C^{max} = X_C I^{max} = 177 \times 0.135 = 23.9 \text{ V}$$



1 cm = 6 V

$$a) X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{(24 \times 10^{-6})(2\pi \times 400)} = 16.6 \Omega$$

$$b) Z = \sqrt{R^2 + (X_L - X_c)^2}$$

$$X_L = L(2\pi f) = (150 \times 10^{-3}) \times 2\pi \times 400 = 377 \Omega$$

$$\Rightarrow Z = \sqrt{220^2 + (377 - 16.6)^2} = 422 \Omega$$

$$c) I^{max} = \frac{\mathcal{E}^{max}}{Z} = \frac{220}{422} = 0.521 A$$

$$d) C_{eq} < C_1 \Rightarrow X'_c > X_{c1} \quad X_c \text{ increases.}$$

$$C_{eq} = \frac{1}{2} C \Rightarrow X'_c = 2 X_{c1}$$

e)

$$Z' = \sqrt{R^2 + (X_L - \underbrace{2X_c}_{23.2})^2} < Z \quad Z \text{ decreases.}$$

$\downarrow$ 377 $\downarrow$ 23.2

f) I increases because impedance (Z) decreases.