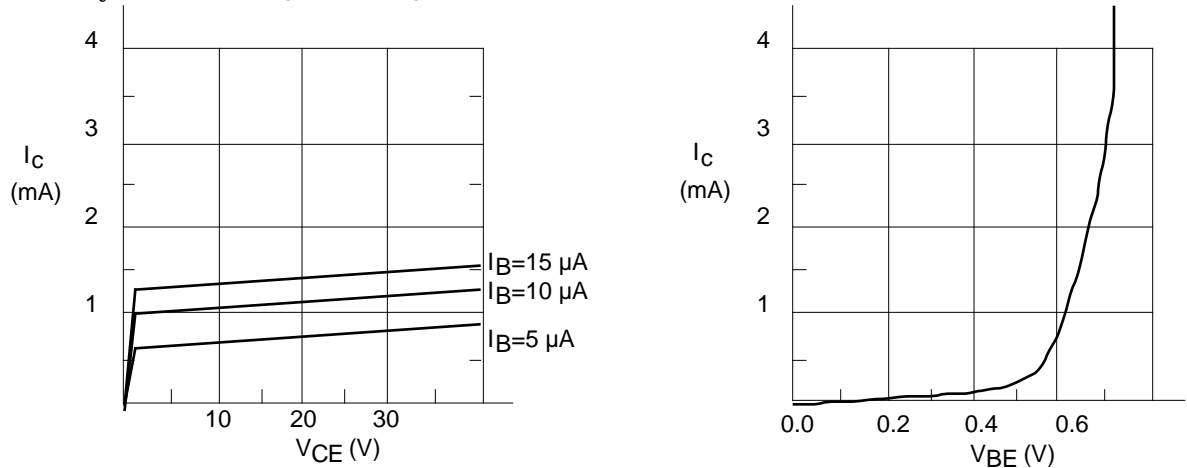


Physics 326 Final Exam
Aug. 4, 1998

Time: 3 hrs.


1. An 1 mH inductor has internal resistance of 5 Ω . This inductor is connected to the output of the function generator whose output impedance is 50 Ω . The function generator is adjusted so that its output would be 10 V peak-to-peak with a load of infinite impedance.
- (a) What peak-to-peak voltage would you predict when the frequency is 1 Hz? [2]
 (b) What peak-to-peak voltage would you predict when the frequency is 31.4 kHz? [4]
 (c) What peak-to-peak voltage would you predict when the frequency is 3.14 MHz? [4]

2. Use the following idealized characteristic curves of an npn bipolar junction transistor to estimate $h_{FE} (dc)$, $h_{fe} (ac)$, h_{ie} and h_{oe} . Justify your estimates by calculations or graphical analysis. Assume $V_{CE} = 10$ V, $I_C = 1.1$ mA. [10]




3. Using the transistor of problem 2, design a one-transistor, common-emitter amplifier with the emitter resistor bypassed for maximum gain. Let $V_{CC} = 20$ V and make the quiescent collector current about 1 mA. Put the low-frequency roll-off around 20 Hz. Estimate the AC voltage gain. [10]

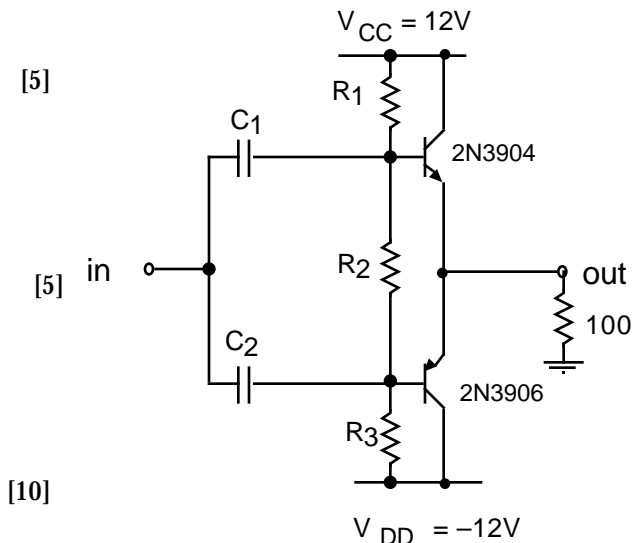4. (a) Find R_1 , R_2 and R_3 which will minimize crossover distortion in the push-pull circuit. [5]
 (b) A 1 kHz signal with 20 V peak-to-peak is applied to the input but the output is less than 20 V_{pp} despite complete elimination of crossover distortion. Why? Estimate the expected attenuation. [5]



5. You have a JFET with $V_{GS(off)} = -3.5$ V and $I_{DSS} = 11$ mA. Design a source follower using self bias. What is its amplification? Discuss in what way or ways it is most likely to be useful. [10]

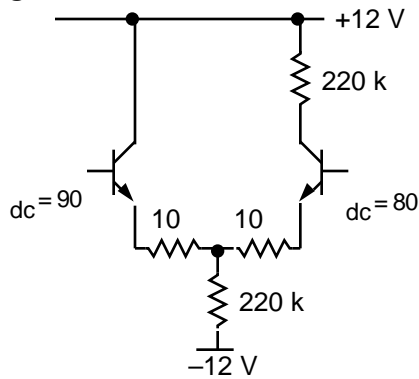
6. Below is the circuit for a differential amplifier using two transistors with (left) $\beta = 90$ and (right) $\beta = 80$.



- Find the common-mode gain. [2]
- Find the differential gain. [2]
- Calculate the common mode rejection ratio in dB. [2]
- What do you expect the input bias current, $I_{in(bias)}$, to be? [2]
- What do you expect the input offset current, $I_{in(off)}$, to be? [2]

- Design an amplifier with non-inverting voltage feed-back and a 741 or equivalent operational amplifier with a voltage gain of 25. Estimate its input impedance. [5]
 - Design an amplifier with inverting voltage feed-back and a 741 or equivalent operational amplifier with a voltage gain of -25. Estimate its input impedance. [5]

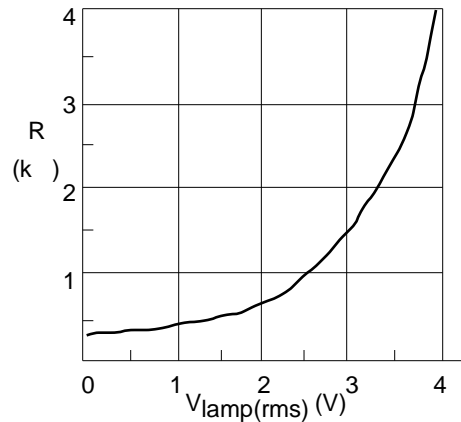- Design Wien bridge sine wave oscillator to produce a 3 V peak-to-peak 100 kHz sine wave output. Use a lamp in the feedback circuit with the following resistance characteristics.




[10]

- Design an active band pass filter using a pair of two-pole active filters. The pass band should be between 100 Hz and 10 kHz.

- Specify values for resistors and capacitors conforming to a Butterworth filter design. [5]
- Sketch the Bode plot (log-log) of output voltage vs. frequency for two decades above and two decades below the critical frequency. (Label axes quantitatively) [5]

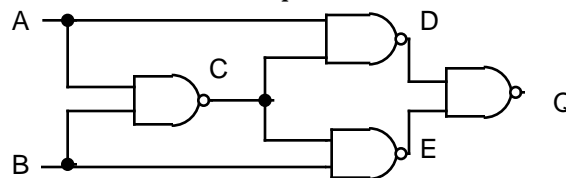- Find the function of the following circuit by making a truth table showing the logic values at C, D, E and Q for all values of A and B inputs. [10]



End