

## LAB 3

### Transistor Fundamentals

Reading: Malvino: Ch. 6 through Ch. 9.

You will study bipolar junction transistors (BJTs) in this lab. Most of the exercises will be done with the 2N3904 NPN transistor. The terminal connections are illustrated in Fig. 3.1 below.



Fig 3.1

#### 1. Using Transistor Curve Tracers to Measure Operating Characteristics

a) Determine the collector characteristics,  $I_C$  vs.  $V_{CE}$  with  $I_B$  as a parameter. The 571 curve tracer has a printer interface to let you make a hard copy of your curves. Save the curves in your lab book and keep the particular transistor belonging to those curves. Suggested settings for the curve tracer are listed below.

Function	Acquisition
NPN	
Vce max	20 V
Ic max	20 mA
Ib/step	10 $\mu$ A
Steps	10
R load	100 Ohm
P max	2 Watt

The series resistor is to limit power dissipation. The maximum ratings are

$V_{CE}$	40 V
$V_{CB}$	60 V
$V_{EB}$	6 V
$I_C$	200 mA

The slope of the collector curves is a measure of how imperfectly the transistor acts as a current source. The parameter  $h_{oe}$  is called the output admittance. In the h-equivalent model of the transistor the collector-emitter output is modelled by an ideal current source in parallel with a

resistance;  $h_{oe}$  is the inverse of this resistance. Measure  $h_{oe}$  from your curves. What is the accuracy and over what range of  $V_{CE}$  is this result valid?

**b) Plot the transfer characteristics  $I_C$  vs  $I_B$ .**

Use the cursor to read values of  $I_C$  for the ten  $I_B$  values at  $V_{CE} = 0, 5$  and  $15$  V. Plot these values on a graph.

Calculate the dc current gain  $h_{FE} = \beta_{dc} = I_C / I_B$  at  $I_C = 1$  mA,  $V_{CE} = 5$  V.

Compare this value of  $\beta_{dc}$  with that measured by the multi-meter. At this point find another transistor with  $\beta_{dc}$  at least 20% different. Note the values of  $h_{FE}$  measured by the multi-meter for both transistors, label them and keep for later use.

**c) Measure  $I_C$  vs.  $V_{BE}$**

Connect the base and collector of the first transistor together as shown in Fig. 3.2. Measure its diode characteristic curve using the method of Lab 2. This will give you  $I_C$  vs  $V_{BE}$ . The effective emitter resistance should be approximately  $r_e' = (25 \text{ mV}) / I_C$ . How closely does the transistor obey this relationship?



Fig 3.2

## 2. Transistor Biasing

a) Assume that  $V_{BB} = 9\text{V}$  in the circuit of Fig 3.3. For homework you should calculate what values of  $R_B$  will

- i) put  $V_C$  at 7.5 V,
- ii) put  $V_C$  at 10 V
- iii) put  $V_C$  at 1 V.

Note: Use the breadboard supply for  $V_{CC}$  and an external supply or a battery for  $V_{BB}$

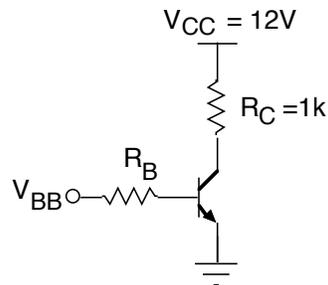


Fig 3.3

b) Find standard resistor values closest to those calculated in (a), build the circuit and measure  $V_C$  for each case. Make a table of calculated  $R_B$ , actual  $R_B$  and the expected and actual values of  $V_C$ . Mark any unexpected deviations from what was expected and hazard and explanation.

Now replace the transistor with the other one with a different  $\beta_{dc}$ . Compare  $V_C$  with that of the first transistor leaving  $R_B$  the same in both cases. Does the change match your predictions based on the measured values of  $\beta_{dc}$ ?

c) Investigate how well the transistor circuit acts as a current source. Measure the current flowing through the collector resistor for  $R_C = 500\ \Omega$  and  $2\ \text{k}\Omega$ . Model the response with a Norton equivalent circuit.

d) Design and build an emitter-biased LED driver to switch off and on with 0 and 5V.

e) Design a voltage divider biased circuit (Fig 3.4) with the following specifications:  $V_{CC} = 12\ \text{V}$ ,  $I_C = 2\ \text{mA}$ ,  $V_C = 7.5\ \text{V}$  and  $V_E = 1\ \text{V}$ . Build your circuit. Compare calculated and measured values  $V_{BB}$ ,  $V_E$  and  $V_C$  for both of your transistors.

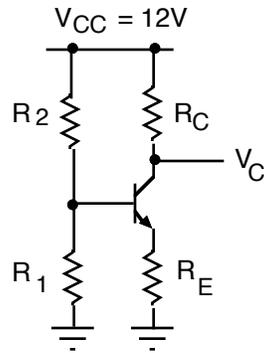


Fig 3.4

### Homework Problems

1. Calculate the resistor values for part 2(a).
2. Design the voltage-divider bias circuit of part 2(e) and write a computer program or make a spreadsheet that calculates the resistor values. Your input parameters are  $V_{CC}$ ,  $I_C$ ,  $V_C$  and  $V_{CE}$ .
3. Do the algebra you will need for part 2(c) to obtain the Norton equivalent circuit from the currents obtained using the two values of  $R_C$ ; i.e., derive the equations for  $I_N$  and  $R_N$  in terms of the quantities you will measure.