

Physics 102

Lecture 9

Mon. Sept. 27, 2004

Ref: ch. 21.

• Electric Current.

— A flow of electric charge.

Definition of electric current I :


$$I = \frac{\Delta Q}{\Delta t}$$

 ΔQ — amount of charge flowing through a wire in Δt .

 Unit: $A = C/s$ charge per unit time
 (ampere)

• What drives the flow?

— potential difference (Voltage)

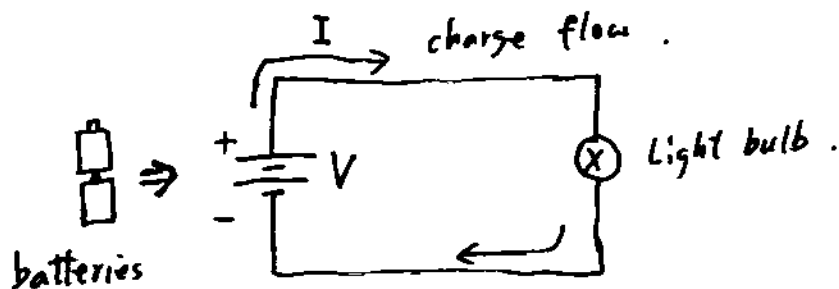

real conductor. (NOT ideal)

- Ohm's Law. A wire has a resistance R to the electric current

$$V = IR.$$

$$R = \frac{V}{I}.$$


Resistance. unit: Ohm (Ω)

When a device obeys Ohm's law, it is said to be ohmic.

OR it is a resistor.

- Resistivity. ρ . of a material. ρ a property of the material

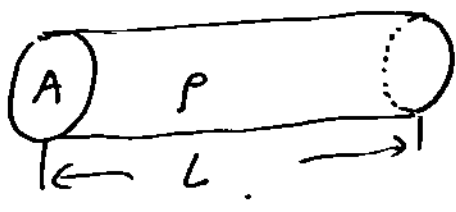for a wire made of material with resistivity ρ .




the Resistance :

$$R = \rho \frac{L}{A}.$$

$$R \propto L$$

$$R \propto \frac{1}{A}.$$

- Resistors in Series

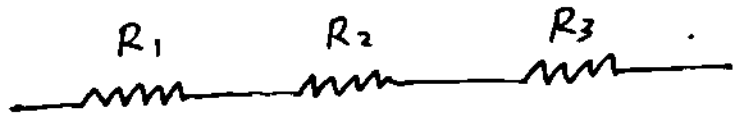

same as.




Series

$$R = R_1 + R_2 + R_3$$

$$(R > R_i)$$

Easy to understand :
 (Imagine 3 wires connected in series the lengths add)
 $L = L_1 + L_2 + L_3.$

- Resistors in Parallel

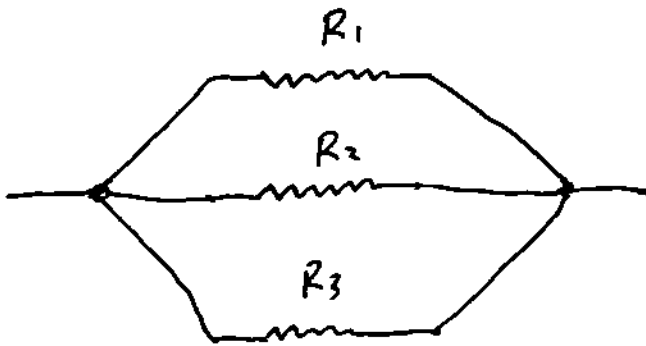

Same as

R .



Now: for parallel


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$(R < R_i.)$$


Imagine, the cross section area effectively becomes larger.

$\therefore R$ becomes smaller.

e.g.:

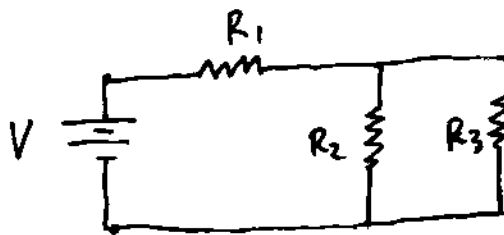


equivalent to

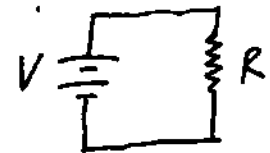

$$R = R_1 + R_{23}$$

$$= R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

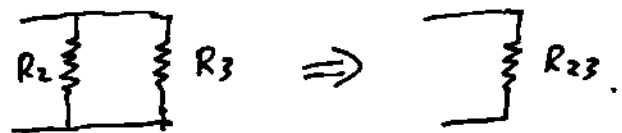

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{R_2 + R_3}{R_2 R_3}$$


$$R_{23} = \frac{R_2 R_3}{R_2 + R_3}$$

eg. 21-7. p. 693.

given: $R = 200 \Omega$.

$\mathcal{E} = 12.0 \text{ V}$.

find: $I = ?$

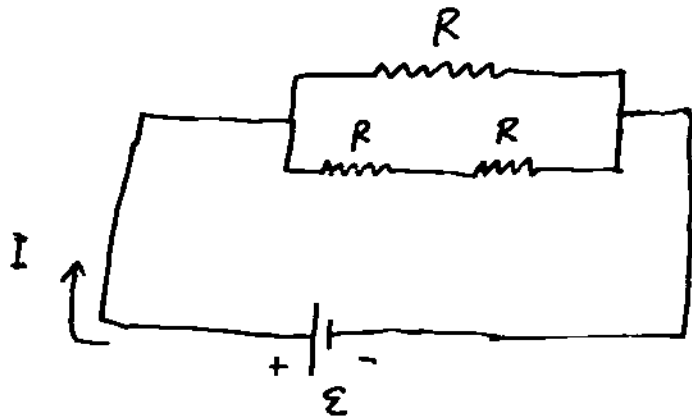

Total resistance:

$$R_T = R \parallel (R + R).$$

$$\frac{1}{R_T} = \frac{1}{R} + \frac{1}{R+R}.$$

$$\frac{1}{R_T} = \frac{1}{R} + \frac{1}{2R} = \frac{3}{2R}$$

$$R_T = \frac{2R}{3}.$$

$$\therefore I = \frac{V}{R_T} = \frac{V}{\frac{2R}{3}} = V \cdot \frac{3}{2R}$$

$$= 12.0 \text{ (V)} \times \frac{3}{2 \times 200 \Omega}.$$

$$= 0.0900 \text{ A}$$


\mathcal{E} — electromotive force (emf)
of the battery.

(It creates a vollege of \mathcal{E} volts
at the terminals of the battery)

• Power in an electric circuit .

When a charge ΔQ moves across the resistor .

the change in potential energy is:

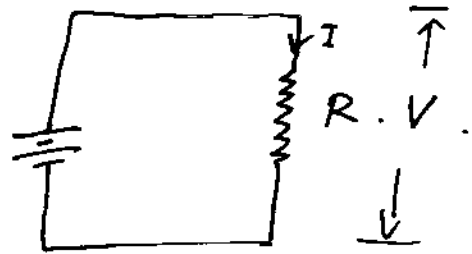

$$\Delta U = \Delta Q \cdot V .$$

The power :
$$P = \frac{\Delta U}{\Delta t} = \frac{\Delta Q}{\Delta t} \cdot V = IV .$$


$$\therefore \boxed{P = IV .}$$

Ohm's Law :
$$I = \frac{V}{R} , \quad V = IR .$$

$$\therefore \boxed{P = I^2 R = \frac{V^2}{R}}$$

• Demo. ① .

Series connection of 3 light bulbs :

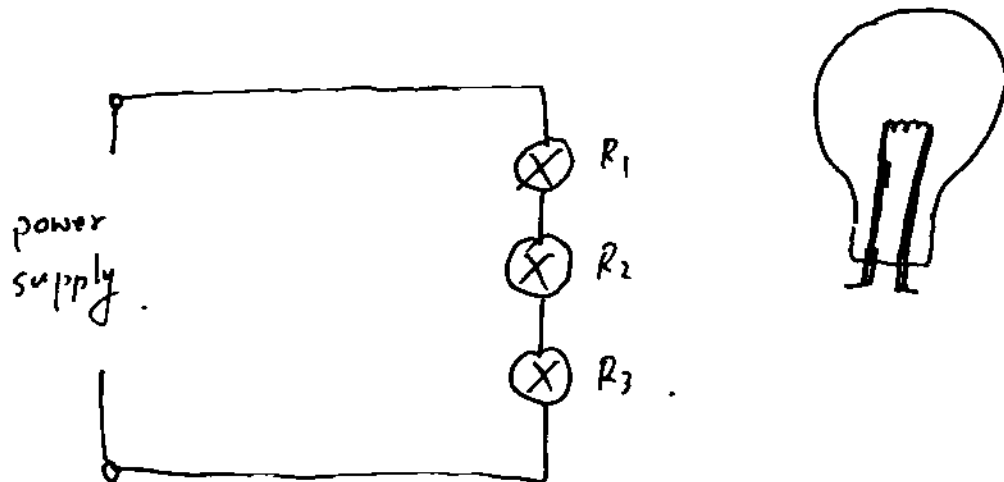

When one of the 3 bulbs is broken,

~~the~~ the other two also go off .

Why? — the same current flows through .

If the current is "blocked" at one location,


~~it - is - stop can not continue to flow.~~

It can not flow any more .

i.e. $I = 0$ everywhere .

• Demo (2).

Parallel connection of 3 light bulbs.

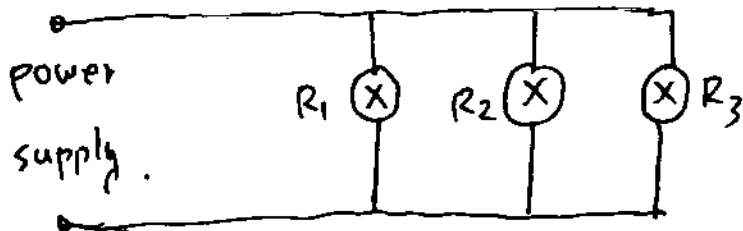

When a bulb is ~~broken~~, broken
the other two are still on.

Why? — The currents are "independent".

The voltages are the same. $V_1 = V_2 = V_3$

• Demo (3).

2 light bulbs : 60W and 25W . { 110V. }

which one is brighter? parallel :

Series .

why?