

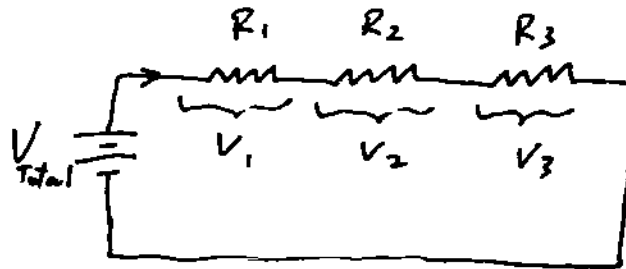
Physics 102 .

Lecture 10 .


Wed. Sept. 29. 2004

• Parallel and series connections :

1. Series :

Same current : $I_1 = I_2 = I_3 = I$.Voltages add : $V_{Total} = V_1 + V_2 + V_3$.(Resistance : $R = R_1 + R_2 + R_3$)

2. Parallel :

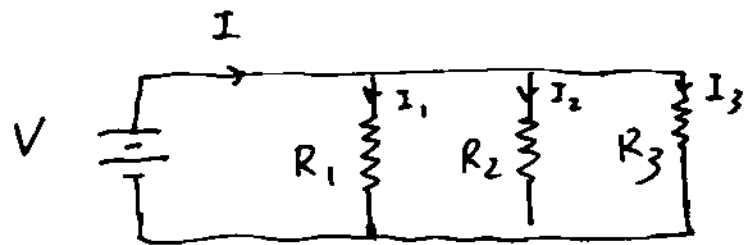Same voltage : $V_1 = V_2 = V_3 = V$ currents add : $I = I_1 + I_2 + I_3$.(Resistance : $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$)

Physics 102


Lecture 10.

Demo: 60W and 25W light bulbs.


Question: which one is brighter?

when the voltage across each bulb is 110V
the 60W bulb is brighter.

e.g.: parallel connection

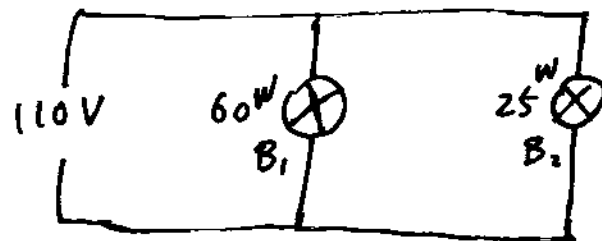

What about series?

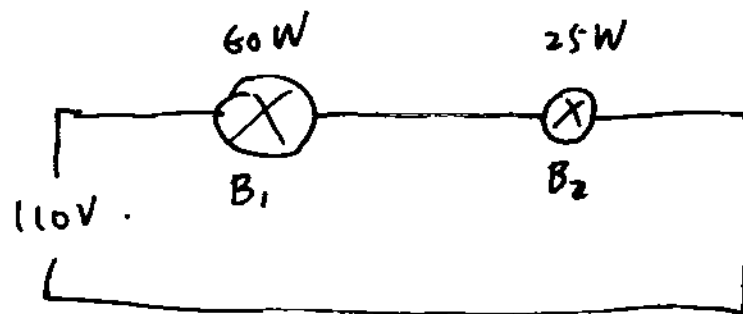

The 25W bulb is brighter!

Why?

what does the label "60W, 110V" mean? (0-3)

$$P = 60 \text{ W} \quad \text{when } V = 110 \text{ V}.$$

$$\text{Then } P = \frac{V^2}{R}, \quad R_1 = \frac{V_1^2}{P_1} = \frac{(110 \text{ V})^2}{60 \text{ W}} = 202 \Omega.$$

for the 25W bulb:

$$R_2 = \frac{V_2^2}{P_2} = \frac{(110 \text{ V})^2}{25 \text{ W}} = 484 \Omega.$$


Now, when they are connected in series.

$$V_1 \neq V. \\ \therefore V_2 = V_1 + V_2.$$

$$V_1 < 110 \text{ V}$$

$$V_2 < 110 \text{ V}.$$
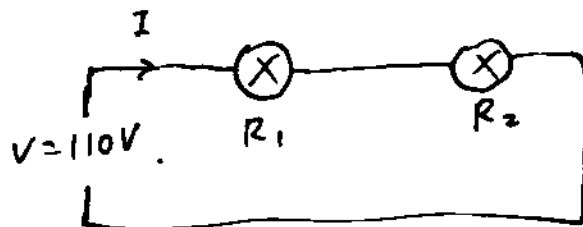
$$P_1 \neq 60 \text{ W}, \quad P_2 \neq 25 \text{ W}.$$



$$\text{Total Resistance: } R = R_1 + R_2 = 686 \Omega.$$

$$\text{Total current: } I = \frac{V}{R} = \frac{110 \text{ V}}{686 \Omega} = 0.160 \text{ A} = I_1 = I_2$$

$$\text{Voltage } V_1 = R_1 I_1 = 202 \Omega \times 0.160 \text{ A} = 32.3 \text{ V}.$$

$$V_2 = R_2 I_2 = 484 \Omega \times 0.160 \text{ A} = 77.4 \text{ V}.$$

Power:

$$P_1 = I_1 V_1 = 0.160 \text{ A} \times 32.3 \text{ V} = 5.15 \text{ W}.$$


$$P_2 = I_2 V_2 = 0.160 \text{ A} \times 77.4 \text{ V} = 12.4 \text{ W}$$

$\therefore P_2 > P_1$. The 25W bulb is more powerful.

• Kirchoff's Rules .

1. The junction rule .

for any point in a circuit . such as A .

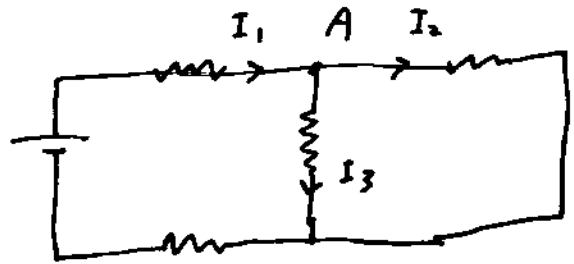

current in = current out .

i.e . $I_1 = I_2 + I_3$. (charge conservation)


OR : $I_1 - I_2 - I_3 = 0$.

The algebraic sum of all currents meeting at any junction, equal to zero .

Sign of current : in (+)
out (-) .

2. The loop rule .

In any closed loop .

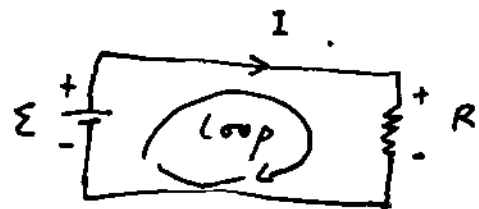

the algebraic sum of the voltages is equal to zero .

Sign : up (+)
down (-) .

↑
energy conservation .