

## Physics 102.

## Lecture 12.

## • Alternating Currents

$I(t)$ ,  $V(t)$  — time dependent

can be described by sinusoidal functions


e.g.:  $V = A_v \cos(\omega t + \varphi_v)$

$$I = A_i \cos(\omega t + \varphi_i)$$

$\omega$  — angular frequency ( $\omega = 2\pi f$   
 $f$  — frequency)

$A$  — Amplitude

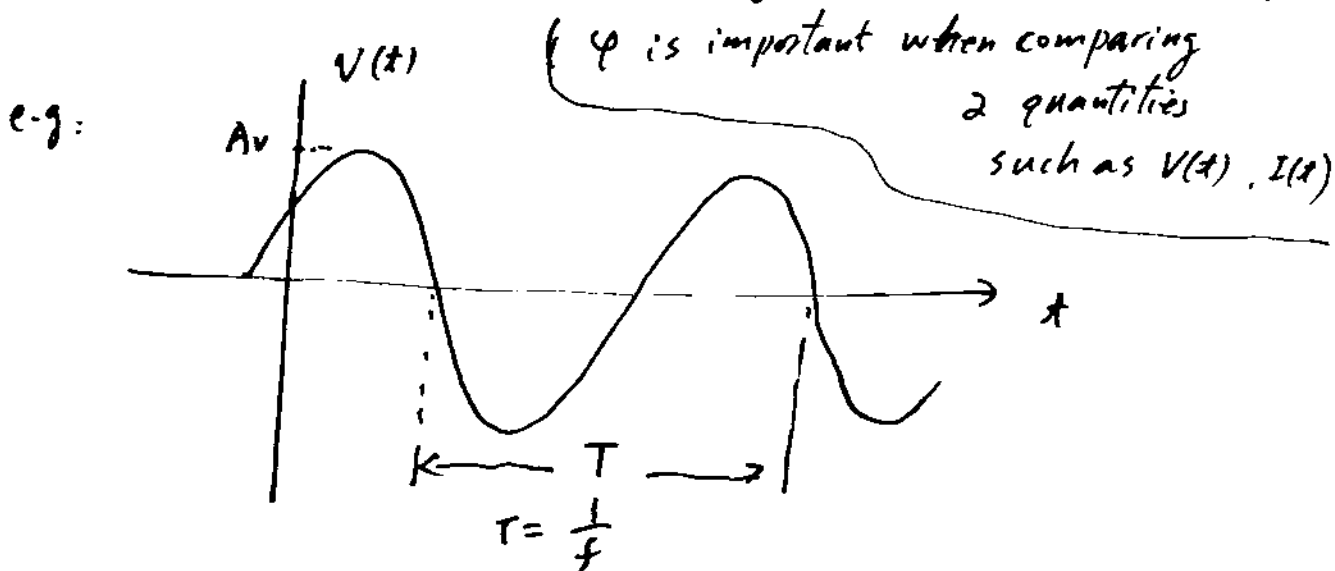$\varphi$  — initial phase (phase shift — relative to  $\varphi=0$ )



- e.g. line voltage in Vancouver:

$$f = 60 \text{ Hz}, \quad \omega = 2\pi f = 120\pi \text{ (rad/sec)}.$$

$$A = 155 \text{ Volts. (NOT 110 volts).}$$

- what is 110 volts?

— RMS value (Root Mean Square).

$$V_{\text{rms}} = \sqrt{(V^2)_{\text{ave}}} = \frac{A_v}{\sqrt{2}} \approx 70\% A_v.$$

Math:  ~~$(V^2)_{\text{ave}}$~~   $(V^2)_{\text{ave}} = \frac{\int_0^T V(t) dt}{T}$

$$= \frac{\int_0^T A_v^2 \cos^2(\omega t) dt}{T}$$

$$= \frac{A_v^2}{2}.$$

$$\therefore V_{\text{rms}} = \sqrt{\frac{A_v^2}{2}} = \frac{A_v}{\sqrt{2}}.$$

- Why do we use the RMS value to describe the level of an ac voltage?

— for comparison with DC voltage in terms of power.

$$\text{power} = VI = \frac{V^2}{R} = I^2 R.$$

The average power of ac:  ~~$P_{\text{ave}} \propto V^2$~~

$$P_{\text{ave}} = (V^2)_{\text{ave}} / R = \frac{V_{\text{rms}}^2}{R} = I_{\text{rms}}^2 R.$$

DC power:  $P = \frac{V^2}{R} = I^2 R.$

∴ The line voltage with  $V_{\text{rms}} = 110$  volts delivers the same power as a DC voltage  $V_{\text{dc}} = 110$  volts.

- Phasor :

In an ac circuit,  $\omega$  is the same everywhere.  
We only need  $A$  and  $\varphi$  to describe an AC voltage or current.

Idea:  $x = A \cos(\omega t + \varphi)$

can be graphically described by a rotating

Vector  $\vec{A}$  :


The  $x$ -component:

$$x = A \cdot \cos \theta$$

When  $\vec{A}$  is rotating at a constant angular velocity  $\omega$  and with an initial angle  $\varphi$ :

$$\theta = \omega t + \varphi$$


$$\theta = \omega t + \varphi$$

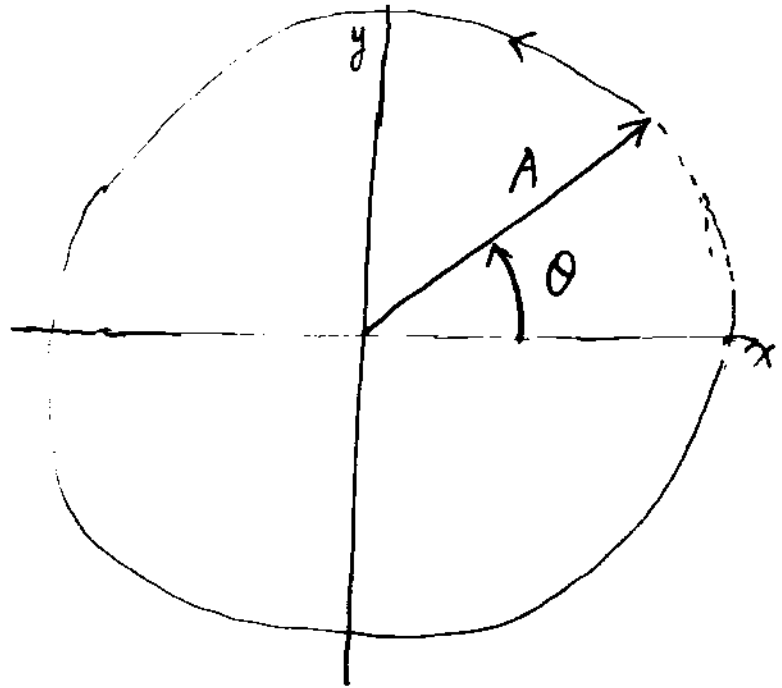

Then:  $x = A \cdot \cos(\omega t + \varphi)$

( $x$  can be  $V(t)$  or  $I(t)$ )

e.g. an RC circuit:

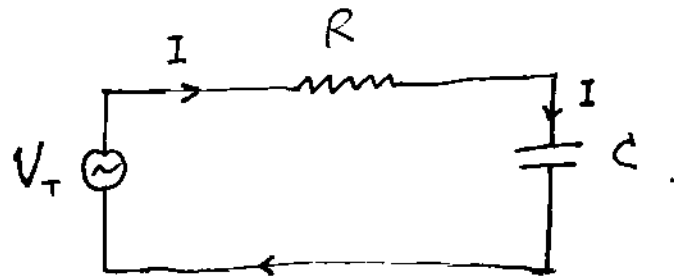

—  $I$  is the same everywhere (because of the series connection).

$\therefore$  choose the phase of  $I$  to be 0. ( $\varphi_I = 0$ )

$$I = A_I \cdot \cos(\omega t) \quad (\text{use it as the phase reference}).$$

— The voltage across  $R$ :

$$V_R = I R = R A_I \cos(\omega t)$$

$\therefore V_R$  and  $I$  are in phase.

— The voltage across  $C$ : (NOT simple multiplication ~~!!!~~)

$$I = \frac{dQ}{dt} = C \cdot \frac{dV_C}{dt} \quad (Q = C V_C).$$

$$\text{Then: } \frac{dV_C}{dt} = \frac{1}{C} \cdot A_I \cdot \cos(\omega t).$$

$$V_C = \frac{1}{\omega C} A_I \sin(\omega t) = \frac{1}{\omega C} A_I \cdot \cos(\omega t - \frac{\pi}{2}) \\ = A_{V_C} \cdot \cos(\omega t + \varphi_{V_C})$$

$$\therefore \varphi_{V_C} = -\frac{\pi}{2}. \quad A_{V_C} = \frac{1}{\omega C} A_I.$$


Meaning of  $\phi_{V_c} = -\frac{\pi}{2}$  :

There is a phase shift between the current and voltage of the capacitor !


i.e. the voltage lags by  $\frac{\pi}{2}$ .

OR The current leads by  $\frac{\pi}{2}$ .

In a phasor representation :

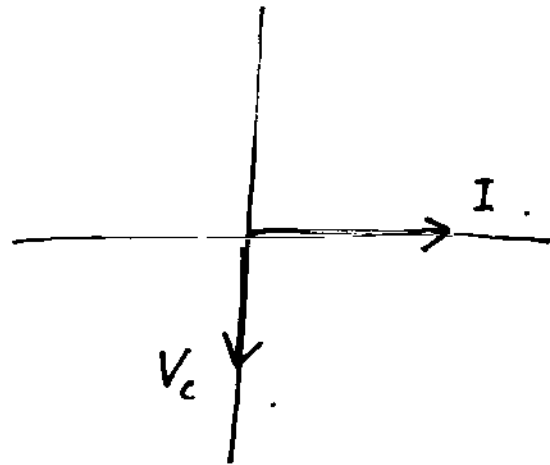

OR.

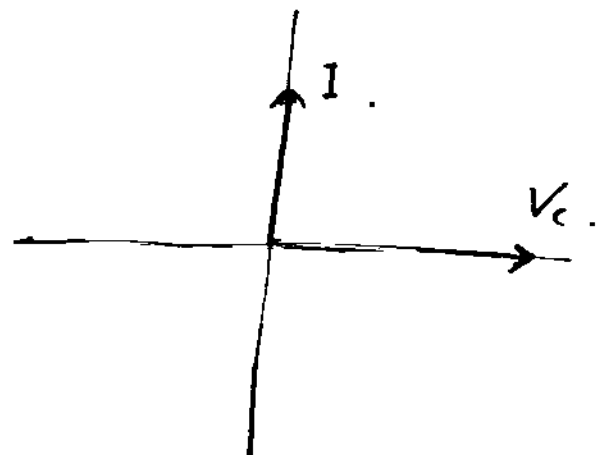

( "ICE" )

for a capacitor.

I goes first, V is behind.  
(E)

— define  $X_C = \frac{1}{\omega C}$

as the reactance of the capacitor.

(just like the resistance of a resistor).

$$V_{\max} = X_C \cdot I_{\max} \cdot \left( \begin{array}{l} \text{factor} \\ \text{for capacitors} \end{array} \right)$$

— The voltages  $V_R$ ,  $V_C$  and  $V_T$ .

In the phasor diagram, use  $I$  as the reference.

$$V_T = V_R + V_C.$$

Vector sum!

