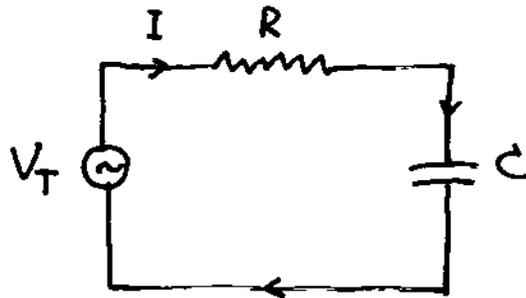


Lecture 13 .

- RC circuit as a low pass filter



We are interested in the relationship among  $I(t)$ ,  $V_R(t)$ ,  $V_C(t)$ ,  $V_T(t)$ .

$I$  — common, choose  $\varphi_I = 0$  . as phase reference .

$$I = A_I \cos(\omega t)$$

$$V_R = A_{VR} \cdot \cos(\omega t) , \quad A_{VR} = R \cdot A_I .$$

$$V_C = A_{VC} \cdot \cos(\omega t - \frac{\pi}{2}) , \quad A_{VC} = \frac{1}{\omega C} \cdot A_I = X_C \cdot A_I .$$

$$V_T = A_{VT} \cdot \cos(\omega t + \varphi_T)$$


Since  $V_T = V_R + V_C$

In the phasor diagram .

this is a vector sum .

$$\therefore A_T = \sqrt{A_{VR}^2 + A_{VC}^2}$$
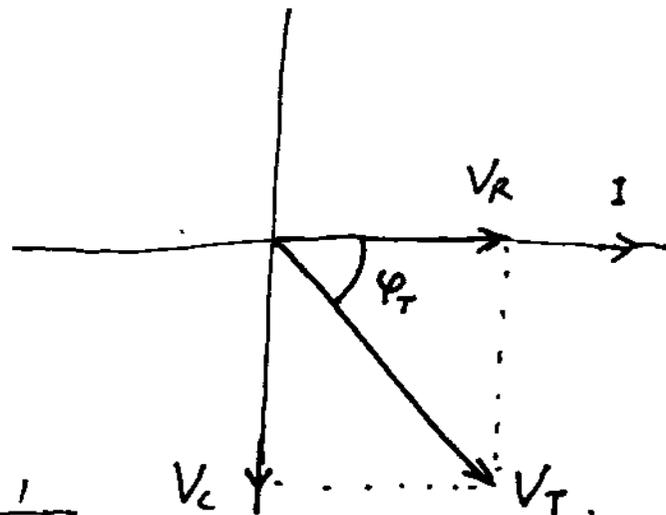
$$\varphi_T = -\tan^{-1} \frac{A_{VC}}{A_{VR}} = -\tan^{-1} \frac{1}{\omega RC} .$$



• low- and high- frequency behaviours.

(Due to  $X_C = \frac{1}{\omega C}$ )

Capacitor has a small reactance at high frequencies.

e.g. when  $\omega = 0$ , it's DC.

$X_C \rightarrow \infty$ . the current cannot get through continuously because it will stop when the capacitor is fully charged.

In the RC circuit,

low-f: when  $\frac{1}{\omega C} \gg R$ , i.e.,  $\omega \ll \frac{1}{RC}$ .


amplitudes:

$$V_C \gg V_R.$$

$$\left. \begin{array}{l} I \cdot \frac{1}{\omega C} \\ IR \end{array} \right\}$$

i.e.  $V_C \approx V_T$ .

$$\therefore V_T = V_C + V_R.$$

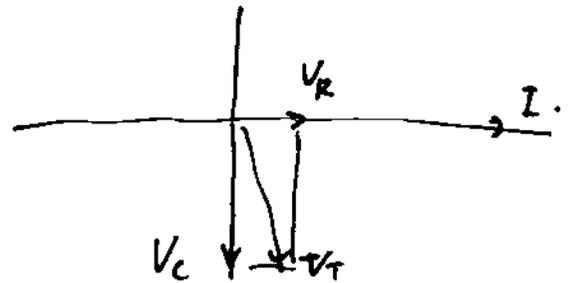


high-f: when  $\frac{1}{\omega C} \ll R$ . i.e.,  $\omega \gg \frac{1}{RC}$ .

$$V_R \gg V_C.$$


$$V_T \approx V_R,$$

~~$$V_C \ll V_T.$$~~

$$V_C \ll V_T.$$

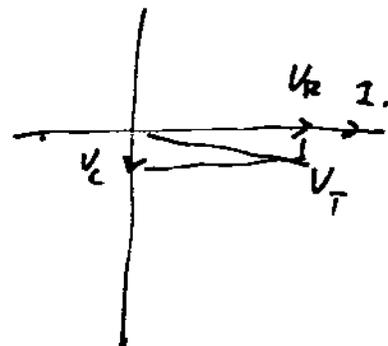

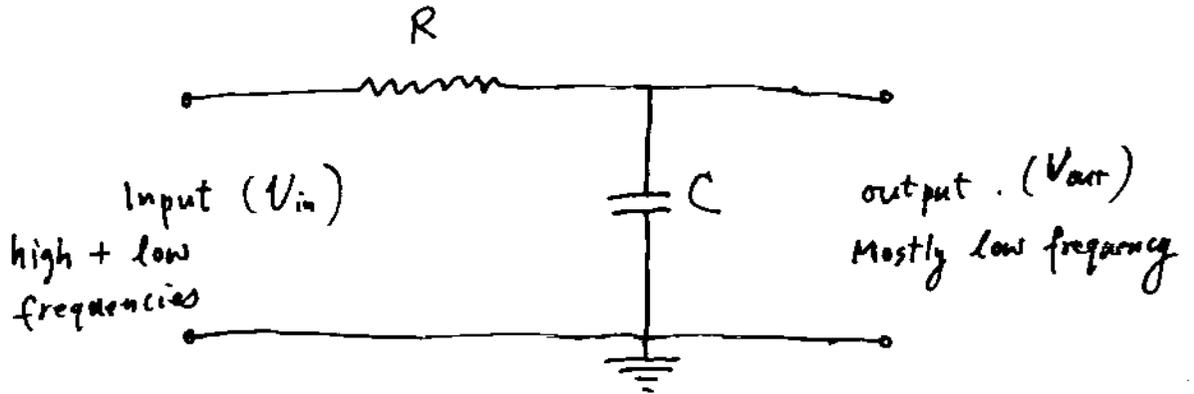- So, we can use the RC circuit as a low pass filter.



why? (physically)

Explanation: It takes time to charge/discharge.





\* at low-freq:

We have long enough time to charge up the capacitor.

~~before it~~

\* at high-freq.

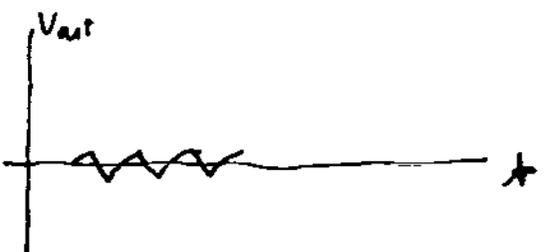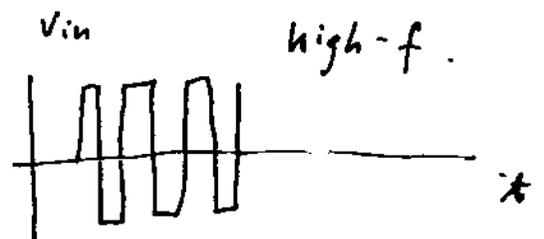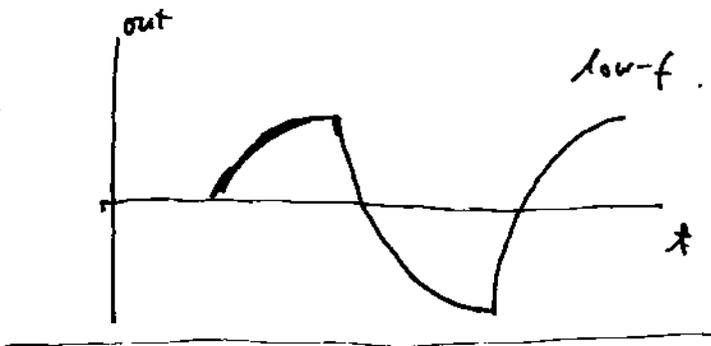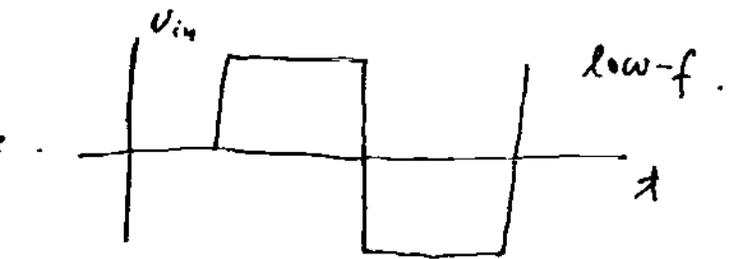The driving signal  $V_{in}$  change direction quickly. the capacitor doesn't get enough time to charge up. i.e, the voltage across  $C$  can only go up a little, then the driving voltage starts to force it to discharge.



$\therefore |V_{out}| \ll |V_{in}|$

• Cut off freq.  $\omega_c = \frac{1}{RC}$  (rad/sec)

$$f_c = \frac{1}{2\pi RC} \quad (\text{Hz})$$

at cut off frequency.  $\frac{1}{\omega_c} = R$


Amplitude:  $V_c = V_R$

$$|V_{out}| = \frac{|V_{in}|}{\sqrt{2}}$$


phase:

$45^\circ$  phase shift

between  $V_{in}$  and  $V_{out}$

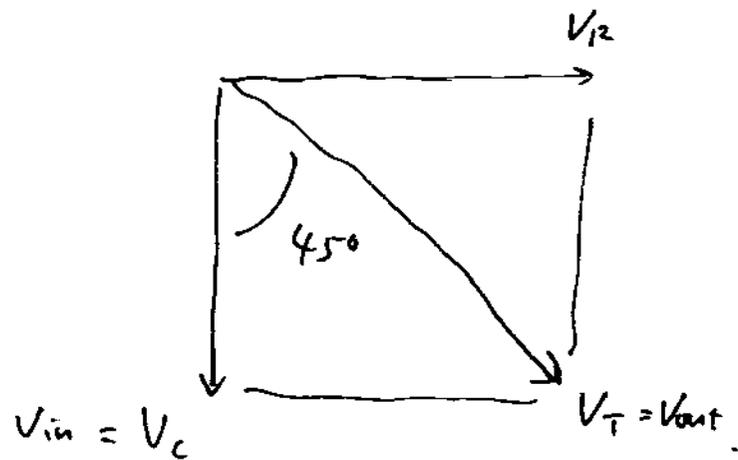

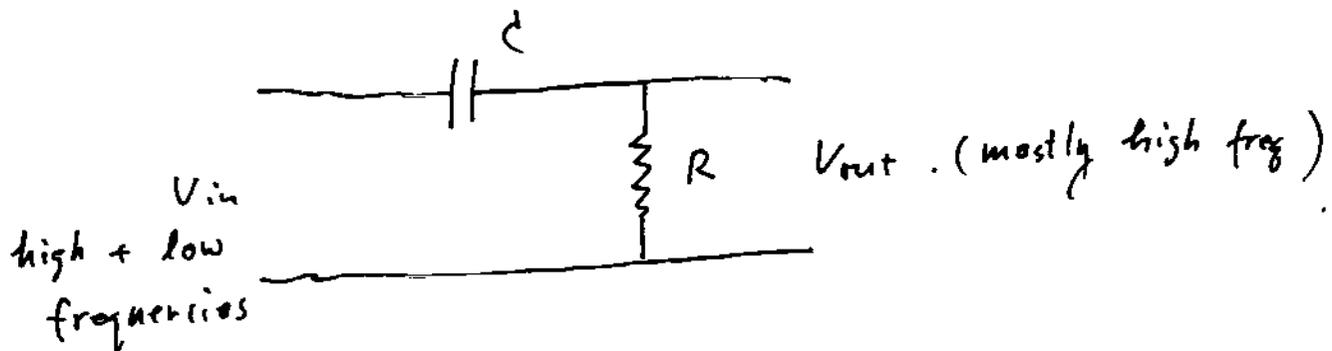• An RC circuit can be used as a high-pass filter too.



Same analysis as the low-pass filter.

Next: Magnetism. ch. 22.