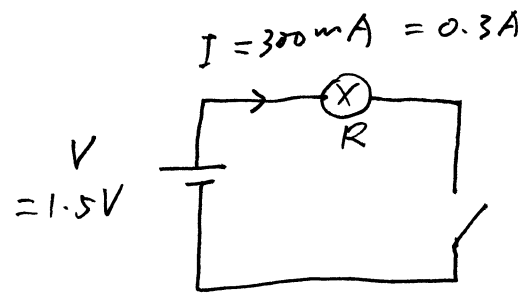


e.g. 25-4.

a). $R = ?$

$$\begin{aligned} R &= \frac{V}{I} \\ &= \frac{1.5V}{0.3A} \\ &= 5\Omega . \end{aligned}$$




b). Now $V = 1.2V$.

$I = ?$


$$\begin{aligned} I &= \frac{V}{R} \\ &= \frac{1.2V}{5\Omega} \\ &= 0.24A \\ &= 240\text{ mA} \end{aligned}$$

e.g. 25-6. Stretching a wire.

$$R_1 = \rho \frac{l_1}{A_1}$$

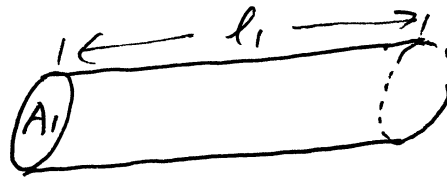

$$R_2 = \rho \frac{l_2}{A_2}$$

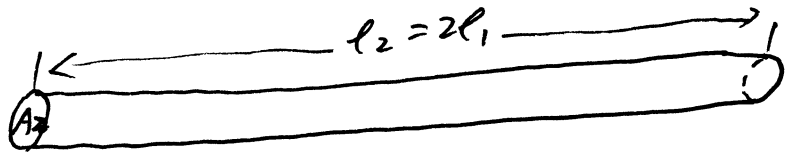

Same volume : $l_1 A_1 = l_2 A_2$.

$$A_2 = \frac{l_1}{l_2} A_1 = \frac{l_1}{2l_1} A_1 = \frac{A_1}{2}$$

$$R_2 = \rho \frac{2l_1}{A_1/2} = \rho \frac{4l_1}{A_1} = 4R_1$$

$\therefore$ The resistance is increased by a factor of 4.

2 effects: $\left. \begin{array}{l} \text{longer in length} \\ \text{smaller in area} \end{array} \right\} \text{ both reduce } R.$

What's the resistance of a 40-W light bulb?

[It depends on the voltage specification]

Here, the light bulb is for 12 V.

$$\therefore P = 40 \text{ W}, \quad V = 12 \text{ V}. \quad R = ?$$

$$\begin{aligned} P &= \frac{V^2}{R} \quad , \quad R = \frac{V^2}{P} \\ &= \frac{12^2}{40} \\ &= 3.6 \, \Omega. \end{aligned}$$

What if the light bulb is for $V = 120 \text{ V}$?

$$R = \frac{V^2}{P} = \frac{120^2}{40} = 360 \, \Omega.$$

e.g. 25-12. Extension cord .

12-4.

$$P = 1800 \text{ W} .$$

$$V = 120 \text{ V} .$$

$$P = IV .$$

$$I = \frac{P}{V} = \frac{1800 \text{ W}}{120 \text{ V}} = 15 \text{ A} .$$

Extension cord: 11 A . — too small !

e.g. 25-13. Hair dryer .

$$V = 120 \text{ V} \quad P = 1000 \text{ W} .$$

$$= V_{\text{rms}} .$$

$$a) . R : \quad P = I_{\text{rms}} V_{\text{rms}} . = \frac{V_{\text{rms}}^2}{R}$$

$$R = \frac{V_{\text{rms}}^2}{P} = \frac{120^2}{1000} = 14.4 \Omega .$$

$$I_{\text{rms}} = \frac{P}{V_{\text{rms}}} = \frac{1000}{120} = 8.33 \text{ A} .$$

$$b) . \quad \bar{P} = \frac{V_{\text{rms}}^2}{R} = \frac{240^2}{1000} = 4000 \text{ W} .$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{R} = \frac{240 \text{ V}}{14.4 \Omega} = 16.7 \text{ A} .$$