

e.g. 26-3.

A 60-W and a 100-W light bulbs are connected in series.  
which one is brighter? The 60-W one!

why? The specifications of 60-W and 100-W.  
assumes a voltage of 120 V.

When the light bulbs are made.  $R$  is fixed.  
NOT the power!


The power depends on voltage:  $P = \frac{V^2}{R}$ .  
└ brightness.

$$R_{60} = \frac{120^2}{60} =$$

In series,  $V \neq 120 \text{ V}$ .  $P$  is NOT 60 W.  
or 100 W  
any more.

$$R_{60} = \frac{120^2}{60} = 240 \Omega$$
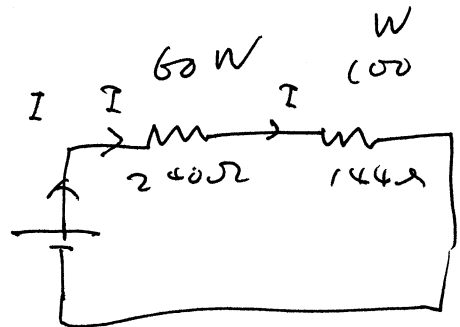
$$R_{100} = \frac{120^2}{100} = 144 \Omega$$



In series..  $R_{\text{total}} = 240 + 144 = 384 \Omega$ .

current.  $I = \frac{V}{R} = \frac{120}{384} = 0.3125 \text{ A}$ .

$$V_{60} = R_{60} \cdot I = 240 \times 0.3125 = 75 \text{ V}$$

$$V_{100} = R_{100} \cdot I = 144 \times 0.3125 = 45 \text{ V}$$

Actually power :

$$P_{60} = \frac{V_{60}^2}{R_{60}} = \frac{75^2}{240} = 23.4 \text{ W}$$

$$P_{100} = \frac{V_{100}^2}{R_{100}} = \frac{45^2}{144} = 14.1 \text{ W}$$

$$\therefore P_{60} > P_{100}$$

↑

brighter.

OR:  $P_{60} = R_{60} I^2 = 240 \times 0.3125^2 = 23.4 \text{ W}$

$$P_{100} = R_{100} I^2 = 144 \times 0.3125^2 = 14.1 \text{ W}$$

e.g 26-4.

Find  $I = ?$

$$R_{12} = R_1 \parallel R_2$$

$$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R_{12} = \frac{R_1 R_2}{R_1 + R_2} = 290 \Omega$$


$$R_{Total} = R_1 + R_{12}$$

$$= 400 + 290$$


$$= 690 \Omega$$

$$I = \frac{V_{Total}}{R_{Total}} = \frac{12}{690} = 0.0174 A$$

$$= 17 \text{ mA}$$

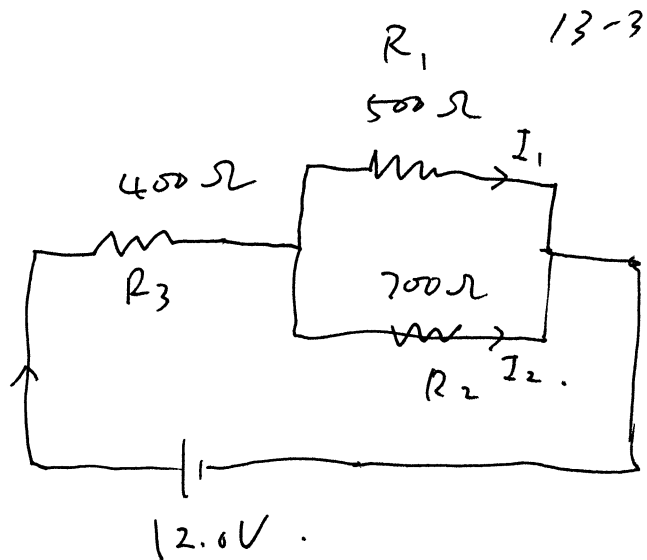

equivalent.

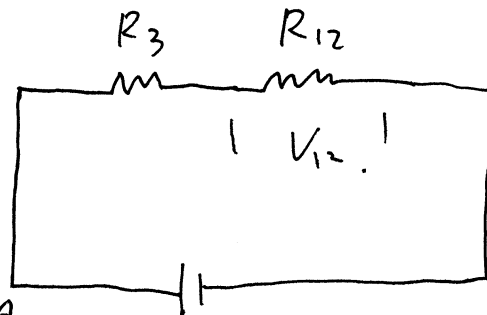

e.g. 26-5 Find  $I_1 = ?$   $I_1 = \frac{V_1}{R_1} = \frac{V_{12}}{R_1}$

$$V_{12} = I \cdot R_{12} = 0.0174 A \times 290 \Omega = 5.0 V$$

$$I_1 = \frac{5.0 V}{500 \Omega} = 10 \text{ mA}$$


$$I_2 = \frac{5.0 V}{700 \Omega} = 7 \text{ mA}$$

e.g. 26-11

13-4.

$$C = 0.30 \mu F, \quad R = 20 K\Omega$$
$$= 3 \times 10^{-7} F, \quad = 2 \times 10^4 \Omega.$$

$$\mathcal{E} = 12 V.$$

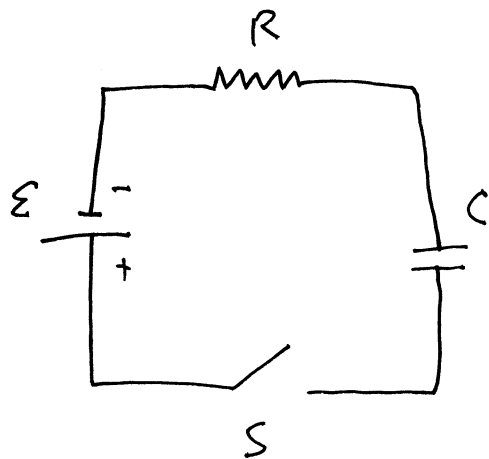

a).  $\tau = ?$

$$\tau = RC = 3 \times 10^{-7} \times 2 \times 10^4 = 6 \times 10^{-3} s = 6 ms.$$

b).  $Q_{max} = Q_{final} = CV = 3 \times 10^{-7} \times 12 = 3.6 \times 10^{-6} C$   
 $= 3.6 \mu C.$

c).  $t = ? \quad Q = 0.99 Q_{final}.$

$$Q = \underbrace{C\mathcal{E}}_{Q_{final}} (1 - e^{-t/\tau}) = Q_{final} (1 - e^{-t/\tau}).$$

Now  $Q = 0.99 Q_{final} : \quad 0.99 = 1 - e^{-t/\tau}.$

Solve for  $t$ :  $0.01 = e^{-t/\tau}.$

$$-\frac{t}{\tau} = \ln 0.01 = -4.605.$$

$$t = 4.605 \tau = 27.6 ms.$$

d).  $I = ?$  when  $Q = \frac{1}{2} Q_{\text{final}}$ .

solve for  $t$ :  $\frac{1}{2} = 1 - e^{-t/\tau}$ .

$$-\frac{1}{2} = -e^{-t/\tau} \quad 0.5 = e^{-t/\tau}$$

$$\ln 0.5 = -t/\tau$$

$$t = 0.693 \tau = 4.16 \text{ ms.}$$

$$I = \frac{\mathcal{E}}{R} e^{-t/\tau} = \frac{12 \text{ V}}{20 \text{ k}\Omega} e^{-t/\tau}$$


$$= \frac{12}{2 \times 10^4} e^{-\frac{4.16 \times 10^{-3}}{6 \times 10^{-3}}}$$

$$= 3 \times 10^{-4} \text{ A} = 0.3 \text{ mA} = 300 \mu\text{A}$$

e).  $I = \underbrace{I_0}_{\substack{\uparrow \\ I_{\text{max}}}} e^{-t/\tau}$

$$I_0 = \frac{12 \text{ V}}{20 \text{ k}\Omega} = 0.6 \text{ mA}$$

$$= 600 \mu\text{A}$$

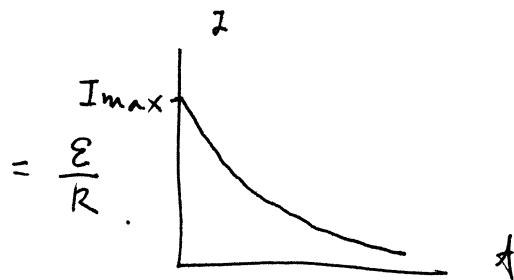

f).  $Q = ?$  when  $\underline{I = 0.2 I_0}$ . solve for  $t$ :  $0.2 I_0 = I_0 e^{-t/\tau}$

$$0.2 = e^{-t/\tau}$$

$$\ln 0.2 = -t/\tau$$

$$t = (1.609) \tau = 9.657 \text{ ms.}$$

$$Q = C \mathcal{E} (1 - e^{-t/\tau})$$

$$= 3.6 (1 - e^{-9.657/6}) \quad (\mu\text{C})$$

$$= 2.88 \mu\text{C}$$