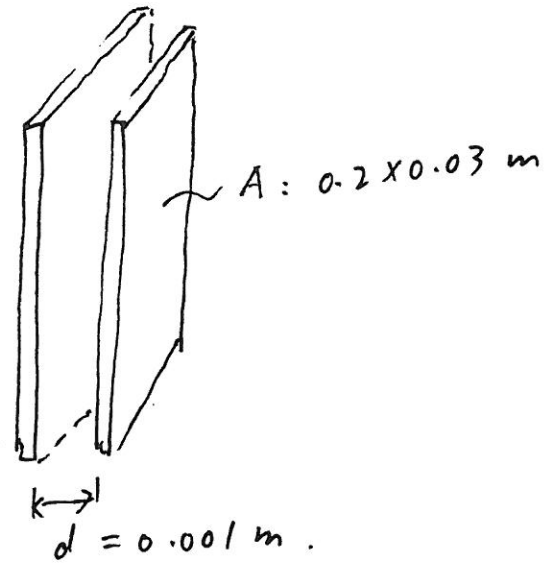


e.g. ~~capacitance~~. Capacitance of a parallel-plate capacitor

7-1

$$a). \quad C = \frac{A \epsilon_0}{d} = \frac{0.2 \times 0.03 \times 8.85 \times 10^{-12}}{0.001} \\ = 5.3 \times 10^{-11} = 53 \text{ pF}.$$



$$b). \quad V = 12. \quad Q = ?$$

$$Q = CV = 53 \times 10^{-12} \times 12 = \\ = 6.4 \times 10^{-10} \text{ C}$$

$$c). \quad \cancel{V} \quad V = Ed$$

$$E = \frac{V}{d} = \frac{12}{0.001} = 1.2 \times 10^4 \text{ V/m}.$$

$$d). \quad \text{Want: } C_2 = 1 \text{ F} = \frac{A_2 \epsilon_0}{d}.$$

$$\frac{C_2}{C} = \frac{A_2}{A}$$

$$\frac{1 \text{ F}}{53 \times 10^{-12} \text{ F}} = \frac{A_2}{0.2 \times 0.03}$$

$$A_2 = \frac{0.2 \times 0.03}{53 \times 10^{-12}} \approx 10^8 \text{ m}^2.$$

$10 \text{ km} \times 10 \text{ km}$

e.g. ~~very~~ Cylindrical Capacitor

l - Very long.

How do we find C ?

• Idea:

If we apply a voltage V ,
we create a potential
difference between the
core and the shell (V).

Then, $\vec{E}$ exists from R_b to R_a .

That means, $+Q$ on R_b
 $-Q$ on R_a .

Since $C = \frac{Q}{V}$,

we need to find relation
between Q and V .



• One way to do that:

from Q find $\vec{E}$: use Gauss's Law. $E = \frac{Q/\ell}{2\pi\epsilon_0 R}$

From E find V : $V = V_b - V_a = - \int_a^b \vec{E} \cdot d\vec{\ell}$

$\therefore C = \frac{Q}{V}$
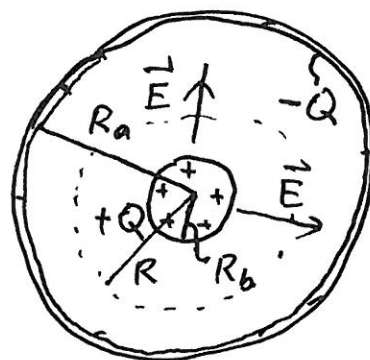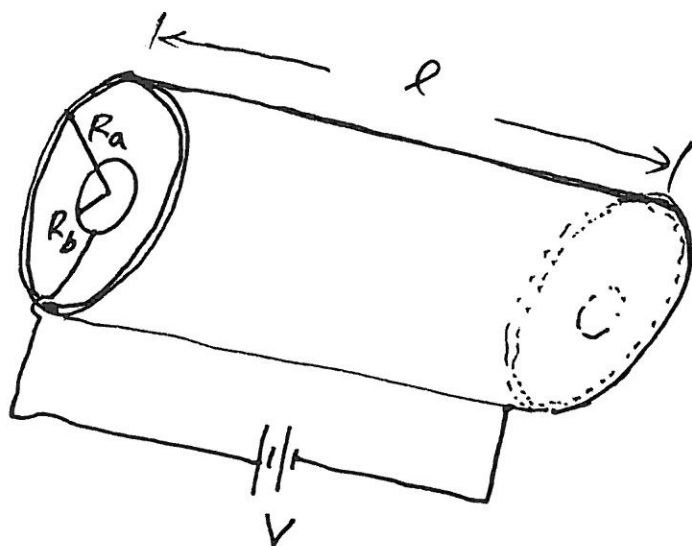
$$= \frac{2\pi\epsilon_0 l}{\ln \frac{R_a}{R_b}}$$



$$= - \int_{R_a}^{R_b} \frac{Q}{2\pi\epsilon_0 l R} dR = - \frac{Q}{2\pi\epsilon_0 l} \ln \frac{R_b}{R_a}$$

$$= \frac{Q}{2\pi\epsilon_0 l} \cdot \ln \frac{R_a}{R_b}$$

- Capacitors in parallel

$$C_{eq} = C_1 + C_2 + C_3.$$

Simple reason:

If they are parallel capacitors with the same gap distance d ,

then, the areas add. $A = A_1 + A_2 + A_3$.

Derivation:

parallel: $V_1 = V_2 = V_3 = V$.


$$Q = Q_1 + Q_2 + Q_3.$$

$$C = \frac{Q}{V}.$$


$$C_{eq} = \frac{Q}{V} = \frac{Q_1 + Q_2 + Q_3}{V}$$

$$= \frac{Q_1}{V_1} + \frac{Q_2}{V_2} + \frac{Q_3}{V_3}$$

$$= C_1 + C_2 + C_3.$$

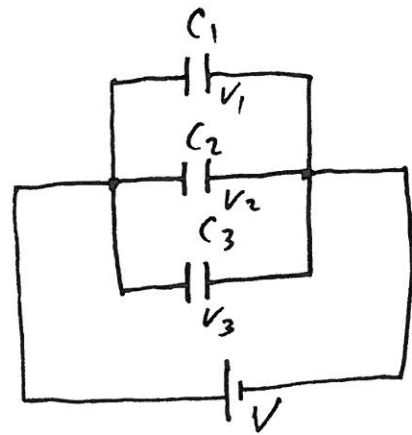

⇓ equivalent to

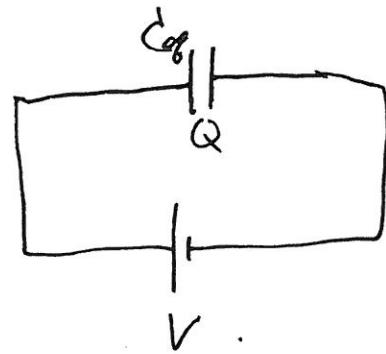


Capacitors in Series.

Series: $Q_1 = Q_2 = Q_3 = Q$


$$V = V_1 + V_2 + V_3$$

$$\therefore \frac{Q}{C_{eq}} = \frac{Q_1}{C_1} + \frac{Q_2}{C_2} + \frac{Q_3}{C_3}$$
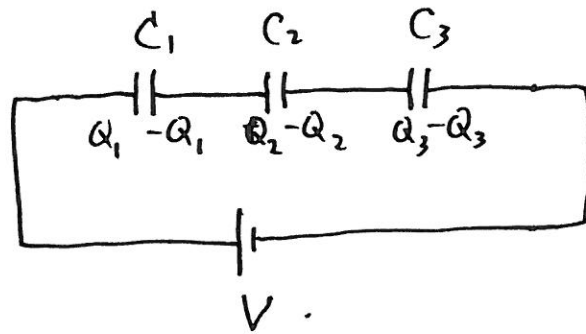
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



$\Downarrow$ equivalent to

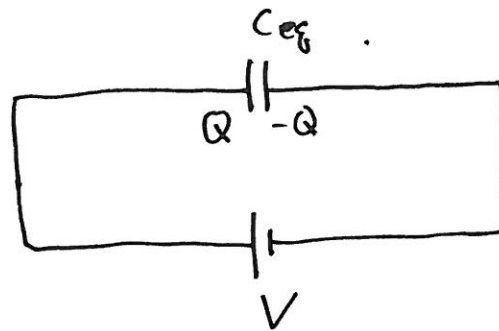

e.g. 24-5.


$$C_{23} = C_2 + C_3$$

$$C_{ab}: \frac{1}{C_{ab}} = \frac{1}{C_{23}} + \frac{1}{C_1}$$


$$\frac{1}{C_{ab}} = \frac{C_1 + C_{23}}{C_{23} C_1}$$

$$C_{ab} = \frac{C_1 C_{23}}{C_1 + C_{23}}$$
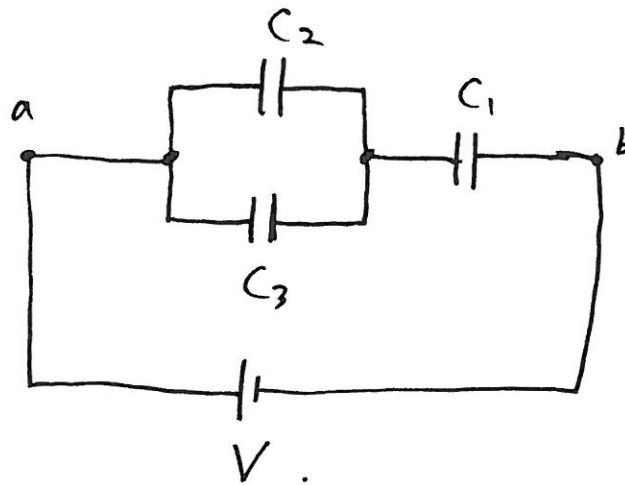
$$= \frac{C_1 (C_2 + C_3)}{C_1 + C_2 + C_3}$$



$\Downarrow$

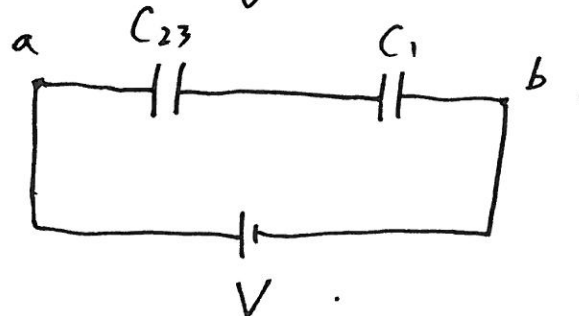

e.g. ~~4.4~~

7-4.

If $C_1 = C_2 = C_3 = C = 3.0 \mu F$.

$$V = 4.0 V.$$




Find. $Q_1, Q_2, Q_3, V_1, V_2, V_3$.

$$C_{ab} = \frac{C(C+C)}{C+C+C} = \frac{2C}{3} = 2 \mu F.$$

$$Q = Q_{ab} \cdot V$$

$$= 2 \mu F \cdot 4 V = 8 \mu C.$$

$$Q_1 = Q = 8 \mu C.$$

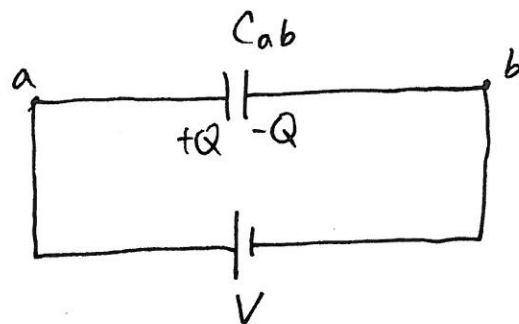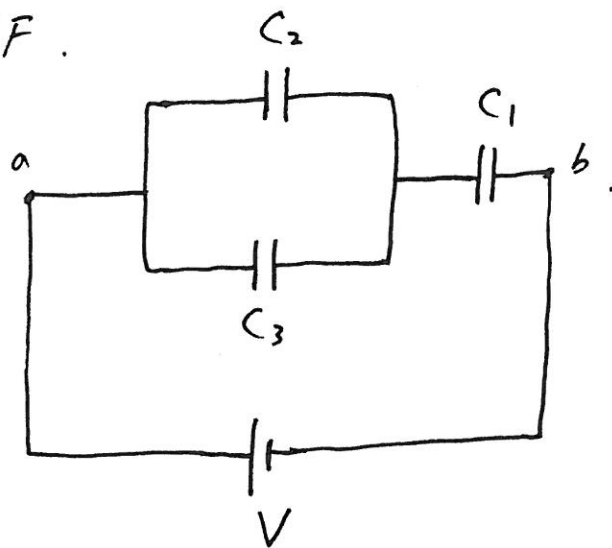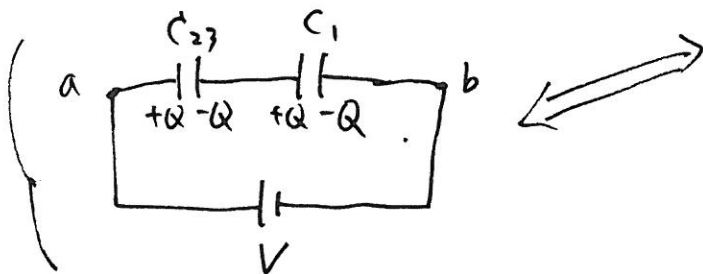

$$V_1 = \frac{Q_1}{C_1} = \frac{8 \mu C}{3 \mu F} = 2.7 V.$$

$$Q_{23} = Q_1 = Q = 8 \mu C.$$

$$Q_2 = Q_3 = \frac{Q_{23}}{2} = 4 \mu C.$$

$$V_2 = V_3 = \frac{Q_2}{C} = \frac{4 \mu C}{3 \mu F} = 1.3 V.$$



$$(V_2 + V_1 = 4 V = V)$$

e.g. ~~initial~~.


$$C_1 = 2.2 \mu F.$$

$$C_2 = 1.2 \mu F.$$

$$V = 24 V.$$

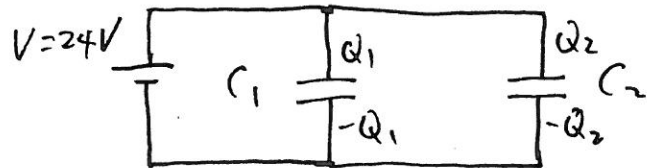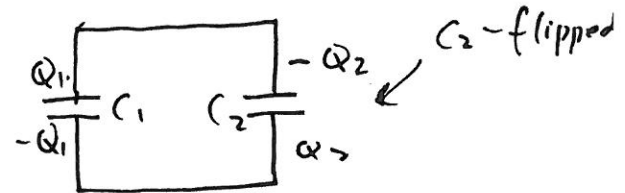Find: q_1, q_2 V_{final} .initial
(charged)Then: (disconnected
and
reconnected)

Finally:

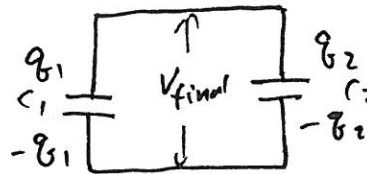(reach
equilibrium)↓ reach
equilibrium.

Initial: $C_{\text{eq}} = C_1 + C_2 = 3.4 \mu F$, $V_1 = V_2 = V = 24 V$.

$$(Q = Q_1 + Q_2 = C_{\text{eq}} \cdot V = 3.4 \mu F \cdot 24 V = 81.6 \mu C)$$

$$Q_1 = C_1 V_1 = 2.2 \mu F \times 24 V = 52.8 \mu C.$$

$$Q_2 = C_2 V_2 = 1.2 \mu F \times 24 V = 28.8 \mu C.$$

Final: $q_1 + q_2 = Q_1 - Q_2 = 24 \mu C = q$.

$$C_{\text{eq}} = C_1 + C_2 = 3.4 \mu F \text{ (unchanged)}.$$

$$V_{\text{final}} = \frac{q}{C_{\text{eq}}} = \frac{24 \mu C}{3.4 \mu F} = 7.1 V.$$

$$q_1 = C_1 V_{\text{final}} = 2.2 \mu F \times 7.1 V = 15.5 \mu C$$

$$q_2 = C_2 V_{\text{final}} = 1.2 \times 7.1 = 8.5 \mu C.$$

• Energy stored in a capacitor.

$$U = \frac{1}{2} Q V.$$

Why not $U = Q V$?


Where does $\frac{1}{2}$ come from?

Remember, if you move a

charge q through a ~~potential~~ potential

difference V , the ~~potential~~ potential energy difference

should be $U = q V$.

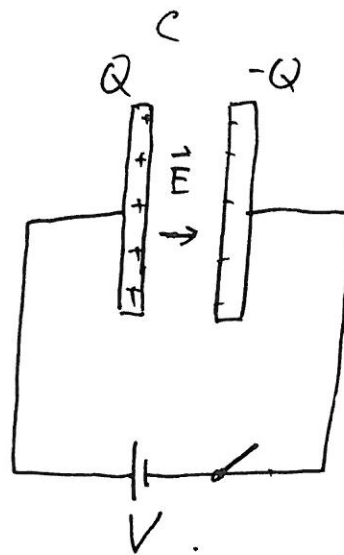

Answer: Q is ~~potential~~ gradually moved across.

Initially, when $Q=0$, $\vec{E}=0$, $V=0$. easy to get across.
(No energy)

Finally, when C is fully charged, $V=V$. it cost energy
to get across. $U = q V$.

Average potential difference between the plates: $\frac{1}{2} V$.

$$\therefore \text{Total } U = Q \cdot \left(\frac{1}{2} V\right) = \frac{1}{2} Q V. \quad \left(\begin{array}{l} V = \frac{Q}{C} \\ Q = C V \end{array} \right)$$

$$= \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} C V^2.$$



e.g. Energy stored in a capacitor .

$$C = 150 \mu F . \quad V = 200 V .$$

$$a) . \quad U = \frac{1}{2} C V^2 = \frac{1}{2} \times 150 \times 10^{-6} \times (200)^2 = 3.0 \text{ J}$$

$$b) . \quad P = \frac{U}{t} = \frac{3.0}{1 \times 10^{-3}} = 3 \text{ kW}$$

Conceptual example .

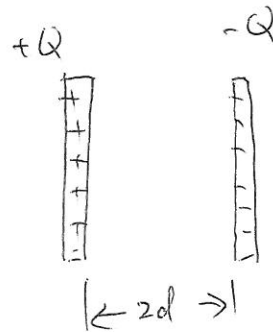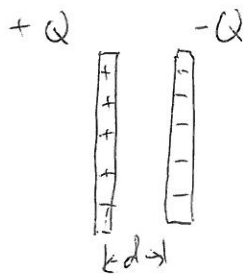

$$C_1 = C_0$$

$$U_1 = \frac{1}{2} \frac{Q^2}{C_0}$$

$$C_2 = \frac{1}{2} C_0$$

$$U_2 = \frac{1}{2} \frac{Q^2}{\frac{1}{2} C_0} = \frac{Q^2}{C_0} = 2 U_1$$

You need to do work to the capacitor in order

to increase the separation d .

e.g. Dielectric removal.

$$A = 4.0 \text{ m}^2 \quad d = 4.0 \times 10^{-3} \text{ m}$$

$$K = 3.4, \quad V = 100 \text{ V}$$

$$K = 3.4$$

$$a) \quad C = \epsilon_0 K \frac{A}{d}$$

$$= 8.85 \times 10^{-12} \times 3.4 \times \frac{4.0}{4.0 \times 10^{-3}}$$

$$= 3.0 \times 10^{-8} \text{ F} = 30 \text{ nF}$$

$$K = 1$$

$$Q = C \cdot V = 3.0 \times 10^{-8} \times 100 = 3.0 \times 10^{-6} \text{ C} = 3.0 \mu\text{C}$$

$$E = \frac{V}{d} = \frac{100}{4.0 \times 10^{-3}} = 25 \text{ kV/m}$$

$$U = \frac{1}{2} C V^2 = \frac{1}{2} \times 3.0 \times 10^{-8} \times (100)^2 = 1.5 \times 10^{-4} \text{ J}$$

$$b) \quad Q = 3.0 \mu\text{C} = 3.0 \times 10^{-6} \text{ C}$$

$$C = \epsilon_0 \frac{A}{d} = 8.85 \times 10^{-9} \text{ F} = 8.85 \text{ nF}$$

$$V = \frac{Q}{C} = \frac{3.0 \times 10^{-6}}{8.85 \times 10^{-9}} \approx 3.4 \times 10^2 \text{ V} = 340 \text{ V}$$

$$E = \frac{V}{d} = \frac{340}{4.0 \times 10^{-3}} = 8.5 \times 10^4 \text{ V/m}$$

$$U = \frac{1}{2} C V^2 = \frac{1}{2} \times 8.85 \times 10^{-9} \times (340)^2 = 5.1 \times 10^{-4} \text{ J}$$

Energy stored has been increased.

The induced charges in the medium are attracted to the free charges on the plates. To move the medium out of the capacitor, we need to do work.