

e.g. ~~surprise~~ An Illuminating Surprise.

10-1.

A 60-W and a 100-W light bulbs are connected in series.
which one is brighter? The 60-W one!

why? The specifications of 60-W and 100-W
assumes a voltage of 120 V.

When the light bulbs are made, R is fixed,
NOT the power!


The power depends on voltage: $P = \frac{V^2}{R}$
└ brightness.

$$R_{60} = \frac{120^2}{60} =$$

In series, $V \neq 120 \text{ V}$. P is NOT 60 W.
or 100 W
any more.

$$R_{60} = \frac{120^2}{60} = 240 \Omega$$
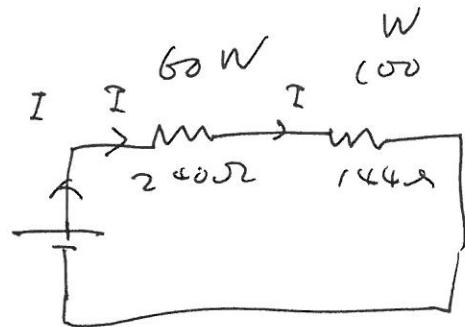
$$R_{100} = \frac{120^2}{100} = 144 \Omega$$



In series.. $R_{\text{total}} = 240 + 144 = 384 \Omega$

current. $I = \frac{V}{R} = \frac{120}{384} = 0.3125 \text{ A}$

$$V_{60} = R_{60} \cdot I = 240 \times 0.3125 = 75 \text{ V}$$

$$V_{100} = R_{100} \cdot I = 144 \times 0.3125 = 45 \text{ V}$$

Actually power :

$$P_{60} = \frac{V_{60}^2}{R_{60}} = \frac{75^2}{240} = 23.4 \text{ W}$$

$$P_{100} = \frac{V_{100}^2}{R_{100}} = \frac{45^2}{144} = 14.1 \text{ W}$$

$$\therefore P_{60} > P_{100}$$

↑

brighter.

$$\text{Q12: } P_{60} = R_{60} I^2 = 240 \times 0.3125^2 = 23.4 \text{ W}$$

$$P_{100} = R_{100} I^2 = 144 \times 0.3125^2 = 14.1 \text{ W}$$

e.g. ~~26-5~~.

Find $I = ?$

$$R_{12} = R_1 \parallel R_2$$

$$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R_{12} = \frac{R_1 R_2}{R_1 + R_2} = 290 \Omega$$

equivalent.



$$R_{Total} = R_1 + R_{12}$$

$$= 400 + 290$$

$$= 690 \Omega$$

$$I = \frac{V_{Total}}{R_{Total}} = \frac{12}{690} = 0.0174 A$$

$$= 17 \text{ mA}$$

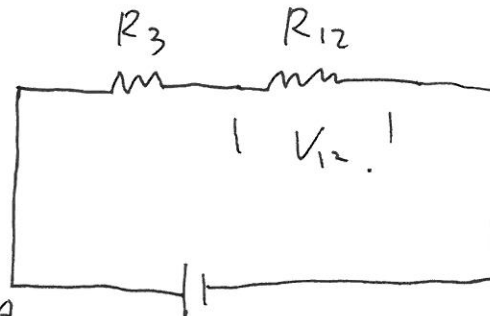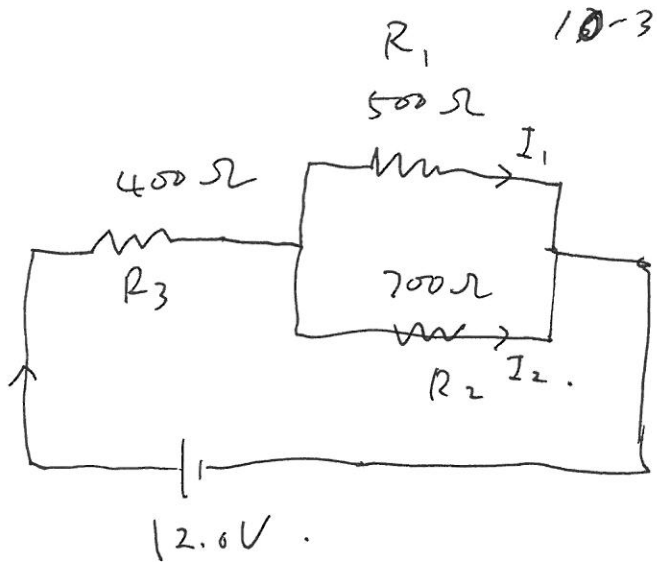

e.g. 26-5 Find $I_1 = ?$ $I_1 = \frac{V_1}{R_1} = \frac{V_{12}}{R_1}$

$$V_{12} = I \cdot R_{12} = 0.0174 A \times 290 \Omega = 5.0 V$$

$$I_1 = \frac{5.0 V}{500 \Omega} = 10 \text{ mA}$$


$$I_2 = \frac{5.0 V}{700 \Omega} = 7 \text{ mA}$$

e.g. RC-circuit.

10-4.

$$C = 0.30 \mu F, \quad R = 20 k\Omega$$
$$= 3 \times 10^{-7} F, \quad = 2 \times 10^4 \Omega.$$

$$\mathcal{E} = 12 V.$$

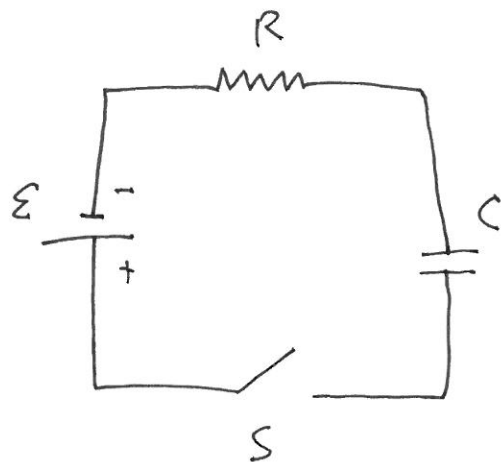

a). $\tau = ?$

$$\tau = RC = 3 \times 10^{-7} \times 2 \times 10^4 = 6 \times 10^{-3} s = 6 ms.$$

b). $Q_{max} = Q_{final} = CV = 3 \times 10^{-7} \times 12 = 3.6 \times 10^{-6} C$
 $= 3.6 \mu C.$

c). $t = ? \quad Q = 0.99 Q_{final}.$

$$Q = \underbrace{C\mathcal{E}}_{Q_{final}} (1 - e^{-t/\tau}) = Q_{final} (1 - e^{-t/\tau}).$$

Now $Q = 0.99 Q_{final} : \quad 0.99 = 1 - e^{-t/\tau}.$

Solve for t : $0.01 = e^{-t/\tau}.$

$$-\frac{t}{\tau} = \ln 0.01 = -4.605.$$

$$t = 4.605 \tau = 27.6 ms.$$

d). $I = ?$ when $Q = \frac{1}{2} Q_{\text{final}}$.

solve for t : $\frac{1}{2} = 1 - e^{-t/\tau}$.

$$-\frac{1}{2} = -e^{-t/\tau} \quad 0.5 = e^{-t/\tau}$$

$$\ln 0.5 = -t/\tau$$

$$t = 0.693 \tau = 4.16 \text{ ms.}$$

$$I = \frac{\mathcal{E}}{R} e^{-t/\tau} = \frac{12 \text{ V}}{20 \text{ k}\Omega} e^{-t/\tau}$$


$$= \frac{12}{2 \times 10^4} e^{-\frac{4.16 \times 10^{-3}}{6 \times 10^{-3}}}$$

$$= 3 \times 10^{-4} \text{ A} = 0.3 \text{ mA} = 300 \mu\text{A}$$

e). $I = I_0 e^{-t/\tau}$

$$\uparrow$$

$$I_{\text{max}}$$

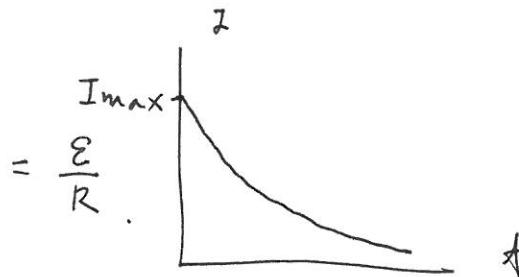

$$I_0 = \frac{12 \text{ V}}{20 \text{ k}\Omega} = 0.6 \text{ mA}$$

$$= 600 \mu\text{A}$$

f). $Q = ?$ when $I = 0.2 I_0$. solve for t : $0.2 I_0 = I_0 e^{-t/\tau}$

$$0.2 = e^{-t/\tau}$$

$$\ln 0.2 = -t/\tau$$

$$t = (1.609) \tau = 9.657 \text{ ms.}$$

$$Q = C \mathcal{E} (1 - e^{-t/\tau})$$

$$= 3.6 (1 - e^{-9.657/6}) \quad (\mu\text{C})$$

$$= 2.88 \mu\text{C}$$

e.g. Discharging RC circuit.

$$Q_0 = C\varepsilon, \quad \tau = RC$$

Discharging:

$$Q = Q_0 e^{-t/RC}$$

$$V_c = V_0 e^{-t/RC}, \quad (V_0 = \varepsilon)$$

$$I = I_0 e^{-t/RC}$$

Given, when $t = 4.0 \times 10^{-5} \text{ s}$, $I = 0.5 I_0$:

$$0.5 I_0 = I_0 e^{-t/RC}$$

$$0.5 = e^{-t/RC}$$

Solve for RC: $-t/RC = \ln 0.5 = -0.693$

$$\tau = RC = \frac{t}{0.693} = \frac{4.0 \times 10^{-5}}{0.693} = 5.77 \times 10^{-5} \text{ s}$$

a). at $t = 0$,

$$Q = Q_0 = C\varepsilon = 1.02 \times 10^{-6} \times 20 = 2.04 \times 10^{-5} \text{ C}$$

b). $\tau = RC$. $R = \frac{\tau}{C} = \frac{5.77 \times 10^{-5}}{1.02 \times 10^{-6}} = 56.6 \, \Omega$

c) $Q = Q_0 e^{-t/RC}$

$$= 2.04 \times 10^{-5} e^{-\frac{6.0 \times 10^{-5}}{5.77 \times 10^{-5}}} = 7.21 \times 10^{-6} \text{ C}$$

$$= 7.21 \, \mu\text{C}$$

