

Phys102 Lecture 12

Kirchhoff's Rules

Key Points


- Kirchhoff's Junction Rule
- Kirchhoff's Loop Rule
- Solving Linear Algebraic Equations

References

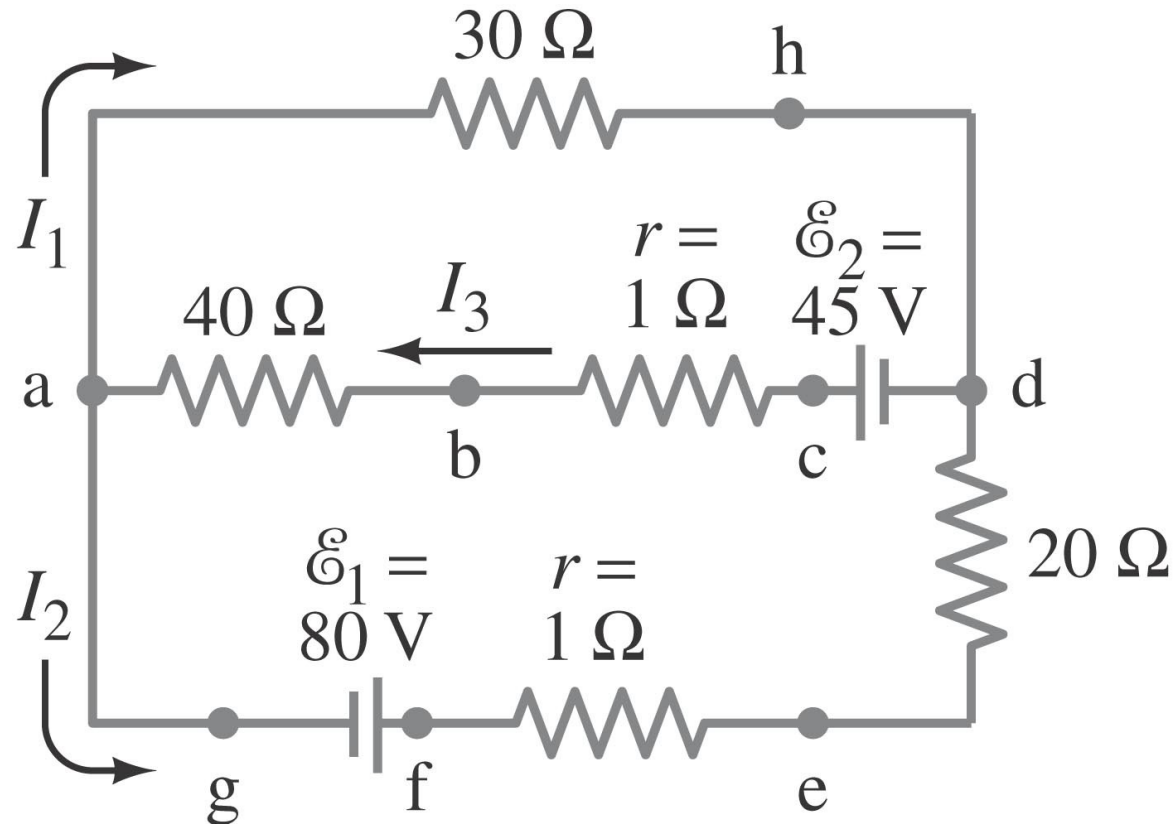19-3.


Kirchhoff's Rules

Some circuits cannot be broken down into series and parallel connections. For these circuits we use Kirchhoff's rules.




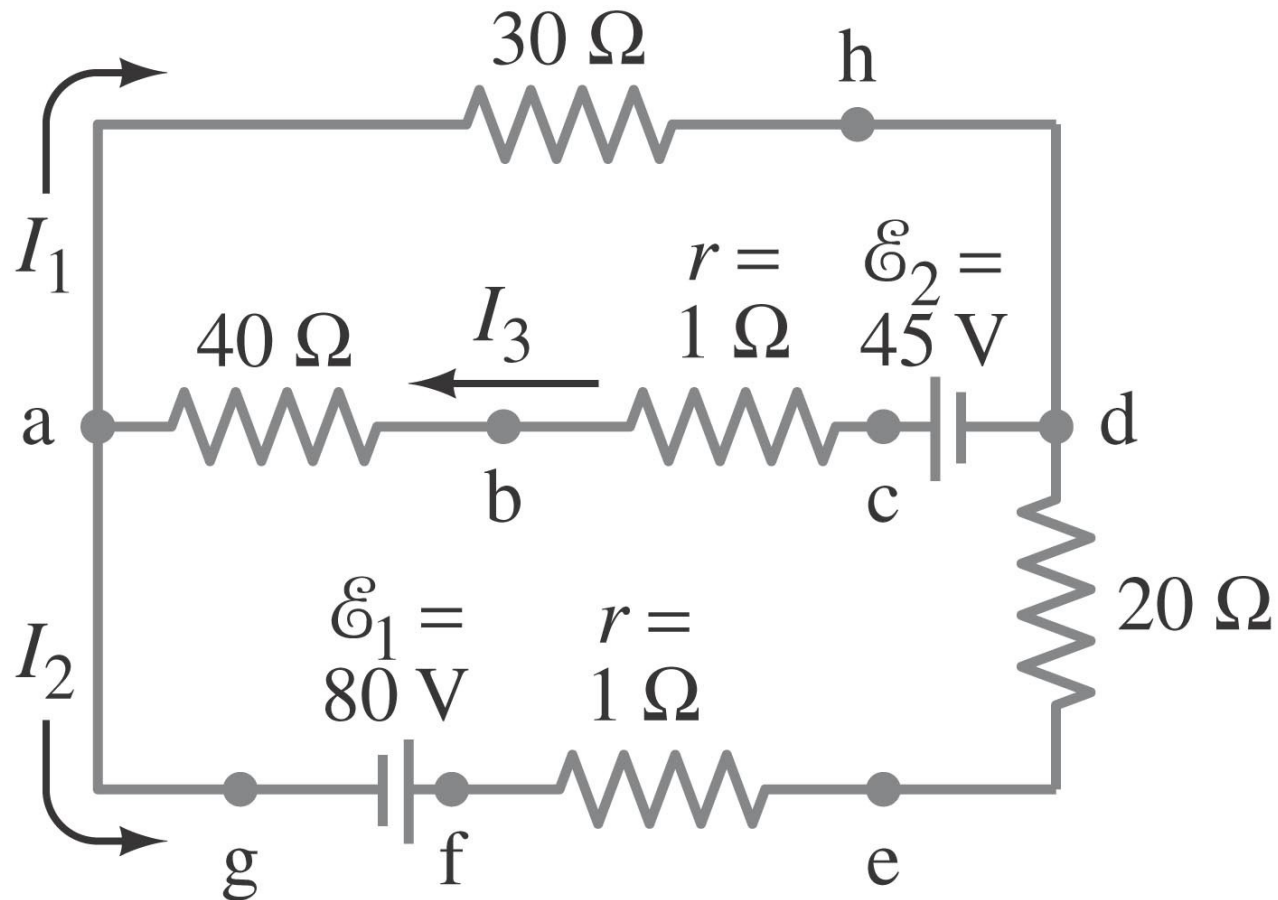
19-3 Kirchhoff's Rules

Junction rule: The sum of currents entering a junction equals the sum of the currents leaving it.



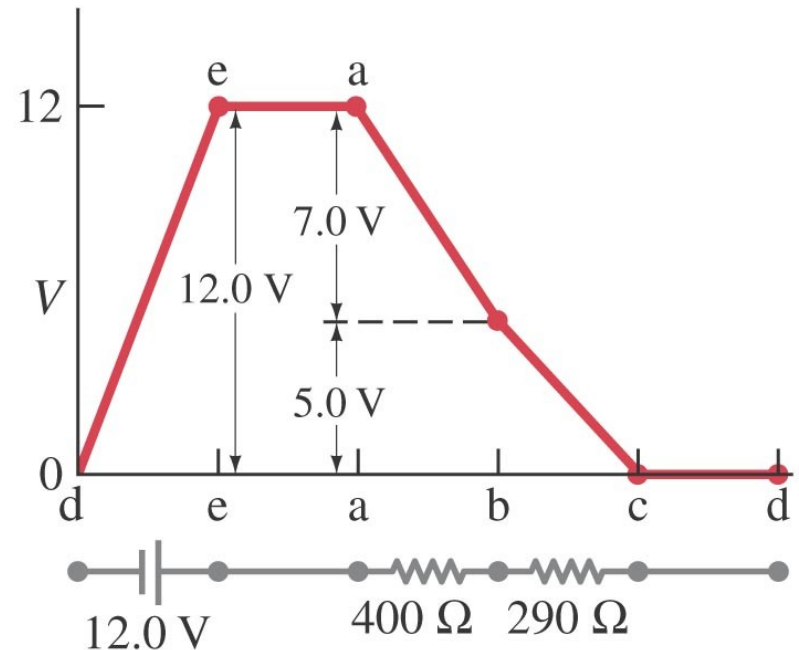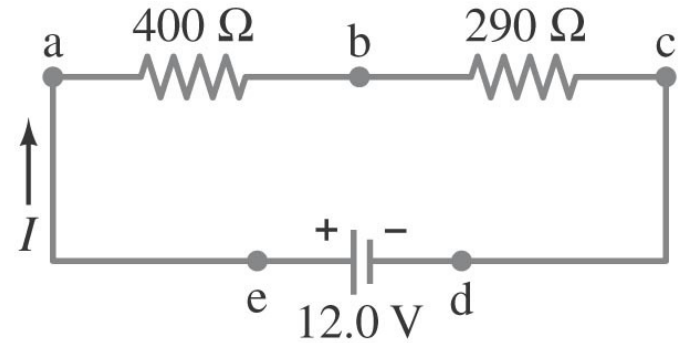19-3 Kirchhoff's Rules

Loop rule: The sum of the changes in potential around a closed loop is zero.



19-3 Kirchhoff's Rules

Problem Solving: Kirchhoff's Rules

1. Label each current, including its direction.
2. Identify unknowns.
3. Apply junction and loop rules; you will need as many independent equations as there are unknowns.
4. Solve the equations, being careful with signs. If the solution for a current is negative, that current is in the opposite direction from the one you have chosen.

Example: Using Kirchhoff's rules.

Calculate the currents I_1 , I_2 , and I_3 in the three branches of the circuit in the figure.

