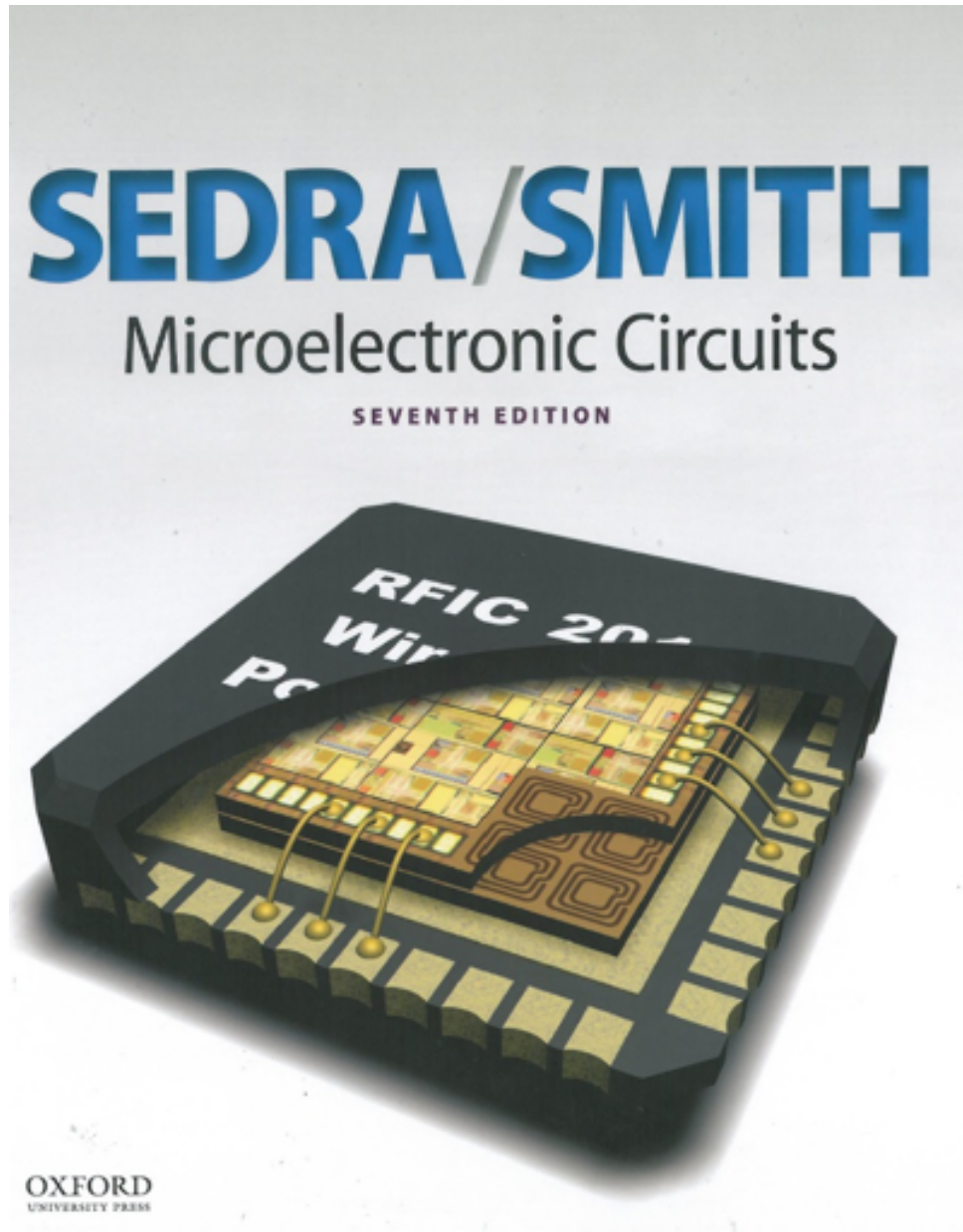


Applications of operational amplifiers




- *Difference amplifier*
- *Instrumentation amplifier*
- *Opamp inverting integrator*
- *Opamp differentiator*
- *Charge-sensitive amplifier*

*Textbook material for self-study:
Ch.2 - Operational Amplifiers,
Sections 2.4 to 2.5*

Open-loop op amp as a difference amplifier

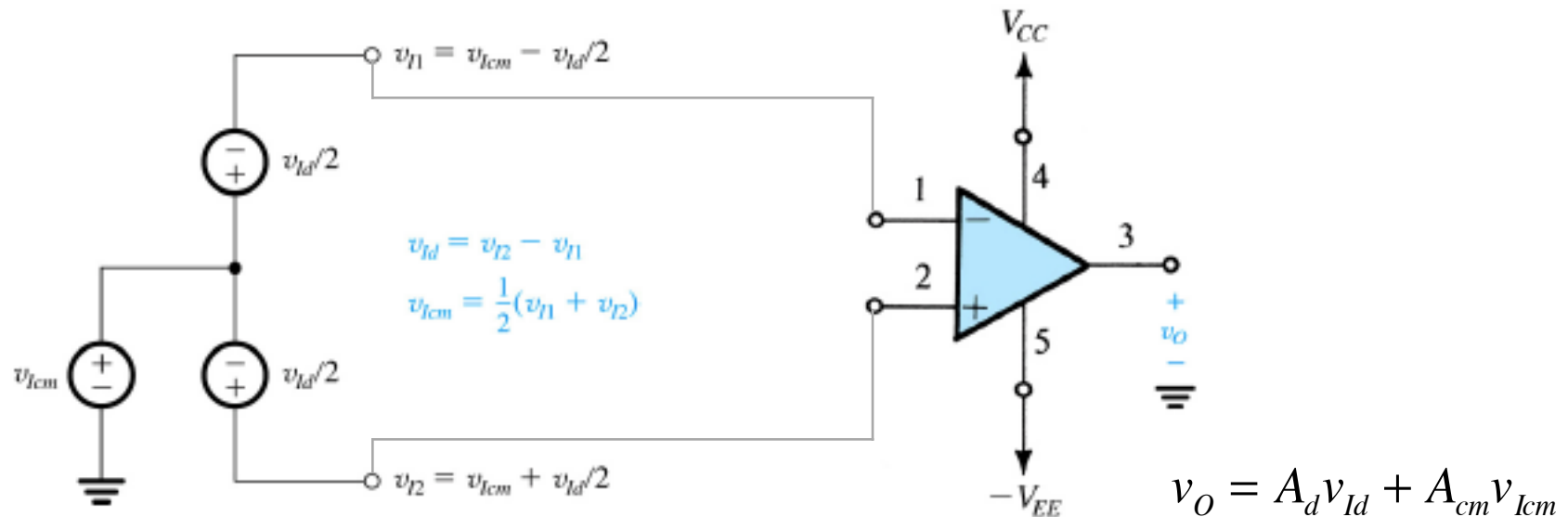Goal: to amplify the difference of signals $v_{I2}-v_{I1}$, while suppressing the common mode gain




Common-Mode Rejection Ratio (CMRR) quantifies the op amp's ability to reject the common mode signals

$$CMRR = 20 \log \frac{|A_d|}{|A_{cm}|}$$

Disadvantages of open-loop op amp as a difference amplifier:

- very high gain but poor controllability
- closed-loop gain more stable and more predictable

A single op amp difference amplifier

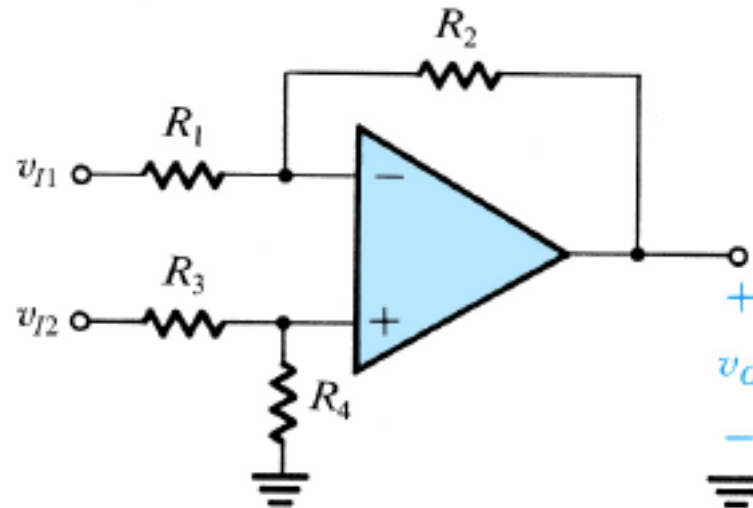



The condition:

$$\frac{R_4}{R_3} = \frac{R_2}{R_1}$$

must be met


Goal: Find v_O as a function of v_{I1} and v_{I2}

Superposition technique

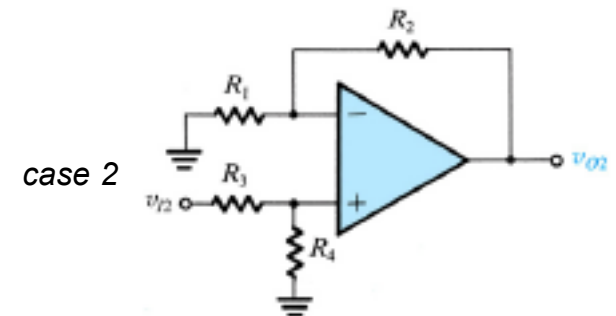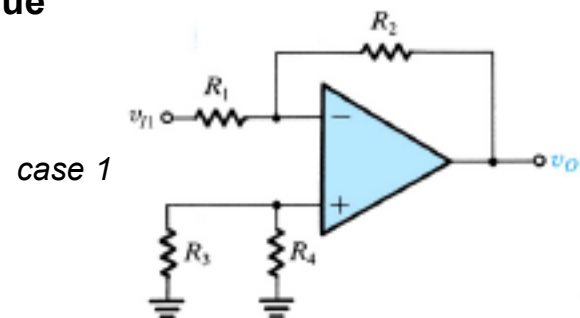


$$v_O = v_{O1(case1)} + v_{O2(case2)}$$

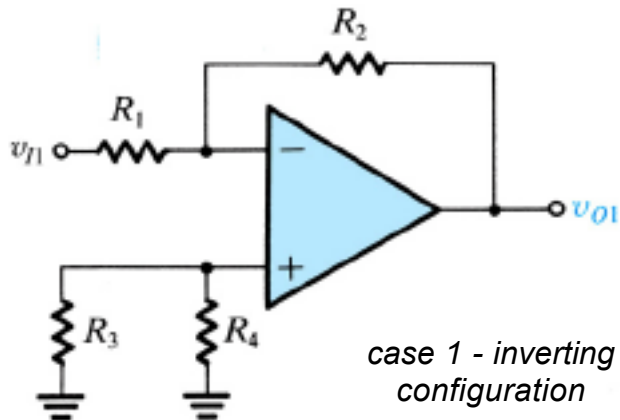Differential gain of the difference amplifier



$$v_{O1} = -\frac{R_2}{R_1}v_{I1}$$

$$\frac{R_4}{R_3} = \frac{R_2}{R_1}$$

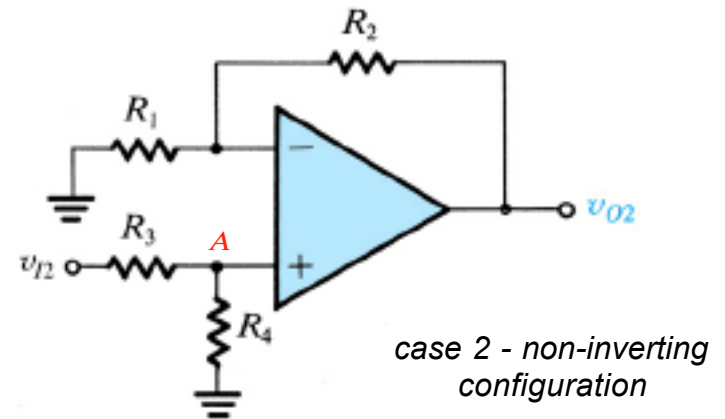

$$\begin{aligned} v_{O2} &= v_A \left(1 + \frac{R_2}{R_1} \right) = v_{I2} \frac{R_4}{R_4 + R_3} \left(1 + \frac{R_2}{R_1} \right) = v_{I2} \frac{\frac{R_4}{R_4}}{\frac{R_4}{R_4} + \frac{R_3}{R_4}} \left(1 + \frac{R_2}{R_1} \right) = \\ &= v_{I2} \frac{1}{1 + \frac{R_1}{R_2}} \left(1 + \frac{R_2}{R_1} \right) = v_{I2} \frac{R_2}{R_2 + R_1} \frac{R_1 + R_2}{R_1} = v_{I2} \frac{R_2}{R_1} \end{aligned}$$

$$v_O = v_{O1} + v_{O2} = -\frac{R_2}{R_1}v_{I1} + \frac{R_2}{R_1}v_{I2} = \frac{R_2}{R_1}(v_{I2} - v_{I1}) = \frac{R_2}{R_1}v_{Id}$$

Differential gain of the difference amplifier:


$$A_{diff} = \frac{R_2}{R_1}$$

when

$$\frac{R_4}{R_3} = \frac{R_2}{R_1}$$

To satisfy the $\frac{R_4}{R_3} = \frac{R_2}{R_1}$ condition while minimizing a possible matching problem, we usually select $R_3 = R_1$ and $R_4 = R_2$

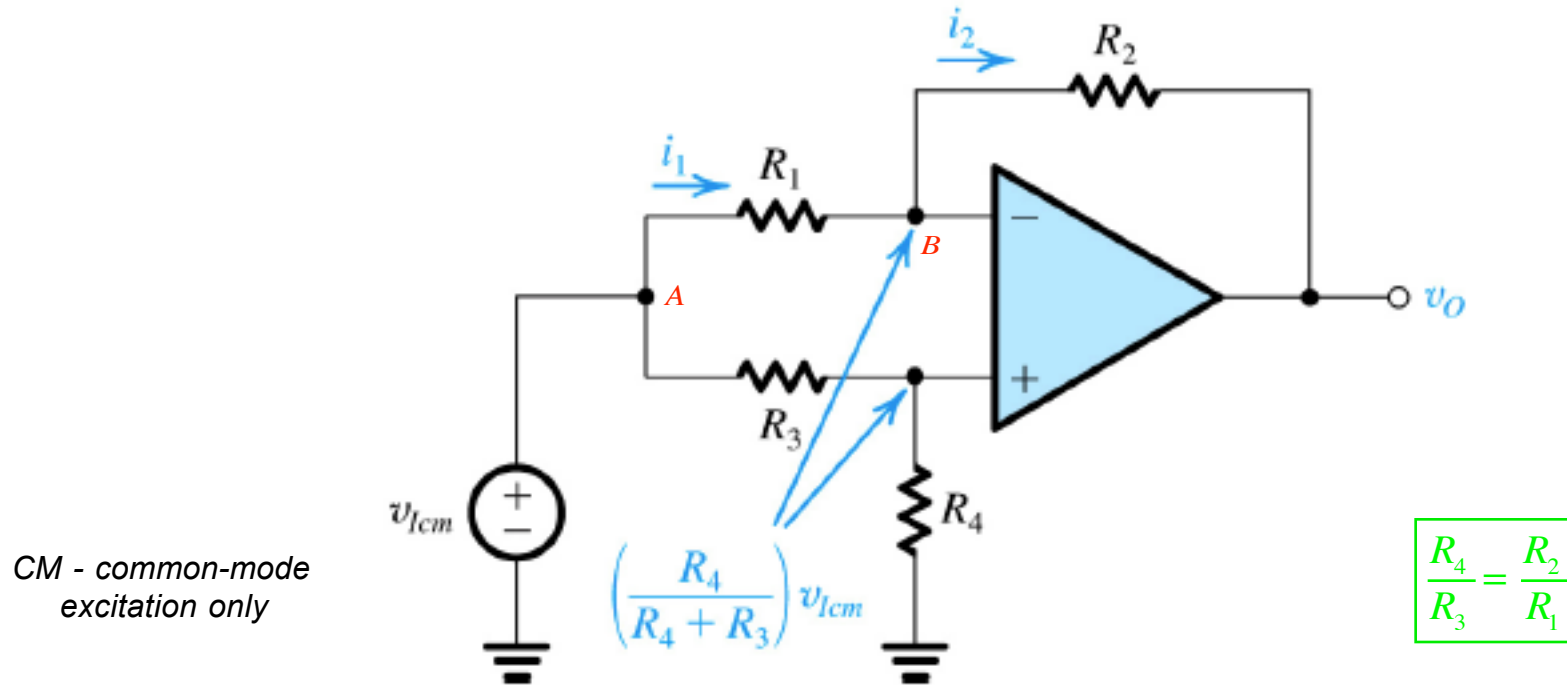Common-mode gain of the difference amplifier



$$i_1 = \frac{v_A - v_B}{R_1} = \frac{1}{R_1} \left(v_{Icm} - \frac{R_4}{R_4 + R_3} v_{Icm} \right) = v_{Icm} \frac{R_3}{R_4 + R_3} \frac{1}{R_1}$$

$$v_O = v_B - i_2 R_2 = \frac{R_4}{R_4 + R_3} v_{Icm} - i_2 R_2 = \frac{R_4}{R_4 + R_3} v_{Icm} - v_{Icm} \frac{R_3}{R_4 + R_3} \frac{R_2}{R_1} = v_{Icm} \left(\frac{R_4}{R_4 + R_3} - \frac{R_3}{R_4 + R_3} \frac{R_2}{R_1} \right) =$$

$$= v_{Icm} \left(\frac{R_4}{R_4 + R_3} - \frac{R_4}{R_4 + R_3} \right) = 0$$


Common-mode gain of the difference amplifier:

$$A_{cm} = \frac{v_O}{v_{Icm}} = \frac{R_4}{R_4 + R_3} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right) = 0$$

when $\frac{R_4}{R_3} = \frac{R_2}{R_1}$

$$\begin{aligned} R_3 &= R_1 \\ R_4 &= R_2 \end{aligned}$$

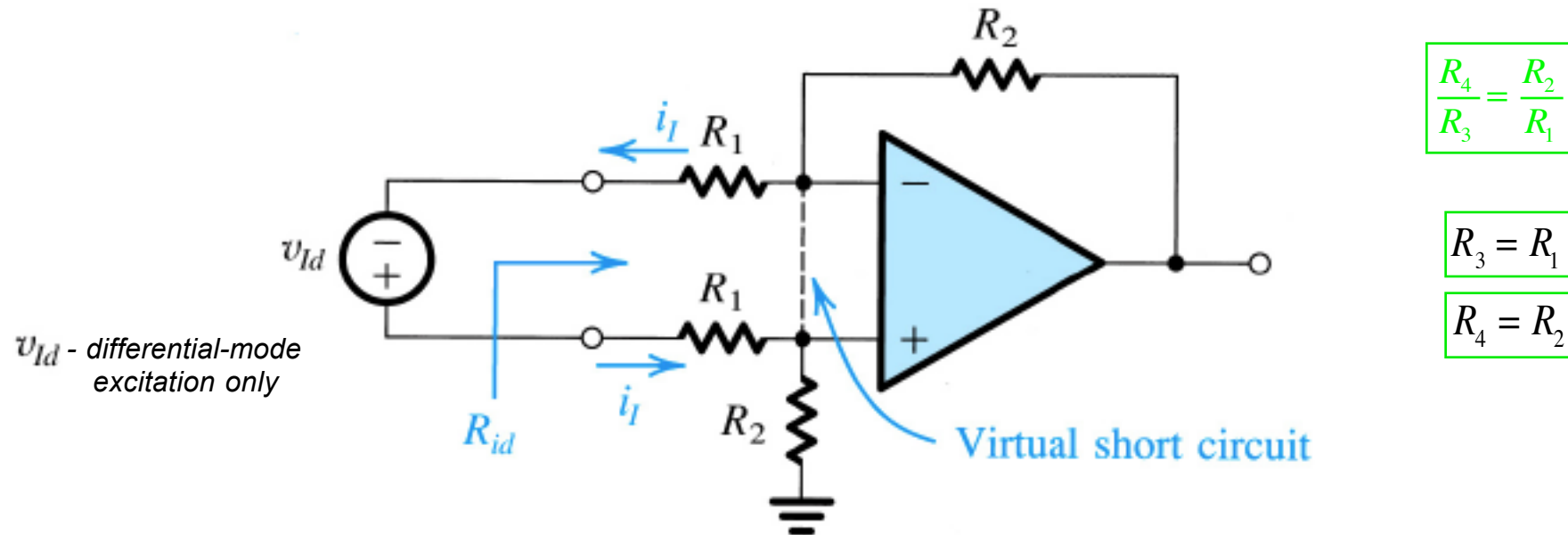Differential input resistance of the difference amplifier




Differential input resistance of the difference amplifier:

$$R_{id} \equiv \frac{v_{Id}}{i_I} = \frac{R_1 i_I + 0 + R_1 i_I}{i_I} = 2R_1$$

Disadvantages of the single op amp difference amplifier:

- small input resistance independent on op amp technology (gain R_2/R_1 must be large)
- to vary differential gain, resistors must be varied simultaneously (a difficult task)

The instrumentation amplifier

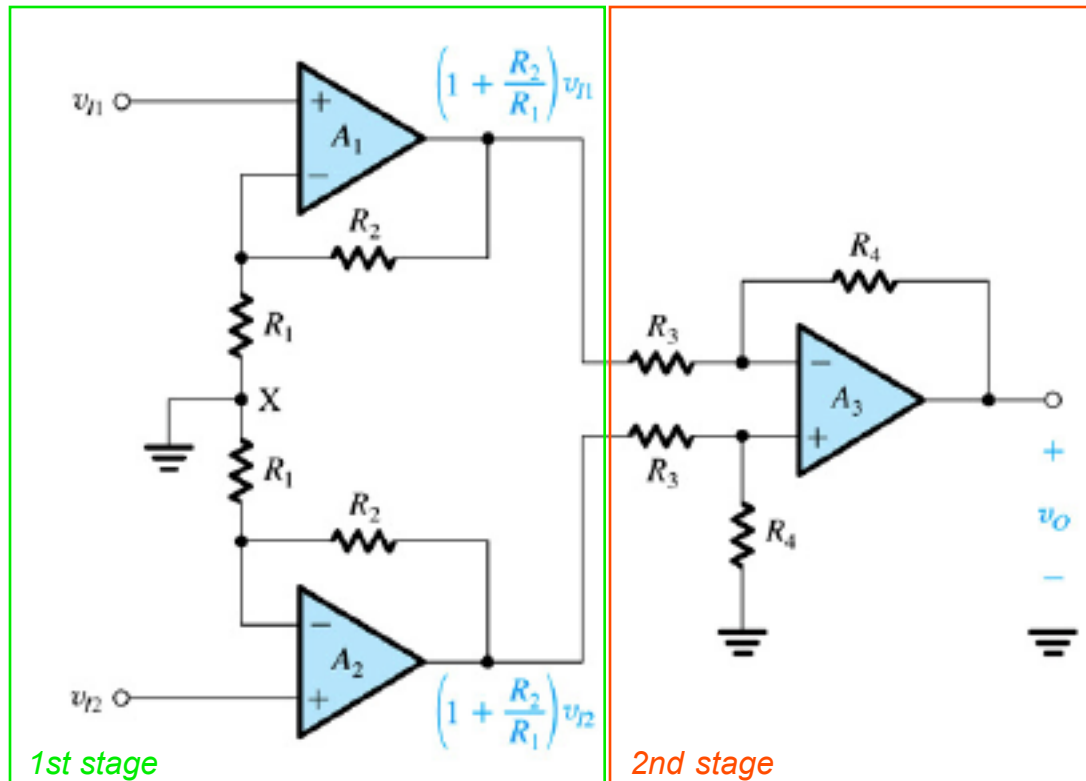

1st stage - noninverting op amps A_1 and A_2 to increase the input resistance

$$A_{1d} = A_{2d} = 1 + \frac{R_2}{R_1}$$

$$R_{id} \approx \infty$$

2nd stage - a single op amp A_3 difference amplifier

$$A_{3d} = \frac{R_4}{R_3}$$


$$A_d = \frac{v_O}{v_{Id}} = \frac{v_O}{v_{I2} - v_{I1}} = A_{1,2d} A_{3d} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3}\right)$$

$$A_{cm} = A_{1,2cm} A_{3cm} = A_{1,2cm} \cdot 0 = 0$$


Disadvantages:

- non-zero common-mode gain of the first stage enlarges CM signal for the second stage
- A_1 and A_2 must be perfectly matched, otherwise their mismatch will be amplified by A_3
- to vary differential gain, two resistors (R_1 , R_2 , etc.) must be varied simultaneously (a difficult task)

The improved instrumentation amplifier

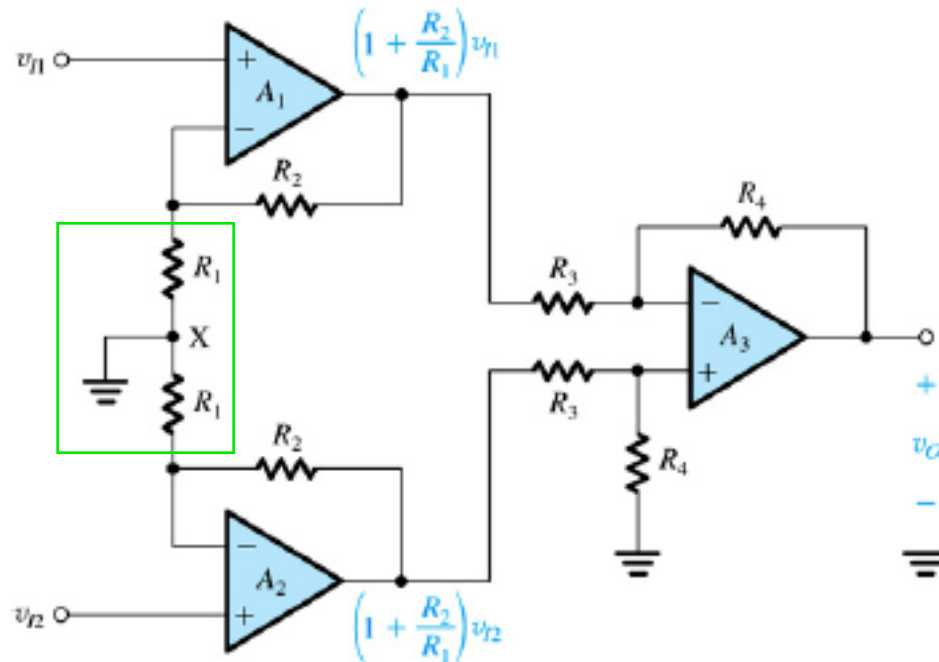


*Original
instrumentation
amplifier*

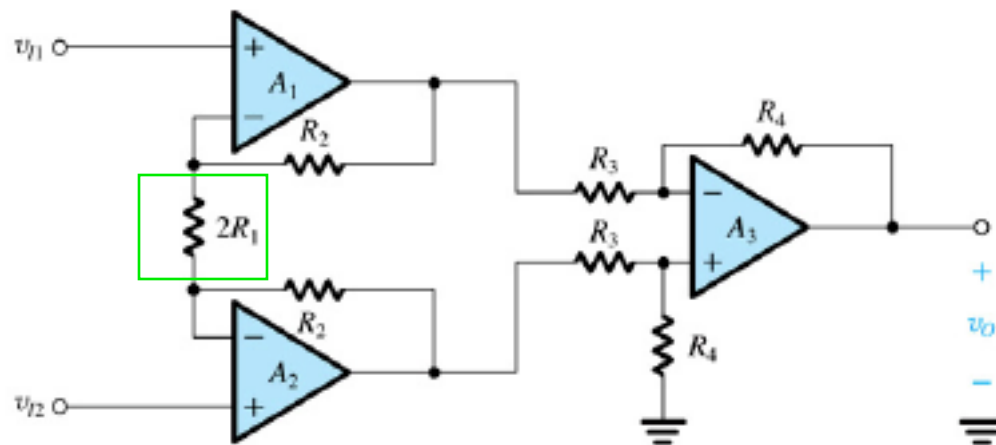

*Improved
instrumentation
amplifier*

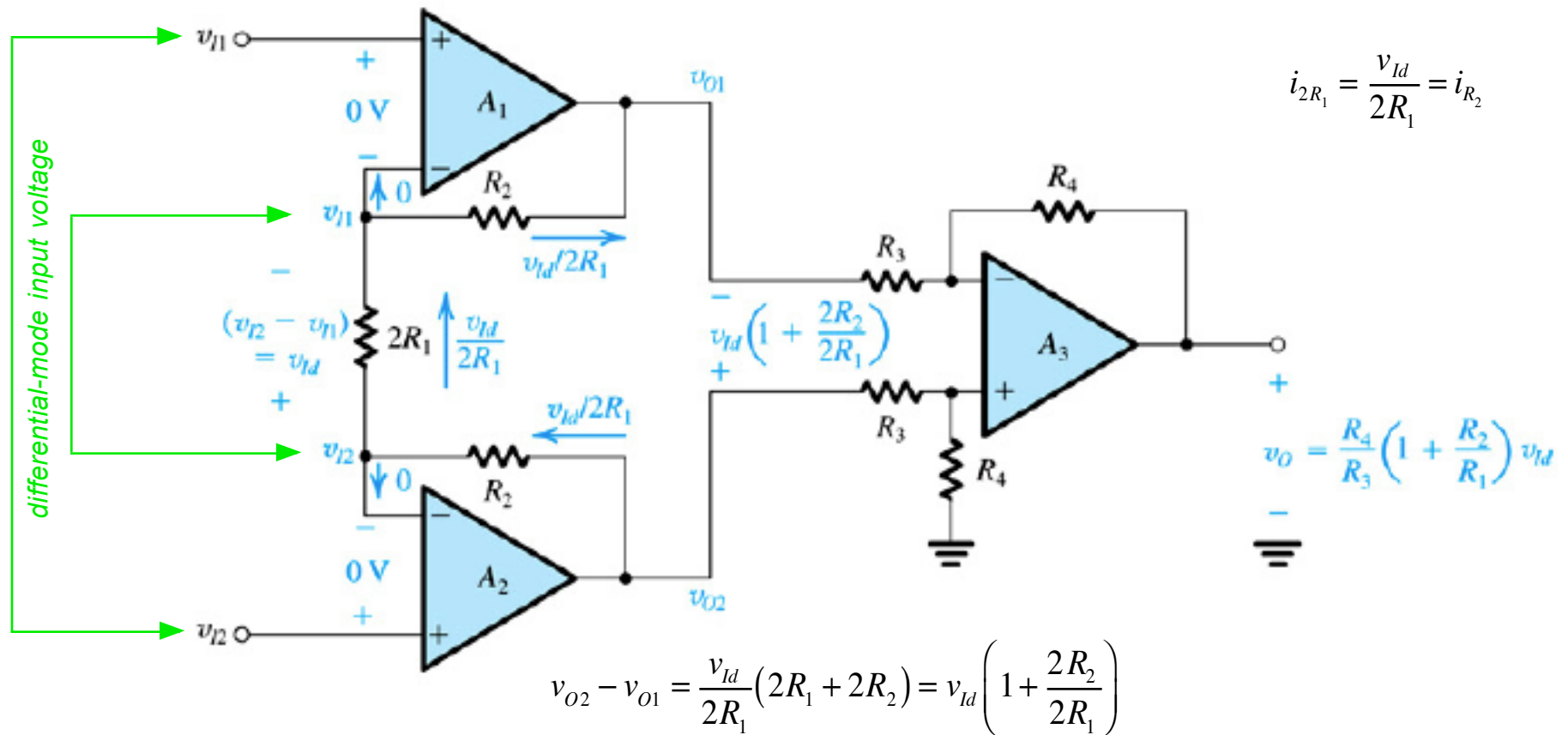Differential gain of the improved instrumentation amplifier



■ Differential gain


$$A_d = \frac{v_O}{v_{Id}} = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1} \right)$$

$$A_d = \frac{v_O}{v_{Id}} = \frac{R_4}{R_3} \left(1 + \frac{R_2' + R_2''}{2R_1} \right)$$

■ Differential gain no longer affected by R_2 mismatch


■ Gain can be varied by changing only one resistor, $2R_1$

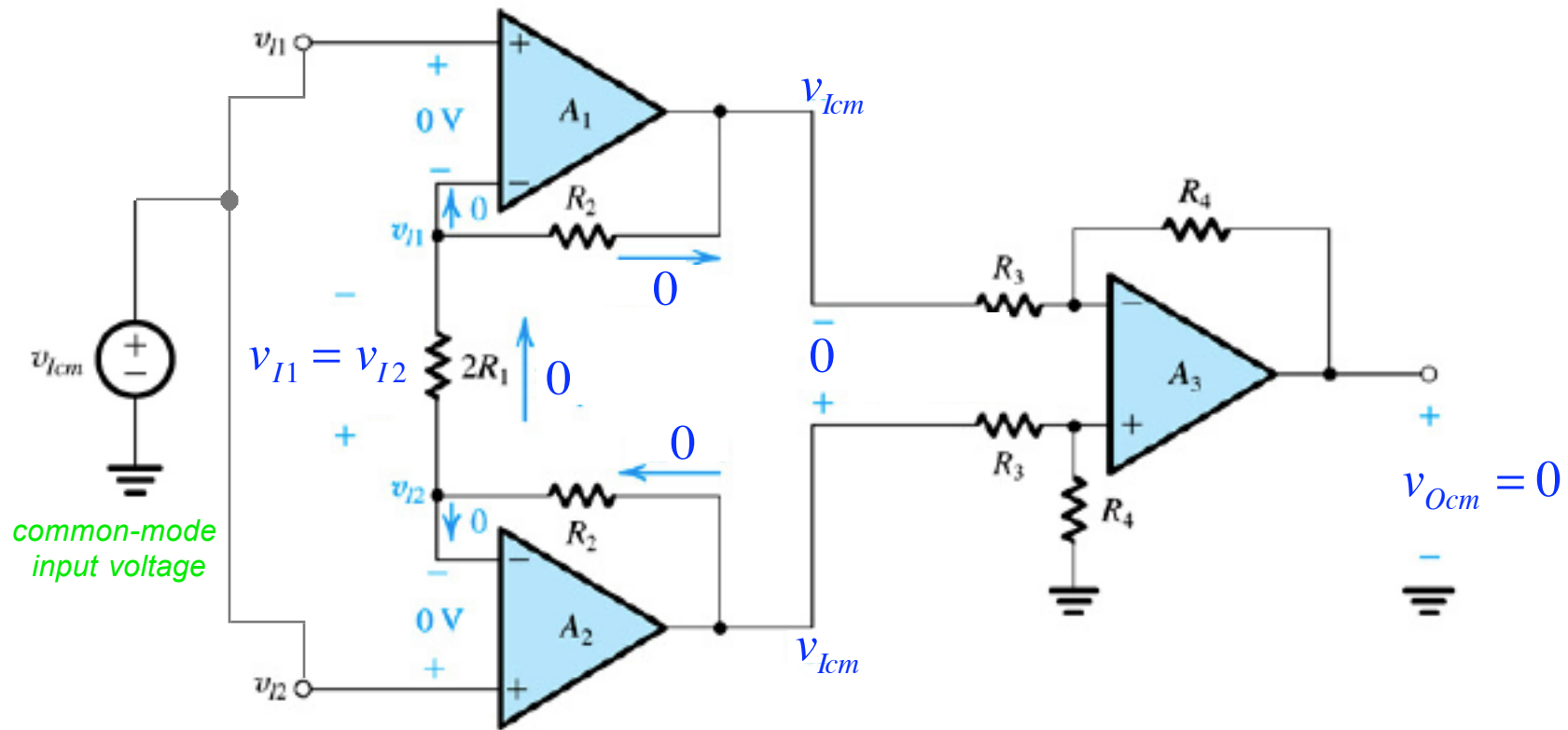Common-mode gain of the improved instrumentation amplifier



- The input stage A_1 , A_2 no longer amplifies the common-mode signal; it simply propagates it to the A_3 input, where it becomes suppressed by A_3 .


Inverting configuration with RC circuits

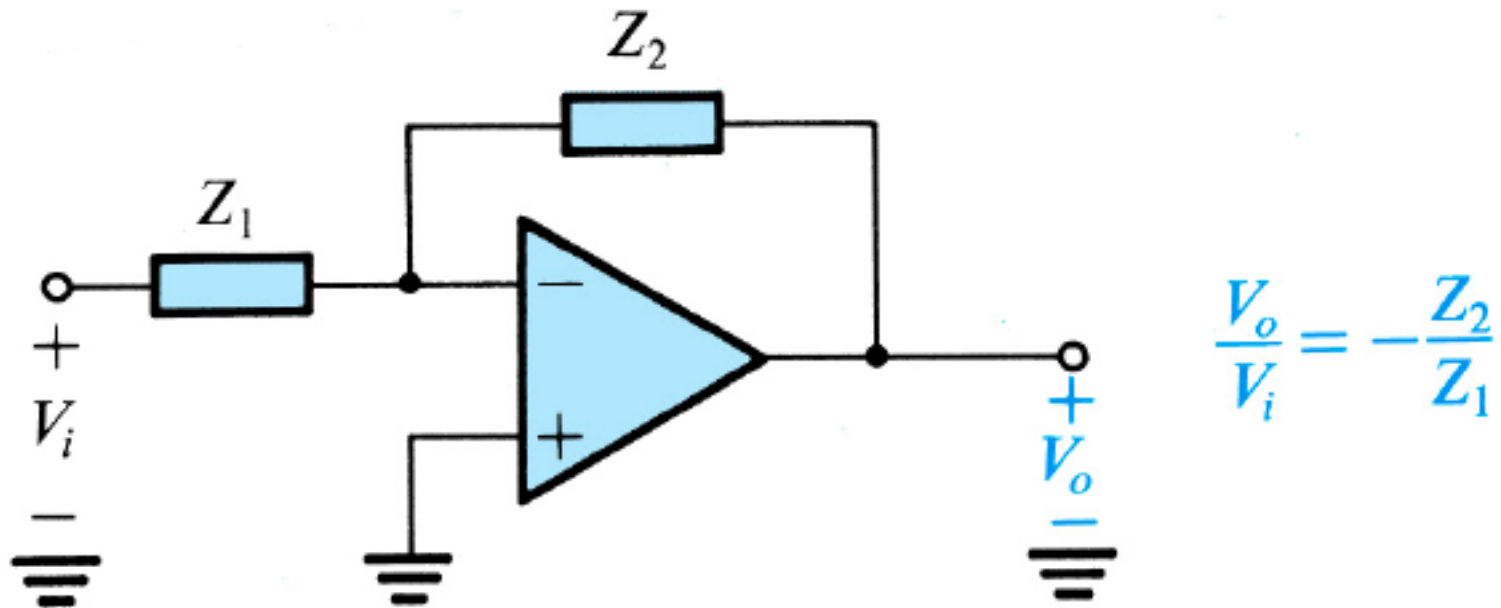

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)}$$

- *Using combinations of RC feedback circuits instead of resistor-only feedback results in new circuits featuring the unique transfer functions that depend on signal frequency ω .*

The inverting integrator

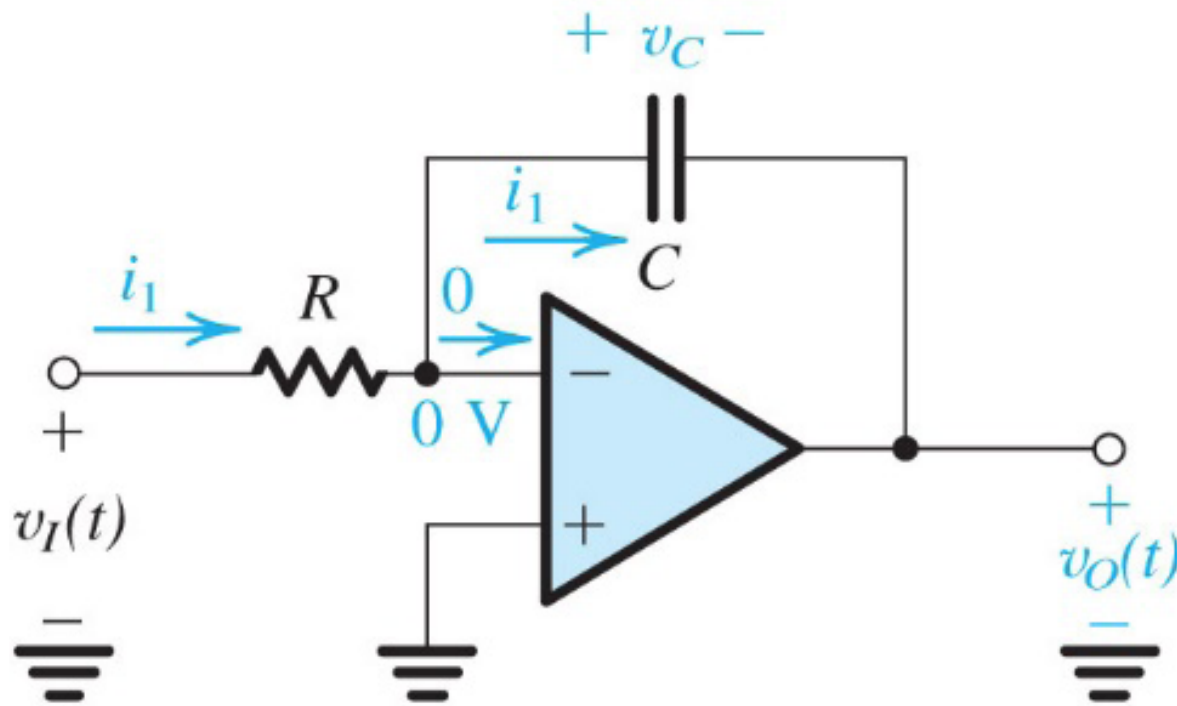

Analysis in the time domain

current through R $i_1(t) = \frac{v_I(t)}{R}$

charge build across C $\int_0^t i_1(t) dt$

voltage across C $\frac{1}{C} \int_0^t i_1(t) dt$


$$v_C(t) = V_C + \frac{1}{C} \int_0^t i_1(t) dt$$

The output voltage $v_O(t) = -\frac{1}{RC} \int_0^t v_I(t) dt - V_C$ where V_C is the initial voltage across C

- The circuit provides an output voltage $v_O(t)$ that is proportional to the time integral of the input voltage $v_I(t)$. The RC product is the *integrator time constant*.

The inverting integrator

Analysis in the frequency domain

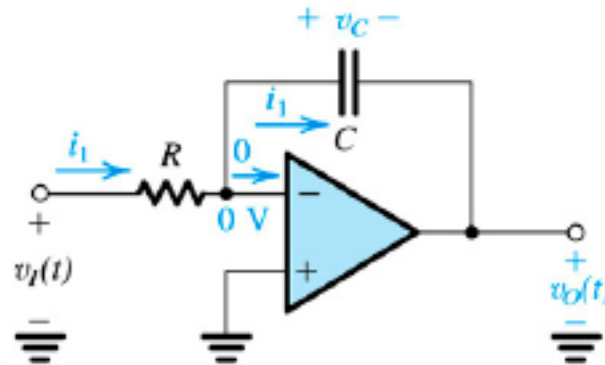


$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)} = -\frac{\frac{1}{sC}}{R} = -\frac{1}{sCR}$$

For physical frequencies $s = j\omega$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{1}{j\omega CR}$$


Magnitude of the transfer function: $\left| \frac{V_o}{V_i} \right| = \frac{1}{j\omega CR}$

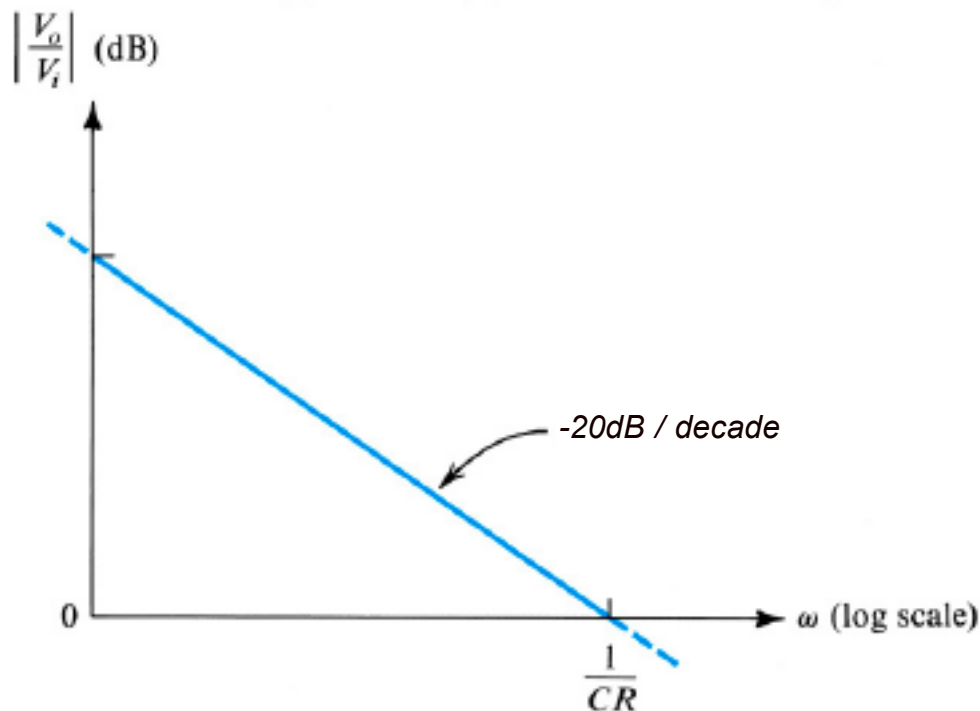

Frequency response of the integrator.

Disadvantage: There is no negative feedback at $\omega = 0$ (-3dB corner frequency), and the gain magnitude is infinite (in practice, the amp does not behave like a linear amplifier and its output voltage is saturated).

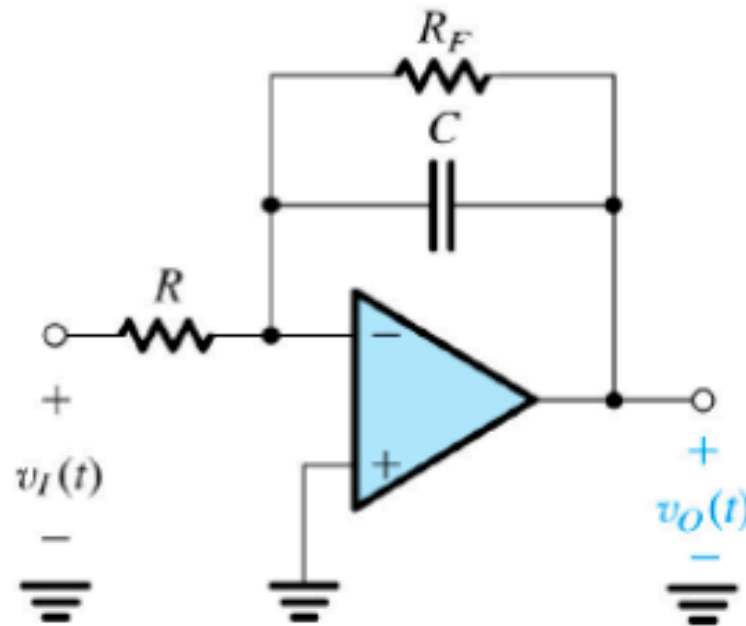The inverting integrator with a finite dc gain




Analysis in the frequency domain

$$\begin{aligned} \frac{V_o(s)}{V_i(s)} &= -\frac{Z_2(s)}{Z_1(s)} = -\frac{1}{Z_1(s)Y_2(s)} = \\ &= -\frac{1}{R\left(\frac{1}{R_F} + sC\right)} = -\frac{1}{\frac{R}{R_F} + sCR} = \frac{-\frac{R_F}{R}}{1 + sCR_F} \end{aligned}$$


For physical frequencies $s = j\omega$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{\frac{R_F}{R}}{1 + j\omega CR_F}$$

Magnitude of the DC gain: $\left|\frac{V_o}{V_i}\right| = \frac{R_F}{R}$

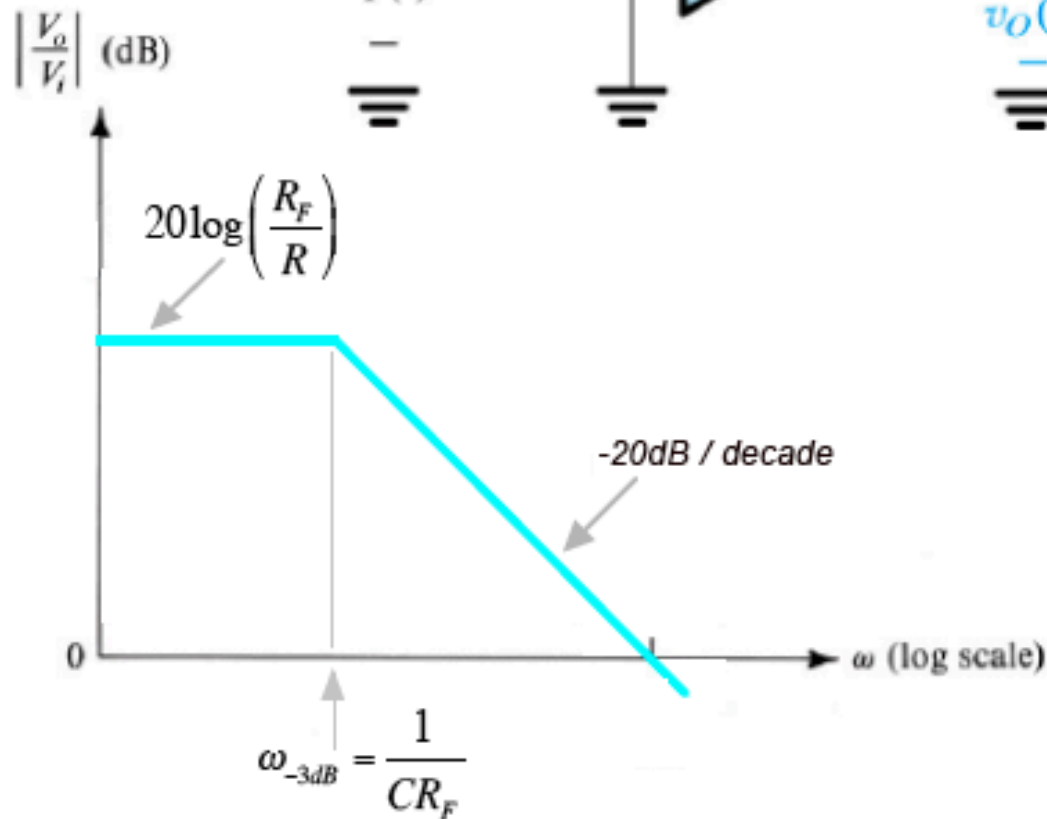

The op amp differentiator

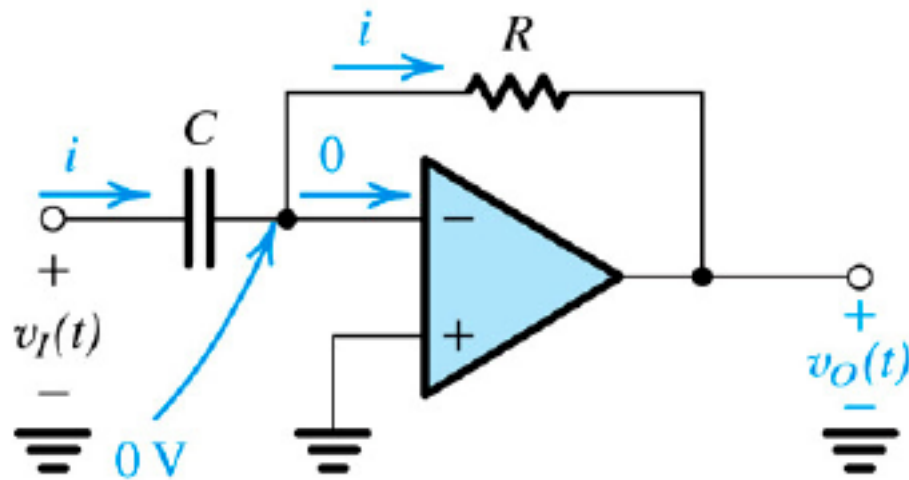


Analysis in the time domain

current through C $i(t) = C \frac{dv_I(t)}{dt}$

the output voltage $v_O(t) = -CR \frac{dv_I(t)}{dt}$

The op amp differentiator

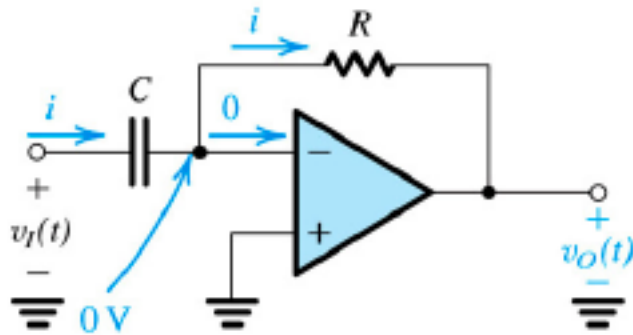


Analysis in the frequency domain

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2(s)}{Z_1(s)} = -\frac{R}{\frac{1}{sC}} = -sCR$$


For physical frequencies $s = j\omega$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = -j\omega CR$$

Magnitude of the transfer function: $\left| \frac{V_o}{V_i} \right| = \omega CR$

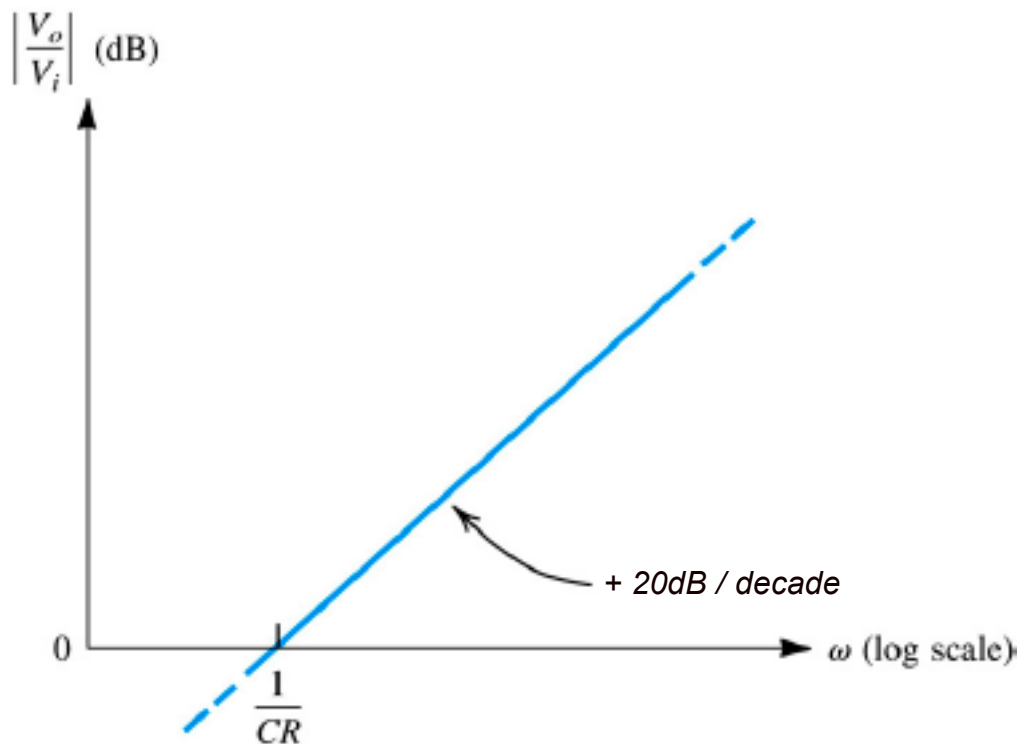

Charge Sensitive Amplifier (CSA)

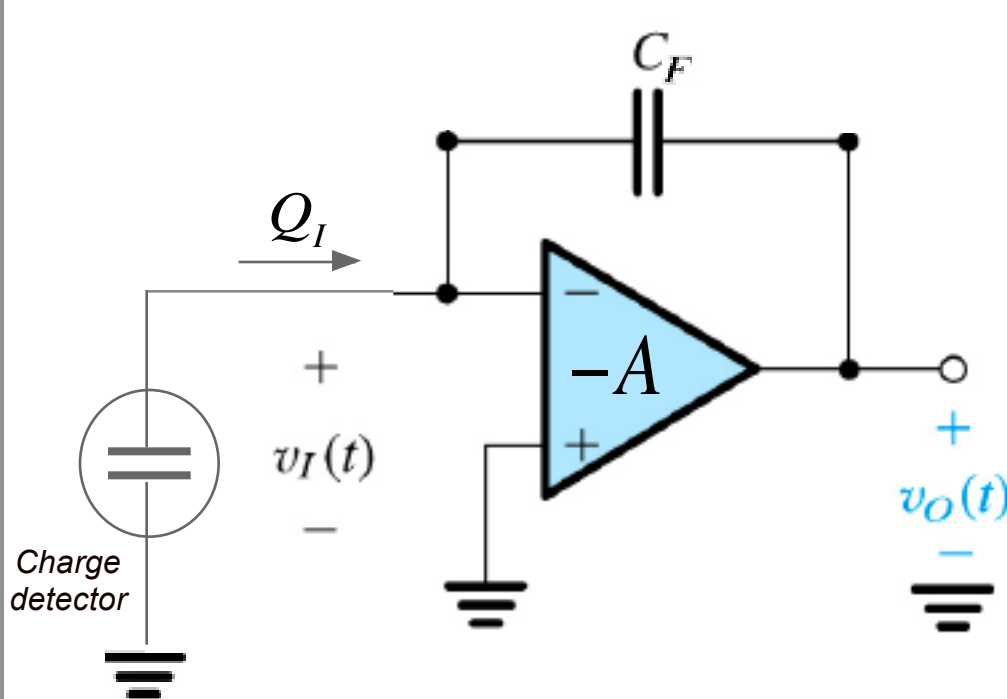

The output voltage $v_O = -Av_I$

The input impedance $Z_I = \infty$

Voltage across C_F

$$v_{C_F} = v_I - v_O = v_I - Av_I = v_I(1 + A)$$

Charge deposited on C_F

$$Q_{C_F} = C_F v_{C_F} = C_F v_I(1 + A)$$

$$Q_I = Q_{C_F} \quad \text{since} \quad Z_I = \infty$$

Effective input capacitance $C_I = \frac{Q_I}{v_I} = C_F(1 + A)$

“Charge” gain $A_Q = \frac{dV_O}{dQ_I} = \frac{Av_I}{C_I v_I} = \frac{A}{C_I} = \frac{A}{C_F(1 + A)} \approx \frac{1}{C_F}$

$$[A_Q] = \frac{\text{Volt}}{\text{Coulomb}} = \frac{1}{\text{Farad}}$$