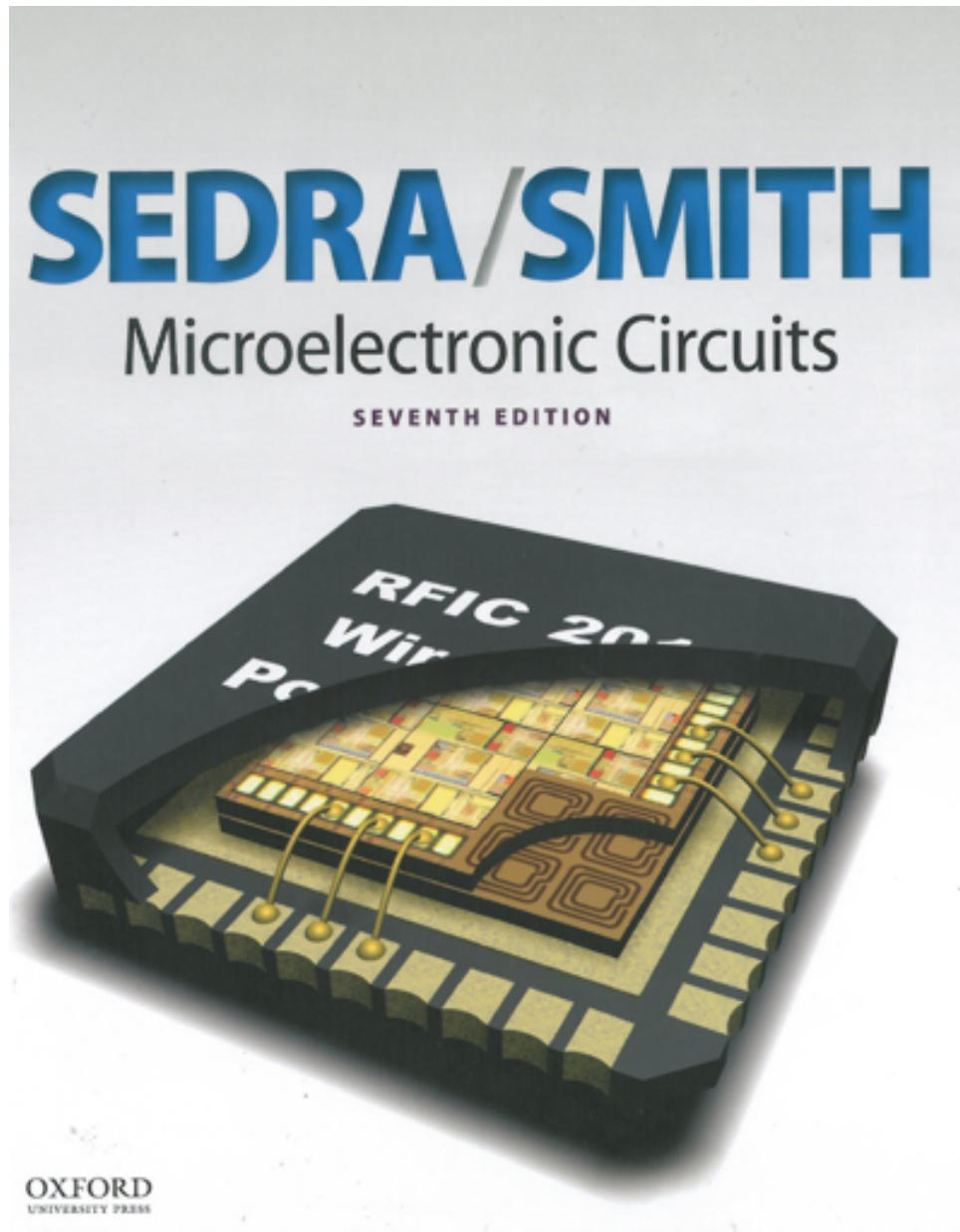




# Small-signal analysis of BJT amplifiers



- ***Amplifier design using BJTs***
  - ***voltage amplifier***
  - ***voltage transfer characteristics***
  - ***small-signal voltage gain***
- ***Small-signal parameters of BJTs operating as amplifiers***
- ***Small-signal BJT models***
  - ***the hybrid- $\pi$  model***
  - ***the T model***
- ***Small-signal analysis using small-signal models***

***Textbook material for self-study:  
Sec.7.1-7.2 - BJT small-signal  
operation and models***

# Simple voltage amplifier using BJT

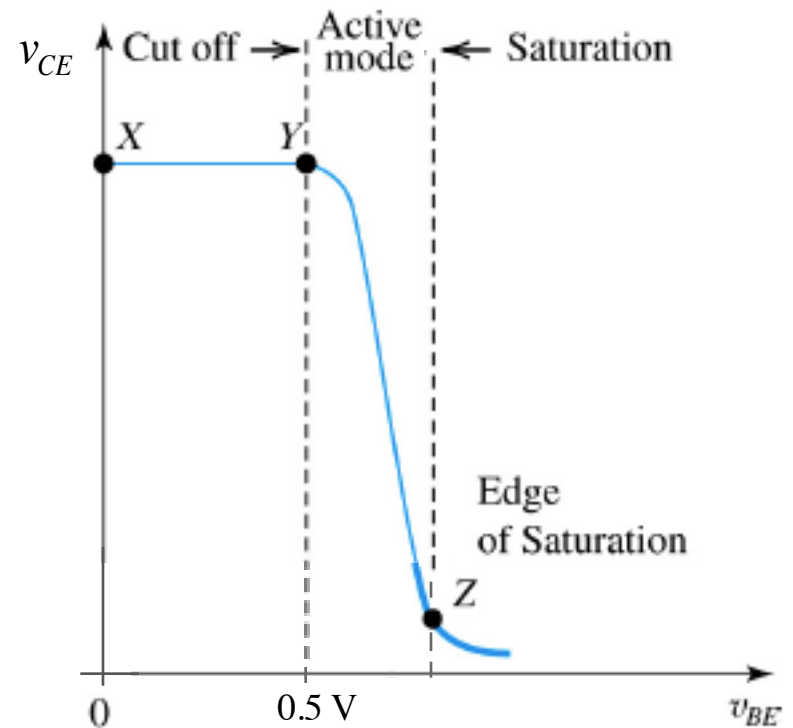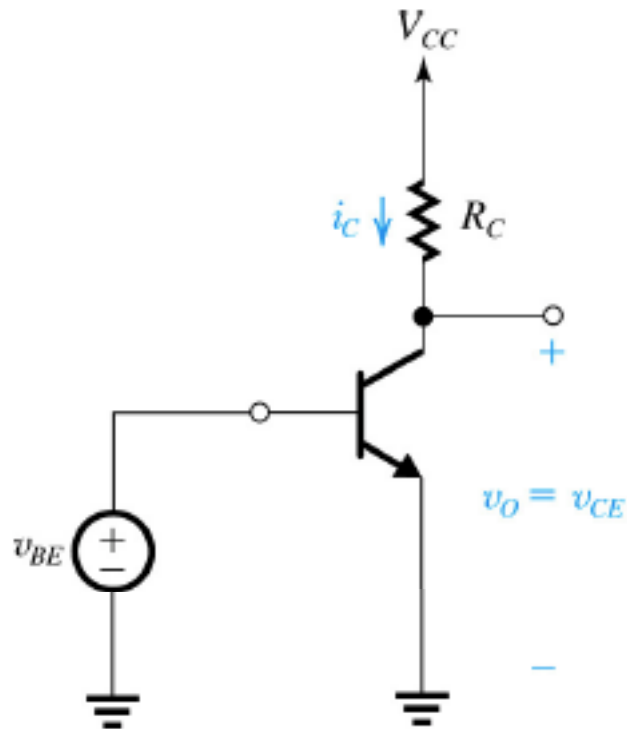



$$v_{CE} = V_{CC} - i_C R_C$$

$$i_C = I_S \exp\left(\frac{v_{BE}}{V_{th}}\right)$$

$$v_{CE} = V_{CC} - R_C I_S \exp\left(\frac{v_{BE}}{V_{th}}\right)$$

$$V_{th} = \frac{kT}{q} = 25.9 \text{ mV} \text{ at } T \approx 300 \text{ K}$$
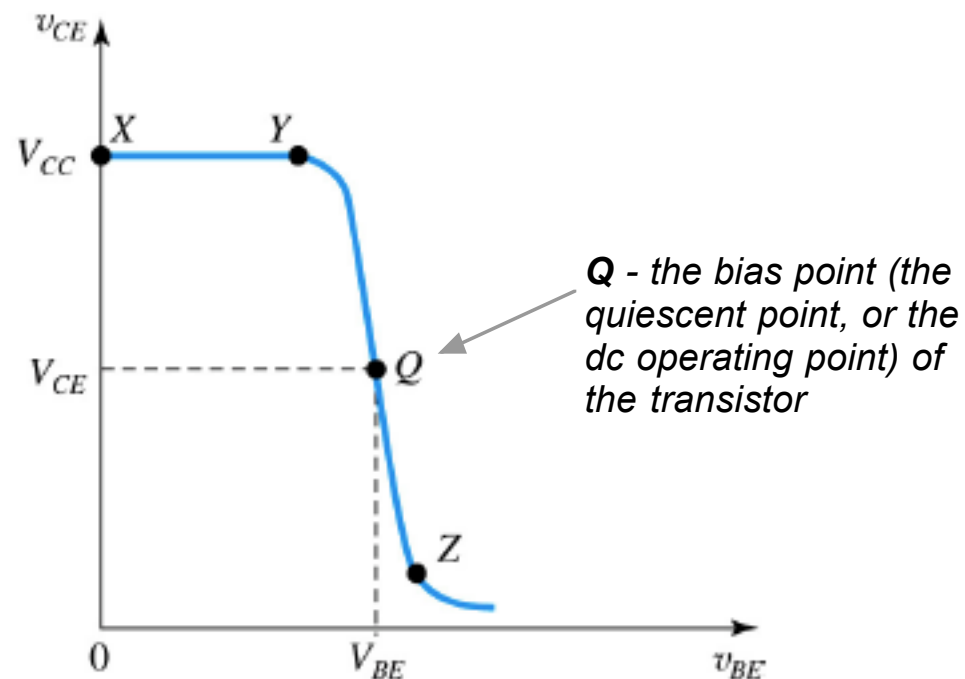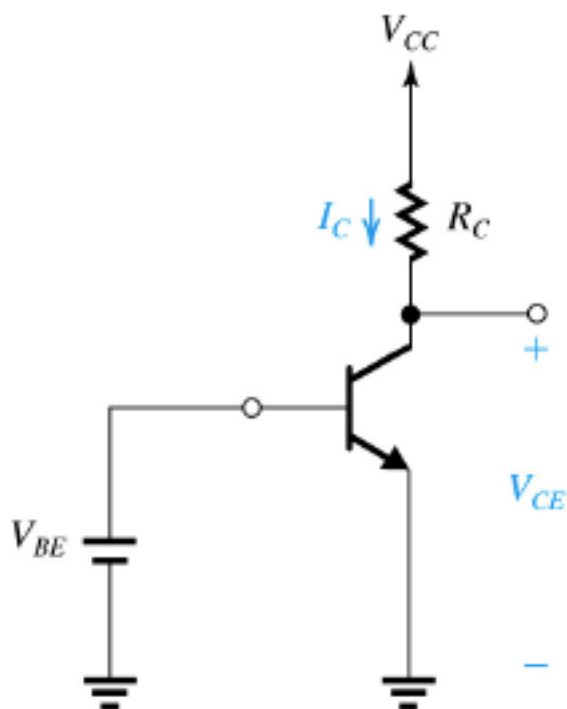
# Biasing the BJT in the voltage amplifier





*The bias point **Q** must be located on the active-mode segment of the voltage transfer curve (VTC)*

$$V_{CE} = V_{CC} - R_C I_S \exp\left(\frac{V_{BE}}{V_{th}}\right)$$

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_{th}}\right)$$

$$V_{th} = \frac{kT}{q} = 25.9 \text{ mV at } T \approx 300 \text{ K}$$

# Application of the small signal

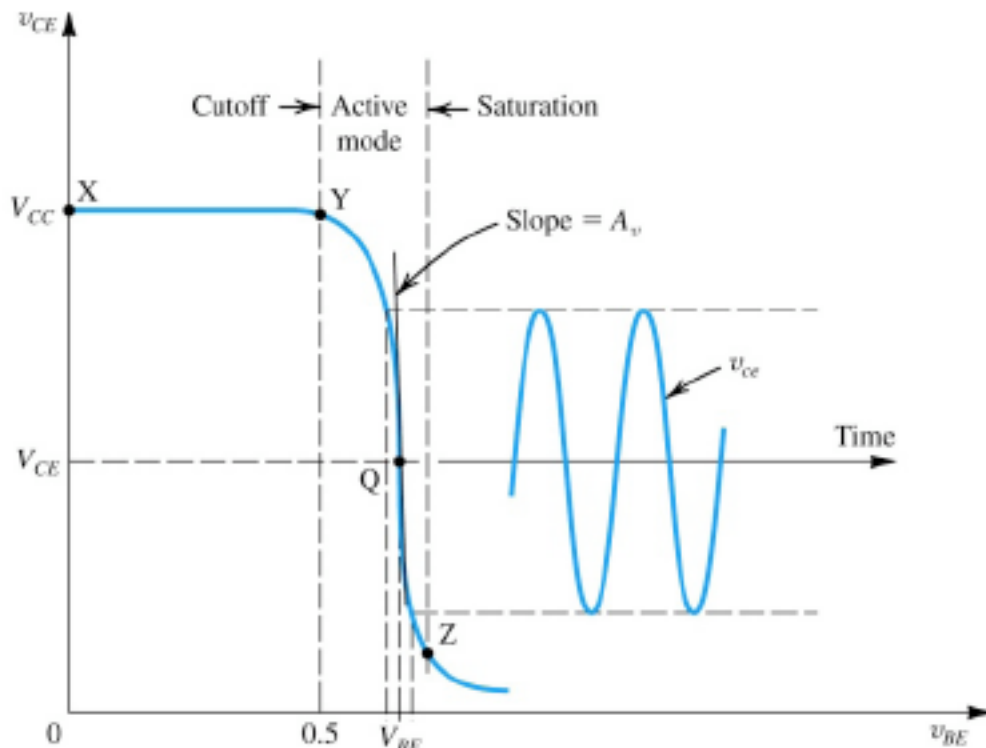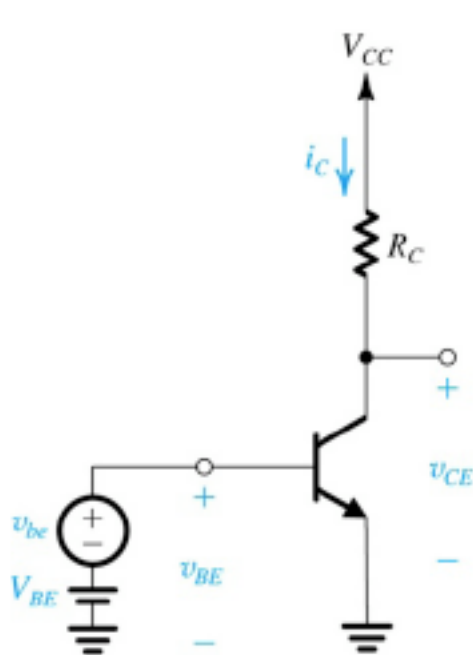


the instantaneous value  
of Base-Emitter voltage

the ac value

$$v_{BE} = V_{BE} + v_{be}(t)$$

$$v_{CE} = V_{CE} + v_{ce}(t)$$


the dc value  
(the Q point)

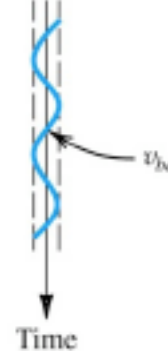

The **small-signal** definition

$$v_{be} \ll V_{th} = \frac{kT}{q}$$

# The small-signal voltage gain

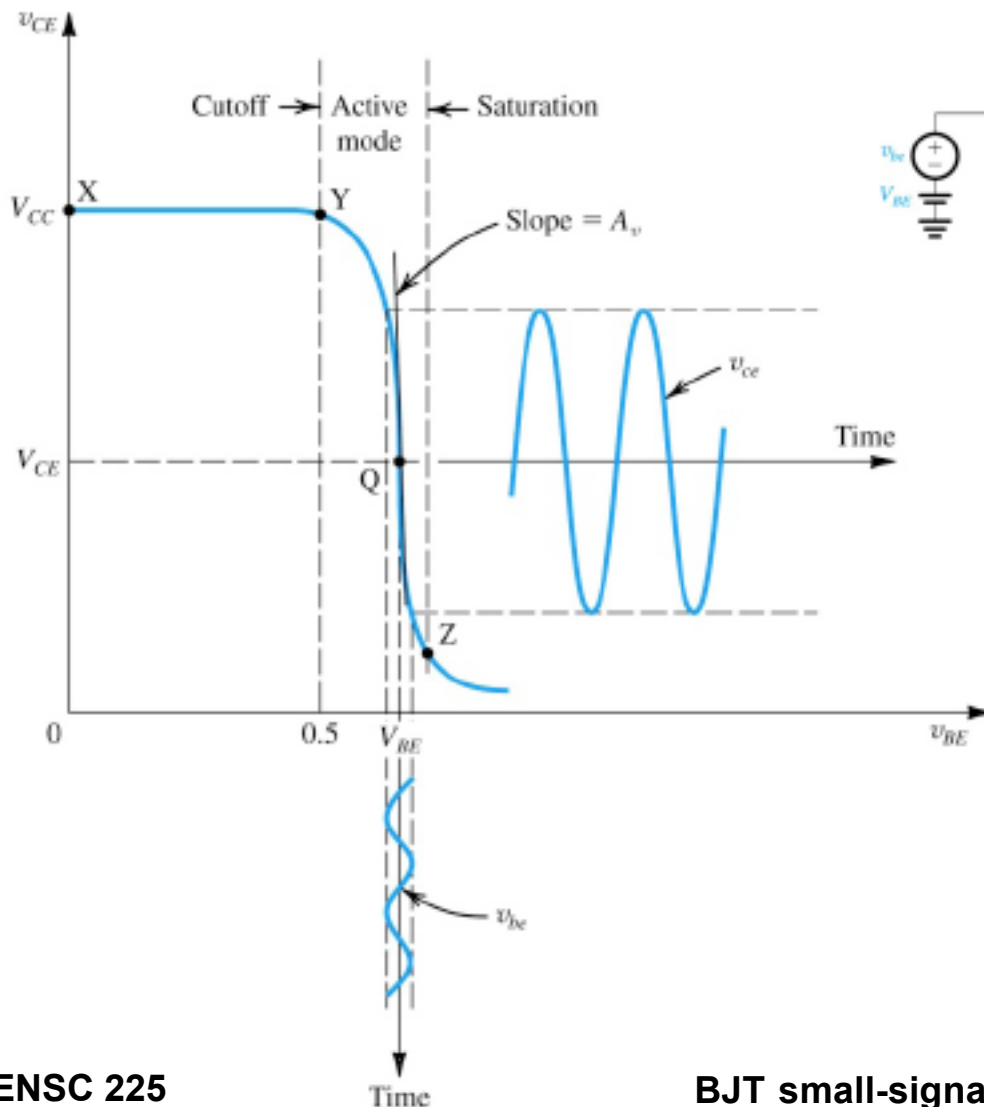

$$A_v = \left. \frac{dv_{CE}}{dv_{BE}} \right|_{v_{BE}=V_{BE}}$$

$$v_{CE} = V_{CC} - R_C I_S \exp\left(\frac{v_{BE}}{V_{th}}\right)$$


$$\begin{aligned} A_v &= \left. \frac{dv_{CE}}{dv_{BE}} \right|_{v_{BE}=V_{BE}} = \left. \frac{d\left[V_{CC} - R_C I_S \exp\left(\frac{v_{BE}}{V_{th}}\right)\right]}{dv_{BE}} \right|_{v_{BE}=V_{BE}} = \\ &= -\left(I_S \exp\left(\frac{V_{BE}}{V_{th}}\right)\right) \frac{R_C}{V_{th}} = -\left(\frac{I_C}{V_{th}}\right) R_C \end{aligned}$$

- The amplifier is inverting - there is a  $180^\circ$  phase shift between the output and the input

$$A_v = -\left(\frac{I_C}{V_{th}}\right) R_C = -\frac{V_{R_C}}{V_{th}} = -\frac{V_{CC} - V_{CE}}{V_{th}}$$

- The gain of the amplifier is proportional to the collector bias current and the load resistance


# Graphical method of constructing VTC

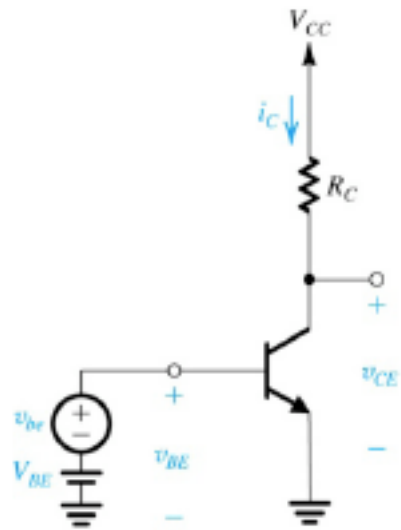


$$v_{CE} = V_{CC} - i_C R_C$$

$$i_C = \frac{1}{R_C} (V_{CC} - v_{CE})$$


$$i_C = i_{R_C}$$

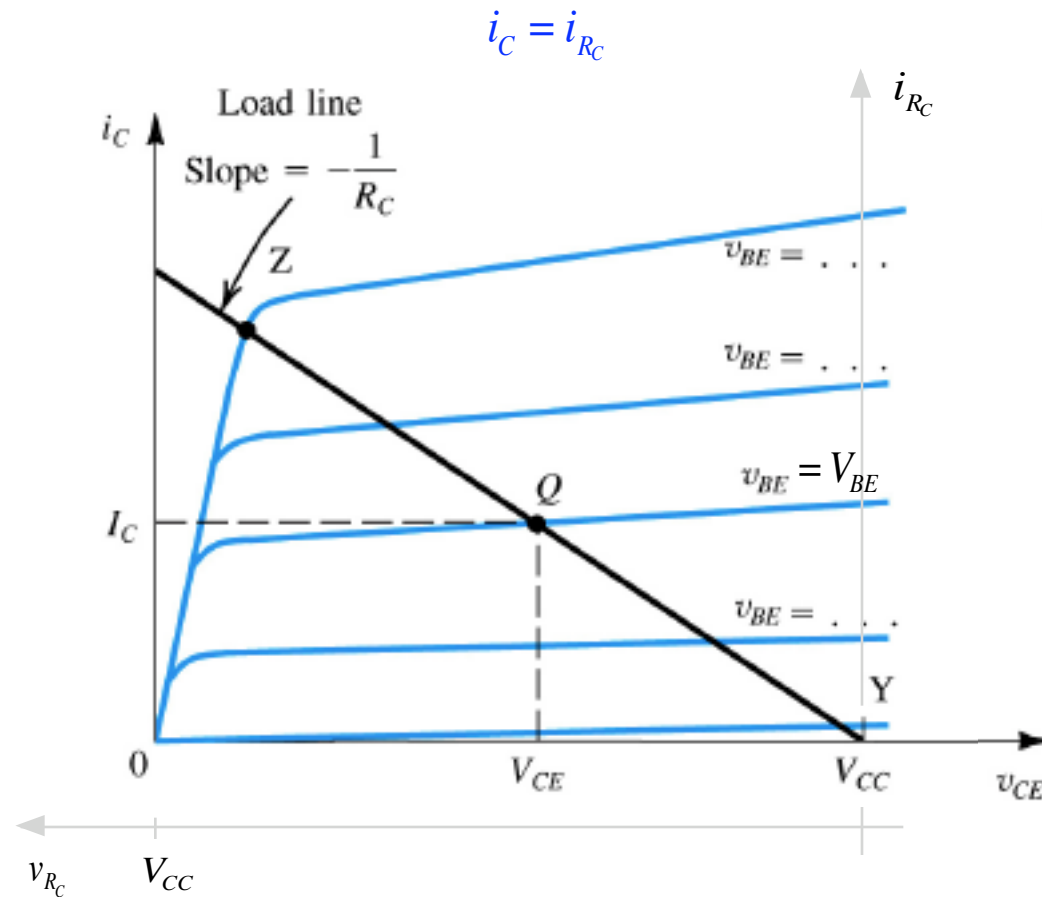
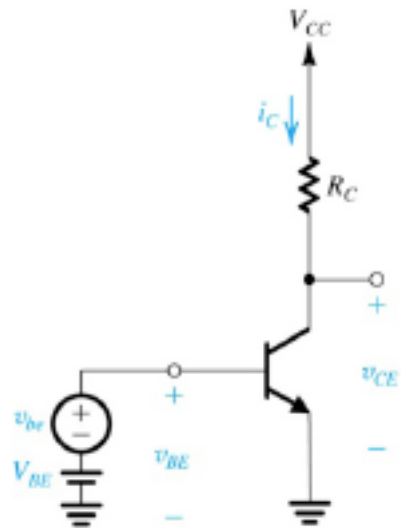
# Effect of bias-point location on allowable voltage swing




$$i_C = \frac{1}{R_C}(V_{CC} - v_{CE})$$

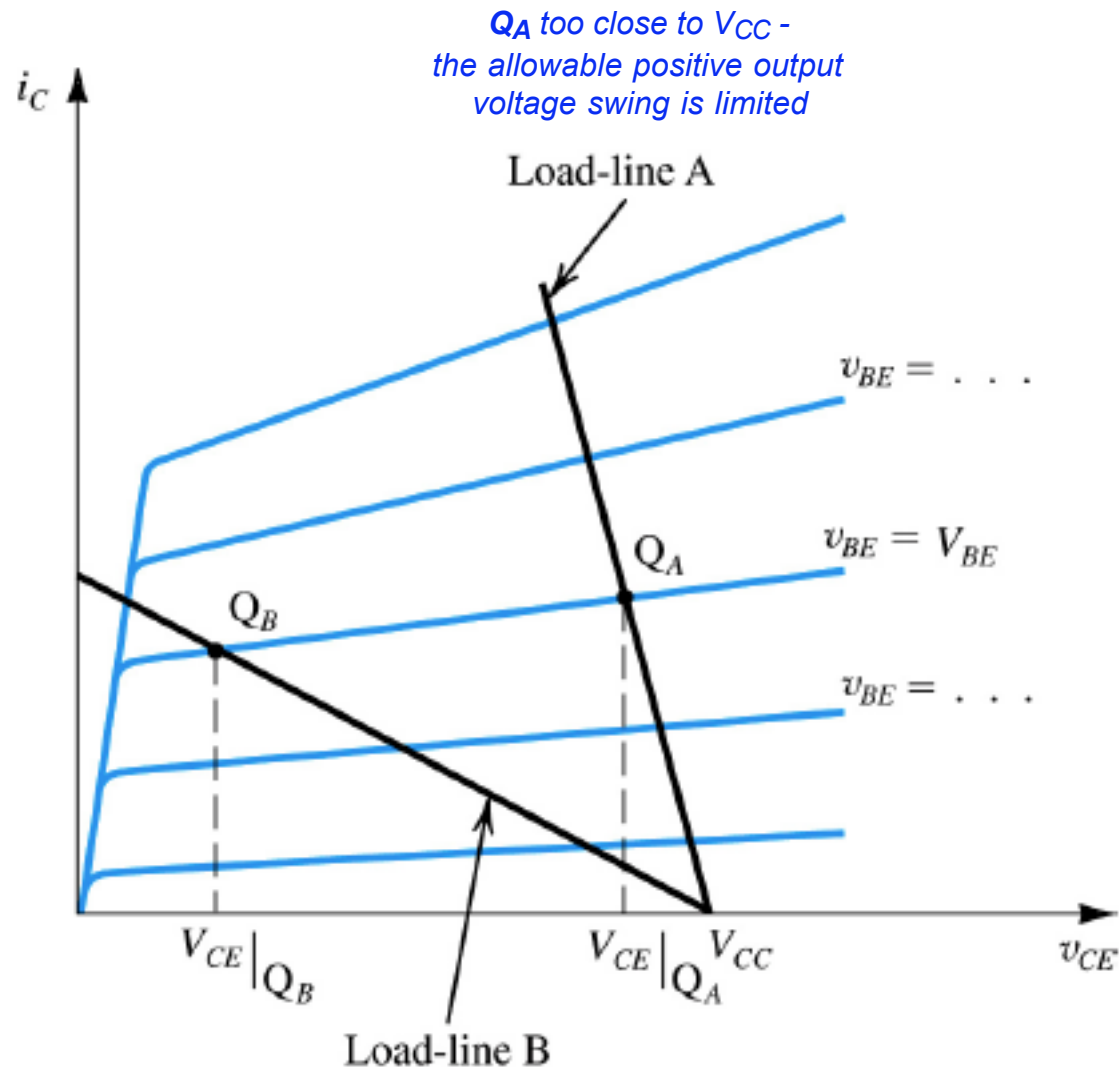



*$Q_B$  too close to saturation region -  
BJT saturation limits the allowable  
negative output voltage swing*

# Amplifier's linearity limits

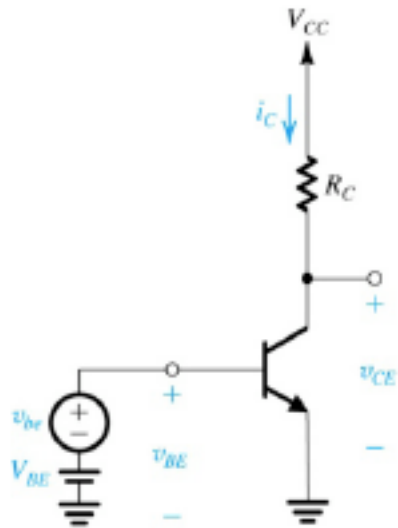

$Q_A$  too close to  $V_{CC}$  -  
the allowable positive output  
voltage swing is limited

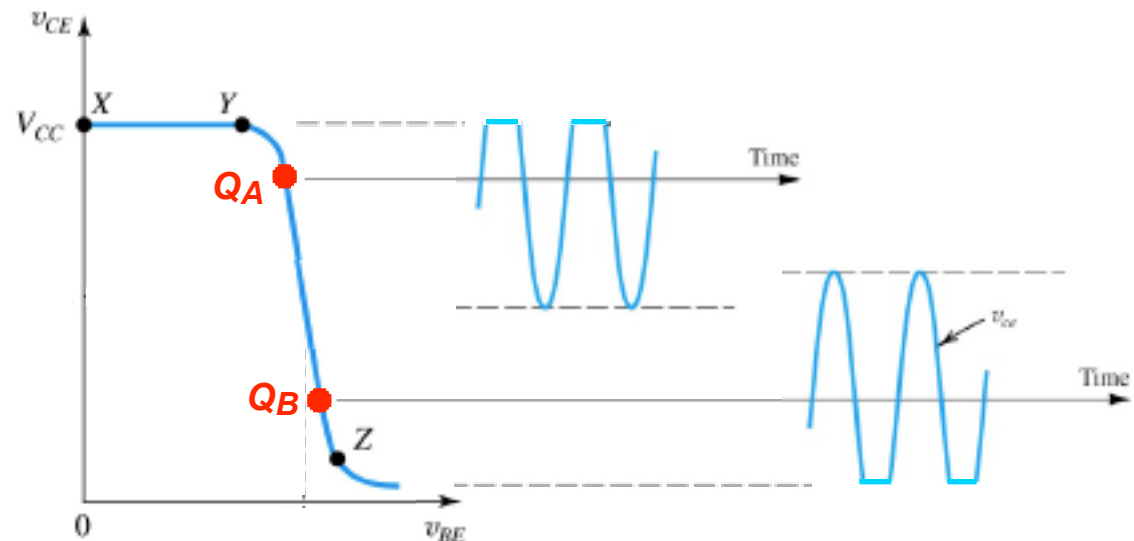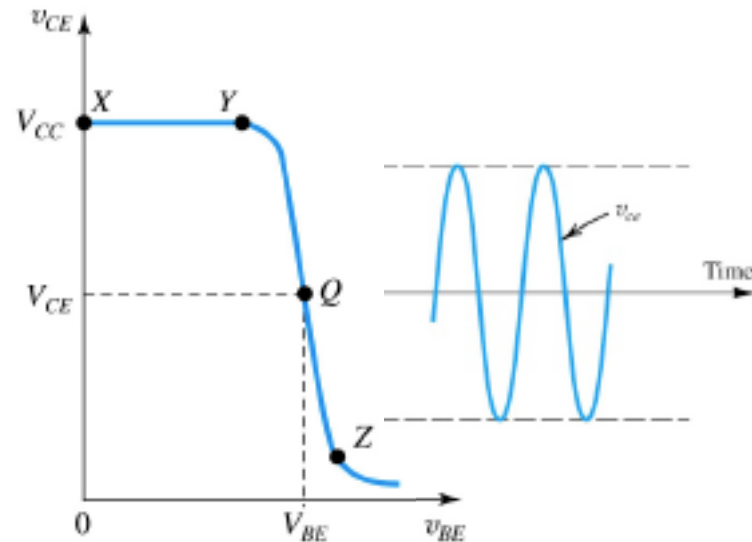
$Q_B$  too close to saturation region -  
BJT saturation limits the allowable  
negative output voltage swing




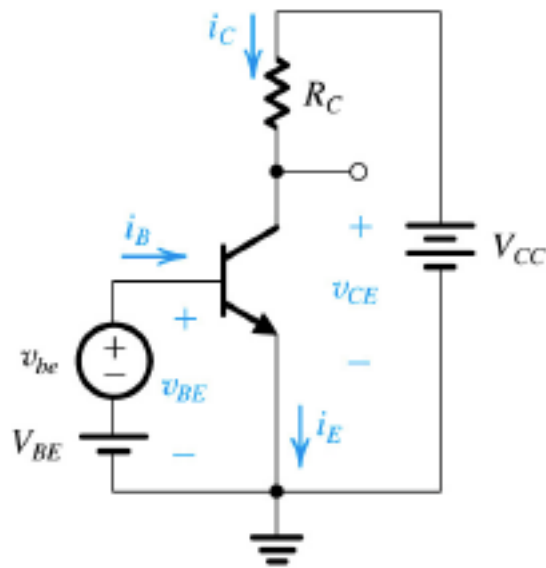
# DC and small-signal analysis

Amplifier circuit with both dc bias and signal source




$$v_{BE} = V_{BE} + v_{be}$$

$$v_{CE} = V_{CE} + v_{ce}$$

$$i_C = I_C + i_c$$

Circuit for dc (bias) analysis

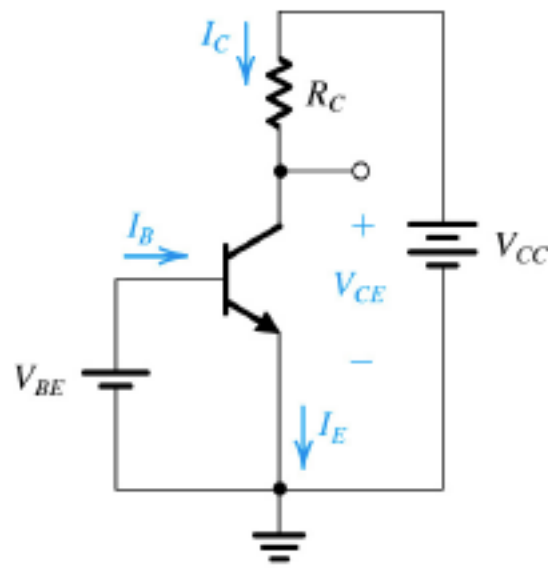


$$I_C = I_s \exp\left(\frac{V_{BE}}{V_{th}}\right)$$

$$I_E = \frac{I_C}{\alpha}$$

$$I_B = \frac{I_C}{\beta}$$


$$V_{CE} = V_{CC} - R_C I_C$$

Circuit for small-signal analysis

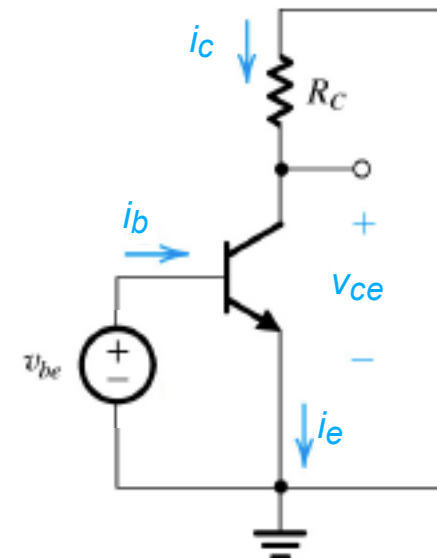
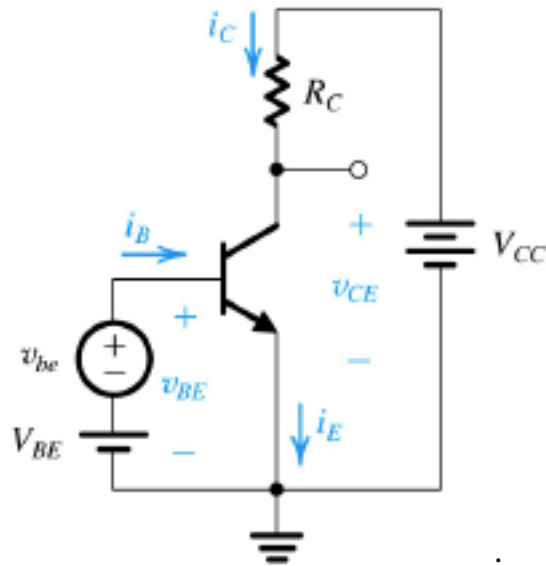
# Small-signal transconductance of the BJT

Amplifier circuit with both dc bias and signal source




$$v_{BE} = V_{BE} + v_{be}$$

$$\begin{aligned} i_C &= I_s \exp\left(\frac{v_{BE}}{V_{th}}\right) = I_s \exp\left(\frac{V_{BE} + v_{be}}{V_{th}}\right) = \\ &= I_s \exp\frac{V_{BE}}{V_{th}} \exp\frac{v_{be}}{V_{th}} = I_C \exp\frac{v_{be}}{V_{th}} \end{aligned}$$

$$i_C = I_C \exp\frac{v_{be}}{V_{th}} \approx I_C \left(1 + \frac{v_{be}}{V_{th}}\right) = I_C + \frac{I_C}{V_{th}} v_{be} = I_C + i_c$$

$$i_c = \frac{I_C}{V_{th}} v_{be} = g_m v_{be} \qquad g_m = \frac{I_C}{V_{th}}$$


Circuit for small-signal analysis

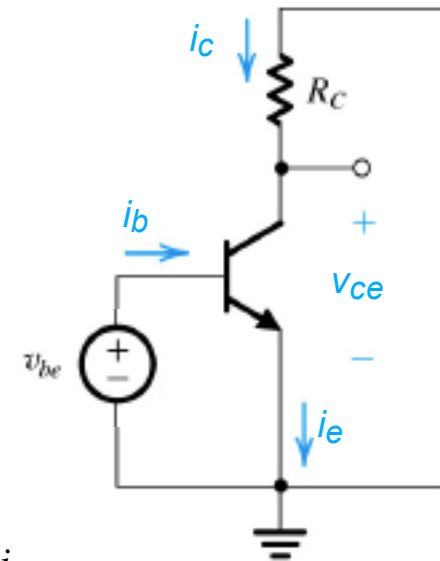


Transconductance of the bipolar transistor

$$g_m = \left. \frac{\delta i_C}{\delta v_{BE}} \right|_{i_C = I_C}$$
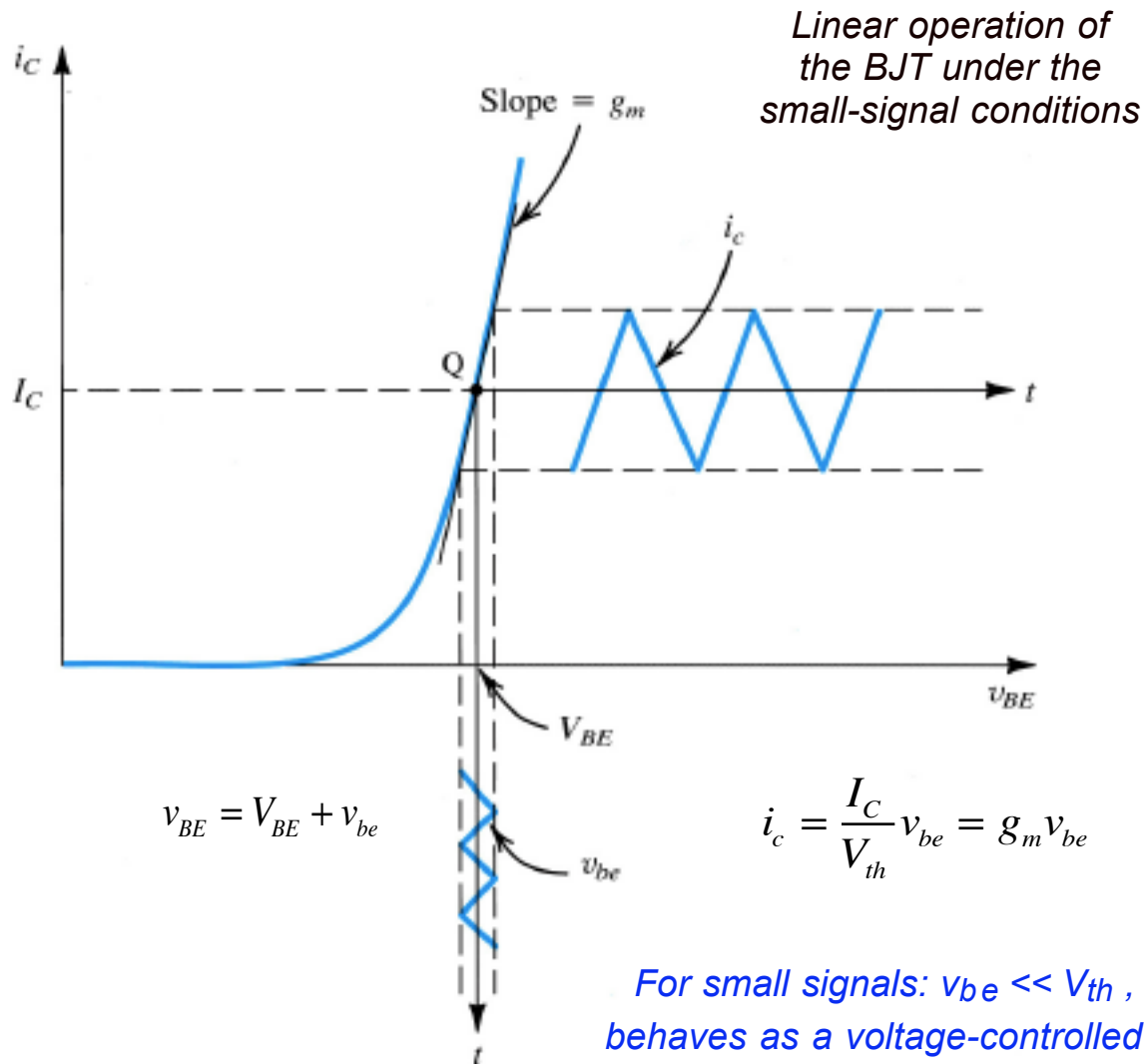
# Small-signal transconductance of the BJT



Circuit for small-signal analysis

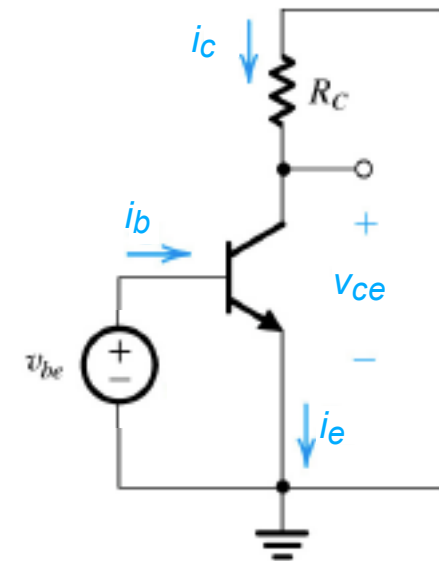


$$g_m = \frac{I_C}{V_{th}}$$

For small signals:  $v_{be} \ll V_{th}$ , the transistor behaves as a voltage-controlled current source

BJT transconductance :  $g_m \approx 40 \text{ mA/V}$  at  $I_C = 1 \text{ mA}$


# Voltage gain of the BJT amplifier

*Circuit for small-signal analysis*

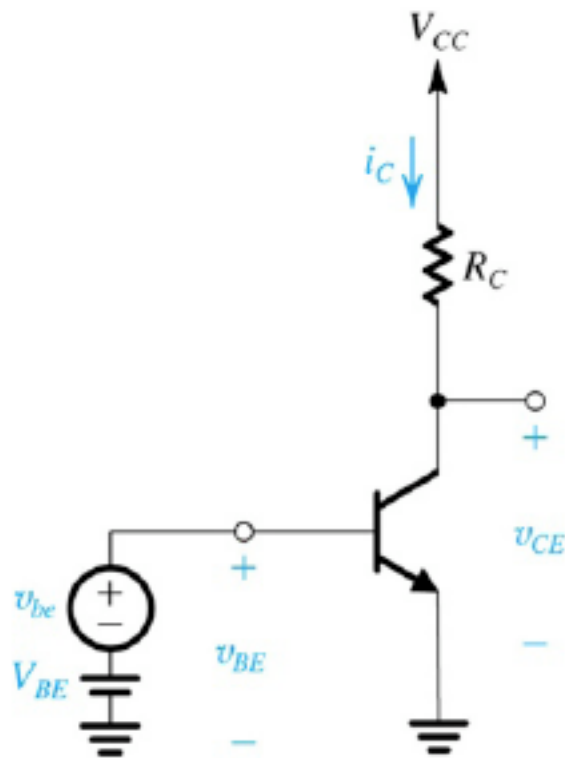

$$A_v = -\left(\frac{I_C}{V_{th}}\right) R_C = -g_m R_C$$

$$g_m = \frac{I_C}{V_{th}}$$

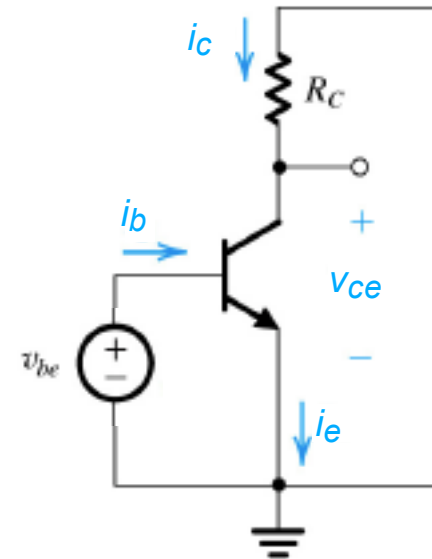

$$v_{ce} = -i_c R_C = -g_m v_{be} R_C$$


$$A_v = \frac{v_{ce}}{v_{be}} = -g_m R_C$$

$$A_v = -g_m R_C$$

*Voltage gain of the BJT amplifier shown above is directly proportional to BJT transconductance  $g_m$  and the load resistance  $R_C$ .*

# Small-signal input resistance at the Base

*Circuit for small-signal analysis*

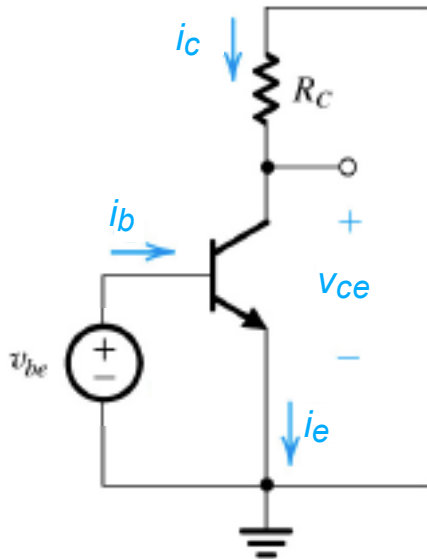


$$i_B = \frac{i_C}{\beta} = \frac{1}{\beta} \left( I_C + \frac{I_C}{V_{th}} v_{be} \right) = \frac{I_C}{\beta} + \frac{I_C}{\beta V_{th}} v_{be} = I_B + i_b$$

$$i_b = \frac{I_C}{\beta V_{th}} v_{be} = \frac{g_m}{\beta} v_{be}$$

$r_\pi$  - small-signal input resistance between Base and Emitter, looking into the Base.


$$r_\pi \equiv \frac{v_{be}}{i_b} = \frac{\beta}{g_m}$$
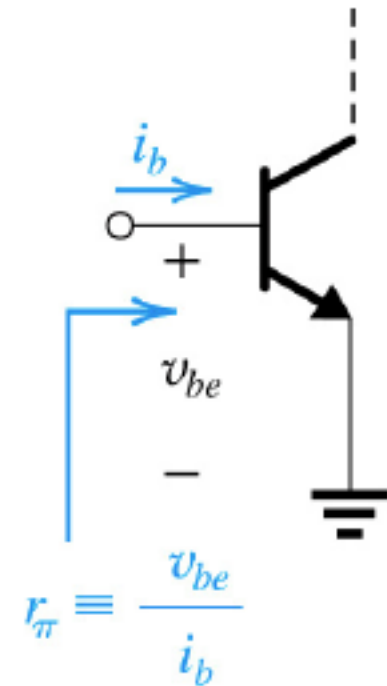
$$r_\pi = \frac{\beta}{g_m} = \frac{\beta}{I_C} V_{th} = \frac{V_{th}}{I_B}$$



# Small-signal input resistance at the Emitter

*Circuit for small-signal analysis*

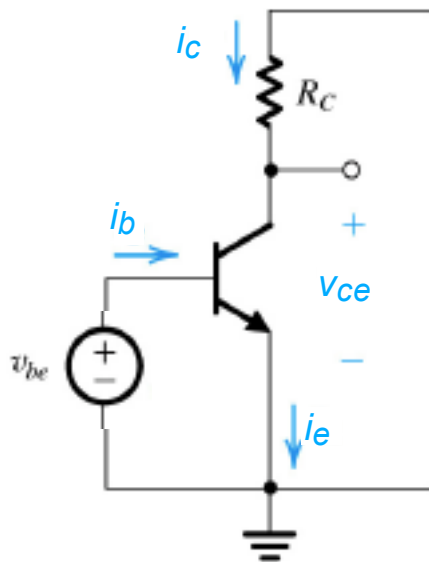

*Relation between  $r_\pi$  and  $r_e$*


$$i_E = \frac{i_c}{\alpha} = \frac{I_C}{\alpha} + \frac{i_c}{\alpha} = I_E + i_e$$

$$i_e = \frac{i_c}{\alpha} = \frac{g_m v_{be}}{\alpha} = \frac{I_C}{\alpha V_{th}} v_{be} = \frac{I_E}{V_{th}} v_{be}$$

*$r_e$  - small-signal input resistance between Base and Emitter, looking into the Emitter.*

$$r_e \equiv \frac{v_{be}}{i_e} = \frac{V_{th}}{I_E}$$
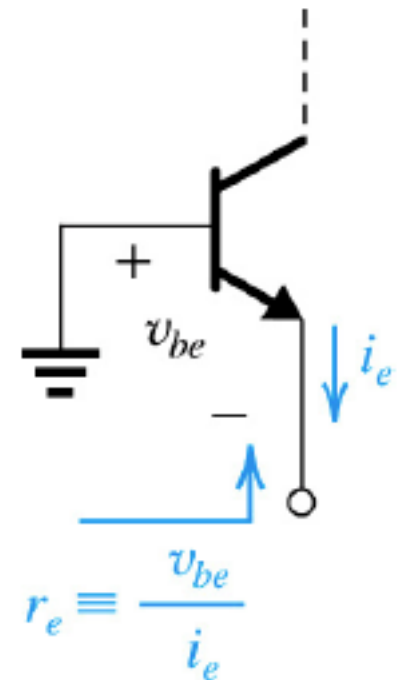
$$r_e = \frac{V_{th}}{I_E} = \frac{V_{th} \alpha}{I_C} = \frac{\alpha}{g_m} \approx \frac{1}{g_m}$$




$$v_{be} = i_b r_\pi = i_e r_e$$

$$r_\pi = \frac{i_e}{i_b} r_e = \frac{i_c + i_b}{i_b} r_e = \frac{(\beta + 1) i_b}{i_b} r_e = (\beta + 1) r_e$$

# Small-signals in the BJT amplifier

*Circuit for small-signal analysis*

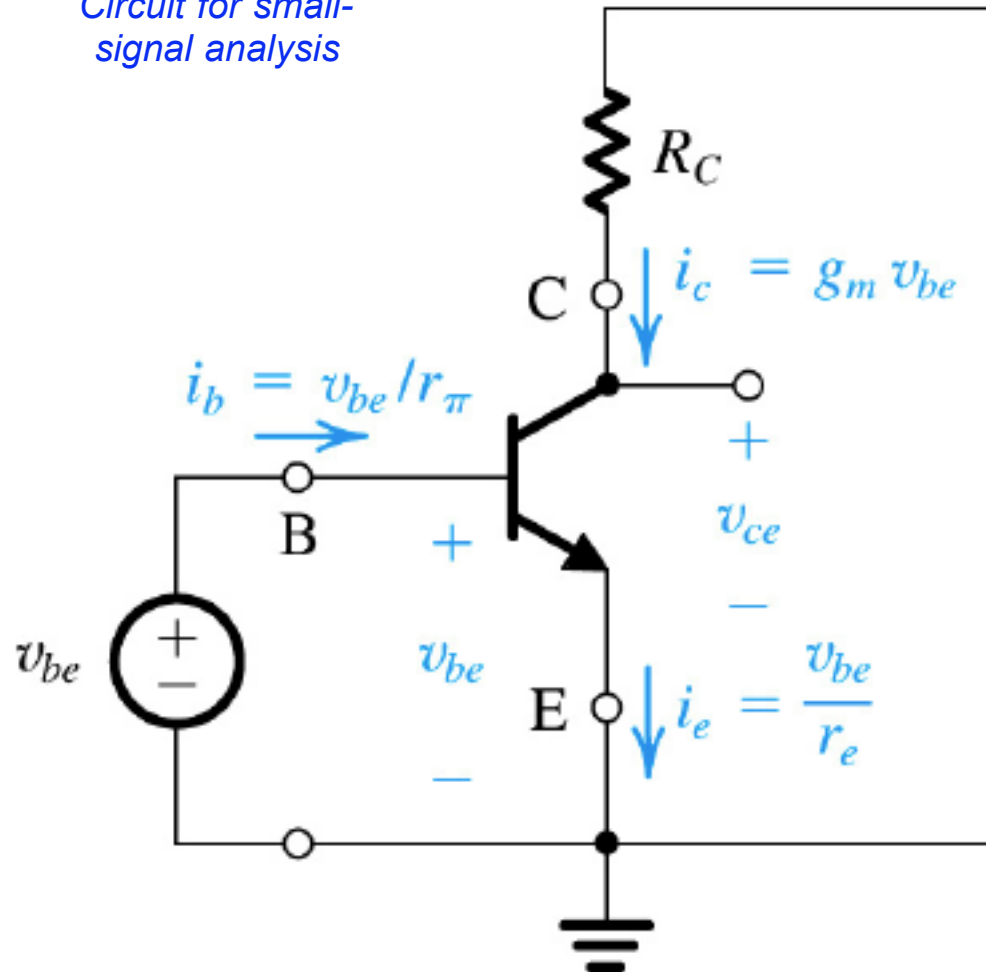


● In the circuit for small-signal analysis, all dc voltage sources must be replaced with short circuits, and all dc current sources must be replaced with open circuits

● In the small-signal analysis, the bipolar transistor must be replaced with its small-signal model
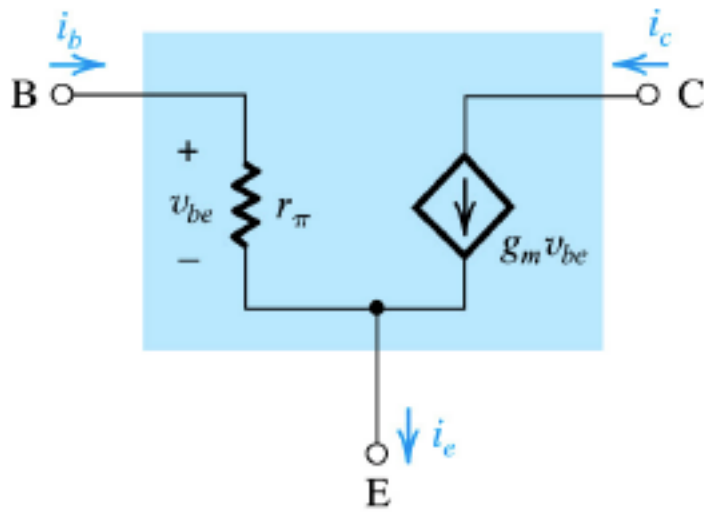
# Small-signal hybrid- $\pi$ model of the BJT


*Voltage-Controlled Current Source  
BJT representation*



$$g_m = \frac{I_C}{V_{th}}$$

$$r_\pi = \frac{\beta}{g_m}$$

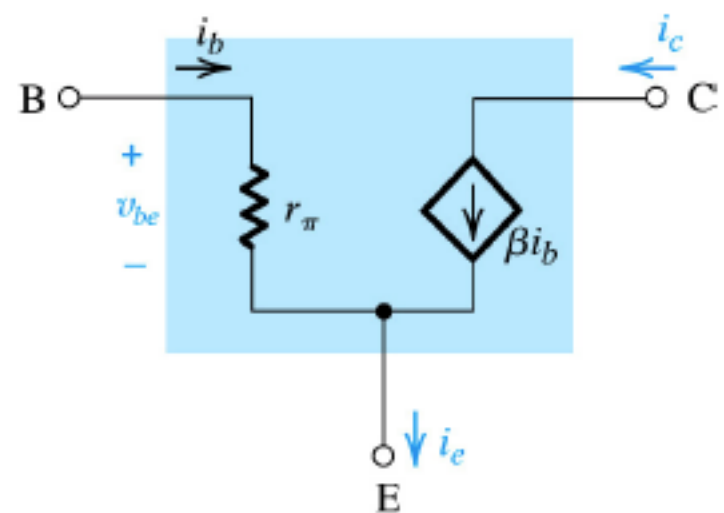*Current-Controlled Current Source  
BJT representation*




$$g_m v_{be} = g_m (i_b r_\pi) = (g_m r_\pi) i_b = \beta i_b$$

$$i_e = i_b + i_c = \frac{v_{be}}{r_\pi} + g_m v_{be} = \frac{v_{be}}{r_\pi} (1 + g_m r_\pi) = \frac{v_{be}}{r_\pi} (1 + \beta) = \frac{v_{be}}{\frac{r_\pi}{(1 + \beta)}} = \frac{v_{be}}{r_e}$$



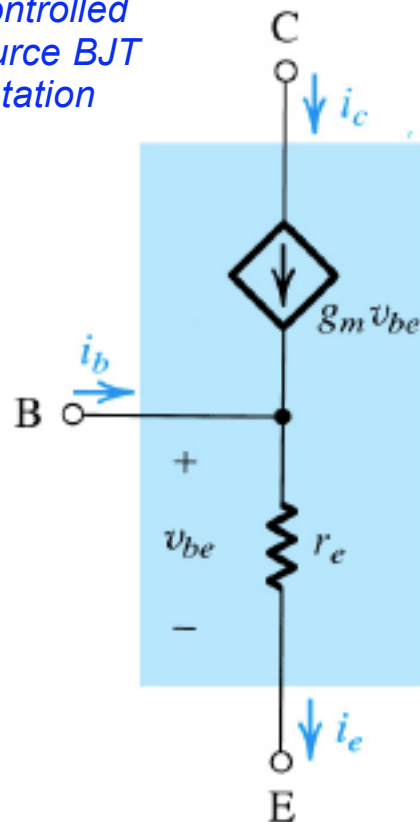
# Small-signal T model of the BJT

Voltage-Controlled  
Current Source BJT  
representation



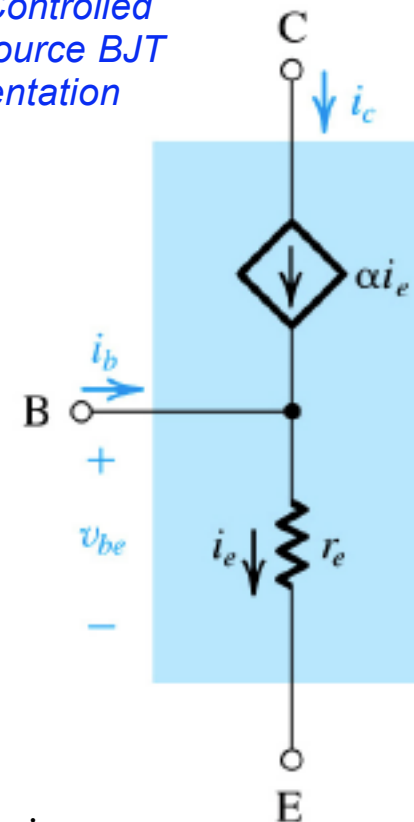Current-Controlled  
Current Source BJT  
representation



$$g_m = \frac{I_C}{V_{th}}$$

$$r_e = \frac{V_{th}}{I_E} = \frac{\alpha}{g_m}$$

$$g_m v_{be} = g_m (i_e r_e) = (g_m r_e) i_e = \alpha i_e$$

$$i_b = i_e - i_c = \frac{v_{be}}{r_e} - g_m v_{be} = \frac{v_{be}}{r_e} (1 - g_m r_e) = \frac{v_{be}}{r_e} (1 - \alpha) = \frac{v_{be}}{r_e} \left( 1 - \frac{\beta}{\beta + 1} \right) = \frac{v_{be}}{r_e} \left( \frac{\beta + 1 - \beta}{\beta + 1} \right) = \frac{v_{be}}{(1 + \beta) r_e} = \frac{v_{be}}{r_\pi}$$

# Small-signal analysis procedure


1. Eliminate the signal sources and determine the dc operating point of the BJT (  $I_C$  )
2. Eliminate the dc sources by replacing each dc voltage source with a short circuit and each dc current source with an open circuit
3. Replace the BJT with one of its small-signal models
4. Calculate the values of small-signal model parameters

$$g_m = \frac{I_C}{V_{th}} \quad r_\pi = \frac{\beta}{g_m} \quad r_e = \frac{V_{th}}{I_E} = \frac{\alpha}{g_m}$$

5. Analyze the resulting small-signal circuit to determine the required quantities (voltage gain, input and output resistances, etc.)
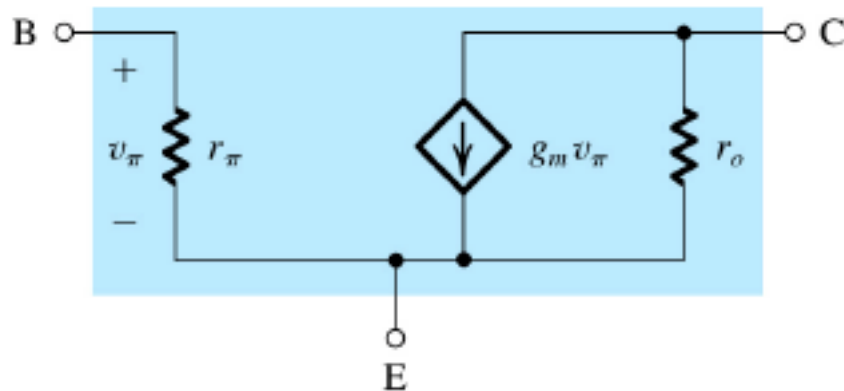
# Small-signal hybrid- $\pi$ model of the BJT including the output resistance

*Voltage-Controlled Current Source  
BJT representation*




$$g_m = \frac{I_C}{V_{th}}$$

$$r_\pi = \frac{\beta}{g_m}$$


$$r_o = \frac{V_A}{I_C}$$

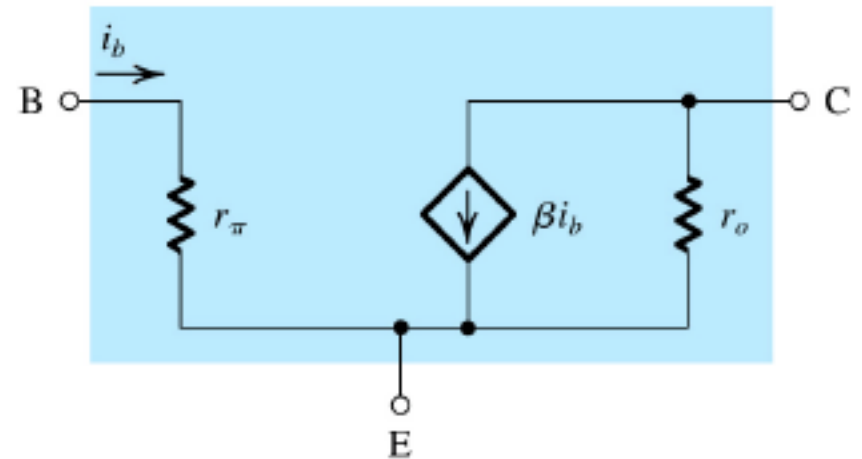*Current-Controlled Current Source  
BJT representation*


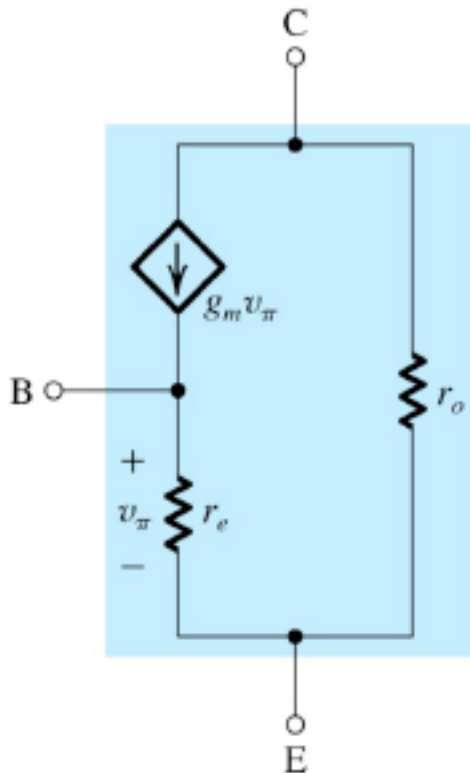
# Small-signal T model of the BJT including the output resistance

*Voltage-Controlled Current Source  
BJT representation*



$$r_o = \frac{V_A}{I_C}$$

$$g_m = \frac{I_C}{V_{th}}$$

$$r_e = \frac{V_{th}}{I_E} = \frac{\alpha}{g_m}$$

*Current-Controlled Current Source  
BJT representation*

