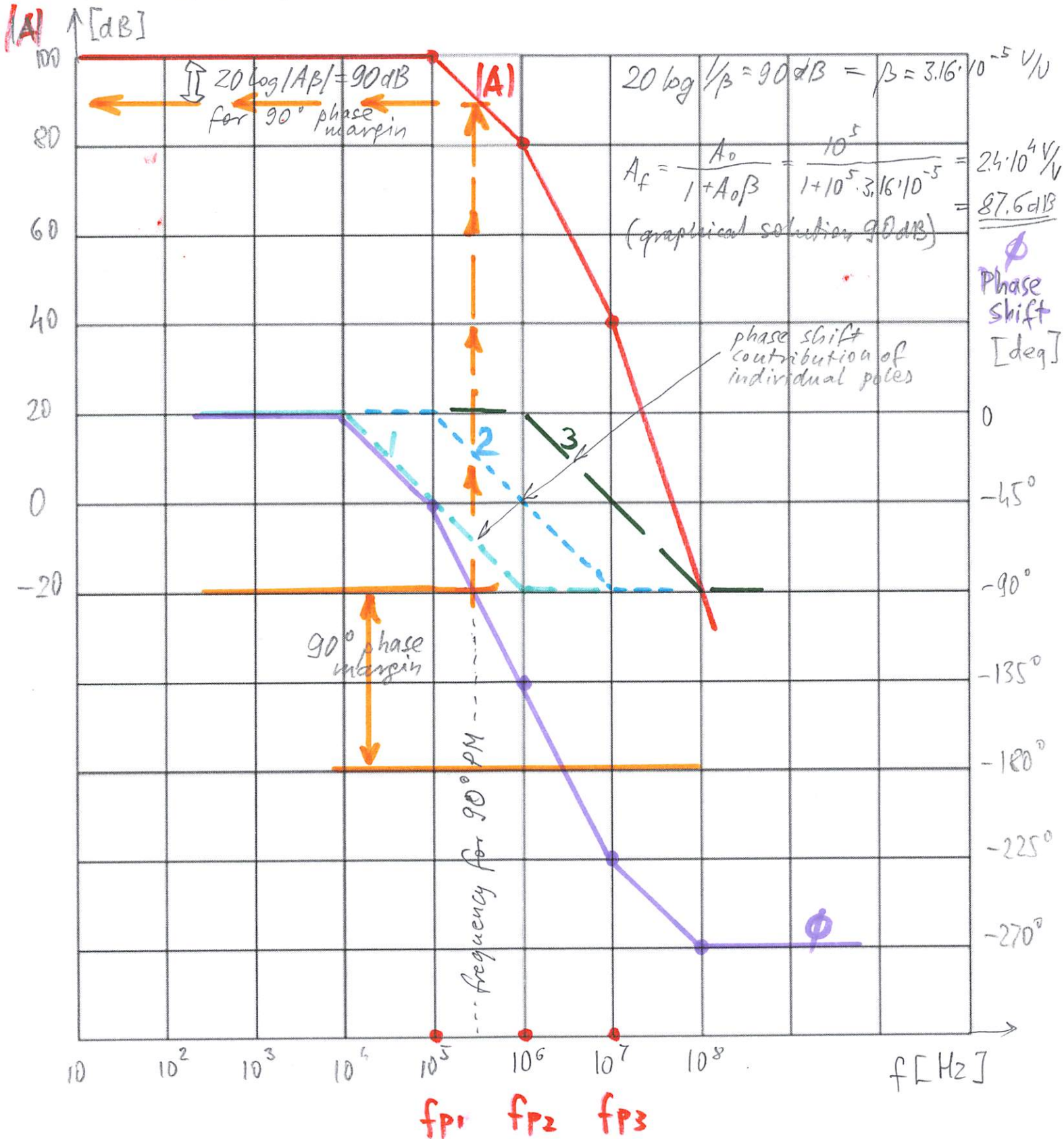



Problem 1

For the three-pole amplifier for which $A_0 = 10^5$ V/V and having poles at 10^5 Hz, 10^6 Hz and 10^7 Hz, and with frequency-independent feedback, what is the minimum closed-loop voltage gain that can be obtained for phase margins of 90° and 45° ?



Problem 1

For the three-pole amplifier for which $A_0 = 10^5$ V/V and having poles at 10^5 Hz, 10^6 Hz and 10^7 Hz, and with frequency-independent feedback, what is the minimum closed-loop voltage gain that can be obtained for phase margins of 90° and 45° ?

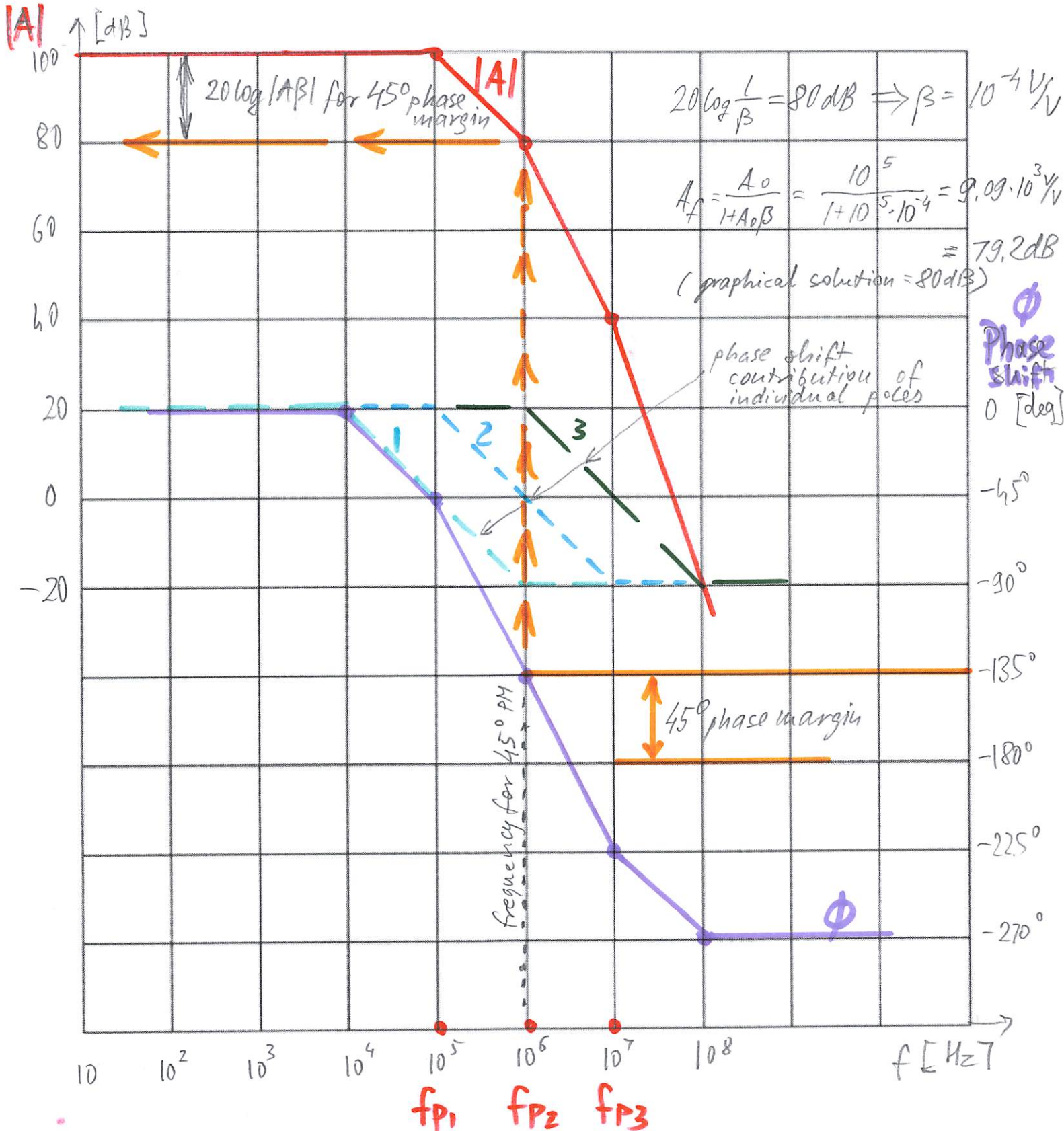

Problem 2

Consider a feedback amplifier for which the open-loop gain $A(s)$ is given by:

$$A(s) = \frac{10,000}{(1 + s/10^4)(1 + s/10^5)^2}$$

If the feedback factor β is independent of frequency, find the frequency at which the phase shift is 180° , and find the critical value of β at which oscillation will commence.

Solve the problem using formulas, as well as graphically. Compare both results.

$$A(j\omega) = \frac{10^4}{(1 + j\frac{\omega}{10^4})(1 + j\frac{\omega}{10^5})^2}$$

$$A_0 = 20 \log(10^4) = 80 \text{ dB}$$

$$\text{phase shift: } \phi = -\tan^{-1}\left(\frac{\omega}{10^4}\right) - 2 \cdot \tan^{-1}\left(\frac{\omega}{10^5}\right)$$

$$180^\circ = -\tan^{-1}\left(\frac{\omega_{180}}{10^4}\right) - 2 \tan^{-1}\left(\frac{\omega_{180}}{10^5}\right)$$

$$\textcircled{1} \text{ iteration: assume } \omega_{180} = 10^5$$

$$-\tan^{-1}\left(\frac{10^5}{10^4}\right) - 2 \tan^{-1}\left(\frac{10^5}{10^5}\right) = -84.3^\circ - 2 \cdot 45^\circ = -174.3^\circ$$

$$\textcircled{2} \text{ iteration: assume } \omega_{180} = 1.1 \cdot 10^5$$

$$-\tan^{-1}\left(\frac{1.1 \cdot 10^5}{10^4}\right) - 2 \tan^{-1}\left(\frac{1.1 \cdot 10^5}{10^5}\right) = -84.8^\circ - 2 \cdot 47.7^\circ = -180.2^\circ$$

$$\text{solution: } \omega_{180} = 1.095 \cdot 10^5 \text{ rad/sec}$$

$$\text{Gain at the } \omega_{180} \text{ frequency: } |A| = \frac{10^4}{\sqrt{1 + \left(\frac{1.095 \cdot 10^5}{10^4}\right)^2} \cdot \left\{ \sqrt{1 + \left(\frac{1.095 \cdot 10^5}{10^5}\right)^2} \right\}^2} = 413.6 \frac{V}{V}$$

$$20 \log 413.6 = 52.3 \text{ dB}$$

For stable operation:

$$|A| \cdot \beta_{cr} < 1$$

$$413.6 \cdot \beta_{cr} < 1$$

$$\beta_{cr} < 2.418 \cdot 10^{-3}$$


The oscillation will commence for $\beta \geq 2.42 \cdot 10^{-3}$

Problem 2

Consider a feedback amplifier for which the open-loop gain $A(s)$ is given by:


$$A(s) = \frac{10,000}{(1 + s/10^4)(1 + s/10^5)^2}$$

If the feedback factor β is independent of frequency, find the frequency at which the phase shift is 180° , and find the critical value of β at which oscillation will commence. Solve the problem using formulas, as well as graphically. Compare both results.

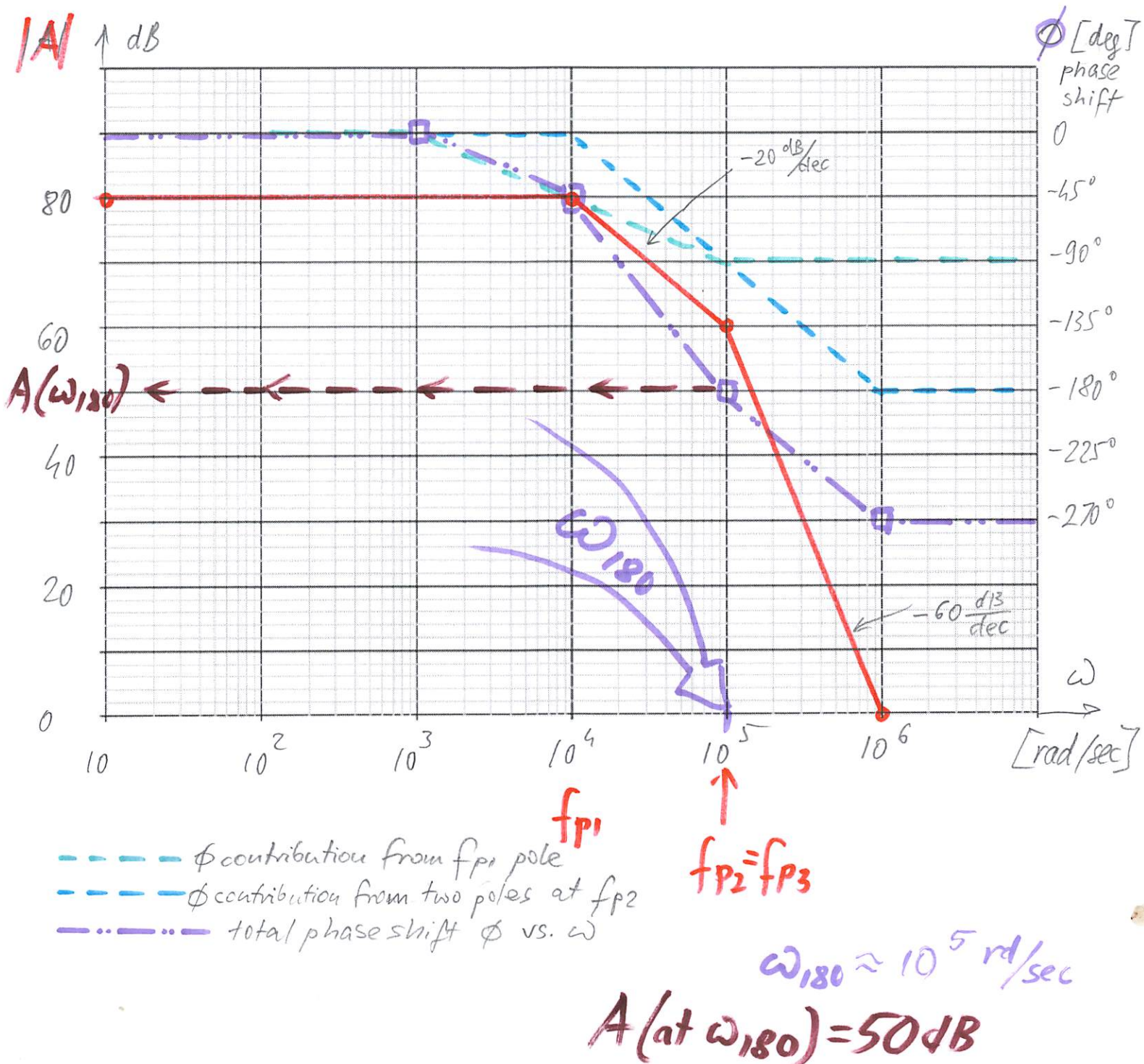

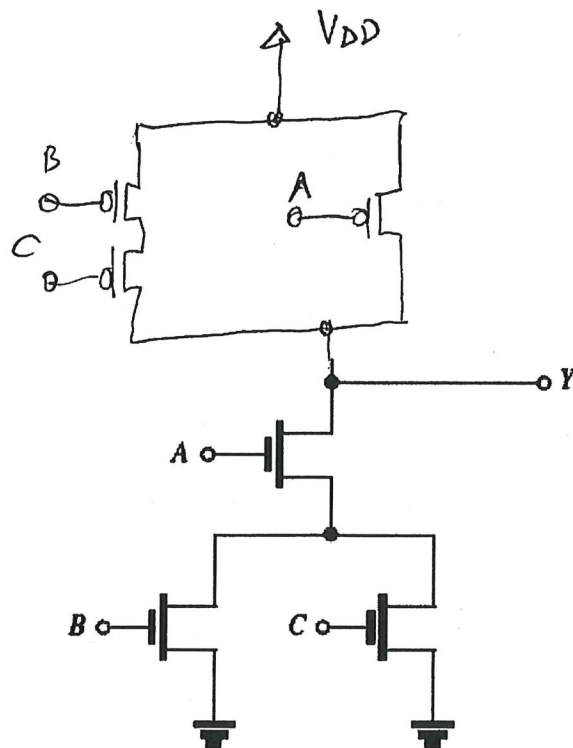Problem 3

Find the pull-up network (PUN) that correspond to the pull-down network (PDN) shown below, and hence draw the complete CMOS logic circuit. What is the Boolean function realized by this gate?




$$Y = \overline{A \cdot (B + C)}$$

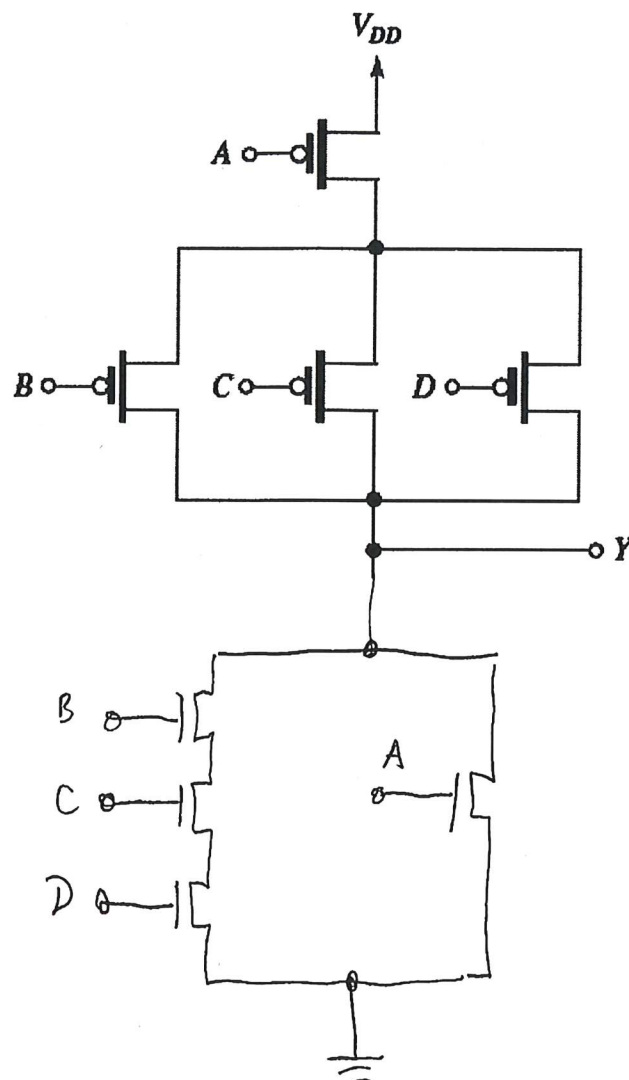Problem 4

Find the pull-down network (PDN) that correspond to the pull-up network (PUN) shown below, and hence draw the complete CMOS logic circuit.

What is the Boolean function realized by this gate?



$$Y = \overline{A + B \cdot C \cdot D}$$