

Electricity & Magnetism

Lecture 8: Capacitors

Today's Concept:

Capacitors

(Capacitors in a circuits, Dielectrics, Energy in capacitors)

Alternate terms: “condensors”, “capacitators”,

Stuff you asked about:

- “the formula for calculating capacitance in parallel and series are the opposite of the formula for resistance “
- “Please go over the Capacitors with and without a dielectric from checkpoint.”
- “this stuff is a lot harder than what we’ve been doing before, one thing i don’t understand is when you disconnect a battery from a capacitor what exactly happens, how come it still has a charge?? ”

Capacitors, connected and unconnected


- ★ A capacitor that is **un**connected to a battery has constant charge: $V = Q/C$ (V is determined by Q)
- ★ Capacitors in parallel have the same voltage. Charge may redistribute among them: $Q_1/C_1 = Q_2/C_2 = Q_2/C_2 \dots$
- ★ A capacitor connected to a battery has a constant voltage. $Q = CV$ (Q is determined by V)

Dielectric

- ★ Charged capacitor, not connected to battery
- ★ Dielectric makes ΔV smaller

air capacitor


$$\kappa = 1$$

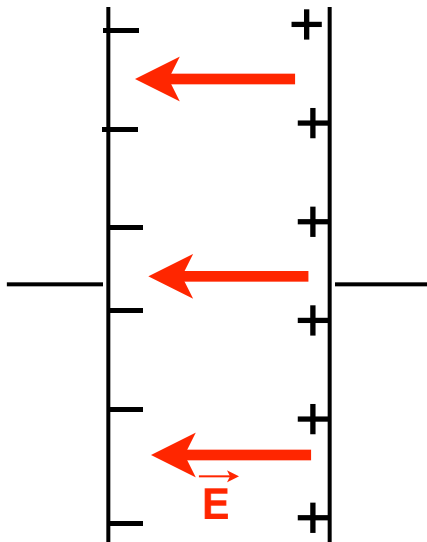

$$C = \epsilon_0 A/L$$

dielectric capacitor


$$\kappa > 1$$

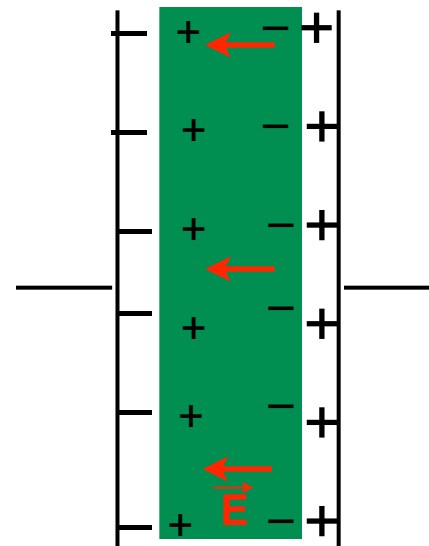

$$C = \kappa \epsilon_0 A/L$$


E inside dielectric is smaller than E outside.
The charge on the surface of the dielectric partially cancels the E field from the charge on the plates.
Therefore the ΔV between the plates is less.

Simple Capacitor Circuit

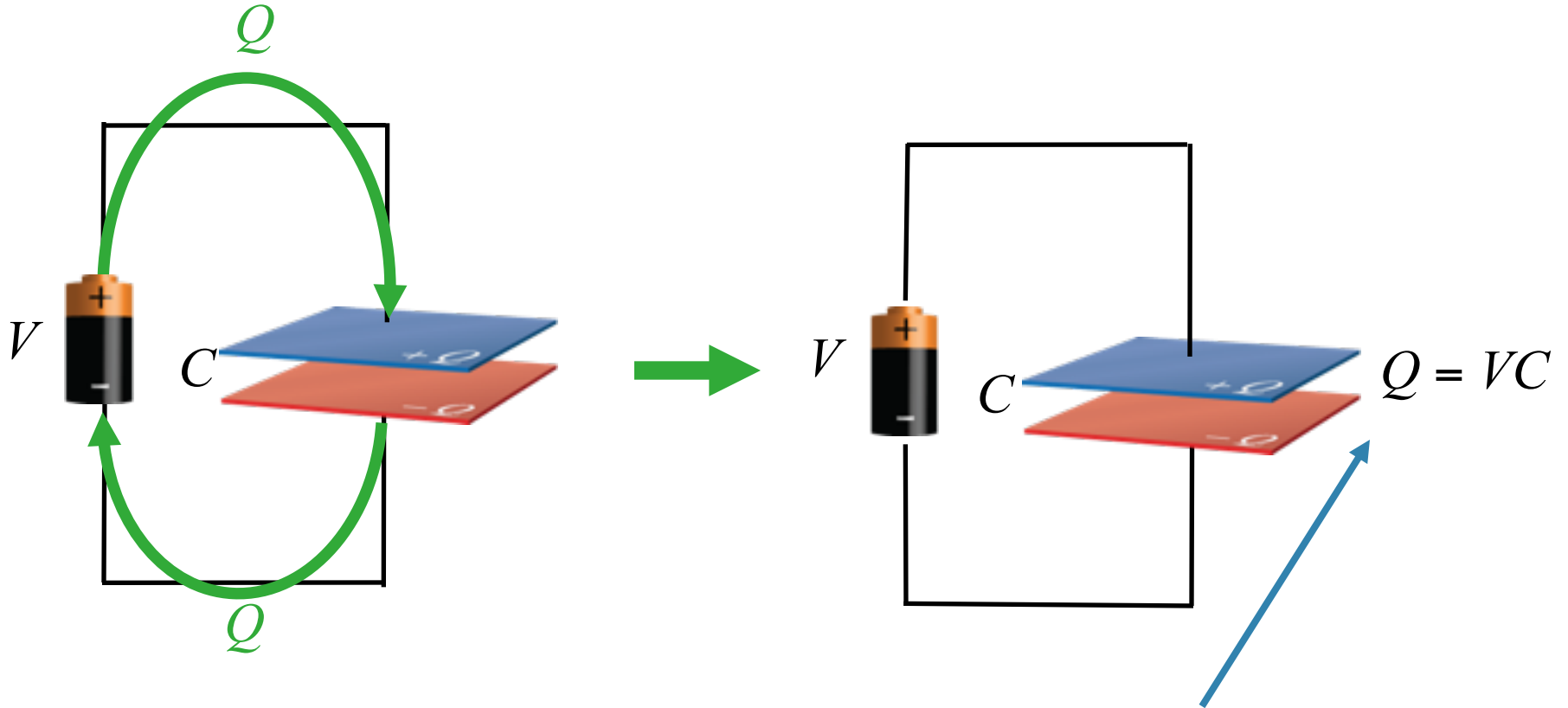


This “ Q ” really means that the battery has moved charge Q from one plate to the other, so that one plate holds $+Q$ and the other $-Q$.

Dielectrics

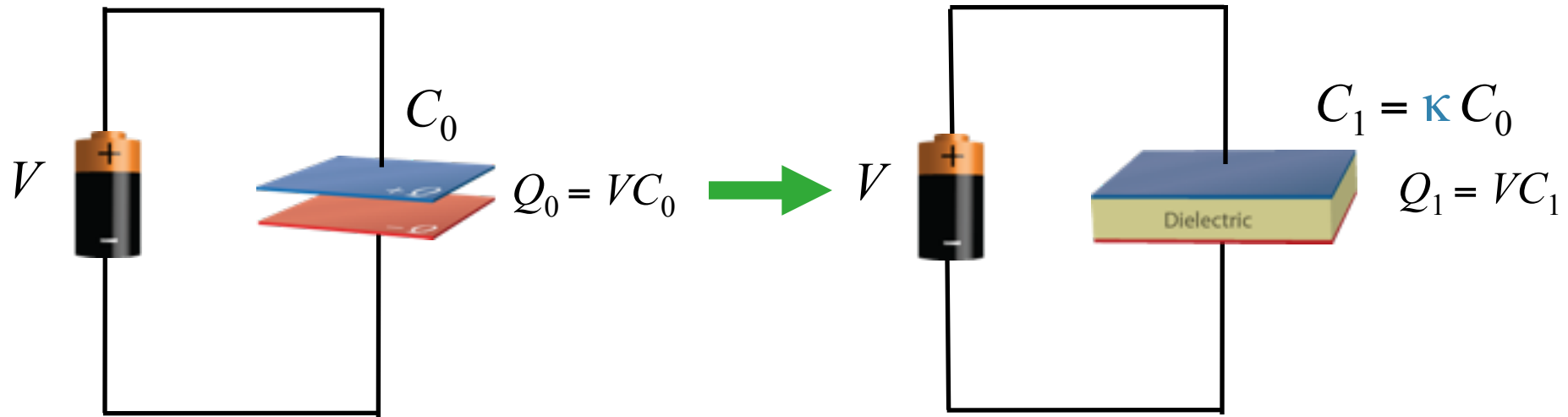

By adding a dielectric you are just making a new capacitor with larger capacitance (factor of κ)

Parallel Capacitor Circuit

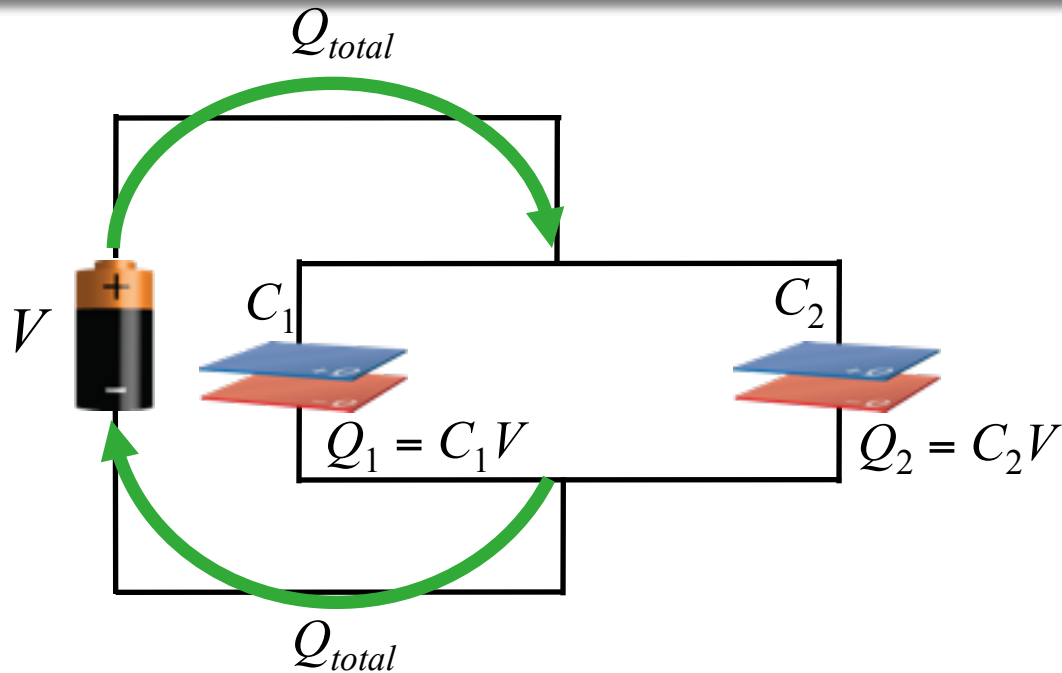


Key point: V is the same for both capacitors

Key Point: $Q_{total} = Q_1 + Q_2 = VC_1 + VC_2 = V(C_1 + C_2)$

$$C_{total} = C_1 + C_2$$

Series Capacitor Circuit

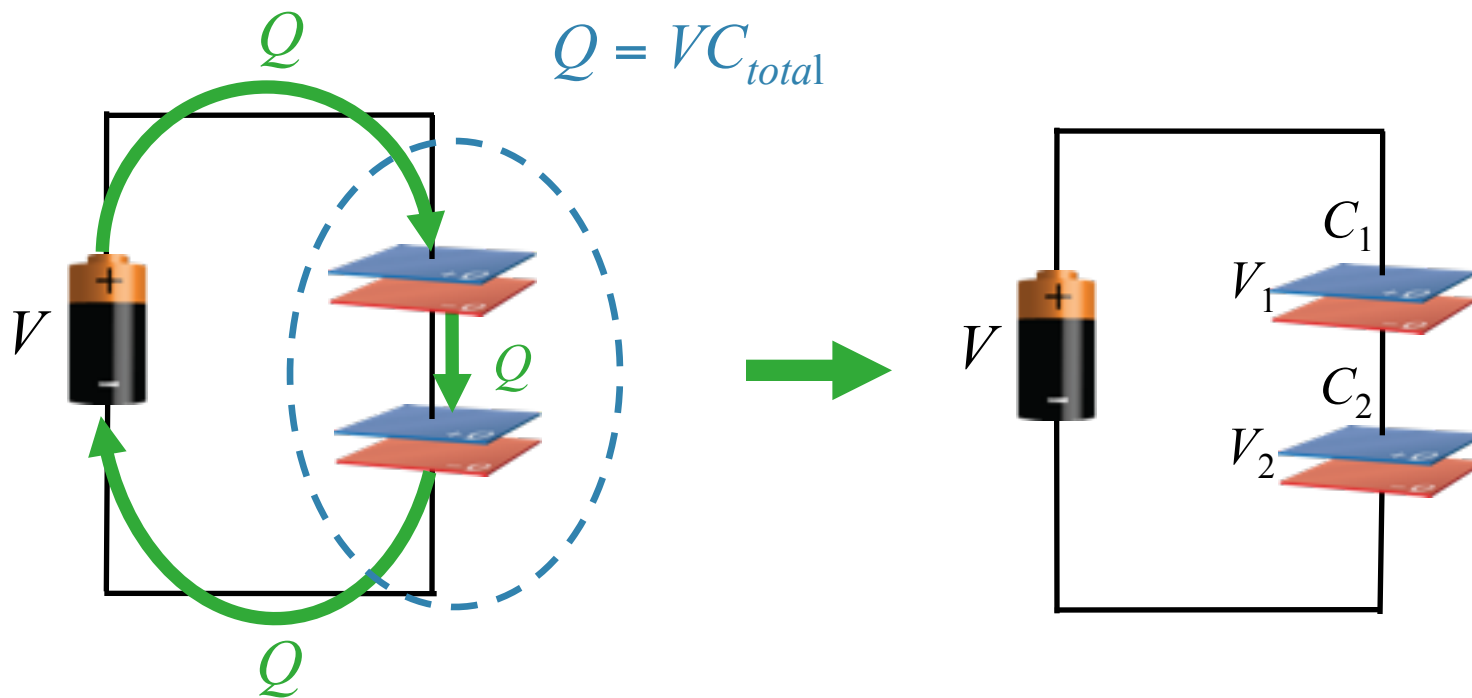

Key point: Q is the same for both capacitors


Key point: $Q = VC_{total} = V_1C_1 = V_2C_2$

Also: $V = V_1 + V_2$ \longrightarrow $Q/C_{total} = Q/C_1 + Q/C_2$


$$\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2}$$

CheckPoint: Three Capacitor Configurations

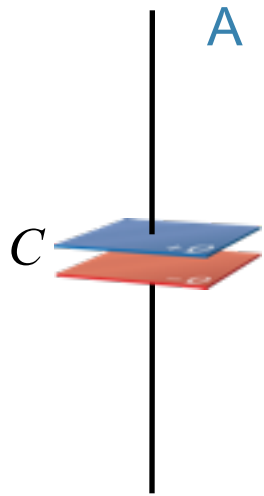The three configurations shown below are constructed using identical capacitors. Which of these configurations has lowest total capacitance?




$$C_{total} = C$$

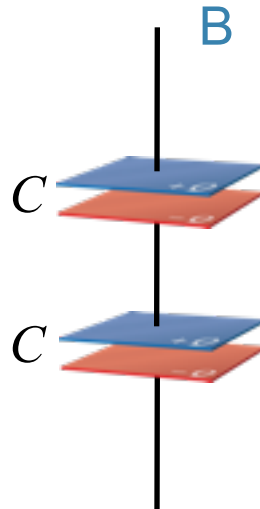

$$\begin{aligned} 1/C_{total} &= 1/C + 1/C \\ &= 2/C \end{aligned}$$


$$C_{total} = C/2$$

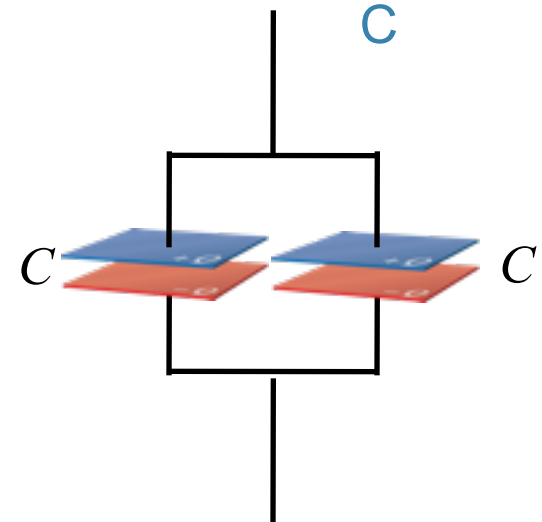

$$C_{total} = 2C$$


D: All 3 are the same

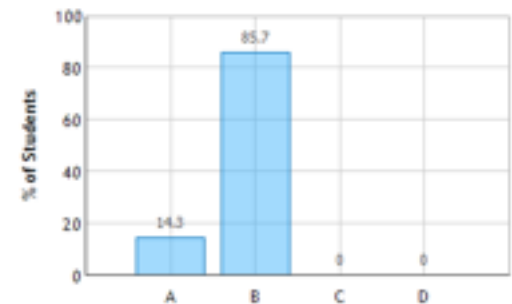Three Capacitor Configurations: Question 1 (N = 7)




CheckPoint: Two Capacitor Configurations

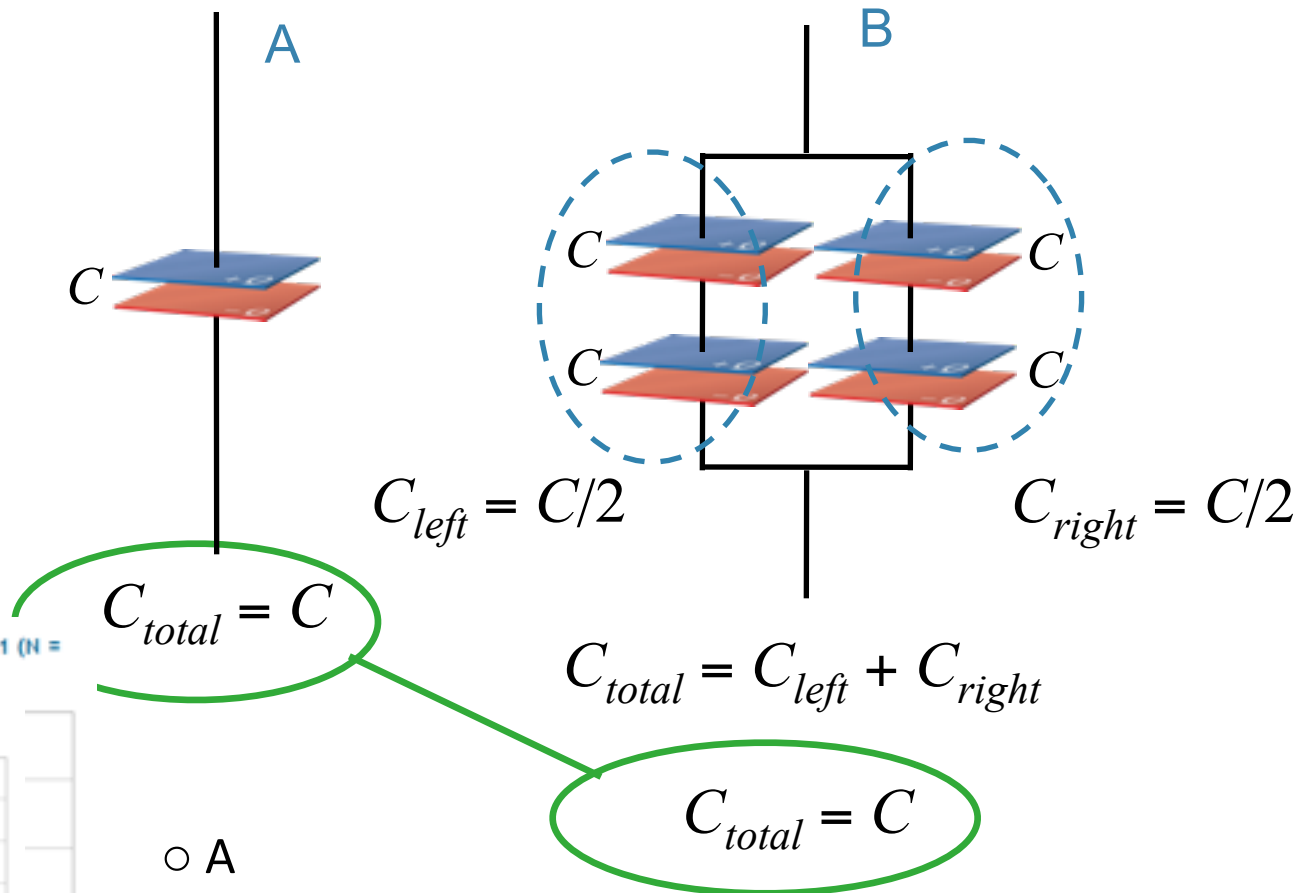The two configurations shown below are constructed using identical capacitors. Which of these configurations has the lowest overall capacitance?



Two Capacitor Configurations: Question 1 (N = 20)

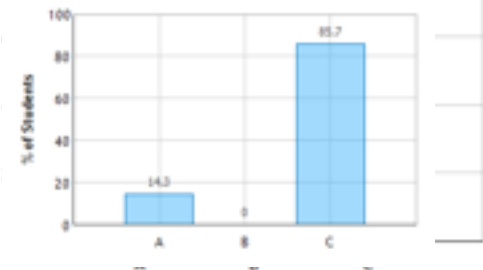Two Capacitor Configurations: Question 1 (N = 7)




A

B

Both configurations have the same capacitance

Clicker Question: Capacitor Network

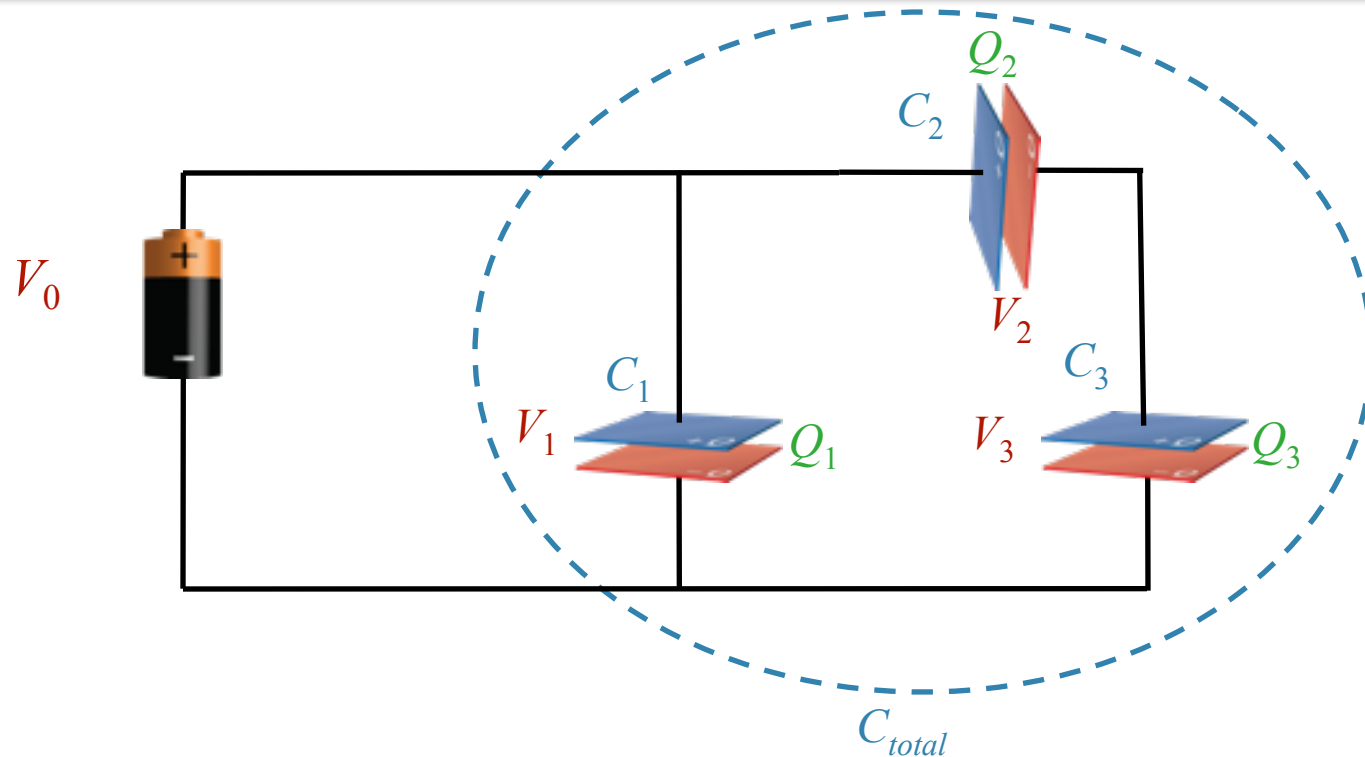

Which of the following is **NOT** necessarily true:

- A) $V_0 = V_1$
- B) $C_{total} > C_1$
- C) $V_2 = V_3$**
- D) $Q_2 = Q_3$
- E) $V_1 = V_2 + V_3$

CheckPoint: Capacitor Network

A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitance of C_2 is twice that of C_1 . The capacitance of C_3 is three times that of C_1 . The capacitors obtain charges Q_1 , Q_2 , and Q_3 .

Compare Q_1 , Q_2 , and Q_3 .


A. $Q_1 > Q_3 > Q_2$

B. $Q_1 > Q_2 > Q_3$


C. $Q_1 > Q_2 = Q_3$

D. $Q_1 = Q_2 = Q_3$

E. $Q_1 < Q_2 = Q_3$

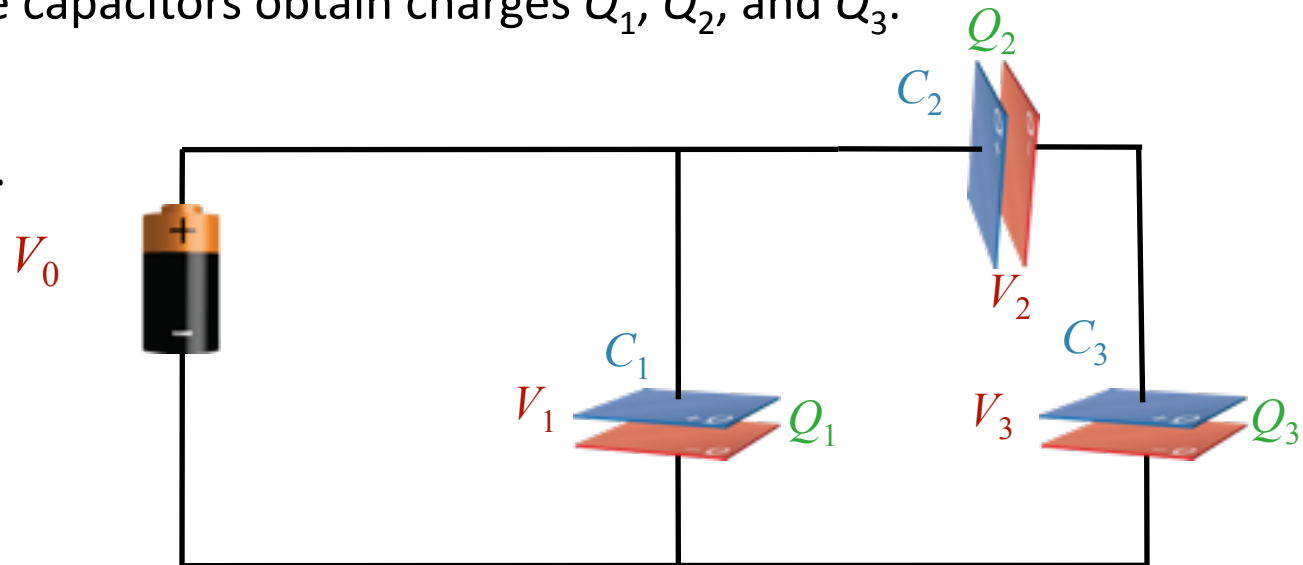


Capacitor Network: Question 1 (N = 7)

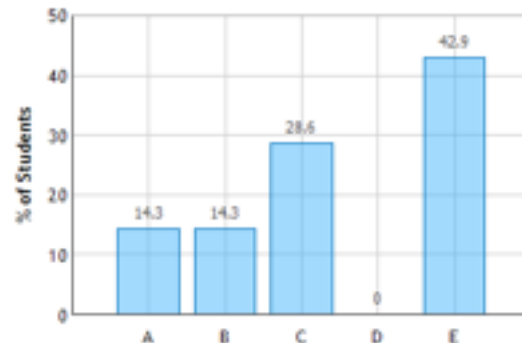

Energy in a Capacitor


In Prelecture 7 we calculated the work done to move charge Q from one plate to another:

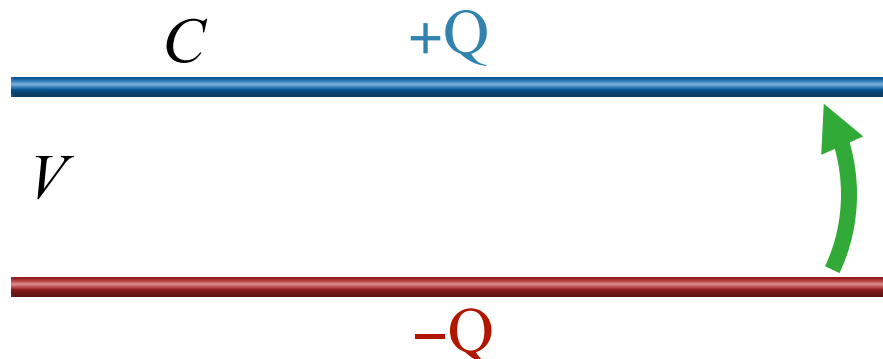
$$\begin{aligned}U &= \frac{1}{2}QV \\ &= \frac{1}{2}CV^2 \\ &= \frac{1}{2}Q^2/C\end{aligned}\quad \left. \vphantom{\begin{aligned}U &= \frac{1}{2}QV \\ &= \frac{1}{2}CV^2 \\ &= \frac{1}{2}Q^2/C\end{aligned}} \right\} \text{Since } Q = VC$$

This is potential energy waiting to be used...

Messing with Capacitors

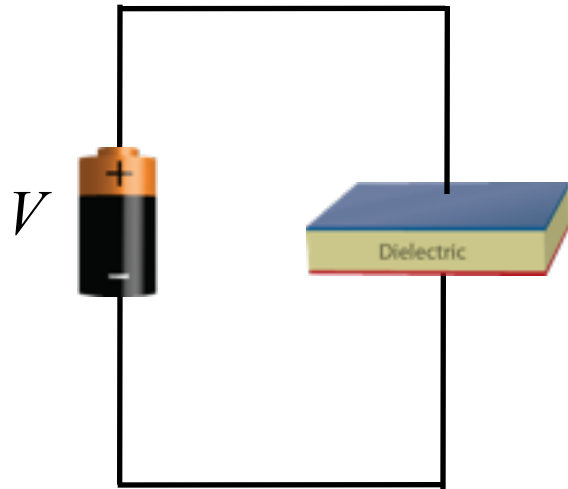If connected to a battery V stays constant




$$V_1 = V$$

$$C_1 = \kappa C$$

$$\left. \begin{array}{l} V_1 = V \\ C_1 = \kappa C \end{array} \right\} \rightarrow Q_1 = C_1 V_1$$

$$= \kappa C V = \kappa Q$$

If isolated then total Q stays constant

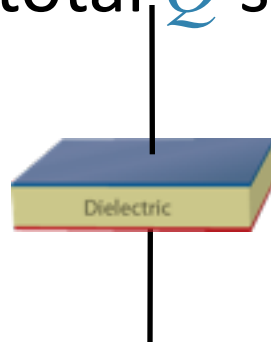

$$Q_1 = Q$$


$$C_1 = \kappa C$$

$$\left. \begin{array}{l} Q_1 = Q \\ C_1 = \kappa C \end{array} \right\} \rightarrow V_1 = Q_1 / C_1$$

$$= Q / \kappa C = V / \kappa$$

CheckPoint: Capacitors and Dielectrics 1

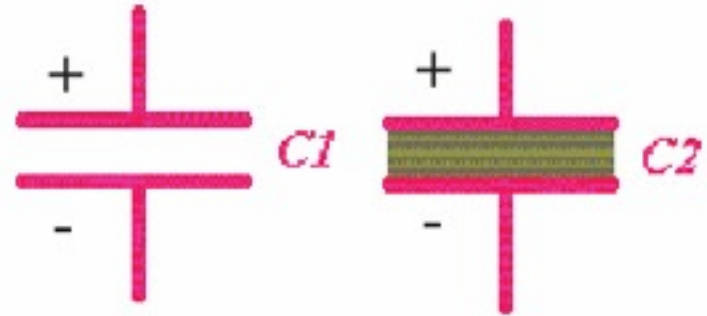Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric.



Compare the voltages of the two capacitors.

A. $V_1 > V_2$

B. $V_1 = V_2$

C. $V_1 < V_2$


“The electric field decreases on the second due to the dielectric, so its voltage must decrease.”

“The little brown thing is stopping the pikachus from reaching the other side.”

“ Dielectrics don't change voltages. ”

“Capacitance lowers in case 2, meaning V increases in case 2. ’


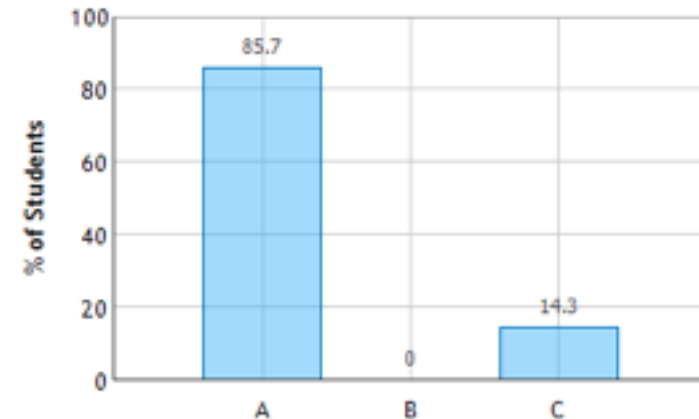
Capacitors with and without a Dielectric:
Question 1 (N = 7)



Clicker Question: Messing with Capacitors



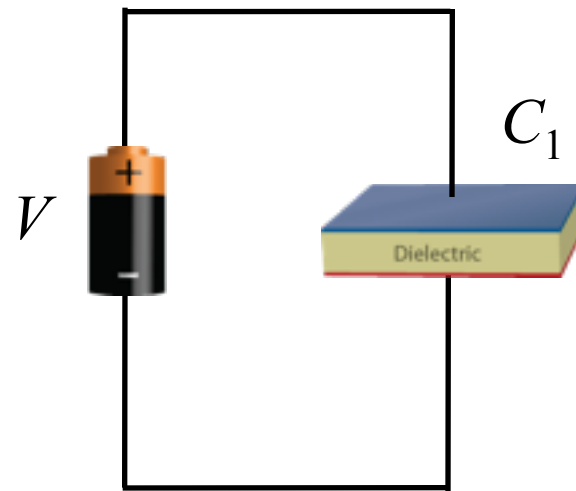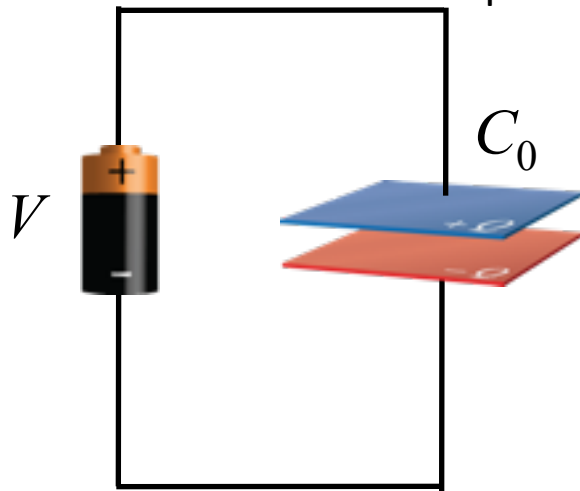Two identical parallel plate capacitors are connected to identical batteries. Then a dielectric is inserted between the plates of capacitor C_1 . Compare the energy stored in the two capacitors.



A) $U_1 < U_0$

B) $U_0 = U_1$

C) $U_1 > U_0$

Compare using $U = \frac{1}{2}CV^2$


$$U_1/U_0 = \kappa$$

→ Potential Energy goes UP

Checkpoint: Capacitors and Dielectrics 2

Two identical parallel plate capacitors are given the same charge Q , after which they are disconnected from the battery. After C_2 has been charged and disconnected, it is filled with a dielectric.

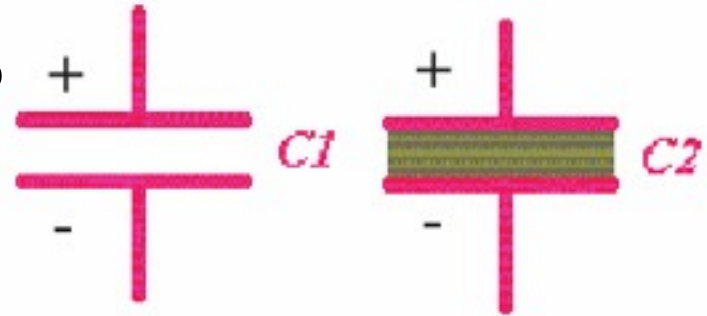Compare the potential energy stored by the two capacitors.



A. $U_1 > U_2$

B. $U_1 = U_2$


C. $U_1 < U_2$

“If the electric field goes down, then so does the potential energy of the second system..”

“Dielectrics don't affect potential.”


“ $U = QV$. Since voltage remains constant and charge increases, potential energy must also increase.”

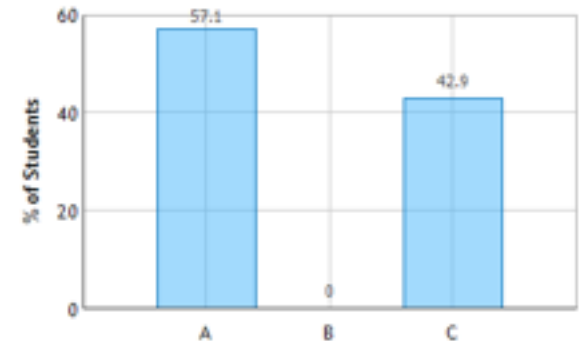Capacitors with and without a Dielectric:
Question 3 (N = 7)



CheckPoint: Capacitors and Dielectrics 3

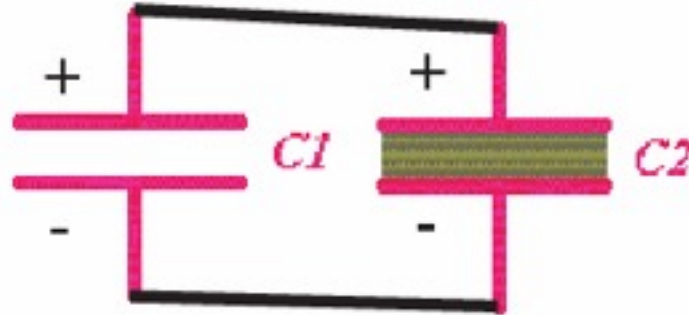The two capacitors are now connected to each other by wires as shown. How will the charge redistribute itself, if at all?




V must be the same !

- The charges will flow so that the charge on C1 will become equal to the charge on C2.
- The charges will flow so that the energy stored in C1 will become equal to the energy stored in C2
- The charges will flow so that the potential difference across C1 will become the same as the potential difference across C2.
- No charges will flow. The charge on the capacitors will remain what it was before they were connected


$$Q: \quad \frac{Q_1}{C_1} = \frac{Q_2}{C_2} \quad \longrightarrow \quad Q_1 = \frac{C_1}{C_2} Q_2$$

$$U: \quad \begin{aligned} U_1 &= \frac{1}{2} C_1 V^2 \\ U_2 &= \frac{1}{2} C_2 V^2 \end{aligned} \quad \longrightarrow \quad U_1 = \frac{C_1}{C_2} U_2$$

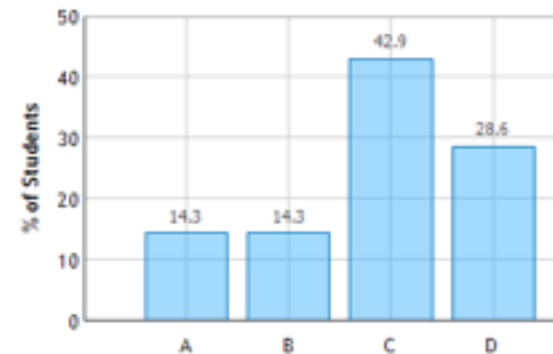Capacitors with and without a Dielectric:
Question 5 (N = 7)



Calculation

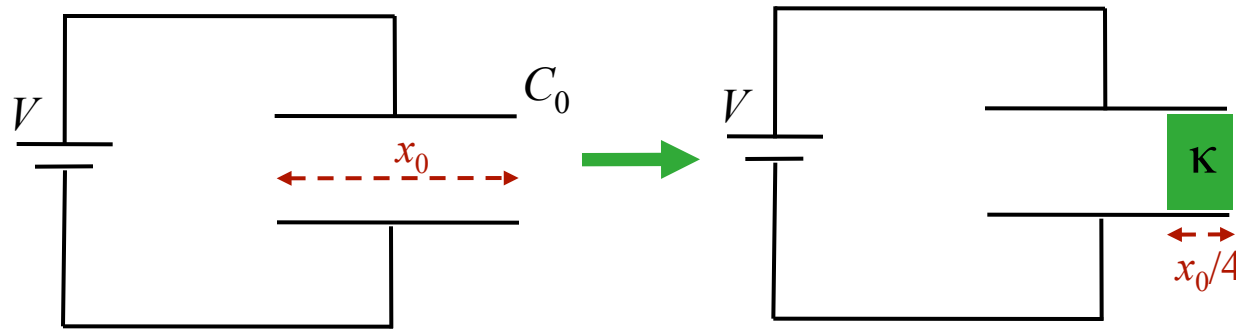

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Conceptual Analysis:

$$C \equiv \frac{Q}{V}$$

What changes when the dielectric added?

- A) Only C B) only Q C) only V **D) C and Q** E) V and Q

Adding dielectric changes the physical capacitor



C changes


V does not change and C changes



Q changes

What is Q_f , the final charge on the capacitor?

Calculation

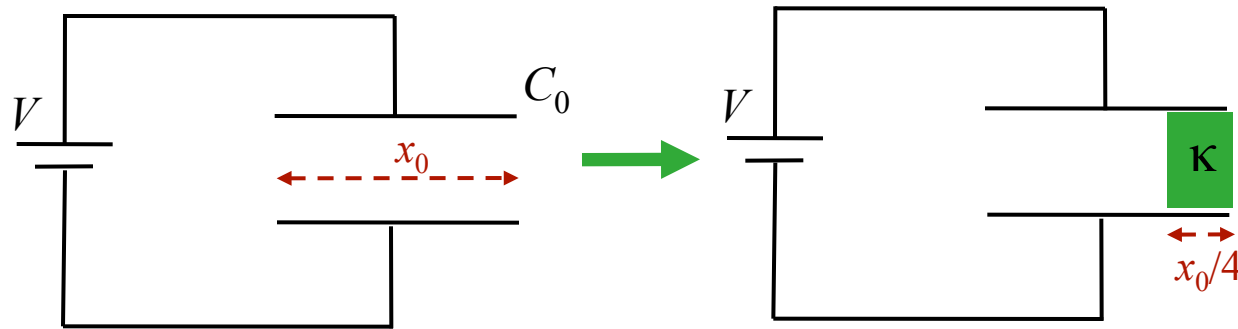

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

Strategic Analysis:

- Calculate new capacitance C
- Apply definition of capacitance to determine Q

To calculate C , let's first look at:



A) $V_{left} < V_{right}$


B) $V_{left} = V_{right}$

C) $V_{left} > V_{right}$

What is Q_f , the final charge on the capacitor?

The conducting plate is an equipotential !

Calculation

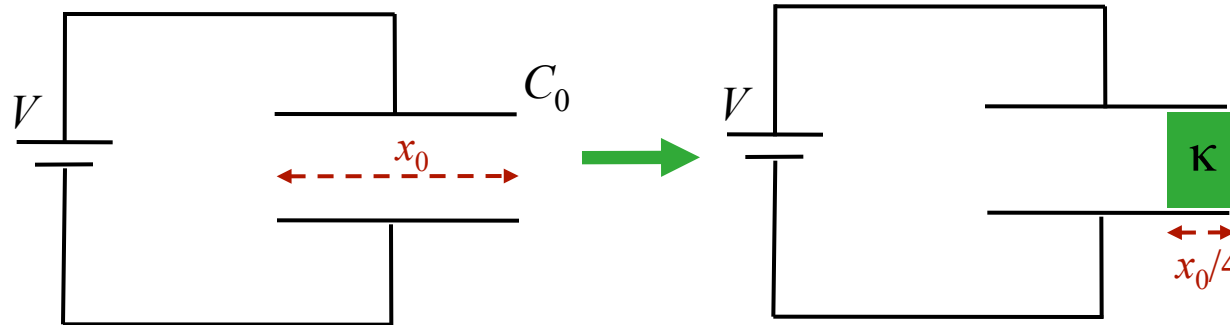


An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.

What is Q_f , the final charge on the capacitor?

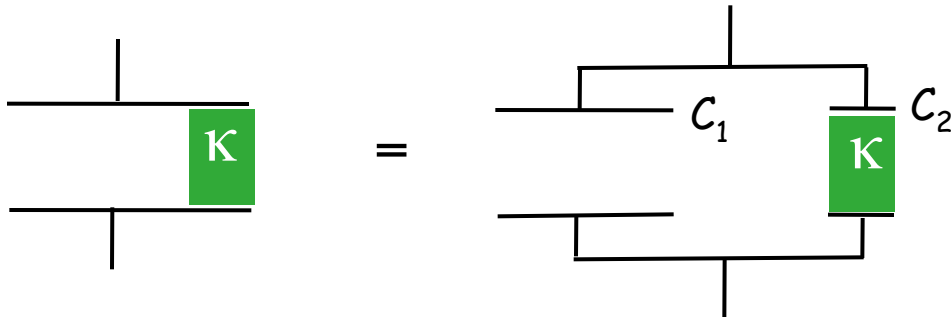Can consider capacitor to be two capacitances, C_1 and C_2 , in parallel




What is C_1 ?

- A) $C_1 = C_0$ **B) $C_1 = \frac{3}{4}C_0$** C) $C_1 = \frac{4}{3}C_0$ D) $C_1 = \frac{1}{4}C_0$

In general. For parallel plate capacitor: $C = \epsilon_0 A/d$


$$\begin{matrix} A = \frac{3}{4}A_0 \\ d = d_0 \end{matrix} \quad \square \quad \longrightarrow \quad C_1 = \frac{3}{4}(\epsilon_0 A_0/d_0) \quad \longrightarrow \quad \boxed{C_1 = \frac{3}{4}C_0}$$

Calculation

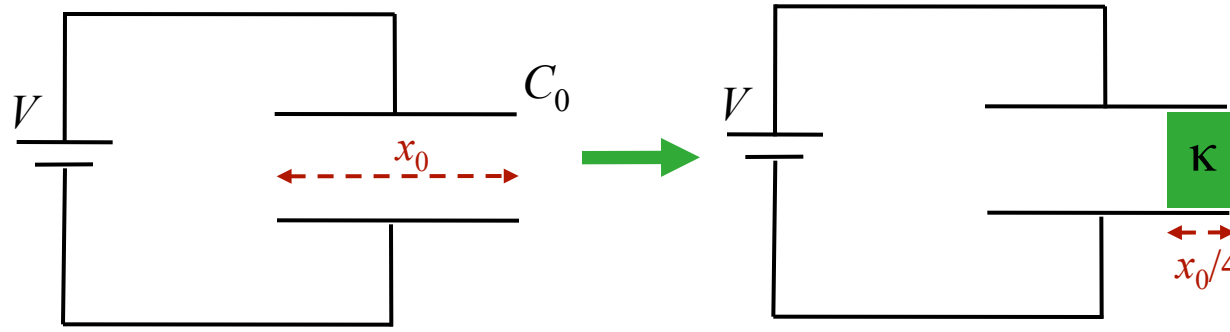

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

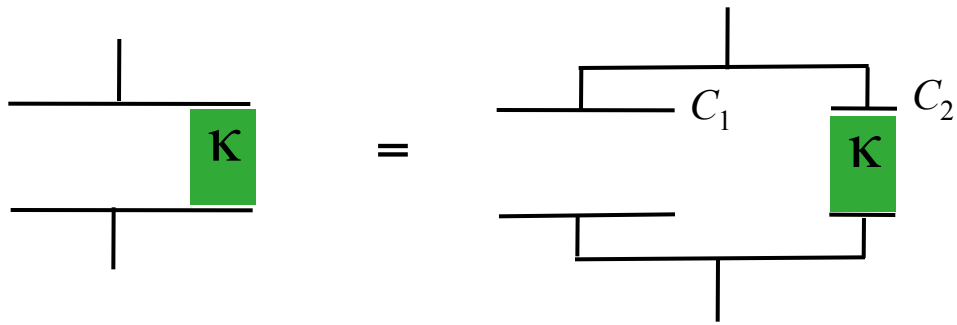A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.



What is Q_f , the final charge on the capacitor?
 $C_1 = \frac{3}{4}C_0$


What is C_2 ?

- A) $C_2 = \kappa C_0$ B) $C_2 = \frac{3}{4} \kappa C_0$ C) $C_2 = \frac{4}{3} \kappa C_0$ **D) $C_2 = \frac{1}{4} \kappa C_0$**

In general. For parallel plate capacitor filled with dielectric: $C = \kappa \epsilon_0 A/d$


$$\begin{matrix} A = \frac{1}{4}A_0 \\ d = d_0 \end{matrix} \quad \left. \begin{matrix} \text{---} \\ \text{---} \end{matrix} \right\} \longrightarrow C = \frac{1}{4}(\kappa \epsilon_0 A_0/d_0) \longrightarrow C_2 = \frac{1}{4} \kappa C_0$$

Calculation

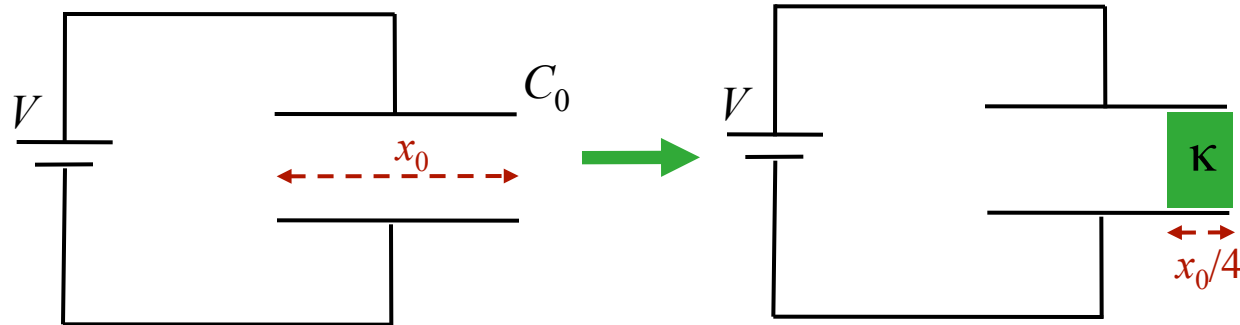

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

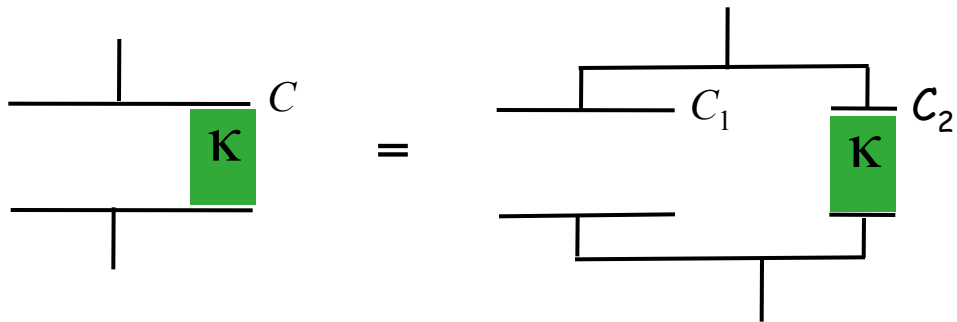A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.



$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$

What is Q_f , the final charge on the capacitor?

What is C ?

A) $C = C_1 + C_2$


B) $C = C_1 + \kappa C_2$

C) $C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$

$C =$ parallel combination of C_1 and C_2 : $C = C_1 + C_2$


$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$

Calculation

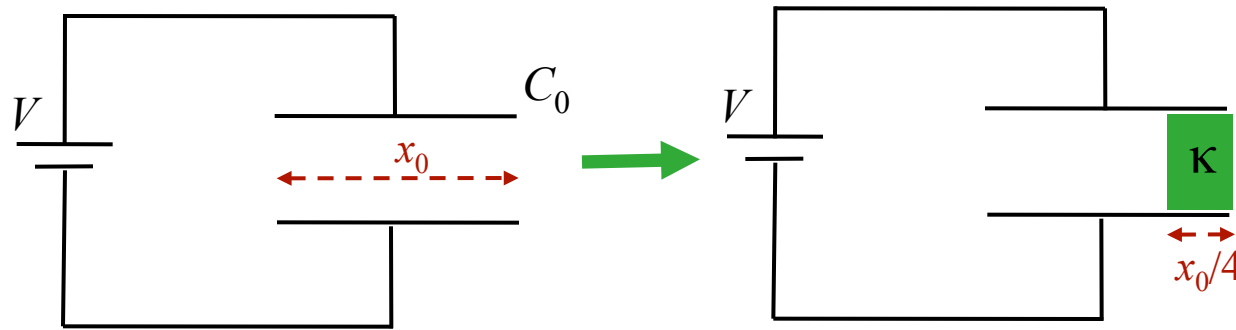

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V .

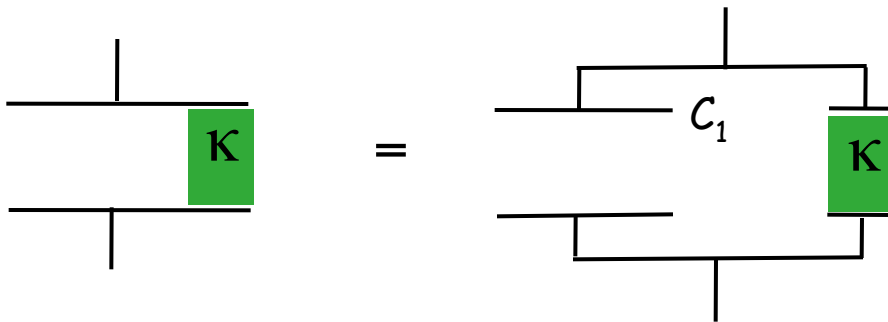A dielectric (κ) of width $x_0/4$ is inserted into the gap as shown.



What is Q_f , the final charge on the capacitor?

$$C_1 = \frac{3}{4}C_0$$

$$C_2 = \frac{1}{4}\kappa C_0$$


$$\rightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$$

What is Q ?

$$C \equiv \frac{Q}{V} \rightarrow Q = VC$$

$$Q = VC_0 \left(\frac{3}{4} + \frac{1}{4}\kappa \right)$$

Different Problem

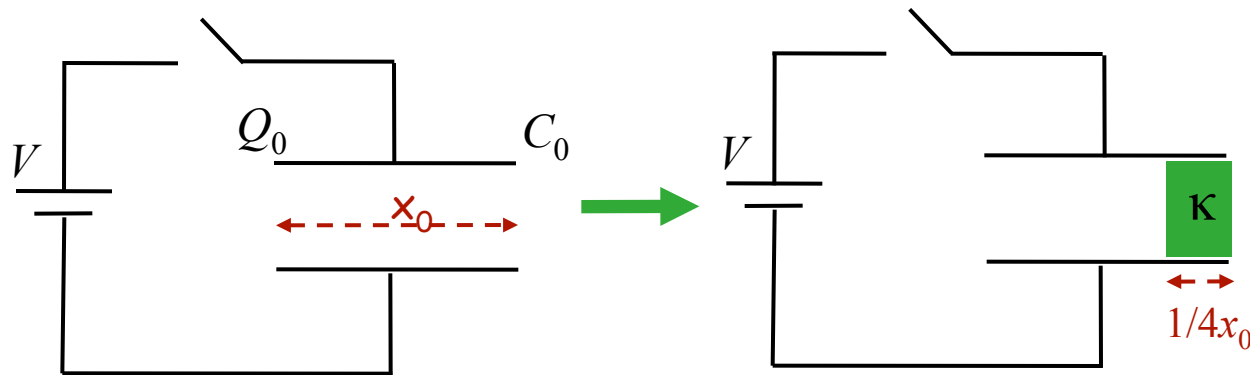

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?

A) $V_f < V$

B) $V_f = V$

C) $V_f > V$

Q stays same: no way to add or subtract


$$\longrightarrow Q = Q_0 = C_0 V$$

We know C : (property of capacitor)

$$\longrightarrow C = C_0 \left(\frac{3}{4} + \frac{1}{4} \kappa \right)$$

$$\longrightarrow V_f = Q/C = V / \left(\frac{3}{4} + \frac{1}{4} \kappa \right)$$

Different Problem

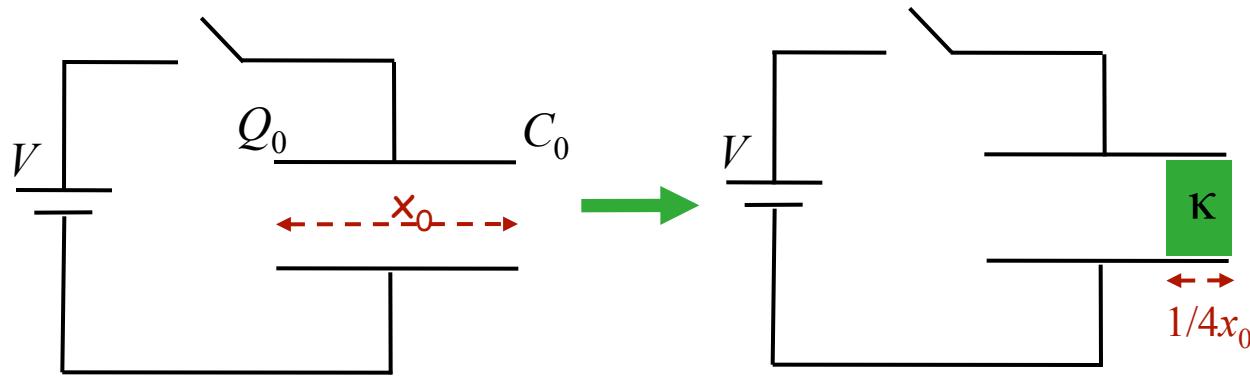

An air-gap capacitor, having capacitance C_0 and width x_0 is connected to a battery of voltage V and then **battery is disconnected**.

A dielectric (κ) of width $1/4x_0$ is inserted into the gap as shown.

What is V_f , the final voltage on the capacitor?

$$V_f = Q/C = V/(3/4 + 1/4 \kappa)$$

How did energy stored in capacitor change when dielectric inserted?

- A) U increased B) U stayed same **C) U decreased**

$$U = \frac{1}{2} Q^2/C$$

Q remained same

C increased



U decreased