
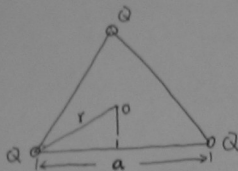


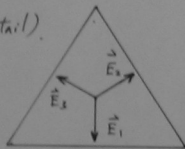1. $a = 0.06 \text{ m}$
 $Q = 2.0 \times 10^{-6} \text{ C}$
 $r = \frac{a}{\sqrt{3}} = 3.464 \times 10^{-2} \text{ m}$



(a) $V = 3 \cdot \frac{kQ}{r}$
 $= \frac{(3)(8.99 \times 10^9)(2.0 \times 10^{-6})}{3.464 \times 10^{-2}}$
 $= 1.56 \times 10^6 \text{ V}$


(b) By symmetry (OR Head-to-tail).
 $\vec{E} = \vec{E}_1 + \vec{E}_2 + \vec{E}_3 = 0$



2. Total charge after combination:

$$Q = Q_1 + Q_2$$

Total capacitance: $C = C_1 + C_2$

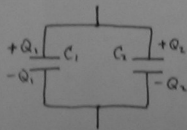

(a) Final Voltage: $V = \frac{Q}{C}$

$$= \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{10.0 \times 10^{-6} + 18.0 \times 10^{-6}}{3.0 \times 10^{-6} + 4.0 \times 10^{-6}}$$

$$= 4.0 \text{ Volts}$$

(b) Now: $C_1' = K C_1 = 25 C_1$

Total capacitance: $C' = C_1' + C_2 = 25 C_1 + C_2$


$$V = \frac{Q_1 + Q_2}{25 C_1 + C_2} = V_2$$

(The voltage across the second capacitor is the same as the total voltage.)


$$= \frac{(10.0 + 18.0) \times 10^{-6}}{(3 \times 25 + 4) \times 10^{-6}}$$

$$= 0.354 \text{ Volts}$$

3. (a)

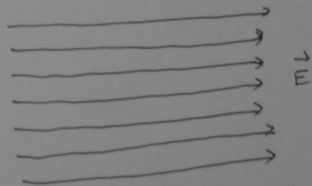

(b)

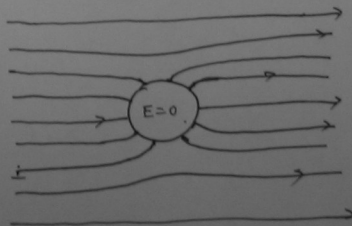

4. Total resistance:

$$R = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Total current:



$$I = \frac{V_0}{R} e^{-\frac{t}{RC}}$$

(a) at $t=0$, $I_0 = \frac{V_0}{R}$ The current through R_1 at $t=0$:

$$I_1 = \frac{V_0}{R_1} = \frac{20.0 \text{ V}}{11.0 \Omega} = 1.82 \text{ A}$$


$$(b) \quad I_0 = \frac{V_0}{R} = \frac{20.0 \text{ V}}{\frac{R_1 R_2}{R_1 + R_2}} = \frac{20.0 (11.0 + 18.5)}{11.0 \times 18.5} = 2.90 \text{ A}$$

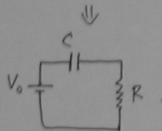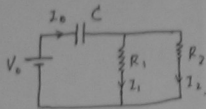(c) $I_1 = 0$ for $t \rightarrow \infty$ { Since the capacitor will be fully charged, the voltage across the capacitor will be the same as the battery. Then, No current can flow.



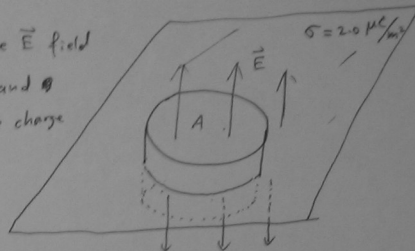5.

By symmetry, the $\vec{E}$ field should be uniform and perpendicular to the charge sheet.



consider a gaussian surface being in a cylindrical shape.

The electric field lines will go through the top and bottom areas. Then, the total flux through the Gaussian surface:

$$\therefore \Phi = \Phi_{\text{top}} + \Phi_{\text{bottom}} + \Phi_{\text{side}}$$

$$= E \cdot A + E \cdot A + 0$$

$$= 2EA$$

$$\text{Charge enclosed: } Q = \sigma A$$

$$\text{Gauss's Law: } \Phi = \frac{Q}{\epsilon_0}$$

$$2EA = \frac{\sigma A}{\epsilon_0}$$

$$\therefore E = \frac{\sigma}{2\epsilon_0} = \frac{2.0 \times 10^{-6}}{2 \times 8.85 \times 10^{-12}} = 1.13 \times 10^{-5} \text{ N/C}$$